
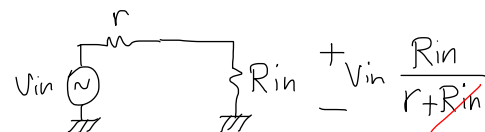
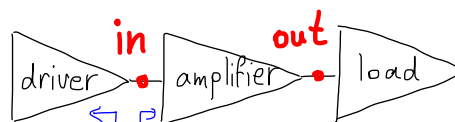


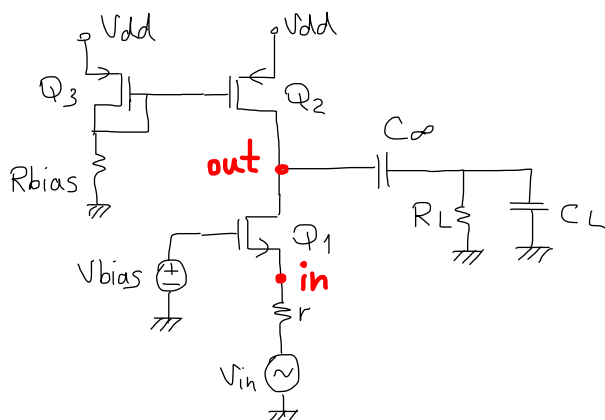
* Input and output resistances of the common gate amplifier :



$$r \gg R_{in} \Rightarrow \frac{R_{in}}{r} \ll 1$$



* AC analysis :

1. discard DC sources
2. short C_∞

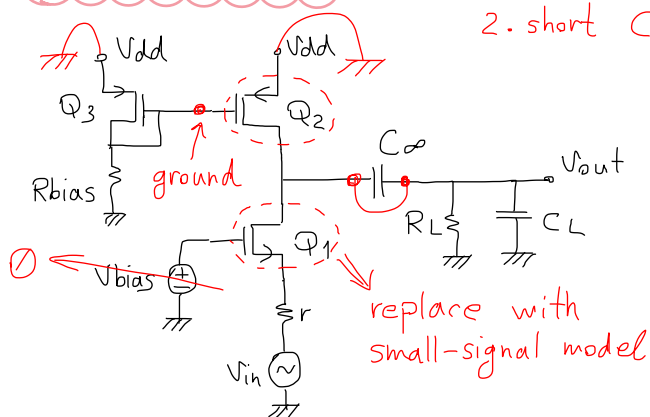

$$V_{gs1} = V_{g1} - V_{s1} = -V_{s1}$$

$$V_{bs1} = V_{b1} - V_{s1} = -V_{s1}$$

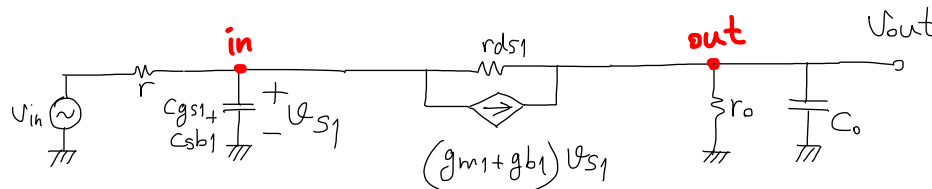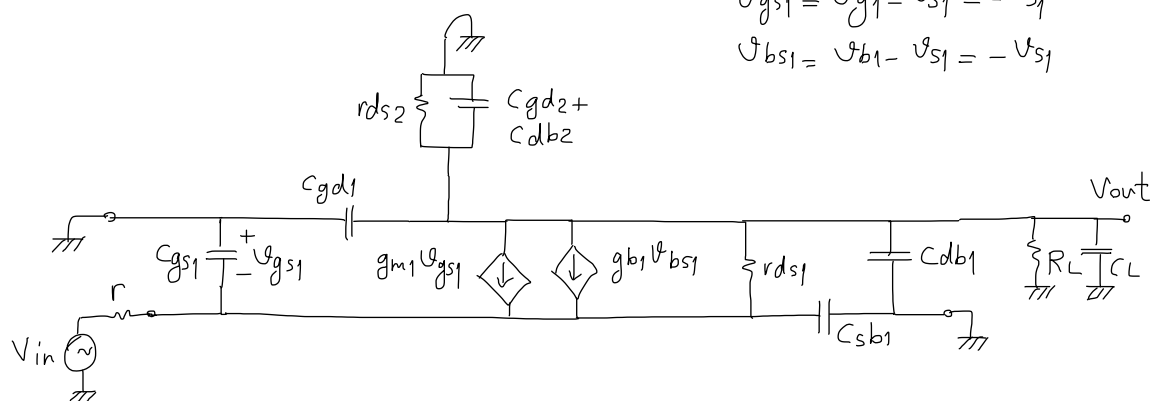


$$r_o = r_{ds2} \parallel R_L$$

$$C_o = C_{db1} + C_L + C_{gd2} + C_{db2} + C_{gd1}$$

$$Z = R \pm jX$$

* find input resistance:

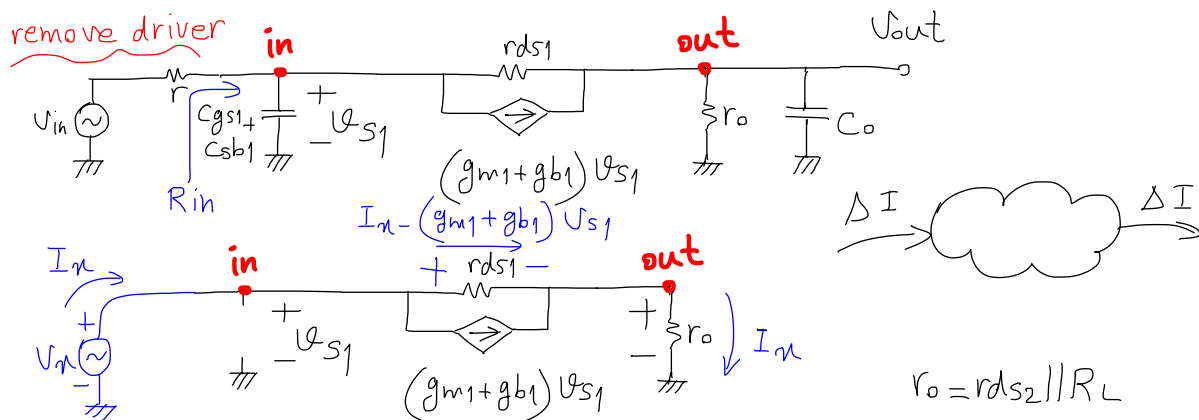1. remove driver stage
2. add a V_n test source ; discard any other independent source
3. find V_n/I_n after opening all caps



$$\begin{cases} V_n = r_{ds1} [I_n - (g_{m1} + g_{b1}) V_{s1}] + r_o I_n \\ V_n = V_{s1} \end{cases} \Rightarrow$$

$$\frac{V_n}{I_n} = \frac{r_o + r_{ds1}}{(g_{m1} + g_{b1}) r_{ds1} + 1}$$


ignore

$$\Rightarrow R_{in} = \frac{(r_{ds2} \parallel R_L) + r_{ds1}}{g_{m1} r_{ds1}} ; \text{ if } r_{ds1} = r_{ds2} = R_L \Rightarrow R_{in} = \frac{3}{2g_{m1}}$$



$$\begin{cases} r_{ds1} = r_{ds2} = 100 \text{ k}\Omega \\ R_L = 1 \text{ k}\Omega \\ g_m = 20 \times 10^{-3} \left[\frac{\text{A}}{\text{V}} \right] \end{cases} \Rightarrow R_{in} = \frac{(100 \text{ k} \parallel 1 \text{ k}) + 100 \text{ k}}{20 \times 10^{-3} \times 100 \text{ k}} \approx \frac{1}{20 \times 10^{-3}} = \frac{1}{g_{m1}}$$

→ * find output resistance R_{out} ?

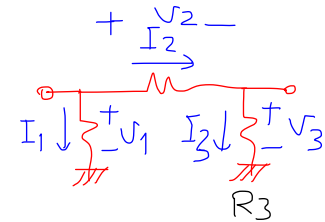
1. connect V_n test source to output
2. discard all other independent sources
3. open all capacitors
4. find $R_{out} = \frac{V_n}{I_n}$


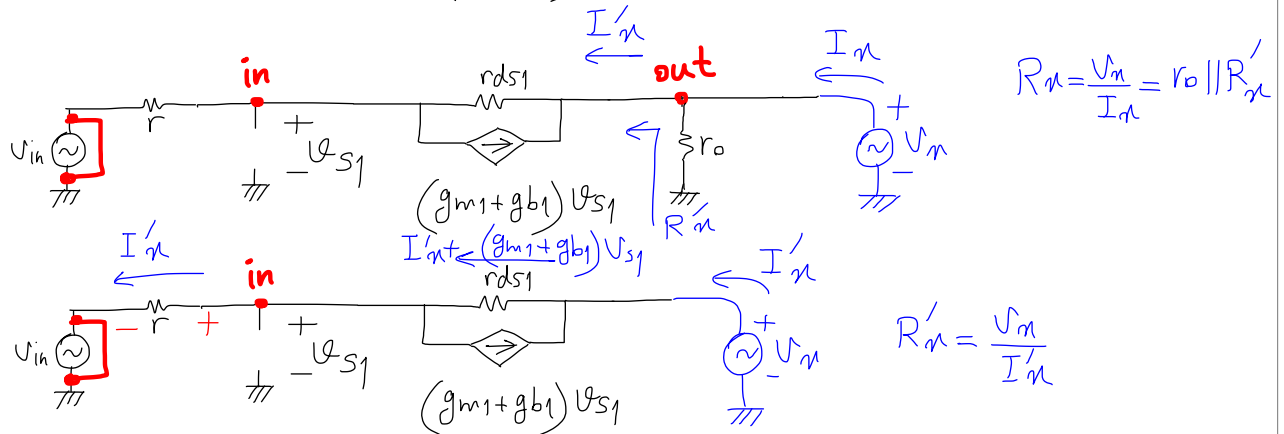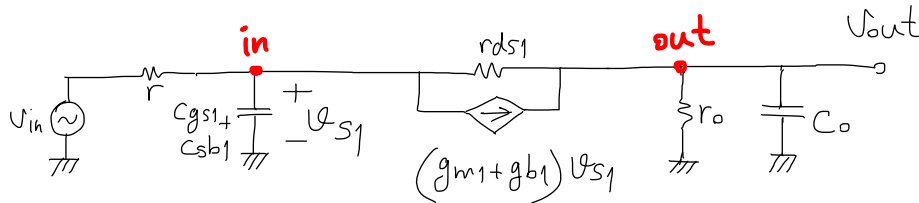
$$\frac{V_3}{I_3} = R_3 \quad \frac{V_3}{I_1} = R_{m31}$$


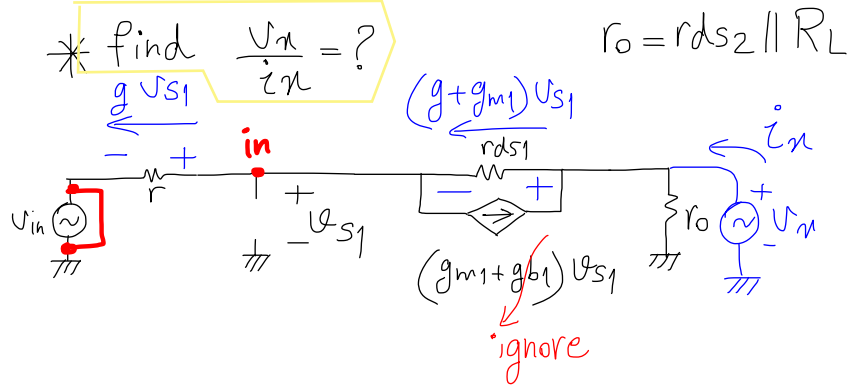
$$\begin{cases} V_{s1} = r I'_n \\ V_n = r_{ds1} \left[I'_n + (g_{m1} + g_{b1}) V_{s1} \right] + r I'_n \end{cases} \Rightarrow \frac{V_n}{I'_n} = r_{ds1} + r + (g_{m1} + g_{b1}) r \cdot r_{ds1}$$



$$\begin{cases} V_n = r_{ds1} [g + g_{m1}] V_{s1} + V_{s1} \\ i_n = g_o V_n + g V_{s1} \end{cases} \Rightarrow V_n = [1 + (g + g_{m1}) r_{ds1}] \left[\frac{i_n - g_o V_n}{g} \right]$$

$$V_n [g + g_o (1 + (g + g_{m1}) r_{ds1})] = i_n [1 + (g + g_{m1}) r_{ds1}] \Rightarrow \frac{V_n}{i_n} = \frac{1 + (g + g_{m1}) r_{ds1}}{g + g_o (1 + (g + g_{m1}) r_{ds1})}$$

Answer: $\frac{V_n}{i_n} = r_o \parallel (r + r_{ds1} + g_{m1} r_{ds1} r)$


$$R_1 \parallel R_2 = \frac{1}{G_1 + G_2}$$


$$\frac{1}{G_1 \parallel G_2} = R_1 + R_2$$

$$G_a = \frac{G_1 G_3}{G_1 + G_2 + G_3}$$



$$G_b = \frac{G_1 G_2}{G_1 + G_2 + G_3}$$

* Delta Δ to Y transformation:

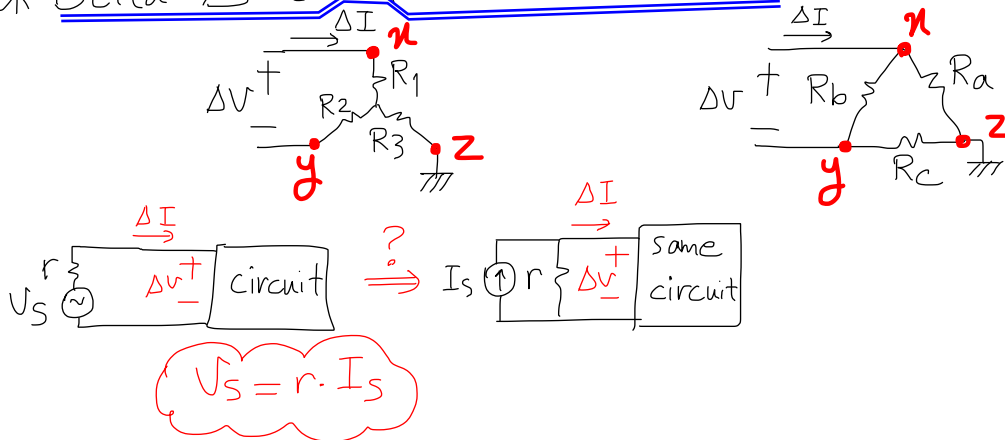

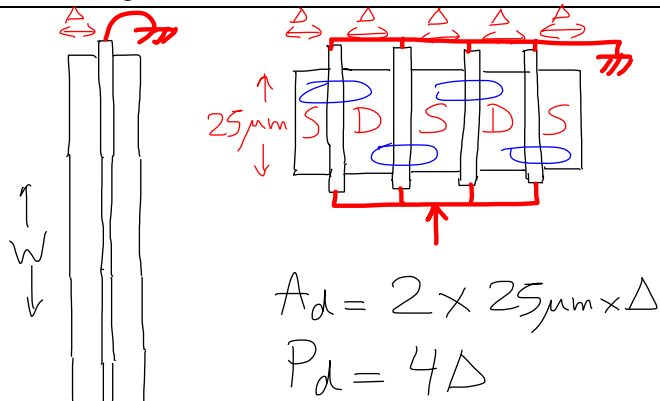

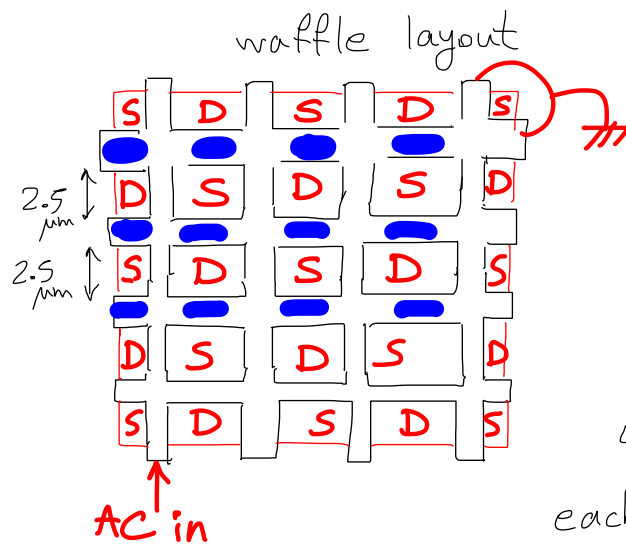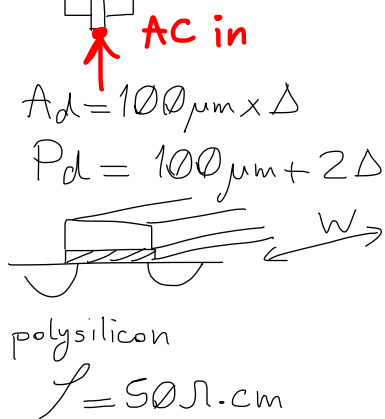$\Delta = 18 \mu\text{m}$
 $\Delta = 500 \text{ nm}$
 $W = 100 \mu\text{m}$



40 transistor
 each transistor
 width = 2.5 μm

