 


Elmore 2

Lecture 17


Advanced Digital IC Design



Khosrow Ghadiri




- nMOSFET

 


Operation Regions	Voltages	Current
Cut Off	$V_{GS} \leq V_{Tn}$	$I_{DS} = 0$
Saturation	$V_{GS} > V_{Tn}$ $V_{DS} > V_{GS} - V_{Tn}$	$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{Tn})^2 (1 + \lambda V_{DS})$
Resistive	$V_{GS} > V_{Tn}$ $V_{DS} < V_{GS} - V_{Tn}$	$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right]$



- pMOSFET

 

Operation Regions	Voltages	Current
Cut Off	$V_{SG} \leq V_{Tp} $	$I_{SD} = 0$
Saturation	$V_{SG} > V_{Tp} $ $V_{SD} > V_{SG} - V_{Tp} $	$I_{SD} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - V_{Tp})^2 (1 + \lambda V_{SD})$
Resistive	$V_{SG} > V_{Tp} $ $V_{SD} < V_{SG} - V_{Tp} $	$I_{SD} = \mu_p C_{ox} \frac{W}{L} \left[(V_{SG} - V_{Tp}) V_{SD} - \frac{V_{SD}^2}{2} \right]$

 


- Enhancement mode MOSFET transistor region of operation

	Cut-off	Resistive	Saturation
nMOS	$V_{GSn} < V_{Tn}$ $V_{IN} < V_{Tn}$	$V_{GSn} > V_{Tn}$ $V_{IN} > V_{Tn}$ $V_{DSn} < V_{GSn} - V_{Tn}$ $V_{OUT} < V_{IN} - V_{Tn}$	$V_{GSn} > V_{Tn}$ $V_{IN} > V_{Tn}$ $V_{DSn} > V_{GSn} - V_{Tn}$ $V_{OUT} > V_{IN} - V_{Tn}$
pMOS	$V_{GSp} > V_{Tp}$ $V_{IN} > V_{Tp} + V_{DD}$	$V_{GSp} < V_{Tp}$ $V_{IN} < V_{Tp} + V_{DD}$ $V_{DSp} > V_{GSp} - V_{Tp}$ $V_{OUT} > V_{IN} - V_{Tp}$	$V_{GSp} = V_{Tp}$ $V_{IN} < V_{Tp} + V_{DD}$ $V_{DSp} < V_{GSp} - V_{Tp}$ $V_{OUT} < V_{IN} - V_{Tp}$



 - Intrinsic capacitors in the cut-off $V_{GS} < V_{TN}$




- Channel is not inverted

$$C_{gate} = C_{gate-body} = C_0 = C_{ox} WL = \frac{\epsilon_{ox}}{t_{ox}} WL$$



 - Intrinsic capacitors in the non-saturation $V_{GS} > V_{TN}$ & $V_{DS} < V_{GS} - V_{TN}$




$$C_{gate} = C_{gate-body} + C_{gate-source} + C_{gate-drain}$$

$$C_{gate} = 0 + \frac{C_0}{2} + \frac{C_0}{2} = C_0$$




 - Intrinsic capacitors in the saturation $V_{GS} > V_{TN}$ & $V_{DS} > V_{GS} - V_{TN}$



$$C_{gate} = C_{gate-body} + C_{gate-source} + C_{gate-drain}$$
 
$$C_{gate} = 0 + \frac{2C_0}{3} + 0 = \frac{2C_0}{3}$$




- Intrinsic MOS gate capacitor

Operation	Cut-off	Saturation	Resistive
C_{gs}	0	$\frac{2}{3}C_{ox}WL_{eff}$	$\frac{1}{2}C_{ox}WL_{eff}$
C_{gd}	0	0	$\frac{1}{2}C_{ox}WL_{eff}$
C_{gb}	$C_{ox}WL_{eff}$	0	0
C_g	$C_{ox}WL_{eff}$	$\frac{2}{3}C_{ox}WL_{eff}$	$C_{ox}WL_{eff}$




- Detailed gate capacitors

Operation	Cut-off	Saturation	Resistive
C_{gs}	$C_{OX}WL_D$	$\frac{2}{3}C_{OX}WL_{eff} + C_{OX}WL_D$	$\frac{1}{2}C_{OX}WL_{eff} + C_{OX}WL_D$
C_{gd}	$C_{OX}WL_D$	$C_{OX}WL_D$	$\frac{1}{2}C_{OX}WL_{eff} + C_{OX}WL_D$
C_{gb}	$C_{OX}WL_{eff}$	0	0

 


- Find the Elmore delay

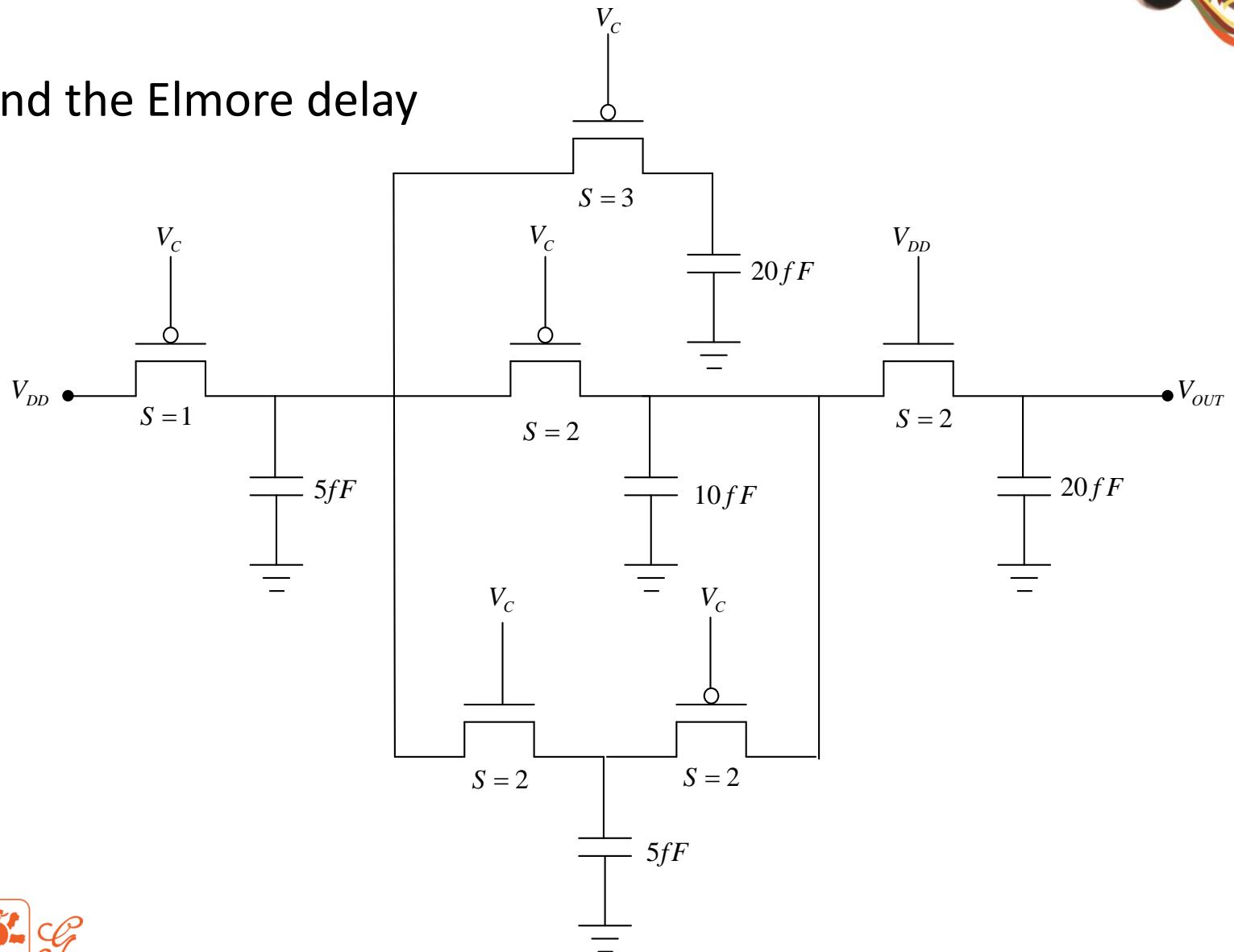




 - Find the Elmore delay after T_1 , given:
- Minimum size: $s = 1, W = W_{\min}$
- Size: $s = 2, W = 2W_{\min}$
- Resistances: $R_{eqnMOS} = 10k\Omega, R_{eqpMOS} = 20k\Omega$
- Capacitances: $C_{gs} = C_{gd} = 0.5fF$
 $C_{db} = C_{sb} = 1fF$
- Ignore overlap capacitance and feedthrough.
- Except $V_{in} = V_{DD}$, initially all nodes are at zero.





- Equivalent RC circuit.

 



- R and C equivalent

$$R_1 = R_{eqMOS} = 20k\Omega$$


$$C_1 = 5fF + 6C_{gs} + 8C_{db} = 5fF + 6(0.5) + 8(1) = 16fF$$

$$R_2 = \frac{R_{eqMOS}}{3} = 6.7k\Omega$$

$$C_2 = 20fF + 3C_{gs} + 3C_{db} = 20fF + 3(0.5) + 3(1) = 24.5fF$$

$$R_3 = \frac{R_{eqMOS}}{2} = 10k\Omega$$
 
$$C_3 = 10fF + 4C_{gs} + 4C_{db} = 10fF + 4(0.5) + 4(1) = 16fF$$



- R and C equivalent


$$R_4 = \frac{R_{eqnMOS}}{2} = 5k\Omega$$

$$C_4 = 10fF + 4C_{gs} + 4C_{db} = 20fF + 4(0.5) + 4(1) = 26fF$$


$$R_5 = \frac{R_{eqpMOS}}{2} = 10k\Omega$$


$$C_5 = 5fF + 2C_{gs} + 4C_{db} = 5fF + 4(0.5) + 4(1) = 10fF$$

$$R_6 = \infty$$

 

- Tree-structured RC network

 

 

- The Elmore delay

$$\tau_{out} = R_1 C_1 + R_1 C_2 + (R_1 + R_3) C_3 + (R_1 + R_3) C_5 \\ + (R_1 + R_3 + R_4) C_5$$

$$t_{PHL} = 0.69 \tau_{V_{OUT}}$$