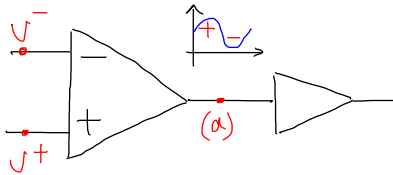


* Advantage of using differential signals:

Single ended Signal


(probe with respect to ground)



$$\begin{cases} V_{in} = V^+ - \bar{V}^- \\ V_{out} = V_a \end{cases}$$


* Assume opamp output has distortion
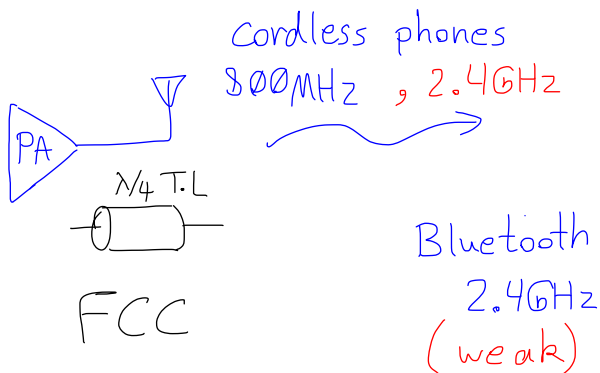
$$V(a) = k_1 V_{in} + k_2 V_{in}^2 + k_3 V_{in}^3 + \dots + \text{Noise}$$



Differential ended Signal

(probe with respect to other node)

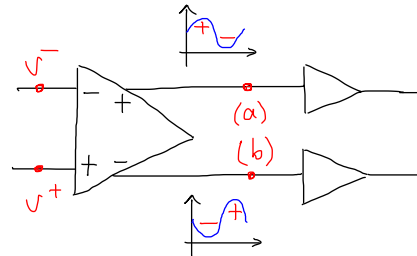

$$\begin{cases} V_{in} = V^+ - \bar{V}^- \\ V_{out} = V_b - V_a \end{cases}$$

* Assume opamp output has distortion

$$\begin{cases} V(a) = k_1 V^- + k_2 (V^-)^2 + k_3 (V^-)^3 + \dots + \text{Noise} \\ V(b) = k_1 V^+ + k_2 (V^+)^2 + k_3 (V^+)^3 + \dots + \text{Noise} \end{cases}$$

$$V^- = -V^+$$

① $V_{out} = V_b - V_a$ has twice amplitude



$$V_b - V_a = k_1 (V^+ - V^-) + \dots + k_3 (V^{+3} - V^{-3}) + \dots$$

② common Noise term gets cancelled

③ even harmonic distortions are cancelled

④ But circuit size and power dissipation might get doubled

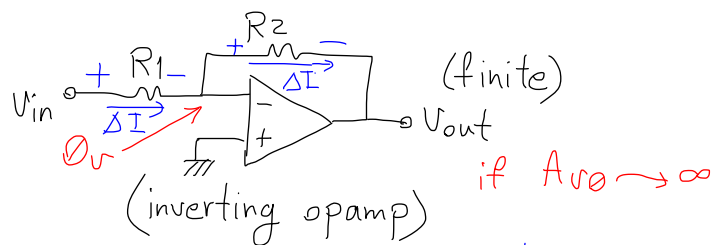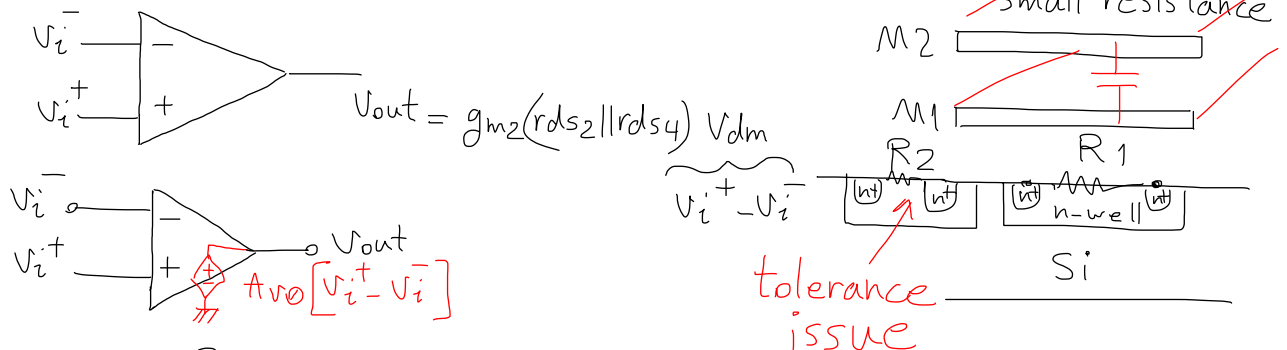
* Closed-loop versus Open-loop configuration :




$$\frac{f_{finite}}{\infty} = 0 \implies \frac{V_{out}}{A_v} = 0$$

$$V_i^+ - V_i^- = 0$$


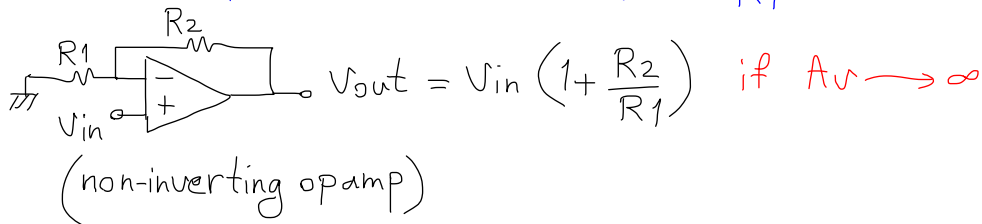
$$\Delta I = \frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_2} \implies \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$



* Complete Opamp Modeling:

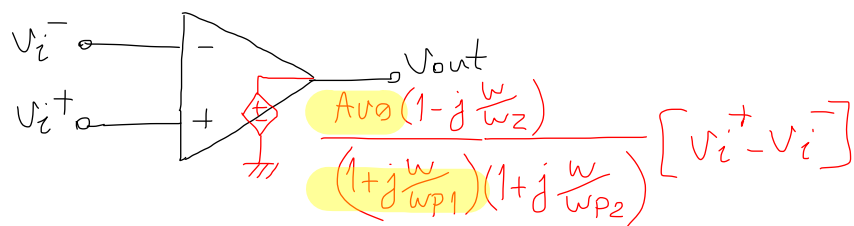

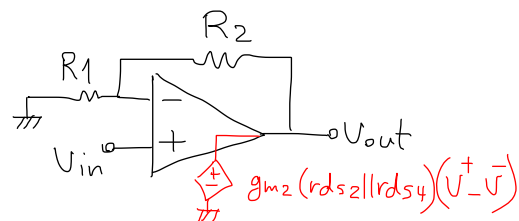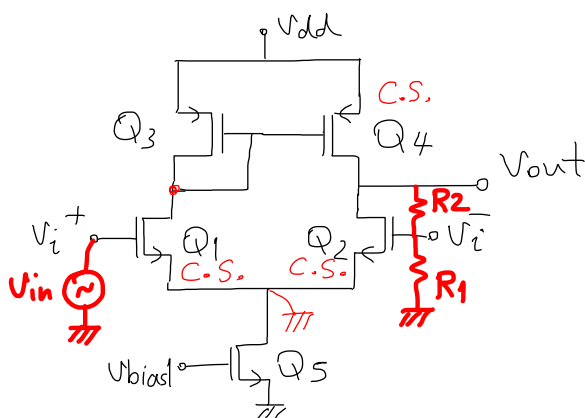* Closed-loop gain of +3 \rightarrow non-inverting architecture




$$\begin{cases} R_2 = 20k\Omega \\ R_1 = 10k\Omega \end{cases}$$


$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1} = 3$$

* Why use closed-loop amplifiers (instead of open-loop) in Electronic systems?

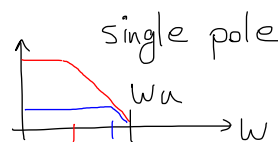
\rightarrow Because R_1 and R_2 can be used off-chip and trimmed to minimize the effect of process variation



* opamp model

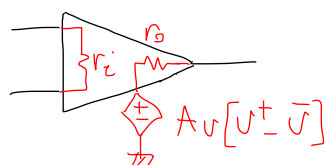

\Rightarrow

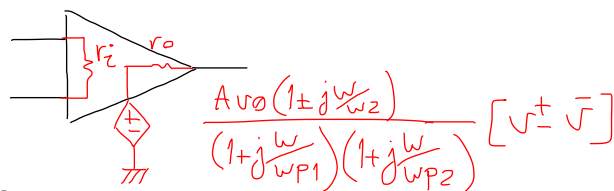

example: $r_i = 100k\Omega$, $r_o = 5\Omega$, $A_v = 1000$

$$\text{ideal} \begin{cases} r_i \rightarrow \infty \\ r_o \approx 0 \\ A_v \rightarrow \infty \end{cases}$$