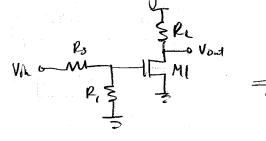
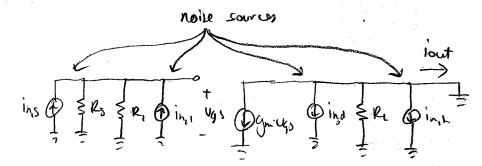


Draw Small signed model (reject all capacitmes)





three are 4 seperate roise sources, calculate jout dre to each (while reglecting the others)

1) Noise due to source resistor (only in,s noise source is active, others are open-circuited)

$$V_{qs} = i_{n,s} \cdot \frac{R}{2}$$

i lout =-gni Ugs =
$$-gni l_{AS} \cdot \underline{R}$$

 \rightarrow We want power: $i_{out}^2 = g_n^2 \cdot \frac{R^2}{4} \cdot i_{ns}^2$

$$ind^2 = g^2 R^2 \cdot 4 + \frac{1}{R} = \left[\frac{g^2 R \cdot 4 + 1}{4} \right]$$

noise at O/P are to R_s

@ Now repeat for noise are to R. (in,i)

- from Aspection, this will experience the same gook to the es ins did.

$$\int_{1004}^{100} dt^2 = g_m^2 \cdot R \cdot 4kTDF$$

troile at OIP we to R,

3 Now consider noise due to drain Hernal noise (in,d) - from impaction, jout = ind 2. lout = inid + S.b A expression for in, d: ind = 4kT8.gas. Of int' = HET 8. gdo Df Twise at O/P he to draw thermal noise of MI. @ Firally, consider noise from Re (in, e) - also appears directly at O/P - 16ut = 1n,2 -P Sus in in = 4ETOF 16ut2 = 4ETDA COLP roise du to resister RL. - Now, to find noise factor: F = total noise at 01P noise at 01P he to Rs = [gm2. R.44TDF + gm2. R.44TDF + 4kTO go.DF + 4KTOF]
4

PL gne R. 4ETOF = 2 + 4.8 gdo + 4 gn2 R gn2. R.R. Lost ferm due to load was not helided in class. $F = 2 + \frac{48}{\text{x.R.gm}} + \frac{4}{\text{gn}^2 \text{R.R.}}$