

## Department of Electrical Engineering and Computer Sciences

EECS 141

Figure 2: Schematic for the simulation

## 2. Transient response of the inverter

 


Figure 3: Complete transient response of the inverter

 


Figure 4: Inverter delay for the rising signal edge at input

Delay for the rising edge at input: 32.23 ps

 


Figure 5: Inverter delay for the falling signal edge at input

Delay for the falling edge at input: 39.47 ps

### 3. Voltage-Transfer Characteristic

 


Figure 6: Voltage-transfer characteristic of the inverter