

EE 538B CMOS RF IC DESIGN

Midterm Examination No. 2: May 24, 2004

Time Allowed: 110 Minutes


Student Name: Solution

UW Student ID #: 1234567

You are allowed two sheets of notes. Write legibly. Show all work. State assumptions.

Problem #	Points Possible	Points
1	15	
2	15	
3	30	
4	25	
5	15	

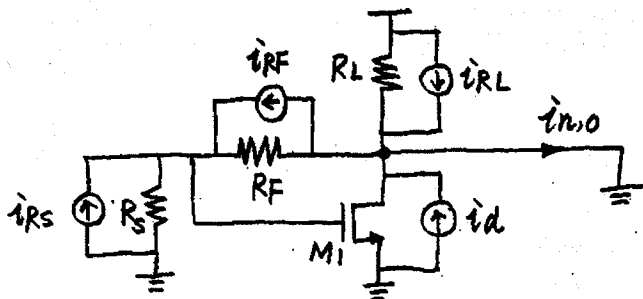1. (15 points) Determine the noise factor of the circuit shown with respect to the source resistance R_S . Neglect channel length modulation effects, all parasitic capacitors and induced gate noise of the MOSFETs. Assume that all the MOSFETs operate in the saturation region.



There are four noise sources:

$$\overline{i_{RS}^2} = \frac{4kT}{R_S} \Delta f, \quad \overline{i_{RF}^2} = \frac{4kT}{R_F} \Delta f, \quad \overline{i_{RL}^2} = \frac{4kT}{R_L} \Delta f, \quad \overline{i_d^2} = 4kT\gamma g_{do} \Delta f$$

$$\overline{i_{n,RS}^2} = \overline{i_{RS}^2} \cdot \left(\frac{R_F R_S}{R_F + R_S} \right)^2 \cdot \left(\frac{1}{R_F} - g_m \right)^2$$

$$\begin{aligned} \overline{i_{n,RF}^2}: \quad v_x &= i_{RF} \cdot \left(\frac{R_F R_S}{R_F + R_S} \right) \\ i_x &= i_{RF} \cdot \left(\frac{R_S}{R_S + R_F} \right) \end{aligned}$$

$$\begin{aligned} i_{n,RF} &= i_x - i_{RF} - g_m v_x \\ &= i_{RF} \cdot \frac{R_S}{R_S + R_F} - i_{RF} - g_m i_{RF} \cdot \frac{R_F R_S}{R_F + R_S} \\ &= -i_{RF} \cdot \frac{R_F}{R_F + R_S} \cdot (1 + g_m R_S) \end{aligned}$$

$$\overline{i_{n,RF}^2} = \overline{i_{RF}^2} \cdot \left(\frac{R_F}{R_F + R_S} \right)^2 (1 + g_m R_S)^2$$



$$\overline{i_{n,RL}^2} = \frac{4kT}{R_L} \Delta f$$

$$\overline{i_{n,d}^2} = 4kT\gamma g_{do} \Delta f$$

$$F = 1 + \frac{\overline{i_{n,RF}^2} + \overline{i_{n,RL}^2} + \overline{i_{n,d}^2}}{\overline{i_{n,RS}^2}}$$

$$\begin{aligned} &= 1 + \frac{\frac{4kT}{R_F} \Delta f \left(\frac{R_F}{R_F + R_S} \right)^2 (1 + g_m R_S)^2 + \frac{4kT}{R_L} \Delta f + 4kT\gamma g_{do} \Delta f}{\frac{4kT}{R_S} \Delta f \cdot \left(\frac{R_F R_S}{R_F + R_S} \right)^2 \cdot \left(g_m - \frac{1}{R_F} \right)^2} \end{aligned}$$

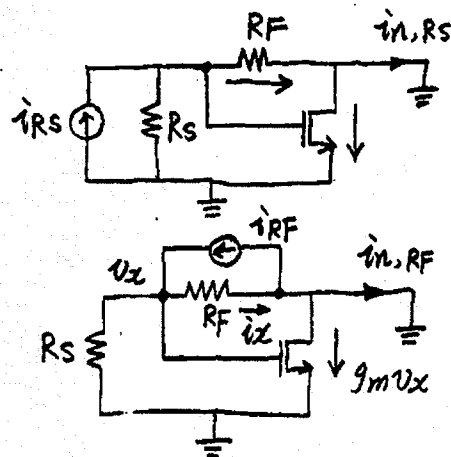
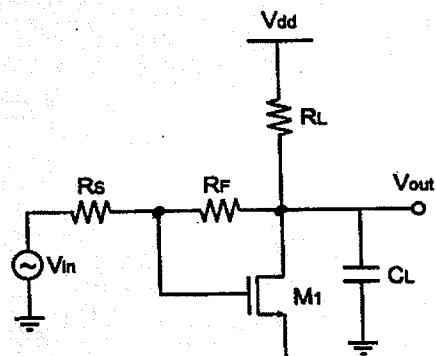
$$\Rightarrow F = 1 + \frac{R_F}{R_S} \cdot \frac{(1 + g_m R_S)^2}{(1 - g_m R_F)^2} + \frac{1}{R_S} \left(\frac{1}{R_L} + \gamma g_{do} \right) \cdot \frac{(R_F + R_S)^2}{(1 - g_m R_F)^2}$$




2. (15 points) A double balanced passive mixer is shown below. The IF port is terminated by a resistance $R_L = R_S$. What is the conversion gain? Assume the LO is driven by square wave the switching is infinitely fast. The RF signal is sinusoidal with peak value A and the LO square wave has peak value B .

LO port is driven by ideal square wave.

i) If $L_O(t) > \overline{L_O}(t)$:

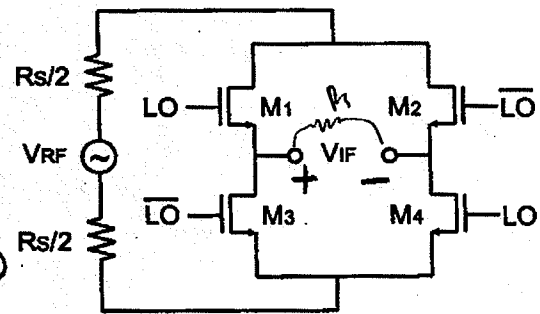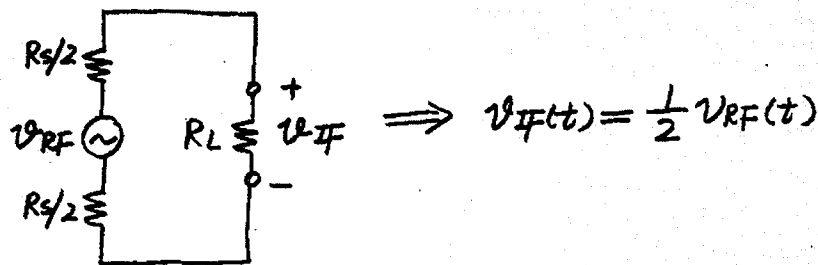

ii) If $L_O(t) < \overline{L_O}(t)$:

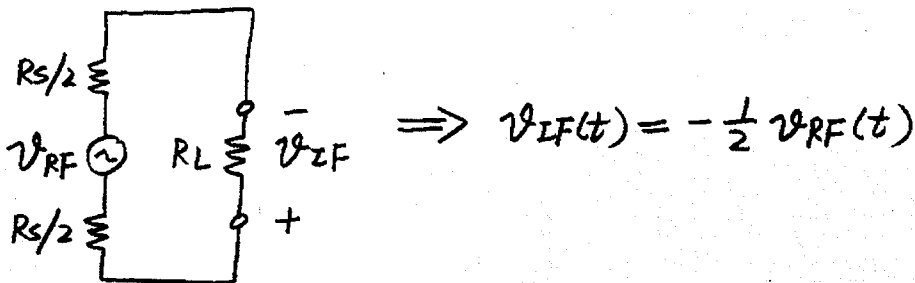

Therefore,
$$V_{IF}(t) = \frac{1}{2} V_{RF}(t) \cdot \frac{4B}{\pi} \left[\cos \omega_{LO} t + \frac{1}{3} \cos 3\omega_{LO} t + \frac{1}{5} \cos 5\omega_{LO} t + \dots \right]$$

$$= \frac{1}{2} A \cos \omega_{RF} t \cdot \frac{4B}{\pi} \left[\cos \omega_{LO} t + \frac{1}{3} \cos 3\omega_{LO} t + \frac{1}{5} \cos 5\omega_{LO} t + \dots \right]$$

Desired IF output term is $\frac{1}{2} \cdot A \cdot \frac{4B}{\pi} \cdot \frac{1}{2} \cos(\omega_{RF} - \omega_{LO})t$

\Rightarrow Conversion Gain $G_c = \frac{\frac{1}{2} \cdot A \cdot \frac{4B}{\pi} \cdot \frac{1}{2}}{A}$

$\therefore G_c = \frac{B}{\pi}$

3. (30 points) (a) A Hartley receiver is shown below. The RF signal power (@ node A) is -103dBm. The power of image interferer (also @ node A) is as high as -51dBm. The gain from node A to node B is 50dB. After down-conversion, the acceptable interference from image frequency can be 12dB higher than the desired signal. Determine the required image reject ratio (IRR).

$$P_{RF}|_A = -103 \text{ dBm}$$

$$P_{IM}|_A = -51 \text{ dBm}$$


Without image rejection:

$$P_{RF}|_B = -103 + 50 = -53 \text{ dBm}$$

$$P_{IM}|_B = -51 + 50 = -1 \text{ dBm}$$


$$P_{IM}|_B, \text{ acceptable} = -53 + 12 = -41 \text{ dBm}$$
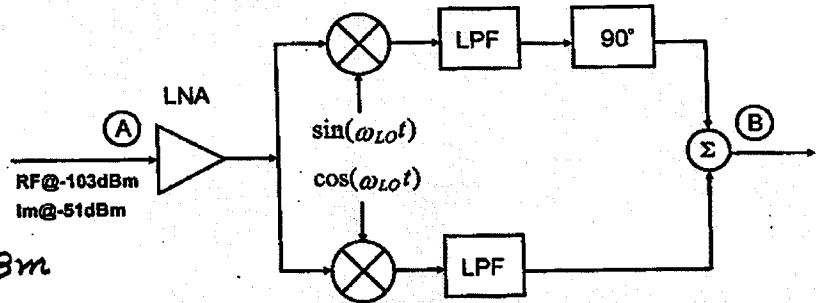
$$\therefore \text{The required IRR} = -1 - (-41) = 40 \text{ dB}$$





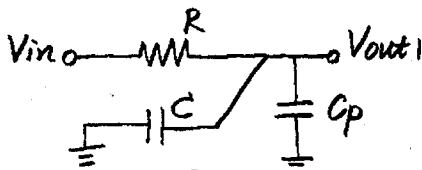(b) Suppose the phase shift of 90° is realized by the one stage polyphase filter, as shown below. That is, -45° is realized in one branch and $+45^\circ$ is realized in the other branch. The parasitic capacitance at the output node is $C_p = 0.1 \text{ pF}$, $R = 1 \text{ K}\Omega$, $C = 1 \text{ pF}$. What is the IRR of the Hartley receiver? Assume that IRR degradation is only caused by the existence of C_p .

Considering C_p , the transfer function can be calculated as


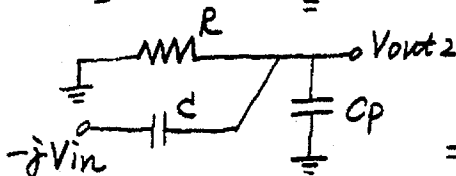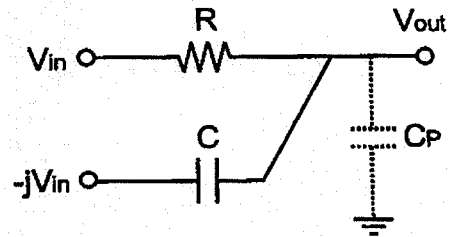
$$\frac{V_{out1}}{V_{in}} = \frac{1}{1 + j\omega R(C + C_p)}$$



$$\frac{V_{out2}}{(-jV_{in})} = \frac{Rj\omega C}{1 + j\omega R(C + C_p)}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1 + \omega RC}{1 + j\omega R(C + C_p)}$$

Therefore, C_p affects the phase of transfer function, not the amplitude.

At $\omega_0 = -\frac{1}{RC}$, $|H(j\omega_0)| = 0$. So image signal is suppressed.

$\Rightarrow \text{IRR} = \infty \text{ dB}$. phase errors cause IRR degradation too!

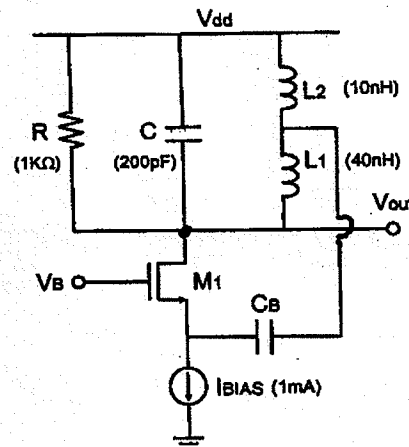4. (25 points) For the Hartley oscillator shown below, calculate (a) frequency of oscillation, (b) peak output amplitude, (c) loaded and unloaded Q_s of the tank, and (d) minimum transconductance required for startup (assume a safety margin of 3X to ensure start-up).



(a) $L_{eq} = L_1 + L_2 = 50 \text{ nH}$

$$\omega_0 = \frac{1}{\sqrt{L_{eq} \cdot C}} = \frac{1}{\sqrt{50 \times 10^{-9} \times 200 \times 10^{-12}}} \\ = 3.16 \times 10^8 \text{ rad/s}$$

$$f_0 = \frac{\omega_0}{2\pi} = 50.3 \text{ MHz}$$

(b) $V_{\text{tank}} \approx 2 I_{\text{BIAS}} R (1 - n)$

$$n = \frac{L_2}{L_1 + L_2} = \frac{10}{10 + 40} = 0.2$$

$$V_{\text{tank}} \approx 2 \times 10^{-3} \times 10^3 \times (1 - 0.2)$$

$$\therefore V_{\text{tank}} \approx 1.6 \text{ V}$$

(c) $G_m = \frac{2 I_{\text{BIAS}}}{V_1}$, $V_1 = n \cdot V_{\text{tank}} = 0.2 \times 1.6 = 0.32 \text{ V}$

$$G_m = \frac{2 \times 10^{-3}}{0.32} = 6.25 \text{ mS}$$

$$R_{eq} = R \parallel \frac{1}{n^2 G_m} = 800 \Omega$$



$$Q_{\text{unloaded}} = \omega_0 R C = 63.25$$

$$Q_{\text{loaded}} = \omega_0 R_{eq} C = 50.60$$

(d) $g_m \geq \frac{1}{R(n - n^2)} = \frac{1}{10^3 \times (0.2 - 0.2^2)} = 6.25 \text{ mS}$

$$g_{m, \text{min}} = 3 \times 6.25 = 18.75 \text{ mS}$$

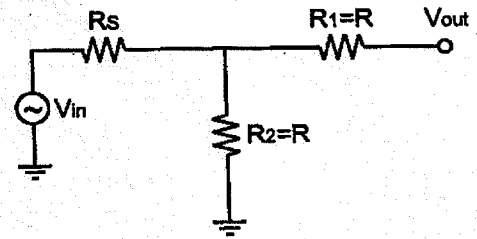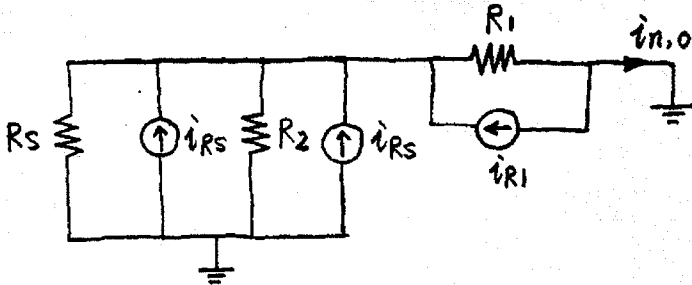5. (15 points) A resistive network is shown below:



(a) What is the noise factor of the above circuit with respect to source resistance R_s ?

There are three noise sources:

$$\overline{i_{R_s}^2} = \frac{4kT}{R_s} \Delta f, \quad \overline{i_{R_1}^2} = \frac{4kT}{R_1} \Delta f, \quad \overline{i_{R_2}^2} = \frac{4kT}{R_2} \Delta f$$

$$\overline{i_{n,R_s}^2} = \overline{i_{R_s}^2} \cdot \left(\frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_s}} \right)^2 = \frac{4kT}{R_s} \Delta f \cdot \frac{R_s^2}{(2R_s + R)^2}$$

$$\overline{i_{n,R_2}^2} = \overline{i_{R_2}^2} \cdot \left(\frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_s}} \right)^2 = \frac{4kT}{R} \Delta f \cdot \frac{R_s^2}{(2R_s + R)^2}$$

$$\overline{i_{n,R_1}^2} = \overline{i_{R_1}^2} \cdot \left(1 - \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_s}} \right)^2 = \frac{4kT}{R} \Delta f \cdot \left(\frac{R_s + R}{2R_s + R} \right)^2$$

$$\therefore F = 1 + \frac{\overline{i_{n,R_1}^2} + \overline{i_{n,R_2}^2}}{\overline{i_{n,R_s}^2}} = 1 + \frac{R_s}{R} + \frac{R_s}{R} \cdot \left(\frac{R_s + R}{R_s} \right)^2$$

$$\Rightarrow \boxed{F = 3 + 2 \cdot \frac{R_s}{R} + \frac{R}{R_s}}$$

(b) What value of R minimizes the noise factor F ?

$$\frac{\partial F}{\partial R} = -2 \frac{R_s}{R^2} + \frac{1}{R_s} = 0$$

$$\Rightarrow \boxed{R_{opt} = \sqrt{2} R_s}$$