



University of California
College of Engineering
Department of Electrical Engineering
and Computer Sciences

J. Rabaey

WeFr 2-3:30pm

Fr, February 19, 6:30-8:00pm

EECS 141: SPRING 10—MIDTERM 1

NAME	Last	First
-------------	------	-------

SID	
------------	--

Problem 1 (15):

Problem 2 (12):

Problem 3 (15):

Total (42)	
-------------------	--

[PROBLEM 1] CMOS NON-INVERTING BUFFER (15 pts)

The following circuit can be seemed as a “DIGITAL NON-INVERTING BUFFER”.

 


Fig.1 (a) DIGITAL BUFFER & VTC

(a) (3pts) Compute V_{IL} , V_{IH} , V_{OL} , V_{OH} , NM_L , and NM_H .

(i) V_{IL}	=
(ii) V_{IH}	=
(iii) V_{OL}	=
(iv) V_{OH}	=
(v) NM_L	=
(vi) NM_H	=

 


Fig.1 (b) One-stage DIGITAL BUFFER with 100fF C_L

(b) (6pts) For Fig.1.(b), the output voltage, V_{OUT} , is initially discharged, $V_{OUT}=0$. You may ignore the intrinsic capacitance, or diffusion capacitance, of the buffer.

Find the energy dissipated in the buffer during the first 0 to 1.2V step input (i), **First E_{DISS}** .

Then, after the output reaches its final value, a 1.2V to 0 step is applied to the input (ii). Find the energy dissipated in the buffer, **Second E_{DISS}** .

A second 0 to 1.2V step follows (iii). Find again the energy dissipated in the buffer (**Third E_{DISS}**).

(i) 1st $E_{DISS} =$

(ii) 2nd $E_{DISS} =$

(iii) 3rd $E_{DISS} =$


 


Fig.1 (c)

- (c) (4 pts) One engineer tried to develop a transistor-level implementation of the buffer as shown in Fig.1(c). Draw the VTC of the circuit where V_{IN} goes from 0V to 1.2V and then goes back to 0V. Here, the $V_{TN}=|V_{TP}|=0.2V$, $R_{OFF}=\text{inf.}$, and no body effect, that is the threshold voltage is not dependent upon the voltage of the body.

 

(d) (2pts) Can the gate of Fig 1.c still be considered a digital gate (or, is it still regenerative)? Explain in a couple of words why or why not.

[PROBLEM 2] RING OSCILLATOR (12pts)

Consider the 5-stage ring oscillator shown in Fig.2a, which is used to generate a clock signal. The input gate capacitance of a minimum-sized inverter (size=1) is $C_{IN}=10\text{fF}$, while $R_{ON,N}=R_{ON,P}=7.22\text{k}\Omega$, and $R_{OFF}=\text{inf}$. Assume that the input capacitance is proportional to its size, and R_{ON} is inversely proportional to its size. The diffusion capacitance, or intrinsic capacitance, of inverter is the same as the gate capacitance, $\gamma=1$. Ignore resistance and capacitance of the wires between the inverters.


 


Fig.2 (a) 5-stage Ring Oscillator

 - (a) (6pts) Determine the oscillation frequency of this circuit at V_{OUT} for $R=1$ (that is, using unit inverters). Determine also the power dissipation of the circuit P_{SUPPLY} for $V_{DD} = 1.2\text{V}$. You should take into account the gate and diffusion capacitances.



$f =$
 $P_{SUPPLY} =$

- (b) (6pt) Determine the oscillation frequency of ring oscillator and as well as the power dissipation, when the inverters are sized at $R=2$, $R=4$, and $R=8$, respectively. Please normalize your results with respect to $f_{R=1}$ and $P_{\text{SUPPLY},R=1}$.

R	$f_R / f_{R=1}$	$P_{\text{SUPPLY},R} / P_{\text{SUPPLY},R=1}$
2		
4		
8		

[PROBLEM 3] COMPLEX LOGIC AND LOGICAL EFFORT (15 pts)

(a) (2pts) Implement the logic function $F = \overline{A \cdot B + C}$ by using a complex static CMOS Gate. Place the PMOS and NMOS driven by input A closest to the output node, F, in your transistor stacks.

 


Fig.3 (a) Complex Gate

(b) (3pts) The unit inverter is shown in Fig. 3(b). Assume that $C_D = C_G = 2\text{fF}/\mu\text{m}$. Size the *transistors of the complex gate in (a)* such that the worst cast driving strength for all inputs is the same as a unit inverter. Give the width of all transistors in units of μm . Determine the logical effort for each input?

 


Fig.3 (b) Unit Inverter

**Sizes of all transistors:
(In units of μm)**

$LE_A =$

$LE_B =$

$LE_C =$

(c) (5 pts) In Fig. 3(c), we insert two unit-sized inverters to drive input A of the complex gate. For the complex gate, use the sizes of transistors that you derived in (b). Assume that $C_D = C_G = 2\text{fF}/\mu\text{m}$. The delay, T_{d1} , measured from **In** to **X** is 40ps. What is the delay, T_{d2} , measured from **In** to **Y**?

(Note: If you don't know the answer for (a) and (b), replace the complex gate with a 3-input NOR gate, $F = \overline{A + B + C}$. Size the transistors of 3-input NOR gate such that the worst cast driving strength for all inputs is the same as a unit inverter.)

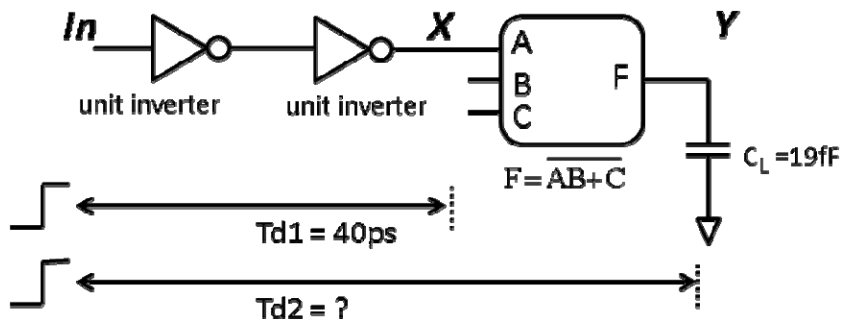


Fig.3 (c) Delay of the Complex Gate

Td2=

(d) (5pts) The complex gate that you designed in (a) is used in the critical path of the logical network shown in Fig. 3(d). Assume that $C_D = C_G = 2fF/\mu m$. What is the total path effort from In to Out? In order to minimize the delay, what should the effective fan-out per stage for this chain of gates be?

(Note: If you don't know the answer in (a) and (b), replace the complex gate with a 3-input NOR gate, $F = A + B + C$.)

 


Fig.3 (d) Critical Path of Combinational Logic

PE =

EF =