

---




# EE230-02 RFIC II

## Fall 2018

### Lecture 17: Phase-Locked Loops 2


Prof. Sang-Soo Lee  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)  
ENG-259
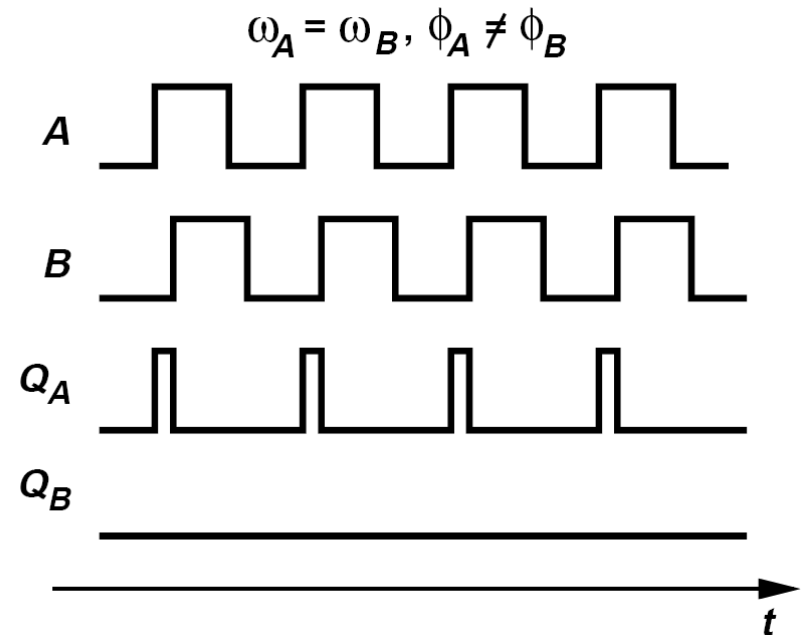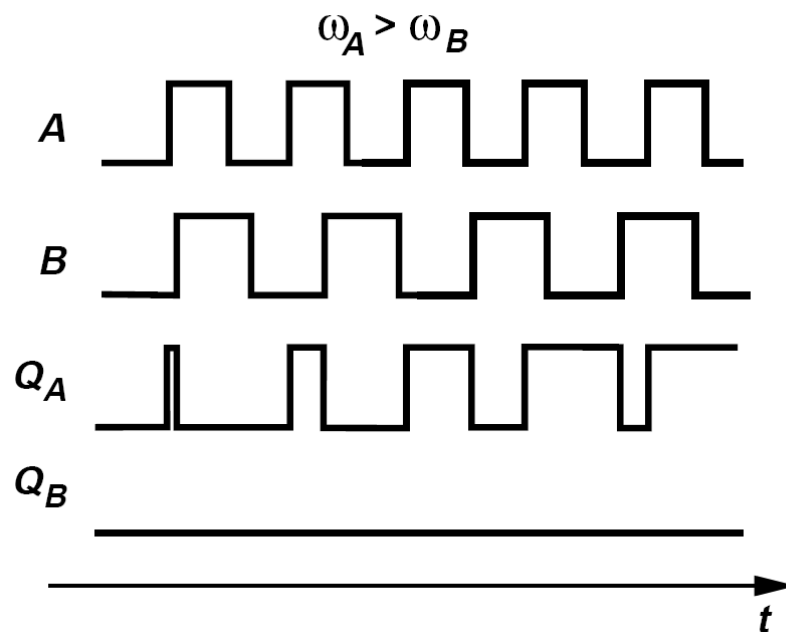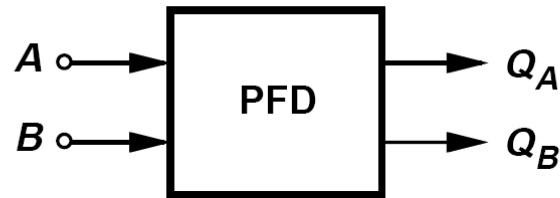
# Type-II PLLs: Phase/Frequency Detectors




- A rising edge on  $A$  yields a rising edge on  $Q_A$  (if  $Q_A$  is low)
- A rising edge on  $B$  resets  $Q_A$  (if  $Q_A$  is high)
- The circuit is symmetric with respect to  $A$  and  $B$  (and  $Q_A$  and  $Q_B$ )

# PFD: Logical Implementation

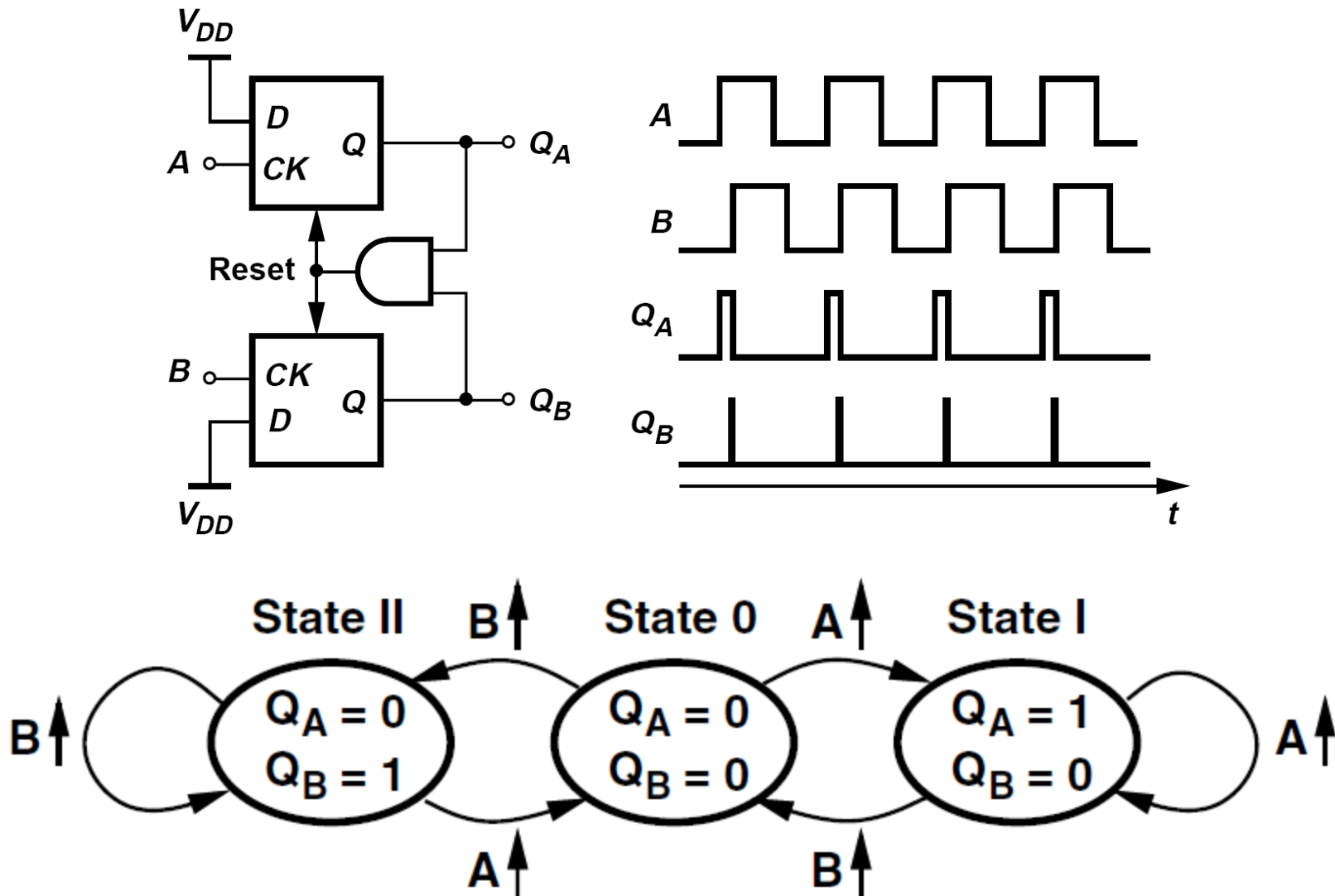

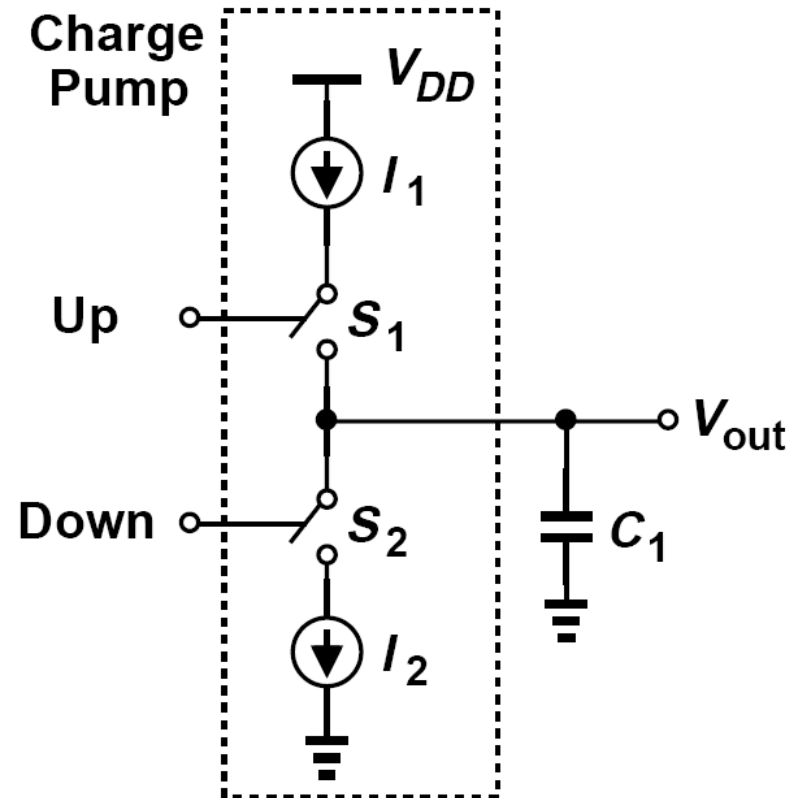
# Charge Pumps: an Overview

- Switches  $S_1$  and  $S_2$  are controlled by the inputs “UP” and “Down”
- A pulse on Up for  $\Delta T$  on  $S_1$  makes  $V_{out}$  goes up by  $\Delta T \cdot I_1/C_1$
- A pulse on Down yields a drop in  $V_{out}$ .



# Charge Pump PLLs: First Attempt

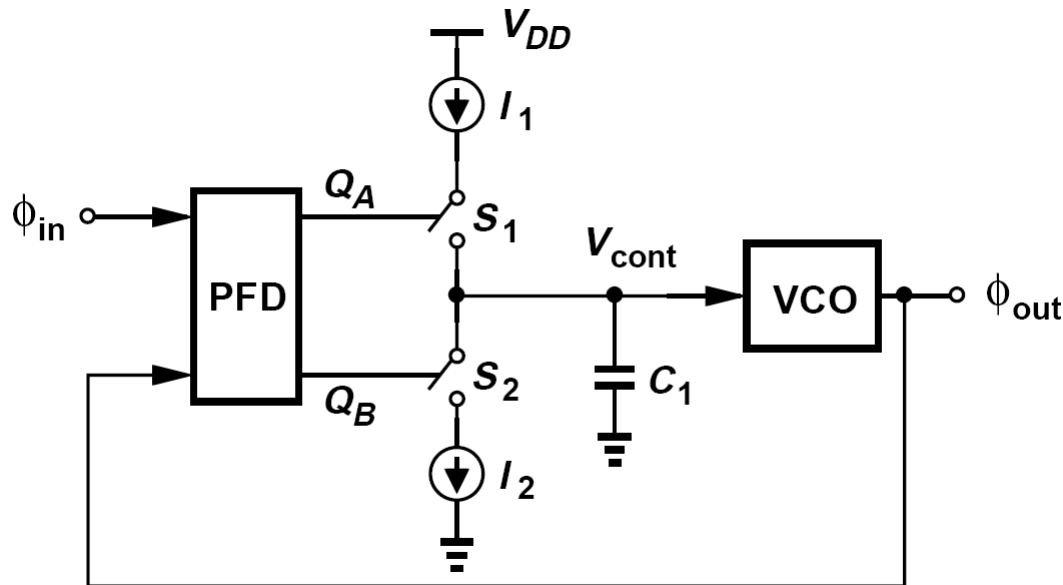


$$H(s) = \frac{\frac{I_p}{2\pi C_1 s} \cdot \frac{K_{VCO}}{s}}{1 + \frac{I_p}{2\pi C_1 s} \cdot \frac{K_{VCO}}{s}}$$

$$= \frac{I_p K_{VCO}}{2\pi C_1 s^2 + I_p K_{VCO}}$$

- Ideally forces the input phase error to zero because a finite error would lead to an unbounded value for  $V_{cont}$ .
- Called Type-II PLL because its open-loop transfer function contains two poles at the origin

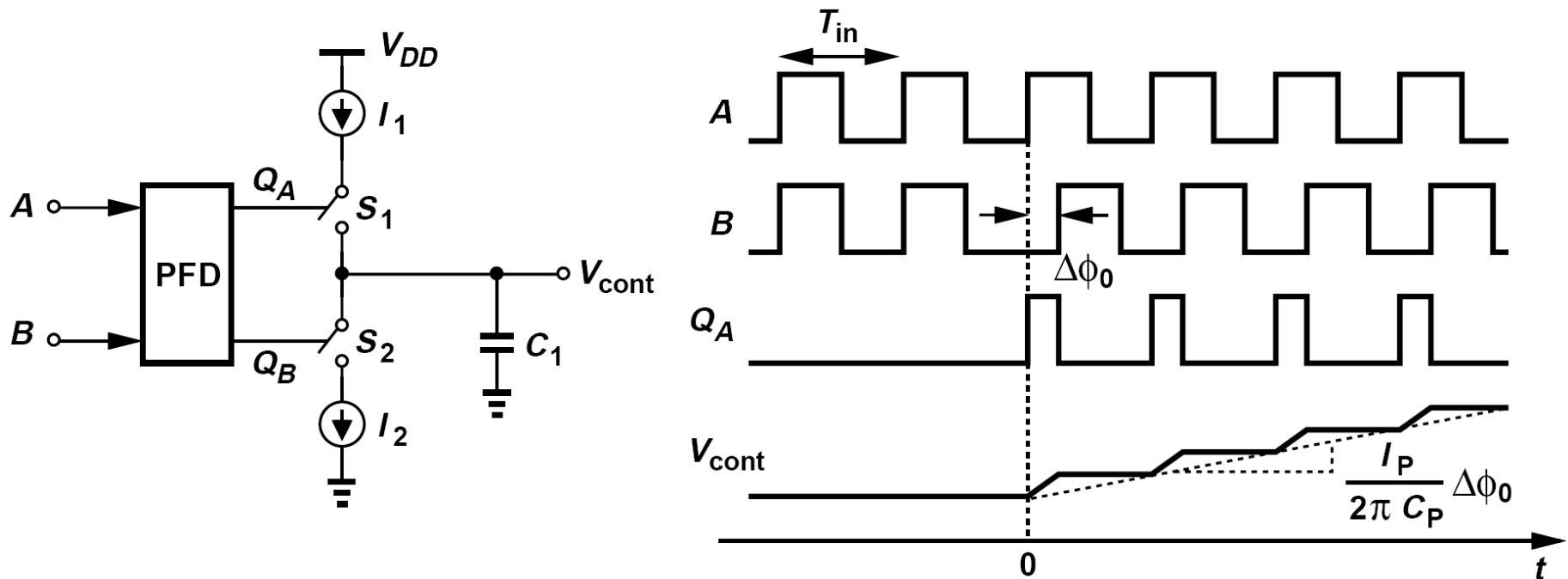
# Transfer Function: Continuous-Time Approximation



Approximate this waveform by a ramp --- as if the charge pump continuously injected current into  $C_1$


$$V_{cont}(t) \approx \frac{\Delta\phi_0}{2\pi} \frac{I_p}{C_1} t u(t) \quad \Longrightarrow \quad \frac{V_{cont}}{\Delta\phi}(s) = \frac{I_p}{2\pi C_1} \frac{1}{s}$$

# Charge-Pump PLL

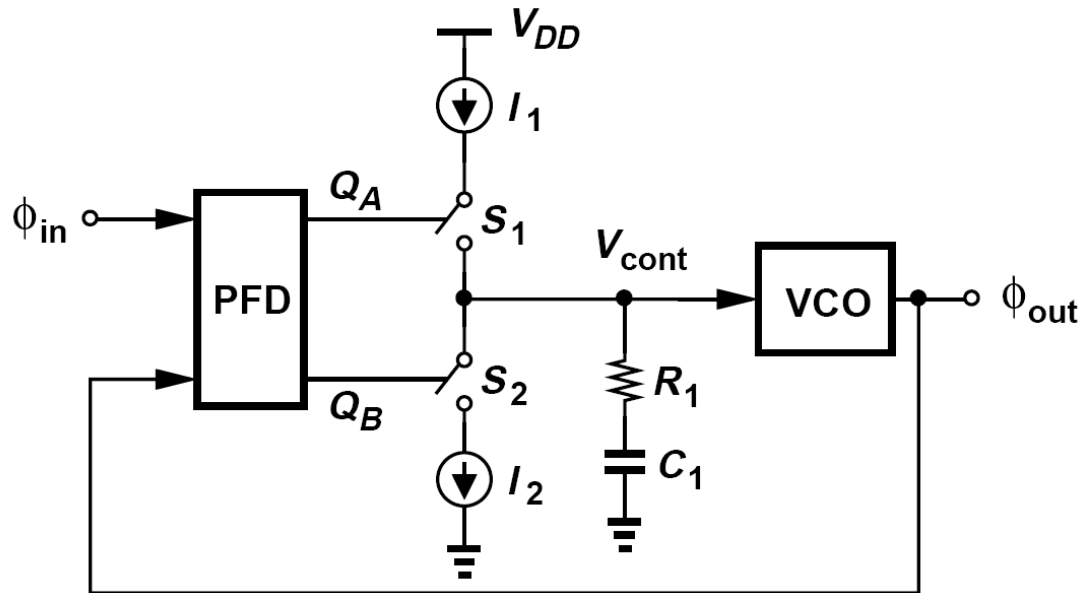

- If one of the integrators becomes lossy, the system can be stabilized.
- This can be accomplished by inserting a resistor in series with  $C_1$ . The resulting circuit is called a “Charge Pump PLL” (CPPLL)

# Computation of the Transfer Function

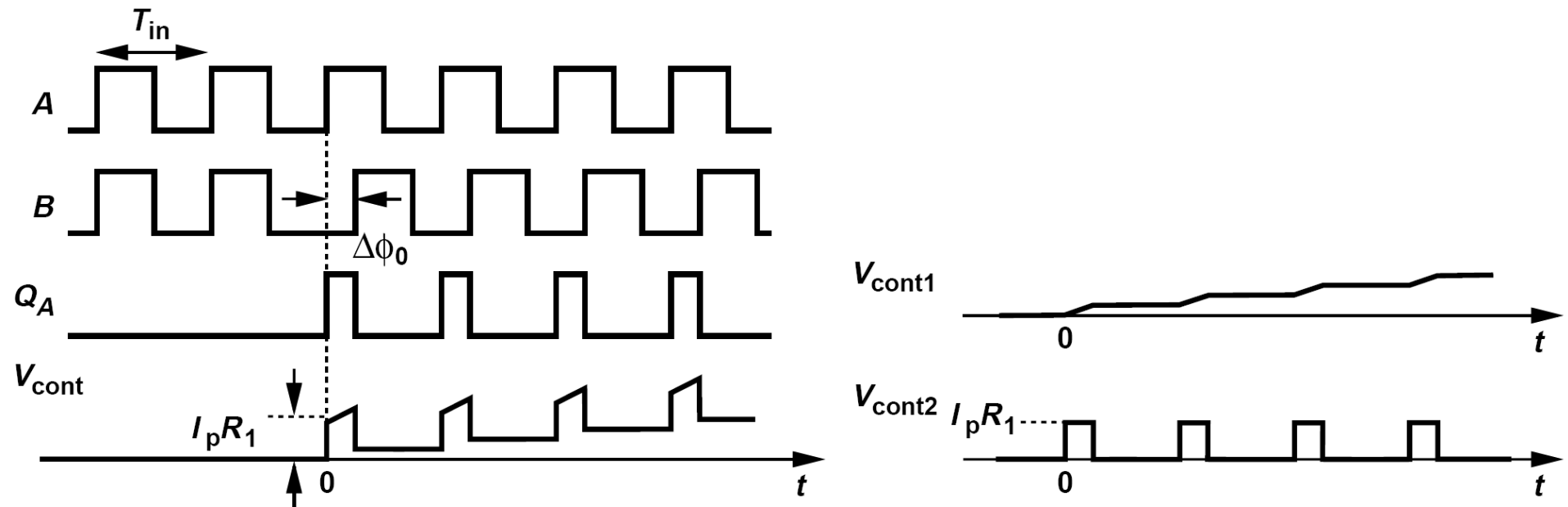

Approximate the pulse sequence by a step of height  $(I_p R_1)[\Delta\phi_0/(2\pi)]$ :

$$V_{cont}(t) = \frac{\Delta\phi_0}{2\pi} \frac{I_p}{C_1} t u(t) + \frac{\Delta\phi_0}{2\pi} I_p R_1 u(t)$$

$$\frac{V_{cont}}{\Delta\phi}(s) = \frac{I_p}{2\pi} \left( \frac{1}{C_1 s} + R_1 \right) \Rightarrow H(s) = \frac{\frac{I_p K_{VCO}}{2\pi C_1} (R_1 C_1 s + 1)}{s^2 + \frac{I_p}{2\pi} K_{VCO} R_1 s + \frac{I_p}{2\pi C_1} K_{VCO}}$$



# Stability of Charge-Pump PLL

Write the denominator as  $s^2 + 2\zeta\omega_n s + \omega_n^2$



$$\zeta = \frac{R_1}{2} \sqrt{\frac{I_p C_1 K_{VCO}}{2\pi}}$$


$$\omega_n = \sqrt{\frac{I_p K_{VCO}}{2\pi C_1}}$$

➤ As  $C_1$  increases, so does  $\zeta$  --- a trend opposite of that observed in type-I PLL: trade-off between stability and ripple amplitude thus removed.

Closed-loop poles are given by

$$\omega_{p1,2} = [-\zeta \pm \sqrt{\zeta^2 - 1}] \omega_n$$

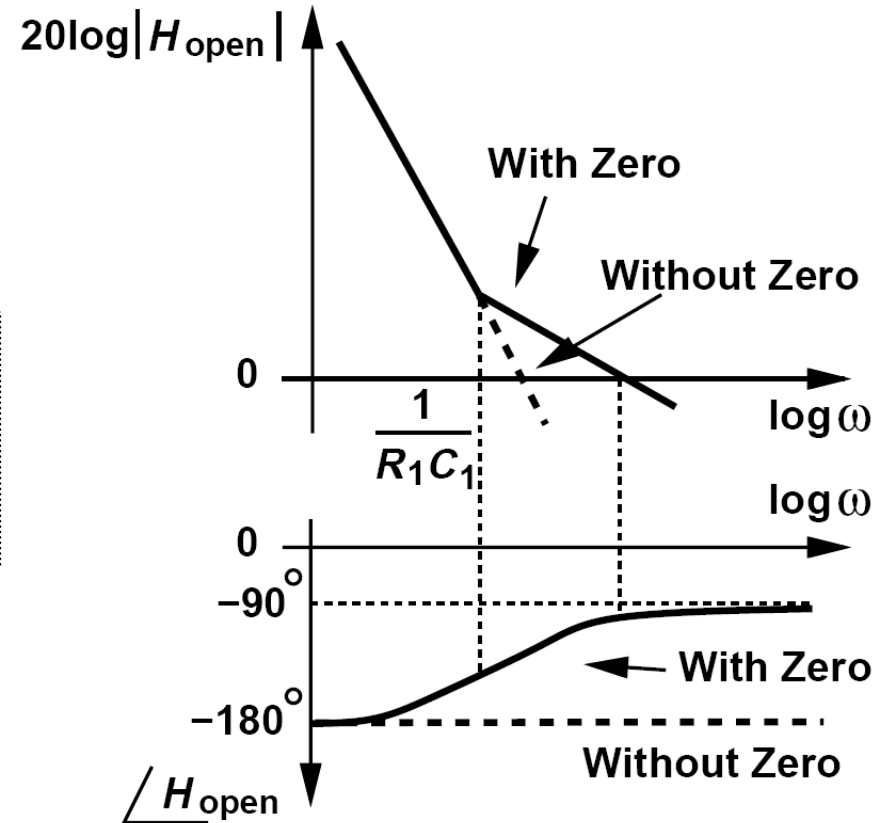A closed-loop zero at  $-\omega_n / 2\zeta$



$$\frac{V_{cont}}{\Delta\phi}(s) = \frac{I_p}{2\pi} \left( \frac{R_1 C_1 s + 1}{C_1 s} \right)$$