
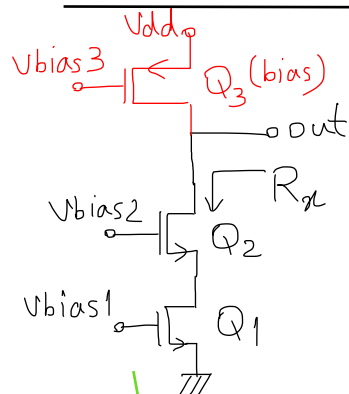


# \* Resistance of cascode transistors:

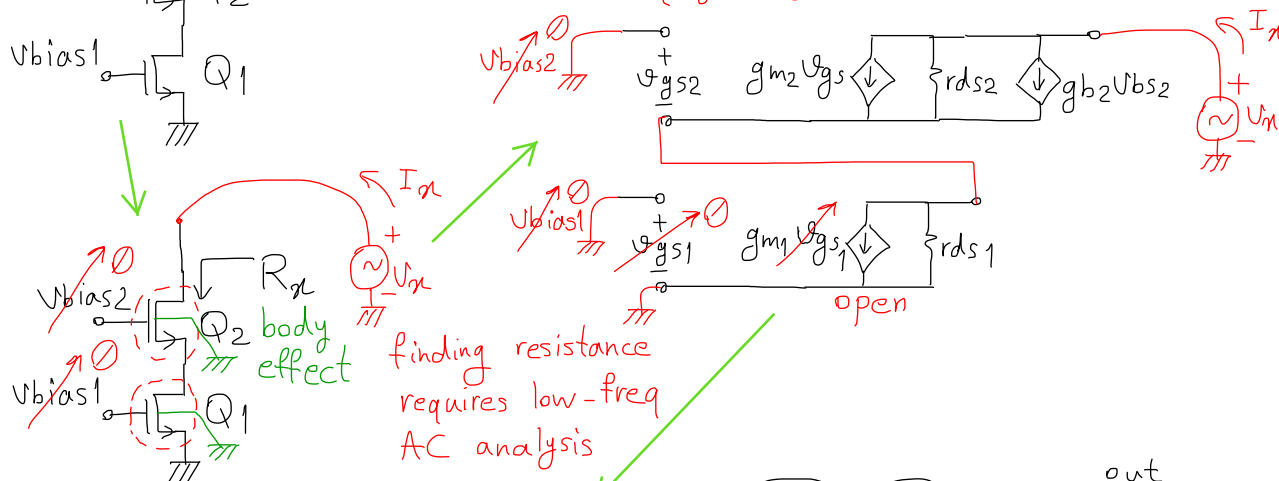


$$R_{out} = R_{\pi} \parallel r_{ds3}$$

$$\begin{cases} V_{bs2} = V_{b2} - V_{s2} = -V_{s2} \\ V_{gs2} = V_{g2} - V_{s2} = -V_{s2} \end{cases}$$



→ create T arrayed circuit:

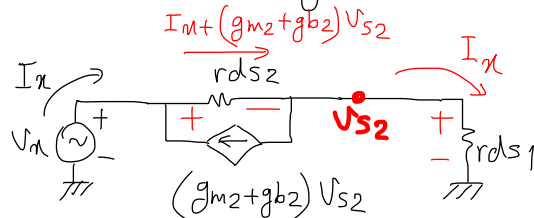

$$\begin{cases} V_n = r_{ds2} [I_n + (g_{m2} + g_{b2}) V_{s2}] + r_{ds1} I_n \\ V_{s2} = r_{ds1} \cdot I_n \end{cases}$$

$$\Rightarrow R_{\pi} = \frac{V_n}{I_n} = r_{ds1} + r_{ds2} + (g_{m2} + g_{b2}) r_{ds1} r_{ds2} = (g_{m2} r_{ds2}) r_{ds1}$$

intrinsic gain



$$\begin{cases} g_m \cdot r_{ds} \gg 1 \\ g_m \gg g_b \end{cases}$$

\* current mirrors:


dominant

$$A_v = g_m (r_{ds} \parallel g_m r_{ds}^2)$$

large

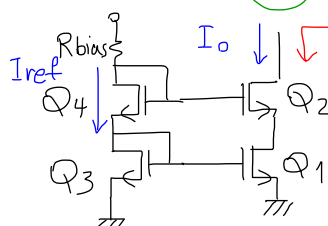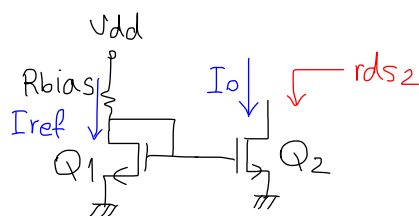


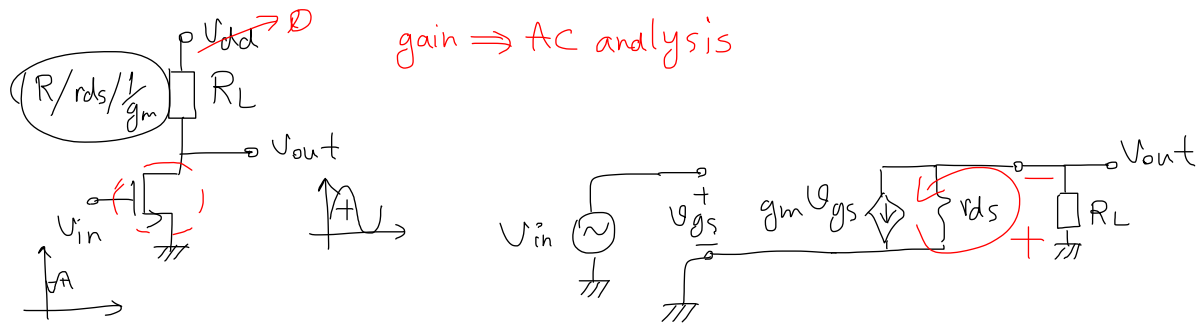here the difference between  $I_o$  and  $I_{ref}$  decreases.




$$\begin{cases} V_{out} = -g_m V_{gs} (r_{ds} \parallel R_L) \\ V_{gs} = V_{in} \end{cases} \Rightarrow \text{gain} = \frac{V_{out}}{V_{in}} = -g_m (r_{ds} \parallel R_L)$$

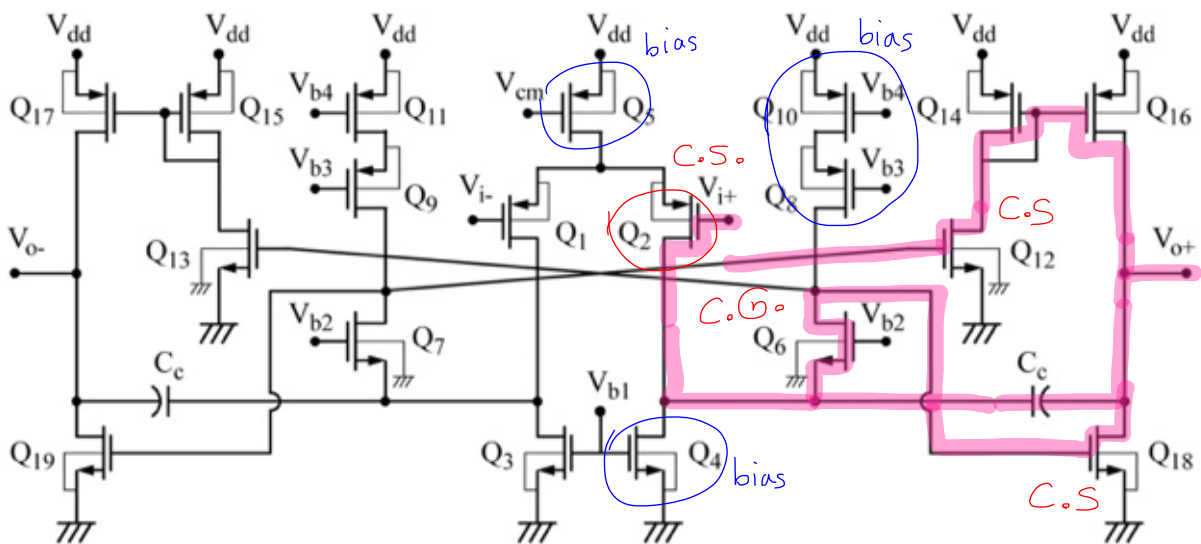$R_L$  must be very large to increase gain. As a result, drain of biasing transistor is always connected to output node.



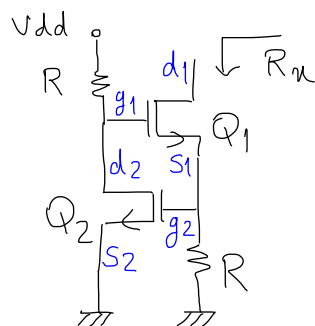\* Assume all transistors operate in saturation. ignore body effect. find  $R_n$ ?



→ discard all DC sources


short voltage sources

open current sources


→ replace transistors with small-signal model

→ connect  $V_n$ , find  $R_n = \frac{V_n}{i_n}$

\* Small-signal AC model

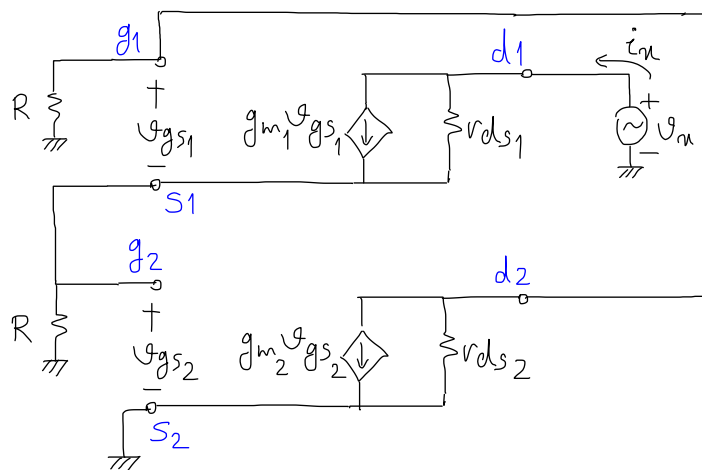

\* T-arrayed small-signal AC model

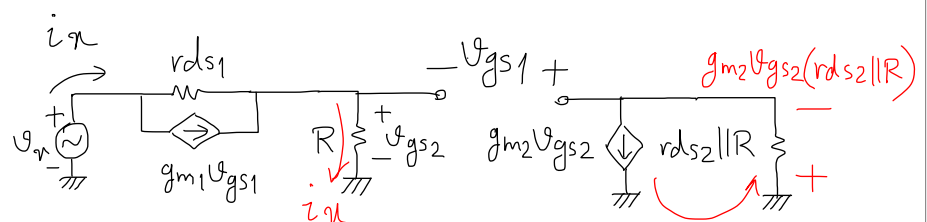

$$\begin{cases} V_{gs2} = -V_{gs1} - g_{m2}V_{gs2}(r_{ds2} \parallel R) \\ V_{gs2} = R i_n \\ V_n = r_{ds1} [i_n - g_{m1}V_{gs1}] + V_{gs2} \end{cases} \Rightarrow R_n = \frac{V_n}{i_n} = r_{ds1} + R + \dots$$