
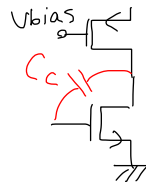


* opamp design :

Compensation capacitor

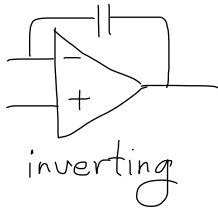


$$C_c \gg 100 \times C_{gs}$$

$$C_{gs} = 15 \text{ fF}$$


$$C_c = 1.5 \text{ pF}$$

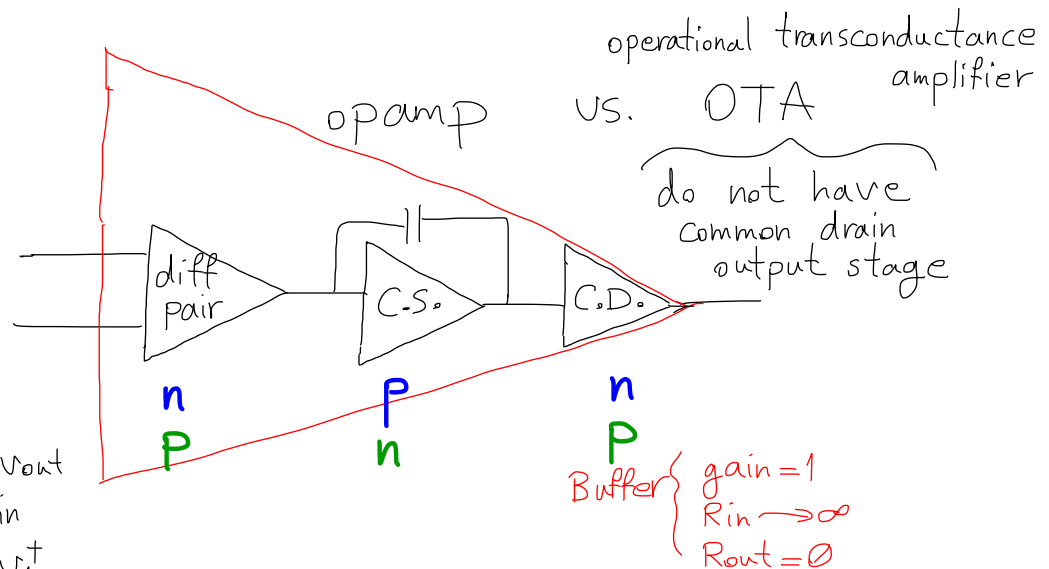resistance of previous stage $\rightarrow \frac{1}{rC_c} \leftarrow \omega_{p1}$ first pole of common source amplifier



unity gain

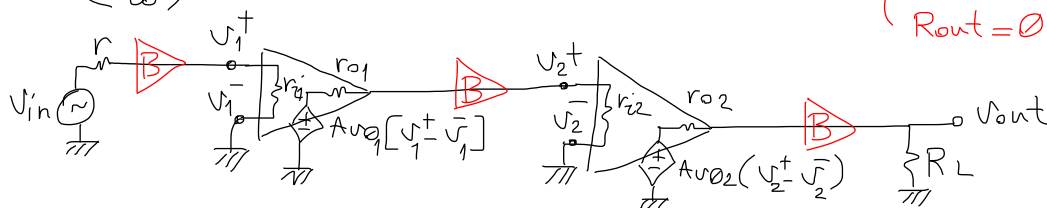
$V_{out} = \left(1 + \frac{0}{\infty}\right) V_{in}$



$$V_{out} = A_{v02} \frac{R_L}{r_{o2} + R_L} \times A_{v01} \frac{r_{i2}}{r_{o1} + r_{i2}} \times V_{in} \frac{r_{i1}}{r + r_{i1}}$$

if all resistors are equal :
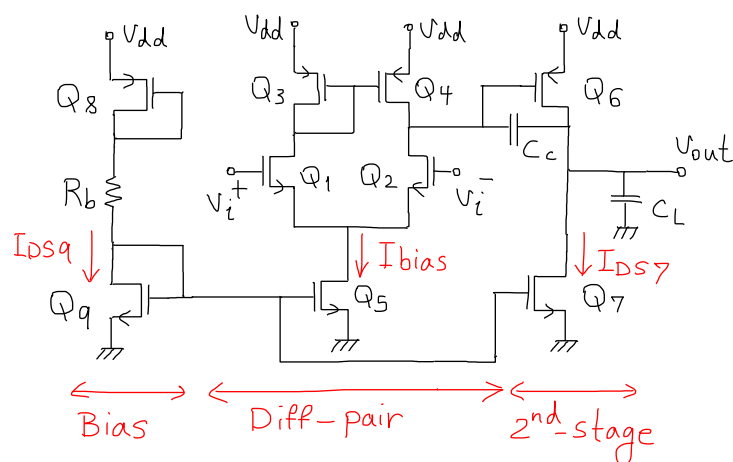
$$\frac{V_{out}}{V_{in}} = \frac{A_{v01} \cdot A_{v02}}{8}$$





$$A_{v02} = -g_{m2}(r_{ds2} || r_{d4})$$

$$A_{\varnothing 6} = -g_{m6}(r_{ds6} || r_{ds7})$$


Av02.Av06


$$g_{m2} = \mu_n C_{ox} \frac{W}{L} V_{eff}$$
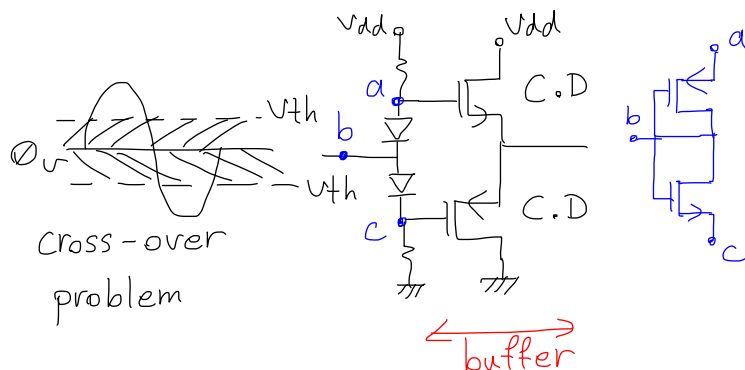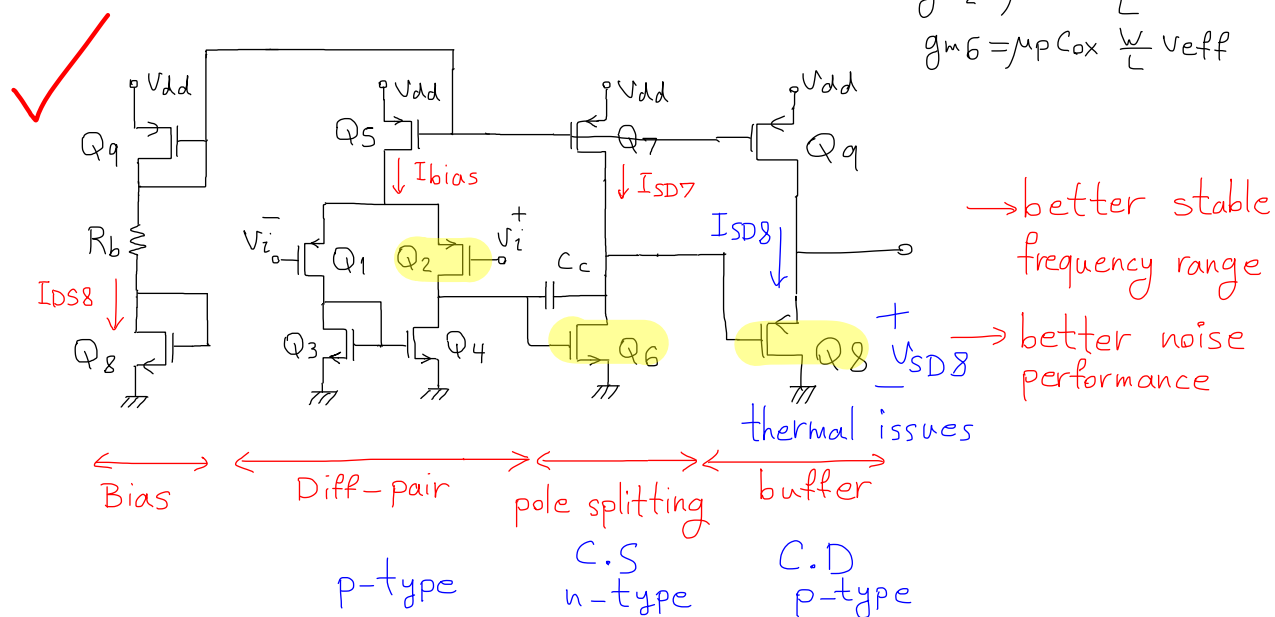
$$g_m = \mu_p C_{ox} \frac{W}{L} v_{eff}$$



$v_{dd} \gg 2V_{ON}$
push-pull amplifier

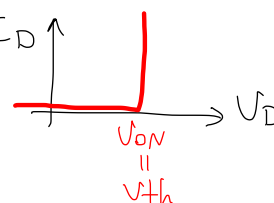

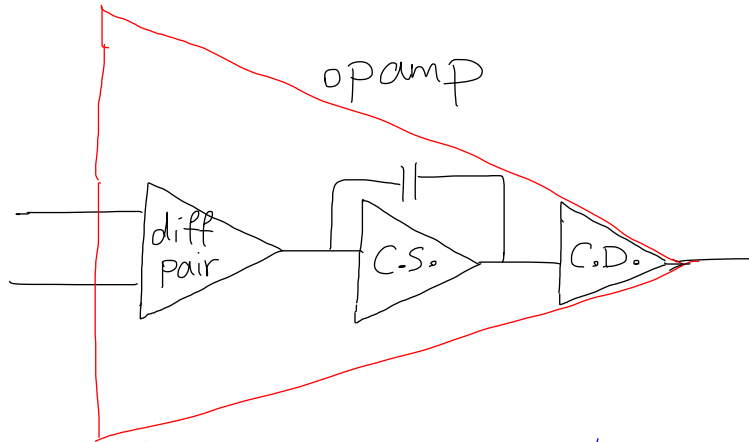

① \Rightarrow n-type p-type n-type
 ② \Rightarrow p-type n-type p-type

} Both have the same gain

2nd approach is better because it provides more pole splitting

