

Midterm Exam

March 6, 9:10-10:30am

Name: _____

(50 points total)

PROBLEM 1: Consider the common source amplifier shown in Fig. 1. [12 points]

- (a) Calculate the noise factor of this circuit, assuming it is driven by a source with an output impedance of R_S . For the transistor, include C_{gs} in the small signal model. You may neglect induced gate noise, $1/f$ noise, r_o , and all other small signal capacitances. [10]
- (b) Now assume that the amplifier is being designed to operate at the frequency ω_c , and C_{gd} is no longer small enough to be neglected. We have connected an inductor from the gate to the drain of $M1$ to increase the reverse isolation. How should the inductor be sized? [2]

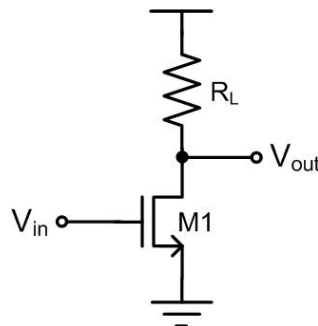


Figure 1: Common source amplifier schematic for Problem 1.

PROBLEM 1 (cont'd)

PROBLEM 2: Consider the matching network shown in Fig. 2, consisting of two inductors and one capacitor. **[12 points]**

- (a) If R_L is $50\ \Omega$, choose values for C , L_1 , and L_2 so that R_{IN} is $10\ \Omega$ at $\omega = 5 \times 10^9$ rad/s (hint: more than one solution is possible). **[10]**
- (b) What advantages (if any) does this matching network have over a standard L-match? **[2]**

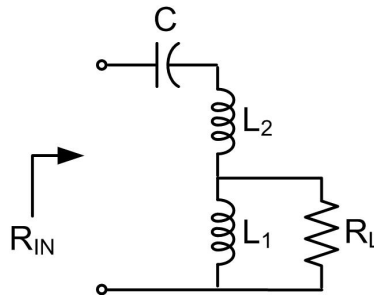


Figure 2: Matching network for Problem 2.

PROBLEM 3: Your manager has asked you to evaluate the linearity of an RF front end. You know that for a signal input power of -30 dBm the power of the fundamental component at the output is -10 dBm, and for two tones with an input power of -30 dBm, the IM3 components have a power of -70 dBm at the output. **[12 points]**

- What is the gain of the system? **[1]**
- Using the plot in Fig. 3, calculate the IIP3 for the system. Draw in the relevant curves, and label the IP3 point on the plot. **[3]**
- If the bandwidth of the system is 10 MHz, the noise figure is 14 dB, what is the input referred noise floor (hint: this was contained in the formula given in class for the sensitivity)? What is the output referred noise floor? **[5]**
- Draw the output referred noise floor into the plot in Fig. 3, and mark the SFDR. What is the SFDR for this system? **[3]**

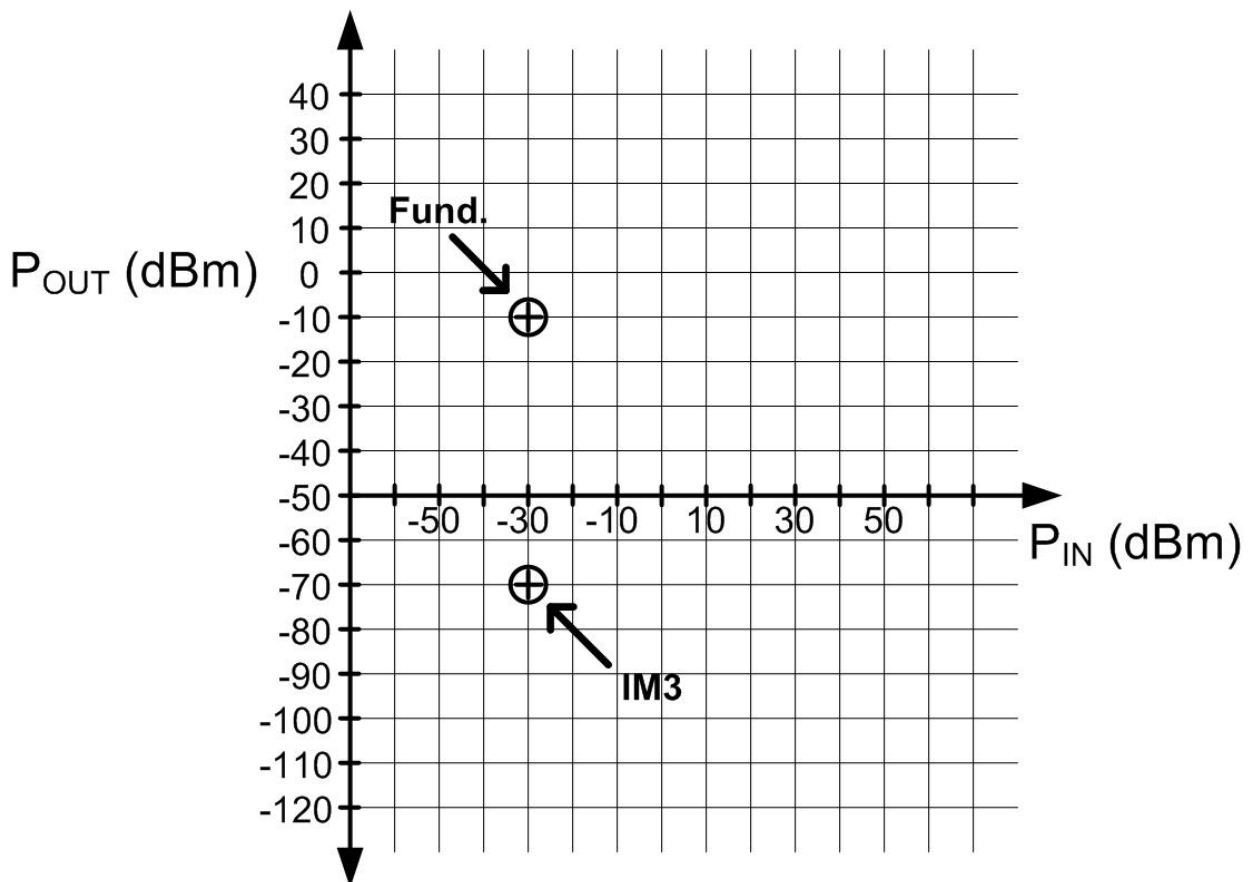


Figure 3: SFDR plot for Problem 3.

PROBLEM 3 (cont'd)

PROBLEM 4: Shown in Fig. 4 is the down-conversion chain for an RF receiver. The incoming signal of interest is centered around $f_C = 900$ MHz, and low-side LO injection is used for down-conversion, with $f_{LO} = 850$ MHz. [12 points]

- What is the intermediate frequency (f_{IF}) for this system? [1]
- If the bandwidth of each channel is 2 MHz, what is the approximate Q required for the channel select filter? [2]
- What is the image frequency for the signal of interest? [1]
- Now assume that the specifications for each of the system blocks are as shown in Table 1. What is the noise figure of the down-conversion chain as a whole (note the distinction between the noise figure (NF, in dB) as provided in Table 1 and the noise factor also discussed in class (F, in linear units))? [8]

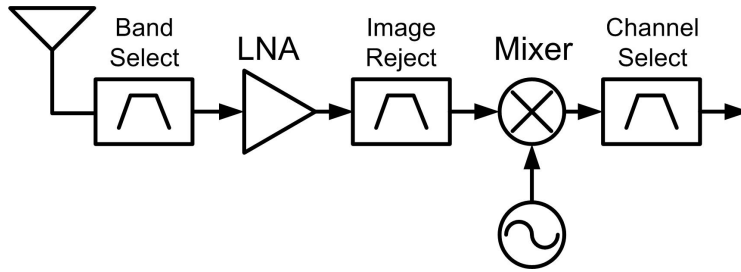


Figure 4: Down-conversion chain for Problem 4.

| Component | Noise Figure (dB) | Available Power Gain (dB) |
|-----------------------|-------------------|---------------------------|
| Band Select filter | 0 | -3 |
| Low Noise Amplifier | 3 | 20 |
| Image Reject filter | 0 | -3 |
| Mixer | 10 | 0 |
| Channel Select filter | 0 | -3 |

Table 1: Noise Figures and Available Power Gains for components in Fig. 4.

PROBLEM 4 (cont'd)

PROBLEM 5: Your boss has asked you to interview someone for a new position in the RFIC design group at your company. So far only one candidate has applied (see Fig. 5)? **[2 points]**

- (a) Who is this man? **[1]**
- (b) Would you trust him to design your RF front ends? **[1]**



Figure 5: Job applicant for RFIC position.