# EE223 Homework 3 Designed of a Beta Multiplier Enrique Hernandez Sanchez 10/13/18

### 1. Run a Dc simulation with VDD = 1V, Temperature = 27c in Typical Corner.

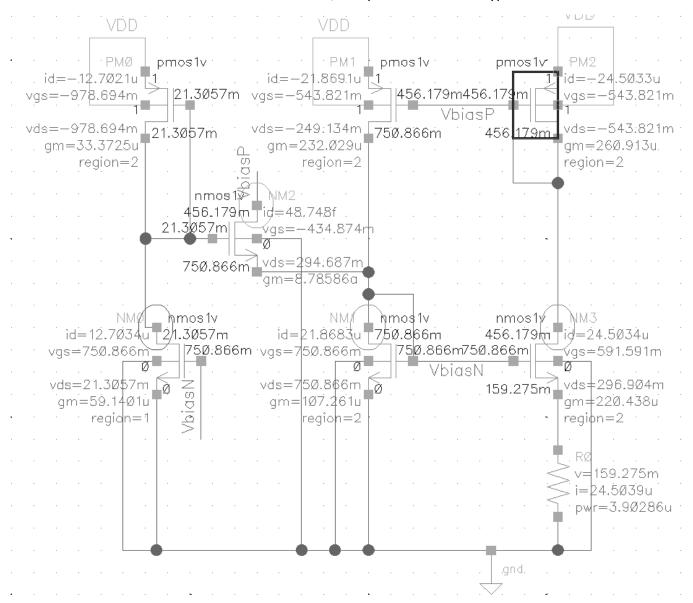


Figure 1: Operating Point information and node voltages

### 2. ADE-XL transient simulation for 1u

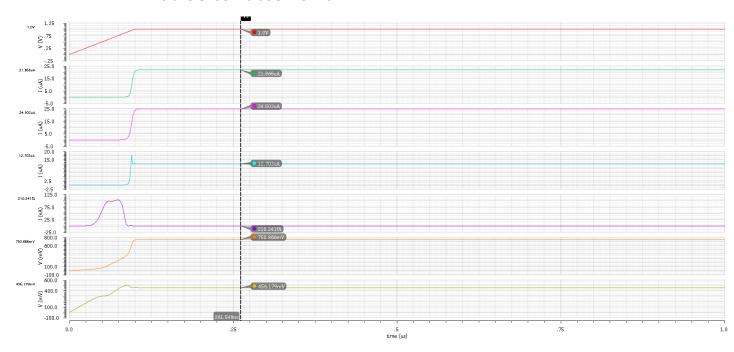


Figure 2: Transient waveforms with startup circuit. (VDD= red trace, Vbiasn = orange trace, Vbiasp=yellow trace, NM1 = green trace, NM3=violate trace, NMo=blue trance, NM2=purple trance)

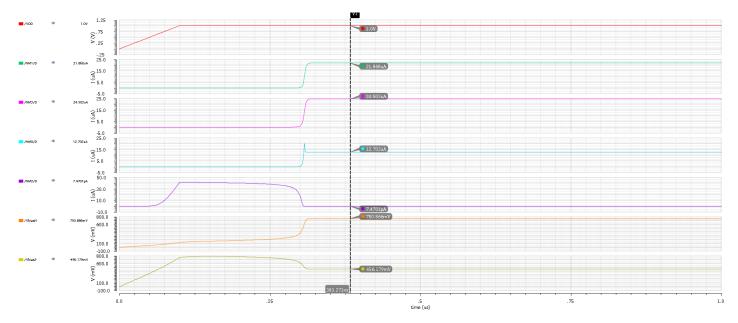


Figure 3: Transient waveforms with startup circuit. (VDD= red trace, Vbiasn = orange trace, Vbiasp=yellow trace, NM1 = green trace, NM3=violate trace, NMo=blue trance, NM2=purple trance)

3. From simulation find Kp value

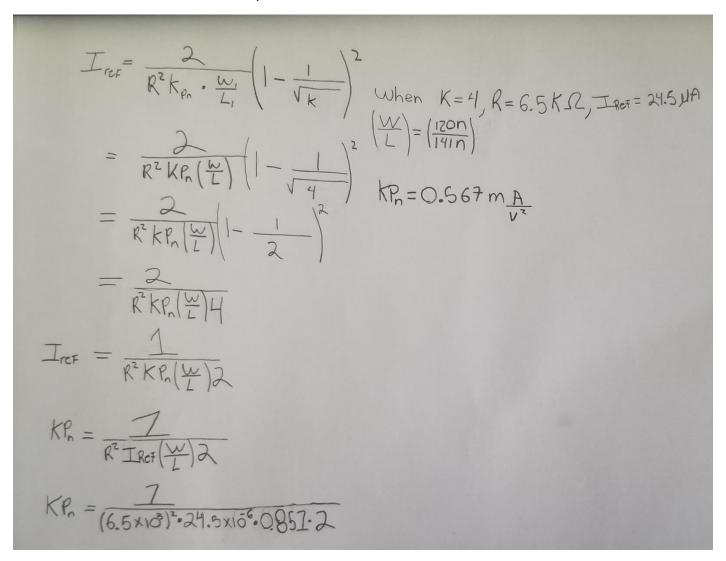


Figure 4: Kp value using simulation Iref

- 4. Using ADL-XL, simulate the circuit in the fallowing conditions and check if the circuit starts without problem. Measure the current through M4 at 1us and Plot it over the fallowing PVT corners.
  - a. Process variation:

Parameter	Min	Max	C5_0	C5_1	C5_2	C5_3	C5_4
VDD			1	1	1	1	1
gpdk045.scs			ff	fs	sf	SS	tt
temperature			27	27	27	27	27
value(IT("/NM3/S") 1e-06)	-2.54E-05	-2.35E-05	-2.54E-05	-2.44E-05	-2.46E-05	-2.35E-05	-2.45E-05

# b. Supply variation:

Parameter			C6_0	C6_1	C6_2	C6_3	C6_4
VDD			8.00E-01	9.00E-01	1	1.1	1.2
gpdk045.scs			tt	tt	tt	tt	tt
temperature			27	27	27	27	27
Output	Min	Max	C6_0	C6_1	C6_2	C6_3	C6_4
value(IT("/NM3/S") 1e-06)	-2.96E-05	-1.66E-05	-1.66E-05	-2.10E-05	-2.45E-05	-2.73E-05	-2.96E-05

# c. Temperature Variation:

Parameter	Min	Max	C7_0	C7_1	C7_2	C7_3	C7_4
VDD			1	1	1	1	1
gpdk045.scs			tt	tt	tt	tt	tt
temperature			-40	0	25	50	100
value(IT("/NM3/S") 1e-06)	-2.73E-05	-1.85E-05	-1.85E-05	-2.22E-05	-2.44E-05	-2.60E-05	-2.73E-05

# d. All PVT variations:

Parameter	Min	Max	C9_0	C9_1	C9_2	C9_3	C9_4	C9_5
VDD			9.00E-01	9.00E-01	9.00E-01	9.00E-01	1	1
gpdk045.scs			ff	ff	ff	ff	ff	ff
temperature			-40	0	50	100	-40	0
value(IT("/PM2/D") 1e-06)	-3.39E-05	-1.55E-05	-1.73E-05	-2.06E-05	-2.35E-05	-2.43E-05	-1.92E-05	-2.30E-05
C9_6	C9_7	C9_8	C9_9	C9_10	C9_11	C9_12	C9_13	C9_14
1	1	1.1	1.1	1.1	1.1	9.00E-01	9.00E-01	9.00E-01
ff	ff	ff	ff	ff	ff	fs	fs	fs
50	100	-40	0	50	100	-40	0	50
-2.72E-05	-2.93E-05	-2.10E-05	-2.51E-05	-3.02E-05	-3.39E-05	-1.64E-05	-1.95E-05	-2.18E-05
C9_15	C9_16	C9_17	C9_18	C9_19	C9_20	C9_21	C9_22	C9_23
9.00E-01	1	1	1	1	1.1	1.1	1.1	1.1
fs	fs	fs	fs	fs	fs	fs	fs	fs
100	-40	0	50	100	-40	0	50	100
-2.20E-05	-1.84E-05	-2.21E-05	-2.59E-05	-2.73E-05	-2.01E-05	-2.42E-05	-2.92E-05	-3.22E-05
C9_24	C9_25	C9_26	C9_27	C9_28	C9_29	C9_30	C9_31	C9_32
9.00E-01	9.00E-01	9.00E-01	9.00E-01	1	1	1	1	1.1
sf	sf	sf	sf	sf	sf	sf	sf	sf
-40	0	50	100	-40	0	50	100	-40
-1.64E-05	-1.94E-05	-2.15E-05	-2.19E-05	-1.86E-05	-2.24E-05	-2.59E-05	-2.71E-05	-2.05E-05
C9_33	C9_34	C9_35	C9_36	C9_37	C9_38	C9_39	C9_40	C9_41
1.1	1.1	1.1	9.00E-01	9.00E-01	9.00E-01	9.00E-01	1	1
sf	sf	sf	SS	SS	SS	SS	SS	SS
0	50	100	-40	0	50	100	-40	0
-2.48E-05	-2.97E-05	-3.22E-05	-1.55E-05	-1.83E-05	-1.98E-05	-1.98E-05	-1.78E-05	-2.15E-05
C9_42	C9_43	C9_44	C9_45	C9_46	C9_47	C9_48	C9_49	C9_50
1	1	1.1	1.1	1.1	1.1	9.00E-01	9.00E-01	9.00E-01
SS	SS	SS	SS	SS	SS	tt	tt	tt
50	100	-40	0	50	100	-40	0	50
-2.45E-05	-2.51E-05	-1.98E-05	-2.41E-05	-2.86E-05	-3.03E-05	-1.64E-05	-1.95E-05	-2.17E-05
C9_51	C9_52	C9_53	C9_54	C9_55	C9_56	C9_57	C9_58	C9_59
9.00E-01	1	1	1	1	1.1	1.1	1.1	1.1
tt	tt	tt	tt	tt	tt	tt	tt	tt
100	-40	0	50	100	-40	0	50	100
-2.21E-05	-1.84E-05	-2.22E-05	-2.60E-05	-2.73E-05	-2.03E-05	-2.45E-05	-2.94E-05	-3.23E-05

Mean	sum of squares	sum of squares /(n-1)	Mean + sigma	Mean - sigma
-2.33168E-05	1.24249E-09	4.58902E-06	-1.87278E-05	-2.79059E-05

# e. Plot Gm vs Temp of Mn1

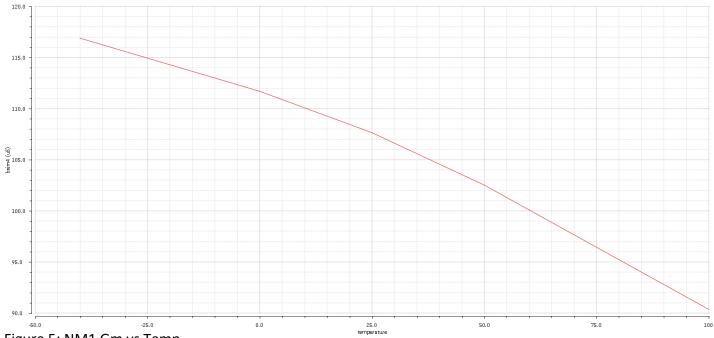


Figure 5: NM1 Gm vs Temp