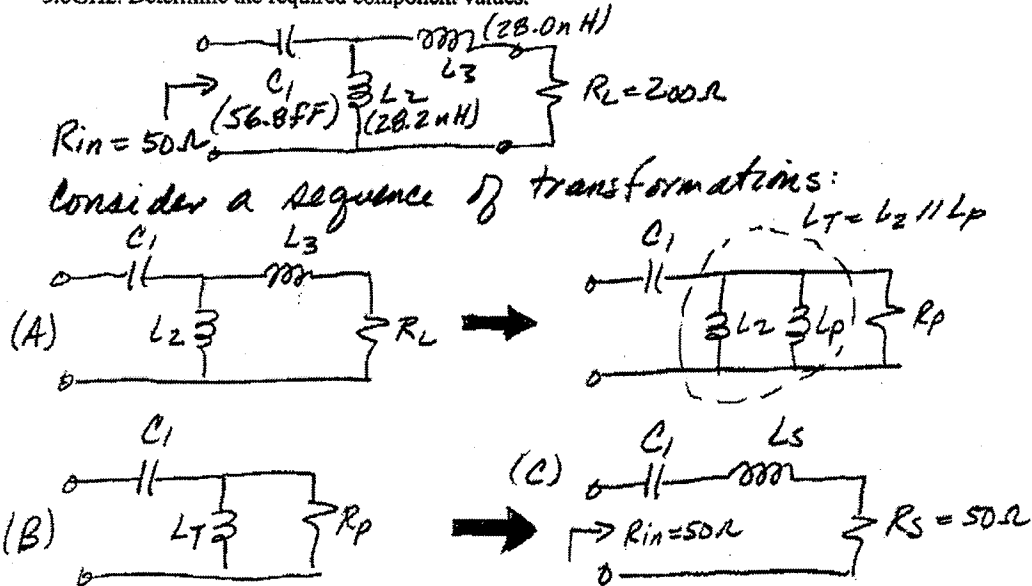


**EE 538B CMOS RF IC DESIGN****Midterm Examination: May 14, 2003**Student Name: SolutionsUW Student ID #: 123-45-6789*You are allowed one sheet of notes. Write legibly. Show all work. State assumptions.*

Problem #	Points Possible	Points
1	25	25
2	25	25
3	25	25
4	25	25
		<del>100</del>

1. (25 points) With  $Q=10$ , the matching circuit below is used to convert  $R_L = 200\Omega$  to  $R_{in} = 50\Omega$  at  $f_0 = 5.6\text{GHz}$ . Determine the required component values.



The final circuit is pure series RLC circuit:  
 $Q = 10$ ;  $R_s = R_{in} = 50\Omega$ ;  $f_0 = 5.6\text{GHz}$

For (C):  $Q = 10 = \frac{\omega_0 L_3}{R_s} \Rightarrow L_3 = \frac{Q R_s}{\omega_0} = \boxed{14.2\text{ nH}}$

$Q = 10 = \frac{1}{\omega_0 R_s C_1} \Rightarrow C_1 = \frac{1}{\omega_0 R_s Q} = \boxed{56.8\text{ fF}}$

For B:  $R_p = R_s (Q^2 + 1) = 50 (101) = \boxed{5050\Omega}$

$L_T = L_s \frac{(Q^2 + 1)}{Q^2} = \frac{(14.2\text{ nH})(101)}{100} = \boxed{14.4\text{ nH}}$

Transformation from  $R_L = 200\Omega$  to  $R_p = 5050\Omega$  via  $Q_2$ :

$Q_2 = \sqrt{\frac{R_p}{R_L} - 1} = 4.92$


$Q_2 = \frac{\omega_0 L_3}{R_L} \Rightarrow L_3 = \frac{Q_2 R_L}{\omega_0} = \boxed{28.0\text{ nH}}$

$Q_2 = \frac{R_p}{\omega_0 L_p} \Rightarrow L_p = \frac{R_p}{Q_2 \omega_0} = \boxed{29.2\text{ nH}}$

$L_2 = \frac{L_T L_p}{L_p - L_T} = \boxed{28.2\text{ nH}}$


test midterm\_1 schematic : May 22 14:14:00 2003

S-Parameter Response

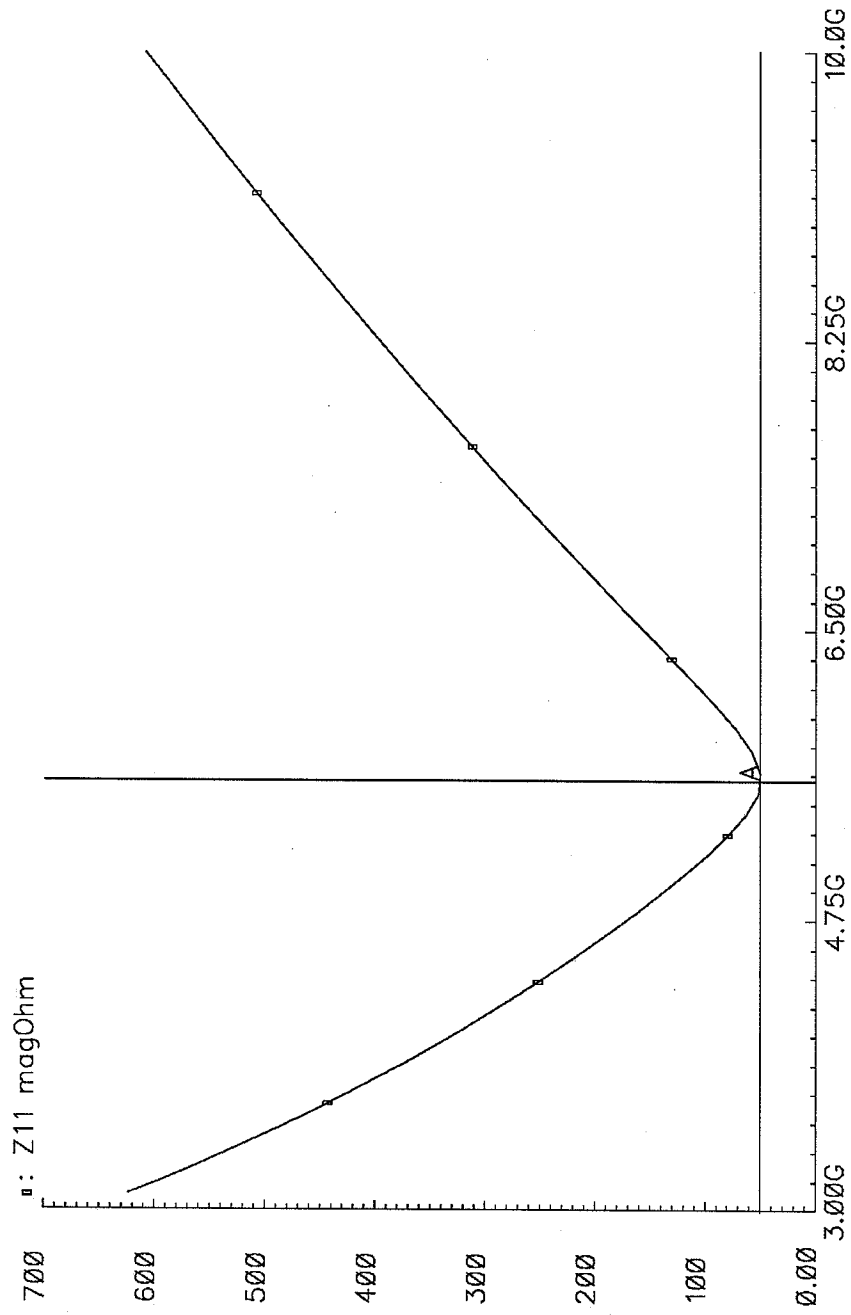

A: (5.5953G 51.0492)

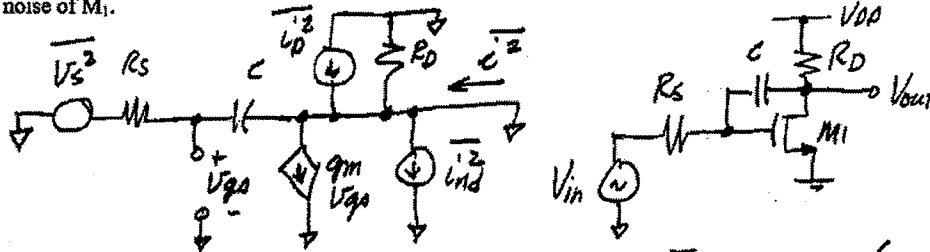2. (25 points) Find the noise factor of the circuit shown with respect to the source resistance  $R_s$ . Neglect channel length modulation effects and all parasitic capacitors. Consider only drain current noise of  $M_1$ .



$$\overline{V_s^2} = 4kTR_s \Delta f; \quad \overline{i_d^2} = 4kT \gamma g_{d0} \Delta f; \quad \overline{i_D^2} = \frac{4kT}{R_D} \Delta f$$

(i) Consider  $\overline{i_D^2}$ :  $\overline{i_1^2} = \overline{i_D^2} = \frac{4kT}{R_D} \Delta f$

(ii) Consider  $\overline{i_{nd}^2}$ :  $\overline{i_2^2} = \overline{i_{nd}^2} = 4kT \gamma g_{d0} \Delta f$

(iii) Consider  $\overline{V_s^2}$ : Note that  $\overline{V_s}$  creates a noise current that flows through  $R_s$  and  $C$  to the output.  $\overline{V_s}$  also creates  $\overline{V_{gs}}$  via the  $R_s$  and  $C$  voltage divider and  $\overline{V_{gs}}$  multiplied by  $g_m$  creates another output current noise component. These two components are completely correlated.

$$\overline{V_{gs}} = \frac{1/sC}{R_s + 1/sC} \overline{V_s} = \frac{1}{sR_sC + 1} \overline{V_s} \Rightarrow \overline{V_{gs}^2} = \frac{1}{(WR_sC)^2 + 1} \overline{V_s^2}$$


$$\overline{i_3} = g_m \overline{V_{gs}} - sC \overline{V_{gs}} = \overline{V_{gs}} (g_m - sC)$$

$$\therefore \overline{i_3^2} = \overline{V_{gs}^2} (g_m^2 + (WC)^2) = \frac{g_m^2 + (WC)^2}{(WR_sC)^2 + 1} \overline{V_s^2}$$



$$F = (\overline{i_1^2} + \overline{i_2^2} + \overline{i_3^2}) / \overline{i_1^2}$$

$$= 1 + \frac{[(WR_sC)^2 + 1]}{[g_m^2 + (WC)^2]} \cdot \left( \frac{1}{R_D R_s} + \frac{\gamma g_{d0}}{R_s} \right) \quad \leftarrow \text{ANS.}$$

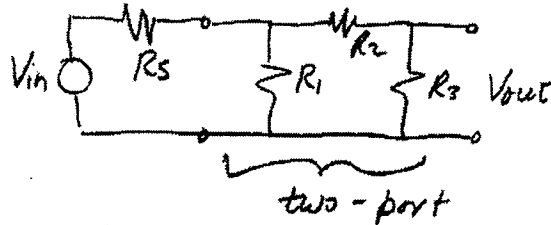3. (25 points) Determine expressions for the equivalent two-port input noise voltage and current power sources for the two-port network shown assuming it is driven from a source resistance  $R_s$ .



Consider the two port:

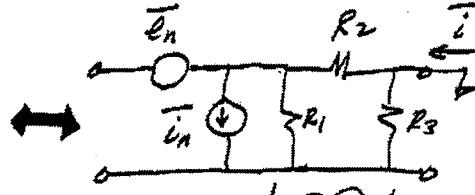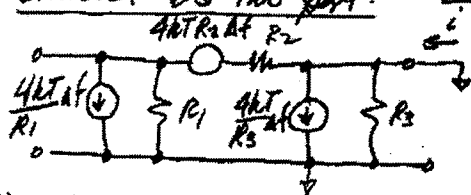

(a) Short input:

$$\begin{aligned} \overline{i^2} &= \frac{4kT\Delta f}{R_3} + \frac{4kT\Delta f R_2}{R_2^2} \\ &= 4kT\Delta f \left( \frac{1}{R_2} + \frac{1}{R_3} \right) \end{aligned}$$

(a) Short input:

$$\overline{i^2} = \frac{\overline{i_n^2}}{R_2^2}$$

Hence,  $\overline{i_n^2} = 4kT\Delta f R_2^2 \left( \frac{1}{R_2} + \frac{1}{R_3} \right) \leftarrow \overline{i_n^2}$



(b) Open circuit input:

$$\begin{aligned} \overline{i^2} &= \frac{4kT\Delta f}{R_1} \left( \frac{R_1}{R_1+R_2} \right)^2 + \frac{4kT\Delta f}{R_3} + \frac{4kT\Delta f R_2}{(R_1+R_2)^2} \left\{ \overline{i^2} = \overline{i_n^2} \cdot \left( \frac{R_1}{R_1+R_2} \right)^2 \right. \\ &= 4kT\Delta f \left[ \frac{R_1}{(R_1+R_2)^2} + \frac{1}{R_3} + \frac{R_2}{(R_1+R_2)^2} \right] \end{aligned}$$


$$\begin{aligned} \therefore \overline{i_n^2} &= \overline{i^2} \cdot \frac{(R_1+R_2)^2}{R_1^2} = 4kT\Delta f \left[ \frac{R_1}{(R_1+R_2)^2} + \frac{1}{R_3} + \frac{R_2}{(R_1+R_2)^2} \right] \frac{(R_1+R_2)^2}{R_1^2} \\ &= 4kT\Delta f \left[ \frac{1}{R_1} + \frac{(R_1+R_2)^2}{R_1^2 R_3} + \frac{R_2}{R_1^2} \right] \leftarrow \overline{i_n^2} \end{aligned}$$

4. (25 points) Find an expression for the noise factor of the circuit below with respect to the source resistance  $R_s$ . Neglect channel length modulation and all parasitic capacitors; also, neglect induced gate current noise.

The noise sources are uncorrelated:

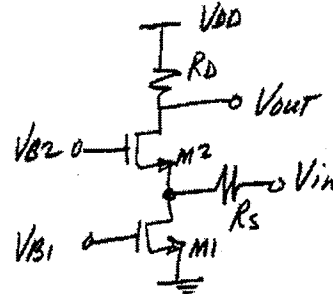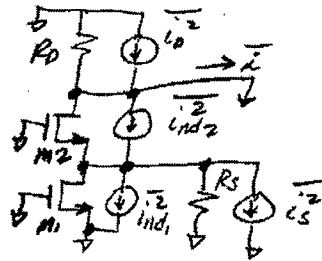

$$\begin{aligned} \overline{i_{n,R_s}^2} &= \frac{4kT\Delta f}{R_s} \left( \frac{R_s}{R_s + 1/g_{m2}} \right)^2 \\ \overline{i_{n,M1}^2} &= 4kT\gamma g_{d01}\Delta f \left( \frac{R_s}{R_s + 1/g_{m2}} \right)^2 \\ \overline{i_{n,R_D}^2} &= \frac{4kT\Delta f}{R_D} \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} \text{note current} \\ \text{divider between} \\ R_s \text{ and } 1/g_{m2}. \end{array}$$

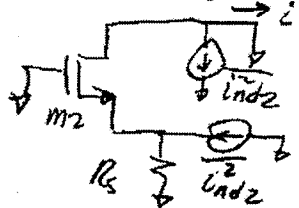

In this model, the components of  $i$  are obviously correlated.

$$\begin{aligned} \overline{i_{n,M2}^2} &= 4kT\gamma g_{d02}\Delta f \left[ \frac{R_s}{R_s + 1/g_{m2}} - 1 \right]^2 \\ &= 4kT\gamma g_{d02}\Delta f \left[ \frac{1}{1 + g_{m2}R_s} \right]^2 \end{aligned}$$

Finally,

$$F = \frac{4kT\Delta f g_{m2}^2 R_s}{(1 + g_{m2}R_s)^2} + \frac{4kT\Delta f \gamma g_{d01} g_{m2}^2 R_s}{(1 + g_{m2}R_s)^2} + \frac{4kT\Delta f \gamma g_{d02}}{(1 + g_{m2}R_s)^2} + \frac{4kT\Delta f}{R_D}$$

$$= 1 + \gamma_1 g_{d01} R_s + \frac{\gamma_2 g_{d02}}{g_{m2}^2 R_s} + \frac{(1 + g_{m2}R_s)^2}{g_{m2}^2 R_D R_s} \leftarrow F$$