 


Sequential Circuit

Lecture 16


Advanced Digital IC Design



Khosrow Ghadiri




 - Finite State Machine:
- Four states: **00**, **01**, **10**, and **11** represented by two bits: S_0S_1
- One input i with values 0, and 1.
- Transition structure:






- Finite State Machine:
- Truth table:

 

| i | S_0 | S_1 | S_0^+ | S_1^+ |
|-----|-------|-------|---------|---------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 |




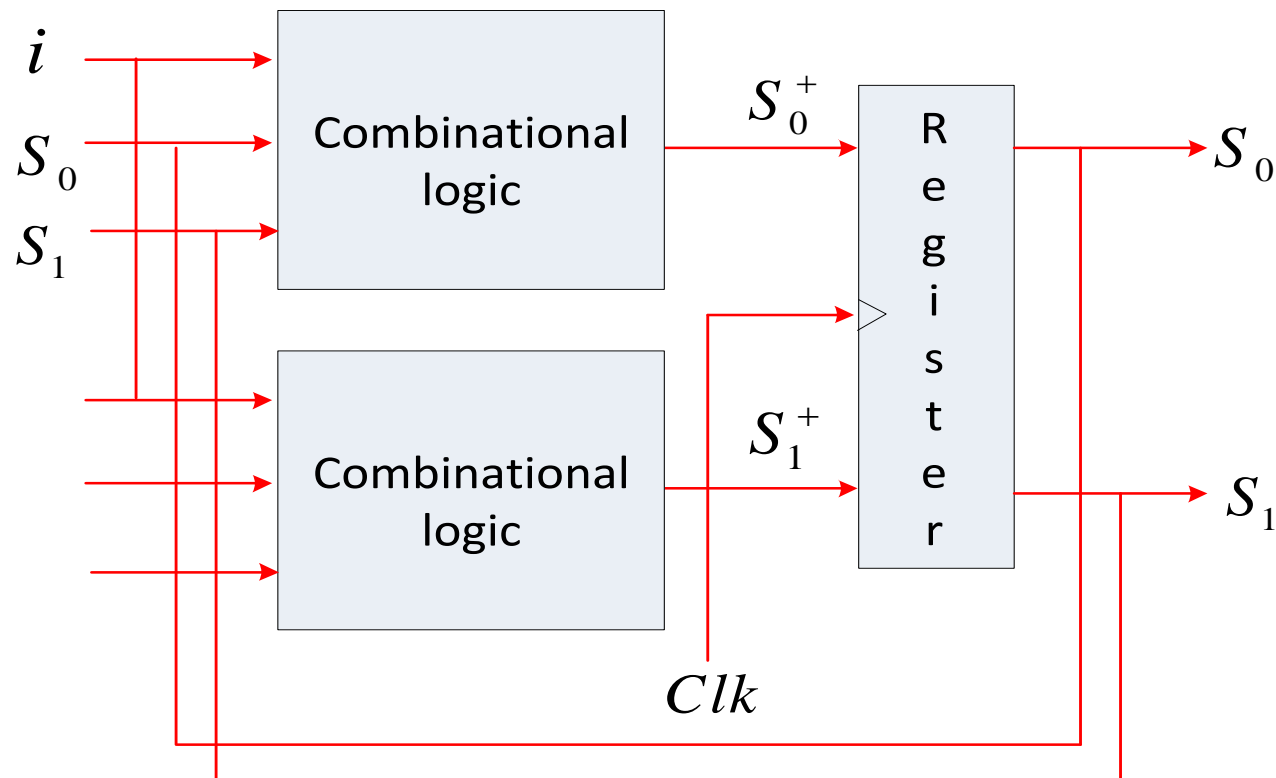- Finite State Machine:
- Implementing the two Boolean variable S_0S_1 .
- Stored in the register






- Finite State Machine:

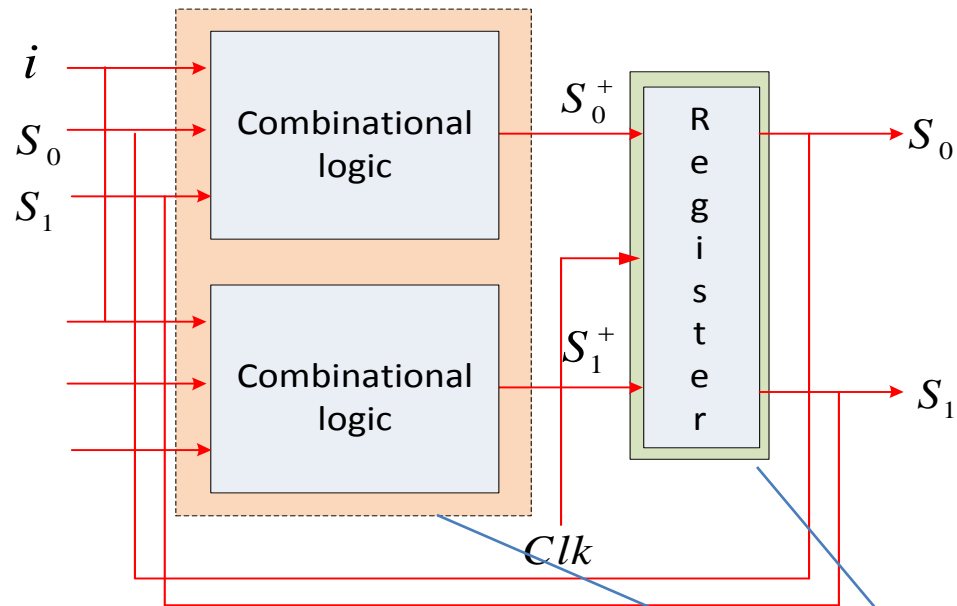


| i | S_0 | S_1 | S_0^+ | S_1^+ | Q_1 | Q_2 |
|-----|-------|-------|---------|---------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | | |
| 0 | 0 | 1 | 1 | 1 | | |
| 0 | 1 | 0 | 0 | 0 | | |
| 0 | 1 | 1 | 1 | 1 | | |
| 1 | 0 | 0 | 0 | 1 | | |
| 1 | 0 | 1 | 0 | 1 | | |
| 1 | 1 | 0 | 1 | 0 | | |
| 1 | 1 | 1 | 1 | 0 | | |

- Mealy Machine

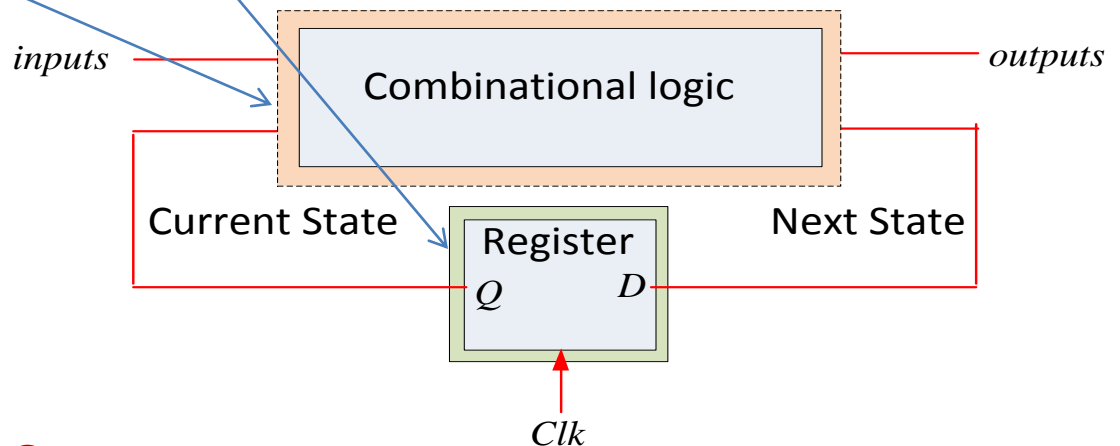





- Timing definition:

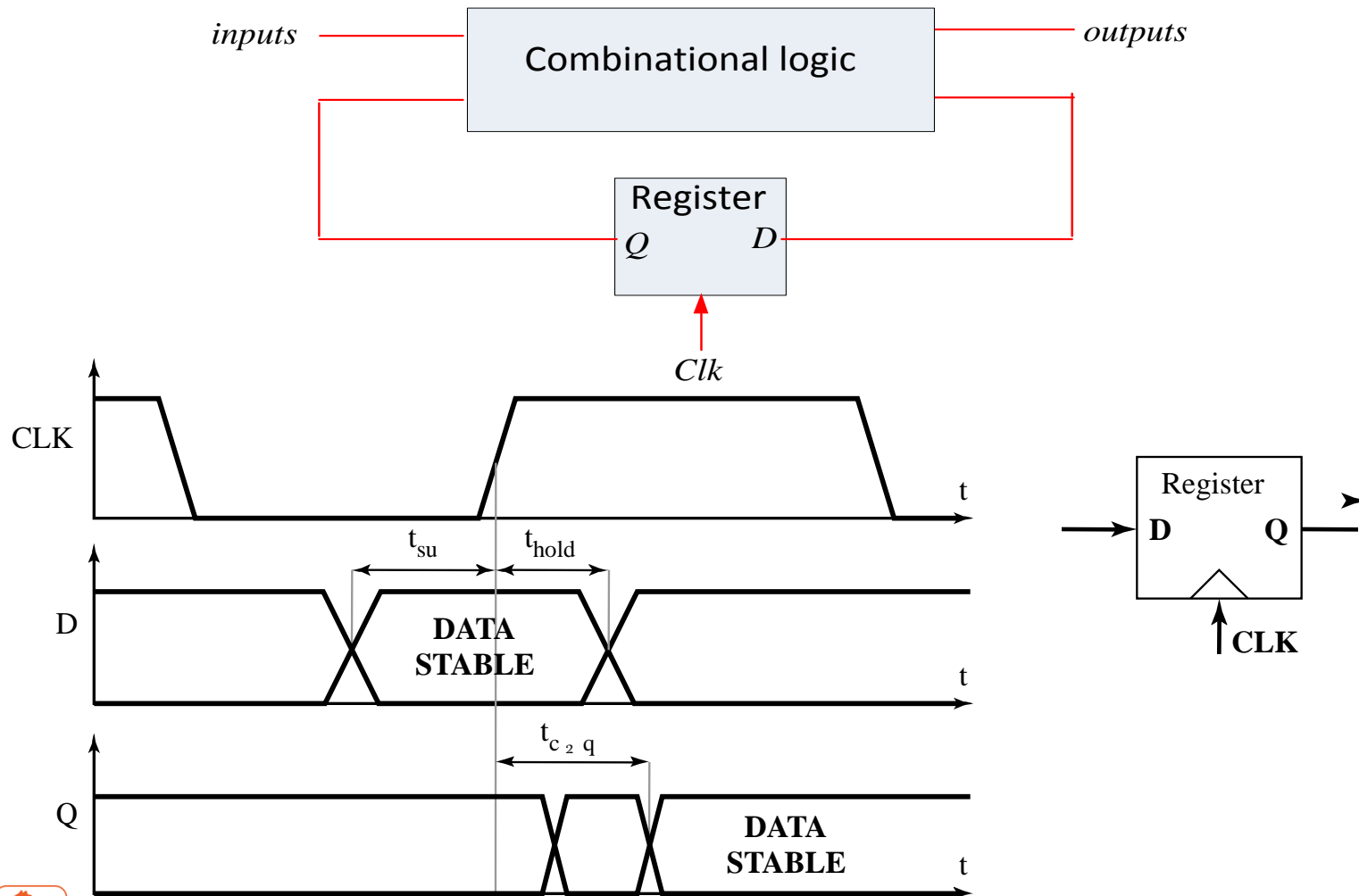





 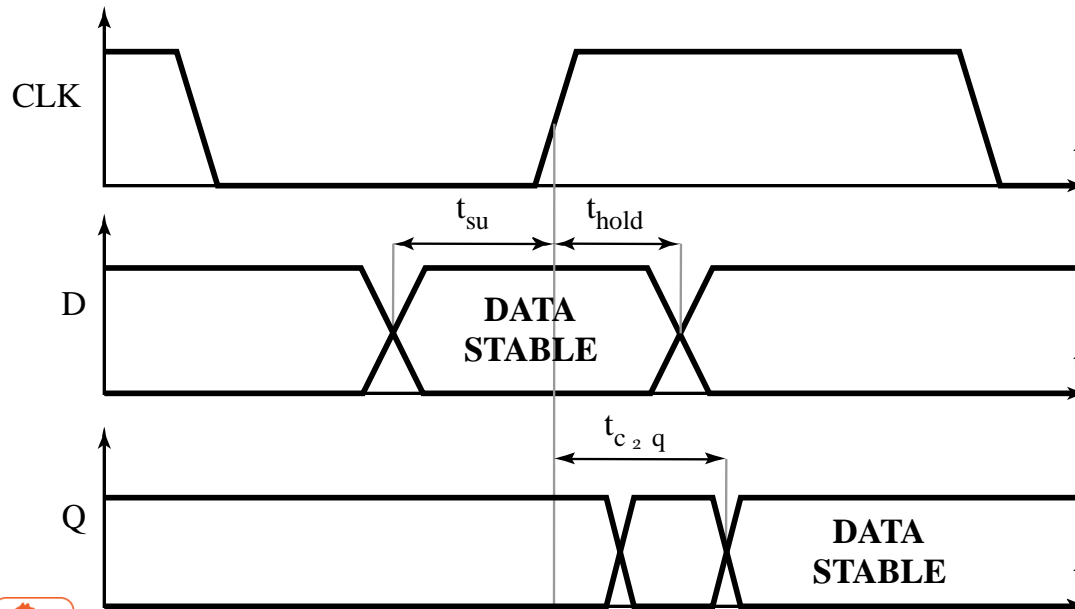- Timing definition:
 - ① Set-up time t_{su} : the duration that data inputs (D) must be valid before the clk transition edge.
 - ② Hold time t_{hold} : the duration that data inputs (D) must be valid after the clk transition edge.
 - ③ The propagation delay t_{c2q} : the worst-case propagation delay the data at D is copied to Q reference to clk







  - Timing definition:
- The switching take place concurrently in response to a clock stimulus in the synchronous sequential circuit.
- Result of operations await the next till next clock transition before progressing to the next stage.





 
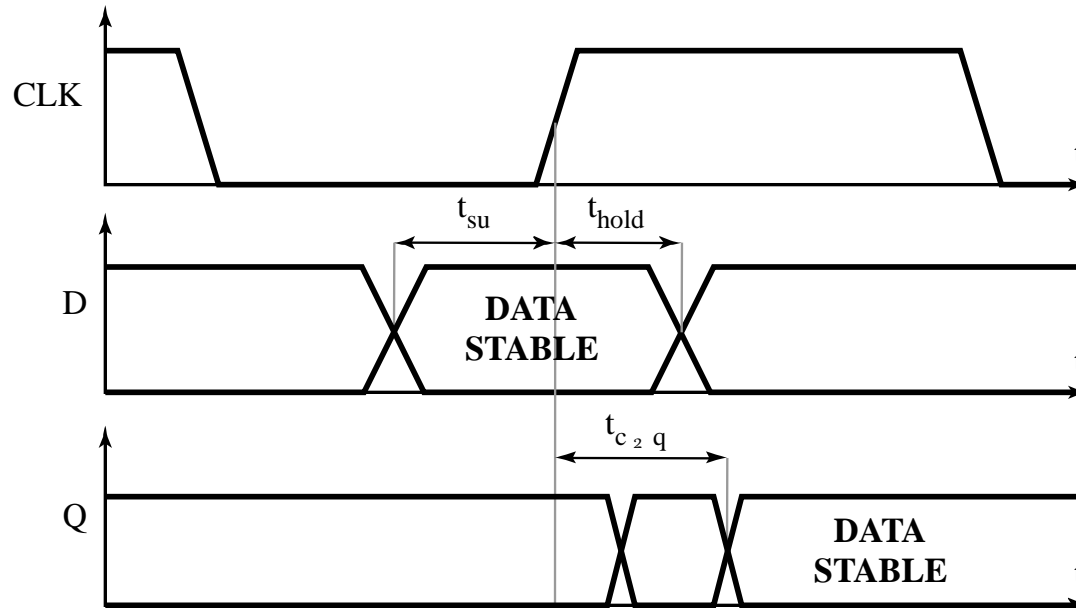
- Timing definition:
- All current computation must complete and the system has to come to rest before next cycle can begin.
- The clock period T at which the sequential circuit operates, must accommodate the longest delay of any stage in the network.






- Timing definition:
- The worst delay propagation delay of the logic: t_{plogic}
- The minimum delay of the logic (contamination delay): t_{cd}
- Constraint **1** : The minimum clock period T

$$T \geq t_{c2q} + t_{plogic} + t_{su}$$

  



- Maximum clock Frequency:

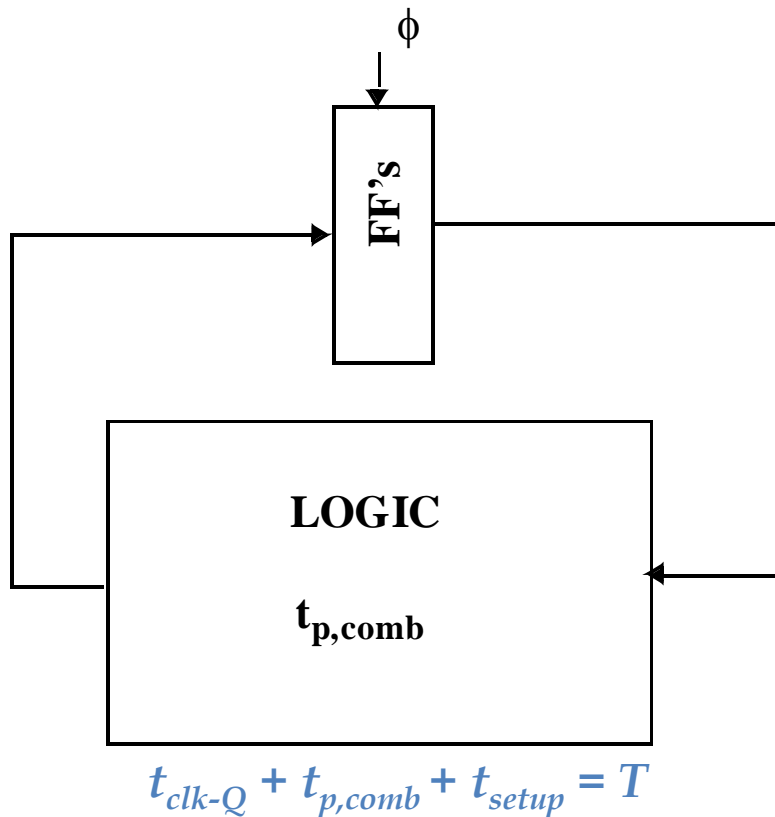


Also:

$$t_{cdreg} + t_{cdlogic} > t_{hold}$$


t_{cd} : contamination delay =
minimum delay



- Characteristic Timing:

 

Register


 


Latch



- Timing definition:
- The minimum propagation delay of the register $t_{cdregister}$
- Constraint 2 : The hold time of the register.
  
$$t_{cdregister} + t_{cdlogic} \geq t_{hold}$$









- Memory classification:
- **1 Foreground**: embedded into the logic.
- **2 Background**: large centralized memories
- Memory classification:
- **1 Static**: preserve the state as long as power is on. They are regenerative, positive feedback.
- **2 Dynamic**: large centralized memories. Store data for short period time. Temporary charge storage in MOS parasitic capacitors.





    - Register (Flip-flop): An edge-triggered storage elements. Any bistable component formed by the cross coupling of gates.
- Latch: a level sensitive device.
- Latch stores data when Clk is low. Register stores data when Clk rises.







- Latch stores data when Clk is low.

  


Register stores data when Clk rises.

  




- Latches

Positive Latch

 

Negative Latch

 




- A Positive Latches (Transparent High)
- Clk: High
- Pass the D-input to Q-output (transparent mode)
- Clk: Low
- The input data sampled on the falling edge of Clk is held stable at the output for the entire phase. (latch in hold mode)
- A Positive Latches (Transparent low)
- Clk: low
- Pass the D-input to Q-output (transparent mode)
- Clk: Low
- The input data sampled on the falling edge of Clk is held stable at the output for the entire phase. (latch in hold mode)





 - Latch-based design:
- N latch is transparent when $\phi = 0$
- P latch is transparent when $\phi = 1$







- Positive Feedback: Bistability

  



  
- Cross-coupled inverter is biased at point metastable C.



- Gain should be larger than 1 in the transition region A and B are the only stable state
- d is applied to V_{i1}




- Multiplexer (Data Selector)

 



- Multiplexer (Data Selector)
- Boolean equation

$$Z = A.\bar{S} + B.S$$

 

| S | A | B | Z |
|---|---|---|---|
| 0 | 1 | 1 | 1 |
| | | 0 | 1 |
| | 0 | 1 | 0 |
| | | 0 | 0 |
| 1 | 1 | 1 | 1 |
| | | 0 | 0 |
| | 0 | 1 | 1 |
| | | 0 | 0 |

| S | Z |
|---|---|
| 0 | A |
| 1 | B |




- Multiplexer (Data Selector)

| s | a | b | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |




- Mux-based Latches

Negative latch
(transparent when CLK= 0)

 

$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)

 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$




- Writing into a static latch

 Use the clock as a decoupling signal,
that distinguishes between the transparent and opaque states




Converting into a MUX

 

Forcing the state
(can implement as NMOS-only)




- Mux-based positive Latch

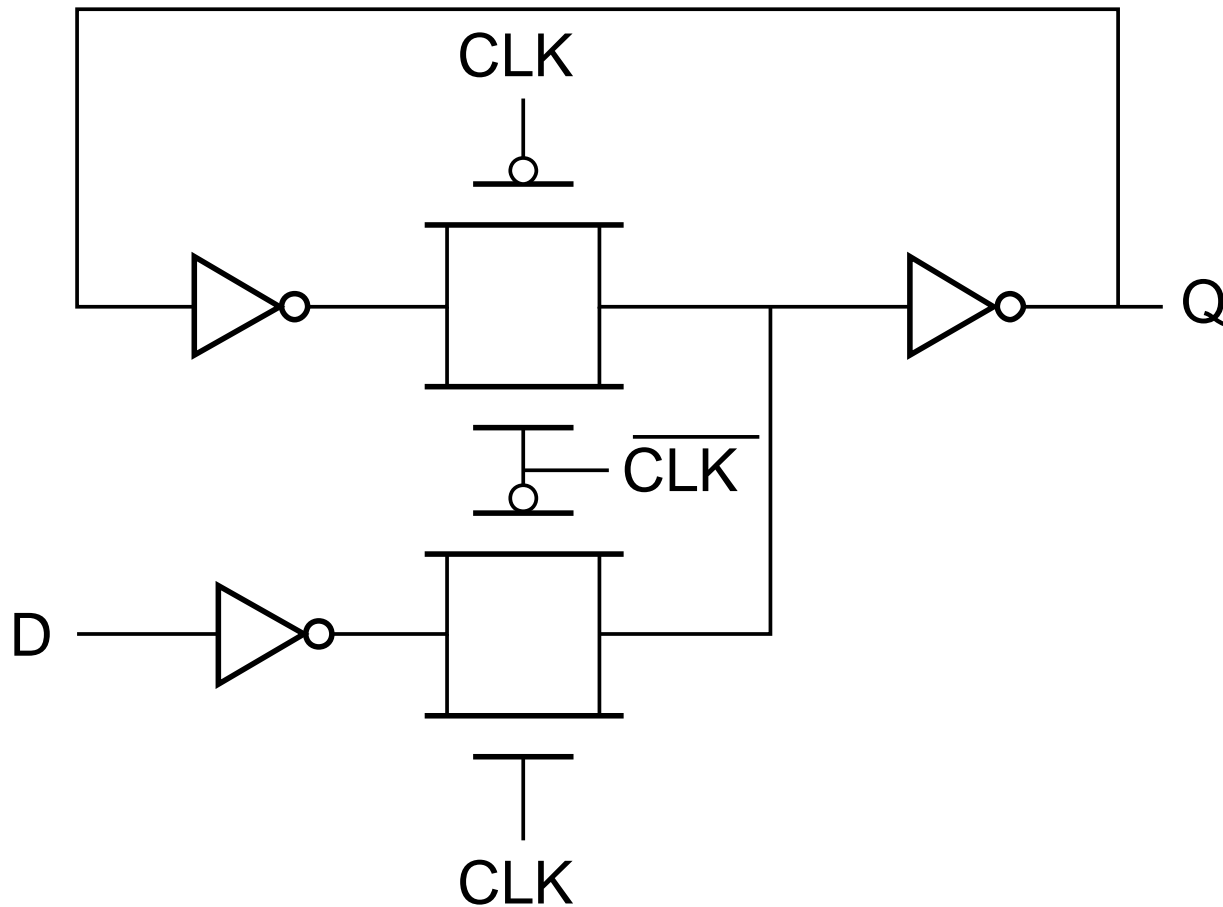




- Mux-based positive Latch operation:

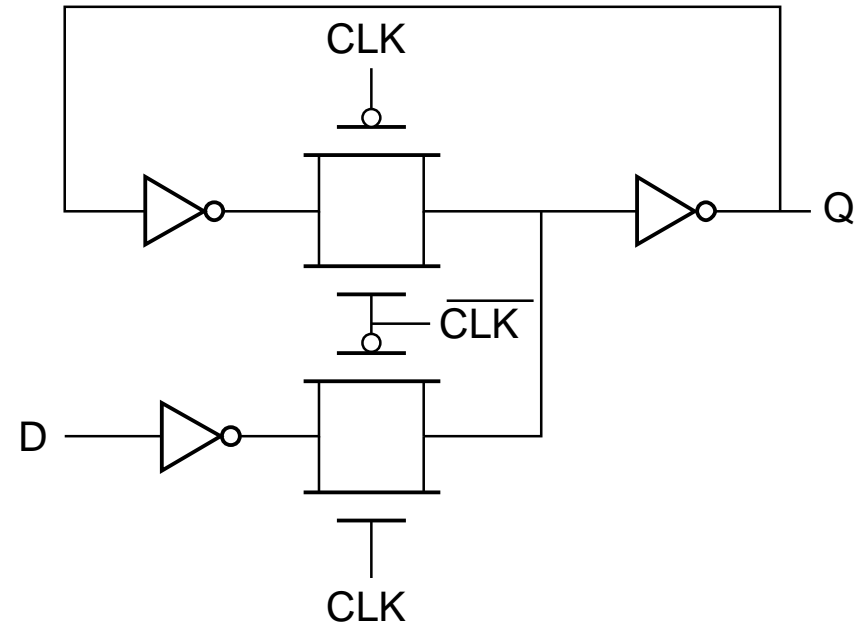
- Clk high, bottom transmission gate is ON and the latch is transparent. –D input is copied to Q output-



 
- Top transmission gate is OFF
Feedback loop is open
- It is not very efficient - It present
- the load of 4 transistors to the clock-.



- Mux-based nMOS-only Latches

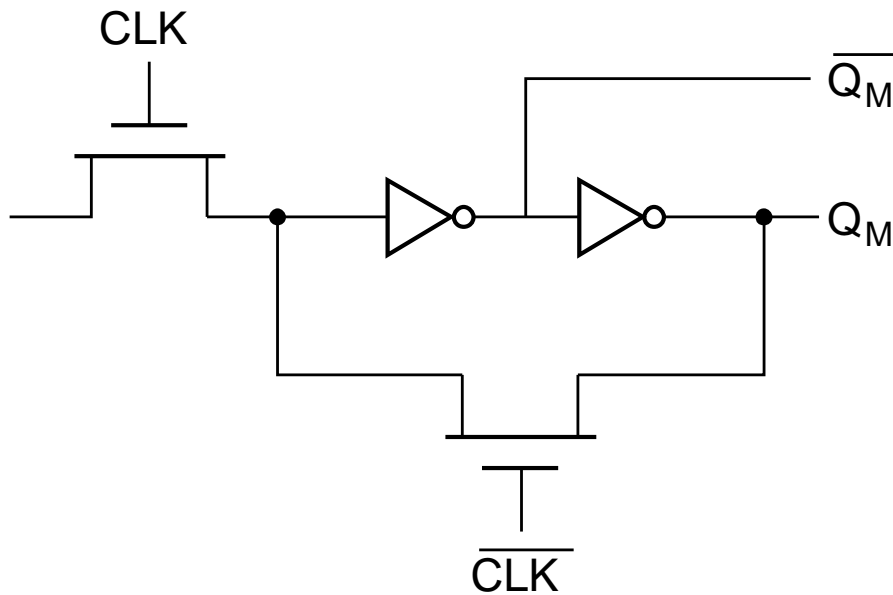



NMOS only

 

Non-overlapping clocks





 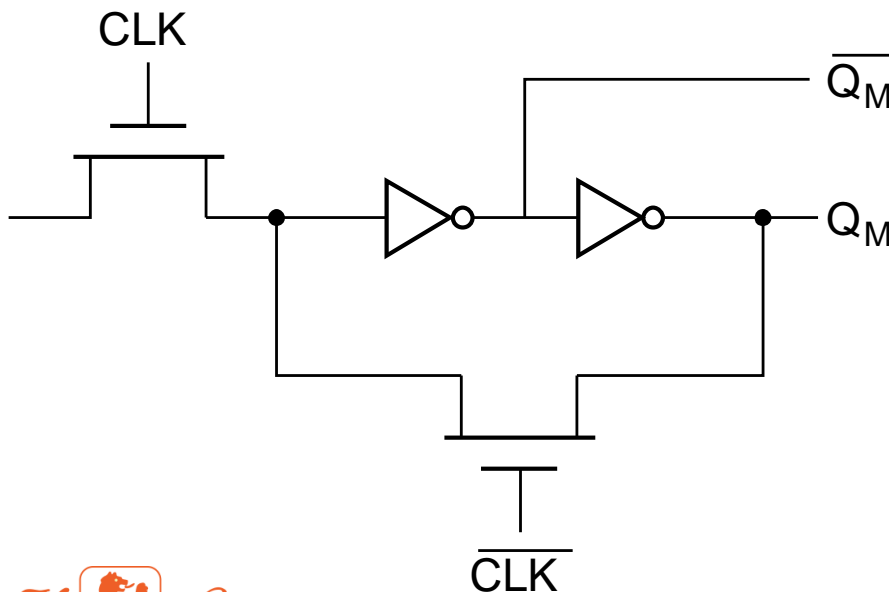- Mux-based nMOS-only Latches
- Clk: high, the latch samples the D input.
- Clk: low enables the feedback loop, and puts the latch in the hold mode.
- Disadvantages: It pass the degraded high voltages of $V_{DD} - V_{Tn}$
- To the input of the first inverter.






  - Mux-based nMOS-only Latches
- Disadvantages: It pass the degraded high voltages of
- to the input of the first inverter.
- Impact noise margin and switching performance.
- Static power dissipation because the maximum voltage equals $V_{DD} - V_{Tn}$ and the pMOS of inverter never fully OFF





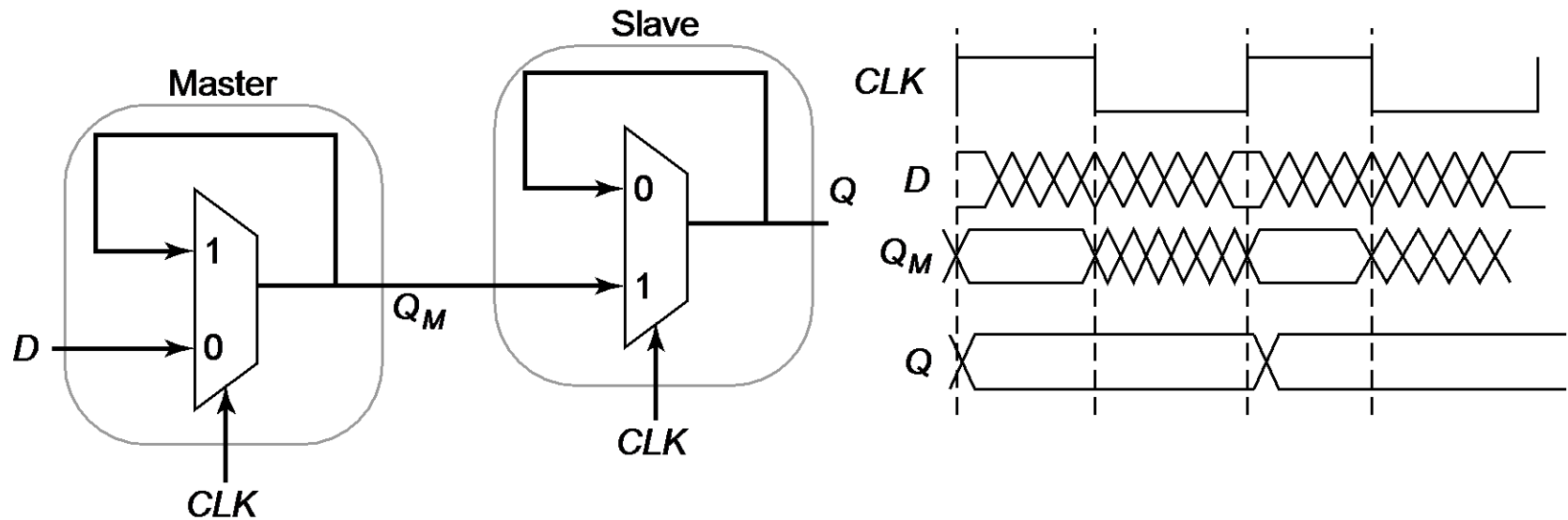- Master-slave (edge-triggered) Register:




- Cascading a negative and positive latches.


Two opposite latches trigger on edge
Also called master-slave latch pair




- Master-slave (edge-triggered) Register:

Multiplexer-based latch pair

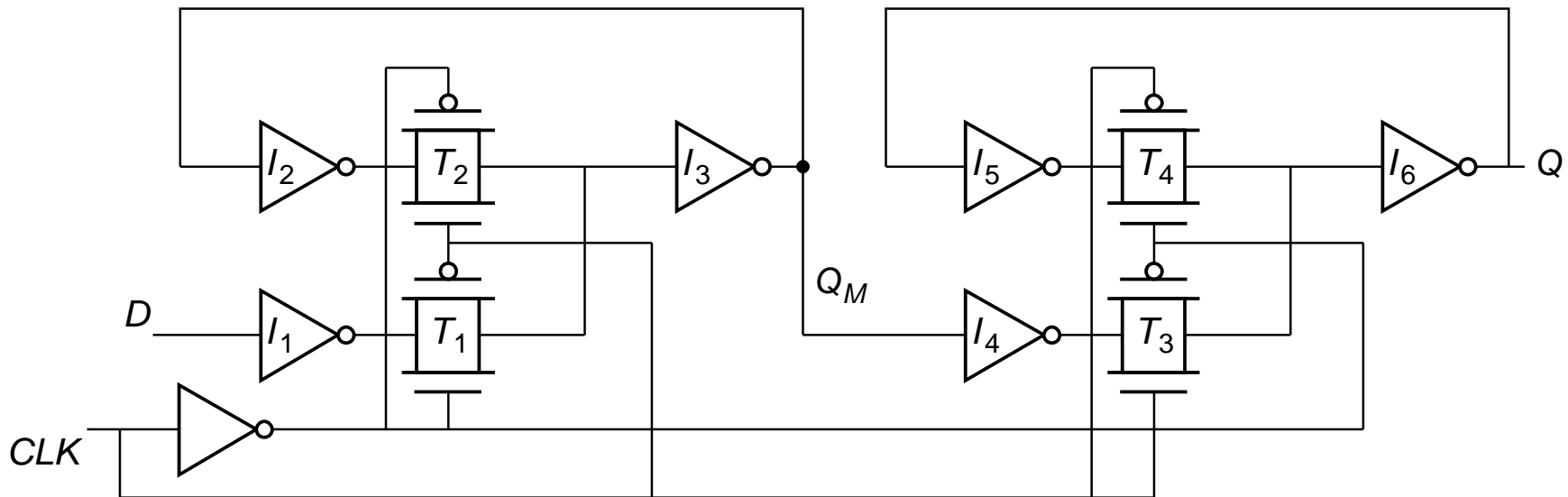

 


- Clk-Q delay:

 




- Set-up time:

 


(a) $T_{\text{setup}} = 0.21$ nsec

 


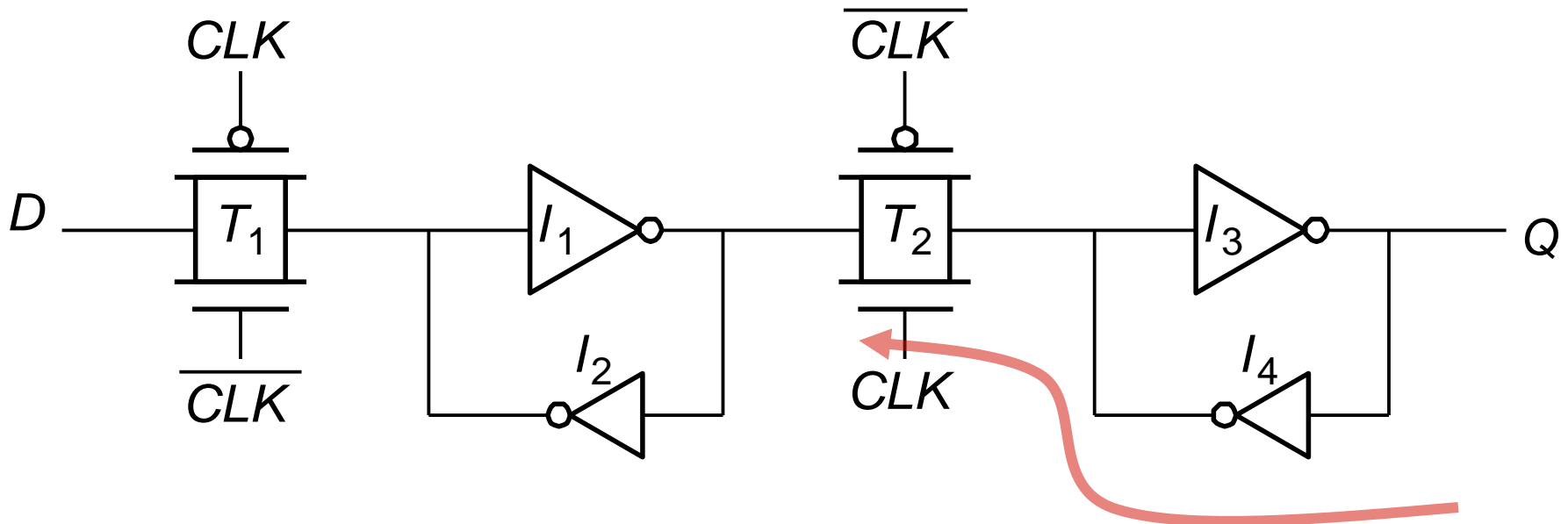(b) $T_{\text{setup}} = 0.20$ nsec




- Reduced clock load master=slave register:




 

- Avoiding clock overlap:

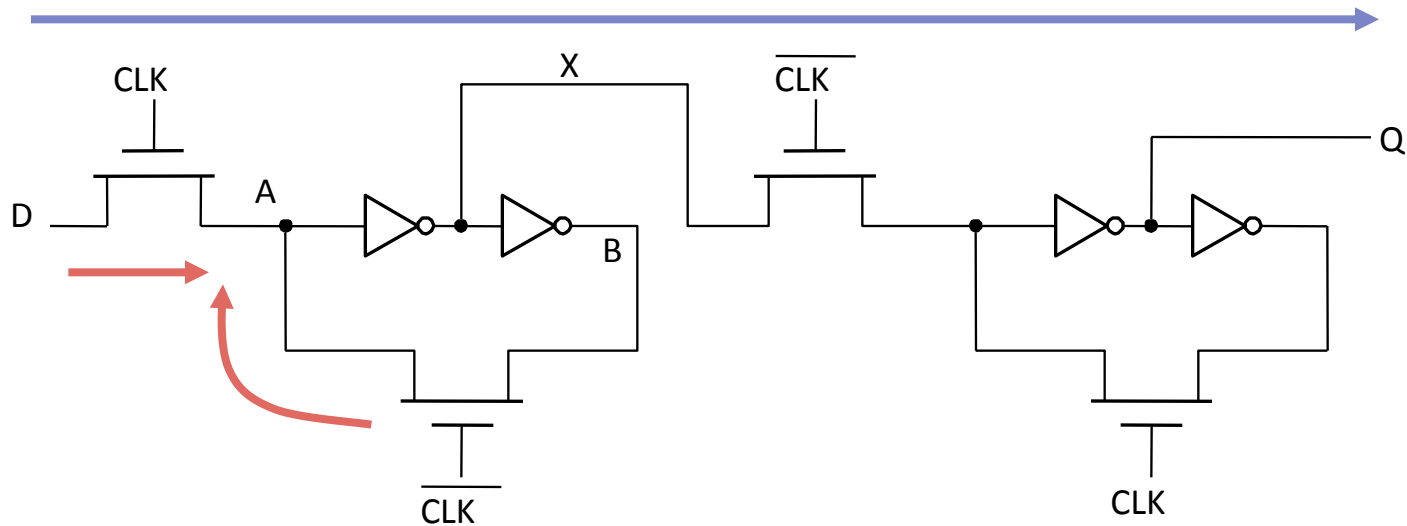

(a) Schematic diagram


 


(b) Overlapping clock pairs



- Overpowering the feedback loop
- Cross-coupled pairs:

NOR-based set-reset

  



| S | R | Q | \bar{Q} |
|-----|-----|-----|-----------|
| 0 | 0 | Q | \bar{Q} |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 |

Forbidden State



- Cross-coupled NAND


Cross-coupled NANDs

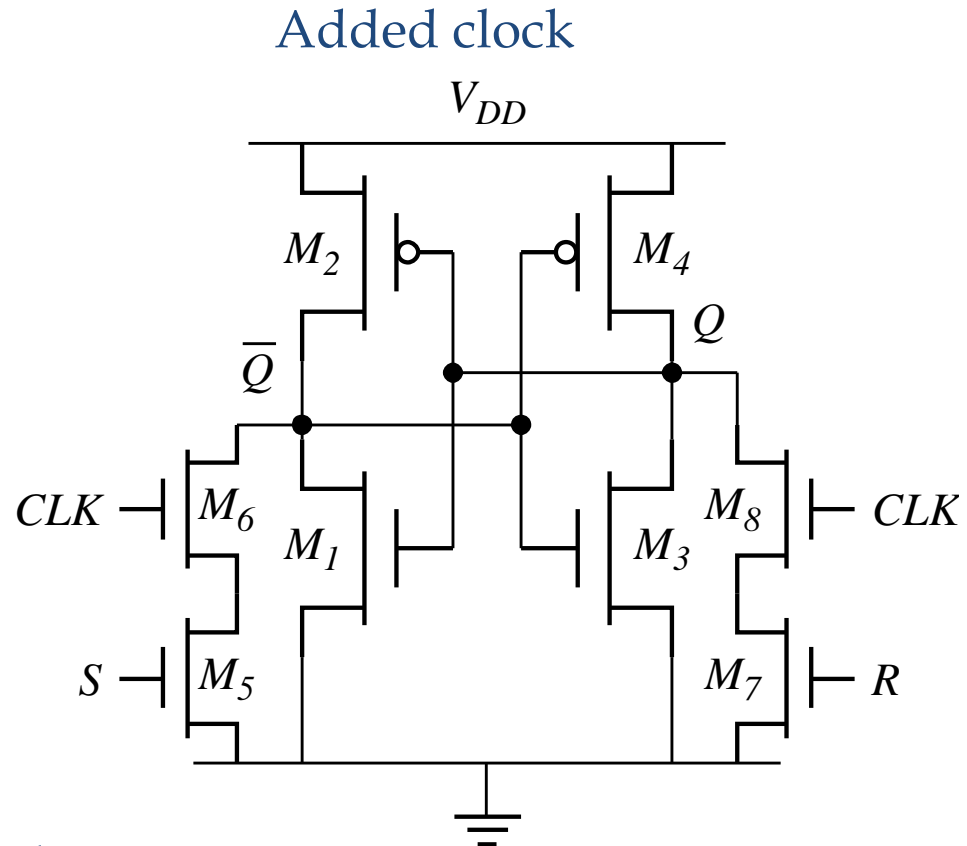 

This is not used in datapaths any more,
but is a basic building memory cell




- Sizing issues

 


(a)

 Output voltage dependence
on transistor width




(b)

Transient response

 


- Storage mechanism

Static

 



Dynamic (charge-based)

 




- A dynamic latch pseudo-static:

 


 


- A dynamic latch pseudo-static:

 






- More precise setup time:

  



 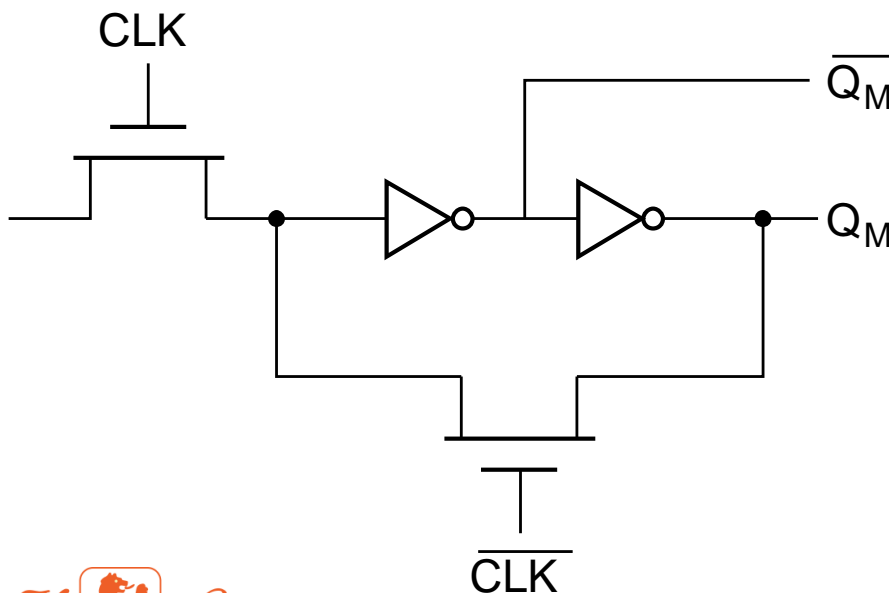
- Mux-based nMOS-only Latches
- Clk: high, the latch samples the D input.
- Clk: low enables the feedback loop, and puts the latch in the hold mode.
- Disadvantages: It pass the degraded high voltages of $V_{DD} - V_{Tn}$
- To the input of the first inverter.



 

- Setup and Hold time illustrate:

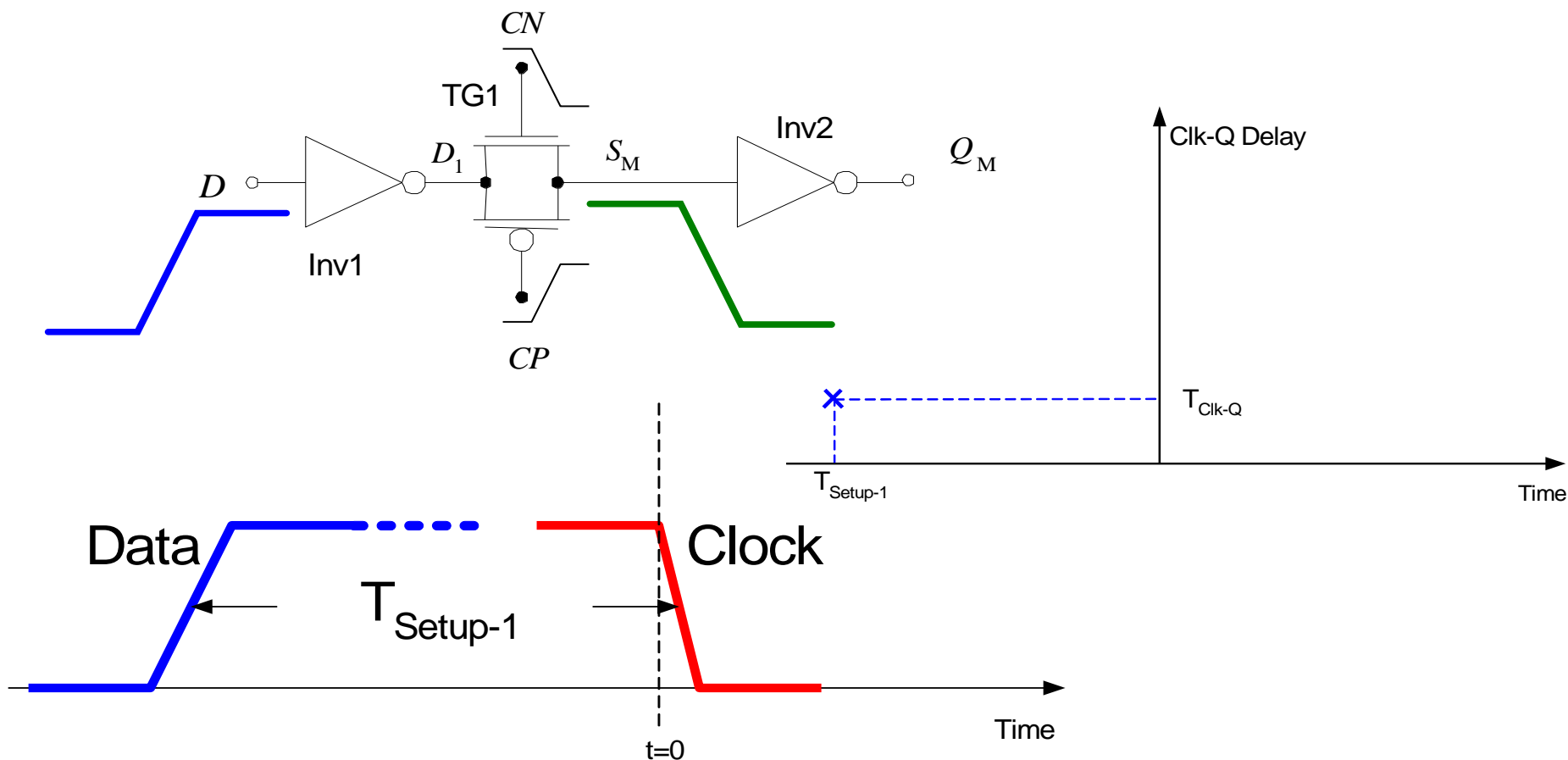
Circuit before clock arrival (Setup-1 case)






- Setup and Hold time illustrate:

 
Circuit before clock arrival (Setup-1 case)




 

- Setup and Hold time illustrate:

 
Circuit before clock arrival (Setup-1 case)



 

- Setup and Hold time illustrate:



 
Circuit before clock arrival (Setup-1 case)





- Setup and Hold time illustrate:




Hold-1 case

  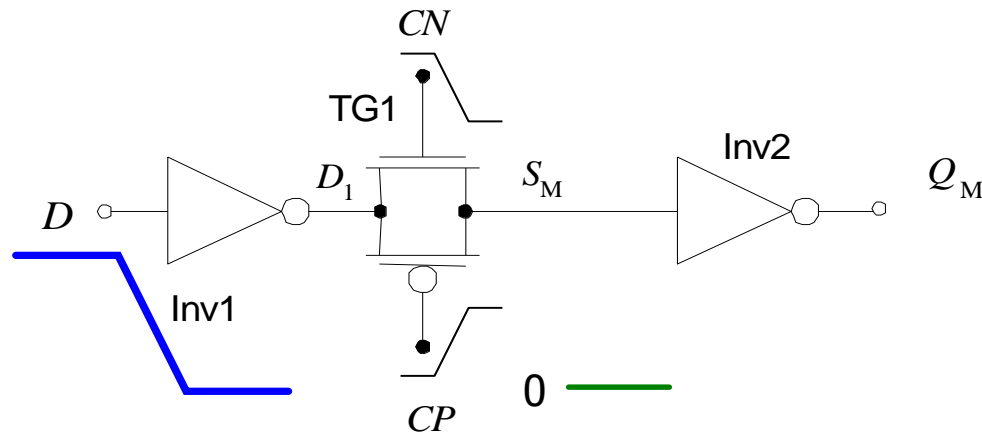



- Setup and Hold time illustrate:




Hold-1 case

  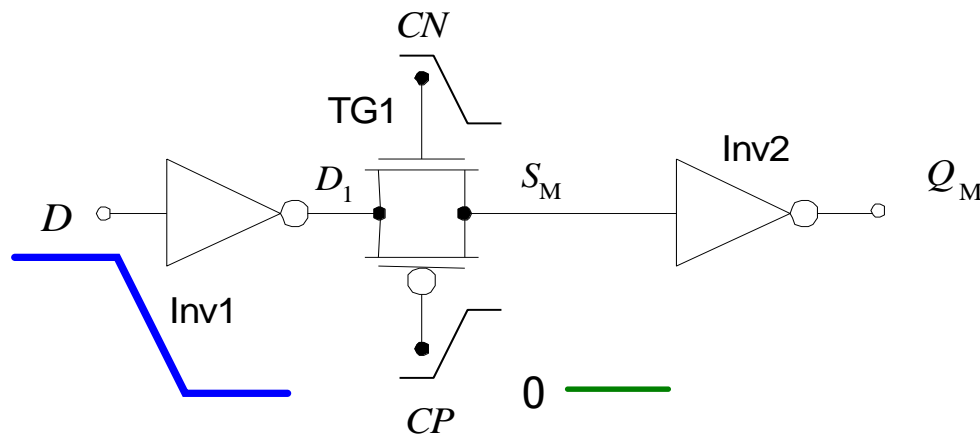




- Setup and Hold time illustrate:




Hold-1 case

  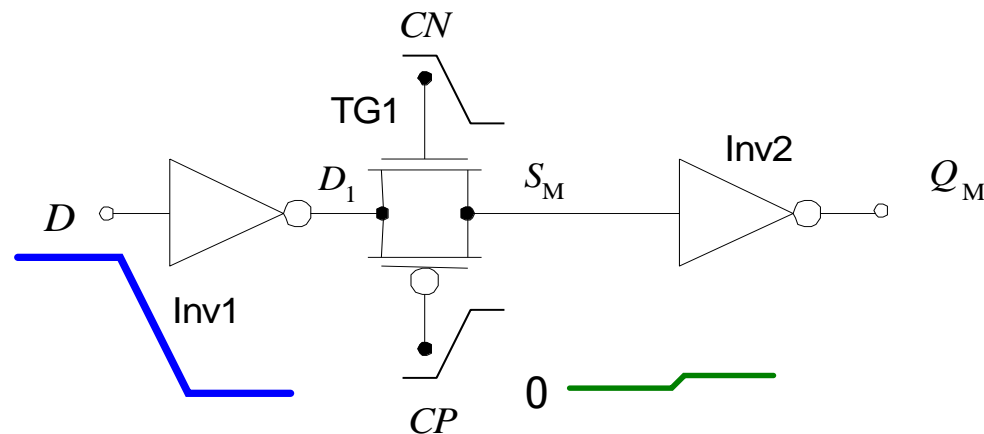

 

- Setup and Hold time illustrate:




Hold-1 case

  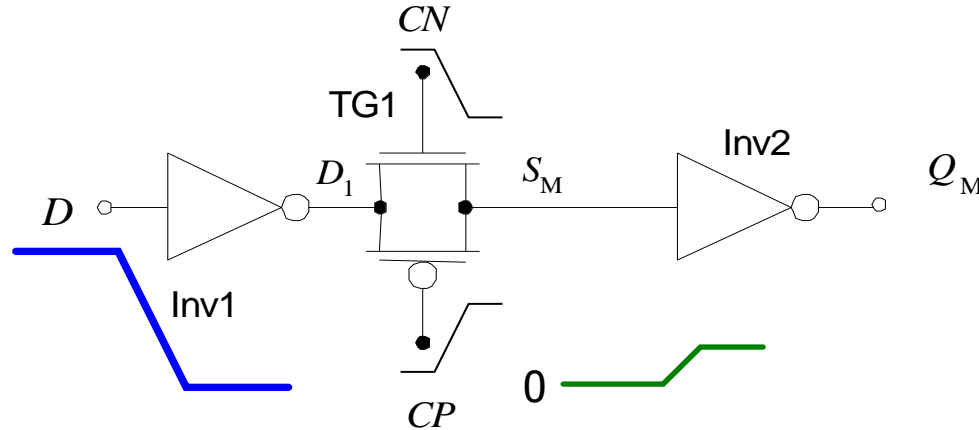




- Setup and Hold time illustrate:

Hold-1 case

  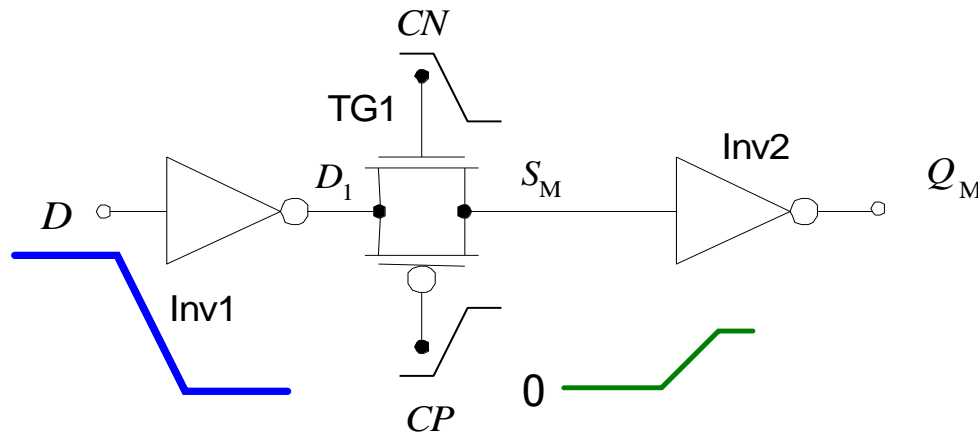





- Other latches/Registers:C2MOS

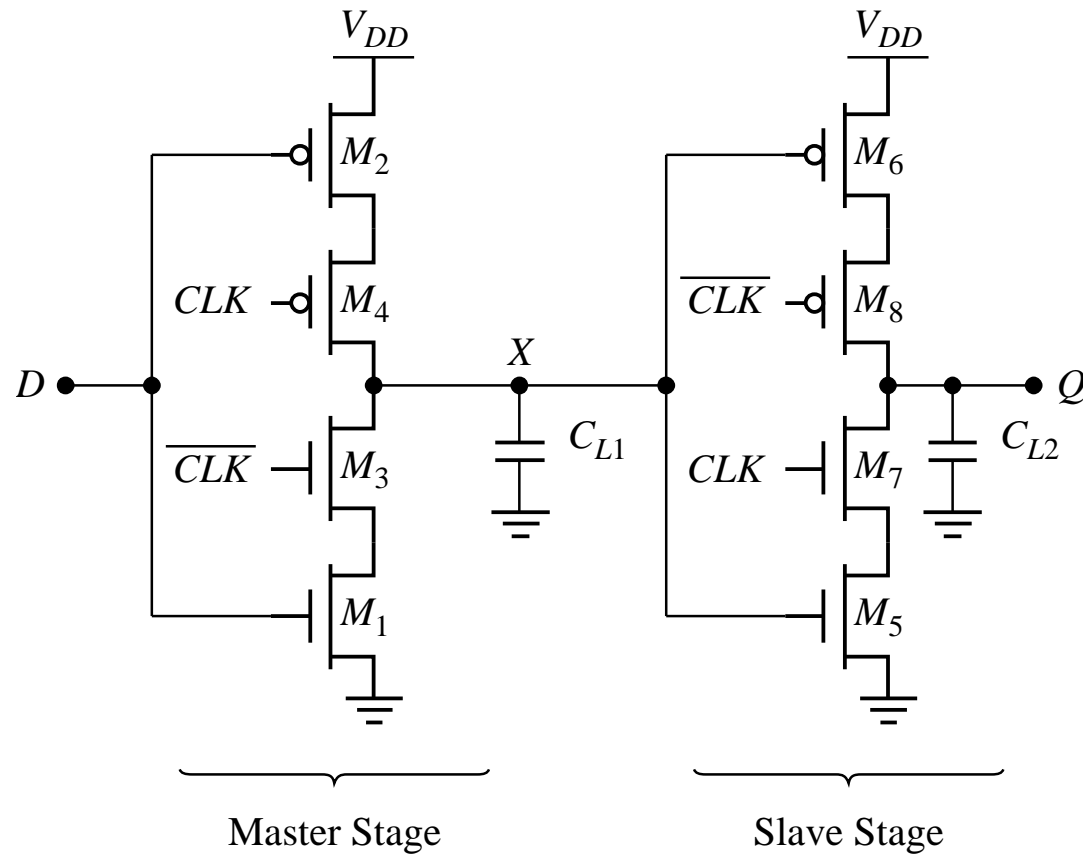

 
“Keepers” can be added to make circuit pseudo-static



- Insensitive to Clk-overlap:

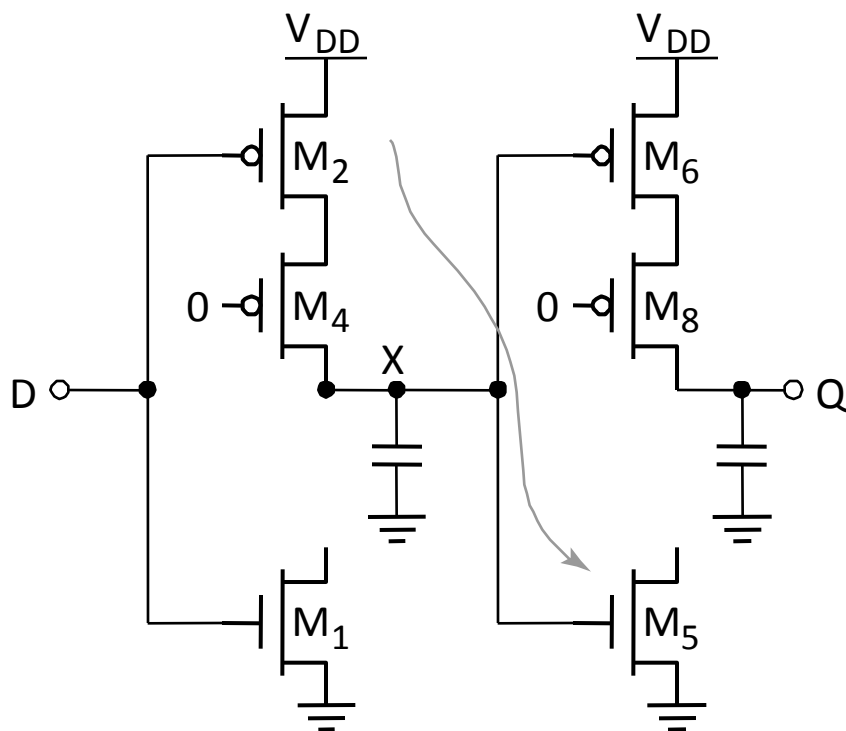


(a) (0-0) overlap

 


(b) (1-1) overlap



• Pipelining:

 

Reference

 


Pipelined

| Clock Period | Adder | Absolute Value | Logarithm |
|--------------|-------------|----------------|---------------------|
| 1 | $a_1 + b_1$ | | |
| 2 | $a_2 + b_2$ | $ a_1 + b_1 $ | |
| 3 | $a_3 + b_3$ | $ a_2 + b_2 $ | $\log(a_1 + b_1)$ |
| 4 | $a_4 + b_4$ | $ a_3 + b_3 $ | $\log(a_2 + b_2)$ |
| 5 | $a_5 + b_5$ | $ a_4 + b_4 $ | $\log(a_3 + b_3)$ |




- Other latches/registers: TSPC

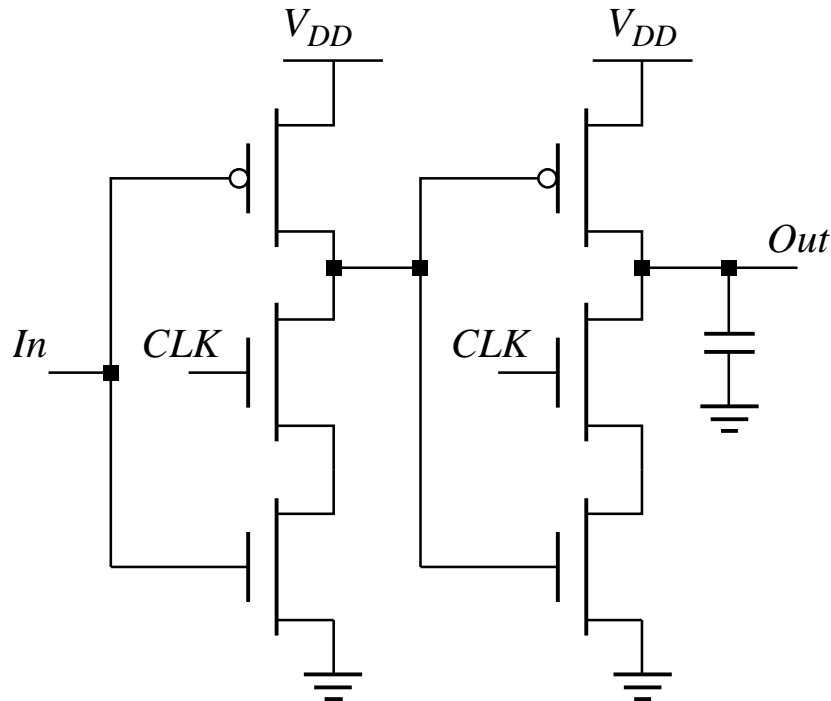

Positive latch

(transparent when CLK= 1)


 


Negative latch

(transparent when CLK= 0)



- Including logic in TSPC

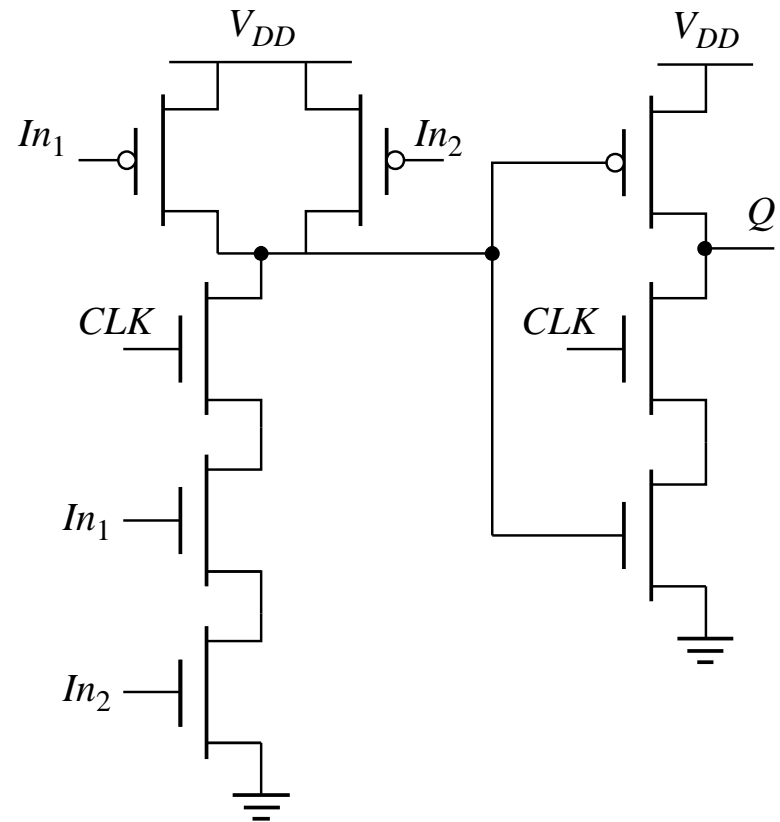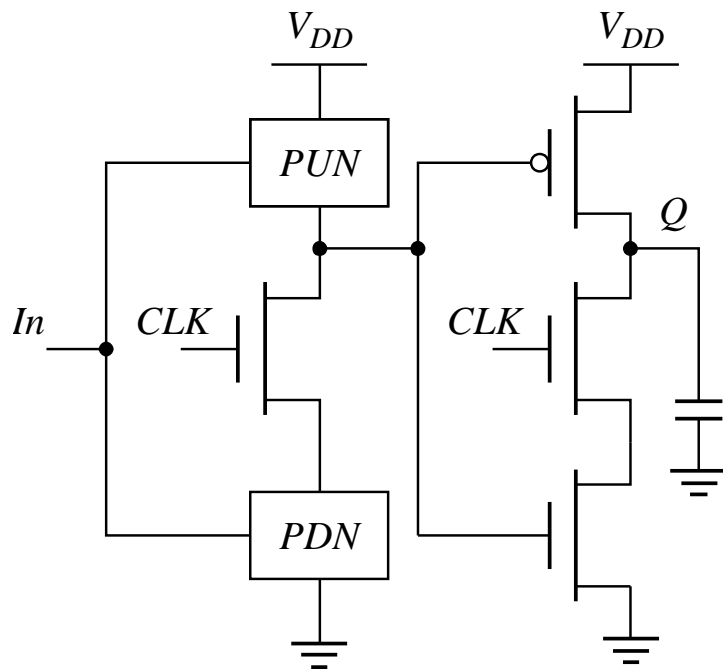


Example: logic inside the latch

AND latch



- TSPC register

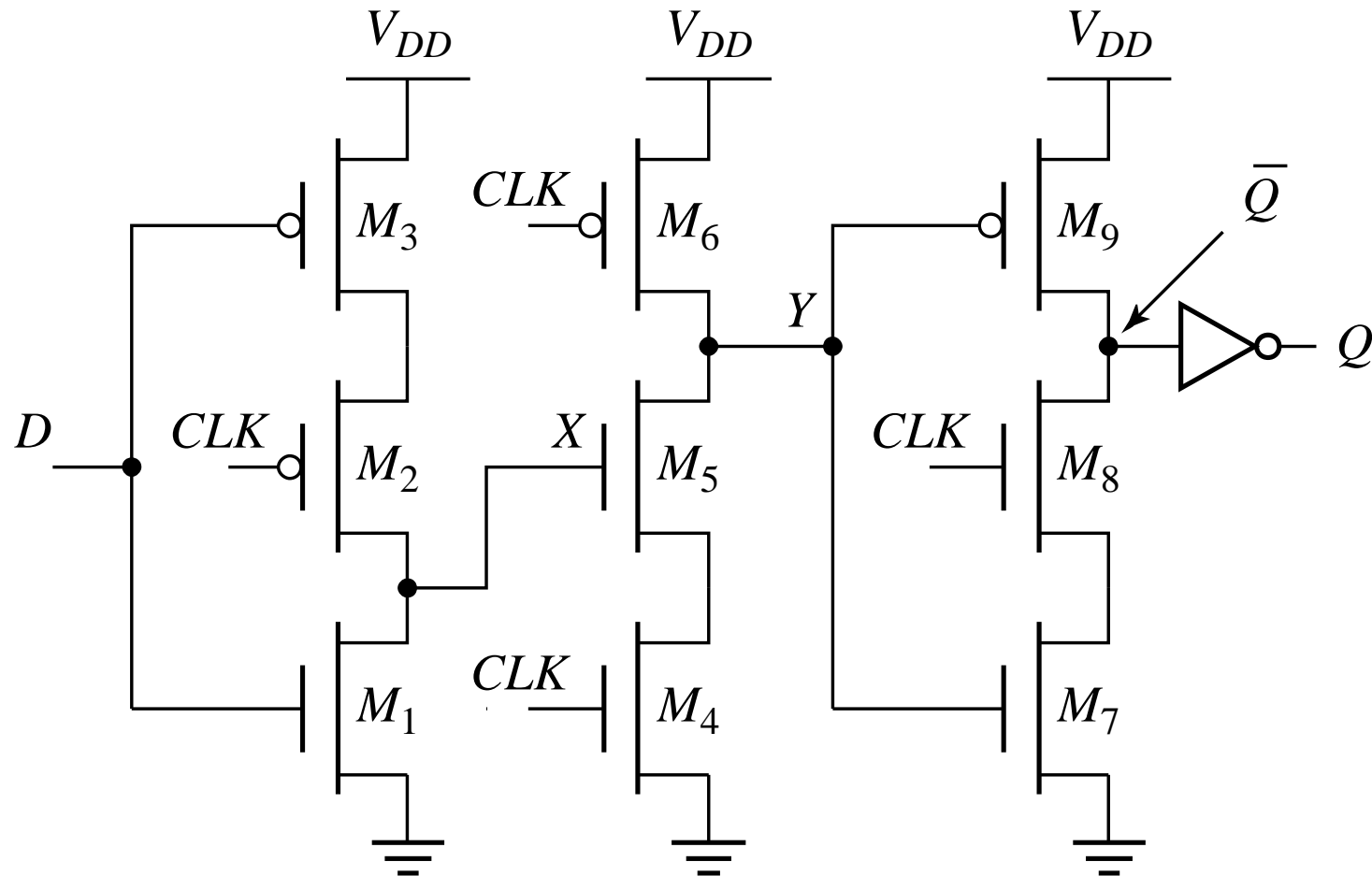





- Pulse-triggered latches, An alternative approach


Ways to design an edge-triggered sequential cell:

Master-Slave Latches

 


Pulse-Triggered Latch

 


 


- Pulse latches

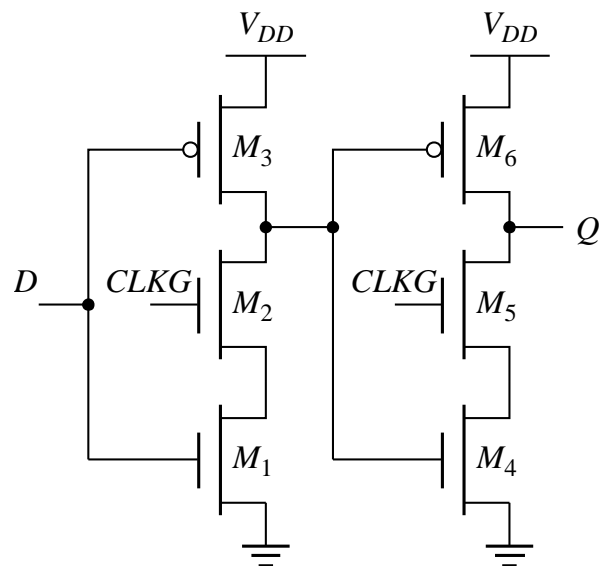

(a) register

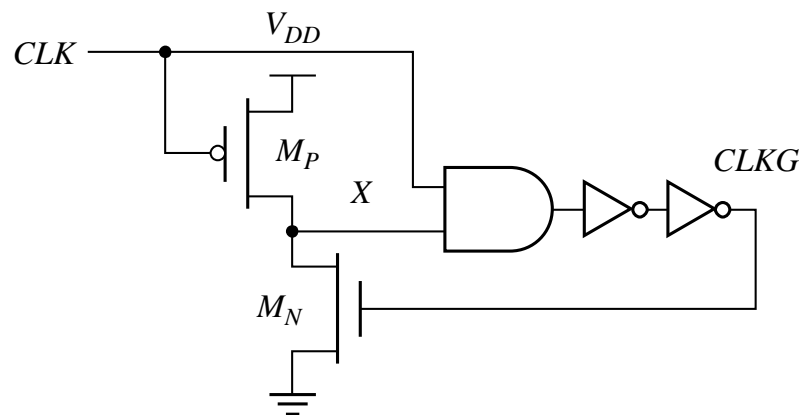

(b) glitch generation

 


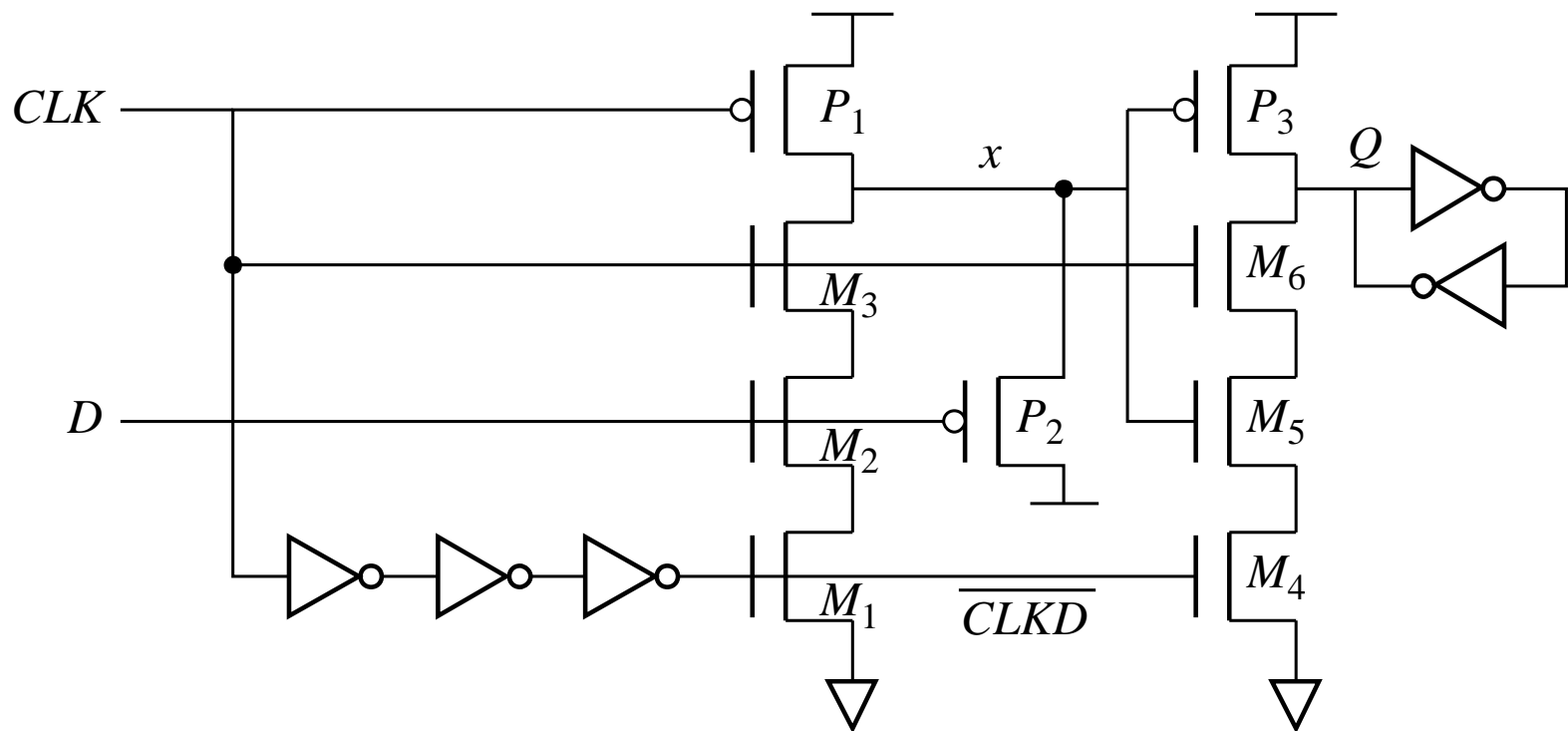(c) glitch clock




- Pulse latches

Hybrid Latch – Flip-flop (HLFF), AMD K-6 and K-7 :








- Hybrid Latch-FF timing

 




- Latch-based pipeline

  


 

 - Non-bistable sequential circuits Schmitt trigger




 - VTC with hysteresis
- Restores signal slopes






 - Noise suppression using Schmitt trigger






- CMOS Schmitt trigger

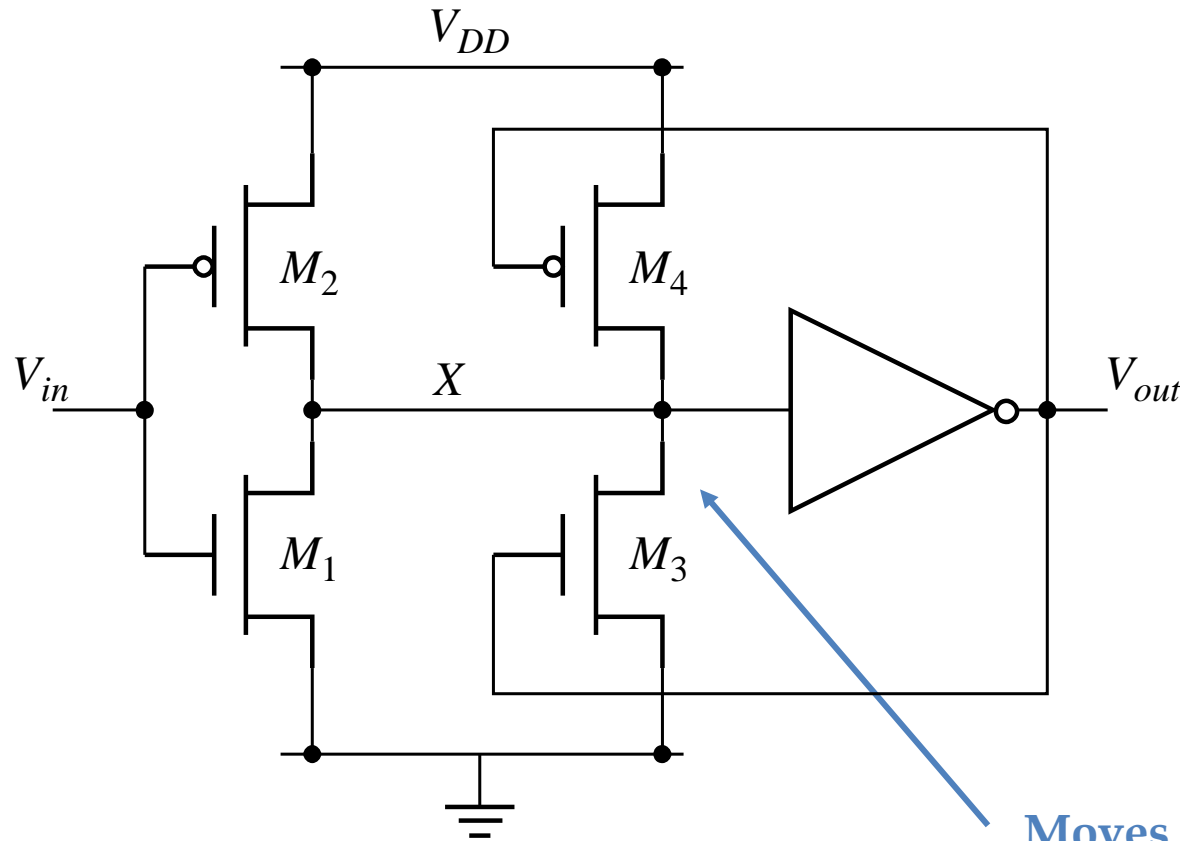


Moves switching threshold
of the first inverter



- Schmitt trigger simulated VTC

 

 Voltage-transfer characteristics with hysteresis.



The effect of varying the ratio of the PMOS device M_4 . The width is $k \cdot 0.5 \mu\text{m}$.