

**EE 538B CMOS RF IC DESIGN**

Midterm Examination No. 1: April 24, 2002

Time Allowed: 110 Minutes

Student Name: \_\_\_\_\_

UW Student ID #: \_\_\_\_\_

*Solutions*

*123-45-6789*


$$\left. \begin{array}{l} H_i = 100 \\ L_o = 70 \\ \mu = 86.5 \\ \sigma = 8.4 \end{array} \right\}$$

*You are allowed one sheet of notes. Write legibly. Show all work. State assumptions.*

Problem #	Points Possible	Points
1	20	20
2	10	10
3	25	25
4	25	25
5	20	20

*100*

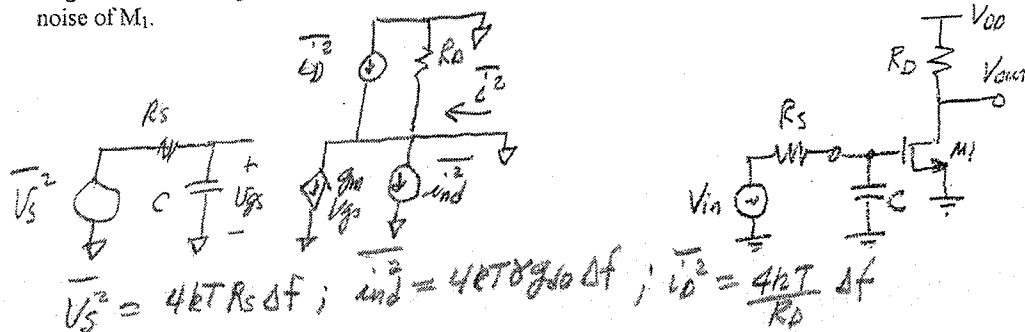1. (20 points) Find the noise factor of the circuit shown with respect to the source resistance  $R_S$ . Neglect channel length modulation effects and all parasitic capacitors. Consider only drain current noise of  $M_1$ .



The three noise sources are uncorrelated:

- (i) Consider  $\overline{i_D^2}$ :  $\overline{i_1^2} = \overline{i_D^2} = \frac{4kT}{R_D} \Delta f$   
 (ii) Consider  $\overline{i_{ind}^2}$ :  $\overline{i_2^2} = \overline{i_{ind}^2} = 4kT\gamma g_{m0} \Delta f$   
 (iii) Consider  $\overline{V_S^2}$ :

$$V_{GS} = \frac{1/sC}{R_S + 1/sC} \overline{V_S} = \frac{1}{sR_SC + 1} \overline{V_S}$$

$$\Rightarrow \overline{V_{GS}^2} = \frac{1}{(\omega R_SC)^2 + 1} \overline{V_S^2}$$

$$\overline{i_3^2} = g_m^2 \overline{V_{GS}^2} = \frac{g_m^2}{(\omega R_SC)^2 + 1} \overline{V_S^2}$$


$$\text{Finally, } F = \frac{\overline{i_1^2} + \overline{i_2^2} + \overline{i_3^2}}{\overline{i_1^2}}$$

$$= 1 + \frac{\frac{4kT}{R_D} \Delta f + 4kT\gamma g_{m0} \Delta f + \frac{g_m^2}{(\omega R_SC)^2 + 1} \frac{4kTR_S \Delta f}{g_m^2}}{\frac{4kT}{R_D} \Delta f}$$

$$\therefore F = 1 + \frac{[1 + (\omega R_SC)^2]}{g_m^2 R_D R_S} + \frac{[1 + (\omega R_SC)^2] \gamma g_{m0}}{g_m^2 R_S}$$

Note that  
 F is increased  
 due to the  
 presence of C  
 as expected.)

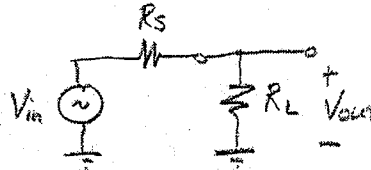
2. (10 points) With respect to a source resistance  $R_S$ :
- (a) What value of  $R_L$  maximizes power transfer?



We obtain maximum power transfer when the load impedance is the complex conjugate of the source impedance; i.e.,  $Z_L = Z_S^*$ . In this case,  $R_L = R_S$ .

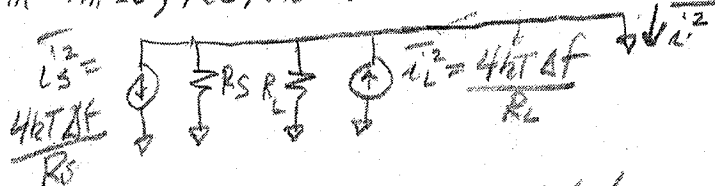- (b) What value of  $R_L$  minimizes the noise factor  $F$ ?

With  $V_{in} = 0$ , redraw circuit with noise:



The noise sources are uncorrelated.


Hence,  $\overline{i^2} = \overline{i_S^2} + \overline{i_L^2}$

$$\therefore F = \frac{\overline{i^2}}{\overline{i_S^2}} = 1 + \frac{\frac{4kT\Delta F}{R_L}}{\frac{4kT\Delta F}{R_S}} = 1 + \frac{R_S}{R_L}$$


Clearly  $F = F_{min} = 1$  when  $R_L = \infty$ .

This simple example illustrates the key point that optimum gain match and optimum noise match are different.

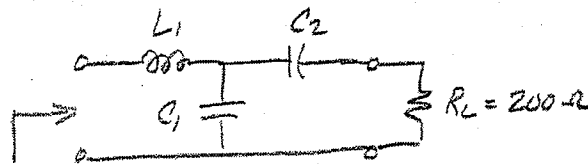3. (25 points) With  $Q=10$ , the matching circuit below is used to convert  $R_L = 200\Omega$  to  $R_{IN} = 50\Omega$  at  $f_0 = 5.6\text{GHz}$ . Determine the required component values.



(This is a band pass matching network)

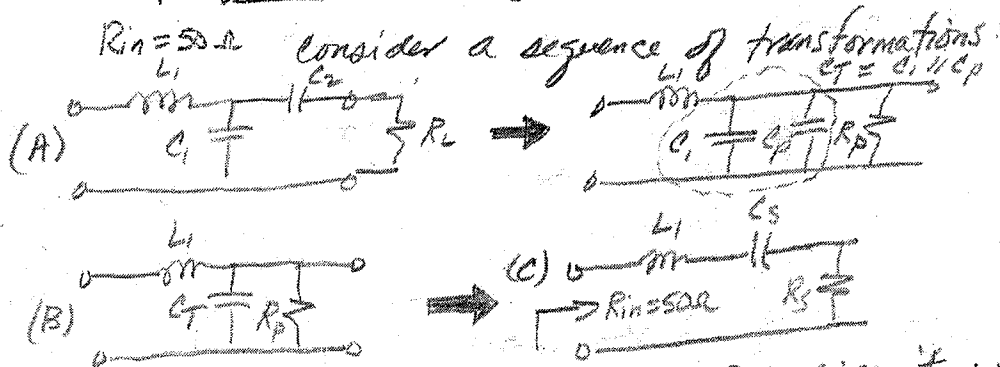

- The final circuit is pure series RLC circuit with:


$$Q=10; R_S = R_{in} = 50\Omega; f_0 = 5.6\text{GHz}$$

For (C):  $Q=10 = \frac{\omega_0 L_1}{R_S} \Rightarrow L_1 = \frac{Q R_S}{\omega_0} = \boxed{14.2\text{ nH}}$   $\leftarrow L_1$

$$Q=10 = \frac{1}{\omega_0 R_S C_S} \Rightarrow C_S = \frac{1}{Q R_S \omega_0} = \boxed{56.8\text{ fF}}$$

For (B):  $R_P = R_S (Q^2 + 1) = 50 (101) = \boxed{5050\Omega}$
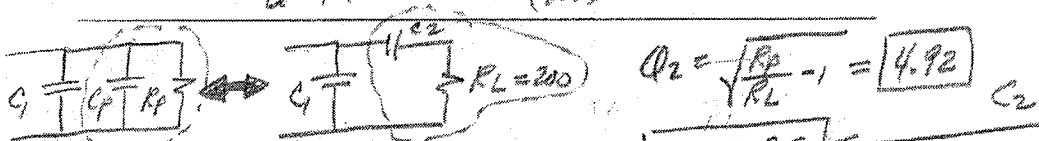
$$C_T = \frac{C_S Q^2}{Q^2 + 1} = \frac{(56.8\text{ fF})(100)}{(101)} = \boxed{56.3\text{ fF}}$$



$$Q_2 = \frac{1}{\omega_0 R_L C_2} \Rightarrow C_2 = \frac{1}{Q_2 \omega_0 R_L} = \boxed{28.9\text{ fF}}$$


$$Q_2 = \omega_0 R_P C_P \Rightarrow C_P = \frac{Q_2}{\omega_0 R_P} = \boxed{27.7\text{ fF}}$$

Finally,  $C_1 = C_T - C_P = \boxed{28.6\text{ fF}}$   $\leftarrow C_1$

This means  $r_{ds1} = r_{ds2} = \infty$ .

4. (25 points) Find an expression for the noise factor of the circuit below with respect to the source resistance  $R_S$ . Neglect channel length modulation and all parasitic capacitors; also, neglect induced gate current noise. Assume that the DC bias voltage across  $L$  is zero.

The noise sources are uncorrelated:

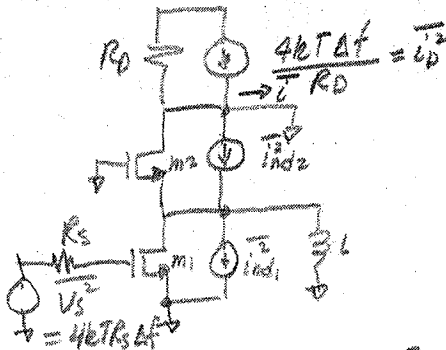


$$\overline{i_{n,R_S}^2} = \frac{4kTR_S \Delta f}{V_S^2} \cdot g_{m1}^2 \cdot \left[ \frac{g_{m2}^2 (WL)^2}{1 + g_{m2}^2 (WL)^2} \right]$$

$$\overline{i_{n,M1}^2} = 4kT \gamma_1 g_{d01} \Delta f \cdot \left[ \frac{g_{m2}^2 (WL)^2}{1 + g_{m2}^2 (WL)^2} \right]$$

Note: Current divider between  $L$  and  $M_2$ .
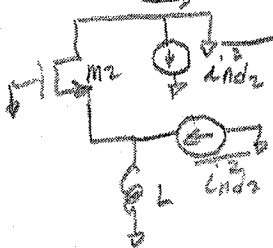
$$\overline{i_{n,R_D}^2} = \frac{4kT \Delta f}{R_D}$$



Note: When we use this equivalent circuit, the components in it are obviously correlated. Hence,

$$\overline{i_{n,M2}^2} = 4kT \gamma_2 g_{d02} \Delta f \left| \frac{\frac{SL}{g_{m2}} - 1}{1 + g_{m2}^2 (WL)^2} \right|^2$$


$$= 4kT \gamma_2 g_{d02} \Delta f \left[ \frac{1}{1 + g_{m2}^2 (WL)^2} \right]$$

Finally,


$$F = 1 + \frac{\gamma_1 g_{d01}}{g_{m1}^2 R_S} + \frac{1}{g_{m1}^2 R_S R_D} + \frac{1 + \gamma_2 g_{d02} R_D}{g_{m1}^2 g_{m2}^2 R_S R_D (WL)^2}$$

Note:  $L$  decreases  $F$ ; in Hw  $C$  increased  $F$ ;

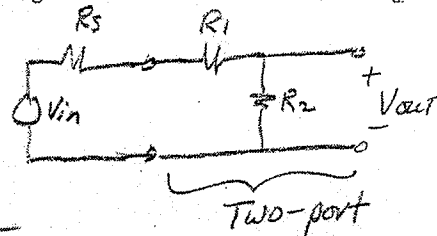
5. (20 points) Determine expressions for the equivalent two-port input noise voltage and current power sources for the two-port network shown assuming it is driven from a source resistor  $R_s$ .



Consider the two port

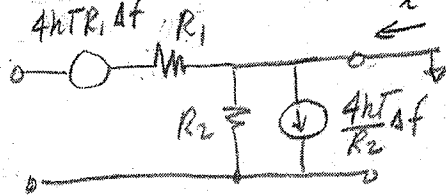

Compute  $\bar{i}$  for both circuits:

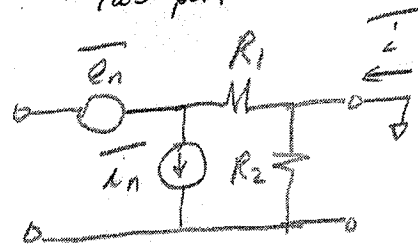

$R_1$  and  $R_2$   
assumed noise  
free in this case.

(a) Short Input:

$$\bar{i}^2 = \frac{4kTR_1\Delta f}{R_1^2} + \frac{4kT\Delta f}{R_2}$$

$$= 4kT\Delta f \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

(a) Short input:

$$\bar{i}^2 = \frac{e_n^2}{R_1^2}$$


Hence,  $e_n^2 = R_1^2 \bar{i}^2 = \boxed{4kT\Delta f R_1^2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)}$  ←  $\bar{e}_n^2$

(b) Open input:

$$\bar{i}^2 = \frac{4kT\Delta f}{R_2}$$

$$\bar{i}^2 = \bar{i}_n^2$$

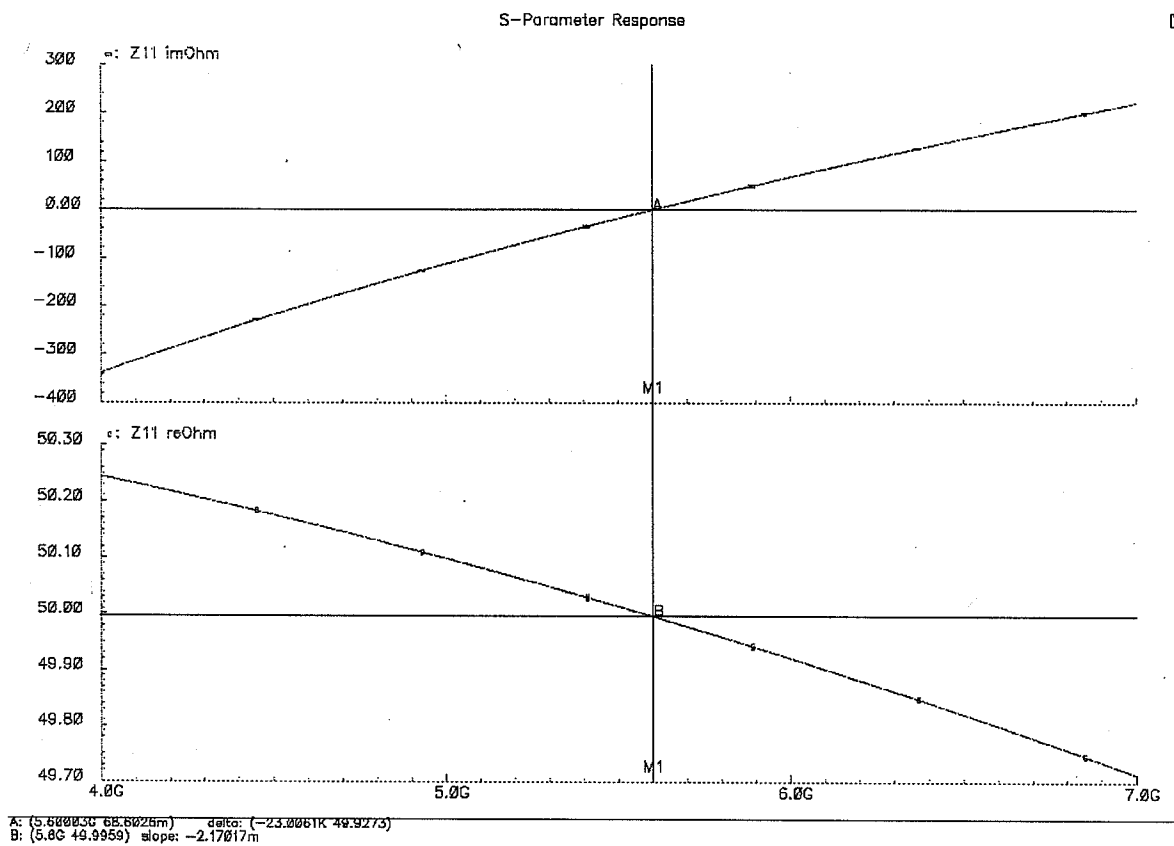
Hence,  $\bar{i}_n^2 = \boxed{\frac{4kT\Delta f}{R_2}}$  ←  $\bar{i}_n^2$



Prob-3  $Z_{in}@5.6\text{GHz} = 50 \text{ ohm}$

ad335a maghem1\_prob3 schematic : Apr 29 21:58:22 2002

# S-Parameter Response

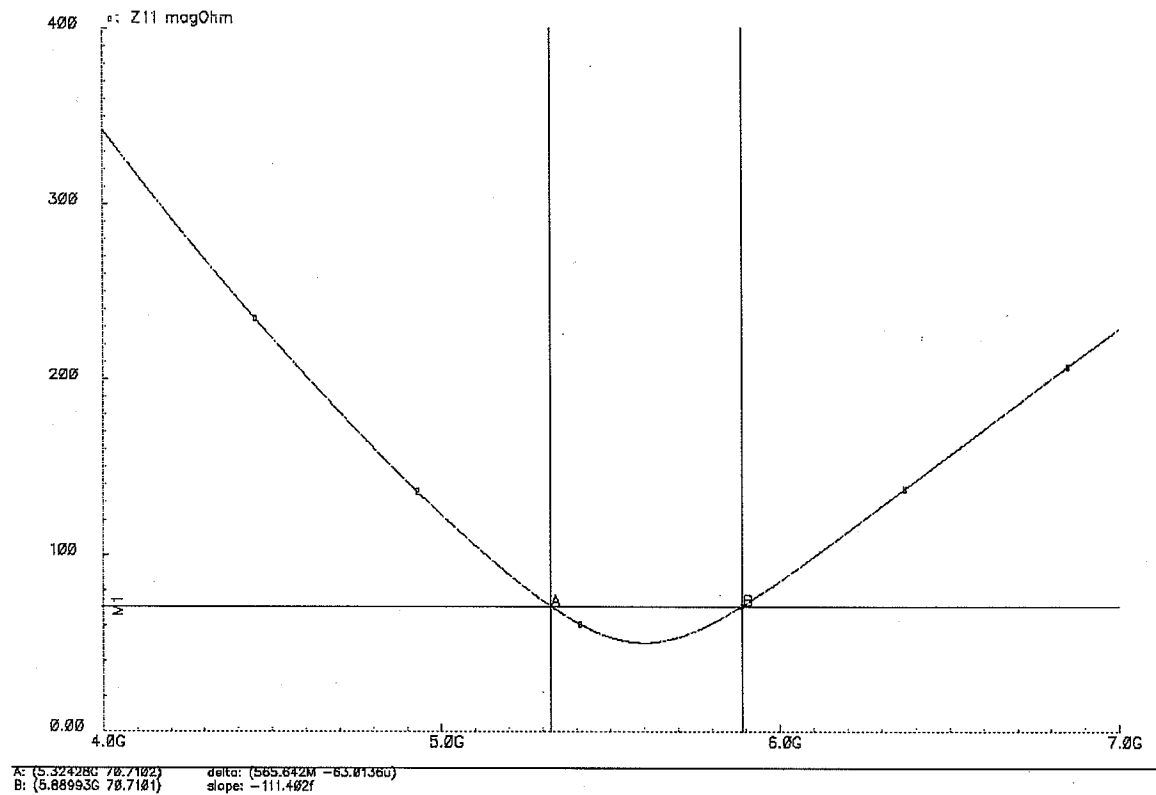

Prob-3 BW  $\cong$  560MHz