 


Elmore

Lecture 17

Advanced Digital IC Design



Khosrow Ghadiri



- Elmore Delay Approximation
- Rational:
- Delay Calculation.
- Static Timing Analysis.
- Logic Synthesis



- Output response:
- Network structure & state
 - Natural response (zero-input response)- (Homogenous,-Math-)
- Input waveform & zero states
 - Forced response (zero-state response) (Particular,-Math-)
- Linear circuits :

$$v_{Total}(t) = v_{Natural}(t) + v_{Forced}(t)$$



- Basic Waveforms
- Impulse input

$$\delta(t) = \begin{cases} 0 & t = 0 \\ 1 & \text{otherwise} \end{cases}$$

- Step input

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$

- Pulse input

$$P_T(t) = \frac{1}{T} \left[u\left(t + \frac{T}{2}\right) - u\left(t - \frac{T}{2}\right) \right]$$


- Sinusoidal input

$$x(t) = A \sin(\omega t + \theta)$$

- Apply simple input waveforms to insight of the network design.




- Analysis of Simple RC Circuit

 


- Loop equation:

$$Ri(t) + v(t) = v_{in}(t)$$
 
$$i(t) = \frac{d(Cv(t))}{dt} = C \frac{dv(t)}{dt}$$



- Analysis of Simple RC Circuit

 

$$RC \frac{dv(t)}{dt} + v(t) = v_{in}(t)$$

- First order linear differential equation with constant coefficient

$v_{in}(t)$ = Input Signal

$v(t)$ = State Variable



- Analysis of Simple RC Circuit:

- Zero input response:

- $$RC \frac{dv(t)}{dt} + v(t) = 0$$

- Natural response.

$$\frac{1}{v(t)} \frac{dv(t)}{dt} = -\frac{1}{RC}$$

$$v_{Natural}(t) = Ce^{-t/RC}$$

- Step input response:

$$RC \frac{dv(t)}{dt} + v(t) = v_0 u(t) \quad v_{Forced}(t) = v_0 u(t) \quad \Rightarrow \quad v(t) = Ce^{-t/RC} + v_0 u(t)$$

- Match initial state:

$$v(t) = 0 \quad \Rightarrow \quad C + v_0 u(t) = 0$$

- Output response for step input:


$$v(t) = v_0 (1 - e^{-t/RC}) u(t)$$

$$v(t) = 0.9v_0 \Rightarrow t = 2.3RC$$

$$v(t) = 0.5v_0 \Rightarrow t = 0.69RC$$



 - The resulting voltage $v_{out}(t)$ across the capacitor over time is shown for the normalized voltage of 1V.





- The Elmore delay:


$$\tau_D = RC$$

- Sink Delay :


$$\tau_d = RC$$

- Driver resistance: R
- Total interconnected capacitance+ loading capacitance: C
- 50% delay under step input :

$$\tau = 0.69RC$$

 


- Find the Time constant at all nodes.

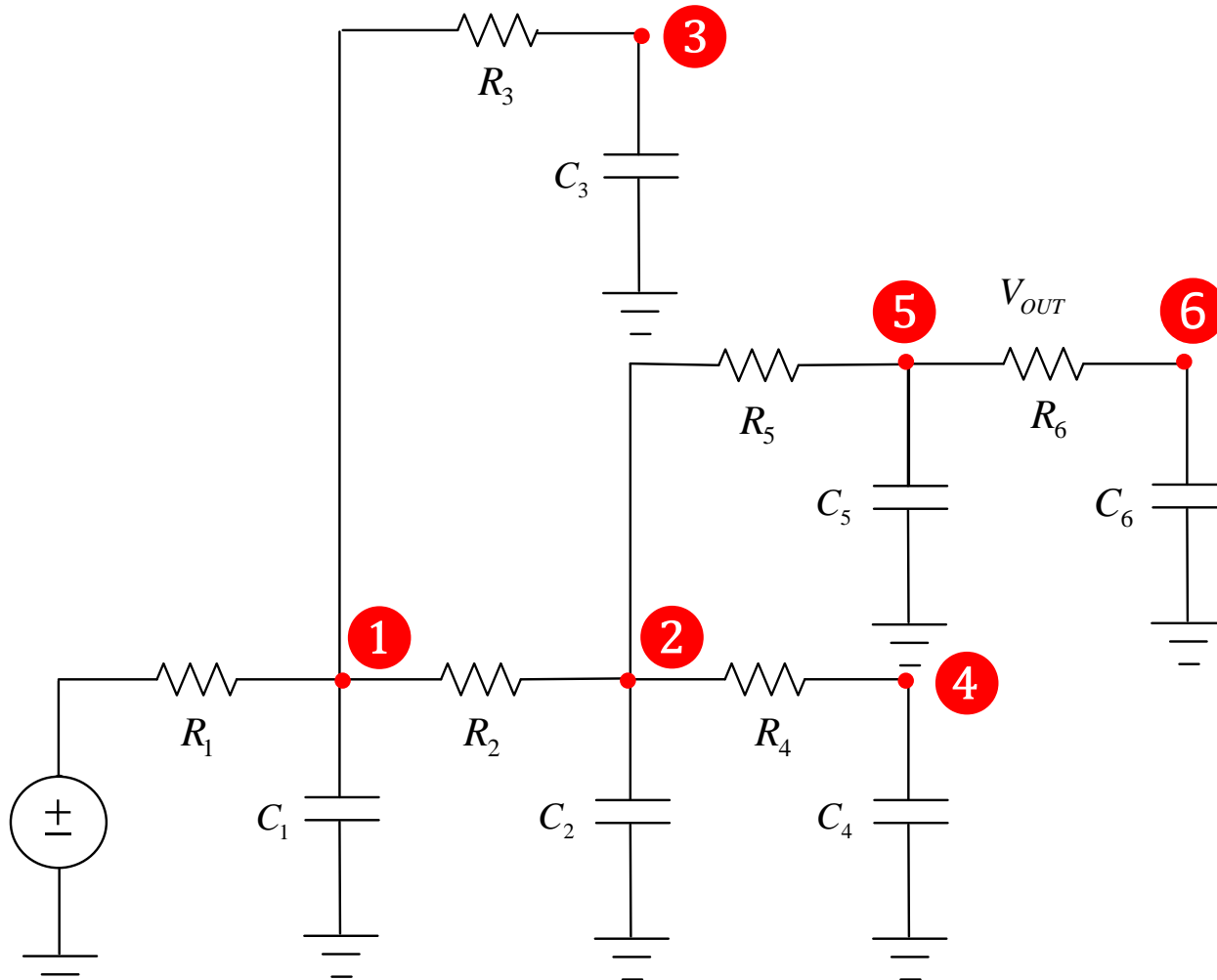




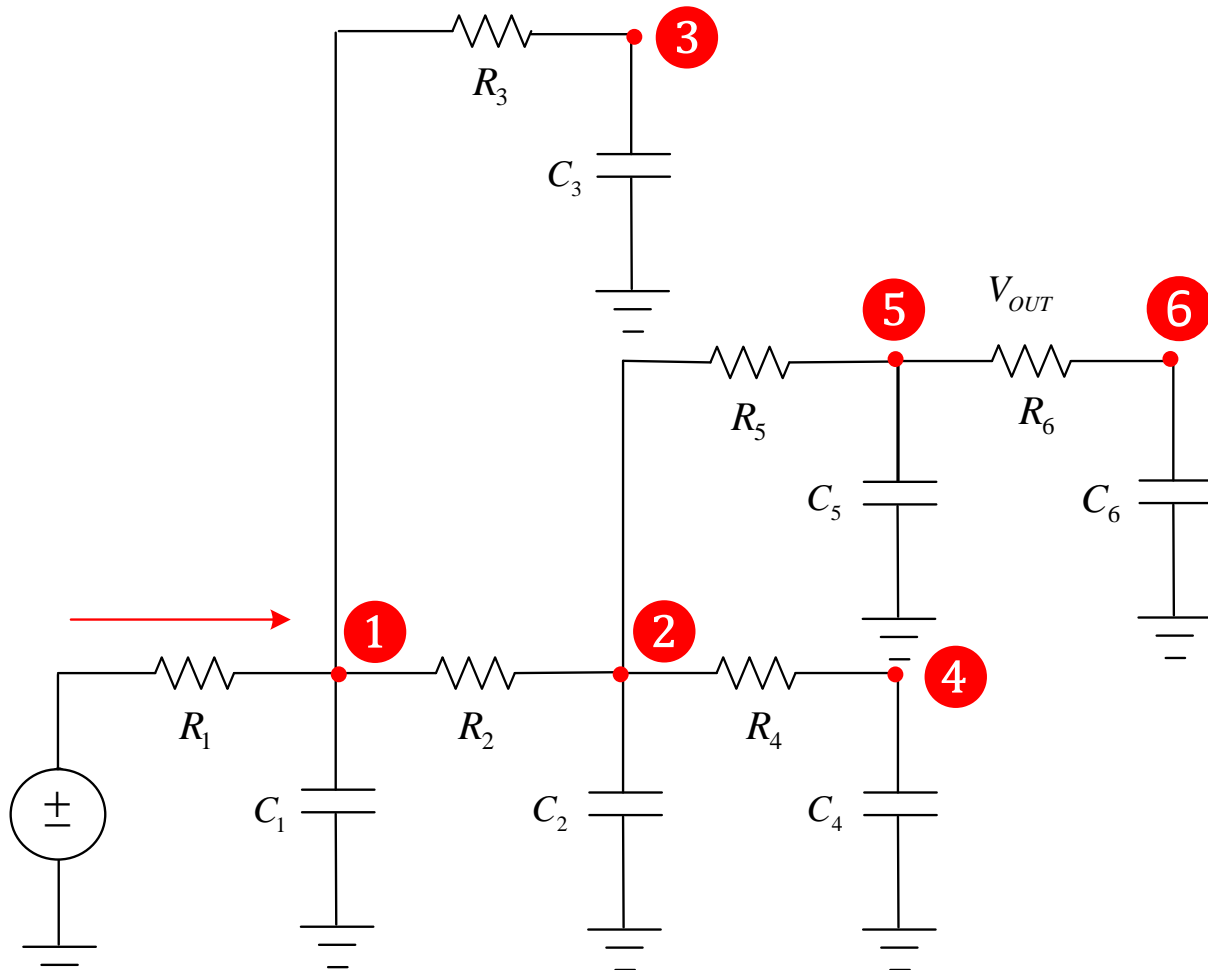
- 1 $\tau_{V_{in}-V_{out1}} = R_1 (C_1 + C_2 + C_3 + C_4 + C_5 + C_6)$






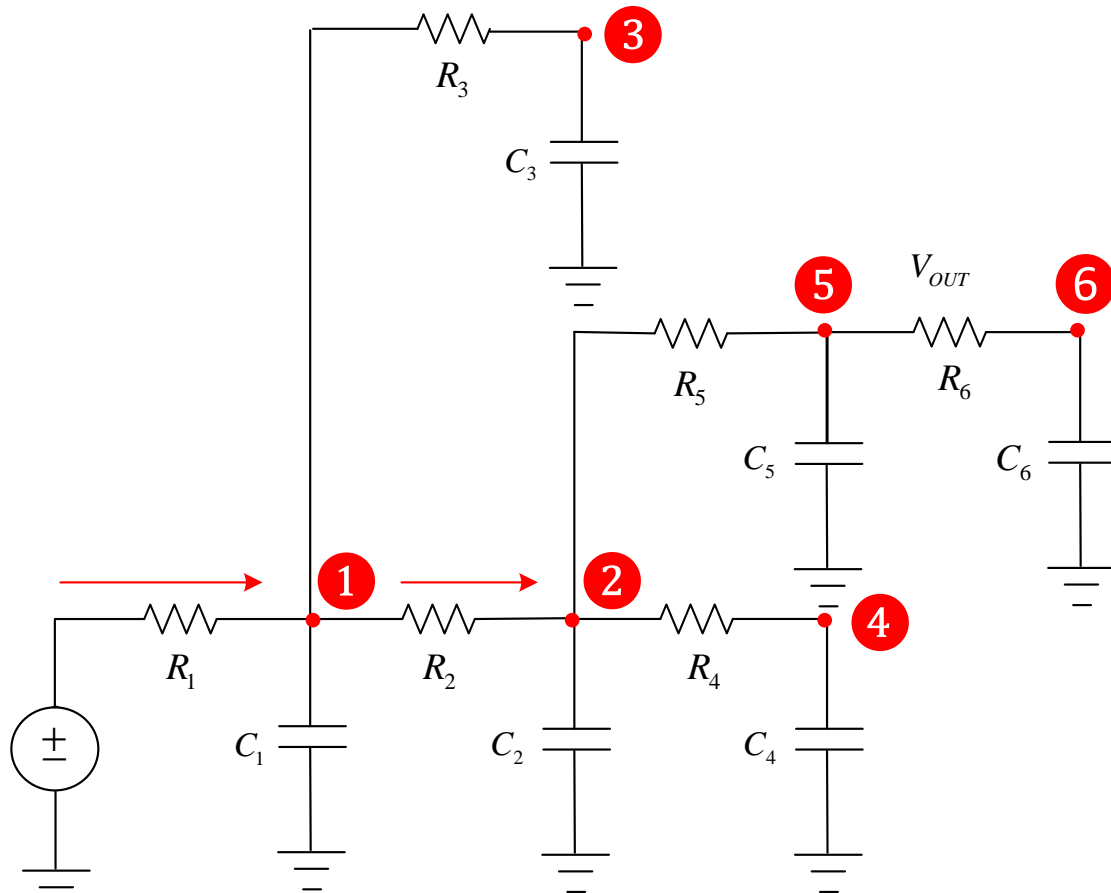- $$2 \quad \tau_{V_{in}-V_{out2}} = R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6) + R_2(C_2 + C_4 + C_5 + C_6)$$



 


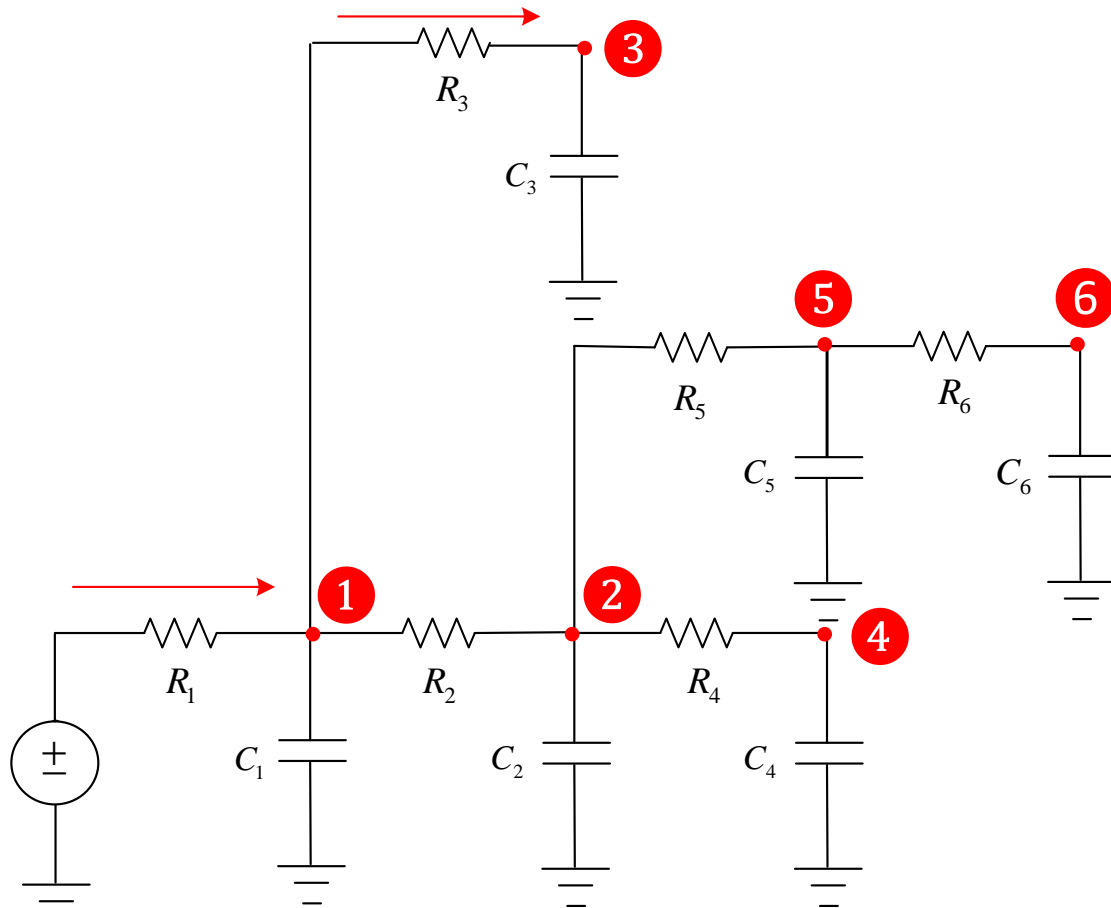
- **3** $\tau_{V_{in}-V_{out3}} = R_1 (C_1 + C_2 + C_3 + C_4 + C_5 + C_6) + R_3 C_3$






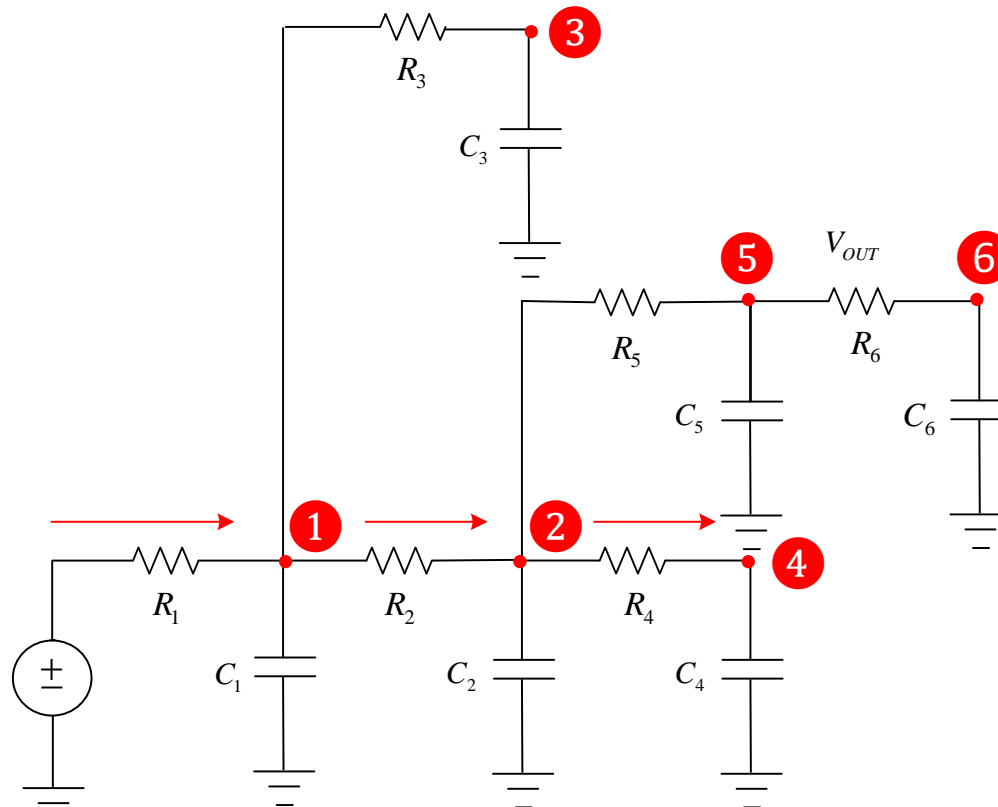
• **4** $\tau_{V_{in}-V_{out4}} = R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6) + R_2(C_2 + C_4 + C_5 + C_6) + R_4C_4$



 


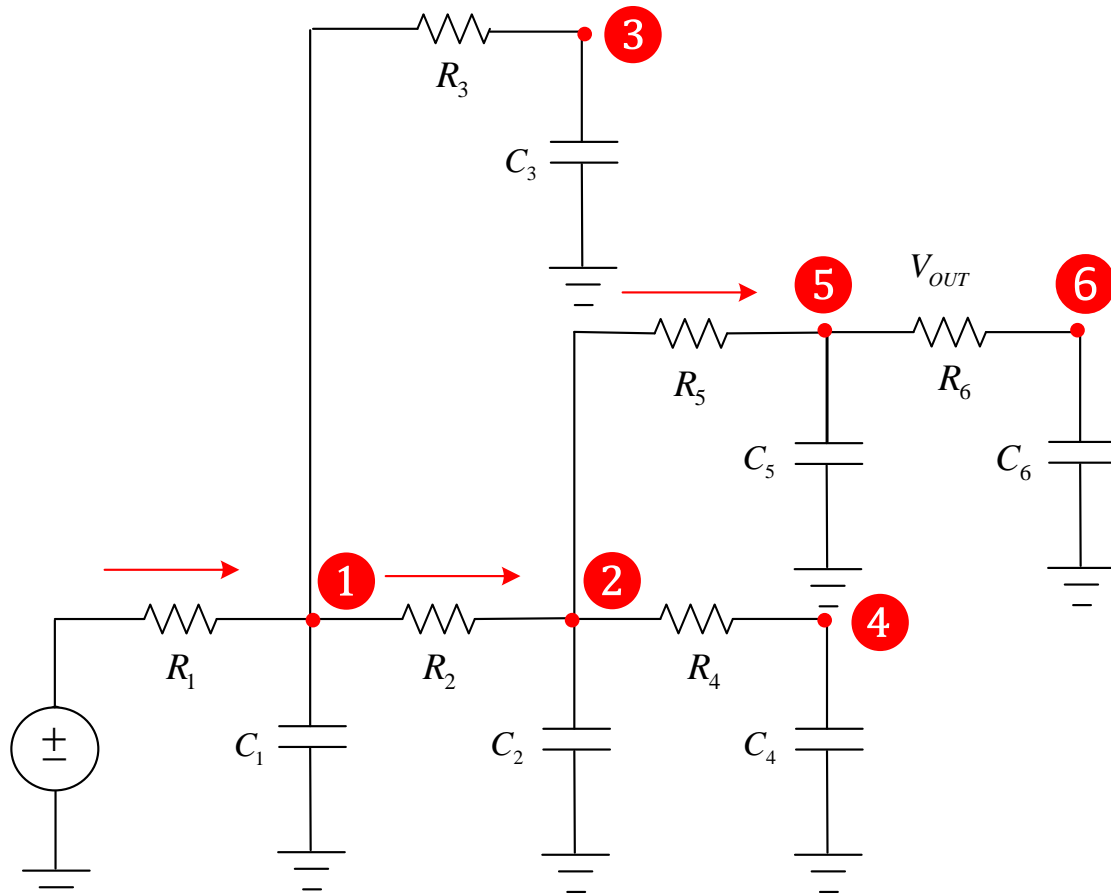
- $$\tau_{V_{in}-V_{out5}} = R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6) + R_2(C_2 + C_4 + C_5 + C_6) + R_5C_5$$



 


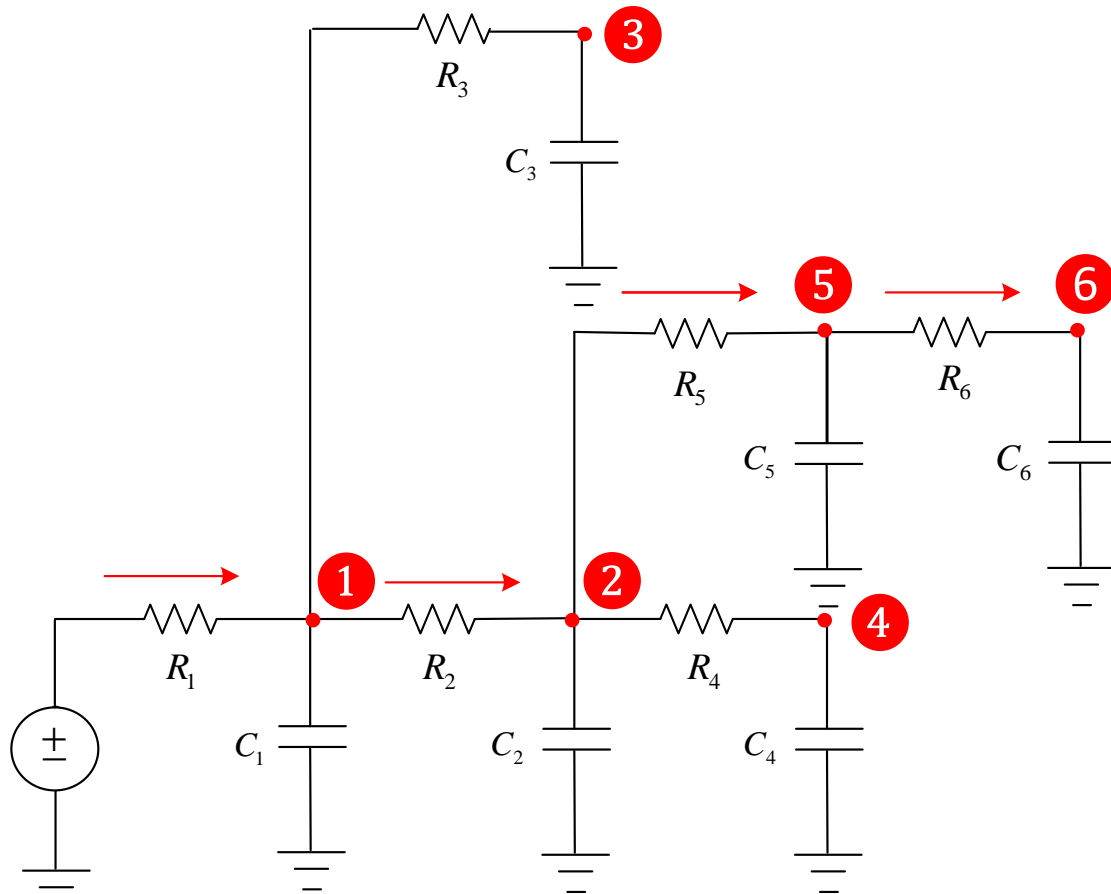
- $$\tau_{V_{in}-V_{out6}} = R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6) + R_2(C_2 + C_4 + C_5 + C_6) + R_5(C_5 + C_6) + R_6C_6$$



 


- Find the Time constant at all nodes.

 

 

- Find the Time constant at all nodes.

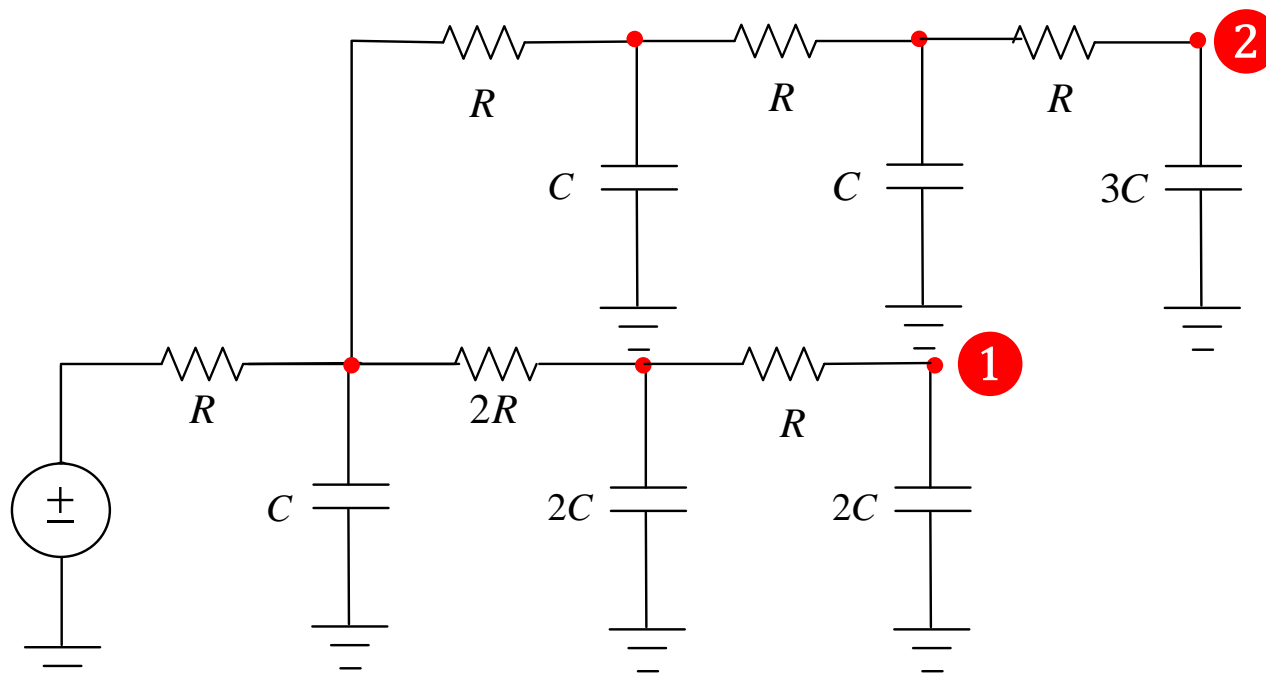
$$\begin{aligned}\tau_{V_{in}-V_{out1}} &= RC + 2C(R + 2R) + 2C(R + 2R + R) \\ &\quad + R(C + C + 3C) = 20RC\end{aligned}$$







- Find the Time constant at all nodes.
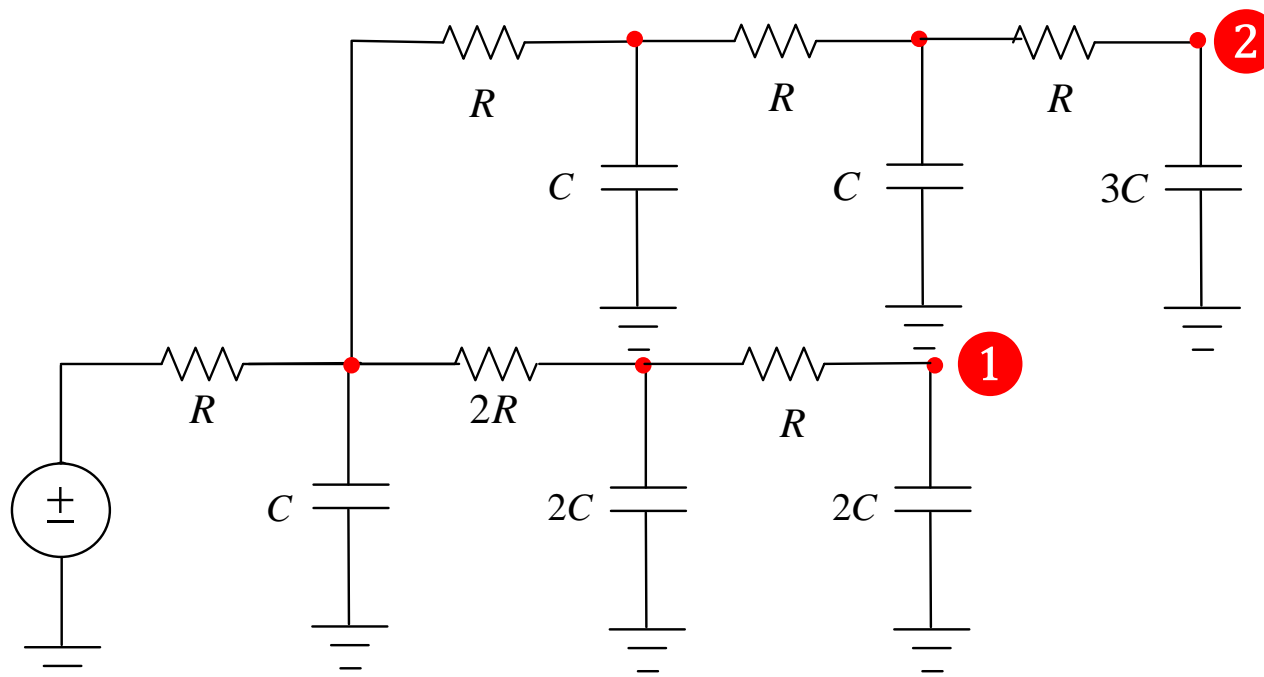
$$\begin{aligned}\tau_{V_{in}-V_{out2}} &= RC + C(R+R) + C(R+R+R) \\ &\quad + 3C(R+R+R+R) + R(2C+2C) = 22RC\end{aligned}$$



 


- nMOSFET

 


Operation Regions	Voltages	Current
Cut Off	$V_{GS} \leq V_{Tn}$	$I_{DS} = 0$
Saturation	$V_{GS} > V_{Tn}$ $V_{DS} > V_{GS} - V_{Tn}$	$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{Tn})^2 (1 + \lambda V_{DS})$
Resistive	$V_{GS} > V_{Tn}$ $V_{DS} < V_{GS} - V_{Tn}$	$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right]$



- pMOSFET

 

Operation Regions	Voltages	Current
Cut Off	$V_{SG} \leq V_{Tp} $	$I_{SD} = 0$
Saturation	$V_{SG} > V_{Tp} $ $V_{SD} > V_{SG} - V_{Tp} $	$I_{SD} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - V_{Tp})^2 (1 + \lambda V_{SD})$
Resistive	$V_{SG} > V_{Tp} $ $V_{SD} < V_{SG} - V_{Tp} $	$I_{SD} = \mu_p C_{ox} \frac{W}{L} \left[(V_{SG} - V_{Tp}) V_{SD} - \frac{V_{SD}^2}{2} \right]$

 


- Enhancement mode MOSFET transistor region of operation

	Cut-off	Resistive	Saturation
nMOS	$V_{GSn} < V_{Tn}$ $V_{IN} < V_{Tn}$	$V_{GSn} > V_{Tn}$ $V_{IN} > V_{Tn}$ $V_{DSn} < V_{GSn} - V_{Tn}$ $V_{OUT} < V_{IN} - V_{Tn}$	$V_{GSn} > V_{Tn}$ $V_{IN} > V_{Tn}$ $V_{DSn} > V_{GSn} - V_{Tn}$ $V_{OUT} > V_{IN} - V_{Tn}$
pMOS	$V_{GS p} > V_{Tp}$ $V_{IN} > V_{Tp} + V_{DD}$	$V_{GS p} < V_{Tp}$ $V_{IN} < V_{Tp} + V_{DD}$ $V_{DS p} > V_{GS p} - V_{Tp}$ $V_{OUT} > V_{IN} - V_{Tp}$	$V_{GS p} = V_{Tp}$ $V_{IN} < V_{Tp} + V_{DD}$ $V_{DS p} < V_{GS p} - V_{Tp}$ $V_{OUT} < V_{IN} - V_{Tp}$



 - Parasitic capacitors in the cut-off $V_{GS} < V_{TN}$




- Channel is not inverted

$$C_{gate} = C_{gate-body} = C_0 = C_{ox} WL = \frac{\epsilon_{ox}}{t_{ox}} WL$$



 - Parasitic capacitors in the non-saturation $V_{GS} > V_{TN}$ & $V_{DS} < V_{GS} - V_{TN}$




$$C_{gate} = C_{gate-body} + C_{gate-source} + C_{gate-drain}$$

$$C_{gate} = 0 + \frac{C_0}{2} + \frac{C_0}{2} = C_0$$



 - Parasitic capacitors in the saturation $V_{GS} > V_{TN}$ & $V_{DS} > V_{GS} - V_{TN}$



$$C_{gate} = C_{gate-body} + C_{gate-source} + C_{gate-drain}$$

$$C_{gate} = 0 + \frac{2C_0}{3} + 0 = \frac{2C_0}{3}$$



- Parasitic capacitors in the cut-off

