

Midterm Exam

March 6, 9:10-10:30am

Name: Solutions

(50 points total)

PROBLEM 1: Consider the common source amplifier shown in Fig. 1. [12 points]

- (a) Calculate the noise factor of this circuit, assuming it is driven by a source with an output impedance of R_S . For the transistor, include C_{gs} in the small signal model. You may neglect induced gate noise, $1/f$ noise, r_o , and all other small signal capacitances. [10]
- (b) Now assume that the amplifier is being designed to operate at the frequency ω_c , and C_{gd} is no longer small enough to be neglected. We have connected an inductor from the gate to the drain of $M1$ to increase the reverse isolation. How should the inductor be sized? [2]


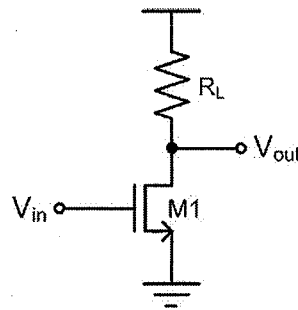


Figure 1: Common source amplifier schematic for Problem 1.

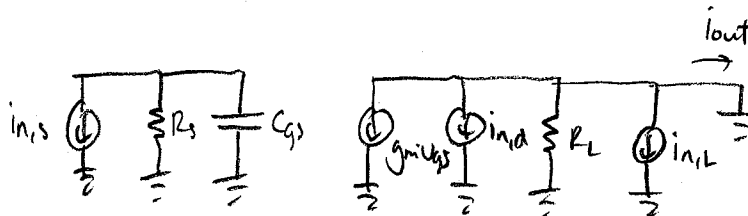c) Draw small signal model with noise sources:



PROBLEM 1 (cont'd)

Consider noise source one at a time:

$$R_S: i_{out} = g_m \cdot i_{ns} \cdot [R_S \parallel C_{gs}] \leftarrow = \left(\frac{1}{R_S + sC_{gs}} \right)^{-1} = \frac{R_S}{1 + sR_S C_{gs}}$$

$$\overline{i_{out}^2} = g_m^2 \cdot \overline{i_{ns}^2} \cdot \frac{R_S^2}{(1 + sR_S C_{gs})^2}$$

$$i_d: \overline{i_{out}^2} = \overline{i_{nd}^2}$$

$$R_L: \overline{i_{out}^2} = \overline{i_{nL}^2}$$

Now sub into expression for F:

$$F = 1 + \frac{\cancel{4kT} \gamma \cdot g_{ds} \cdot \cancel{\Delta f}}{\cancel{4kT} \cdot \cancel{\Delta f}} \cdot \frac{R_S \cdot (1 + sR_S C_{gs})^2}{g_m^2 \cdot R_S^2} + \frac{\cancel{4kT} \Delta f}{R_L \cdot \cancel{4kT} \Delta f} \cdot \frac{R_S \cdot (1 + sR_S C_{gs})^2}{R_S^2 \cdot g_m^2}$$

$$F = 1 + \frac{\gamma \cdot g_{ds} \cdot (1 + \omega^2 R_S^2 C_{gs}^2)}{g_m^2 \cdot R_S} + \frac{(1 + \omega^2 R_S^2 C_{gs}^2)}{R_L \cdot R_S \cdot g_m^2}$$

b) Choose L to resonate with C_{gd}

$$\therefore \omega_c = \frac{1}{\sqrt{L \cdot C_{gd}}} \Rightarrow \boxed{L = \frac{1}{\omega_c^2 \cdot C_{gd}}}$$

PROBLEM 2: Consider the matching network shown in Fig. 2, consisting of two inductors and one capacitor. [12 points]

- (a) If R_L is 50Ω , choose values for C , L_1 , and L_2 so that R_{IN} is 10Ω at $\omega = 5 \times 10^9$ rad/s (hint: more than one solution is possible). [10]
- (b) What advantages (if any) does this matching network have over a standard L-match? [2]


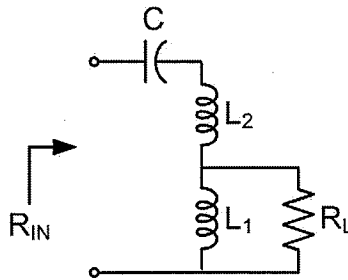


Figure 2: Matching network for Problem 2.

a) Transform to series equivalent:

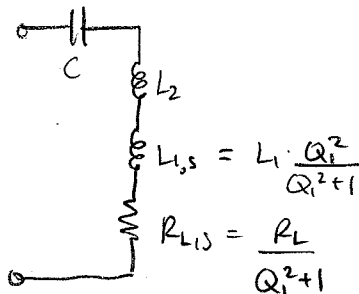

Now, C must resonate with $L_2 + L_{1,s}$ at ω_0 ,
so: $\omega_0 = \frac{1}{\sqrt{C(L_2 + L_{1,s})}}$ *

Also, $R_{in} = R_{L,s} = 10 = \frac{50}{Q_1^2 + 1}$
 $\therefore Q_1^2 = 4 \Rightarrow Q_1 = 2$.

Also, $Q_1 = \frac{\omega_0 \cdot L_{1,s}}{R_{L,s}}$

$\therefore 2 = \frac{5 \times 10^9 \cdot L_{1,s}}{10}$

$\therefore L_{1,s} = 4 \times 10^{-9} \Rightarrow L_1 = 4 \times 10^{-9} \left(\frac{2^2 + 1}{2^2} \right)$

$L_1 = 5 \times 10^{-9} = 5 \text{ nH}$

Now, we have some flexibility in choosing the other components. Choose $C = 1 \text{ pF}$

Now, from *: $L_2 = \frac{1}{\omega_0^2 C} - L_{1,s}$

3

$= \frac{1}{25 \times 10^{18} \cdot 1 \times 10^{-12}} - 4 \times 10^{-9}$

$L_2 = 36 \times 10^{-9} = 36 \text{ nH}$

➔ Note this yields an overall network Q of:

$Q = \frac{\omega_0(L_2 + L_{1,s})}{R_{L,s}}$
 $= \frac{5 \times 10^9 (40 \times 10^{-9})}{10}$

$Q = 20$

b) So, we see that this network provides some flexibility in choosing the Q of the overall network (We can choose it to be higher than the requirement from the transformation ratio, but not lower).

PROBLEM 3: Your manager has asked you to evaluate the linearity of an RF front end. You know that for a signal input power of -30 dBm the power of the fundamental component at the output is -10 dBm, and for two tones with an input power of -30 dBm, the IM3 components have a power of -70 dBm at the output. [12 points]

- What is the gain of the system? [1]
- Using the plot in Fig. 3, calculate the IIP3 for the system. Draw in the relevant curves, and label the IP3 point on the plot. [3]
- If the bandwidth of the system is 10 MHz, the noise figure is 14 dB, what is the input referred noise floor (hint: this was contained in the formula given in class for the sensitivity)? What is the output referred noise floor? [5]
- Draw the output referred noise floor into the plot in Fig. 3, and mark the SFDR. What is the SFDR for this system? [3]

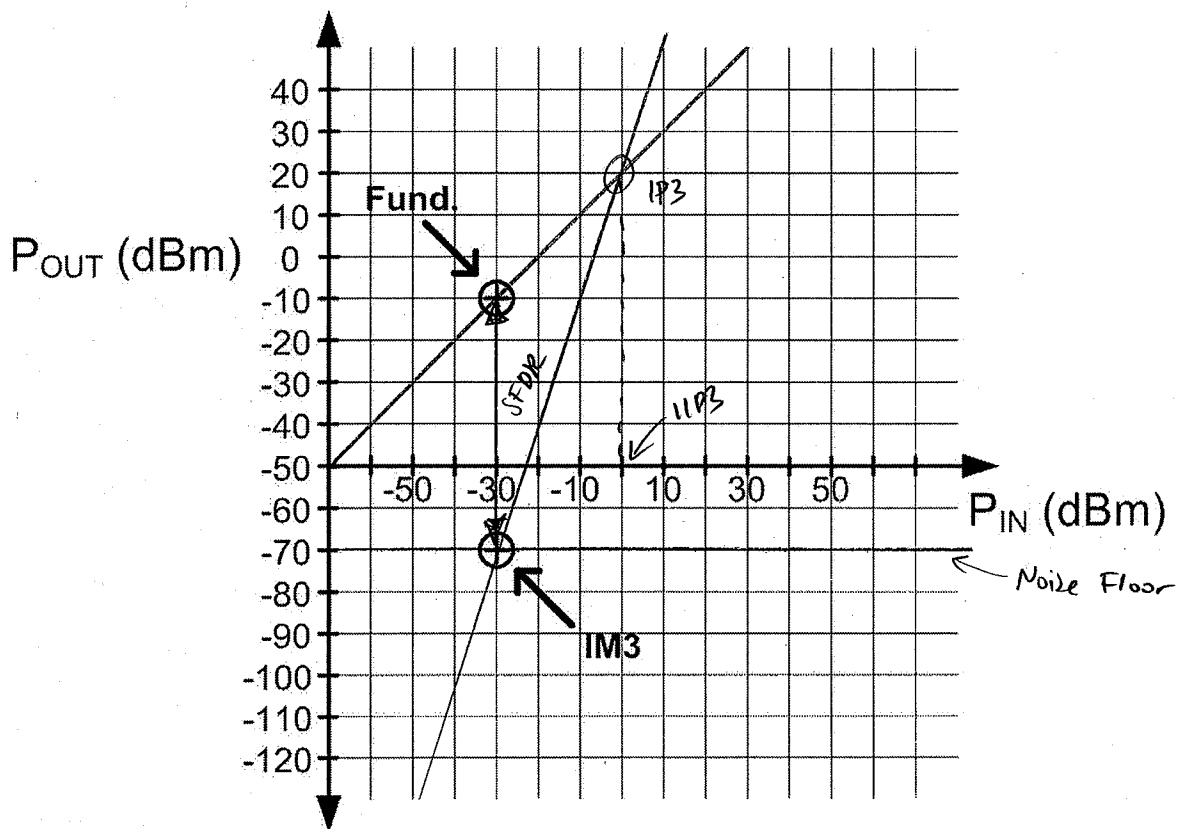


Figure 3: SFDR plot for Problem 3.

PROBLEM 3 (cont'd)

$$(a) \text{ gain} = 20 \text{ dB}$$

$$(b) \text{ IIP3} = 0 \text{ dBm}$$

$$\begin{aligned} (c) \text{ I/P referred noise} &= -174 \text{ dBm} + 10 \cdot \log B + NF \\ &= -174 + 70 + 14 \\ &= -90 \text{ dBm} \end{aligned}$$

$$\begin{aligned} \text{O/P referred noise} &= \text{I/P referred noise} \times \text{gain} \\ &= -90 \text{ dBm} + 20 \text{ dB} \\ &= -70 \text{ dBm} \end{aligned}$$

$$(d) \text{ SFDR} = 60 \text{ dB}$$

Explanation for (c):

$$\begin{aligned} F &= \frac{\text{noise at O/P}}{\text{noise at O/P from I/P}} \\ &= \frac{\text{noise at O/P}}{\text{noise at I/P} \times \text{gain}} \end{aligned}$$

$$\begin{aligned} \therefore \text{noise at O/P} &= F \times \text{gain} \times \text{noise at I/P} \\ &= KT \times BW \end{aligned}$$

$$\begin{aligned} \therefore \text{O/P referred noise [dBm]} &= 10 \cdot \log (F \times \text{gain} \times KT \times BW) \\ &= NF + \text{gain (in dB)} + \underbrace{10 \cdot \log KT}_{\uparrow = -174 \frac{\text{dBm}}{\text{Hz}}} + 10 \cdot \log BW \end{aligned}$$

PROBLEM 4: Shown in Fig. 4 is the down-conversion chain for an RF receiver. The incoming signal of interest is centered around $f_C = 900$ MHz, and low-side LO injection is used for down-conversion, with $f_{LO} = 850$ MHz. [12 points]

- What is the intermediate frequency (f_{IF}) for this system? [1]
- If the bandwidth of each channel is 2 MHz, what is the approximate Q required for the channel select filter? [2]
- What is the image frequency for the signal of interest? [1]
- Now assume that the specifications for each of the system blocks are as shown in Table 1. What is the noise figure of the down-conversion chain as a whole (note the distinction between the noise figure (NF, in dB) as provided in Table 1 and the noise factor also discussed in class (F, in linear units))? [8]

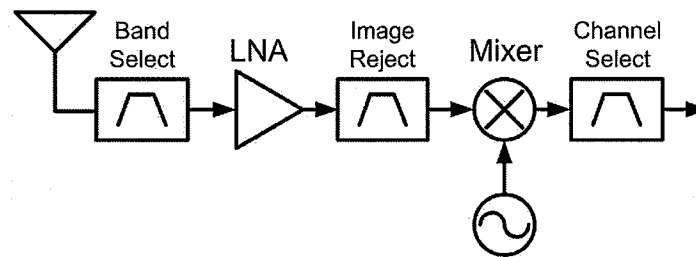


Figure 4: Down-conversion chain for Problem 4.

Component	Noise Figure (dB)	Available Power Gain (dB)
Band Select filter	0	-3
Low Noise Amplifier	3	20
Image Reject filter	0	-3
Mixer	10	0
Channel Select filter	0	-3

Table 1: Noise Figures and Available Power Gains for components in Fig. 4.

a) $f_{IF} = f_C - f_{LO} = 50 \text{ MHz}$.

b) $Q = \frac{f_0}{\Delta f} = \frac{f_{IF}}{BW} = \frac{50 \text{ MHz}}{2 \text{ MHz}} = 25$

c) $f_{IM} = f_{LO} - f_{IF} = 800 \text{ MHz}$.

PROBLEM 4 (cont'd)

d) Write linear units into Table 1.

Friis equation:

$$F_{tot} = 1 + F_1 - 1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots$$

$$\text{Sub in: } F = 1 + (1-1) + \frac{(2-1)}{0.5} + \frac{(1-1)}{0.5 \cdot 100} + \frac{(10-1)}{0.5 \cdot 0.5 \cdot 100} + \frac{(1-1)}{0.5 \cdot 0.5 \cdot 100 \cdot 1}$$

$$= 1 + 2 + \frac{9}{25}$$

$$= 3.36$$

$$\therefore NF = 10 \cdot \log F = 5.26 \text{ dB}$$

PROBLEM 5: Your boss has asked you to interview someone for a new position in the RFIC design group at your company. So far only one candidate has applied (see Fig. 5)? [2 points]

- (a) Who is this man? [1]
- (b) Would you trust him to design your RF front ends? [1]

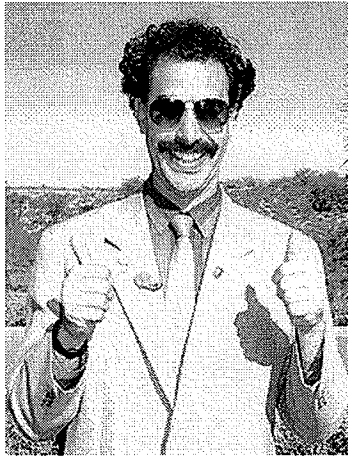


Figure 5: Job applicant for RFIC position.

- a) Mr. Borat Sagdiyev
- b) Yes, I bet his RF design skills are-a very nice!