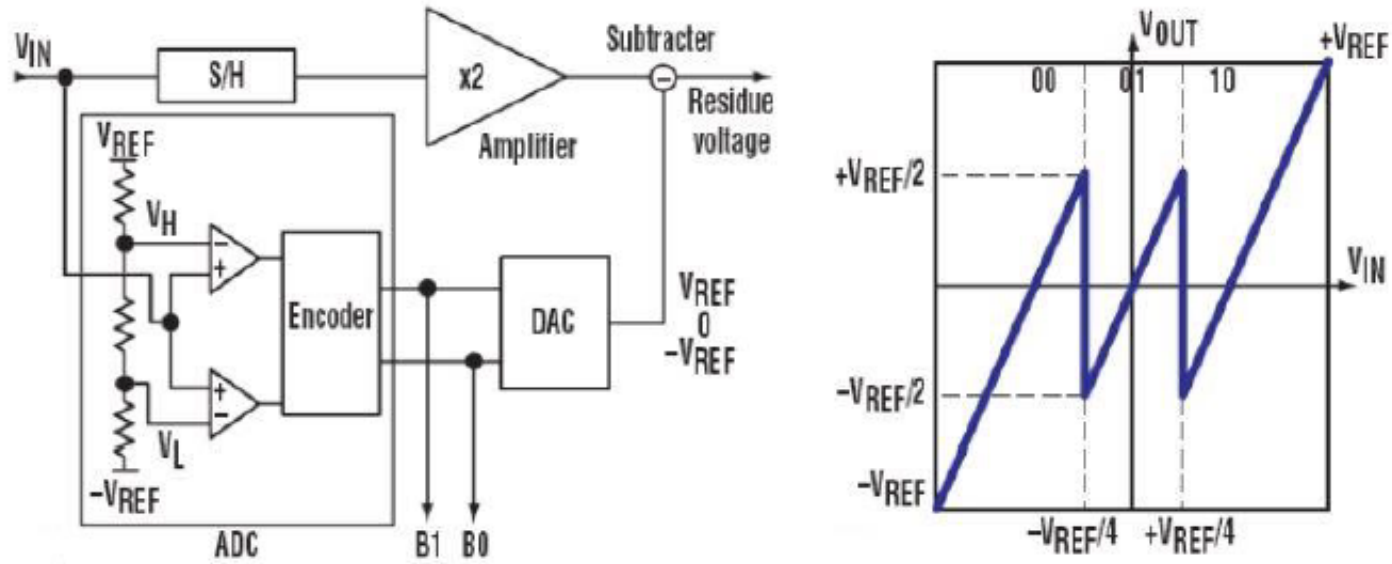

EE288 Data Conversions/Analog Mixed-Signal ICs

Spring 2018

Lecture 20: Pipelined ADC 2


Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

1.5-Bit Stage Architecture




V_{IN}	Range	B1	B0	DAC O/P	Residue
$V_{IN} > V_H$	H	1	0	$+V_{REF}$	$2V_{IN} - V_{REF}$
$V_L < V_{IN} < V_H$	M	0	1	0	$2V_{IN}$
$V_H < V_L$	L	0	0	$-V_{REF}$	$2V_{IN} + V_{REF}$

Timing Diagram of Pipelining


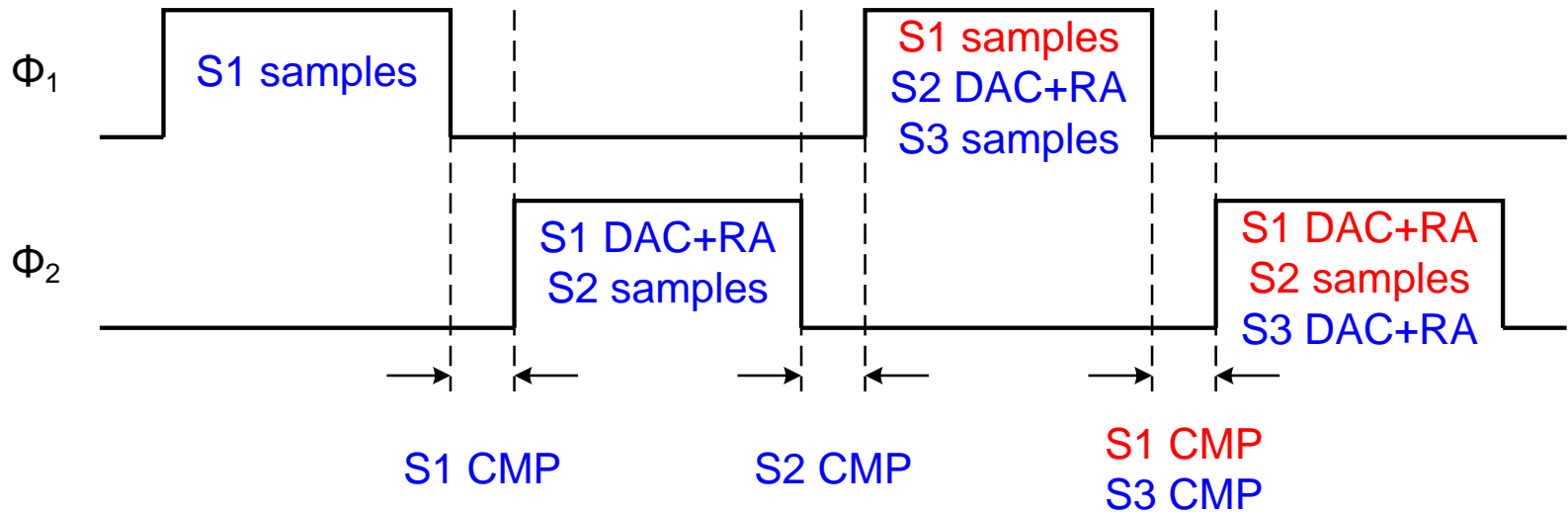


- Two-phase nonoverlapping clock is typically used, with the coarse ADCs operating within the nonoverlapping times
- All pipelined stages operate simultaneously, increasing throughput at the cost of latency


Timing of Pipeline Stages

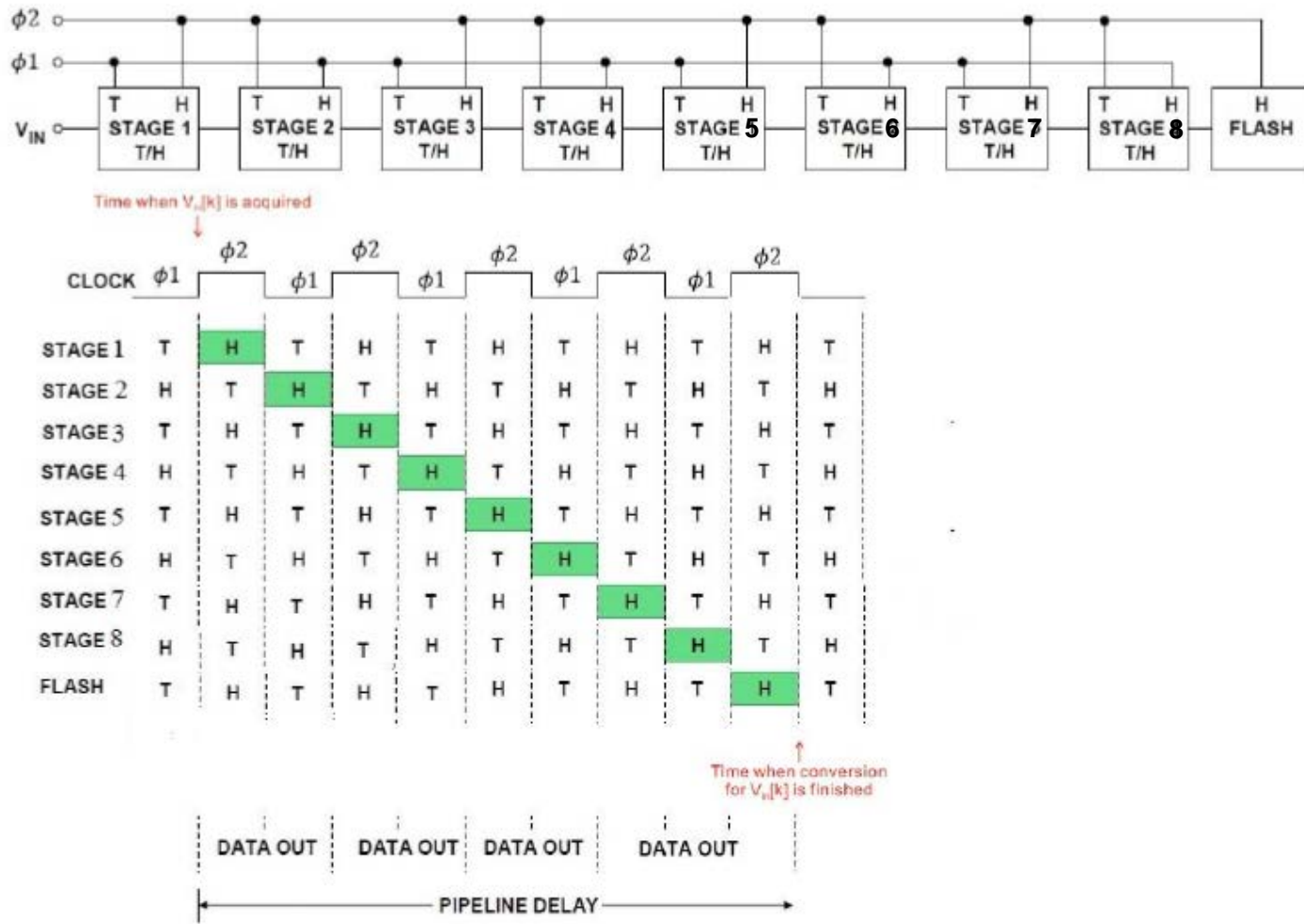

Time-Alignment and Synchronization

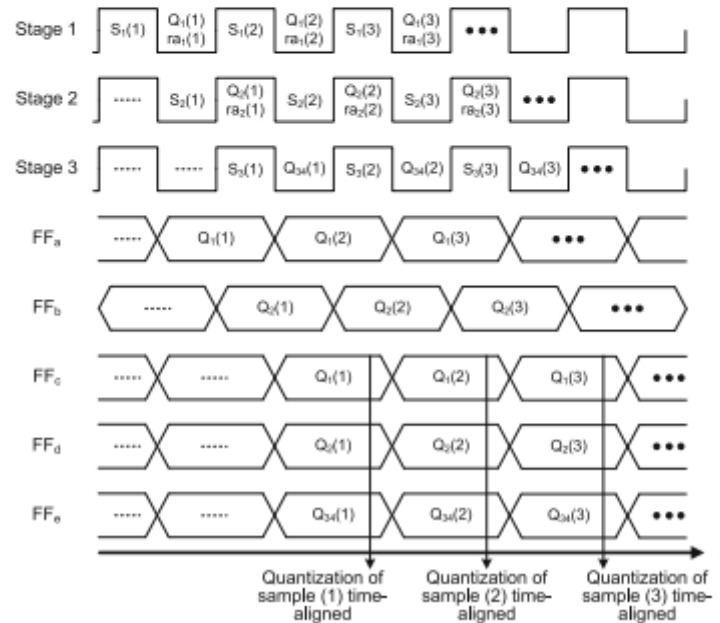 

Digital Error Correction

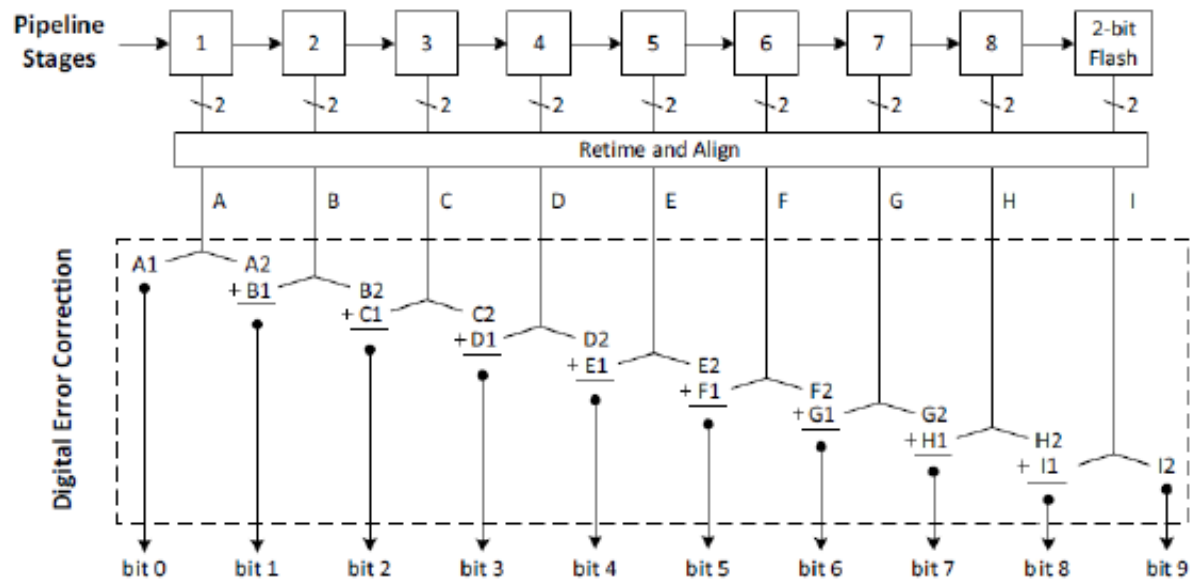

Digital Correction

$$V_o = \begin{cases} 2V_i - V_{ref} & \text{if } V_i > V_{ref}/4 & d = 2 (10)_2 \\ 2V_i & \text{if } -V_{ref}/4 \leq V_i \leq +V_{ref}/4 & d = 1 (01)_2 \\ 2V_i + V_{ref} & \text{if } V_i < -V_{ref}/4 & d = 0 (00)_2 \end{cases}$$

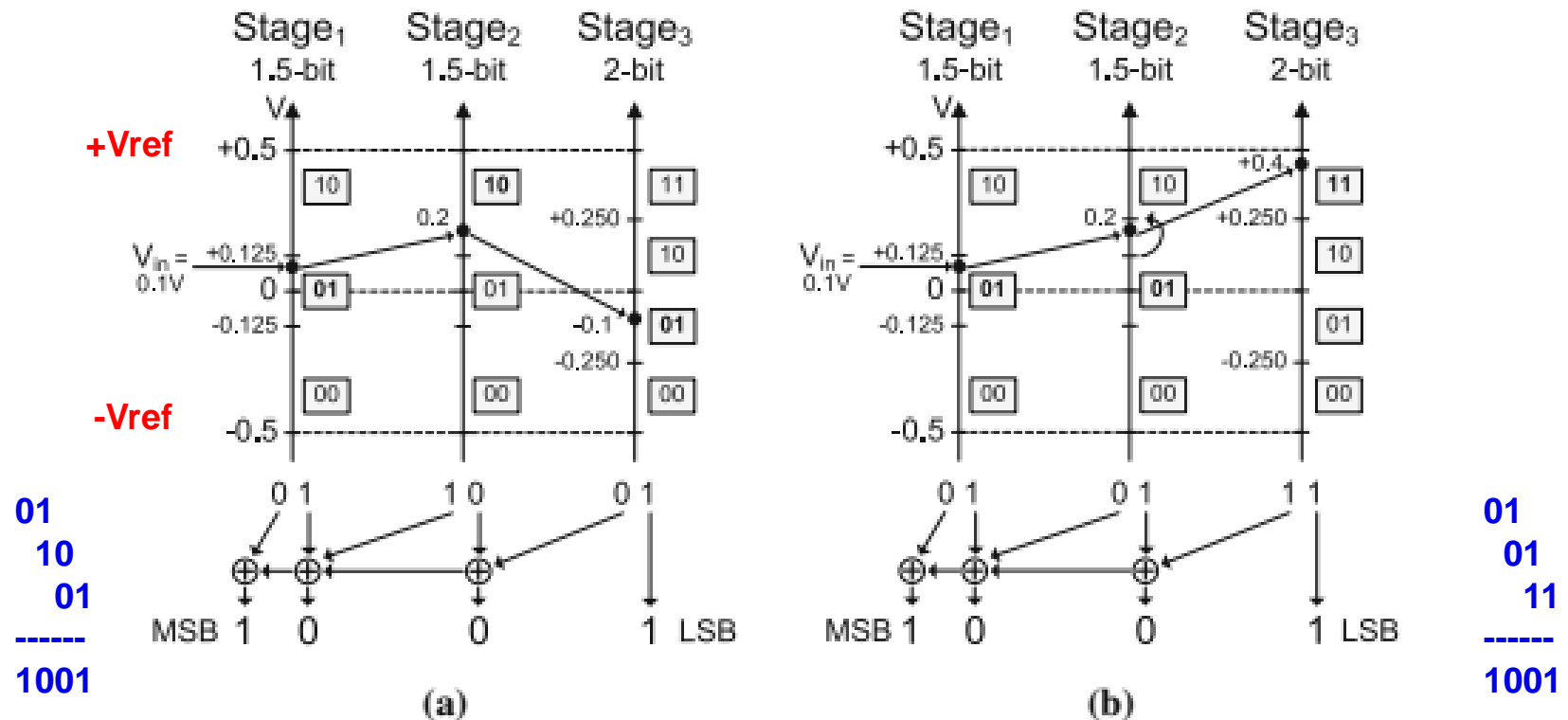


Fig. 2.15 Example of the operation of digital correction: **a** Ideal situation (and indecision corrected). **b** Offset error in stage 2: offset corrected

10-Bit ADC Example

$$\begin{array}{r}
 1 \ 0 \\
 0 \ 1 \\
 0 \ 0 \\
 \hline
 1 \ 0 \ 1 \ 0
 \end{array}$$

Table 4.3: Example of digital error correction

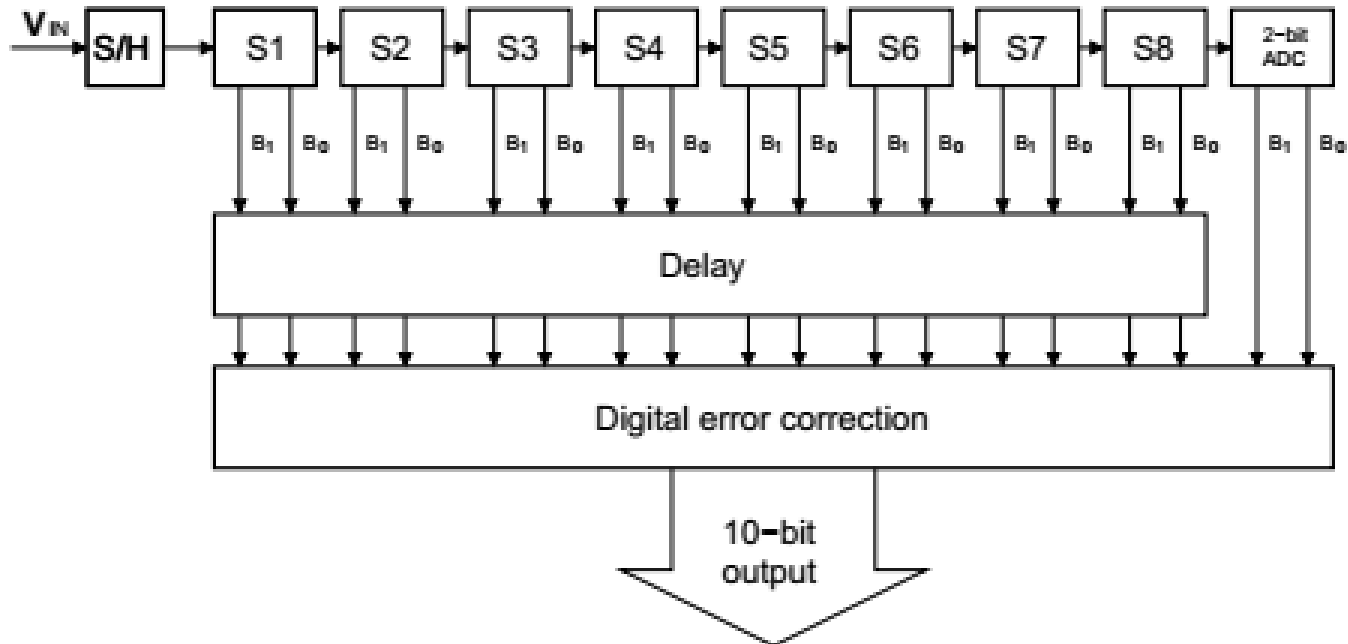


Figure 4.8: The final structure of the pipeline

Pipelined ADC Features


Features

- Architecture complexity is proportional to the resolution $N = \sum n_j$
- Throughput is significantly improved relative to algorithmic or SAR
- Digital redundancy works the same way as algorithmic
- Inter-stage gain enables stage scaling to save power and area

Limitations


- Typically 3 conversion operations are involved
 - Sample-and-hold
 - Sub-ADC comparison
 - Sub-DAC and residue generation
- High-gain op-amps are required to produce residue signals with certain accuracy, which limits the conversion speed
- Long latency may be problematic for certain applications

No Stage Scaling

 


- All stages identically sized – same capacitors, op-amps, comparators
- Later stages are clearly oversized due to inter-stage gains

Aggressive Stage Scaling

 

- Stages sized such that the input-referred noises are identical
- Later stages are clearly downsized too aggressively

Optimum Stage Scaling

 


Optimum scaling lies in between the two extremes $\rightarrow S \approx 2^{n_j}$


Class Project: 10-bit Pipelined ADC

- Process Technology 45nm CMOS with 0.18um I/O devices
 - Supply Voltage $V_{DD} = 1.8V \pm 5\%$
 - Temperature Range $0 \sim 70^{\circ}\text{C}$
 - Sampling Rate, F_s 100 MS/s
 - Input Full Scale, VFS 1.6 Vppd
 - Input Frequency $1 \sim 10\text{ MHz}$
 - FoM $< 3.6\text{ pJ/conv. step}$ (To be confirmed)
 - Process Corners TT, FF, SS
-
- All performance numbers to be confirmed.
 - Use **Ideal capacitor** cell “cap” from analogLib
 - Use “**ideal_bias**” cell in ee288lib for master current sources
 - Use “**ideal_clock**” cell in ee288lib for 2-phase non-overlapping clocks
 - Use **Ideal DC voltage source** for all voltage references such as VREFP, VREFM, and VCM

Signal Swing in Project

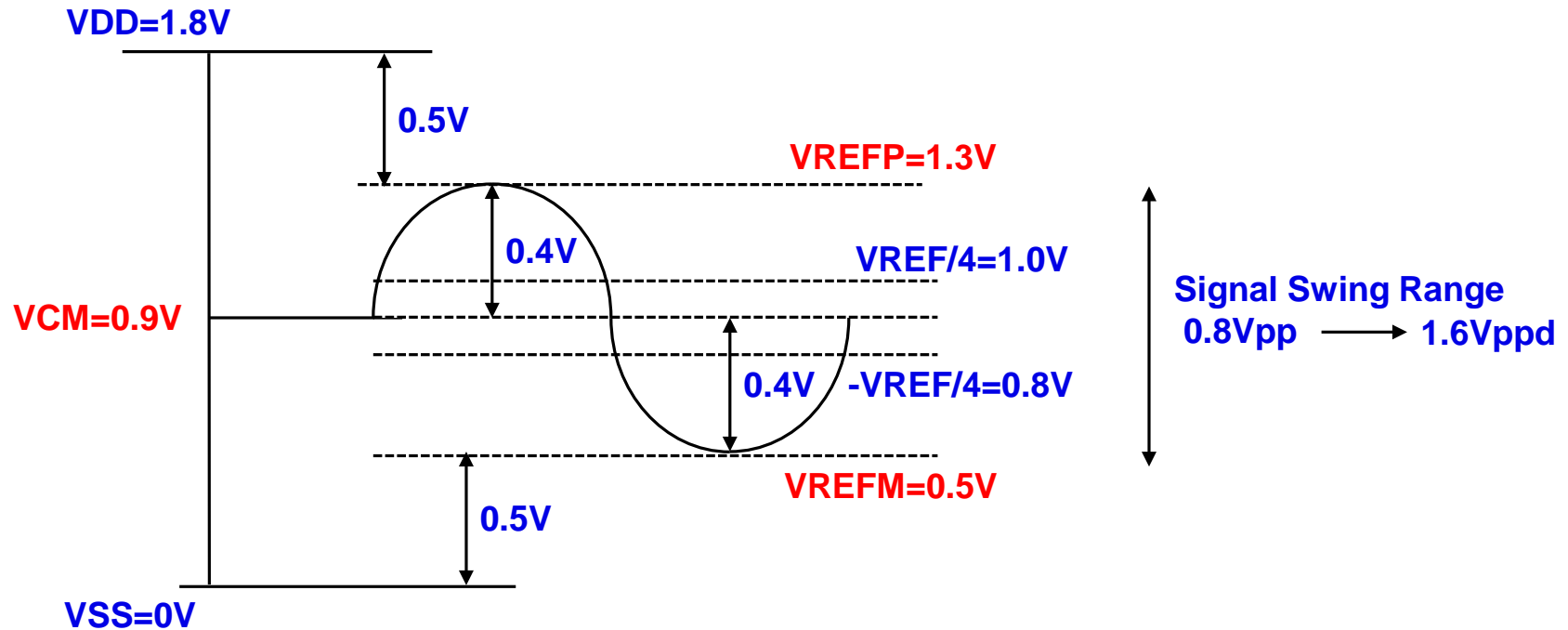


1.5-Bit Stage Architecture

 

Reference Paper:

A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline analog-to-digital converter," *IEEE J. Solid-State Circuits*, vol. 34, pp. 599–606, May 1999

Key Blocks To Design in the Project

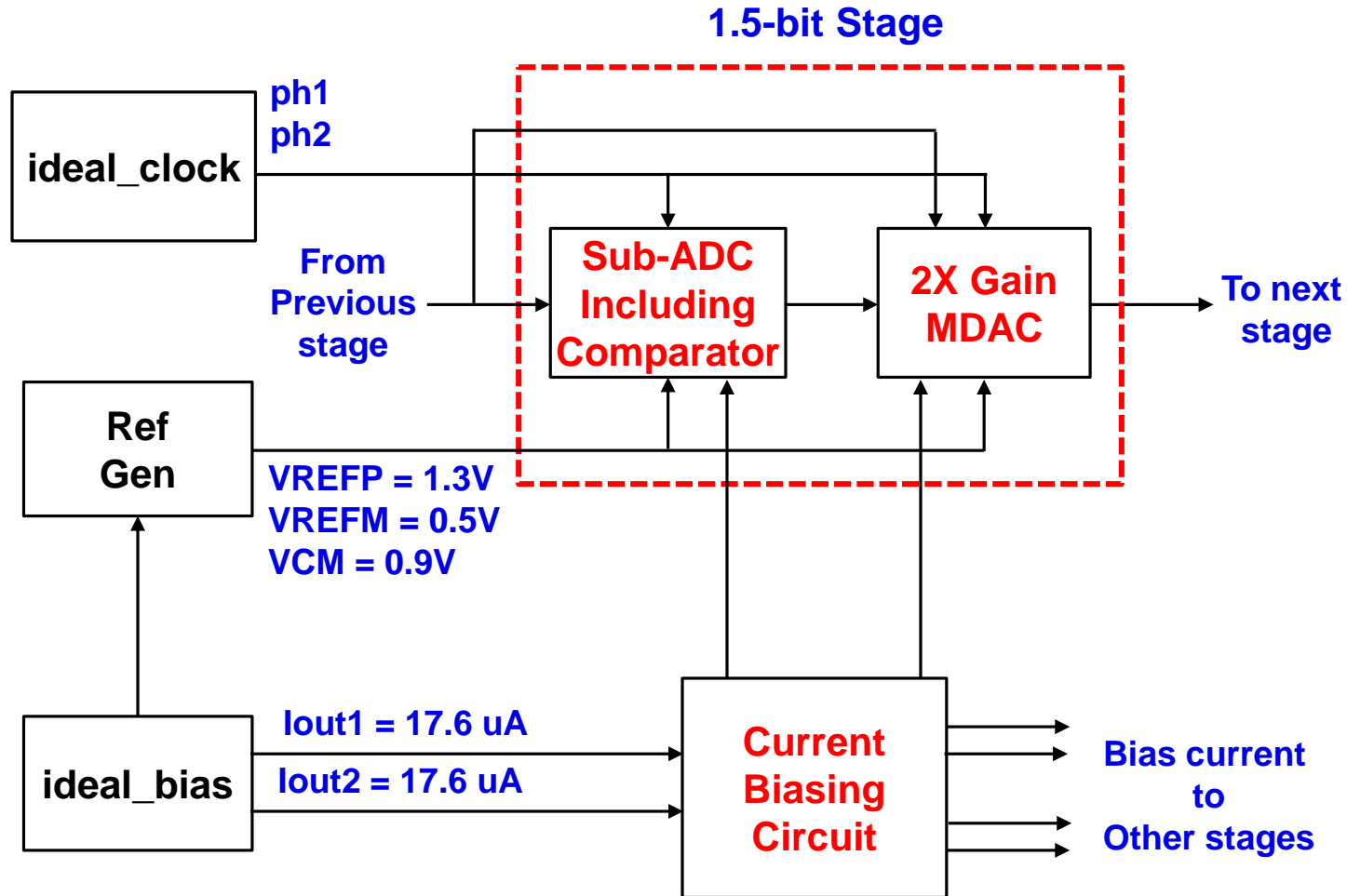

Project Scoring Rule

Total point			40
Condition 1	Functional Fully-Differential 10-bit Pipelined ADC		10
		Typical corner (TT, 1.8V, 27C)	
		Vin (0.5V to 1.3V)	
		$f_{in} = (\text{cycles}/N) * f_s$ where cycles=7 and N=64	
		Fs = 100 MSPS	
		Ideal switches	
		Ideal opamp	
Condition 2	Condition 1 plus	Real switches	5
Condition 3	Condition 2 plus	Real opamp	5
Condition 4	Condition 3 plus	Meeting FoM requirement at Typical corner	5
Condition 5	Condition 4 plus	Meeting FoM requirement at PVT corner	5
		TT, FF, SS, 1.8V +- 5%, 0-70C	
Presentation (10 min)			5
Project report in 4-page IEEE conference paper submission format			5
Extra point		Publication level papers	10

Items to prepare for project presentation

- Summary of your design
- Schematics
- Simulation Test Bench
- Simulation Results
 - OPAMP
 - Comparator
 - 1-stage operation
- FFT plot for the whole ADC

Presentation Score Breakdown

- 20% for Neatness and clearness of the presentation materials to check if the slides are done professionally or not
- 20% for block functionality to check if the individual block design is functional or not
- 10% on if you answered the questions correctly or not in the Q&A session following your presentation


Project Report Guideline

- Use the IEEE template file uploaded in project folder in Canvas
- Total report length should be 4-pages
- Report should include the following sections
 - Abstract
 - Introduction
 - Main sections
 - Conclusion
 - References

Project Report Score Breakdown


- 20% for Neatness and clearness to check if the report is done professionally and if the report follows IEEE format
- 20% for block functionality to check if the individual block design is functional or not
- 10% for full block functionality - if your team cannot show the full functionality, all of your team score will be affected.
- Extra credit for publication-level report

10-bit Pipeline ADC from [Ref. 1]

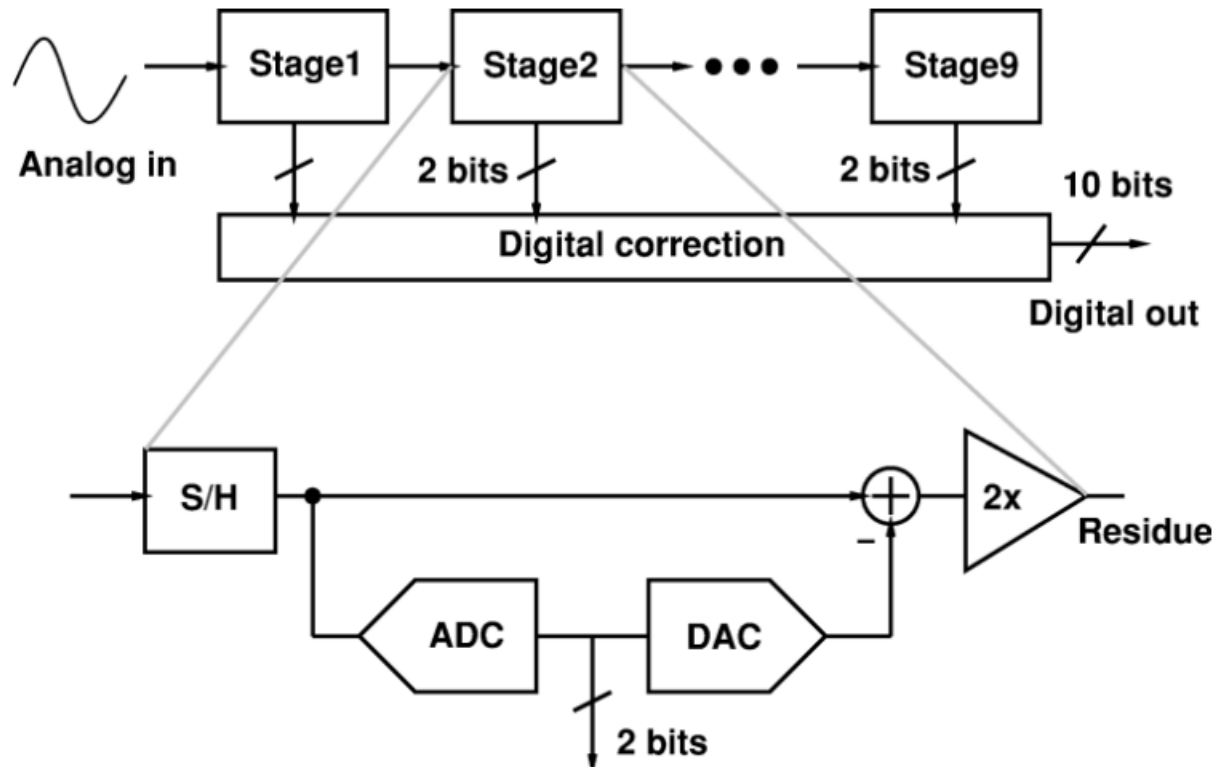


[Ref. 1] A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline analog-to-digital converter," *IEEE J. Solid-State Circuits*, vol. 34, pp. 599–606, May 1999.

10-bit ADC Architecture from [Ref. 2]

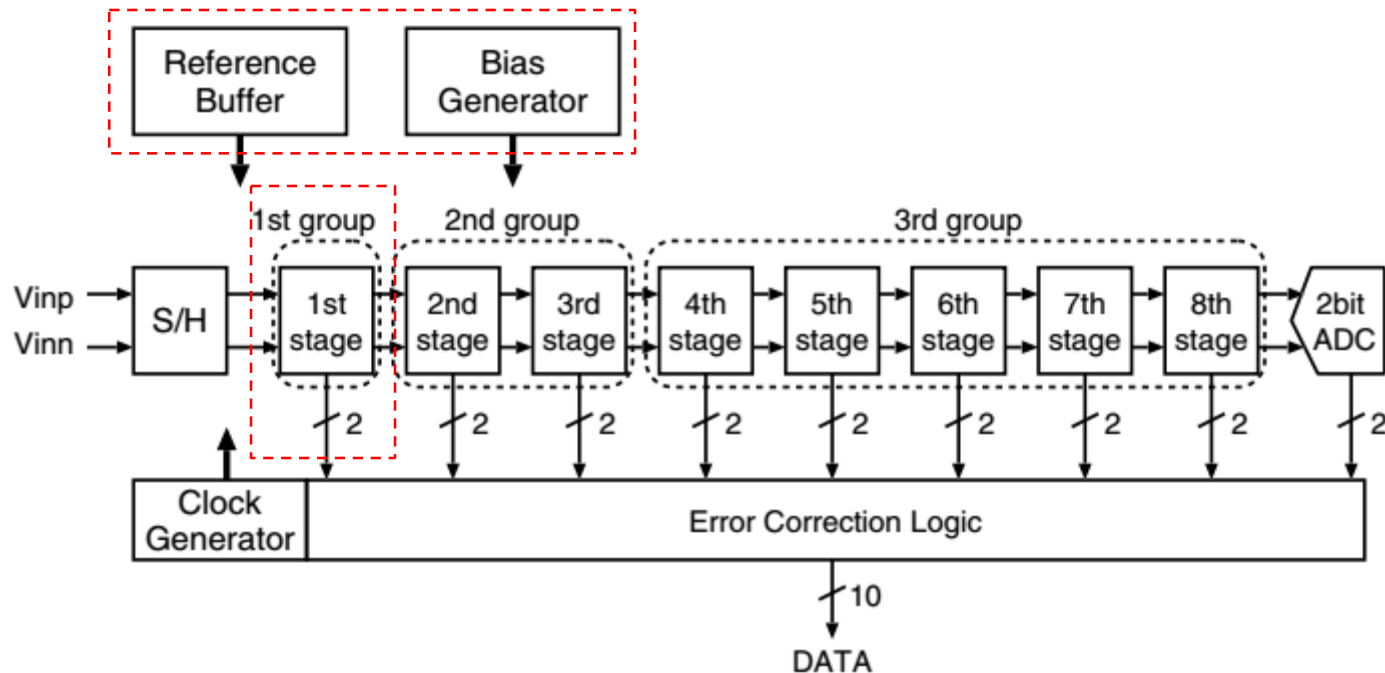


[Ref. 2] H. Ishii, K. Tanabe, and T. Iida, "A 1.0V 40mW 10b 100MS/s Pipeline ADC in 90nm CMOS," *IEEE Custom Integrated Circuits Conference*, pp. 10.5.1–10.5.4, 2005.

Project : 1.5-bit Pipeline Stage [Ref. 2]

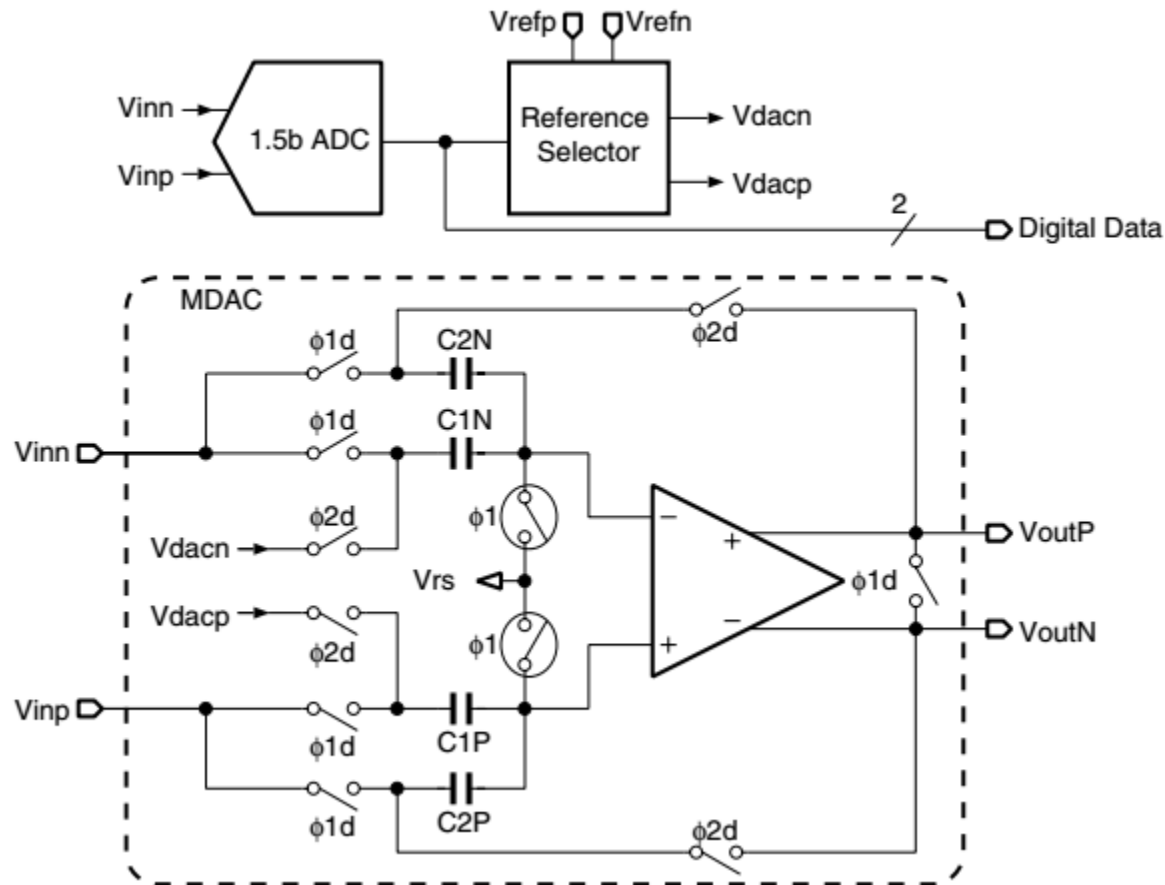


[Ref. 2] H. Ishii, K. Tanabe, and T. Iida, "A 1.0V 40mW 10b 100MS/s Pipeline ADC in 90nm CMOS," *IEEE Custom Integrated Circuits Conference*, pp. 10.5.1–10.5.4, 2005.

Project : 1.5-bit Pipeline Stage [Ref. 3]

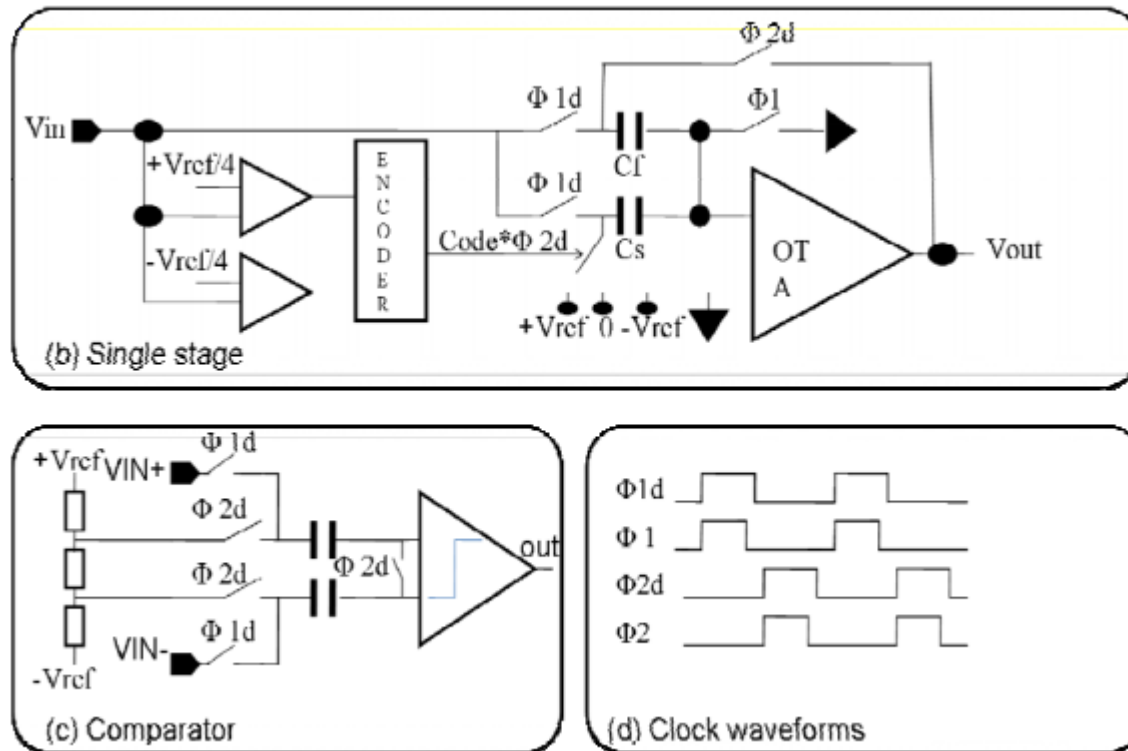


[Ref. 3] M. Boulemnakher, "A 1.2V 4.5mW 10b 100MS/s Pipeline ADC in 65nm CMOS," *IEEE International Solid-State Circuit Conference*, pp. 250-251, 2008


Example OPAMP Circuits

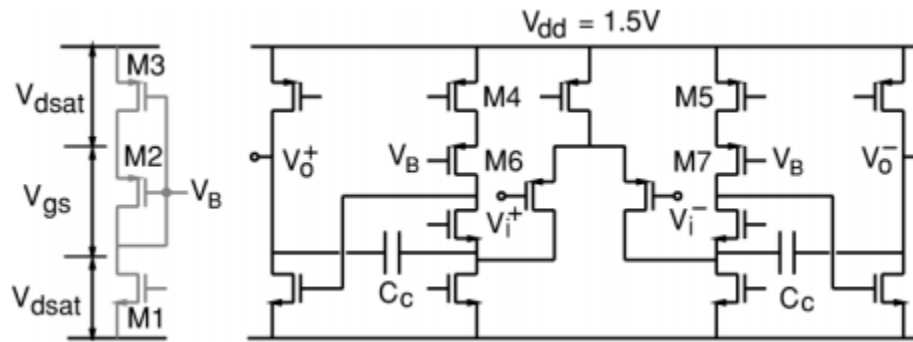

[Ref. 1]



 


[Ref. 2]

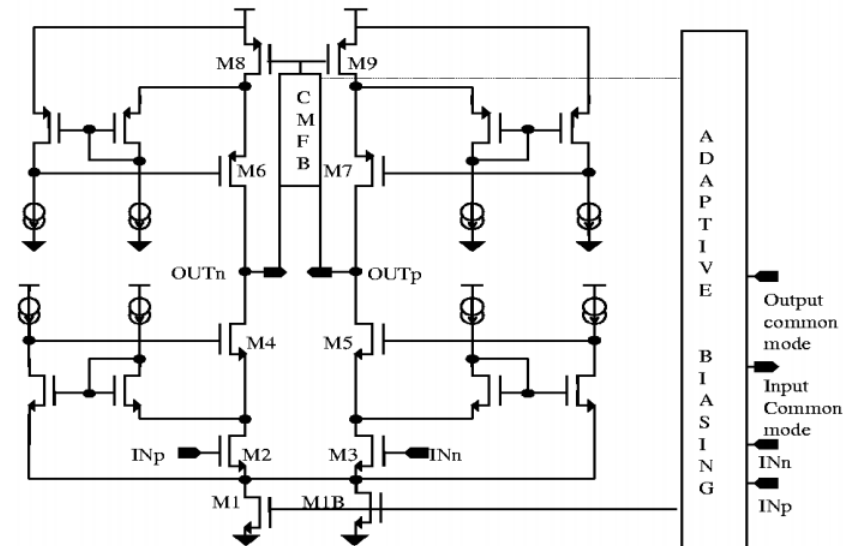

[Ref. 3]

Comparators

   


[Ref. 3]

MDAC


MDAC 2X Gain

B_1	B_0	D_0	D_1	D_2
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	X	X	X

Sub-ADC to DAC Bit Logic

 

[Ref. 2]

 

References

1. A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline analog-to-digital converter," *IEEE J. Solid-State Circuits*, vol. 34, pp. 599–606, May 1999
2. H. Ishii, K. Tanabe, and T. Iida, "A 1.0V 40mW 10b 100MS/s Pipeline ADC in 90nm CMOS," *IEEE Custom Integrated Circuits Conference*, pp. 10.5.1–10.5.4, 2005
3. M. Boulemlakher, "A 1.2V 4.5mW 10b 100MS/s Pipeline ADC in 65nm CMOS," *ISSCC*, pp. 250-251, 2008
4. M. E. Bayoumy, *MS Thesis, University of Texas, Austin*, A Study of 10-bit, 100Msps Pipeline ADC and the Implementation of 1.5-bit Stage, 2013
5. Overview of Pipelined ADC Chapter 13 from the book by M. Figueiredo et al., *Reference-Free CMOS Pipeline Analog-to-Digital Converters*, 2013