



University of California  
College of Engineering  
Department of Electrical Engineering  
and Computer Sciences

J. Rabaey

WeFr 2-3:30pm

We, April 22, 2:00-3:30pm

## EECS 141: SPRING 09—MIDTERM 2

<b>NAME</b>	Last	First
-------------	------	-------

<b>SID</b>	
------------	--

**Problem 1 (10):**

**Problem 2 (9):**

**Problem 3 (11):**

<b>Total (30)</b>	
-------------------	--

### PROBLEM 1: MOS TRANSISTORS (10 Points)

An MOS device can operate in one of the four regions:

- cut off;
- linear;
- saturation;
- velocity saturation.


Transistor parameters are:

NMOS:  $V_T = 0.3\text{V}$ ,  $V_{D,VSAT} = 0.3\text{V}$ ,  $k = \mu C_{OX} = 100\mu\text{A/V}^2$ ,  $\lambda = 0$ ,  $\gamma = 0$

PMOS:  $V_T = -0.3\text{V}$ ,  $V_{D,VSAT} = -0.5\text{V}$ ,  $k = \mu C_{OX} = -50\mu\text{A/V}^2$ ,  $\lambda = 0$ ,  $\gamma = 0$


Determine regions of operation of the devices shown below.

(1) (2 pts)

 


Device	$V_x$	Region of Operation
<b>M1</b>	<b>0.5V</b>	
	<b>0.1V</b>	

(2) (2 pts)

 


Device	Region of Operation
<b>M1</b>	
<b>M2</b>	

(3) (3 pts)

 

Device	Region of Operation
<b>M1</b>	
<b>M2</b>	


(4) (3 pts)

 

Device	Region of Operation
<b>M1</b>	
<b>M2</b>	
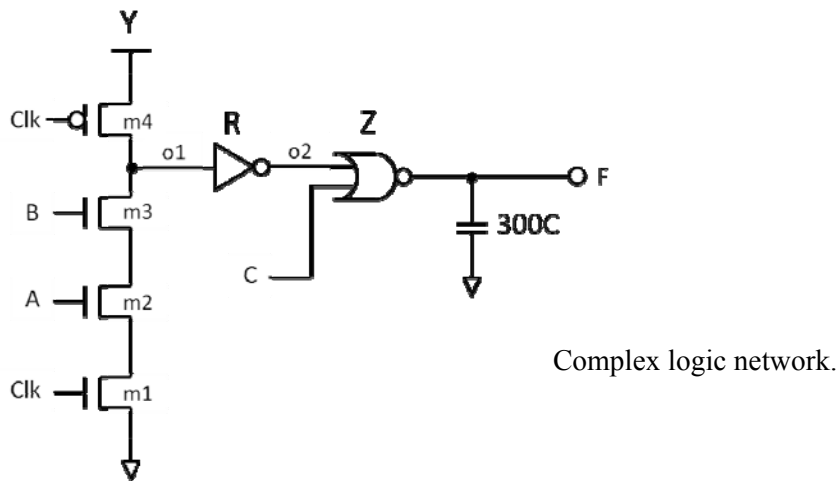
## PROBLEM 2 – Dynamic Logic (9 Points)

Given the logic network below that is composed of a dynamic CMOS gate Y, a static CMOS inverter gate R, and a static CMOS NOR gate Z:



- (1) Size the transistors of the first-stage dynamic CMOS gate Y such that the worst-case drive strength for all inputs is the same as a unit inverter (PMOS to NMOS ratio of 2/1). What is logical effort of Y for input A and B? (Freebee!) (1 pt)

$$m1=m2=m3=$$

$$m4=$$

$$LE_A = LE_B =$$

- (2) Determine the logic function F of the logic network in terms of input A, B, and C. (Another freebee!) (1 pt)

$$F=$$

- (3) It is reasonable to first assume that the critical path for the output F high-to-low transition is from the input A to the output F. Size the gate Y, R, and Z to minimize the propagation delay  $T_{HL}$  **from the input A to the output F**. Assume the input capacitance of the input A cannot exceed  $4C$ , where  $C$  is the input capacitance of a unit size inverter. (3 pts)

Y=

R=

Z=

- (4) Now let's turn to the output F low-to-high transition. Identify the critical path of the network for the output low-to-high transition and explain your choice. Calculate the propagation delay  $T_{LH}$  by using the same transistor sizes you found in (3). Assume  $\gamma = 1$ . (2 pts)

The critical path is

$$T_{LH} = \quad t_{p0}$$

(5) What are the activity factors of nodes o1, o2, and F if  $P(A=0) = P(B=0) = P(C=0) = 0.25$ ? (2 pts)


$$\alpha_{o1(0 \rightarrow 1)} =$$

$$\alpha_{o2(0 \rightarrow 1)} =$$

$$\alpha_{F(0 \rightarrow 1)} =$$
 
### PROBLEM 3: Wire Delay (11 points)

Consider the clock distribution network plotted below. Assume the following design parameters:  $R_d$  and  $C_d$  are the drive resistance and output capacitance of the inverters, and equal  $1\text{ k}\Omega$  and  $4\text{ fF}$ , respectively. You may assume that  $\gamma = 1$  (that is input and output capacitance of the inverter are identical). Wires are characterized by their sheet resistance and area capacitance  $r_w = 0.06\text{ }\Omega/\text{sq}$ ,  $c_w = 0.04\text{ fF}/\mu\text{m}^2$ . The fringing capacitance can be ignored. Each wire segment has a length  $L$  of  $5\text{ mm}$ , while its width  $W$  is kept as a variable. The load capacitance  $C_L$  equals  $10\text{ fF}$ .



- Derive an expression for the delay between nodes  $\text{Clk}_{\text{in}}$  and  $\text{Clk}_{\text{out}}$  as a function of the wire width  $W$ . Carefully identify each component of the delay.  
HINT: Think Elmore! (6 pts)

$t_p =$

- b. Derive the wire width  $W$  that minimizes the delay. (3 pts)

$W =$

- c. Check for each of the following statements if it is TRUE or FALSE or DOES NOT MATTER ( 2 Pts):

- The delay between Clkin and Clkout can be further reduced by partitioning the wires into shorter segments and introducing inverters in between.

TRUE ☐      FALSE ☐      DOES NOT MATTER ☐

- Introducing inverters along the length of the wire helps to reduce power consumption.

TRUE ☐      FALSE ☐      DOES NOT MATTER ☐

- Using Gold instead of Copper for the wires would reduce the delay.

TRUE ☐      FALSE ☐      DOES NOT MATTER ☐

- Suspending the wire in free space rather than surrounding them with SiO<sub>2</sub> would reduce the delay.

TRUE ☐      FALSE ☐      DOES NOT MATTER ☐