
EE288 Data Conversions/Analog Mixed-Signal ICs

Spring 2018

Lecture 11: Bootstrapped Clock Circuits Comparator

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259



Course Schedule – Subject to Change

Date	Topics
24-Jan	Course introduction and ADC architectures
29-Jan	Converter basics: AAF, Sampling, Quantization, Reconstruction
31-Jan	ADC dynamic performance metrics, Spectrum analysis using FFT
5-Feb	ADC & DAC static performance metrics, INL and DNL
7-Feb	OPAMP and bias circuits review
12-Feb	SC circuits review
14-Feb	Sample and Hold Amplifier - Reading materials
19-Feb	Flash ADC and Comparators: Regenerative Latch
21-Feb	Comparators: Latch offset, preamp, auto-zero
26-Feb	Finish Flash ADC
28-Feb	DAC Architectures - Resistor, R-2R
5-Mar	DAC Architectures - Current steering, Segmented
7-Mar	DAC Architectures - Capacitor-based
12-Mar	SAR ADC with bottom plate sampling
14-Mar	SAR ADC with top plate sampling
19-Mar	Midterm Review
21-Mar	Midterm exam
26-Mar	Spring break
28-Mar	Spring break
2-Apr	Pipelined ADC stage - comparator, MDAC, x2 gain
4-Apr	Pipelined ADC bit sync and alignment using Full adders
9-Apr	Pipelined ADC 1.5bit vs multi-bit structures
11-Apr	Fully-differential OPAMP and Switched-capacitor CMFB
16-Apr	Single-slope ADC
18-Apr	Oversampling & Delta-Sigma ADCs
23-Apr	Second- and higher-order Delta-Sigma Modulator.
25-Apr	Hybrid ADC - Pipelined SAR
30-Apr	Hybrid ADC - Time-Interleaving
2-May	ADC testing and FoM
7-May	Project presentation 1
8-May	Project presentation 2
14-May	Final Review
20-May	Project Report Due by 6 PM

← Bootstrap circuits
Comparator


*Midterm Exam dates
are approximate and
subject to change
with reasonable notice.

Clock Bootstrapping

  


- Constant gate overdrive voltage $V_{GS} = V_{DD}$ for the switch
- R_{on} is not dependent on V_{in} to the first order (body effect?)
- NMOS device only with less parasitic capacitance

Clock Bootstrapping

 

(a)

 


(b)

Clock Bootstrapping


Nakagome Charge Pump

 Y. Nakagome et al., "An experimental 1.5 V 64 Mb dram,"
IEEE J. Solid-State Circuits, vol. 26, pp. 465–472, Apr. 1991




Ref: A. M. Abo and P. R. Gray, "A 1.5-V, 10-bit, 14.3-MS/s CMOS pipeline ADC,"
IEEE Journal of Solid-State Circuits, vol. 34, issue 5, pp. 599-606, 1999.


Clock Bootstrapping ($\Phi=0$)

 

Clock Bootstrapping ($\Phi=1$)


 


Clock Bootstrapping

 


Another Clock Bootstrap Circuit

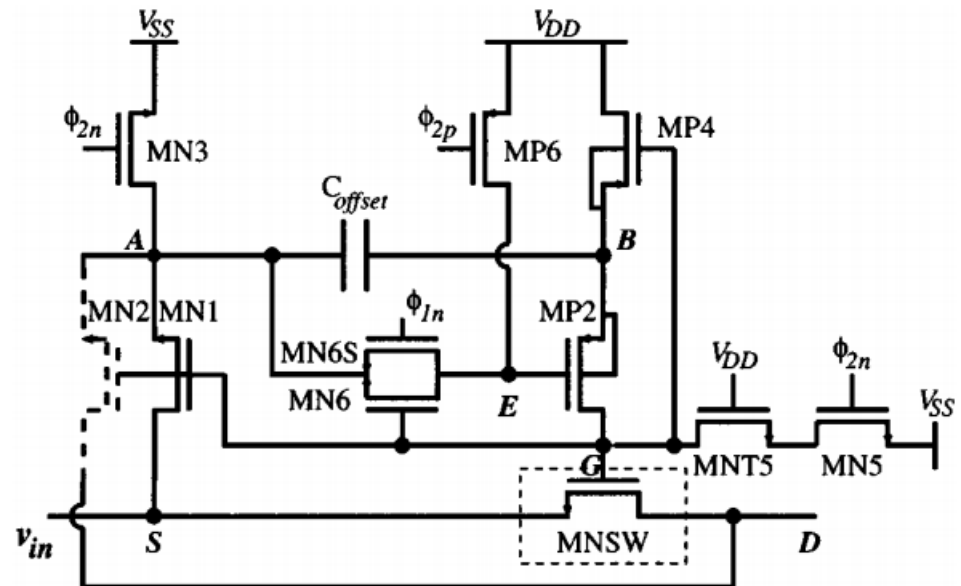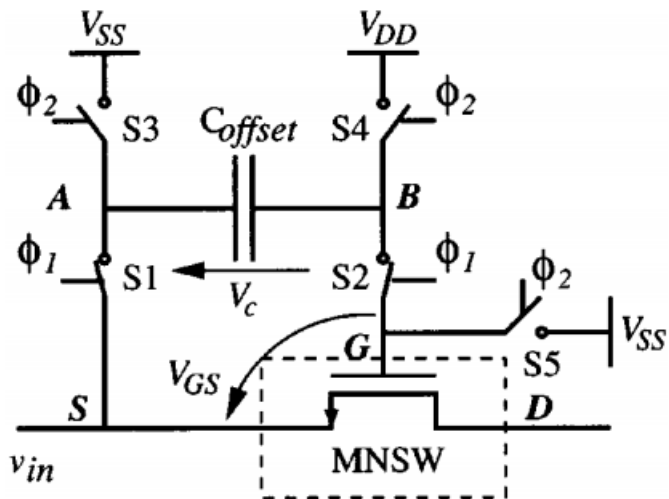Mohamed Dessouky and Andreas Kaiser, "Very Low-Voltage Digital-Audio $\Delta\Sigma$ Modulator with 88-dB Dynamic Range Using Local Switch Bootstrapping,"
IEEE J. Solid-State Circuits, vol. 36, pp. 349–355, Mar. 2001




Another Clock Bootstrap Circuit

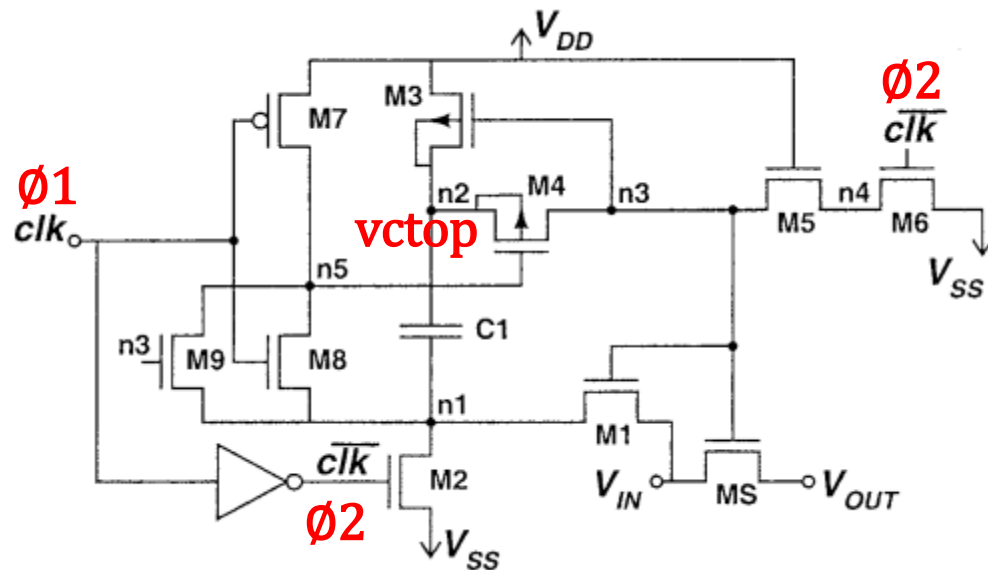M. Waltari, et.al., "A Self-Calibrated Pipeline ADC with 200 MHz IF-Sampling Frontend," *Analog Integrated Circuits and Signal Processing*, vol. 37, pp. 201–213, 2003




Cross-section of MOS Transistors

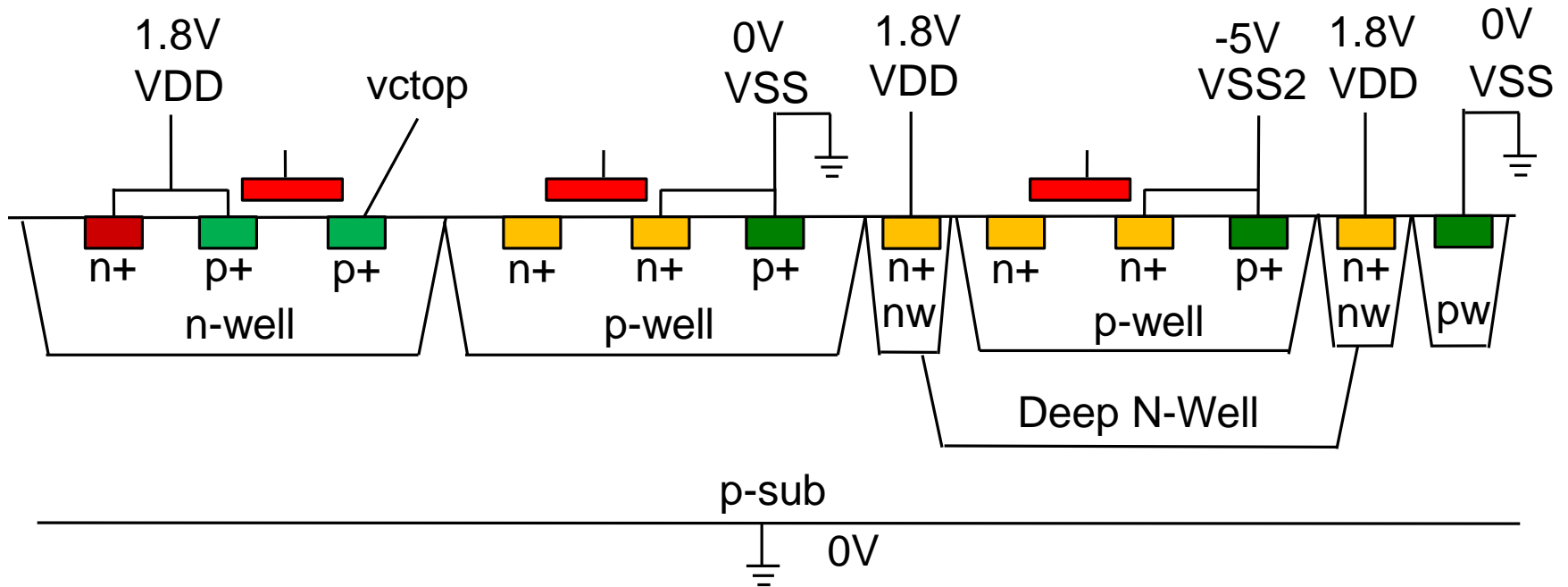


All pn junctions must be reverse-biased at all times.
If $v_{ctop} > VDD$, the n-well tab should be connected to vctop.


Test_Sample_Hold

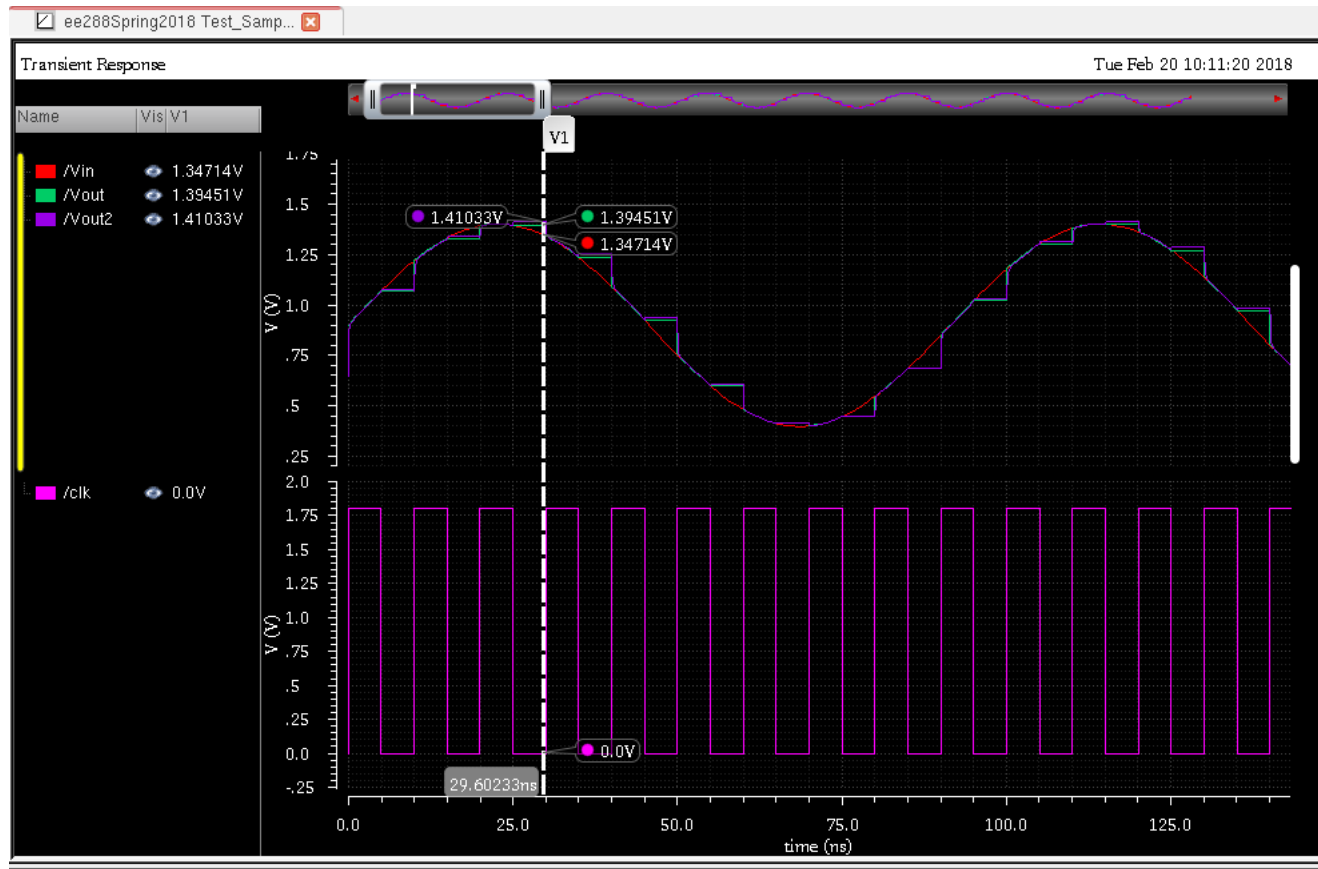


Ideal Switch Spectrum

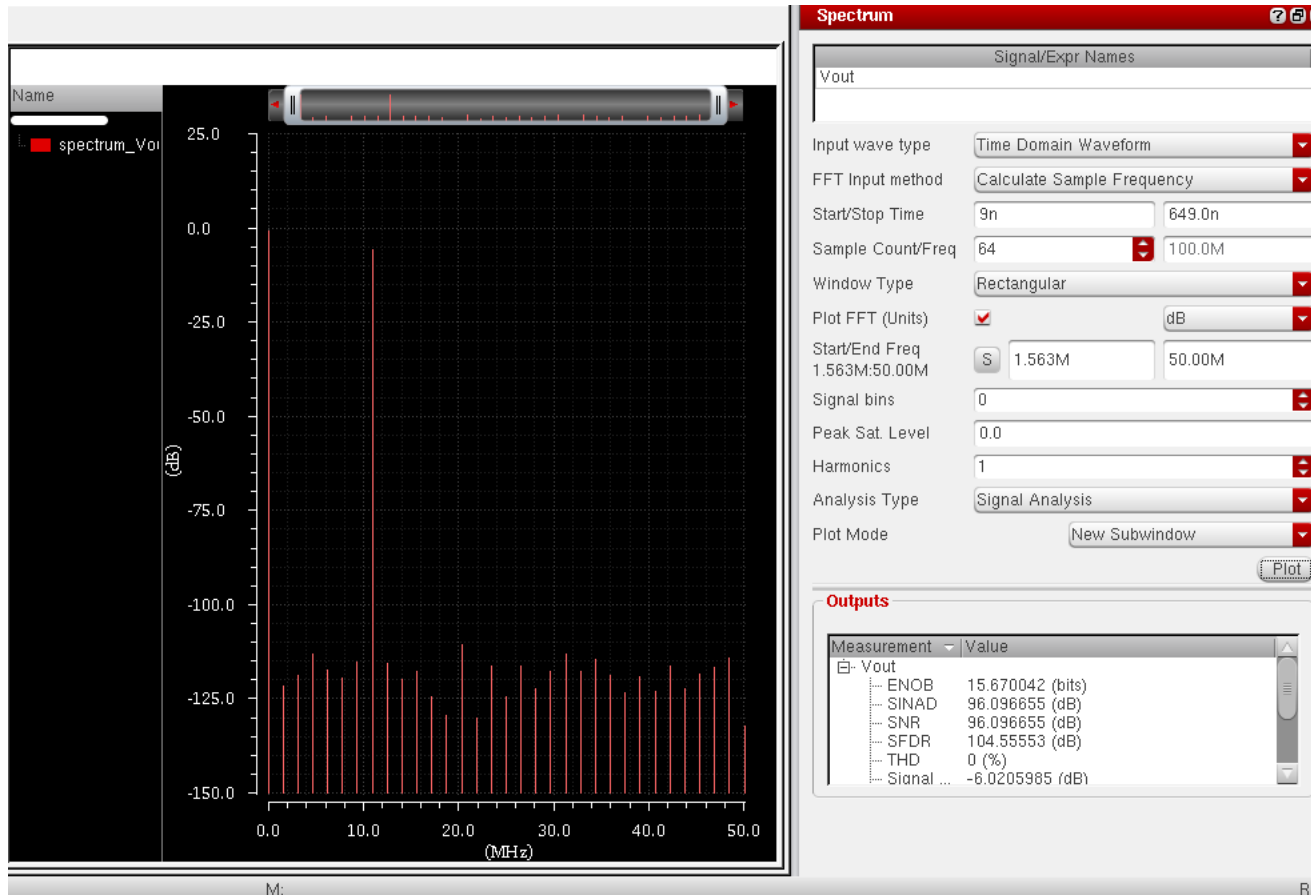


CMOS TG Spectrum

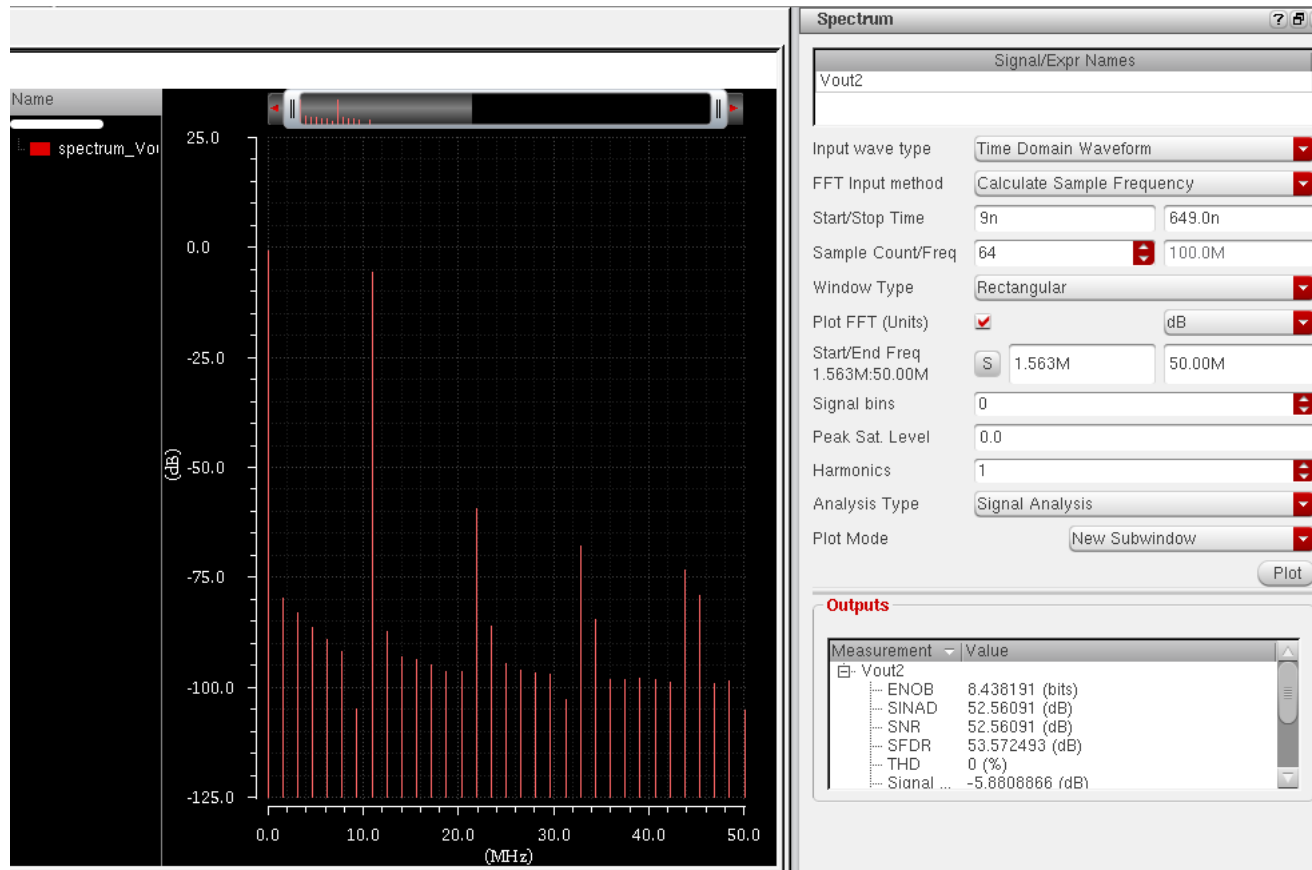



bootstrap_tb

 


Spectrum of Bootstrap Switch

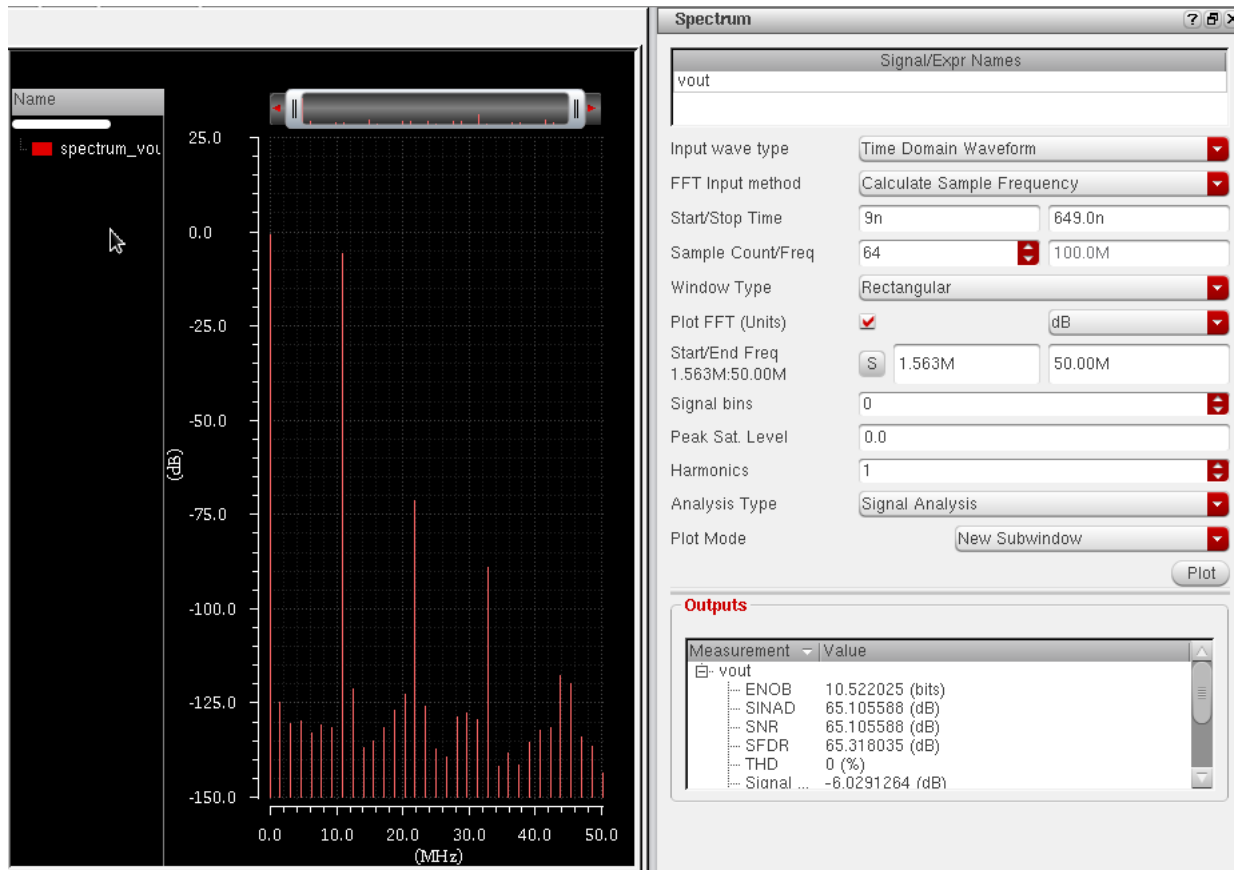

Non-overlapping clock

  


Non-overlapping clock

 


Comparator

Comparator Definition

 

Transfer characteristic
(ideal)

 



Circuit symbol

Detects the polarity of the analog input signal and produces a digital output (1 or 0) accordingly – threshold-crossing detector

Design Considerations

- Accuracy
 - Gain (resolution)
 - Offset
- Speed
 - Small-signal bandwidth
 - Settling time or delay time, slew rate
 - Overdrive recovery
- Power dissipation
- Input properties
 - Sampled data versus continuous time
 - Common-mode rejection
 - Input capacitance and linearity of input capacitance
 - Kickback noise

Gain Requirement

  

For 10-bit ADC, $V_{DD}=1.8V$, $FS=1V$, $LSB=1V/1024 \approx 1mV$


For $\frac{1}{2}$ LSB precision, we need

$$A_v = \frac{1.8V}{0.5 \cdot 1mV} \approx 3686 = 71dB$$

Implementation Options

- Considerations
 - Amplification need not be linear
 - Amplification need not be continuous in time, if comparator is used in a sampled data system
 - Clock signal will tell comparator when to make a decision
- Implementation options to be looked at
 - Single stage amplification
 - E.g. OTA or OpAmp in open loop configuration
 - Multi-stage amplification
 - E.g. cascade of resistively loaded differential pairs
 - Regenerative latch using positive feedback
 - E.g. cross coupled inverters

Using an OPAMP or OTA

 


f_u = unity gain frequency, f_o = - 3dB frequency


$$f_o = \frac{f_u}{A_v} = \frac{1\text{GHz}}{3686} = 271\text{kHz}$$

$$\tau_o = \frac{1}{2\pi f_o} = 0.59\mu\text{s} \quad \longrightarrow \quad \text{Too slow!}$$

Cascade of Open Loop Amplifiers

 

Cascade of Open Loop Amplifiers

 


In each stage: $\omega_u = \frac{g_m}{C_{gs}} \cong \text{const.}$ $A_0 = g_m R = \frac{\omega_u}{\omega_0}$ $\omega_0 = \frac{1}{RC} = \frac{\omega_u}{A_0}$

- Possible choices for a given, constant overall gain objective
 - Lots of stages with low gain
 - Only a few stages with moderate gain

Regenerative Latch

$t < 0$ setup initial condition $V_{10} - V_{20} = V_{d0}$


$t \geq 0$ enable positive feedback

 

$$\frac{dv_1}{dt} = \frac{i_1(t)}{C} = \frac{-g_m v_2(t)}{C}$$

$$\frac{dv_2}{dt} = \frac{i_2(t)}{C} = \frac{-g_m v_1(t)}{C}$$

$$\tau_u = \frac{C}{g_m}$$

 

$$\Rightarrow v_1(t) - v_2(t) = v_d(t) = v_{d0} \cdot e^{t/\tau_u}$$

$$\Rightarrow A(t) = \frac{v_d(t)}{v_{d0}} = e^{t/\tau_u}$$

Latch Gain

$A(\tau_d)$	τ_d/τ_u
10	2.3
100	4.6
1,000	6.9
10,000	9.2

For 10-bit, you need about 7τ