

---


# EE223 Analog Integrated Circuits

## Fall 2018

### Lecture 18: Frequency Response 2

Prof. Sang-Soo Lee  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)  
ENG-259

# Project Description

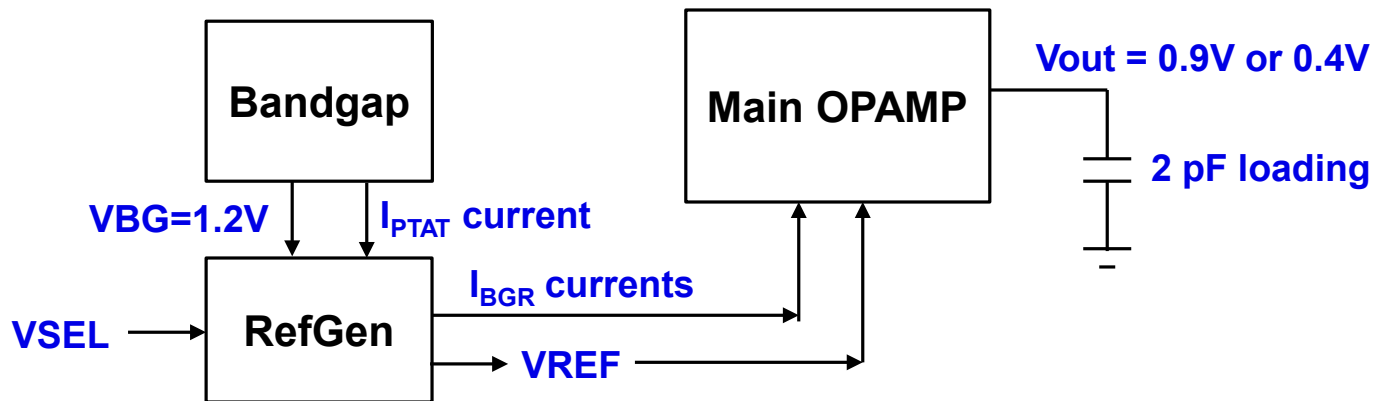


**VSEL pulse is used to create either  $V_{REF} = 0.9V$  or  $0.4V$ .  
See page 6 for the circuit diagram to implement this.**

## Main Circuit – High Gain OPAMP

## Auxiliary Circuits – Bandgap, RefGen

- $V_{DD}=1.8V$
- Device types available for the design
  - nmos2v, pmos2v, nmos2v\_nat, vnp5, resnsppoly, Ideal cap
- Results should meet the requirement over the following PVT corners
  - TT, 1.8V, 27C
  - SS, FF
  - 1.7V, 1.9V
  - -40C, 125C


# Reference Generator

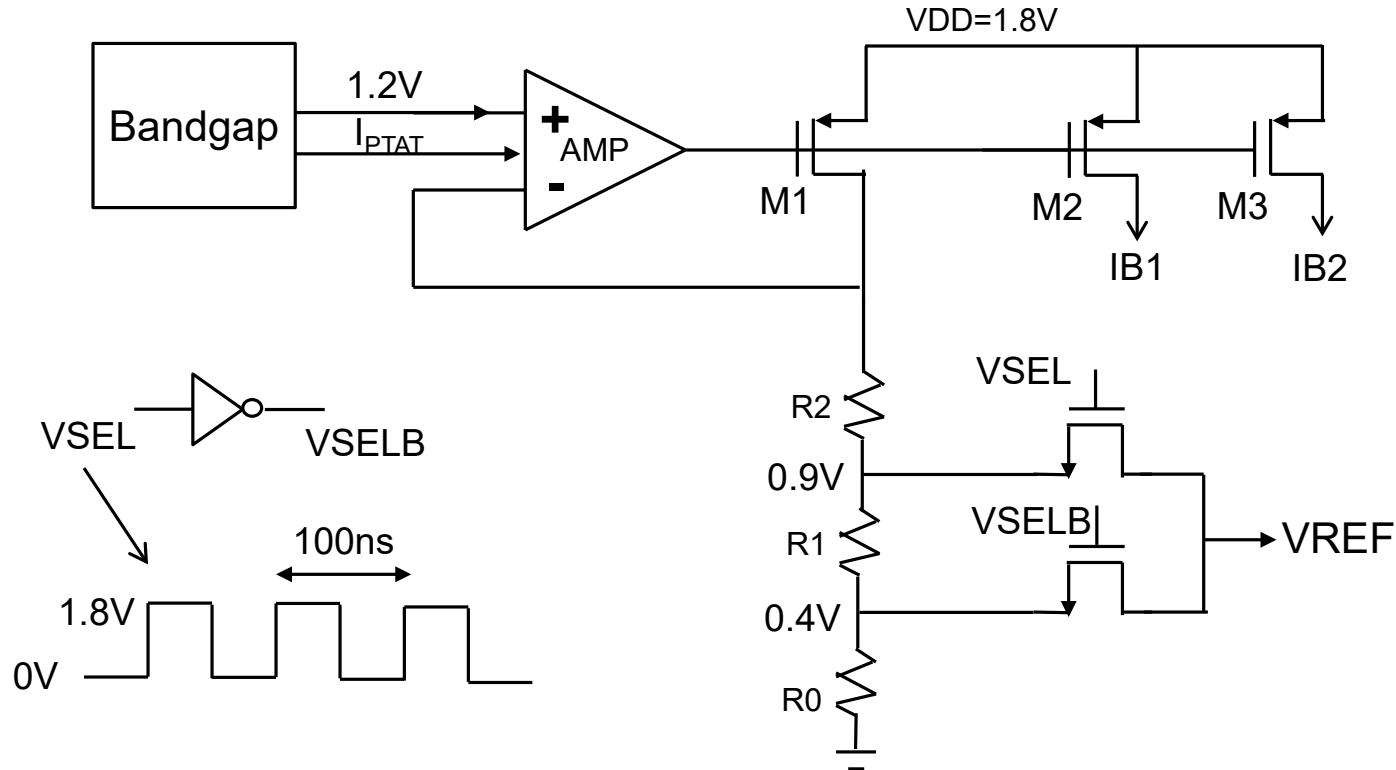

## Design Points


1. AMP and M1 will constitute a 2-stage RC compensated OPAMP.
2. AMP needs to be stable in unity gain configuration.
3.  $V_{REF}$  is the input voltage to the main OPAMP.
4.  $V_{SEL}$  is the input pulse you have to apply to measure the output of the main OPAMP.
5.  $IB1$  and  $IB2$  will supply the currents required in the Main Amplifier.

# Association of Poles with Nodes

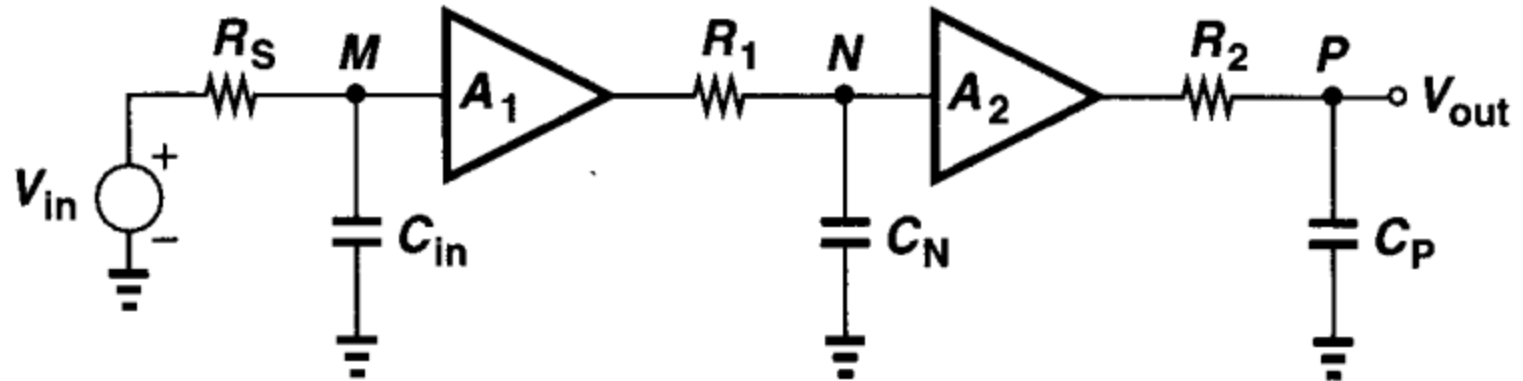


$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + R_S C_{in} s} \cdot \frac{A_2}{1 + R_1 C_N s} \cdot \frac{1}{1 + R_2 C_P s}$$

# Circuit with Floating Capacitor

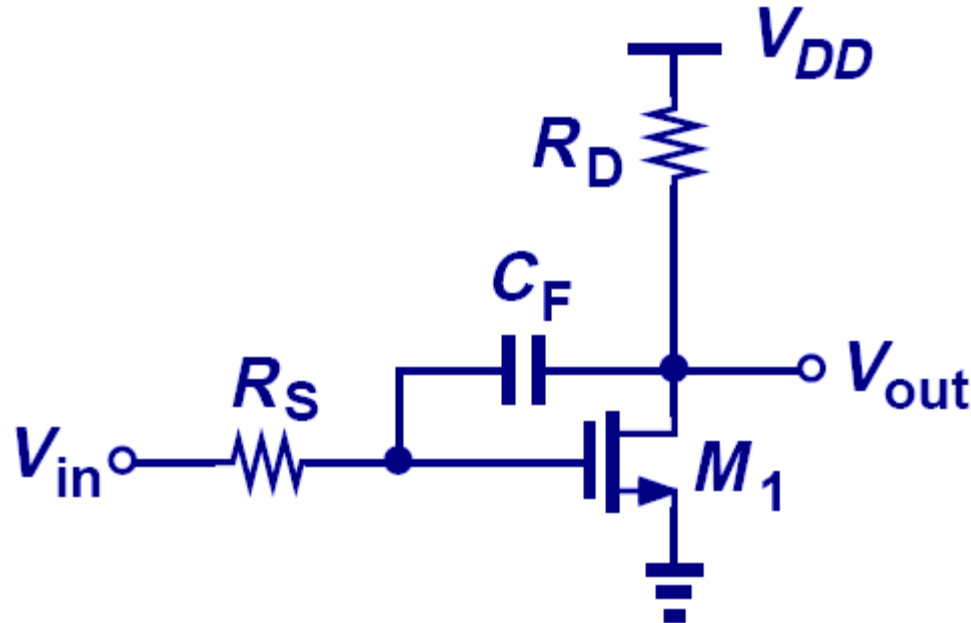

- The pole of a circuit is computed by finding the effective resistance and capacitance from a node to GROUND.
- The circuit above creates a problem since neither terminal of  $C_F$  is grounded.

# Miller's Theorem

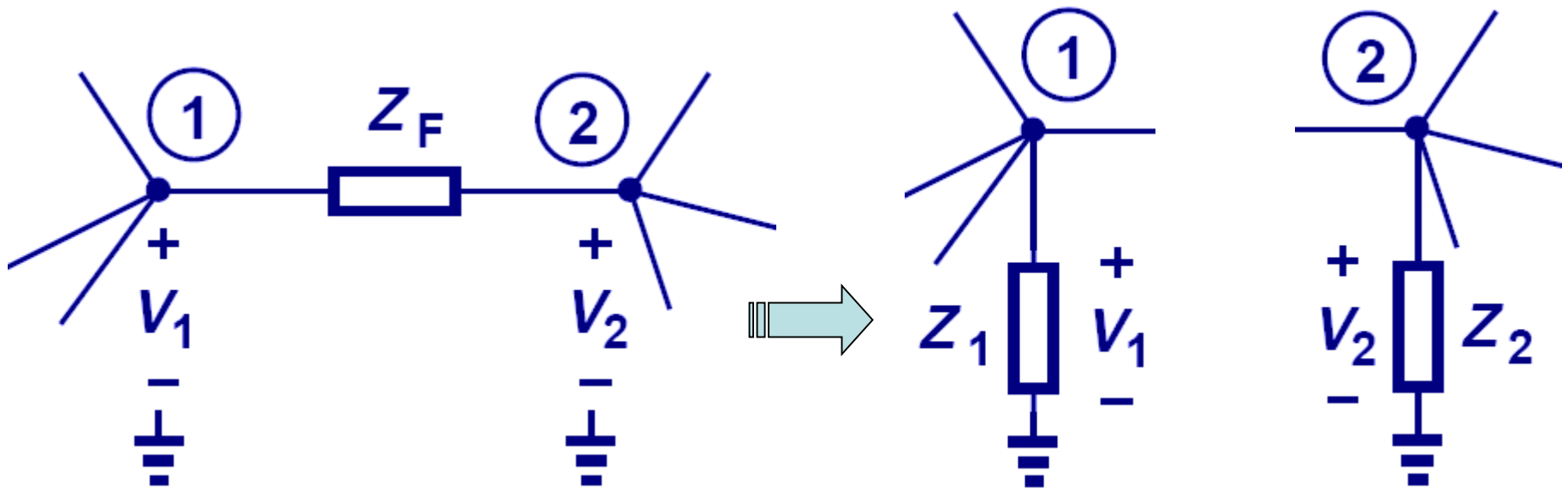


$$Z_1 = \frac{Z_F}{1 - A_v}$$

$$Z_2 = \frac{Z_F}{1 - 1/A_v}$$


➤ If  $A_v$  is the gain from node 1 to 2, then a floating impedance  $Z_F$  can be converted to two grounded impedances  $Z_1$  and  $Z_2$ .

# Miller Multiplication

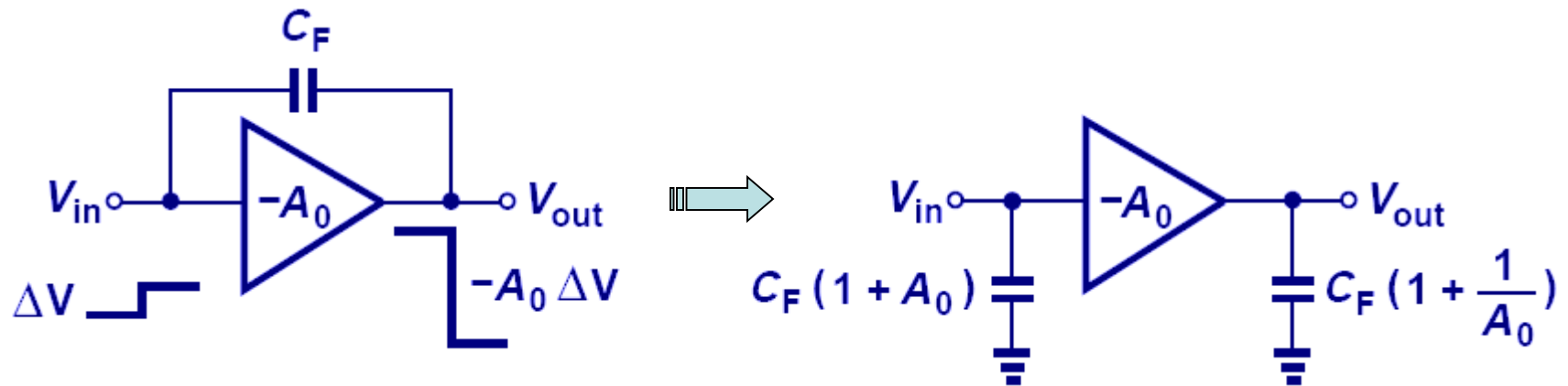

- With Miller's theorem, we can separate the floating capacitor. However, the input capacitor is larger than the original floating capacitor. We call this **Miller multiplication**.
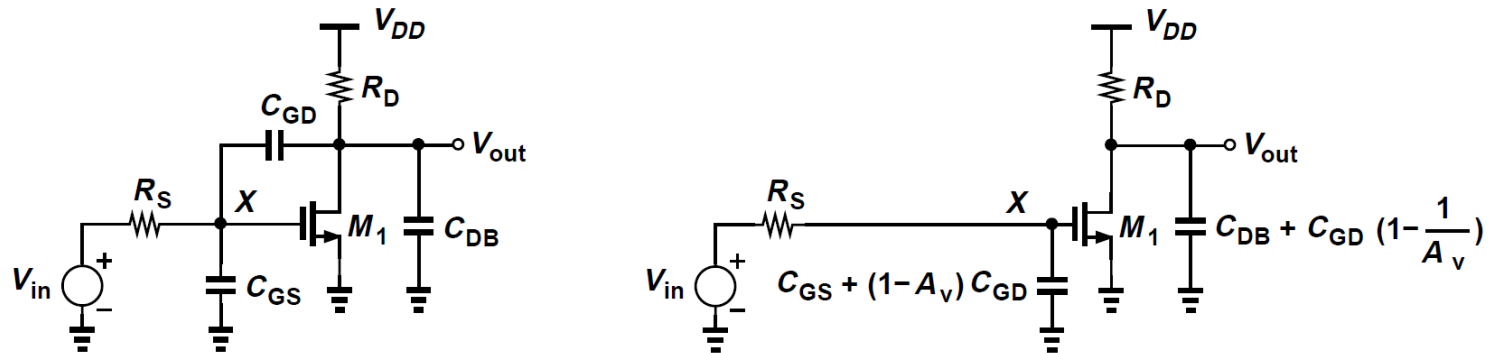
# CS Frequency Response using Miller's Theorem



- The magnitude of the “input” pole

$$\omega_{in} = \frac{1}{R_S[C_{GS} + (1 + g_m R_D)C_{GD}]}$$


- At the output node

$$\omega_{out} = \frac{1}{R_D(C_{DB} + C_{GD})}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$


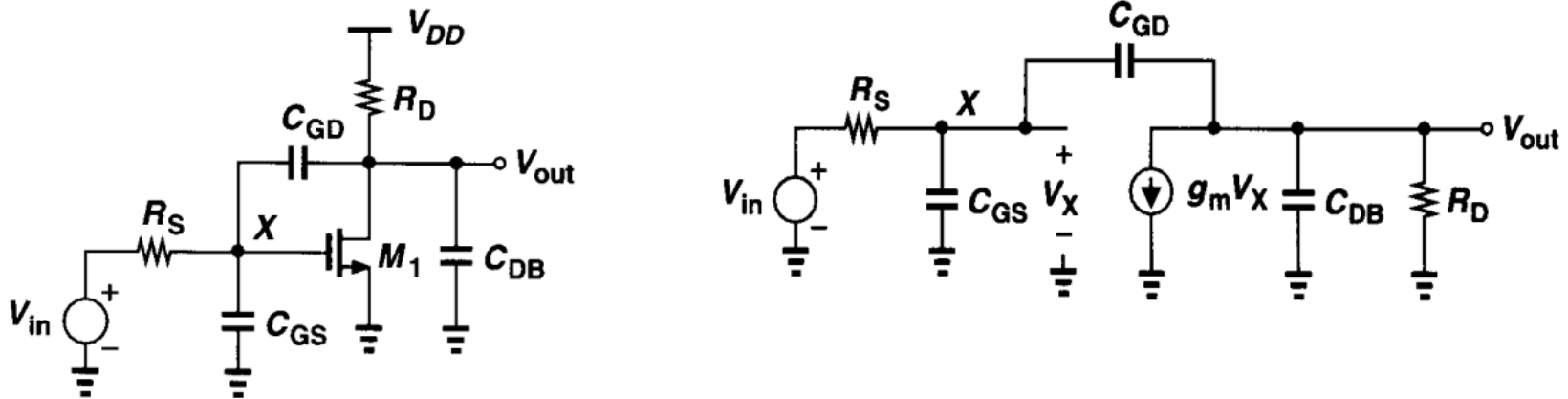
# Exact Analysis of Common Source Frequency Response



$$\frac{V_X - V_{in}}{R_S} + V_X C_{GS} s + (V_X - V_{out}) C_{GD} s = 0$$

$$(V_{out} - V_X) C_{GD} s + g_m V_X + V_{out} \left( \frac{1}{R_D} + C_{DB} s \right) = 0.$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD} s - g_m) R_D}{R_S R_D \xi s^2 + [R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})] s + 1}$$

$$\xi = C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB}$$

# Dominant Pole Approximation

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$




$$\begin{aligned} D &= \left( \frac{s}{\omega_{p1}} + 1 \right) \left( \frac{s}{\omega_{p2}} + 1 \right) \\ &= \frac{s^2}{\omega_{p1}\omega_{p2}} + \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1 = as^2 + bs + 1 \end{aligned}$$

If we assume  $|\omega_{p1}| \ll |\omega_{p2}| \rightarrow b = \frac{1}{\omega_{p1}}$

$$\omega_{p1} = \frac{1}{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})} \approx \omega_{in} = \frac{1}{R_S[C_{GS} + (1 + g_m R_D)C_{GD}]}$$
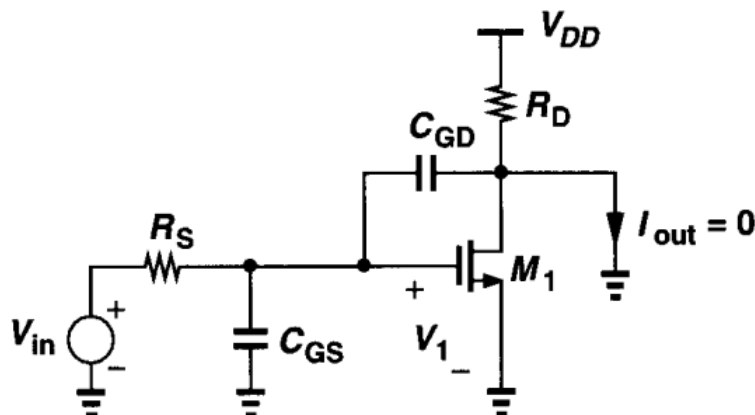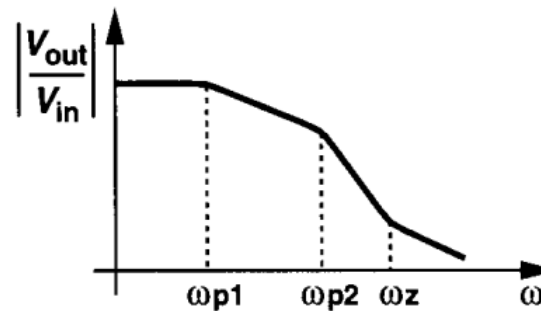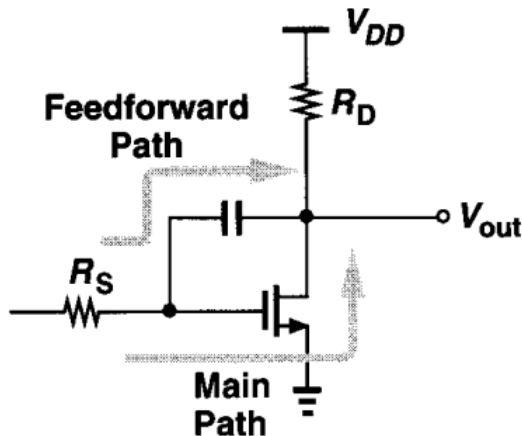
# Zero in the Transfer Function

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$





$$V_1 C_{GD} s_z = g_m V_1$$

$$s_z = +g_m / C_{GD}$$

**RHP Zero :**  
Capacitance between  
input and output  
of inverting stage

# Source Follower Frequency Response

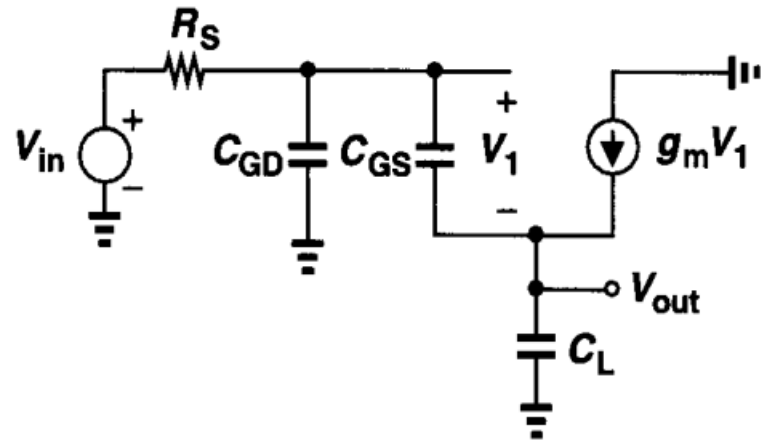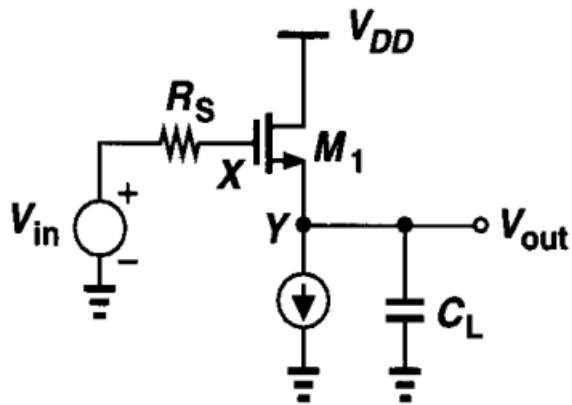

**LHP Zero :**  
**Capacitance between**  
**input and output**  
**of non-inverting stage**



$$V_1 C_{GS} s + g_m V_1 = V_{out} C_L s$$

$$V_1 = \frac{C_L s}{g_m + C_{GS} s} V_{out}$$

$$V_{in} = R_S [V_1 C_{GS} s + (V_1 + V_{out}) C_{GD} s] + V_1 + V_{out}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS} s}{R_S (C_{GS} C_L + C_{GS} C_{GD} + C_{GD} C_L) s^2 + (g_m R_S C_{GD} + C_L + C_{GS}) s + g_m}$$

# Source Follower Frequency Response

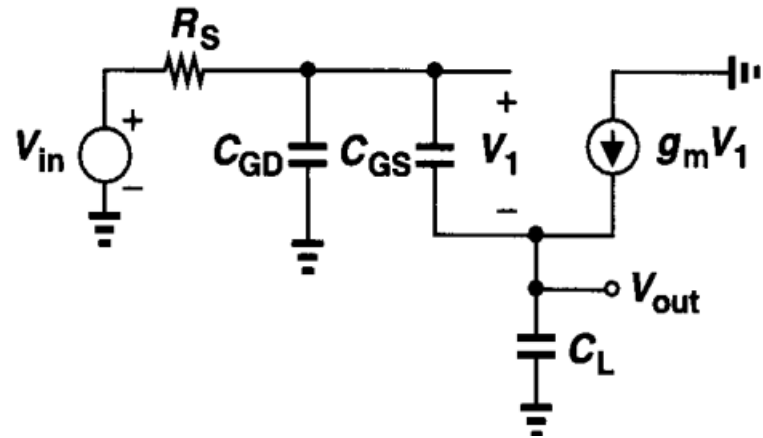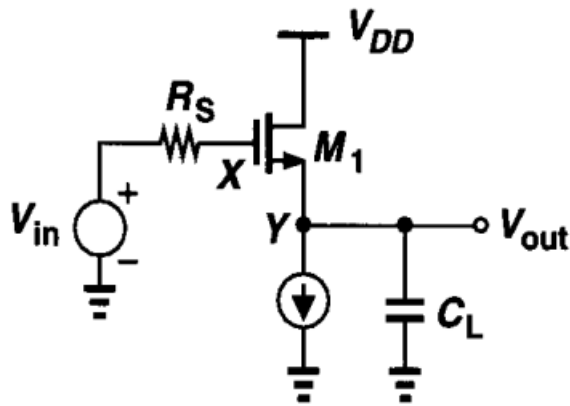


$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

$$\begin{aligned}\omega_{p1} &\approx \frac{g_m}{g_m R_S C_{GD} + C_L + C_{GS}} \\ &= \frac{1}{R_S C_{GD} + \frac{C_L + C_{GS}}{g_m}}\end{aligned}$$

If  $R_S = 0$ , then  $\omega_{p1} = g_m / (C_L + C_{GS})$

# Common Gate Stage

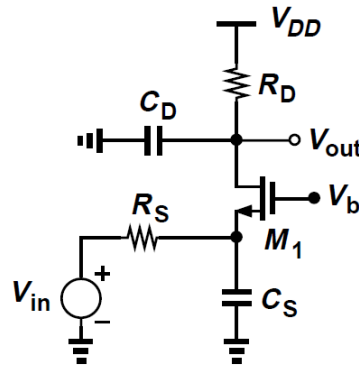


Common-gate stage at high frequencies

- A transfer function

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \frac{1}{\left(1 + \frac{C_S}{g_m + g_{mb} + R_S^{-1}}s\right) (1 + R_D C_D s)}$$

- No Miller multiplication of capacitances.
- Use when a low input impedance is required
- In cascode stages
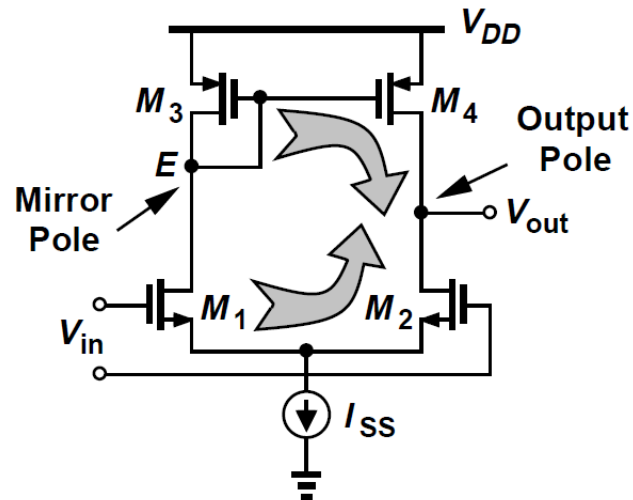
# Differential Pair with Active Loads - OTA




- How many poles does this circuit have?
- The pole associated with node E is called a “mirror pole.”

$$\frac{V_{out}}{V_{in}} = \frac{g_{mN}r_{ON}(2g_{mP} + C_Es)r_{OP}}{2r_{OP}r_{ON}C_EC_Ls^2 + [(2r_{ON} + r_{OP})C_E + r_{OP}(1 + 2g_{mP}r_{ON})C_L]s + 2g_{mP}(r_{ON} + r_{OP})}$$

$$\omega_{p1} \approx \frac{1}{(r_{ON} \parallel r_{OP})C_L} \quad \omega_{p2} \approx \frac{g_{mP}}{C_E}$$

# Differential Pair with Active Loads

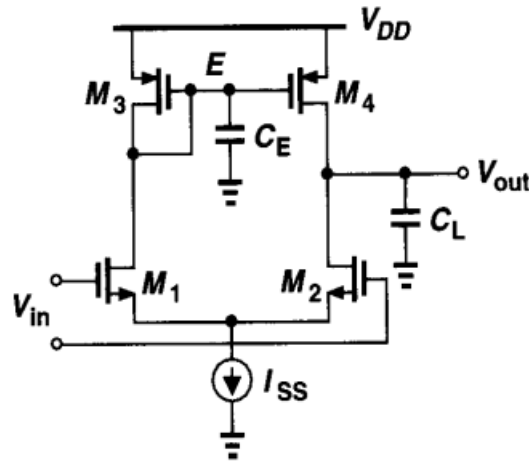


- A zero with a magnitude of  $2g_{mP}/C_E$  in the left half plane.
- The appearance of such a zero is due to
  - “slow path” (M1,M3 and M4 to Vout)  $A_0/[(1 + s/\omega_{p1})(1 + s/\omega_{p2})]$
  - “fast path” (M2 to Vout)  $A_0/(1 + s/\omega_{p1})$

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{A_0}{1 + s/\omega_{p1}} \left( \frac{1}{1 + s/\omega_{p2}} + 1 \right) \\ &= \frac{A_0(2 + s/\omega_{p2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}\end{aligned}$$



# Amplifier Gain-Bandwidth Trade-Offs

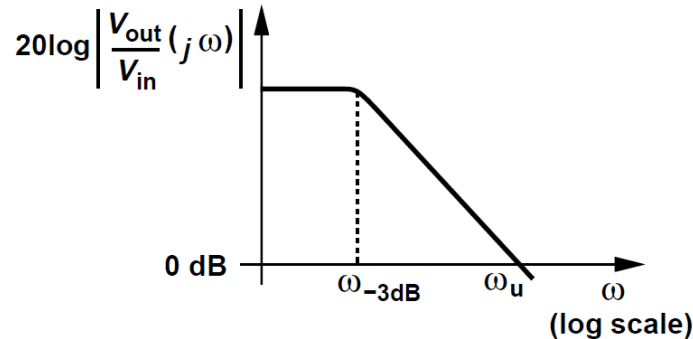

- We wish to maximize both the gain and the bandwidth of amplifiers.
- we are interested in both the 3-dB bandwidth,  $\omega_{-3\text{dB}}$ , and the “unity-gain” bandwidth,  $\omega_u$ .