
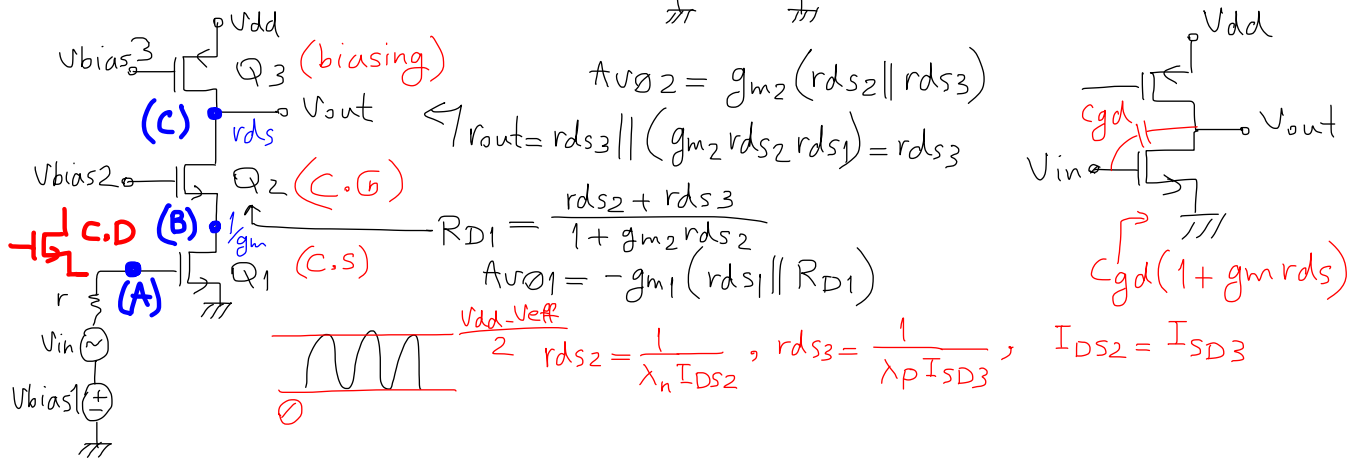


* Cascode Amplifier:

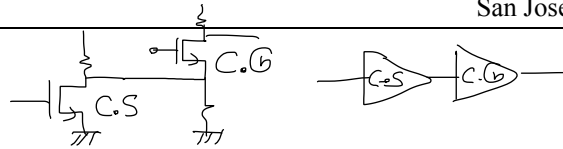

$$A_{v0} = A_{v01} \cdot A_{v02} = -g_{m1} \left(r_{ds1} \parallel \frac{r_{ds2} + r_{ds3}}{1 + g_{m2} r_{ds2}} \right) g_{m2} (r_{ds2} \parallel r_{ds3})$$

$$g_m r_{ds} \gg 1 \Rightarrow r_{ds} \gg \frac{1}{g_m}$$

$$= -2 g_{m1} (r_{ds2} \parallel r_{ds3})$$

$$\Rightarrow A_{v0} = -g_{m1} g_{m2} (r_{ds2} \parallel r_{ds3}) \left(r_{ds1} \parallel \frac{\frac{1}{\lambda_n} + \frac{1}{\lambda_p}}{\frac{1}{\lambda_n}} \times \frac{1}{g_{m2}} \right)$$

$$\Rightarrow A_{v0} = -g_{m1} (r_{ds2} \parallel r_{ds3}) \left[1 + \frac{\lambda_n}{\lambda_p} \right]$$

$$r_{ds} = \frac{1}{\lambda I_{DS}}$$

comparable to the gain of the common source amplifier

$$\tau_1 = r \cdot \left[C_{gs1} + \left(1 + \frac{g_{m1}}{g_{m2}} \left(1 + \frac{\lambda_n}{\lambda_p} \right) \right) C_{gd1} \right]$$

$C_{gs}, C_{gd}, C_{db}, C_{sb}$

$$\tau_2 = \left[r_{ds1} \parallel \frac{r_{ds2} + r_{ds3}}{1 + g_{m2} r_{ds2}} \right] \left[C_{gd1} + C_{db1} + C_{sb2} + C_{gs2} \right]$$

$$\tau_3 = \left[(r_{ds1} + r_{ds2} + g_{m2} r_{ds2} r_{ds1}) \parallel r_{ds3} \right] (C_{gd2} + C_{db2} + C_{gd3} + C_{db3})$$


$$\omega_{P1} = \frac{1}{\tau_1 + \tau_2 + \tau_3} \approx \frac{1}{\tau_3}$$

bandwidth of the cascode amplifier is larger than the bandwidth of the common source amplifier

* For Common Source Amplifier:

$$\tau = r \left[C_{gs1} + \left(1 + g_{m1} (r_{ds1} \parallel r_{ds2}) \right) C_{gd1} \right] + (r_{ds1} \parallel r_{ds2}) \left[C_{gd1} + C_{db1} + C_{gd2} + C_{db2} + C_L \right]$$

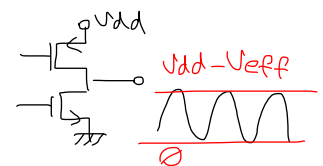$\underbrace{\hspace{10em}}_{C_{in}} \qquad \qquad \qquad \underbrace{\hspace{10em}}_{C_{out}}$







* Comparison of cascode and C.S. amplifiers:


cascode
same gain
slightly higher bandwidth
better isolation

C.S.
higher swing

* Folded cascode amplifiers:

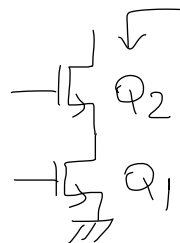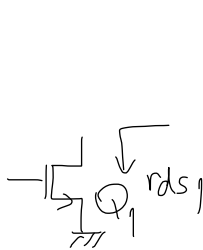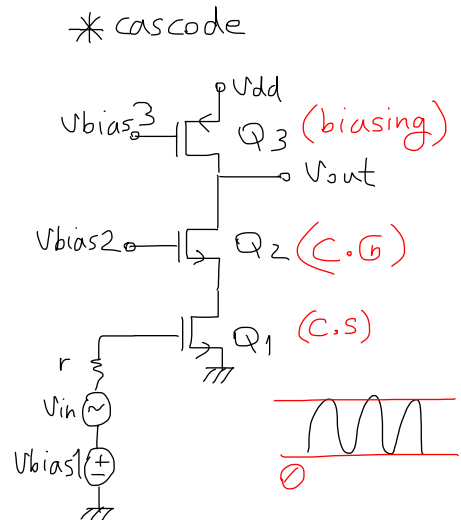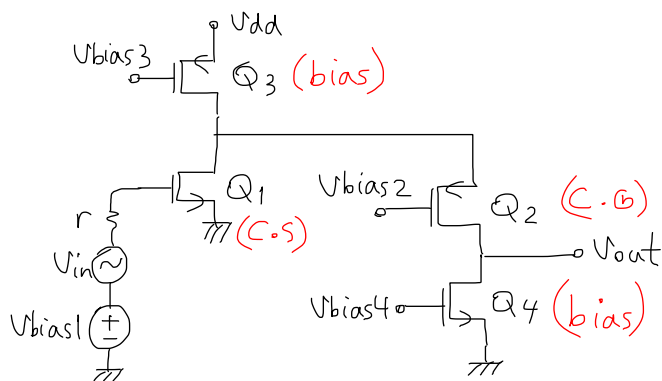

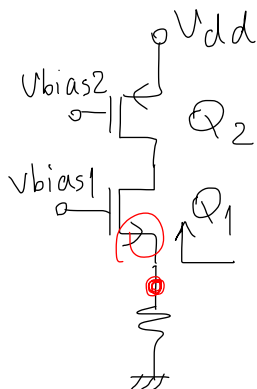
$$g_{m2}r_{ds2}r_{ds1} + r_{ds2} + r_{ds1}$$




$$X \quad g_{m1}r_{ds1}r_{ds2} \quad \frac{r_{ds1} + r_{ds2}}{1 + g_{m1}r_{ds1}}$$
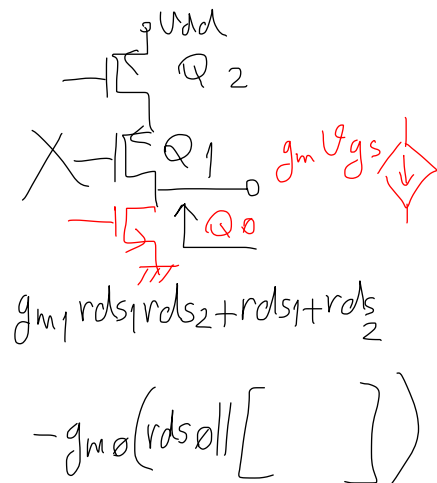
$$g_s \rightarrow \text{triangle} \rightarrow s_d$$






$$g_{m1}r_{ds1}r_{ds2} + r_{ds1} + r_{ds2}$$




$$-g_{m0}(r_{ds0} || [\quad])$$

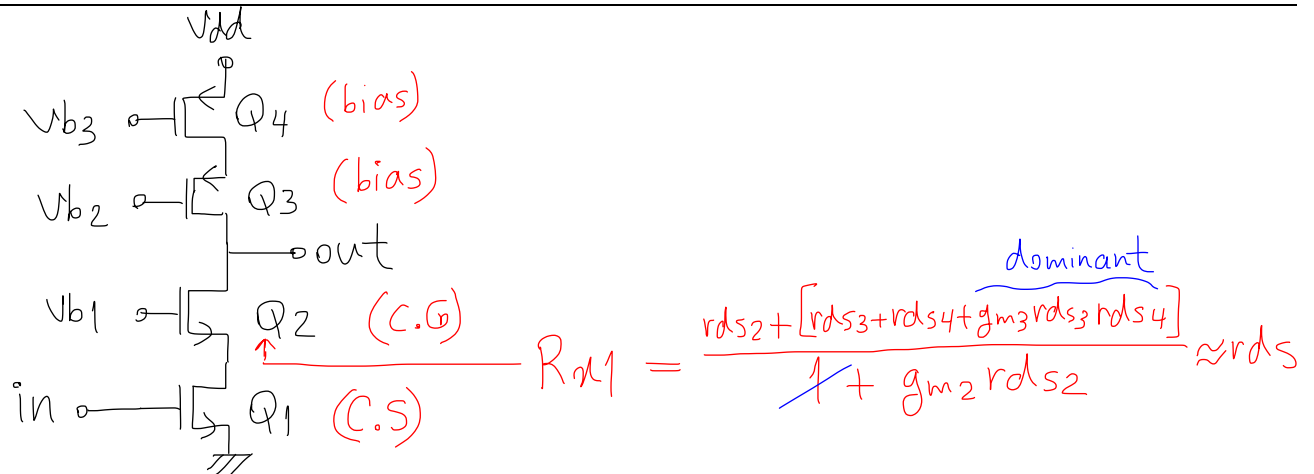




$$A_{v01} = -g_{m1}(r_{ds1} \parallel R_{n1}) \approx -g_m \frac{r_{ds}}{2}$$

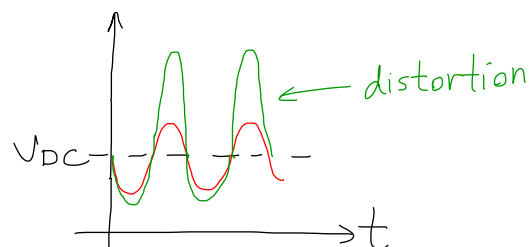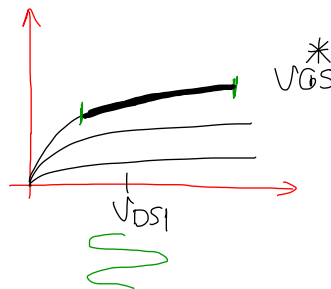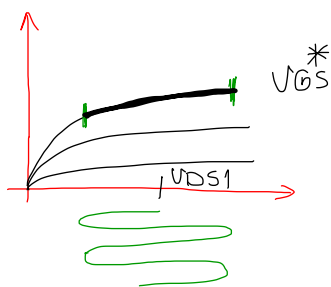
$$A_{v02} = g_{m2}(r_{ds2} \parallel [g_{m3} r_{ds3} r_{ds2} + r_{ds2} + r_{ds3}]) = g_{m2} r_{ds2}$$



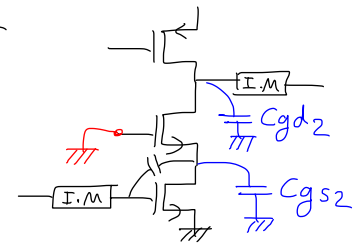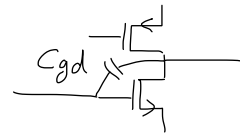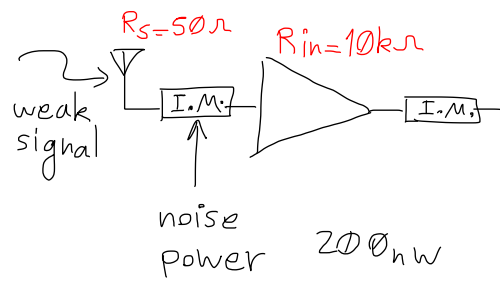


signal power > noise power

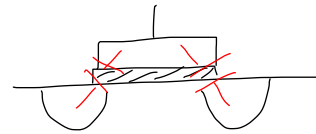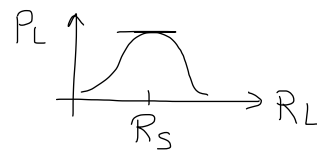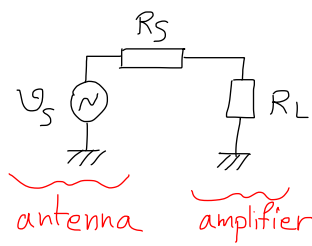

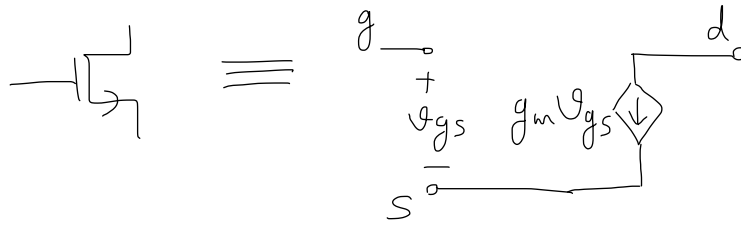

input		output	
✓ g		d	→ C.S
✓ s		d	→ C.G
✓ g		s	→ C.D
X d		g, s	
X s		g	
✓ C.S + C.G			
X C.S + C.D			

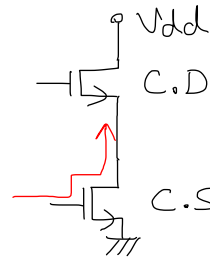

C.S	S.D.	Cascode C.S (n-type) , C.G (n-type)
C.D		folded-cascode C.S (n-type), C.G (p-type)
C.G		diff-pair (n-type)