

Chapter 5. Transceiver Architecture

B. Razavi, *RF Microelectronics*, Prentice Hall

2008-2 RF IC 공학

범 진 욱

서강대학교 전자공학과

Microelectronics Lab.

Contents

5.1 General Considerations

5.2 Receiver Architectures

- 5.2.1 Heterodyne Receivers
- 5.2.2 Homodyne Receivers
- 5.2.3 Image-Rejection Receivers
- 5.2.4 Digital-IF Receivers
- 5.2.5 Subsampling Receivers

5.3 Transmitter Architectures

- 5.3.1 Direct-Conversion Transmitters
- 5.3.2 Two-Step Transmitters

5.4 Transceiver Performance Tests

5.5 Case Studies

- 5.5.1 Motorola's FM Receiver
- 5.5.2 Philips' Pager Receiver
- 5.5.3 Philips' DECT Transceiver
- 5.5.4 Lucent Technologies' GSM Transceiver
- 5.5.4 Philips' GSM Transceiver

General Considerations

☐ Constraints

- Limited spectrum allocated
 - ☐ 30kHz in IS-54, 200kHz in GSM
 - ☐ Limited rate of information : require appropriate coding, compression, bandwidth efficient modulation


☐ Role of transmitters (Tx) and receivers (Rx)

- Tx
 - ☐ narrow-band modulation, amplification, filtering to avoid leakage to adjacent channels
- Rx
 - ☐ Antenna matching
 - ☐ Desired channel selection
 - ☐ Undesired signal rejection
 - ☐ Amplification
 - ☐ Demodulation
 - ☐ Error detection and/or correction
 - ☐ Information conditioning and output

General Considerations – Cont.


□ Difficulty of interference rejection

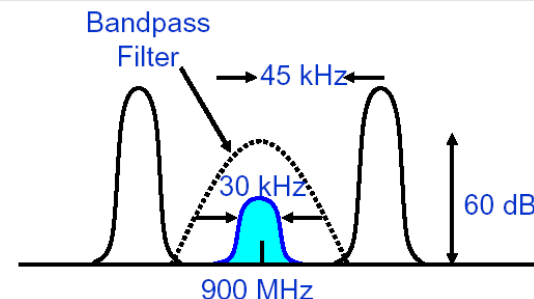- Example: 900 MHz, 30 kHz BW channel rejection at 60 kHz
- Require extremely high-Q Filter
- Typically high Q filter has high insertion loss



□ Band and channel

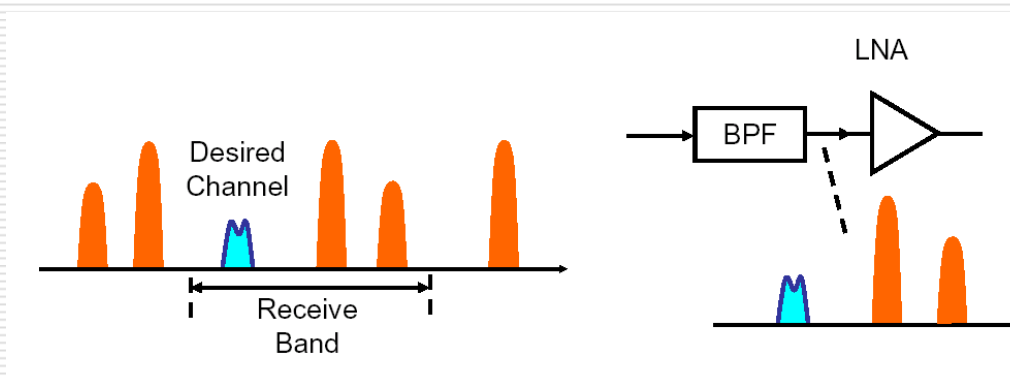- Band: entire spectrum of a standard (25 MHz in GSM)
- Channel: signal BW of only one user (200 kHz in GSM)
- Band selection




Front-End Band Pass Filter (BPF)

□ Front-end BPF

- Finite transition bandwidth
- out-of-band rejection is critical (~ 30 dB)
- Higher out-of-band rejection
 - Means higher in-band loss
 - Higher power amp power loss
- Loss in BPF
 - 2 dB of 1 W is 370 mW

□ Choice of BPF filter

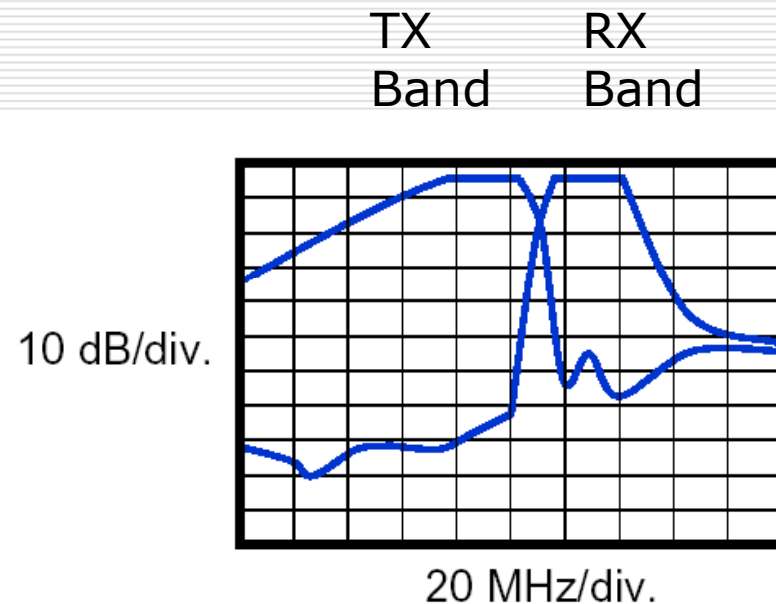
- Trade-off between out-of-band rejection and in-band loss
- In-band loss being the more critical parameter
- Practical front-end BPF can only select band



Linearity

□ Linearity

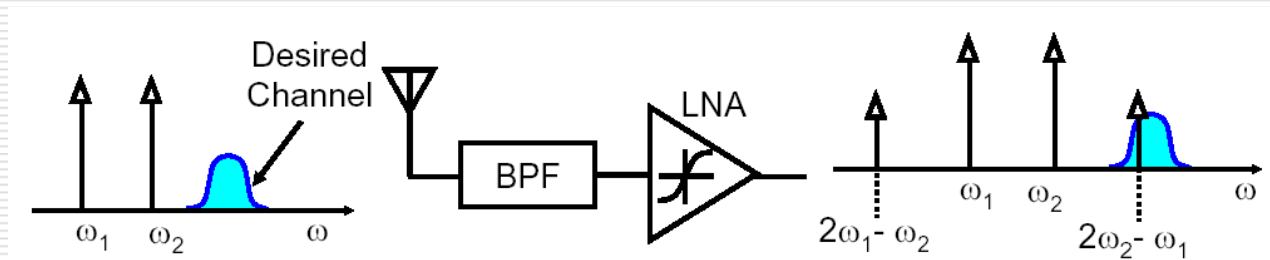- IM3 product of in-band interferers may fall in the desired channel
 - IIP3 of each stage must be sufficiently high
- Nonlinearity is important even if the signal carries information only in phase or frequency
 - Zero-crossing is corrupted by IM product




□ Supply voltage rejection

- PA periodically turns on and off to save power
- Large current drawn by PA and finite output impedance of battery
→ V_{cc} fluctuation and noise
- Require noise immunity and supply rejection of the building blocks

Dynamic Range

- **Required DR for the received signal is typically greater than 100dB**
 - Input range minimum $\sim \mu\text{V} \rightarrow$ Low noise, low cross talk required
- **1W PA and 30dB out-of-band attenuation duplexer**
 - 1 W PA \rightarrow 20 V peak to peak
 - Leakage to Rx path $\sim -26\text{dBm}$ ($= 30\text{mVpp}$) at the LNA input
 - Desensitization of LNA ($P_{1\text{dB}} \sim -25\text{dBm}$) and mixer
 - TDD(NADC & GSM) avoids this by offsetting transmit and receive time slots

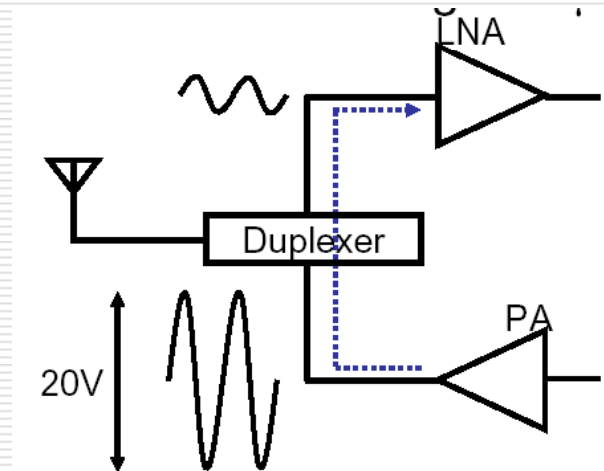

- With a large dynamic range
 - Automatic Gain Control (AGC)

Contents

5.1 General Considerations

5.2 Receiver Architectures

- 5.2.1 Heterodyne Receivers
- 5.2.2 Homodyne Receivers
- 5.2.3 Image-Rejection Receivers
- 5.2.4 Digital-IF Receivers
- 5.2.5 Subsampling Receivers

5.3 Transmitter Architectures

- 5.3.1 Direct-Conversion Transmitters
- 5.3.2 Two-Step Transmitters

5.4 Transceiver Performance Tests

5.5 Case Studies

- 5.5.1 Motorola's FM Receiver
- 5.5.2 Philips' Pager Receiver
- 5.5.3 Philips' DECT Transceiver
- 5.5.4 Lucent Technologies' GSM Transceiver
- 5.5.4 Philips' GSM Transceiver

Heterodyne Receivers

- ❑ **Signal band is translated to much lower frequency**

- ❑ **Background**

- Filtering a narrow channel that is centered at high frequency and is accompanied by large interferers demands prohibitively high Q

- Tradeoff between the filter loss and Q

- ❑ **Simple heterodyne down conversion**

- Mixer (ω_0) : a multiplier

- ❑ converts the signal(ω_1) to

- $\omega_2 = |\omega_0 - \omega_1|$ (downconversion) or $\omega_0 + \omega_1$

- ❑ High-side injection : $\omega_0 > \omega_1$



- ❑ Low-side injection : $\omega_0 < \omega_1$

- LPF removes high frequency signal


- LNA precedes due to the mixer's high NF to lower NF

- ω_0 (ω_{LO}) : generated by local oscillator

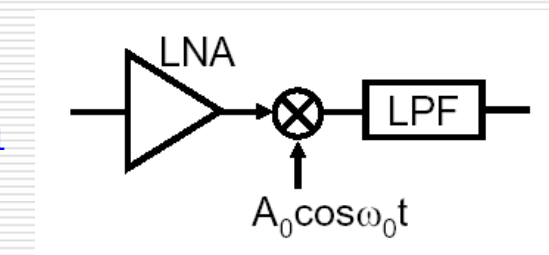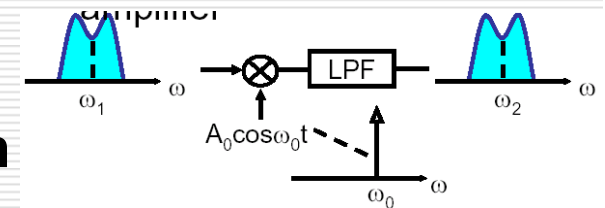- ω_2 (ω_{IF}) : called intermediate frequency (IF)



Problem of Image

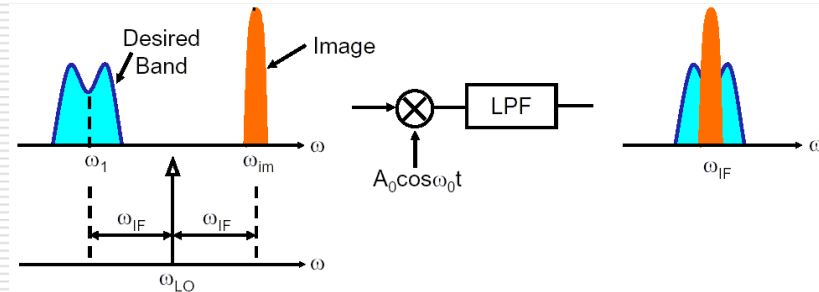

- Signal at $\omega_1 = \omega_{LO} - \omega_{IF}$ and image at $\omega_{im} = \omega_{LO} + \omega_{IF}$ translate to same frequency
- Image power may be much higher than that of desired signal

□ Image rejection required

□ Methods of image rejection

- Image rejection filter before mixer
- Image-reject architecture
 - Hartley architecture
 - Weaver architecture

Image Rejection

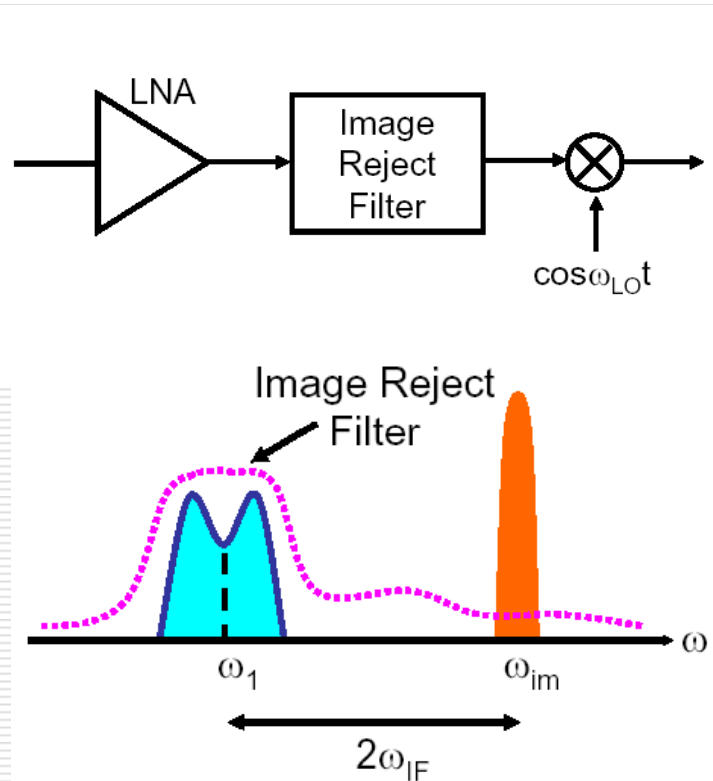


Image-reject (IR) filter

- Small loss in desired band
- Large attenuation in image band

Drawback of heterodyning by IR filter

- IR filter : usually passive, external component
 - 50ohm impedance
- Require 50ohm output impedance for LNA
 - Need more severe trade-off between gain, NF, stability, and power dissipation


ω_{IF}

□ Comparison of high IF and low IF

- High IF: minimum image signal, but poor channel selection
- Low IF: great suppression of nearby interferers, but poor image rejection
- trade off between image rejection and channel selection (sensitivity-since image degrades the sensitivity of the receiver – and selectivity)

□ Choice of ω_{LO}

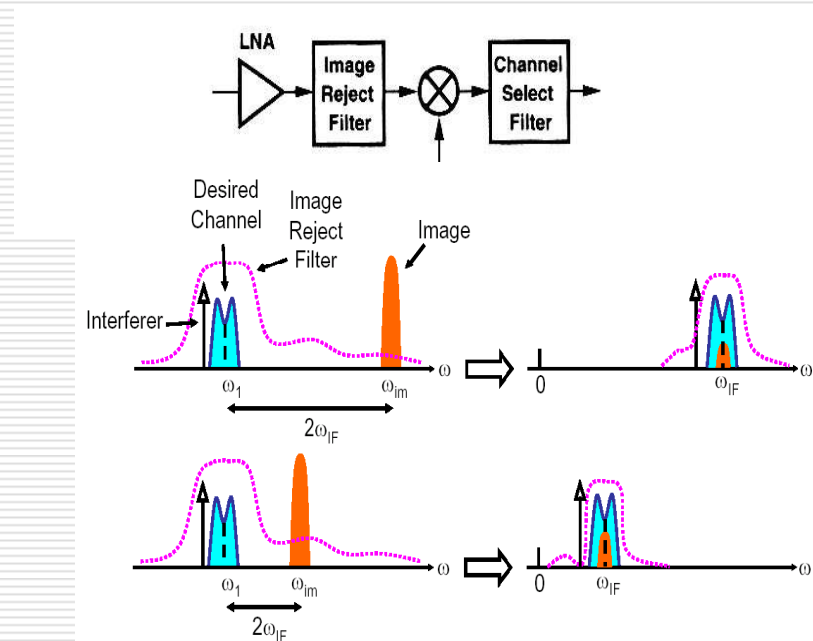- High-side injection $\omega_{LO} > \omega_{RF}$
- Low-side injection $\omega_{LO} < \omega_{RF}$
- ω_{LO} determined to avoid noise from image band



Problem of half IF




□ Problem of half IF

■ Case 1



- If $(\omega_{IN} + \omega_{LO})/2$ experience 2nd-order distortion by LNA $\rightarrow (\omega_{IN} + \omega_{LO})$
- LO contains significant 2nd-order harmonics $> 2 \omega_{LO}$ then
- $|(\omega_{IN} + \omega_{LO}) - 2 \omega_{LO}| = \omega_{IF}$

■ Case 2

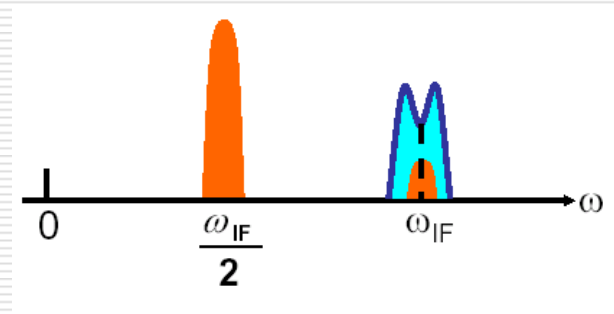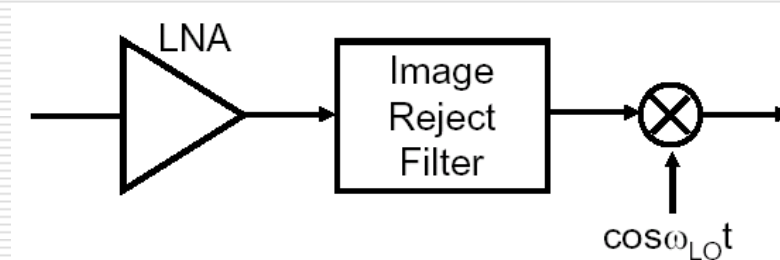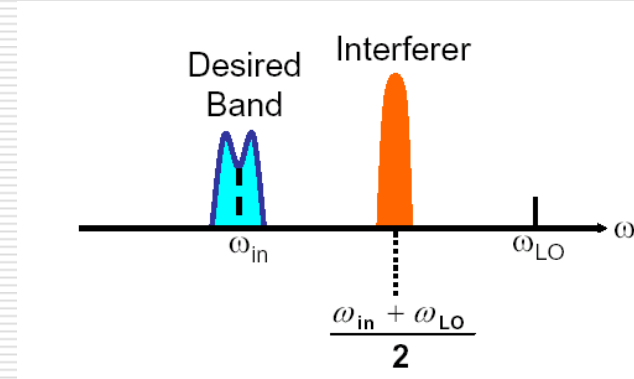- If $(\omega_{IN} + \omega_{LO})/2$ down converts to $\omega_{IF}/2$
- And 2nd-order distortion in the IF band (ex: IF amp), then
- They fall into band of interest $2 * \omega_{IF}/2 = \omega_{IF}$



Dual-IF Topology

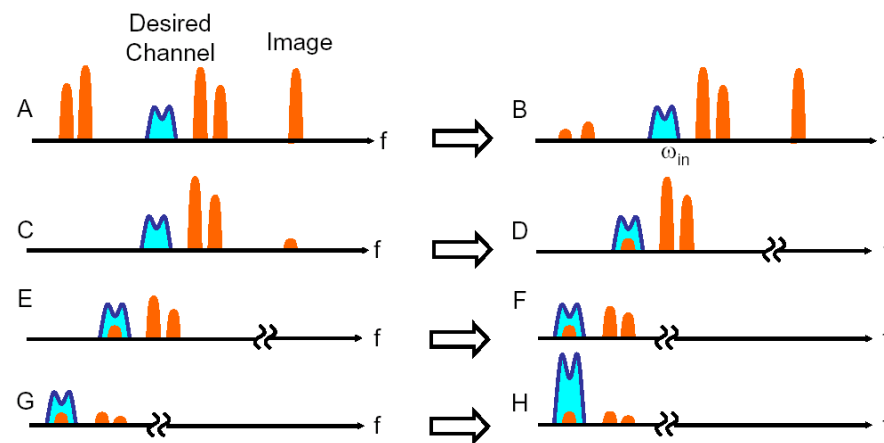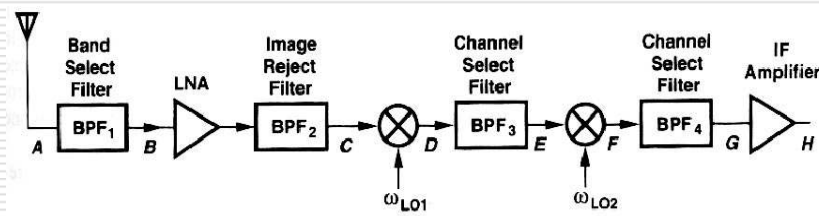


□ Newly introduce wireless applications

- Operating frequency goes up (900MHz, 1.8GHz, 2,4GHz,etc) with signal bandwidth stays the same (200KHz, 2MHz,etc)
- Ratio [operating frequency/wanted signal bandwidth] goes up
- Harder to use single stage IF receiver

Quadrature Downconversion

□ Demodulation at the 2nd IF

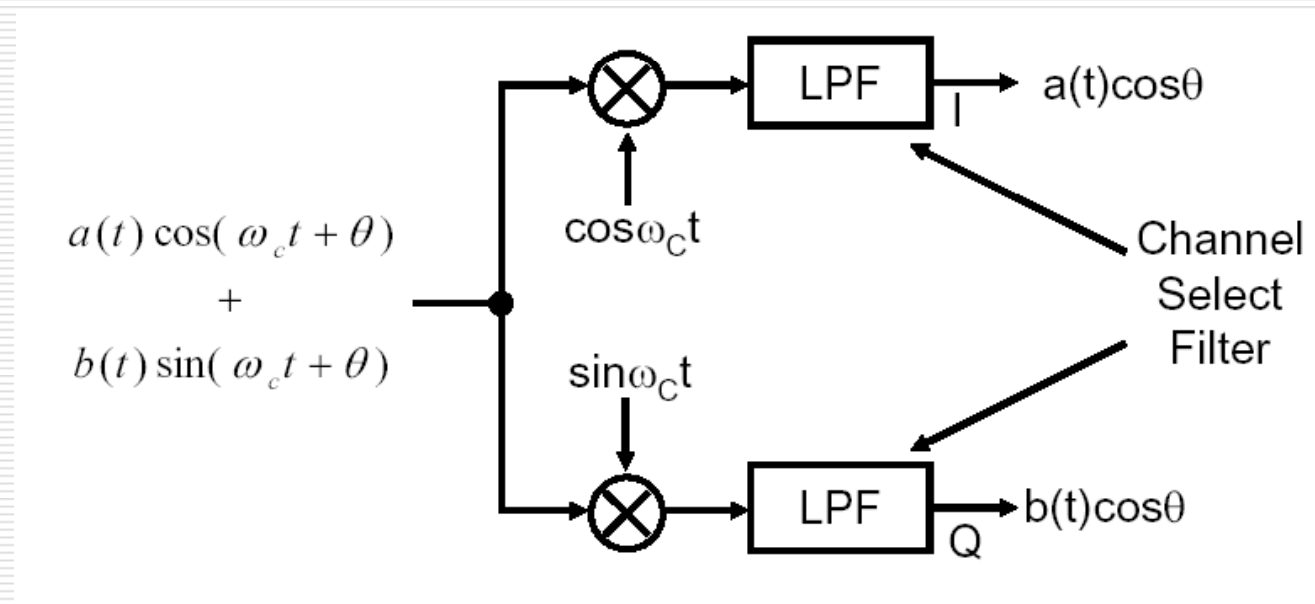- If 2nd mixer translates the spectrum to zero frequency (base band signal)
 - No 2nd IF → “Single IF topology”
- In-phase (I) and Quadrature (Q) components normally at the 2nd mixer



Heterodyne - Summary

□ Dual-IF topology

- Resolve the trade-off between sensitivity and selectivity issue of simple heterodyne receiver
 - Partial channel selection at progressively lower center frequencies
 - Relax required Q
- NF (sensitivity) : critical in the front
- IIP3 (selectivity) : critical in the back end
 - Relax the IP3 requirement through the progressive compression of interferes

□ Heterodyne-summary

- Complex
- Many off chip components : expensive, sensitive to external parasitic signals, higher power consumption
- Most reliable reception technique (sensitivity and selectivity wise)

Homodyne Receivers

❑ Homodyne, direct conversion, zero-IF


- RF spectrum → baseband frequency conversion

- Simple homodyne

- ❑ Double sideband AM

- ❑ Double sideband

- (+) and (-) part of spectrum

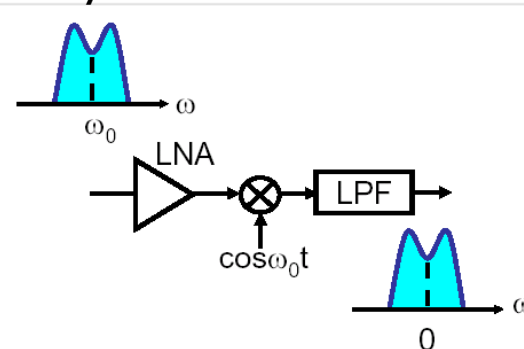

- Homodyne with quadrature downconversion

- ❑ FM, QPSK

- Advantage


- ❑ No image

- No IF filter

- Simple and cheap

- ❑ High output impedance of LNA


- ❑ BPF can be replaced by LPF

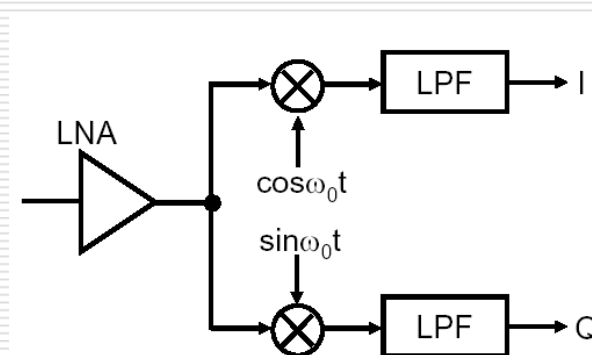

Homodyne Receiver – Channel Selection

❑ Rejection of out-of-channel interferers

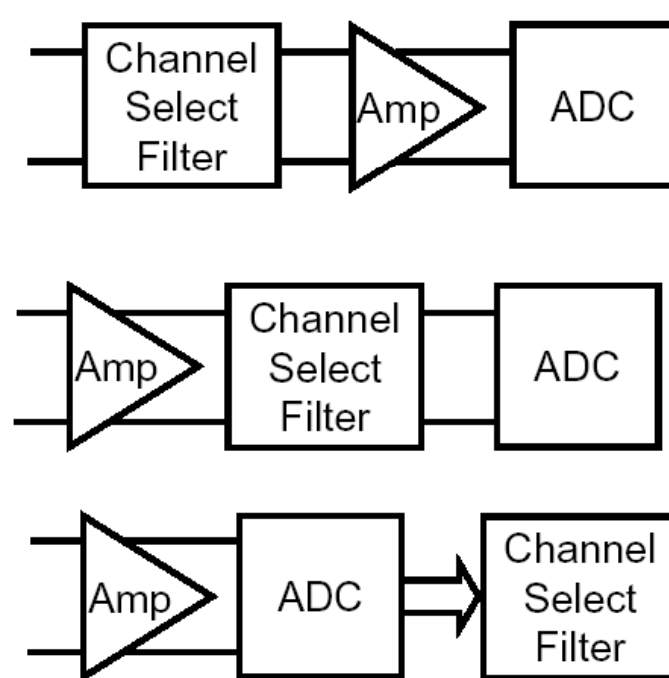- Active filter is more difficult than passive filter.
- Active filter
 - ❑ Noise-linearity-power trade-offs



❑ Out-of-channel suppression

- Amplifier can be nonlinear
- ADC moderate dynamic range
- LPF tight noise-linearity spec

❑ Amplifier should be linear

- Relaxed LPF noise requirement

❑ Amplifier should be linear

- ADC high linearity and low noise


Homodyne Receiver – DC Offsets

❑ Homodyne → Zero-IF


- Offset voltages at DC corrupt the signal

❑ Offset voltage generation

- Self mixing
 - ❑ LO leakage

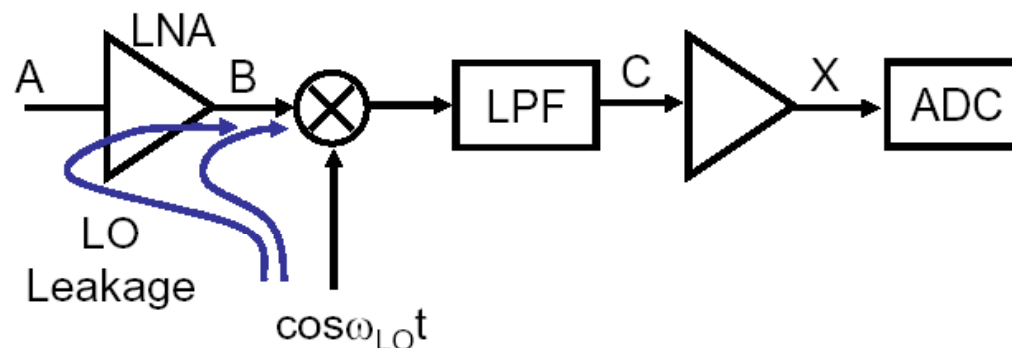

- ❑ Strong interferer

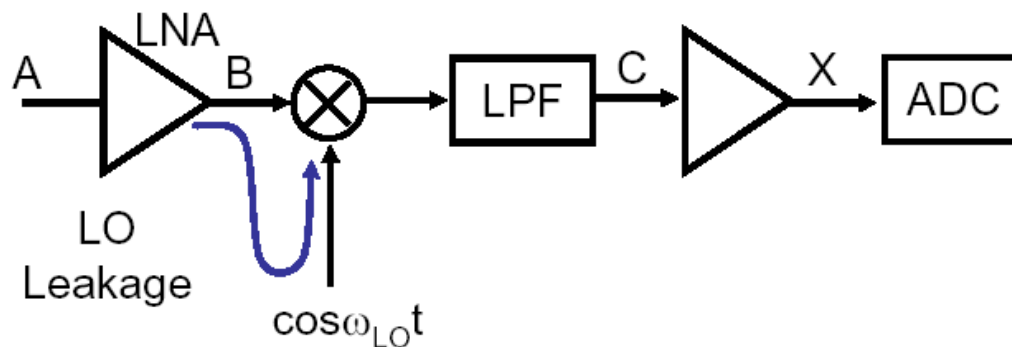

Self-mixing

- ❑ **Gain before ADC**
 - 80-100 dB
- ❑ **LNA/mixer gain**
 - 25-30 dB
- ❑ **Example**
 - LO voltage peak-to-peak 0.63 V (0 dBm)
 - 60 dB LO-RF isolation (-60 dBm)
 - Gain of LNA/Mixer 30 dB (-30 dBm)
 - Offset voltage at the output of mixer ~ 10 mV
 - Signal input ~ 30 μ Vrms
- ❑ **Problem is severe if self-mixing varies with time**
 - LO signal leaks through antenna and reflected back
 - Time-varying offset is difficult to distinguish
- ❑ **DC offset is not a problem in heterodyne**
 - $RF \neq LO$, no DC offset problem
 - IF is selected by BPF.

Solutions for Offset Cancellation

DC-Free Coding

□ High-pass filter

- To remove DC component
- Most of energy is accumulated at DC
 - Example: 200 kHz BW, 0-20 Hz removal $BER > 10^{-5}$
- Large capacitor required
- Fast variation of offset voltage cannot be covered.
- Not a good method

□ Modulation such that little energy at DC


- DC-free coding
- Suitable for wideband channels
- Example: DECT, a few kHz with no data there

Solutions for Offset Cancellation

Offset Cancellation in a TDMA

□ Digital offset cancellation


- C stores offset between TDMA bursts.
- TDMA frame: a few ms
 - Offset cancellation every a few ms
 - Sufficiently fast
- Thermal noise of S_1 is significant
 - kT/C noise
 - C_1 should be a large value.
 - Example
 - 1 μV input signal
 - 30 dB gain before offset cancellation, 32 μV
 - Noise $\sqrt{(kT/C)}$, 15 dB below signal (5.6 μV)
 - $C_1 > 200 \text{ pF}$ $\sqrt{(kT/C)} = 4.5 \mu\text{V}$
- Interferer signal is also stored at C_1
 - Interferer signal changes fast
 - Several sampling and averaging

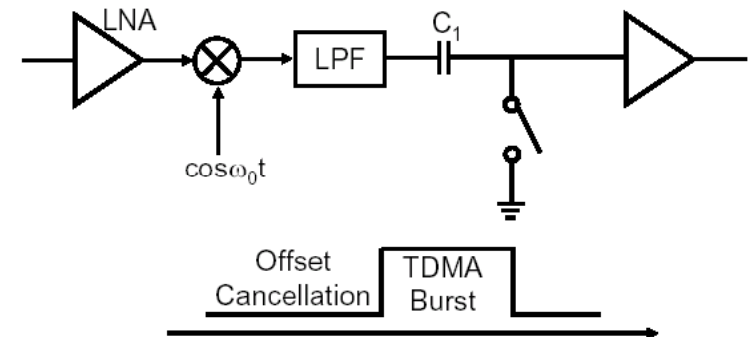


I/Q Mismatch

❑ For phase and frequency modulation

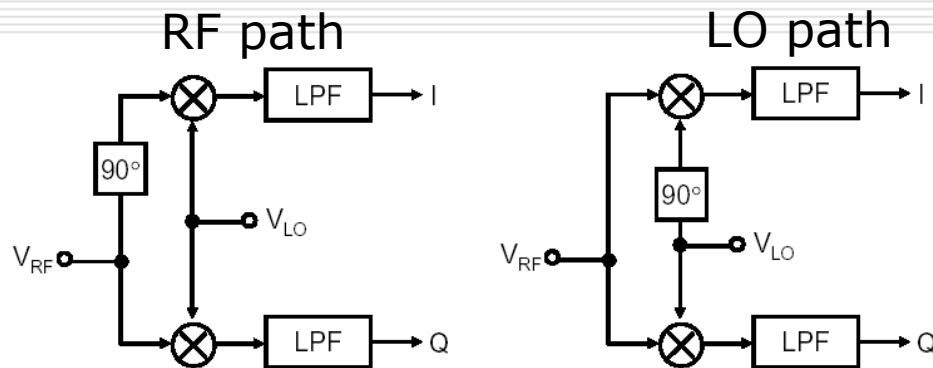- Quadrature mixing is required
- Either RF or LO require 90° shift



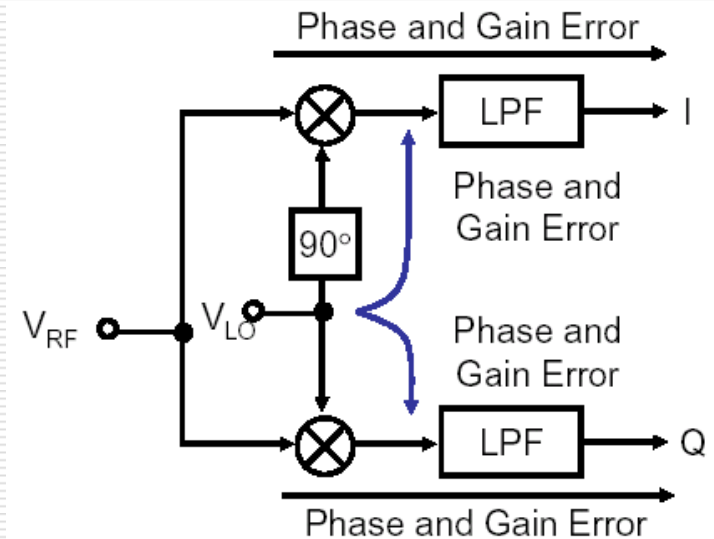- Normally LO 90° shift
- I/Q mismatch
 - ❑ Amplitude mismatch for I and Q LO signal
 - ❑ Phase mismatch for I and Q LO signal
 - ❑ Worse BER



Effect of I/Q Imbalance

Received signal

- $a, b = \pm 1$

$$x_{in}(t) = a \cos \omega_c t + b \sin \omega_c t$$

I and Q phase of LO signal

- $\frac{1}{2}$ for simplification
- ε : amplitude error
- θ : phase error



$$x_{LO,I}(t) = 2 \left(1 + \frac{\varepsilon}{2} \right) \cos \left(\omega_c t + \frac{\theta}{2} \right)$$

$$x_{LO,Q}(t) = 2 \left(1 - \frac{\varepsilon}{2} \right) \sin \left(\omega_c t - \frac{\theta}{2} \right)$$

Baseband signal


$$x_{BB,I}(t) = a \left(1 + \frac{\varepsilon}{2} \right) \cos \left(\frac{\theta}{2} \right) - b \left(1 + \frac{\varepsilon}{2} \right) \sin \left(\frac{\theta}{2} \right)$$
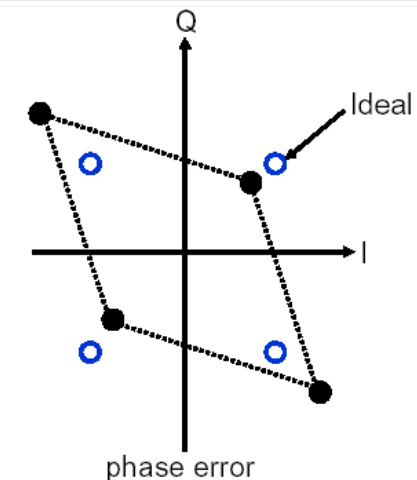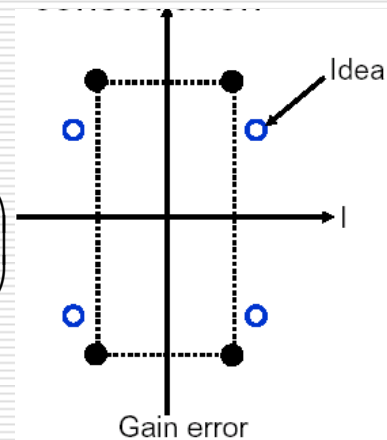
$$x_{BB,Q}(t) = -a \left(1 - \frac{\varepsilon}{2} \right) \sin \left(\frac{\theta}{2} \right) + b \left(1 - \frac{\varepsilon}{2} \right) \cos \left(\frac{\theta}{2} \right)$$




Gain Error and Phase Error

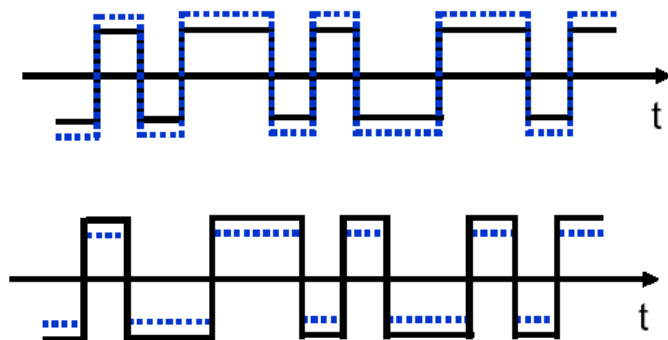- ❑ Effect of I/Q mismatch
- ❑ Gain Error



Phase Error

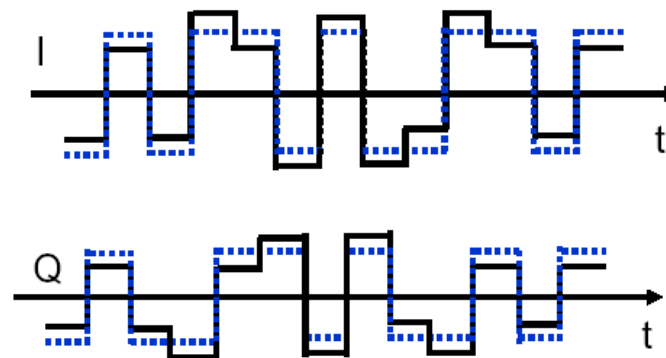


- ❑ Amplitude mismatch < 1 dB
- ❑ Phase error $< 5^\circ$
- ❑ For heterodyne receiver, requirements are relaxed
 - Frequency is lower. Less sensitive to mismatches in parasitics
 - Signals amplified 50-60 dB before I/Q separation
 - ❑ More gain required after I/Q separation \rightarrow gain stage delay
 - Monolithic integration is better than hybrid approach.

Even Order Distortion

□ Even order distortion is important in homodyne.

■ Signal near DC

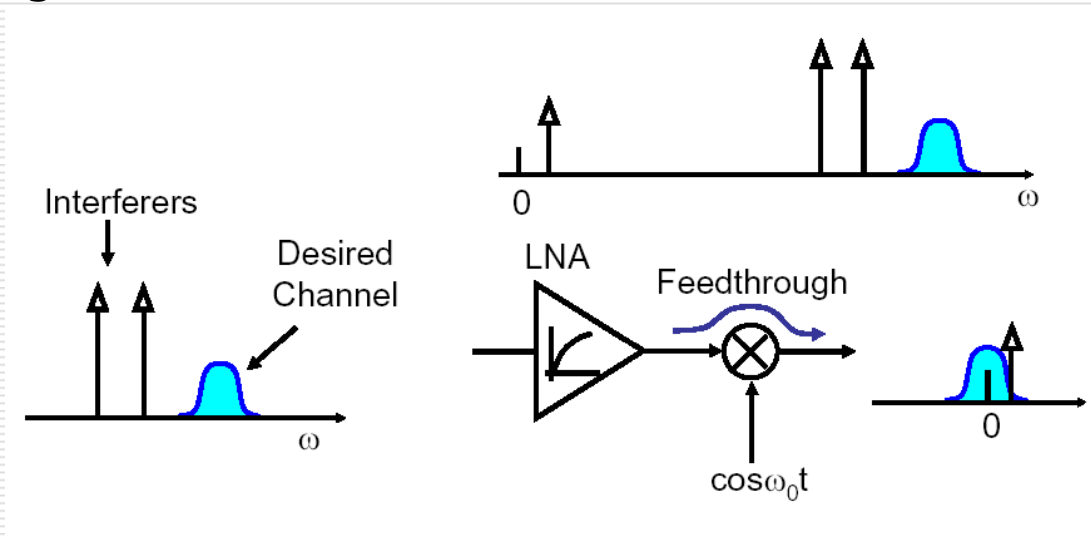

$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t)$$

$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$$

$$\alpha_2 A_1 A_2 \cos(\omega_1 - \omega_2)t$$

- 2nd harmonic (even-order harmonic at low frequency)
- RF to IF feedthrough → interferer at baseband of signal

Even Order Distortion in FSK or PSK

- ❑ **PSK or FSK signal with AM**
- ❑ **PSK or FSK signal go through fading or disturbance during transmission**

$$x_{in}(t) = (A + \varepsilon \cos \omega_m t)(a \cos \omega_c t + b \sin \omega_c t)$$

- $\cos \omega_m t$: low freq. Amplitude modulation
- 2nd order term $(a^2 + b^2)A\varepsilon \cos \omega_m t$
- Even-order distortion demodulates AM
- ❑ **Mixer 2nd order distortion**
 - Mixer RF port also has the same distortion problem
- ❑ **IP2: 2nd order distortion characterization**
 - How small (or large) the 2nd order distortion is
- ❑ **Differential structure suppresses even order distortion**
 - RF component (antenna, duplexers, etc) are single ended.
 - Higher power dissipation than single ended.

Flicker Noise and LO Leakage

□ LNA+mixer 30 dB gain: $\sim 10 \mu\text{V}$ signal


- 1/f noise (low frequency noise) corrupts the signal.
- Employ large size device to minimize the flicker noise at IF amplification
- TDMA periodic offset cancellation
- DC free coding

□ LO leakage

- LO leakage to antenna and received by other users using the same standard
- FCC (Federal Communication Commission)
 - In-band LO radiation requirement ~ -50 to -80 dBm

Image Reject Receiver

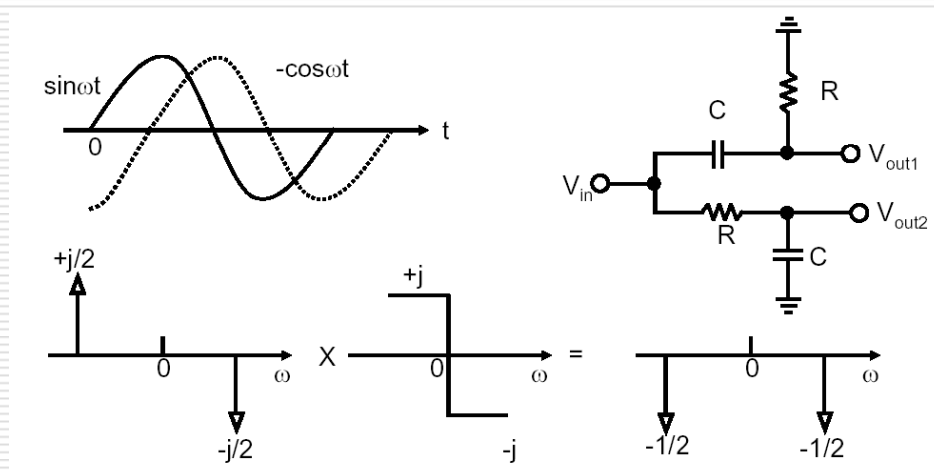- ❑ Without image-reject filter, heterodyne is a viable technology. → Image reject receiver
- ❑ Shift by 90° operation
 - Multiplication of $G(\omega) = -j \operatorname{sgn}(\omega)$
 - Example: $\sin(\omega t) \rightarrow -\cos(\omega t)$, $\cos(\omega t) \rightarrow \sin(\omega t)$



- 90° shift: RC-CR network
 - ❑ Phase shift of V_{out1} and V_{out2}
 - $\pi/2 - \tan^{-1}(RC\omega)$ and $\tan^{-1}(RC\omega) \rightarrow$ always 90° phase shift

Hartley Architecture

□ Hartley, 1928


□ RF input

$$x(t) = A_{RF} \cos \omega_{RF} t + A_{im} \cos \omega_{im} t$$

□ After I/Q mixer

$$x_A(t) = \frac{A_{RF}}{2} \sin(\omega_{LO} - \omega_{RF})t + \frac{A_{im}}{2} \sin(\omega_{LO} - \omega_{im})t$$
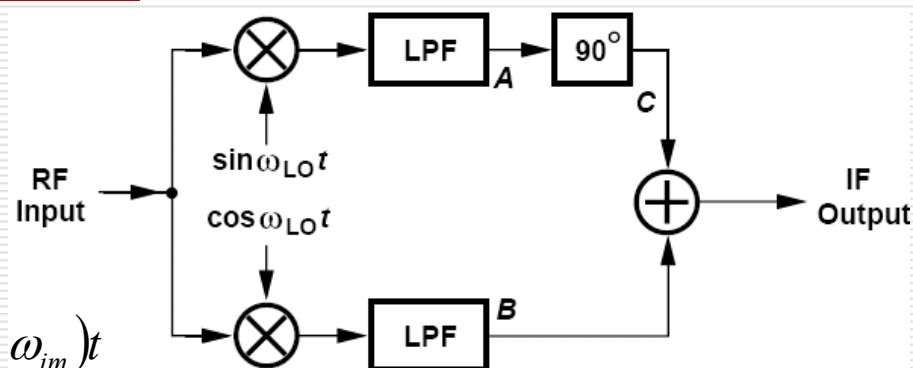
$$x_B(t) = \frac{A_{RF}}{2} \cos(\omega_{LO} - \omega_{RF})t + \frac{A_{im}}{2} \cos(\omega_{LO} - \omega_{im})t$$



□ Rewriting x_A

$$x_A(t) = -\frac{A_{RF}}{2} \sin(\omega_{RF} - \omega_{LO})t + \frac{A_{im}}{2} \sin(\omega_{LO} - \omega_{im})t$$


□ After 90° shift

$$x_C(t) = \frac{A_{RF}}{2} \cos(\omega_{RF} - \omega_{LO})t - \frac{A_{im}}{2} \cos(\omega_{LO} - \omega_{im})t$$

□ Combine B and C


$$x_{IF}(t) = A_{RF} \cos(\omega_{RF} - \omega_{LO})t$$

Graphical Analysis of Hartley Receiver

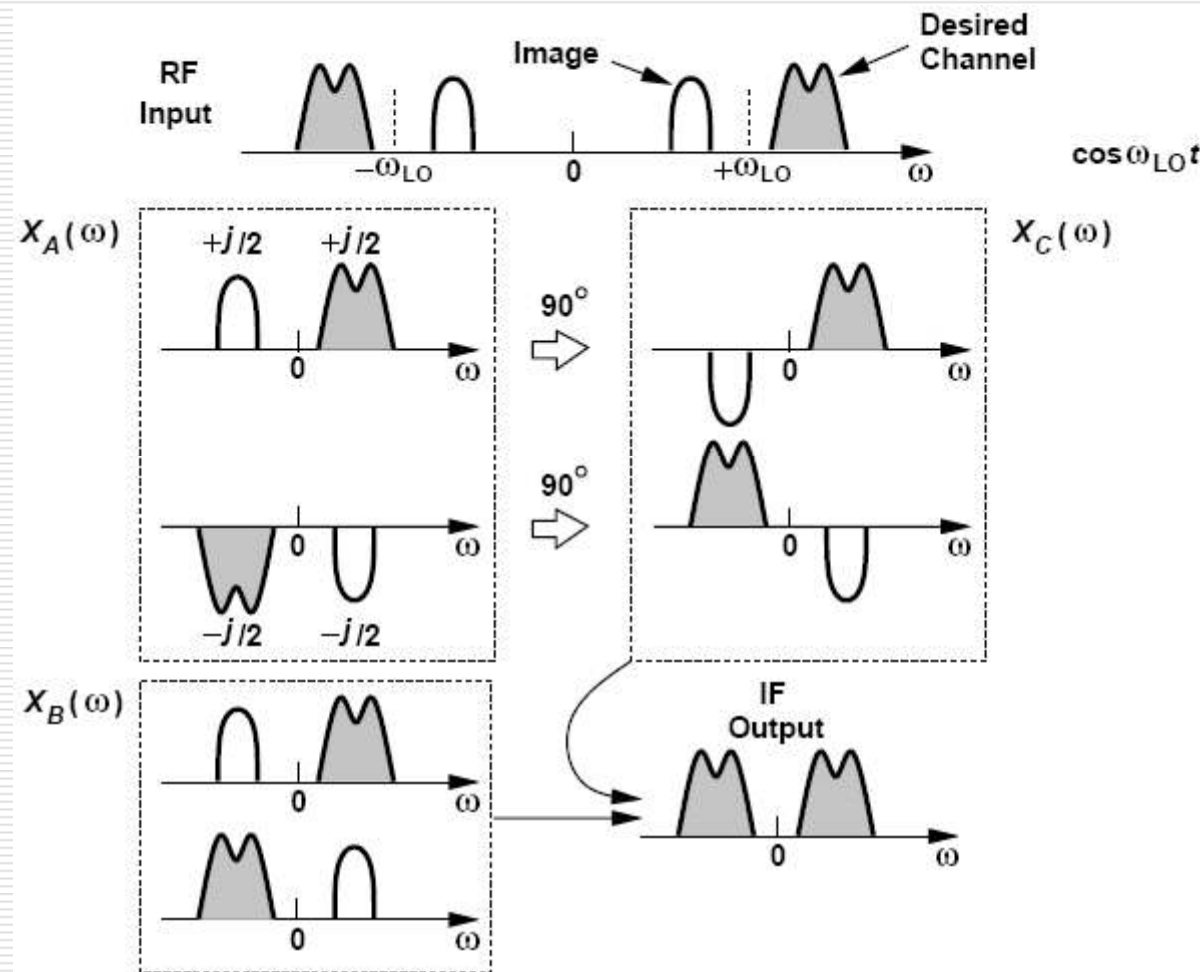

Hartley Receiver in Practice

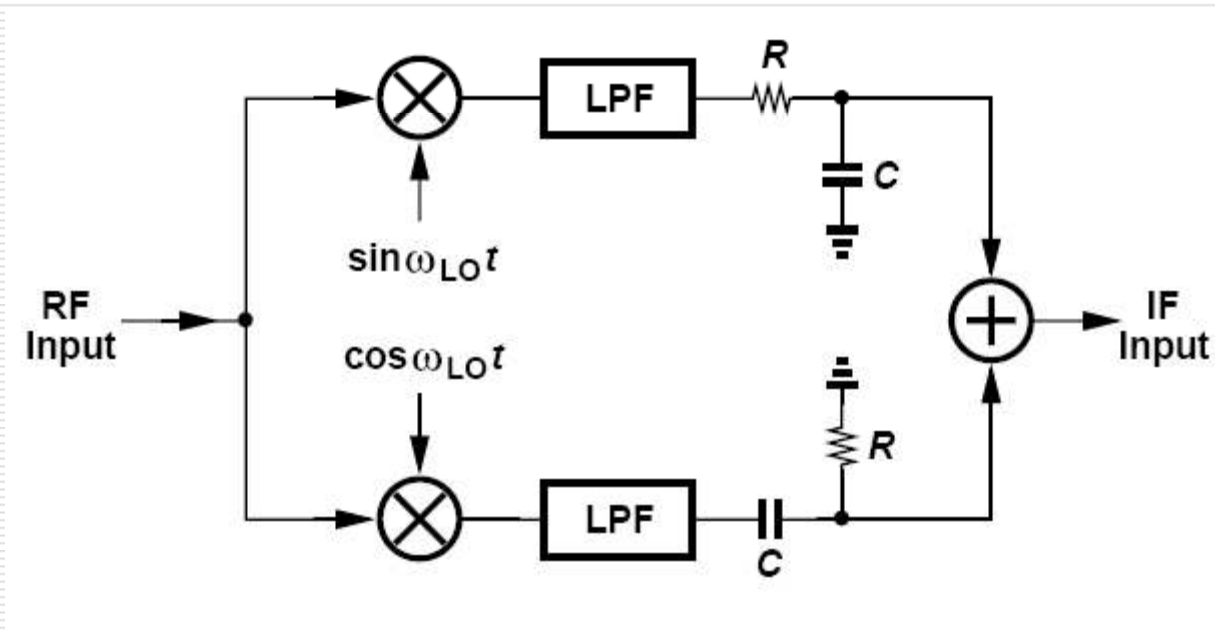- ❑ **90° shift** → **$\pm 45^\circ$ shift**
- ❑ **Drawback: sensitive to mismatches**
 - LO mismatch: cancellation is incomplete.



Mismatch Sensitivity

❑ Mismatch effect

■ At A and B

$$x_A(t) = \frac{A_{RF} A_{LO}}{2} \sin(\omega_{LO} - \omega_{RF})t + \frac{A_{im} A_{LO}}{2} \sin(\omega_{LO} - \omega_{im})t$$

$$x_B(t) = (A_{LO} + \varepsilon) \frac{A_{RF}}{2} \cos[(\omega_{LO} - \omega_{RF})t + \theta] + (A_{LO} + \varepsilon) \frac{A_{im}}{2} \cos[(\omega_{LO} - \omega_{im})t + \theta]$$

■ At C

$$x_C(t) = A_{LO} \left[\frac{A_{RF}}{2} \cos(\omega_{RF} - \omega_{LO})t - \frac{A_{im}}{2} \cos(\omega_{LO} - \omega_{im})t \right]$$

■ Signal and image

$$x_{sig}(t) = \frac{A_{RF} (A_{LO} + \varepsilon)}{2} \cos[(\omega_{LO} - \omega_{RF})t + \theta] + \frac{A_{RF} A_{LO}}{2} \cos(\omega_{LO} - \omega_{im})t$$

$$x_{im}(t) = (A_{LO} + \varepsilon) \frac{A_{im}}{2} \cos[(\omega_{LO} - \omega_{RF})t + \theta] - \frac{A_{LO} A_{im}}{2} \cos(\omega_{LO} - \omega_{im})t$$

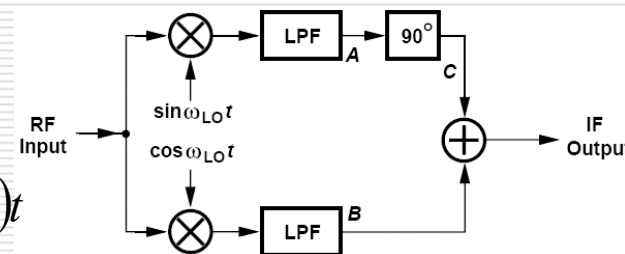


Image Rejection Ratio (IRR)

□ Image-to signal ratio at the output

$$\left. \frac{P_{im}}{P_{sig}} \right|_{out} = \frac{A_{im}^2 (A_{LO} + \varepsilon)^2 - 2A_{LO}(A_{LO} + \varepsilon)\cos\theta + A_{LO}^2}{A_{RF}^2 (A_{LO} + \varepsilon)^2 + 2A_{LO}(A_{LO} + \varepsilon)\cos\theta + A_{LO}^2}$$

□ Image-to-signal ratio at the input = A_{im}^2/A_{LO}^2

□ Image Rejection Ratio (IRR)

$$IRR = \frac{(A_{LO} + \varepsilon)^2 - 2A_{LO}(A_{LO} + \varepsilon)\cos\theta + A_{LO}^2}{(A_{LO} + \varepsilon)^2 + 2A_{LO}(A_{LO} + \varepsilon)\cos\theta + A_{LO}^2} \approx \frac{(\Delta A/A)^2 + \theta^2}{4}$$

□ IRR ~ 30-40 dB from

- Gain mismatch (ΔA) ~ 0.2-0.6 dB
- Phase mismatch (θ) 1-5°

Bandwidth of RC-CR Network

□ $\Delta A/A$ at $f_o - \Delta f$

$$\frac{\frac{1}{sC}}{R + \frac{1}{sC}}, \quad \frac{R}{R + \frac{1}{sC}}$$
$$\frac{\Delta A}{A} = \frac{\frac{sRC - 1}{sRC + 1}}{1} = sRC - 1 \sim \Delta\omega RC = \frac{\Delta\omega}{\omega_o}$$

Gain Mismatch from 90° phase shift

- Equal gain only at $\omega_{IF} = 1/RC$
- R, C can vary with temperature or process.

$$\frac{\Delta A}{A} = \frac{(R + \Delta R)(C + \Delta C)\omega - 1}{\sqrt{1 + (R + \Delta R)^2(C + \Delta C)^2\omega^2}} \bigg/ \frac{1}{\sqrt{1 + (RC\omega)^2}}$$

- In the vicinity of ω_{IF} , $RC\omega = 1$

$$\frac{\Delta A}{A} \approx \frac{\Delta R/R + \Delta C/C}{\sqrt{2 + \Delta R/R + \Delta C/C}} \div \frac{1}{\sqrt{2}} \approx \frac{\Delta R}{R} + \frac{\Delta C}{C}$$

- $\Delta R/R = 0.2$, IRR = 20 dB

- Frequency deviation → Gain mismatch

- Required image rejection : 60-70 dB


- Additional image attenuation from front-end filter possible

- Problems of Hartley architecture



- Matching requirements are more stringent than those in homodyne receivers.
- LPF cannot suppress strong interferer → Higher linearity adder required.
- Loss and noise problem of 90° shift

Weaver Architecture

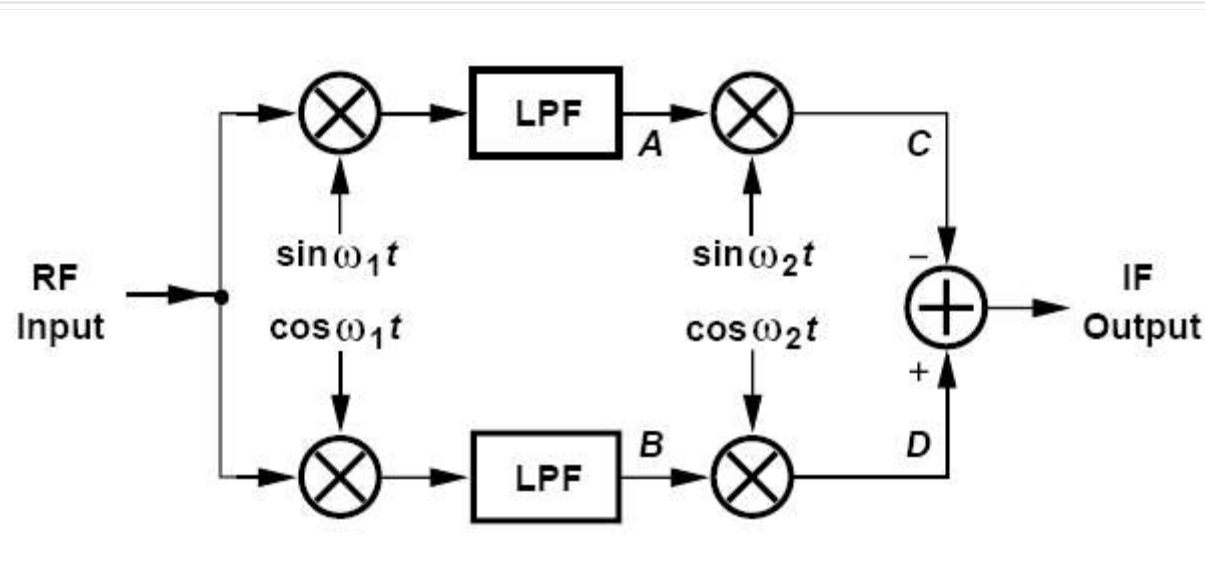- 90° shift in Hartley architecture → second IQ mixer in Weaver architecture




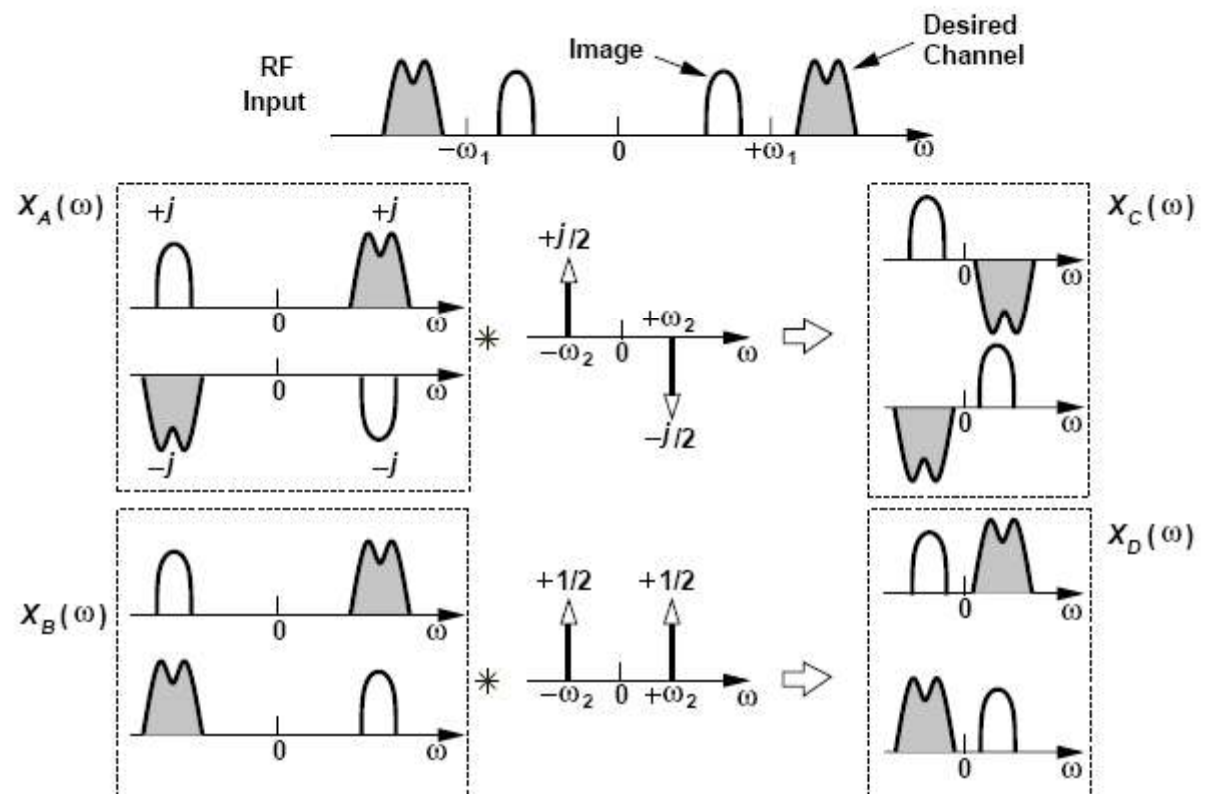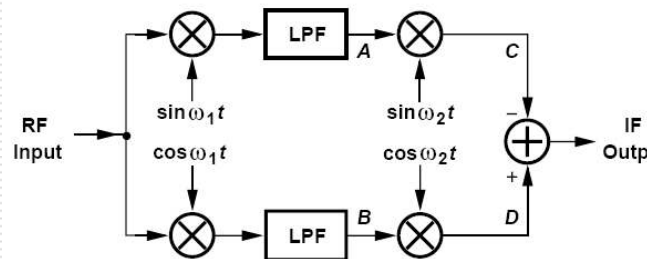Graphical Analysis of Weaver Architecture



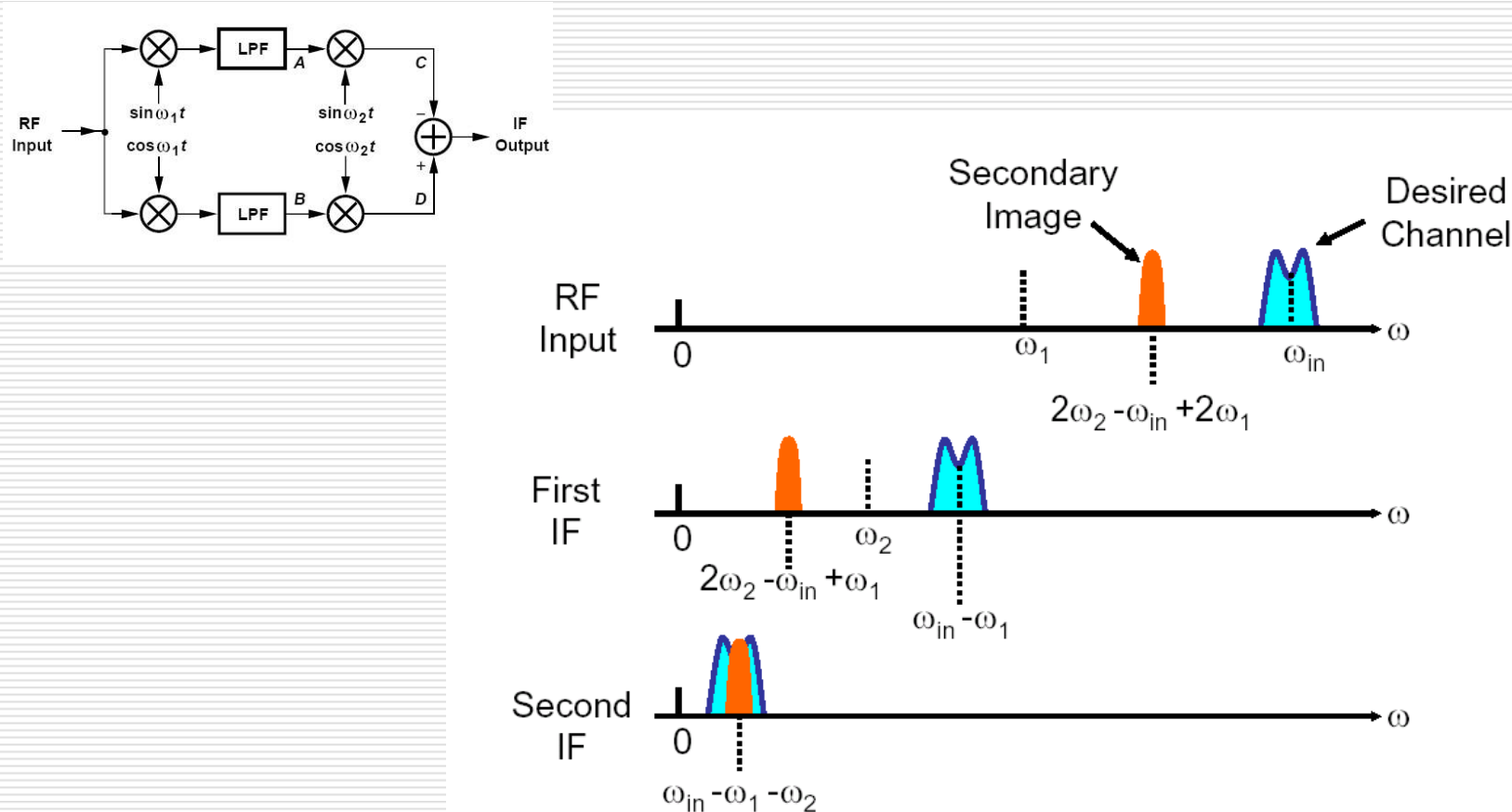Problem of secondary image in Weaver architecture

- ❑ Secondary image is not cancelled
- ❑ $2\omega_2 - \omega_{in} + 2\omega_1 \rightarrow 2\omega_2 - \omega_{in} + \omega_1$ (image with respect to ω_2)



Weaver Summary


□ Weaver Architecture

- To solve secondary image problem
 - Final downconversion to DC
 - $\omega_1 \pm \omega_2 = \omega_{in}$
- Incomplete image rejection due to gain and phase mismatch → Problem for both Hartley and Weaver
- No gain imbalance from RC 90° phase shift network, but secondary image problem

Digital-IF Receivers

□ In the dual-IF heterodyne architecture

- Low frequency operation can be performed in digital domain → digital-IF architecture
- No I and Q mismatch problem

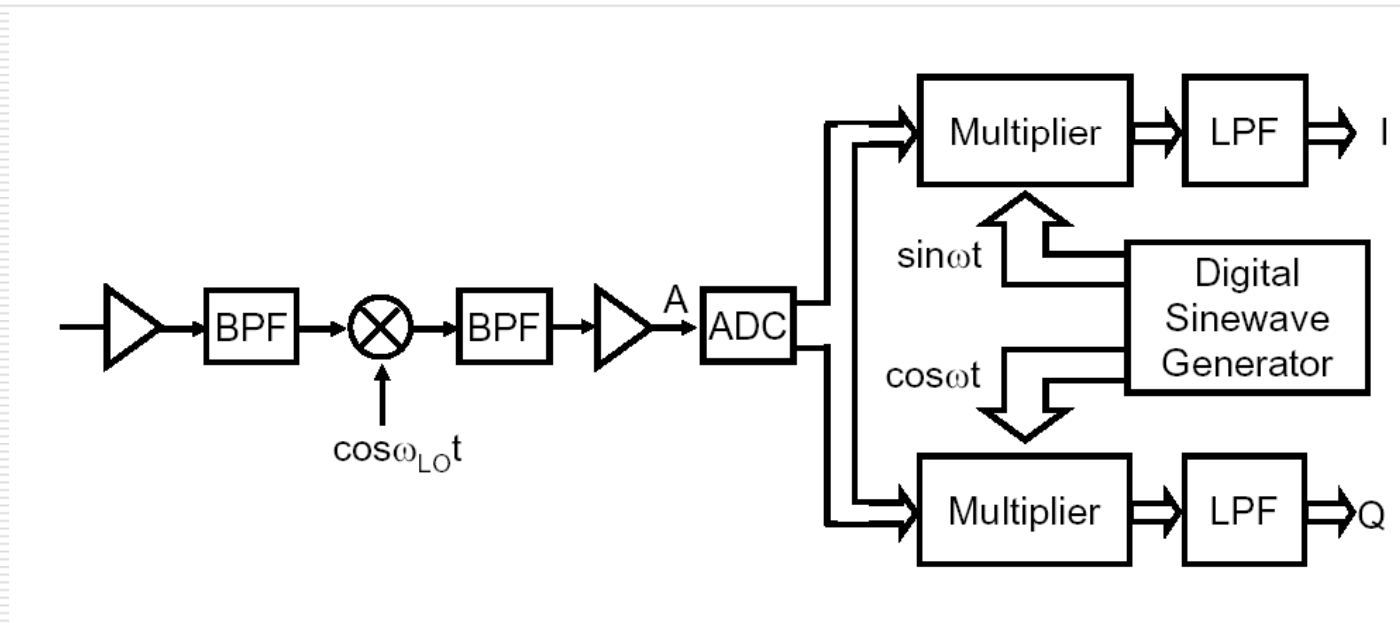


Sampling IF

□ ADC related problems

- Very small ADC input
 - <100 mV before ADC
- High sampling speed
 - For IF 50 to 200 MHz, sampling rate 100 to 400 MHz
- High dynamic range >14 bits

□ Sampling IF architecture

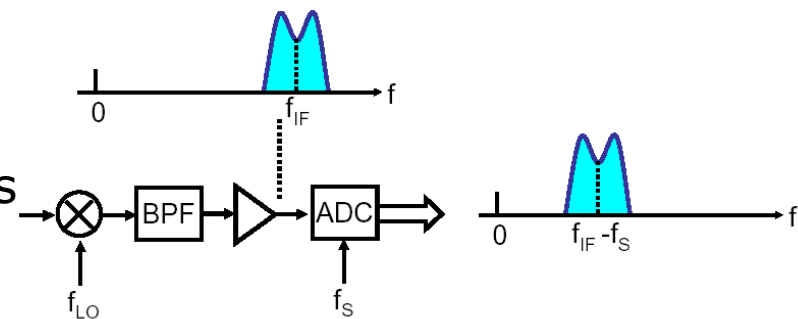
- ADC: sample-and-hold circuits
- Downconversion
- $f_{IF}-f_S$
 - digitized downconverted signal



□ Digital IF and Sampling IF have not been used in portable terminals yet.

Subsampling Receivers

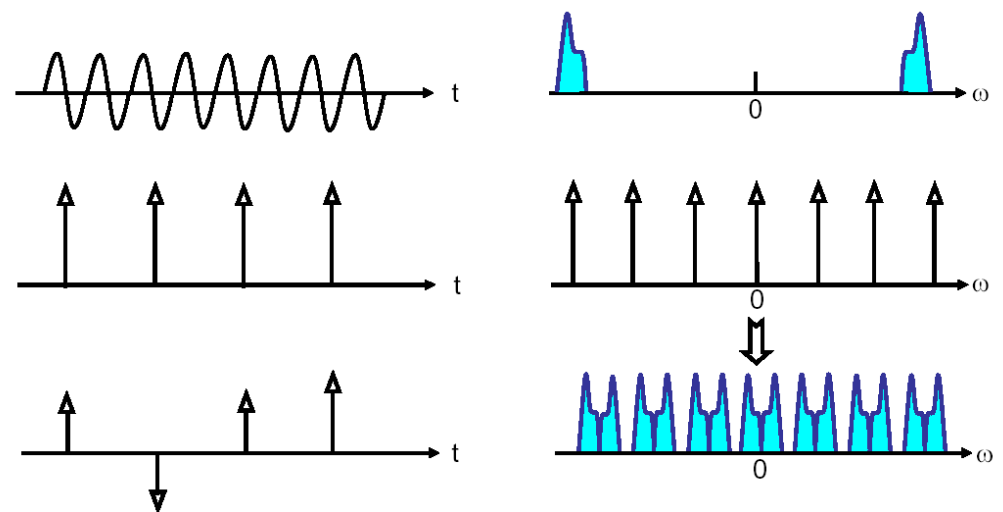- Normally $RF \sim LO$, $IF \sim 0$
- Very low rate sampling of RF
 - Narrow band signal \rightarrow only a small change
- Bandpass signal with bandwidth Δf
 - Sampled by a rate equal to or greater than $2\Delta f$
 - Low frequency conversion
- No high LO required
- Drawback
 - Aliasing of noise



Contents

5.1 General Considerations

5.2 Receiver Architectures

- 5.2.1 Heterodyne Receivers
- 5.2.2 Homodyne Receivers
- 5.2.3 Image-Rejection Receivers
- 5.2.4 Digital-IF Receivers
- 5.2.5 Subsampling Receivers

5.3 Transmitter Architectures

- 5.3.1 Direct-Conversion Transmitters
- 5.3.2 Two-Step Transmitters

5.4 Transceiver Performance Tests

5.5 Case Studies


- 5.5.1 Motorola's FM Receiver
- 5.5.2 Philips' Pager Receiver
- 5.5.3 Philips' DECT Transceiver
- 5.5.4 Lucent Technologies' GSM Transceiver
- 5.5.4 Philips' GSM Transceiver

Transmitter Architectures

□ Role of Transmitter


- Modulation
- Upconversion
- Power amplification

□ Analog or digital FM system

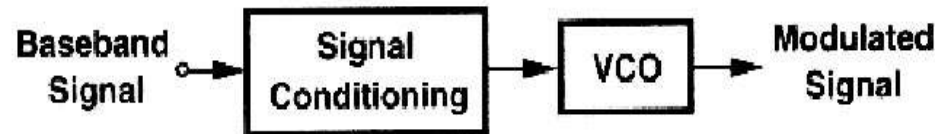


- Base band signal directly modulates the carrier generated by VCO
- Output spectrum depends on the amplitude and bandwidth of the modulating signal as well as the modulation index
- Thus base band signal is first conditioned through filtering and/or variable-gain stage -> compensate for variations in VCO characteristics (VCO must be stabilized by a feedback loop)

Digital Phase Modulation Systems

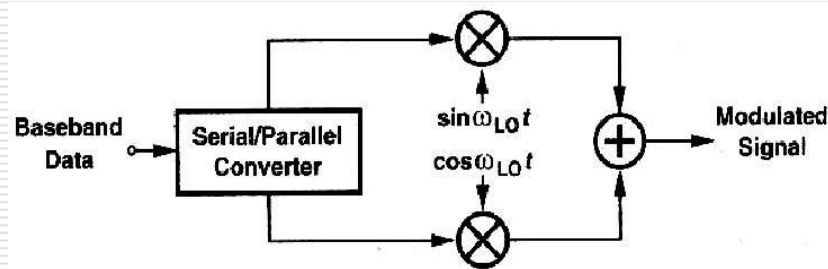

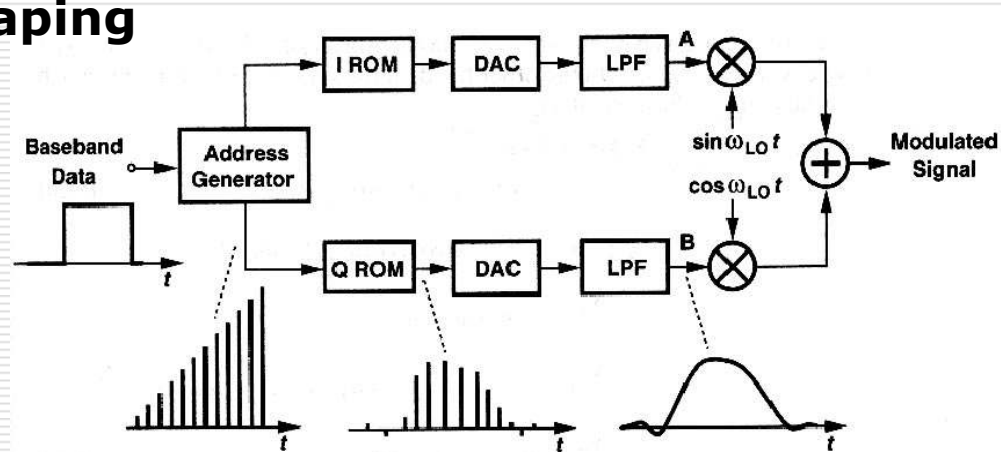- ❑ Data pulse must be shaped to minimize ISI and/or limit the signal BW
- ❑ Pulse shaping in analog domain requires bulky filters
 - Shaping by a combination of digital and analog technique
- ❑ Base band pulse shaping





Baseband Pulse Shaping in GMSK

□ GMSK

$$x_{GMSK}(t) = A \cos[\omega_c t + \phi_k(t)]$$

$$\phi_k(t) = \int \sum h(t) * p(t - kT) dt$$

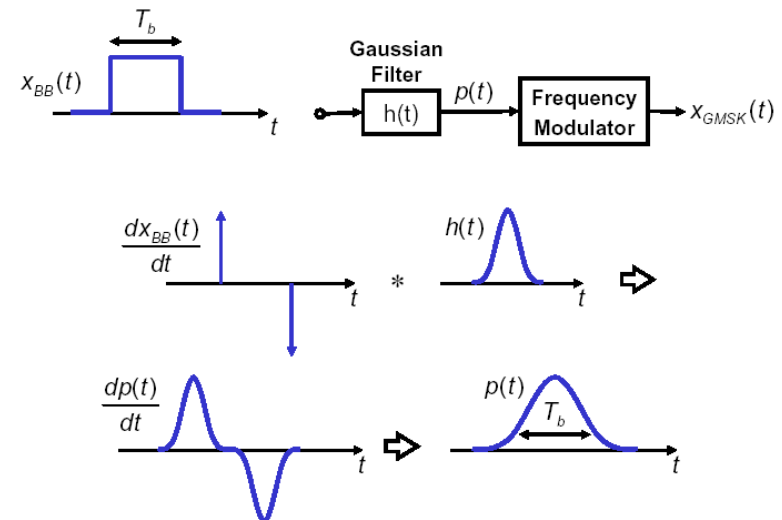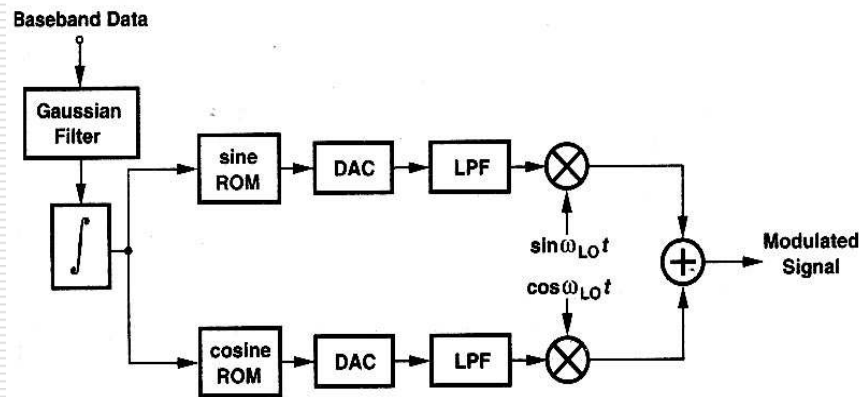- $h(t)$: impulse response of Gaussian filter
- Digital implementation of filter proves more accurate than an analog counterpart



Cf. Fig. 3.44

Cross-talk Issue

- Induced by phase and gain mismatch of I and Q path

$$v_I = V_0 \sin \omega_{in} t \quad v_Q = V_0 \cos \omega_{in} t$$

$$\begin{aligned} v_{out}(t) &= V_0 \sin \omega_{in} t \sin \omega_{LO} t + V_0 \cos \omega_{in} t \cos \omega_{LO} t \\ &= V_0 \cos(\omega_{in} - \omega_{LO})t \end{aligned}$$

- Under mismatch

$$\begin{aligned} v_{out}(t) &= V_0 \sin \omega_{in} t \sin \omega_{LO} t + V_0(1 + \varepsilon) \cos \omega_{in} t \cos(\omega_{LO} t + \theta) \\ &\approx \frac{V_0}{2} [1 + (1 + \varepsilon) \cos \theta] \cos(\omega_{in} - \omega_{LO})t - \frac{V_0}{2} (1 + \varepsilon) \sin \theta \sin(\omega_{LO} - \omega_{in})t \\ &\quad + \frac{V_0}{2} [-1 + (1 + \varepsilon) \cos \theta] \cos(\omega_{in} + \omega_{LO})t - \frac{V_0}{2} (1 + \varepsilon) \sin \theta \sin(\omega_{LO} + \omega_{in})t \end{aligned}$$

- Measure of I/Q imbalance

$$\frac{Power|_{(\omega_{LO} + \omega_{in})}}{Power|_{(\omega_{LO} - \omega_{in})}} \cong \frac{1 - (1 + \varepsilon) \cos \theta + \varepsilon}{1 + (1 + \varepsilon) \cos \theta + \varepsilon}$$

- Crosstalk can be negligible if above yields -30dB

PA/Antenna Interface

- **Transmitter → duplex filter or TDD switch → antenna**


- **Loss of duplex filter ~ 2 to 3 dB**
 - 30 to 50 % loss
 - 1 W power amplifier (PA) → more than 300 mW loss

- **Loss of TDD switch ~ 0.5 to 1 dB**
 - Better efficiency than FDD

Direct Conversion Transmitters

□ Direct conversion

- RF frequency = LO frequency

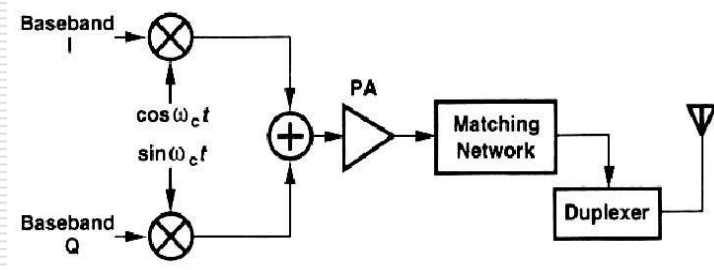

- BPF after mixer to suppress harmonics

□ Mixer noise is less critical



- Since baseband signal is sufficiently strong

□ Drawback

- Disturbance of LO by the power amplifier – injection pulling

□ Alleviating LO pulling

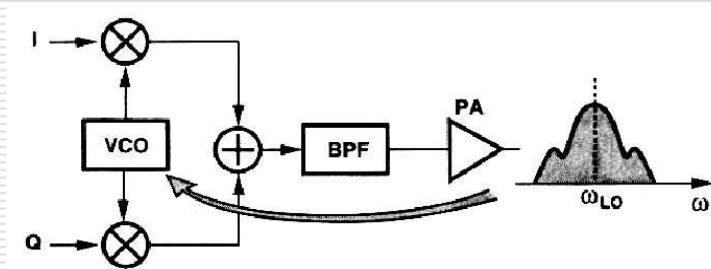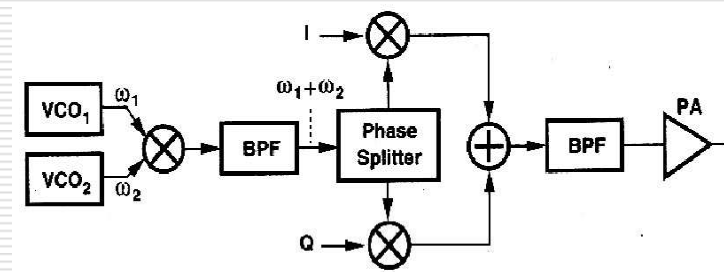
- Offset LO frequency
 - Carrier frequency is equal to $\omega_1 + \omega_2$ far from either ω_1 or ω_2



Two-Step Transmitters

□ Two-step architecture

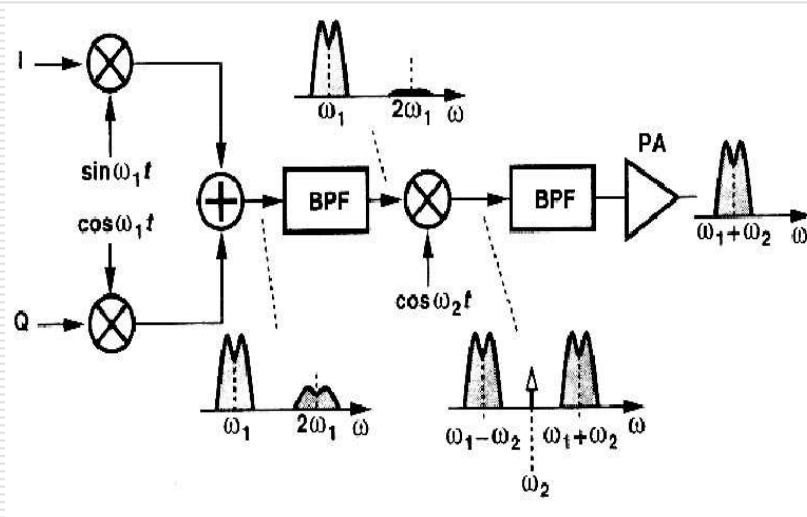- Circumventing the problem of LO pulling



□ Advantages

- Since I/Q modulation performed at lower frequencies, I/Q matching is superior
 - Less crosstalk
- Channel filter may be used at the 1st IF to limit the transmitted noise and spurs in adjacent channel

□ Difficulty

- 2nd BPF require 50-60dB rejection
 - Require off-chip component

Contents

5.1 General Considerations

5.2 Receiver Architectures

5.2.1 Heterodyne Receivers

5.2.2 Homodyne Receivers

5.2.3 Image-Rejection Receivers

5.2.4 Digital-IF Receivers

5.2.5 Subsampling Receivers

5.3 Transmitter Architectures

5.3.1 Direct-Conversion Transmitters

5.3.2 Two-Step Transmitters

5.4 Transceiver Performance Tests

5.5 Case Studies

5.5.1 Motorola's FM Receiver

5.5.2 Philips' Pager Receiver

5.5.3 Philips' DECT Transceiver

5.5.4 Lucent Technologies' GSM Transceiver

5.5.4 Philips' GSM Transceiver

Transceiver Performance Tests

☐ Sensitivity – NF requirements

- MDS: minimum detectable signal
- GSM standard
 - ☐ Required MDS -120 dBm
 - ☐ SNR 9-12dB for 10^{-3} BER
- $P_{\text{mds}} = -174\text{dBm} + 10\log B + \text{NF} + \text{SNR}$
- NF = 7-10 dB

☐ A common test examines the response of the system to blocking signals by measuring

- ☐ In-band intermodulation
- ☐ Out-of-band intermodulation
- ☐ Second-order intermodulation
- ☐ Cross modulation
- ☐ Reciprocal mixing (char 7)




Transceiver Performance Tests

Receiver Requirements

- In-band intermodulation (a)
 - $C/(N+I) > 9 \text{ dB}$
 - C: carrier, N: noise, I: intermodulation
- Out-of-band and second-order intermodulation (b)
 - $C/(N+I) > 9 \text{ dB}$
- Cross modulation (c)
 - $C/(N+I) > 9 \text{ dB}$

Unwanted emissions

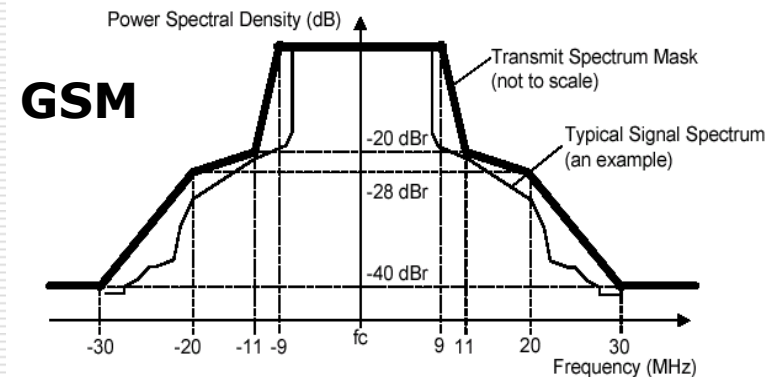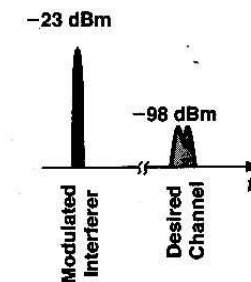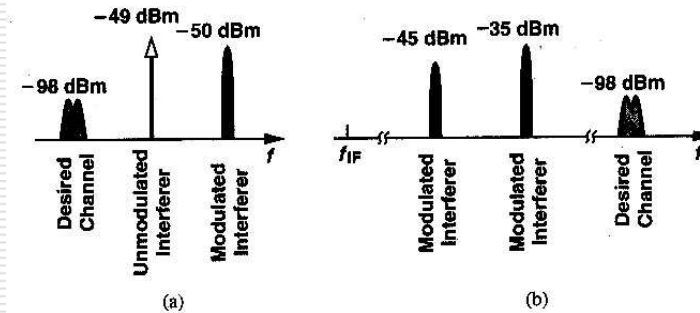- Wireless standard and FCC regulation require "modulation mask".
- ACP: adjacent channel power
- IS-54: ACP -26dBc
- IS-95: ACP -42dBc



Contents

5.1 General Considerations

5.2 Receiver Architectures

5.2.1 Heterodyne Receivers

5.2.2 Homodyne Receivers

5.2.3 Image-Rejection Receivers

5.2.4 Digital-IF Receivers

5.2.5 Subsampling Receivers

5.3 Transmitter Architectures

5.3.1 Direct-Conversion Transmitters

5.3.2 Two-Step Transmitters

5.4 Transceiver Performance Tests

5.5 Case Studies

5.5.1 Motorola's FM Receiver


5.5.2 Philips' Pager Receiver

5.5.3 Philips' DECT Transceiver

5.5.4 Lucent Technologies' GSM Transceiver


5.5.4 Philips' GSM Transceiver

Motorola FM single-chip receiver MC3362

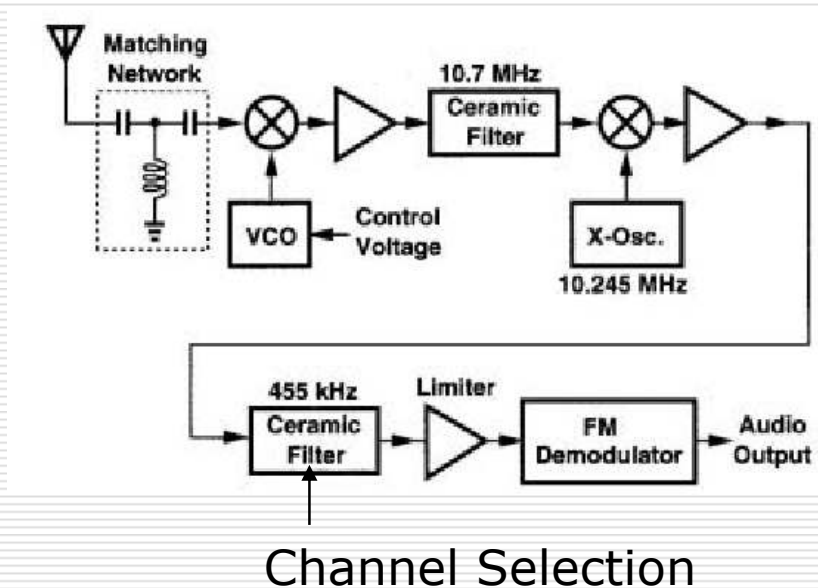


- ❑ **Walkie-talkie, first-generation cordless phone**
 - No LNA used for simplicity
- ❑ **Dual IF Conversion**
 - 50MHz → 10.7MHz → 455kHz
- ❑ **25 external components**
- ❑ **2V supply voltage, 5 mA**
- ❑ **20dB SNR for $0.7\mu\text{V}_{\text{rms}}$ input**

Philips UAA2080T single-chip receiver

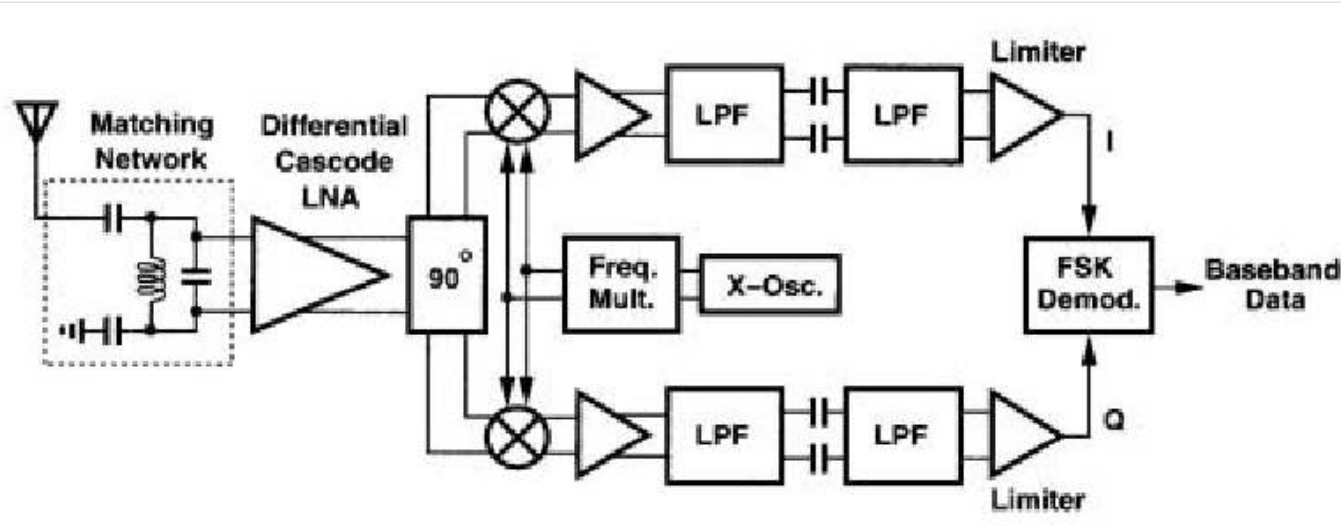

- ❑ Homodyne: 470MHz LO generated by 78.3MHz crystal x3
- ❑ 30 external components
- ❑ 2V, 3mA
- ❑ -125dBm sensitivity for BER=0.03, 1.2kb/s

Philips's DECT Receiver

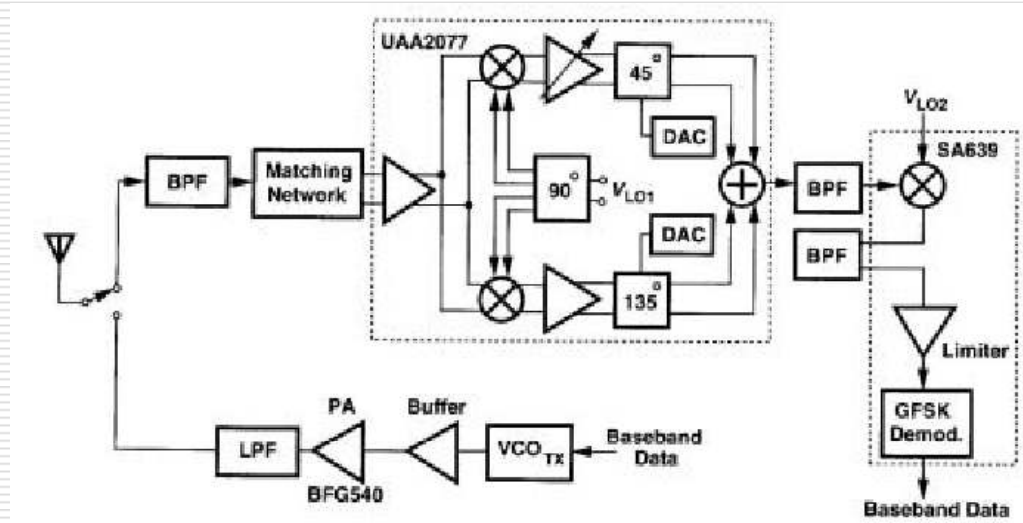

- ❑ **Dual IF receiver**
 - 1880-1900MHz → 110MHz → 9.8MHz
- ❑ **TDD**
- ❑ **Direct-conversion transmitter**
 - Open-loop GFSK modulation
- ❑ **PA pulling effect on VCO locking**

Lucent GSM

❑ Receiver


- 890-915MHz(TX),935-960MHz(RX) → 71MHz

❑ Transmitter

- Direct conversion
- LO: addition of VCO1 and VCO2 to avoid VCO pulling


❑ IQ LO generation by divide-by-4

❑ 2.7V 60mA

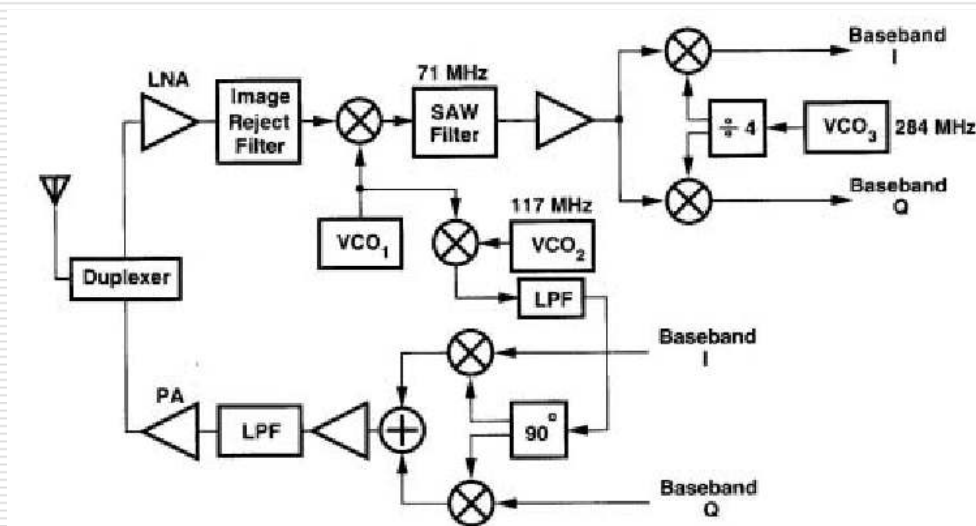


Philips GSM chip Set

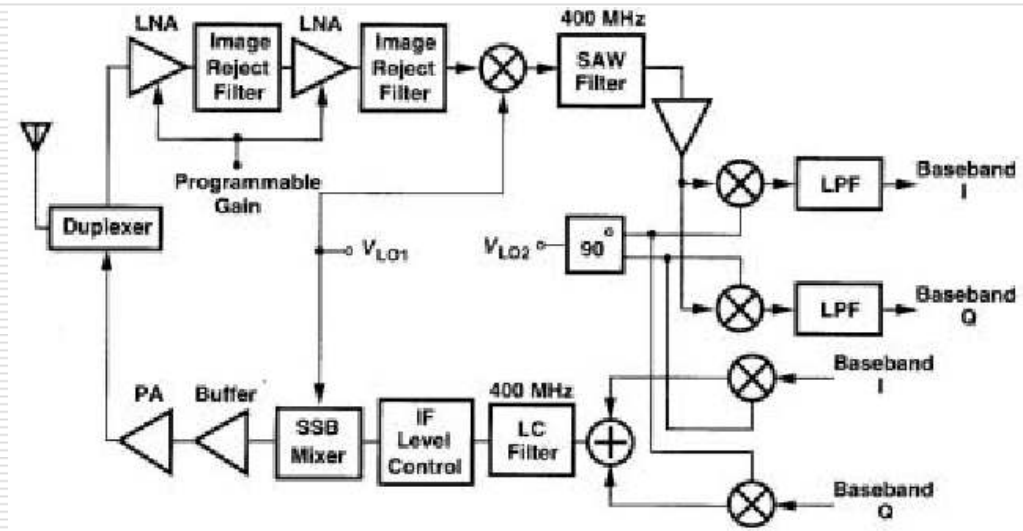- ❑ 890-915MHz(TX),935-960MHz(RX) → 400MHz
- ❑ Variable gain LNA +21 to -38 dB
- ❑ 1300MHz LO1




Receiver Architectures


- AMPS (Advanced Mobile Phone Services)

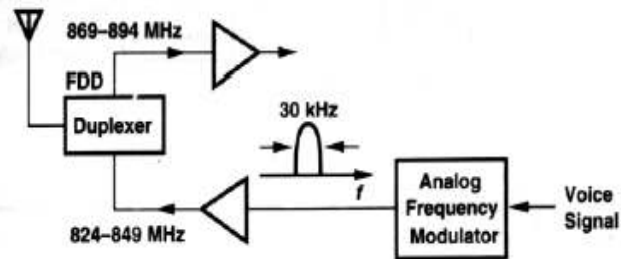

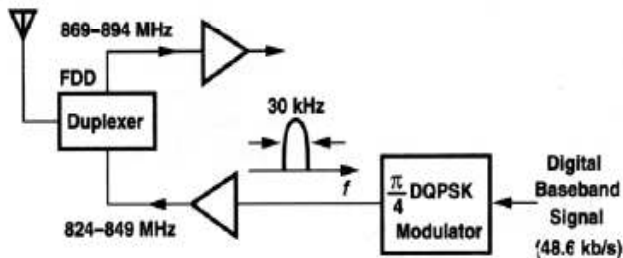
- NADC (North American Digital Standard) - USDC



- GSM (Global System for Mobile Comm.)

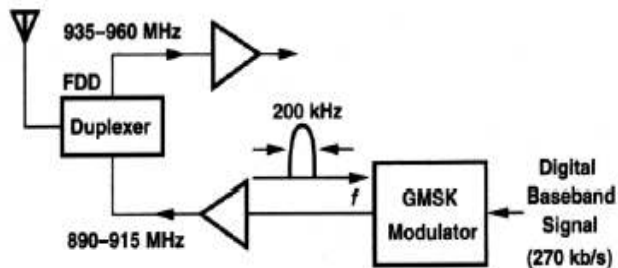

- IS-95 (Interim Standard 95)

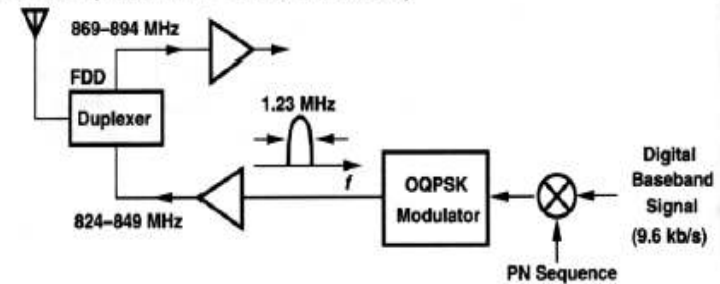

- DECT (Digital European Cordless Telephone)

