



EE141-Spring 2010 Digital Integrated Circuits

Lecture 5 Switch Logic - Optimization

EECS141

Lecture #5

1

Administrativa

- ☐ Homework #2 posted
- ☐ First lab this week

EECS141

Lecture #5

2

Class Material


- Last lecture
 - Design Rules
 - Introduction to switch logic
- Today's lecture
 - Optimization of inverter logic
- Reading (5.4-5.5)

EECS141

Lecture #5

3

CMOS Inverter at First Glance

 


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

EECS141


Lecture #5

4

CMOS Inverter: Transient Response

 

(a) Low-to-high

 

(b) High-to-low


$$t_{pHL} = f(R_{on}C_L) \\ = 0.69 R_n C_L$$

EECS141

Lecture #5

5

The Next Question: Inverter Chain

 

- For some given C_L :
 - How many stages are needed to minimize delay?
 - How to size the inverters?
- Anyone want to guess the solution?


EECS141

Lecture #5

6

Careful about Optimization Problems

 - ❑ Get fastest delay if build one **very** big inverter
 - So big that delay is set only by self-loading



- ❑ Likely not the problem you're interested in
 - Someone has to drive this inverter...

Engineering Optimization Problems in General

- ❑ Need to have a set of constraints
- ❑ Constraints key to:
 - Making the result useful
 - Making the problem have a 'clean' solution
- ❑ For sizing problem:
 - Need to constrain size of first inverter

Delay Optimization Problem #1

- You are given:
 - A fixed number of inverters
 - The size of the first inverter
 - The size of the load that needs to be driven
- Your goal:
 - Minimize the delay of the inverter chain
- Need model for inverter delay vs. size

EECS141

Lecture #5

9


Inverter Delay

Delay: $t_{pHL} = (\ln 2) R_N C_L$ $t_{pLH} = (\ln 2) R_P C_L$

- Assume we want equal rise/fall delays

$$t_{pHL} = t_{pLH}$$

 - Need approximately equal resistances, $R_N = R_P$
- PMOS approximately 2 times larger resistance for same size;
- Must make PMOS 2 times wider, $W_P = 2W_N = 2W$
- $t_p = (\ln 2) (R_{inv}/W) C_L$ with R_{inv} resistance of minimum size NMOS




Loading on the previous stage: $C_{in} = WC_{ginv} = W(3C_G)$

EECS141

Lecture #5

10

Inverter Delay Model

 

$$R = R_{inv}/W$$

$$C_{int} = W(3C_d) = WC_{dinv}$$

Replace $\ln(2)$ with k (a constant):

$$\text{Delay} = kR(C_{int} + C_L)$$



$$\text{Delay} = k(R_{min}/W)(WC_{dinv} + C_L)$$

EECS141

Lecture #5

11

Inverter with Load

  

$$\begin{aligned} \text{Delay} &= kR C_{in}(C_{int}/C_{in} + C_L/C_{in}) \\ &= kR_{min} C_{ginv} [C_{dinv}/C_{ginv} + C_L/(WC_{ginv})] \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$

$$C_{dinv}/C_{ginv} = \gamma = \text{Constant independent of size}$$

EECS141

Lecture #5

12

Delay Formula

$$\text{Delay} \sim R_W (C_{int} + C_L)$$

$$t_p = kR_W C_{in} (C_{int}/C_{in} + C_L / C_{in}) = t_{inv} (\gamma + f)$$


$$C_{int} = \gamma C_{in} (\gamma \approx 1 \text{ for CMOS inverter})$$

$$f = C_L / C_{in} - \text{electrical fanout}$$

$$t_{inv} = kR_{min} C_{ginv}$$

t_{inv} is independent of sizing of the gate!!!

Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} = t_{inv} \left(\gamma + \frac{C_{in,j+1}}{C_{in,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{inv} \sum_{i=1}^N \left(\gamma + \frac{C_{in,j+1}}{C_{in,j}} \right), \quad C_{in,N+1} = C_L$$

Optimal Tapering for Given N

- Delay equation has $N-1$ unknowns, $C_{in,2} \dots C_{in,N}$
- To minimize the delay, find $N-1$ partial derivatives:

$$t_p = \dots + t_{inv} \frac{C_{in,j}}{C_{in,j-1}} + t_{inv} \frac{C_{in,j+1}}{C_{in,j}} + \dots$$

$$\frac{dt_p}{dC_{in,j}} = t_{inv} \frac{1}{C_{in,j-1}} - t_{inv} \frac{C_{in,j+1}}{C_{in,j}^2} = 0$$

EECS141

Lecture #5

15

Optimal Tapering for Given N (cont'd)

- Result: every stage has equal fanout:

$$\frac{C_{in,j}}{C_{in,j-1}} = \frac{C_{in,j+1}}{C_{in,j}}$$

- In other words, size of each stage is geometric mean of two neighbors:

$$C_{in,j} = \sqrt{C_{in,j-1} C_{in,j+1}}$$

- Equal fanout \rightarrow every stage will have same delay

EECS141

Lecture #5

16

Optimum Delay and Number of Stages

- When each stage has same fanout f :

$$f^N = F = C_L / C_{in,1}$$

- Effective fanout of each stage:

$$f = \sqrt[N]{F}$$

- Minimum path delay:


$$t_p = N t_{inv} \left(\gamma + \sqrt[N]{F} \right)$$

EECS141

Lecture #5

17

Example

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2$$

EECS141

Lecture #5

18

Delay Optimization Problem #2

- You are given:
 - The size of the first inverter
 - The size of the load that needs to be driven
- Your goal:
 - Minimize delay by finding optimal number and sizes of gates
- So, need to find N that minimizes:

$$t_p = N t_{inv} \left(\gamma + \sqrt[N]{C_L / C_{in}} \right)$$

Solving the Optimization

- Rewrite N in terms of fanout/stage f :

$$f^N = C_L / C_{in} \rightarrow N = \frac{\ln(C_L / C_{in})}{\ln f}$$

$$t_p = N t_{inv} \left(\left(C_L / C_{in} \right)^{1/N} + \gamma \right) = t_{inv} \ln(C_L / C_{in}) \left(\frac{f + \gamma}{\ln f} \right)$$


$$\frac{\partial t_p}{\partial f} = t_{inv} \ln(C_L / C_{in}) \cdot \frac{\ln f - 1 - \gamma / f}{\ln^2 f} = 0$$

$$f = \exp(1 + \gamma / f) \quad \text{For } \gamma = 0, f = e, N = \ln(C_L / C_{in})$$

Optimum Effective Fanout f

- Optimum f for given process defined by γ

$$f = \exp(1 + \gamma / f)$$

 


EECS141

Lecture #5

21

In Practice: Plot of Total Delay

 

- Curves very flat for $f > 2$

- Simplest/most common choice: $f = 4$

EECS141

Lecture #5

22

Normalized Delay As a Function of F





$$t_p = N t_{inv} \left(\gamma + \sqrt[N]{F} \right), \quad F = C_L / C_{in}$$

F	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1


($\gamma = 1$)

Textbook: page 210

Buffer Design

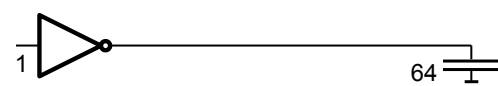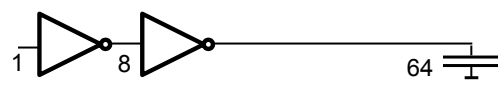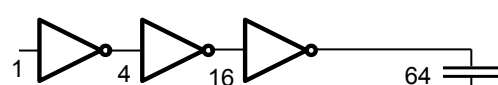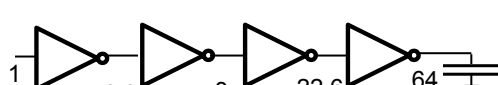	N	f	t_p
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3

What About Energy (and Area)?

 

Ignoring diffusion capacitance:

$$\begin{aligned}
 C_{tot} &= C_{in} + f \cdot C_{in} + \dots + f^N \cdot C_{in} \\
 &= C_{in} \cdot (1 + f + \dots + f^N) \\
 &= C_{in} + C_{in} \cdot f^N + C_{in} \cdot f \cdot (1 + f + \dots + f^{N-2}) \\
 &\quad \text{Overhead !!! } f(f^{N-1}-1) / (f-1)
 \end{aligned}$$

Example ($\gamma=0$): $C_L = 20\text{pF}$; $C_i = 50\text{fF} \rightarrow N = 6$

Fixed: 20pF

Overhead: **11.66pF !!!**

Example Overhead Numbers

Example: $C_L = 20\text{pF}$; $C_{in} = 50\text{fF}$

