

EE 538B CMOS RF IC DESIGN

Midterm Examination No. 2: May 15, 2002

Time Allowed: 110 Minutes

Student Name: Solutions


UW Student ID #: 123-45-6789

You are allowed two sheets of notes. Write legibly. Show all work. State assumptions.

Problem #	Points Possible	Points
1	20	20
2	30	30
3	20	20
4	30	30

~~100~~

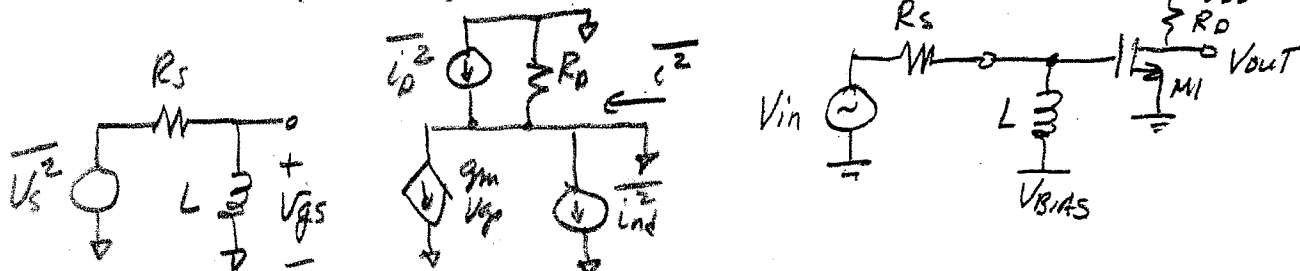1. (20 points) Find the noise factor of the circuit shown with respect to the source resistance R_S . Neglect channel length modulation effects and all parasitic capacitors. Consider only the drain current noise component of M_1 .



$$\overline{V_s^2} = 4kTR_S \Delta f; \quad \overline{i_{Lnd}^2} = 4kT \gamma g_{do} \Delta f; \quad \overline{i_D^2} = \frac{4kT}{R_D} \Delta f$$

The three noise sources are uncorrelated:

(i) Consider $\overline{i_D^2}$: $\overline{i_1^2} = \overline{i_D^2} = \frac{4kT}{R_D} \Delta f$

(ii) Consider $\overline{i_{Lnd}^2}$: $\overline{i_2^2} = \overline{i_{Lnd}^2} = 4kT \gamma g_{do} \Delta f$

(iii) Consider $\overline{V_s^2}$:

$$V_{gs} = \frac{SL}{SL + R_S} \overline{V_s} = \frac{SL/R_S}{SL/R_S + 1} \overline{V_s}$$

$$\Rightarrow \overline{V_{gs}^2} = \frac{(WL/R_S)^2}{(WL/R_S)^2 + 1} \overline{V_s^2} \quad \text{(Here we neglect phase shift since we're dealing with uncorrelated noise)}$$

$$\therefore \overline{i_3^2} = g_m^2 \overline{V_{gs}^2} = \frac{g_m^2 (WL/R_S)^2}{(WL/R_S)^2 + 1} \overline{V_s^2}$$


$$F = \frac{\overline{i_1^2} + \overline{i_2^2} + \overline{i_3^2}}{\overline{i_1^2}} = 1 + \frac{\frac{4kT}{R_D} \Delta f}{\frac{g_m^2 (WL/R_S)^2}{(WL/R_S)^2 + 1} \frac{4kTR_S \Delta f}{(WL/R_S)^2 + 1}} + \frac{\frac{4kT \gamma g_{do} \Delta f}{(WL/R_S)^2 + 1}}{\frac{g_m^2 (WL/R_S)^2}{(WL/R_S)^2 + 1} \frac{4kTR_S \Delta f}{(WL/R_S)^2 + 1}}$$

$$= 1 + \frac{[1 + (WL/R_S)^2]}{g_m^2 R_S R_D (WL/R_S)^2} + \frac{\gamma [1 + (WL/R_S)^2]}{\alpha g_m R_S (WL/R_S)^2} \leftarrow$$



Where $\alpha = g_m / g_{do}$

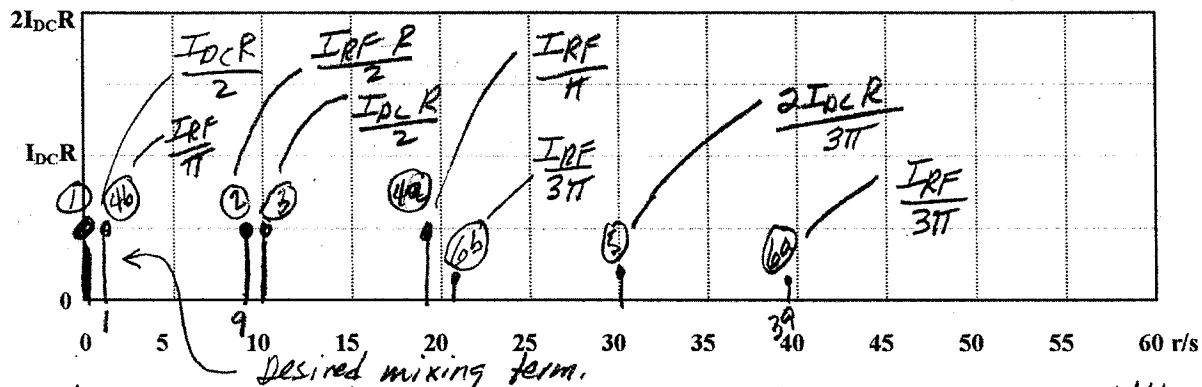2. (30 points) Assume that M_1 and M_2 switch completely and instantaneously at the zero crossings of the RF signal that has a 50% duty cycle. The LO signal is $V_{LO} \cos \omega_{LO} t$ and the tail current is $(I_{DC} + I_{RF} \cos \omega_{RF} t)$. For simplicity, let $\omega_{LO} = 10$ and $\omega_{RF} = 9$.

Determine and plot on the graph below the peak voltage frequency components in V_{out} . Carefully label both the amplitude and frequency of each component. (Neglect switching frequency components higher than the third harmonic)



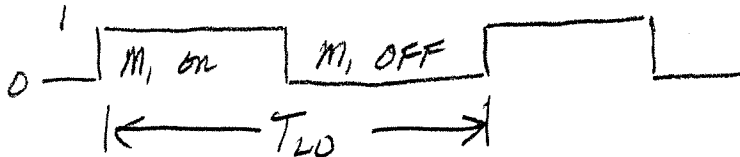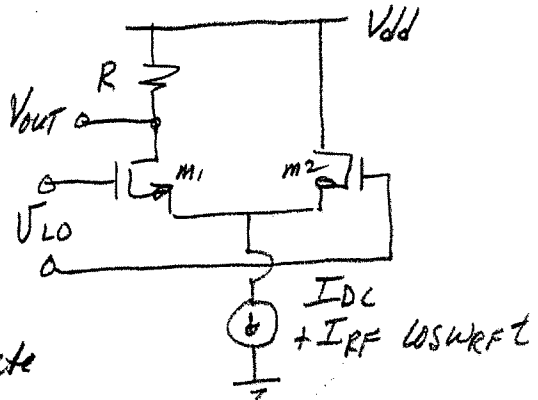Let's assume that V_{LO} is large enough to fully switch m_1 - m_2 . V_{out} Since the circuit is unbalanced, either all or none of the tail current is passed through R to create V_{IF} . Hence, the appropriate switch waveform is at ω_{LO} is:



The Fourier series of this switching waveform is:

$$V(t) = \underbrace{\frac{1}{2}}_{\text{DC Component of switching waveform}} + \sum_{n=1}^{\infty} a_n \cos n \omega_{LO} t$$

DC
Component
of switching
waveform

$$\text{Where } a_n = \frac{\sin n\pi/2}{n\pi/2}$$

$$\begin{cases} a_1 = \frac{2}{\pi} \\ a_2 = 0 \\ a_3 = -\frac{2}{3\pi} \\ a_4 = 0 \\ \vdots \end{cases}$$

2. (cont—blank work page)

$$\begin{aligned}
 \Rightarrow V_{IF} &= \left[\frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO} t - \frac{2}{3\pi} \cos 3\omega_{LO} t \right] \cdot [I_{DC} + I_{RF} \cos \omega_{RF} t] R \\
 &= \left[\overset{\textcircled{1}}{\frac{I_{DC}}{2}} + \overset{\textcircled{2}}{\frac{I_{RF}}{2} \cos \omega_{RF} t} + \overset{\textcircled{3}}{\frac{2I_{DC}}{\pi} \cos \omega_{LO} t} \right. \\
 &\quad + \overset{\textcircled{4}}{\frac{2I_{RF}}{\pi} \cos \omega_{LO} t \cos \omega_{RF} t} - \overset{\textcircled{5}}{\frac{2I_{DC}}{3\pi} \cos 3\omega_{LO} t} \\
 &\quad \left. - \overset{\textcircled{6}}{\frac{2I_{RF}}{3\pi} \cos 3\omega_{LO} t \cos \omega_{RF} t} \right] R
 \end{aligned}$$

Interpretation of terms: (Plotted on graph on previous page.)

① $\frac{I_{DC} R}{2} \Rightarrow$ DC term at output


② $\frac{I_{RF} R}{2} \cos \omega_{RF} t \Rightarrow$ RF feedthrough term at output—
Not present in balanced version of circuit

③ $\frac{2I_{DC} R}{\pi} \cos \omega_{LO} t \Rightarrow$ LO feedthrough term at output

④ $= \frac{I_{RF}}{\pi} \left[\overset{\textcircled{4a}}{\underbrace{\cos(\omega_{LO} + \omega_{RF})t}_{\text{upconverted term}}} + \overset{\textcircled{4b}}{\underbrace{\cos(\omega_{LO} - \omega_{RF})t}_{\text{downconverted term}}} \right]$


⑤ $\frac{2I_{DC} R}{3\pi} \cos 3\omega_{LO} t \Rightarrow$ third harmonic of LO at output

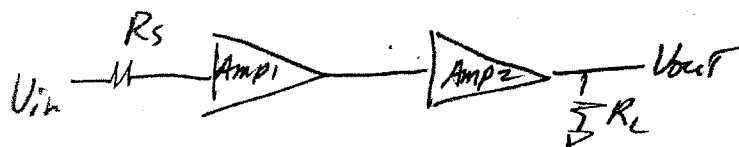⑥ $= \frac{I_{RF}}{3\pi} \left[\overset{\textcircled{6a}}{\cos(3\omega_{LO} + \omega_{RF})t} + \overset{\textcircled{6b}}{\cos(3\omega_{LO} - \omega_{RF})t} \right]$



EE 538B Midterm No. 2 - Spring 2002

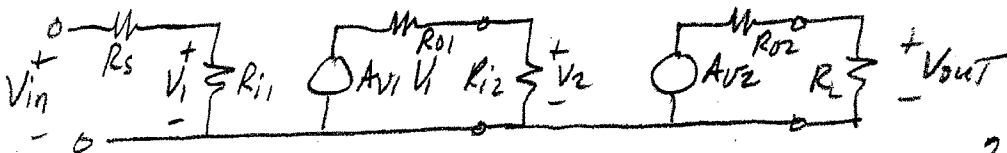3. (20 points) An amplifier with $NF_1 = 6\text{dB}$, power gain $A_{P1} = 4\text{dB}$, and $IIP_{3,1} = 0\text{dBm}$ is cascaded with a second amplifier with $NF_2 = 10\text{dB}$, power gain $A_{P2} = 10\text{dB}$, and $IIP_{3,1} = -6\text{dBm}$. Assuming a matched condition at all nodes, what are the overall NF , A_P and IIP_3 values?



$$P_{OUT} = V_{in}^2 \left(\frac{R_{i1}}{R_s + R_{i1}} \right)^2 \cdot A_{V1}^2 \cdot \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right)^2 \cdot A_{V2}^2 \cdot \left(\frac{R_L}{R_L + R_{o2}} \right)^2 / R_L$$

$$P_{in} = V_{in}^2 \left(\frac{R_{i1}}{R_s + R_{i1}} \right)^2 / R_{i1}$$

$$A_P = \frac{P_{OUT}}{P_{in}} = A_{V1}^2 \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right)^2 \cdot A_{V2}^2 \left(\frac{R_L}{R_L + R_{o2}} \right)^2 \cdot \frac{R_{i1}}{R_L}$$

$$\text{Also, } A_{P1} = \frac{P_{OUT1}}{P_{in}} = A_{V1}^2 \left(\frac{R_{i2}}{R_{o1} + R_{i2}} \right)^2 \cdot \frac{R_{i1}}{R_{i2}} = \frac{A_{V1}^2}{4} \text{ with matched condition}$$

$$\therefore A_P = \frac{P_{OUT}}{P_{in}} = \frac{A_{V1}^2}{4} \cdot \frac{A_{V2}^2}{4} \text{ (with matched conditions)}$$

$$A_P = A_{P1} \cdot A_{P2} = \boxed{14\text{dB}} \leftarrow A_P$$

$$NF_2 = 10\text{dB} \Rightarrow F_2 = 10^{10} = 10 \quad A_{P1} = 4\text{dB} \Rightarrow 10^{0.4} = 2.51$$

$$NF_1 = 6\text{dB} \Rightarrow F_1 = 10^{0.6} = 3.98$$

$$\text{Friis Equation} \Rightarrow NF = 1 + (F_1 - 1) + \frac{(F_2 - 1)}{A_{P1}}$$

$$= 1 + (3.98 - 1) + \frac{(10 - 1)}{2.51} = 7.566 \quad NF$$

$$= 8.79\text{dB} \leftarrow$$

$$\frac{1}{IIP_3^2} = \frac{1}{IIP_{3,AMP1}^2} + \frac{A_{V1}^2}{IIP_{3,AMP2}^2}$$

$$A_{V1}^2 = 4\text{dB} = 2.51$$


$$\frac{4}{4} \therefore A_{V1} = 3.17$$

$$IIP_{3,AMP1} = 0\text{dBm} = 10 \log \frac{V_{rms}^2}{50} \Rightarrow V_{rms1}^2 = 50 \times 10^{-3} \text{V}^2$$

$$IIP_{3,AMP2} = -6\text{dBm} \Rightarrow V_{rms2}^2 = 12.5 \times 10^{-3} \text{V}^2$$

$$\therefore \frac{1}{IIP_3^2} = \frac{1}{50 \times 10^{-3}} + \frac{10}{12.5 \times 10^{-3}} \Rightarrow IIP_3 = 34.9 \times 10^{-3} \text{V} \Rightarrow 10 \log \frac{V_{rms}^2}{50} = -16.1\text{dBm} \leftarrow$$

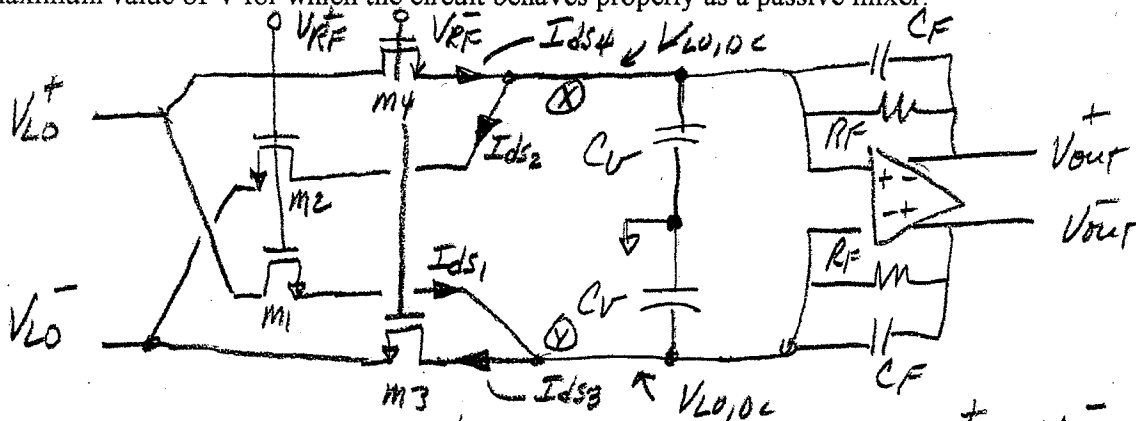4. (20 points) A passive mixer circuit is shown below. Assume $V_{RF,DC}=3.85V$, $V_{LO,DC}=1.15V$, $V_{DD}=5.0V$, and $V_T=1.0V$. Also assume that $V_{RF}=V\cos\omega_{RF}t$ and $V_{LO}=V\cos\omega_{LO}t$. Determine the maximum value of V for which the circuit behaves properly as a passive mixer.



Note $V_{RF} = V_{RF}^+ - V_{RF}^-$ and $V_{LO} = V_{LO}^+ - V_{LO}^-$

$$\Rightarrow V_{RF}^+ = V_{RF,DC} + \frac{V}{2} \cos \omega_{RF} t; V_{RF}^- = V_{RF,DC} - \frac{V}{2} \cos \omega_{RF} t$$

$$\text{and } V_{LO}^+ = V_{LO,DC} + \frac{V}{2} \cos \omega_{LO} t; V_{LO}^- = V_{LO,DC} - \frac{V}{2} \cos \omega_{LO} t$$

Transistors M_1, M_4 must remain ON and in non-saturation:

$$\textcircled{1} (V_{GS} - V_T) \geq \text{for } M_4 \Rightarrow V_{RF,DC} - \frac{V}{2} \cos \omega_{RF} t - V_{LO,DC} - V_T \geq 0$$

$$\cos \omega_{RF} t = 1 \Rightarrow V_{RF,DC} - \frac{V}{2} - V_{LO,DC} - V_T \geq 0$$

$$3.85V - \frac{V}{2} - 1.15V - 1.0V \geq 0$$

WORST-CASE must be satisfied $\therefore V \leq 3.4V$

$$\textcircled{2} V_{DS} < (V_{GS} - V_T) \text{ for } M_4 \text{ in non-saturation:}$$

$$\Rightarrow (V_{LO}^+ - V_{LO,DC}) < (V_{RF}^- - V_{LO,DC} - V_T)$$

$$\Rightarrow V_{LO}^+ < (V_{RF}^- - V_T)$$

$$(V_{LO,DC} + \frac{V}{2} \cos \omega_{LO} t) < (V_{RF,DC} - \frac{V}{2} \cos \omega_{RF} t - V_T)$$

$$\text{WORST-CASE CONDITION } \left\{ (1.15V + \frac{V}{2}) < (3.85V - \frac{V}{2} - 1.0) \right\}$$

$$V < 1.7V$$

Condition $\textcircled{3}$ dominates $\Rightarrow \boxed{V < 1.7V}$