



EE141-Spring 2010 Digital Integrated Circuits

Lecture 12 Inverter Delay + Energy

EECS141

Lecture #12

1

Administrativa


- ❑ HW 4 Due Today. New HW today as well.
- ❑ Final Lab next week
- ❑ Project to be launched on Wednesday!
Probably is wise to be in class that day.

EECS141

Lecture #12

2

CMOS Inverter VTC

 


EECS141

Lecture #13

3

Impact of Sizing

 


EECS141

Lecture #13

4

Impact of Process Variations

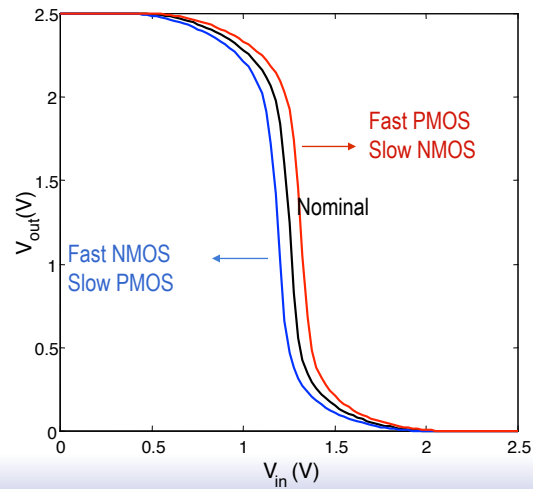


EECS141

Lecture #13

5

Process Variations

 Not all transistors are alike
Impacts parameters such as reliability and performance



Define process corners: SS, FF, SF, FS

EECS141

Lecture #13

6

CMOS Switching Delay




EECS141

Lecture #13

7⁷

MOS Transistor as a Switch


- Discharging a capacitor

 

$$i_D = i_D(v_{DS})$$

$$i_D = C \frac{dV_{DS}}{dt}$$

- We modeled this with:

 

$$t_p = \ln(2) RC$$

EECS141

Lecture #13

8

MOS Transistor as a Switch

- Real transistors aren't exactly resistors
 - Look more like current sources in saturation
- Two questions:
 - Which region of IV curve determines delay?
 - How can that match up with the RC model?



EECS141

Lecture #13

9

Transistor Discharging a Capacitor

- With a step input:

  

- Transistor is in (velocity) saturation during entire transition from V_{DD} to $V_{DD}/2$


EECS141

Lecture #13

10

Switching Delay

 - In saturation, transistor basically acts like a current source:




$$V_{OUT} = V_{DD} - (I_{DSAT}/C)t \longrightarrow \boxed{t_p = C(V_{DD}/2)/I_{DSAT}}$$

Defining I_{DSAT}

Switching Delay (with Output Conductance)

- Including output conductance:

 

$$V_{OUT} = (V_{DD} + \lambda^{-1}) e^{-t/(C/\lambda I_{DSAT})} - \lambda^{-1}$$

- For “small” λ :

$$t_p \approx \frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}}$$


EECS141

Lecture #13

13

RC Model

- Transistor current not linear on V_{OUT} – how is the RC model going to work?
- Look at waveforms:
- Voltage looks like a ramp for RC too

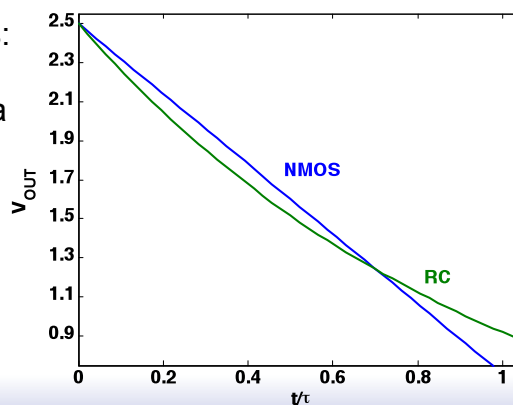

EECS141

Lecture #13

14

Finding Req

- Match the delay of the RC model with the actual delay:

$$\begin{aligned} t_p &= t_{p,RC} \\ \frac{C(V_{DD}/2)}{(1 + \lambda V_{DD}) I_{DSAT}} &= \ln(2) R_{eq} C \quad \longrightarrow \quad R_{eq} = \frac{(V_{DD}/2)}{\ln(2)(1 + \lambda V_{DD}) I_{DSAT}} \end{aligned}$$


- Often just:

$$R_{eq} \approx \frac{1}{2 \cdot \ln(2)} \frac{V_{DD}}{I_{DSAT}}$$

- Note that the book uses a different method and gets $0.75 \cdot V_{DD}/I_{DSAT}$ instead of $\sim 0.72 \cdot V_{DD}/I_{DSAT}$.

The Book's Method

The Transistor as a Switch

 

EECS141

Lecture #13

17

The Transistor as a Switch

Table 3.3 Equivalent resistance R_{eq} ($WL = 1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by WL .


V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

EECS141

Lecture #13

18

Inverter Capacitances

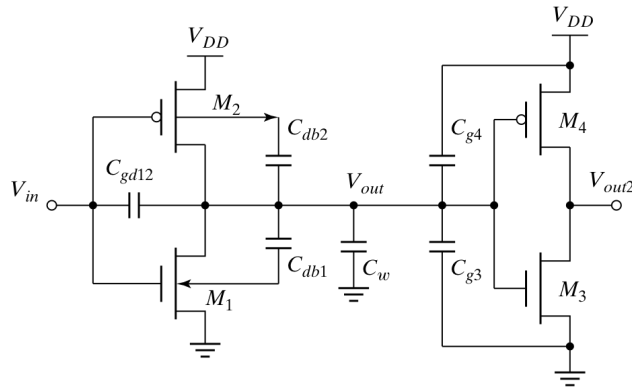

EECS141

Lecture #13

19

Inverter Capacitance Model

- Capacitance models important for analysis and intuition
 - But often need something simpler to work with
- Simpler model:
 - Lump together as effective linear capacitance to (ac) ground
 - In most processes: $C_g = C_d = 1.5 - 2\text{fF} \cdot W(\mu\text{m})$



EECS141

Lecture #13

20

Lumping the Caps


EECS141

Lecture #13

21

The Miller Effect

- As V_{in} increases, V_{out} drops
 - Once get into the transition region, gain from V_{in} to $V_{out} > 1$
- So, C_{gd} experiences voltage swing larger than V_{in}
 - Which means you need to provide more charge
 - Makes C_{gd} look larger than it really is
- Known as the “Miller Effect” in the analog world

 


EECS141

Lecture #13

22

Model Calibration - Capacitance

- Can calculate C_g , C_d based on tech. parameters
 - But these models are simplified too
- Another approach:
 - Tune (e.g., in spice) the linear capacitance until it makes the simplified circuit match the real circuit
 - Matching could be for delay, power, etc.

 


EECS141

Lecture #13

23

Model Calibration for Delay

 


- For gate capacitance:
 - Make inverter fanout 4
 - Adjust C_{load} until $Delay1 = Delay2$
- For diffusion capacitance
 - Replace inverter “A” with a diffusion capacitance load

EECS141

Lecture #13

24

Delay Calibration

 


- Why did we need that last inverter stage?

Propagation Delay



Transient Response

 


EECS141

Lecture #13

27

Delay as a function of V_{DD}

 

EECS141

Lecture #13

28

Step Inputs?


- Derived RC model assuming input was a step
 - But input is not a step
 - Transistor turns on gradually
- Let's look at gate switching more carefully
 - Use our models to understand the effect of input slope

EECS141

Lecture #13

29

Input Slope Dependence

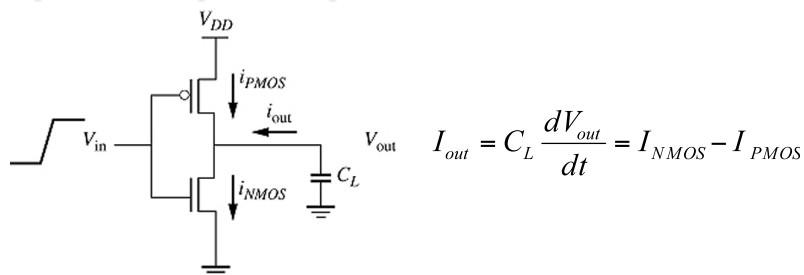

- One way to analyze slope effect
 - Plug non-linear IV into diff. equation and solve...
- Simpler, approximate solution:
 - Use V_T^* model

EECS141

Lecture #13

30

Slope Analysis

- For falling edge at output:
 - For reasonable inputs, can ignore I_{PMOS}
 - Either V_{ds} is very small, or V_{gs} is very small
- So, output current ramp starts when $V_{in} = V_T^*$
 - Could evaluate the integral
 - Learn more by using an intuitive, graphical approach


Result Summary

- For reasonable input slopes:

$$t_{p,ramp} = t_{p,step} + \frac{V_T^*}{V_{DD}} \cdot t_{p,in}$$

Model vs. Spice Data

- For reasonable input slope
 - Model matches Spice very well
- Model breaks with very large t_r
 - Input looks “DC” – traces out VTC
 - Have other problems here anyways
 - Short-circuit current

 

EECS141

Lecture #13

33

CMOS Power Dissipation



EECS141

Lecture #13

34

Where Does Power Go in CMOS?


- ❑ Switching power
 - Charging/discharging capacitors
- ❑ Leakage power
 - Transistors are imperfect switches
- ❑ Short-circuit power
 - Both pull-up and pull-down on during transition
- ❑ Static currents
 - Biasing currents, in e.g. analog, memory

EECS141

Lecture #13

35

Dynamic Power Consumption

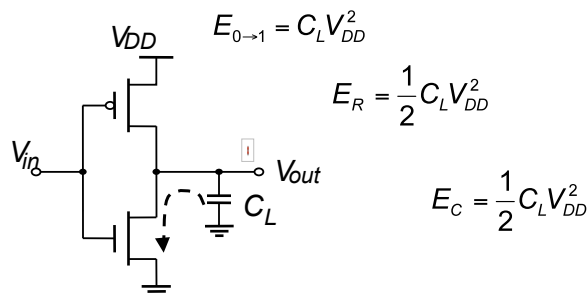

- ❑ One half of the energy from the supply is consumed in the pull-up network, one half is stored on C_L
- ❑ Energy from C_L is dumped during the $1 \rightarrow 0$ transition

EECS141

Lecture #13

36

Dynamic Power Consumption

Power = Energy/transition • Transition rate

$$= C_L V_{DD}^2 \cdot f_{0 \rightarrow 1}$$

$$= C_L V_{DD}^2 \cdot f \cdot \alpha_{0 \rightarrow 1}$$

$$= C_{switched} V_{DD}^2 \cdot f$$

- Power dissipation is data dependent – depends on the switching probability
- Switched capacitance $C_{switched} = C_L \cdot \alpha_{0 \rightarrow 1}$

EECS141

Lecture #13

37

Transition Activity and Power

- Energy consumed in N cycles, E_N :

$$E_N = C_L \cdot V_{DD}^2 \cdot n_{0 \rightarrow 1}$$

$n_{0 \rightarrow 1}$ – number of 0→1 transitions in N cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f = \left(\lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n_{0 \rightarrow 1}}{N}$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$

EECS141

Lecture #13

38