

---

# EE288 Data Conversions/Analog Mixed-Signal ICs

## Spring 2018

### Lecture 12: Latched Comparator

Prof. Sang-Soo Lee  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)  
ENG-259


# Course Schedule – Subject to Change

Date	Topics
24-Jan	Course introduction and ADC architectures
29-Jan	Converter basics: AAF, Sampling, Quantization, Reconstruction
31-Jan	ADC dynamic performance metrics, Spectrum analysis using FFT
5-Feb	ADC & DAC static performance metrics, INL and DNL
7-Feb	OPAMP and bias circuits review
12-Feb	SC circuits review
14-Feb	Sample and Hold Amplifier - Reading materials
19-Feb	Flash ADC and Comparators: Regenerative Latch
21-Feb	Comparators: Latch offset, preamp, auto-zero
26-Feb	<del>Finish Flash ADC</del>
28-Feb	<del>DAC Architectures - Resistor, R-2R</del>
5-Mar	<del>DAC Architectures - Current steering, Segmented</del>
7-Mar	DAC Architectures - Capacitor-based
12-Mar	SAR ADC with bottom plate sampling
14-Mar	SAR ADC with top plate sampling
19-Mar	Midterm Review
21-Mar	Midterm exam
26-Mar	Spring break
28-Mar	Spring break
2-Apr	Pipelined ADC stage - comparator, MDAC, x2 gain
4-Apr	Pipelined ADC bit sync and alignment using Full adders
9-Apr	Pipelined ADC 1.5bit vs multi-bit structures
11-Apr	Fully-differential OPAMP and Switched-capacitor CMFB
16-Apr	Single-slope ADC
18-Apr	Oversampling & Delta-Sigma ADCs
23-Apr	Second- and higher-order Delta-Sigma Modulator.
25-Apr	Hybrid ADC - Pipelined SAR
30-Apr	Hybrid ADC - Time-Interleaving
2-May	ADC testing and FoM
7-May	Project presentation 1
8-May	Project presentation 2
14-May	Final Review
20-May	Project Report Due by 6 PM

← Latched Comparator

**\*Midterm Exam dates are approximate and subject to change with reasonable notice.**

# Single-ended Latched Comparator

 


$$C \frac{dV}{dt} = g_m \Delta V$$

$$V(0) = \Delta V$$

$$V(t) = \Delta V e^{\frac{t}{\tau}}$$



$$\tau = \frac{C}{g_m}$$

 


$$\text{Gain} = \frac{V_{DD}}{\Delta V} = e^{\frac{t}{\tau}}$$

10bit requires  $t = 7\tau$

# Differential Latched Comparator

  

# Differential Latched Comparator

 

During  $\phi_1$ , input is sampled at X & Y  
During  $\phi_2$ , latch regenerates

# Nonidealities in Latched Comparator


---

- Mismatch in transistors
- Mismatch in switch
- Mismatch in Capacitance
- Dynamic mismatch

# MOSFET Mismatch

- Mismatch between two identically drawn transistors

- Vth mismatch
- Beta mismatch

 

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 = \frac{\beta}{2} (V_{GS} - V_{TH})^2$$

- Important contributions are  $t_{ox}$  and Dopant concentration in the channel region
- Improves with scaling in  $t_{ox}$

$$\sigma_{\Delta V_{TH}} = \frac{A_{V_{TH}}}{\sqrt{WL}}$$

Technology parameter


Best guess

$$\frac{A_{V_{TH}}}{t_{ox}} \approx \frac{\text{mV} \cdot \mu\text{m}}{\text{nm}}$$

To reduce Vth mismatch

- (1) Use transistor with low  $A_{vth}$
- (2) Increase the size of the transistors


# Latched Comparator with Preamp

 

- Why bother using pre-amplification ( $A_v$ )?
  - Offset
    - Hard to build latches with offset  $< 10 \dots 100\text{mV}$
    - Use pre-amplification to lower input referred offset
  - Common mode rejection
  - Attenuate "kickback noise"
  - Metastability



# Input Referred Offset

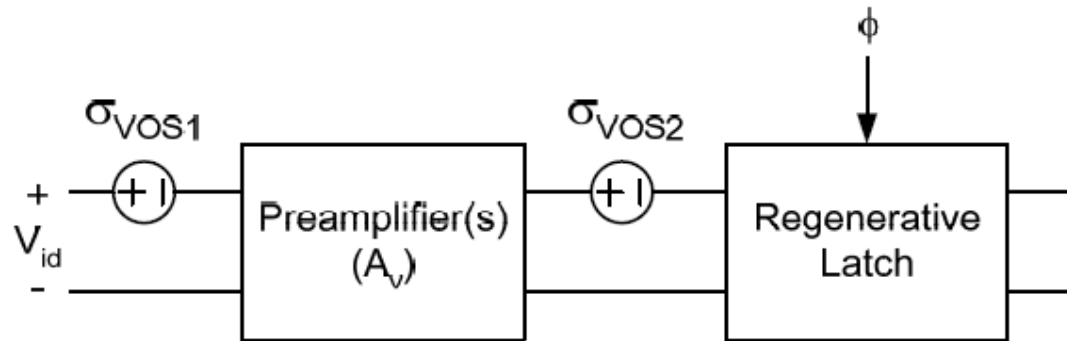


$$\sigma_{VOS}^2 = \sigma_{VOS1}^2 + \frac{1}{A_v^2} \sigma_{VOS2}^2$$


- Example:  $\sigma_{VOS1}=3\text{mV}$ ,  $\sigma_{VOS2}=30\text{mV}$ ,  $A_v=10$

$$\sigma_{VOS} = \sqrt{(3\text{mV})^2 + \frac{1}{10^2} (30\text{mV})^2} = 4.2\text{mV}$$

# Multi-Stage Amp Offset

 

Individual stage

 


Total input-referred

$$V_{out} = V_{os1}A_1A_2A_3 + V_{os2}A_2A_3 + V_{os3}A_3$$

$$V_{out} = V_{os}A_1A_2A_3$$

$$A_T = A_1 \cdot A_2 \cdot A_3$$
$$V_{os} = V_{os1} + \frac{V_{os2}}{A_1} + \frac{V_{os3}}{A_1 \cdot A_2}$$

# Input Offset Cancellation

 


Two-phase operation,

- (a) Reset phase ( $\Phi_1$ ) to store offset into the capacitor
- (b) Comparison phase ( $\Phi_2$ ) to subtract the offset from the input


# Input Offset Cancellation

During  $\phi_1$

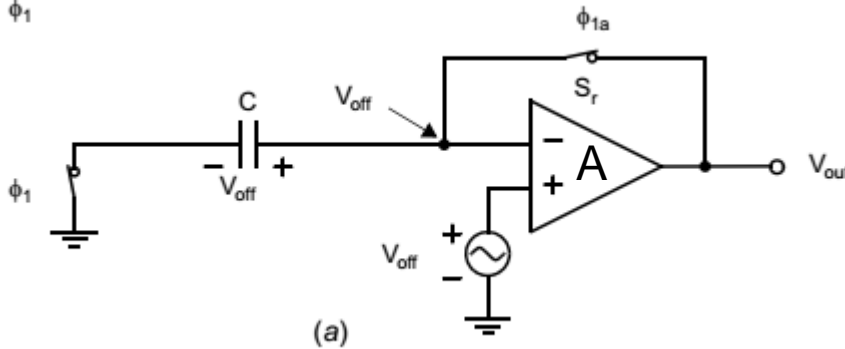

$$\begin{aligned} V_c &= A(V_{\text{off}} - V_c) \\ &= \frac{A}{1+A} \cdot V_{\text{off}} \\ &\approx V_{\text{off}} \end{aligned}$$

During  $\phi_2$

 

$$\begin{aligned} V_{\text{out}} &= -A(V_{\text{in}} + V_c - V_{\text{off}}) \\ &= -A\left(V_{\text{in}} - \frac{V_{\text{off}}}{1+A}\right) \end{aligned}$$

**Closed loop stability required**

Input-referred offset:

$$V_{\text{os,in}} = \frac{V_{\text{os}}}{1+A}$$