 


Inverter Chain

Lecture 10



Advanced Digital IC Design



Khosrow Ghadiri



- Ideal Inverter

  



- Switching Threshold
- The switching threshold defined as a voltage
- Where



$$V_M = V_{OUT} = V_{IN}$$

- Since

$$V_{GS} = V_{DS}$$

- Both pMOS and nMOS are in saturation.
- For velocity saturation
- Ignoring the channel modulation $\lambda = 0$
  
$$k_n V_{DSn}(sat) \left(V_M - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right) + k_p V_{DSP}(sat) \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSP}(sat)}{2} \right) = 0$$





- Switching Threshold



$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r}$$

- Where r compares the relative strength of pMOS and nMOS

$$r = \frac{k_p V_{DSp} (sat)}{k_n V_{DSn} (sat)} = \frac{\mu_p (sat) W_p}{\mu_n (sat) W_n}$$

- For the $t_{ox} (pMOS) = t_{ox} (nMOS)$
  
$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}$$







- Switching Threshold
- For comparable high and low noise margin

$$V_M \approx \frac{rV_{DD}}{1+r} = \frac{V_{DD}}{2}$$

- Which requires $r = 1$
- Then the pMOS device should be sized to

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSn}(sat)}{k'_p V_{DSp}(sat)}$$

  - Making W_p wider results in $r > 1$ and move V_M upper than the middle closer to V_{DD} and increasing the strength of nMOS move the switching voltage V_M closer to GND.





- Switching Threshold

- For desired value of the threshold voltage V_M , the pMOS to nMOS transistor sizes to set



$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSn}(sat) \left(V_M - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right)}{k'_p V_{DSp}(sat) \left(V_{DD} - V_M + V_{Tp} + \frac{V_{DSp}(sat)}{2} \right)}$$

- For $V_{DS}(sat) > V_M - V_T$ where the saturation velocity is not occur, then


$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}$$

- Where

$$r = \sqrt{\frac{-k_p}{k_n}}$$

  

V_{DD}

 

- Length Modulation
- Ignoring length modulation results in infinite gain
- Considering length modulation results in infinite gain

$$k_n V_{DSn} (sat) \left(V_{IN} - V_{Tn} - \frac{V_{DSn} (sat)}{2} \right) (1 + \lambda V_{OUT})$$

$$+ k_p V_{DSp} (sat) \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{DSp} (sat)}{2} \right) (1 + \lambda_p V_{OUT} - \lambda_p V_{DD}) = 0$$

- Differentiating the output with respect to the input


$$\frac{dV_{out}}{dV_{in}} = \frac{k_n V_{DSn} (sat) (1 + \lambda_n V_{OUT}) + k_p V_{DSp} (sat) (1 + \lambda_p V_{OUT} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSn} (sat) \left(V_{IN} - V_{Tn} - \frac{V_{DSn} (sat)}{2} \right) + \lambda_p k_p V_{DSp} (sat) \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{DSp} (sat)}{2} \right)}$$

- Ignoring some second-order terms and setting $V_{IN} = V_M$ results in gain

$$g = \frac{1}{I_{DS} (V_M)} \frac{k_n V_{DSn} (sat) + k_p V_{DSp} (sat)}{\lambda_n - \lambda_p} = \frac{1 + r}{\left(V_M - V_{Tn} - \frac{V_{DSn} (sat)}{2} \right) (\lambda_n - \lambda_p)}$$




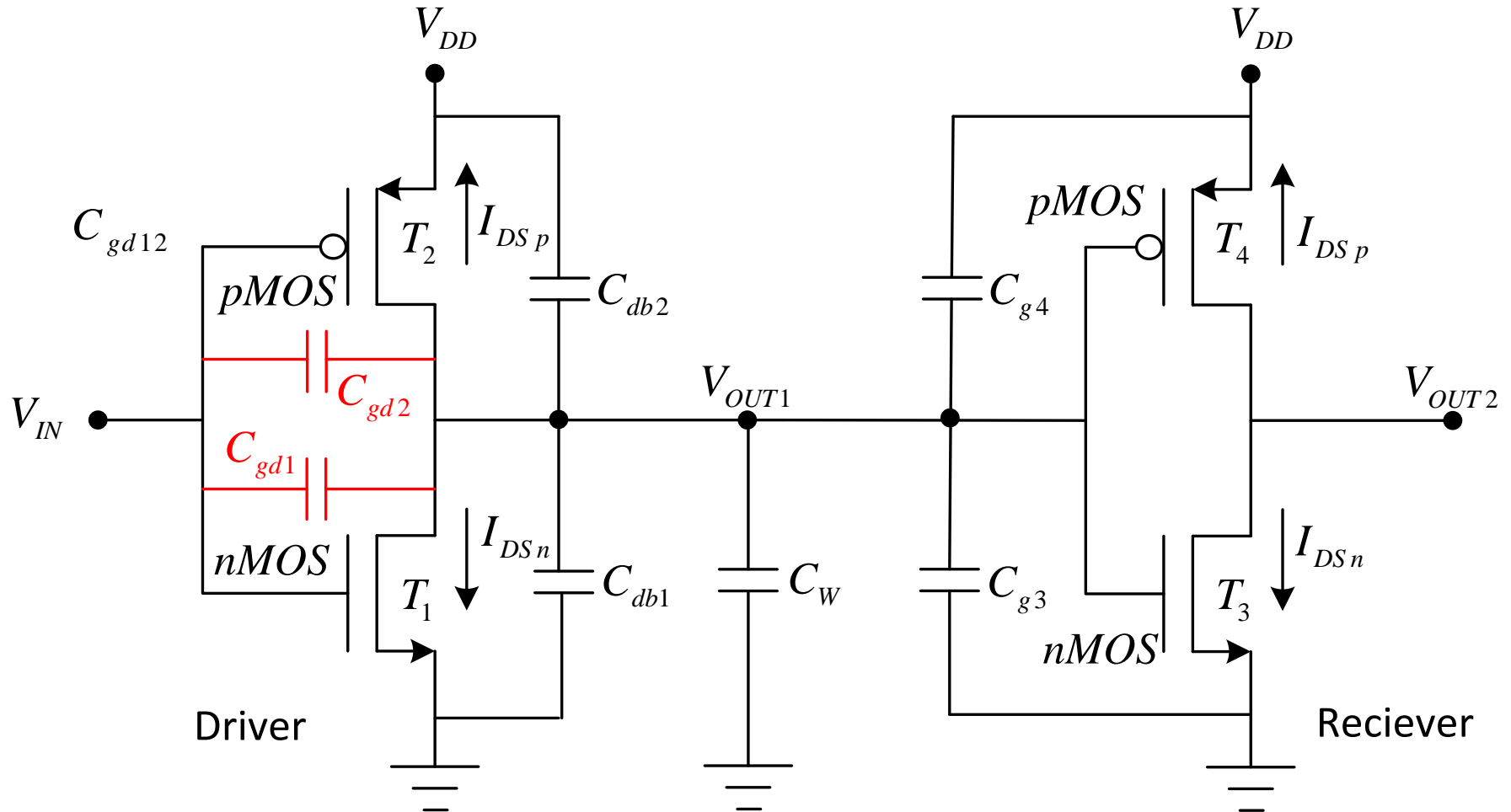- Effect of Capacitance (lumped capacitor model)







- Miller effect:

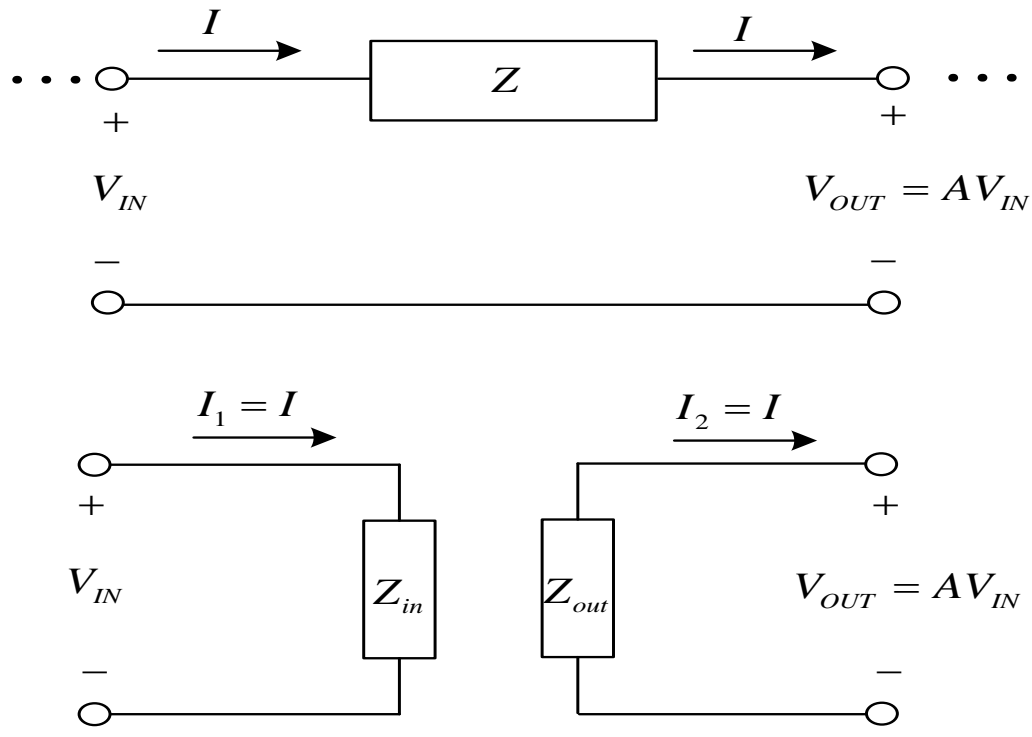

- The impedance Z can be replaced by two impedance Z_{in} connected between input node and ground and Z_{out} between the output node and ground



- Miller effect:

  


$$I_1 = \frac{V_{IN}}{Z_{in}} = I = \frac{V_{IN} - AV_{IN}}{Z} = \frac{V_{IN} - V_{OUT}}{Z}$$

$$Z_{in} = \frac{Z}{1 - A}$$




- Miller effect:

 

$$I_2 = \frac{0 - V_{OUT}}{Z_{OUT}} = \frac{0 - AV_{IN}}{Z_{OUT}} = I = \frac{V_{IN} - V_{OUT}}{Z} = \frac{V_{IN} - AV_{IN}}{Z} \quad Z_{out} = \frac{Z}{1 - \frac{1}{A}}$$



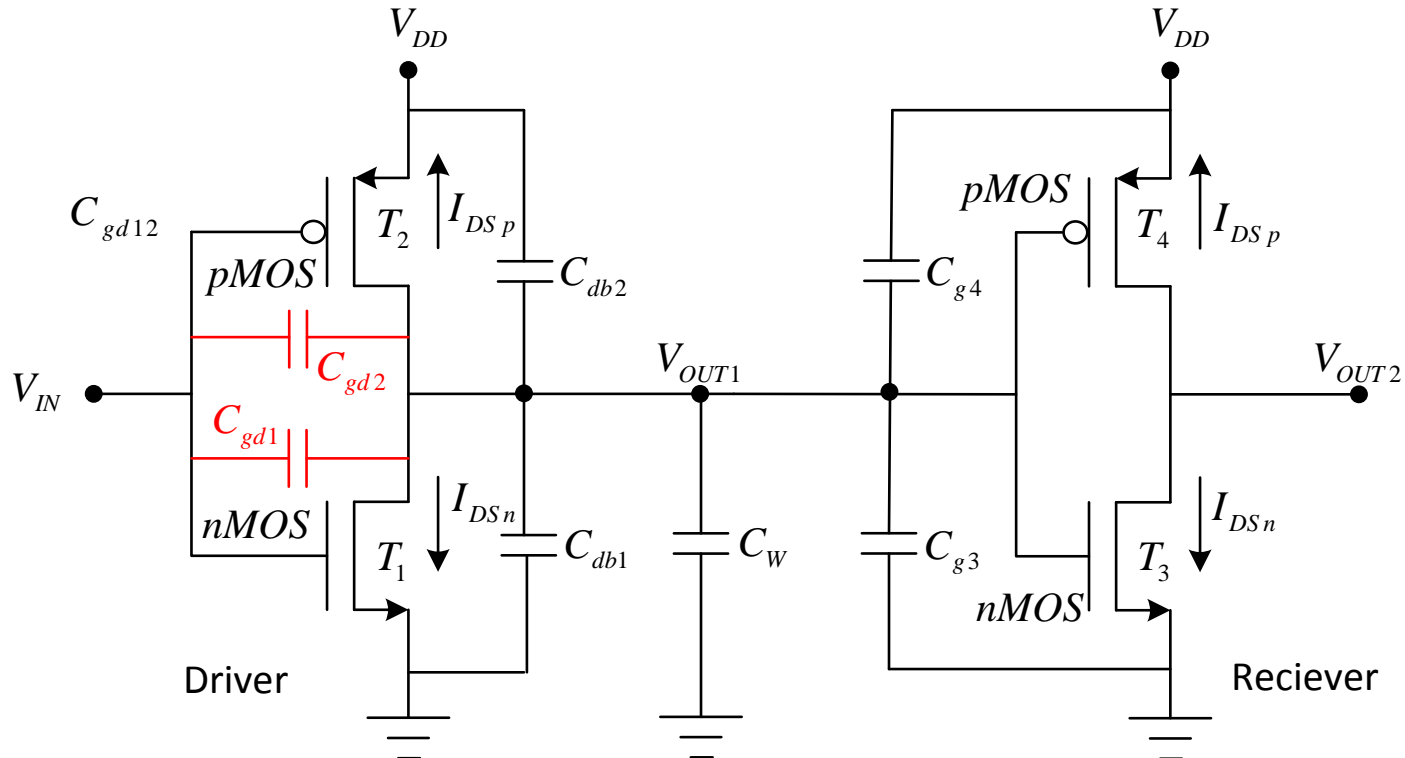
- Modeling floating gate-drain capacitor by a capacitor from output to ground



- The capacitor C_{gd1} can be replaced by an equivalent capacitor $2C_{gd1}$ between output node and ground. V_{IN} goes high and V_{OUT} goes low by the same amount. The voltage change across the capacitor C_{gd1} is twice the amount ($A=2$)



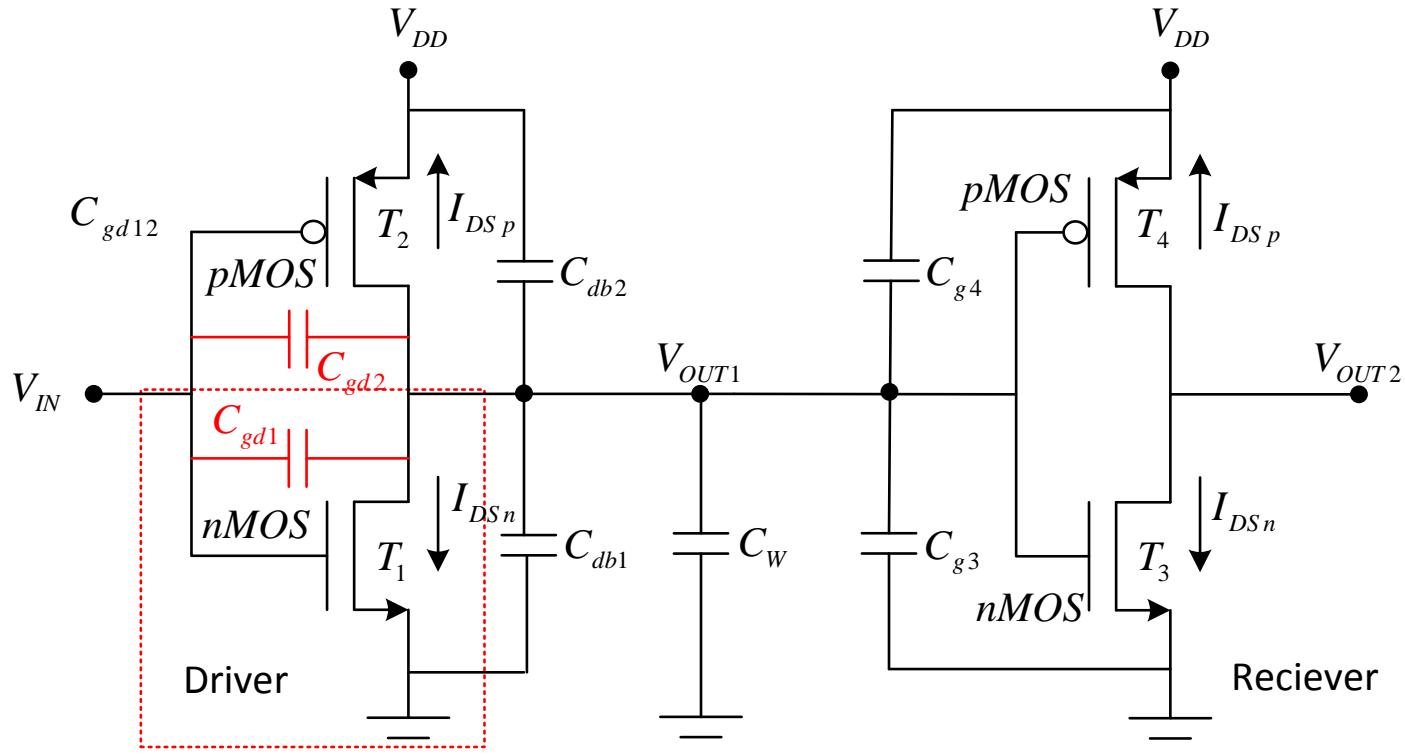
- Modeling floating gate-drain capacitor by a capacitor from output to ground



- The capacitor C_{gd1} can be replaced by an equivalent capacitor $2C_{gd1}$ between output node and ground. V_{IN} goes high and V_{OUT} goes low by the same amount. The voltage change across the capacitor C_{gd1} is twice the amount ($A=2$)



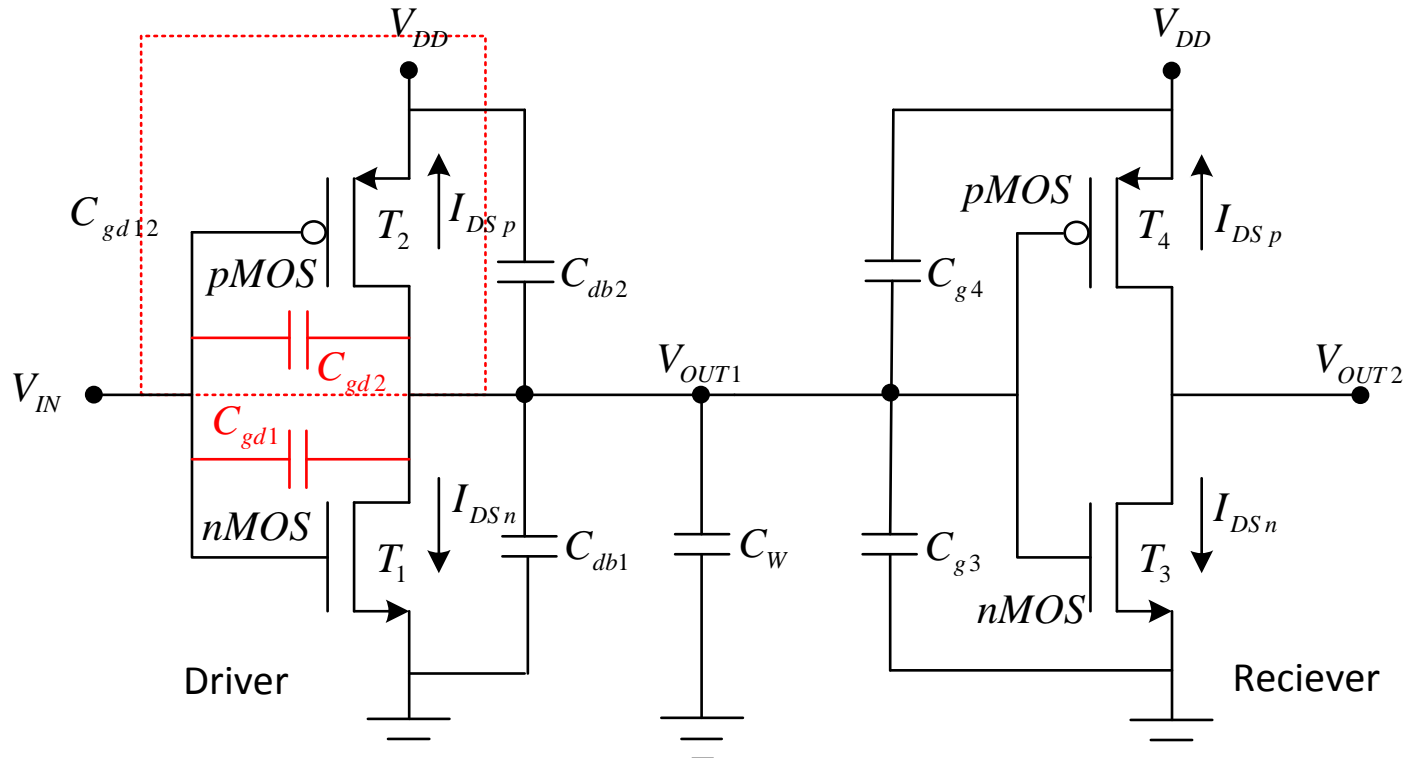
- Modeling floating gate-drain capacitor by a capacitor from output to ground



- The capacitor C_{gd2} can be replaced by an equivalent capacitor $2C_{gd2}$ between output node and ground. V_{IN} goes high and V_{OUT} goes low by the same amount. The voltage change across the capacitor C_{gd2} is twice the amount ($A=2$)



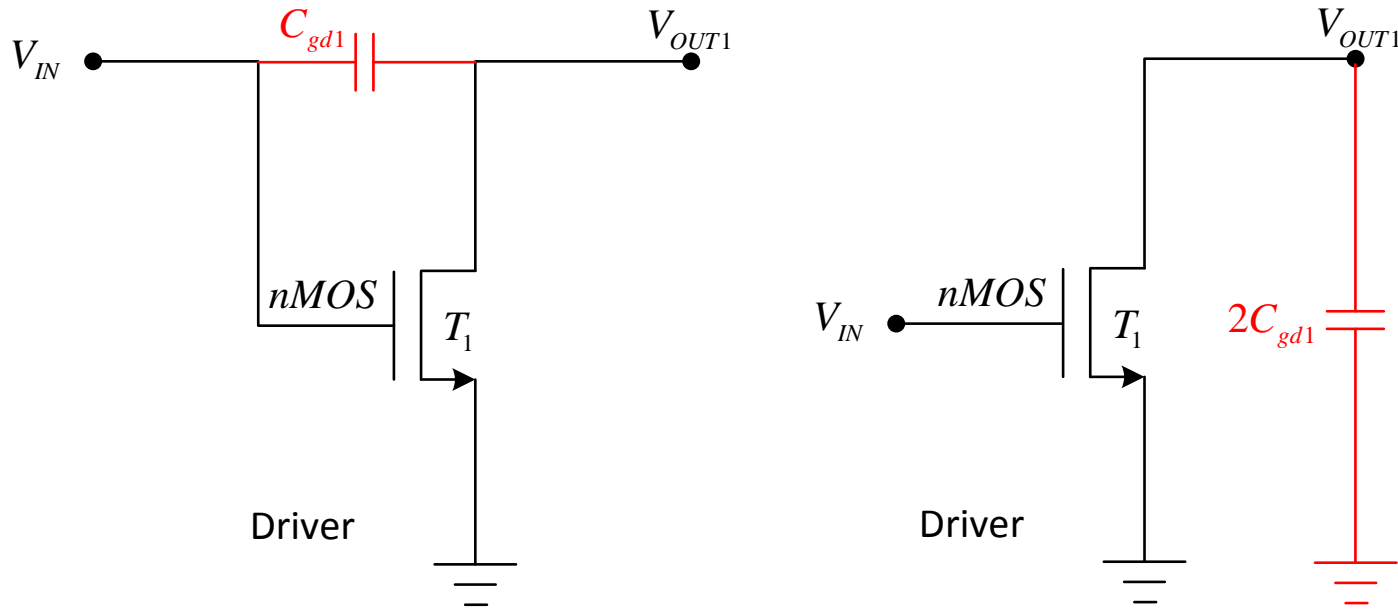
- Modeling floating gate-drain capacitor by a capacitor from output to ground



- Transistor T_1 and T_2 are either in cut-off or in saturation mode during the first half of the output transient up to 50%.
- The capacitor C_{gd1} can be replaced by an equivalent capacitor $2C_{gd1}$ between output node and ground. V_{IN} goes high and V_{OUT} goes low by the same amount. The voltage change across the capacitor C_{gd1} is twice the amount ($A=2$)



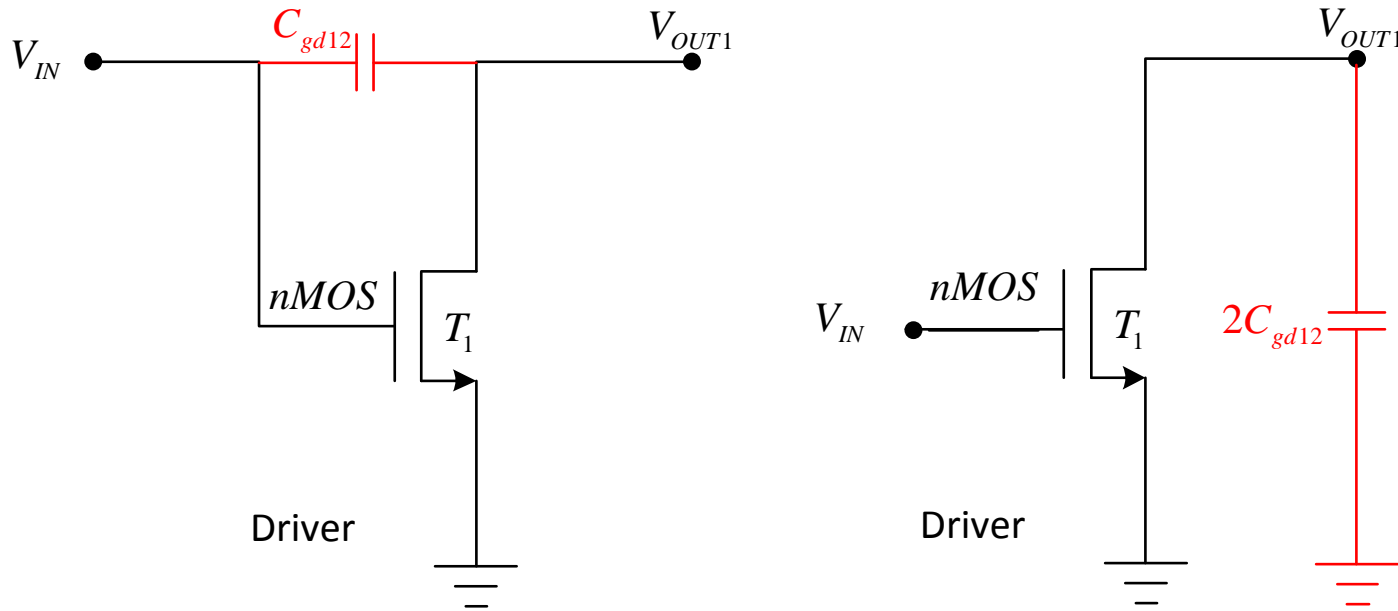
- Modeling floating gate-drain capacitor by a capacitor from output to ground



- Transistor and are either in cut-off or in saturation mode during the first half of the output transient up to 50%.
- The capacitor C_{gd12} can be replaced by an equivalent capacitor $2C_{gd12}$ between output node and ground. V_{IN} goes high and V_{OUT} goes low by the same amount. The voltage change across the capacitor C_{gd12} is twice the amount ($A=2$)



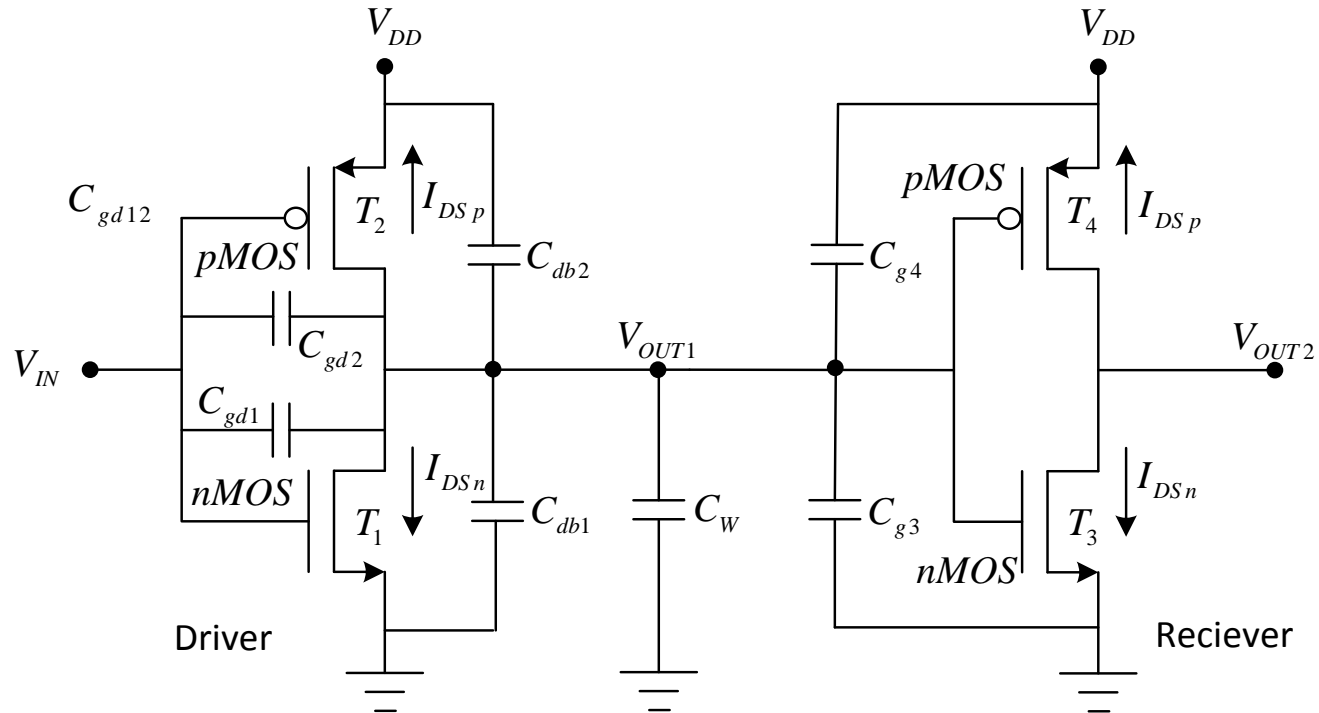
- Effect of Capacitance (lumped capacitor model)



- The capacitor C_{gd12} can be replaced by an equivalent capacitor $2C_{gd12}$ between output node and ground. V_{IN} goes high and V_{OUT} goes low by the same amount. The voltage change across the capacitor C_{gd12} is twice the amount ($A=2$)



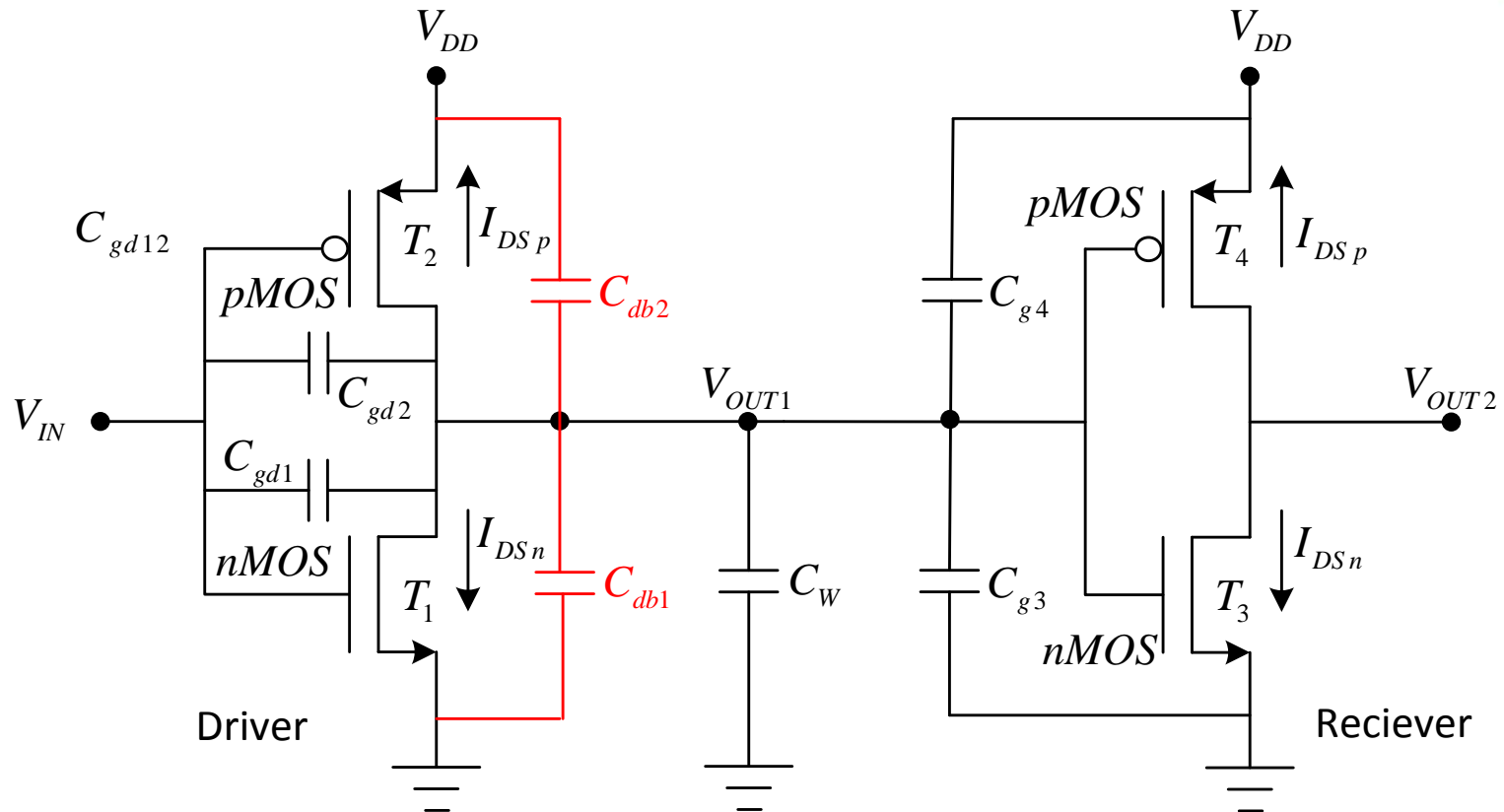
- Effect of Capacitance (lumped capacitor model)



- Capacitor C_{db1} and C_{db2} has a terminal capacitor at a constant voltage.
- C_{db1} and C_{db2} can be replaced with equal capacitance from output node to ground.



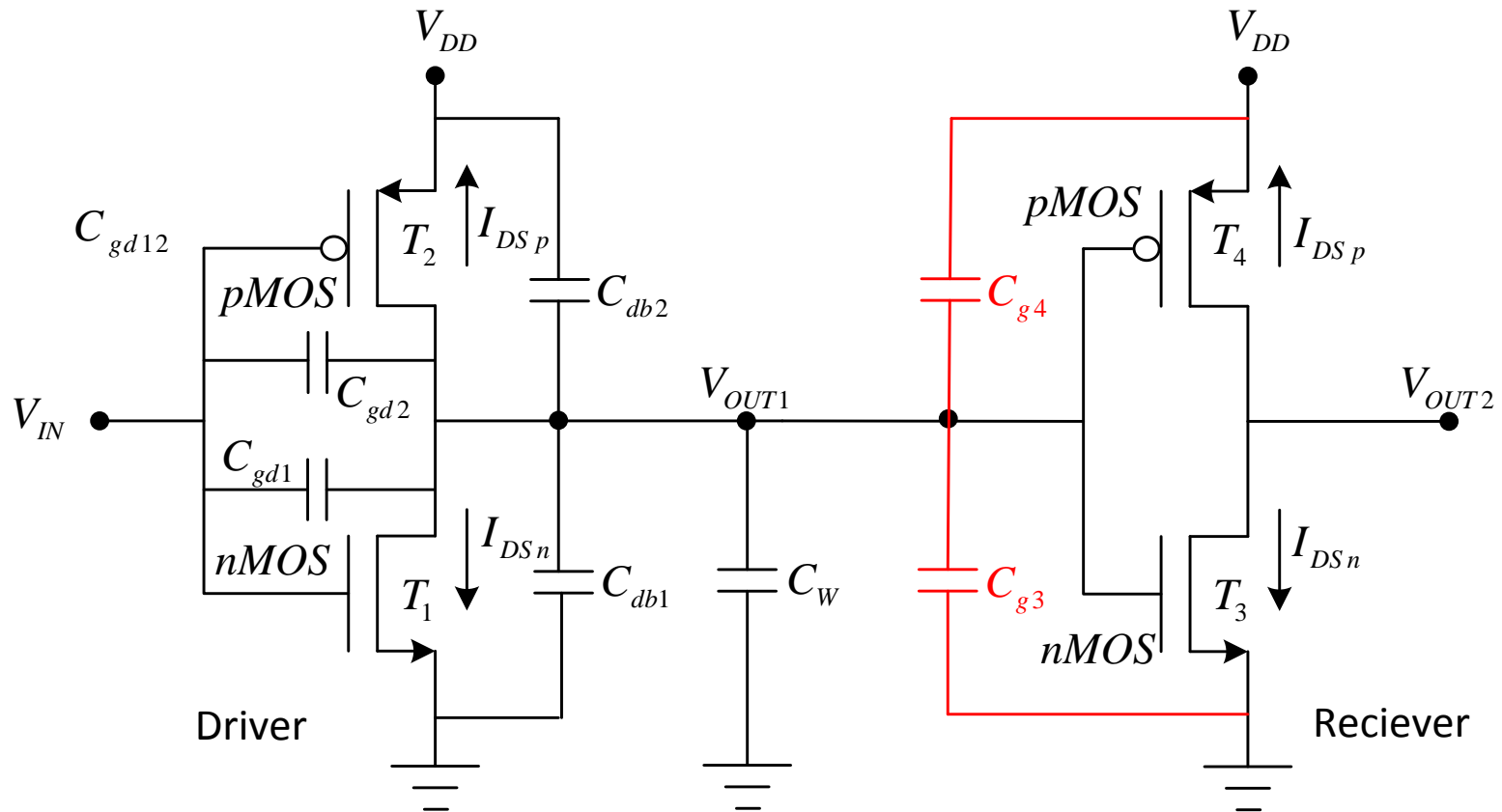- Effect of Capacitance (lumped capacitor model)




- The second inverter does not switch state. Input capacitors remain constant.

$$C_{g3} + C_{g4} = (WL)_3 C_{OX} + (WL)_4 C_{OX} + C_{gsov3} + C_{gdov3} + C_{gsov4} + C_{gdov4}$$



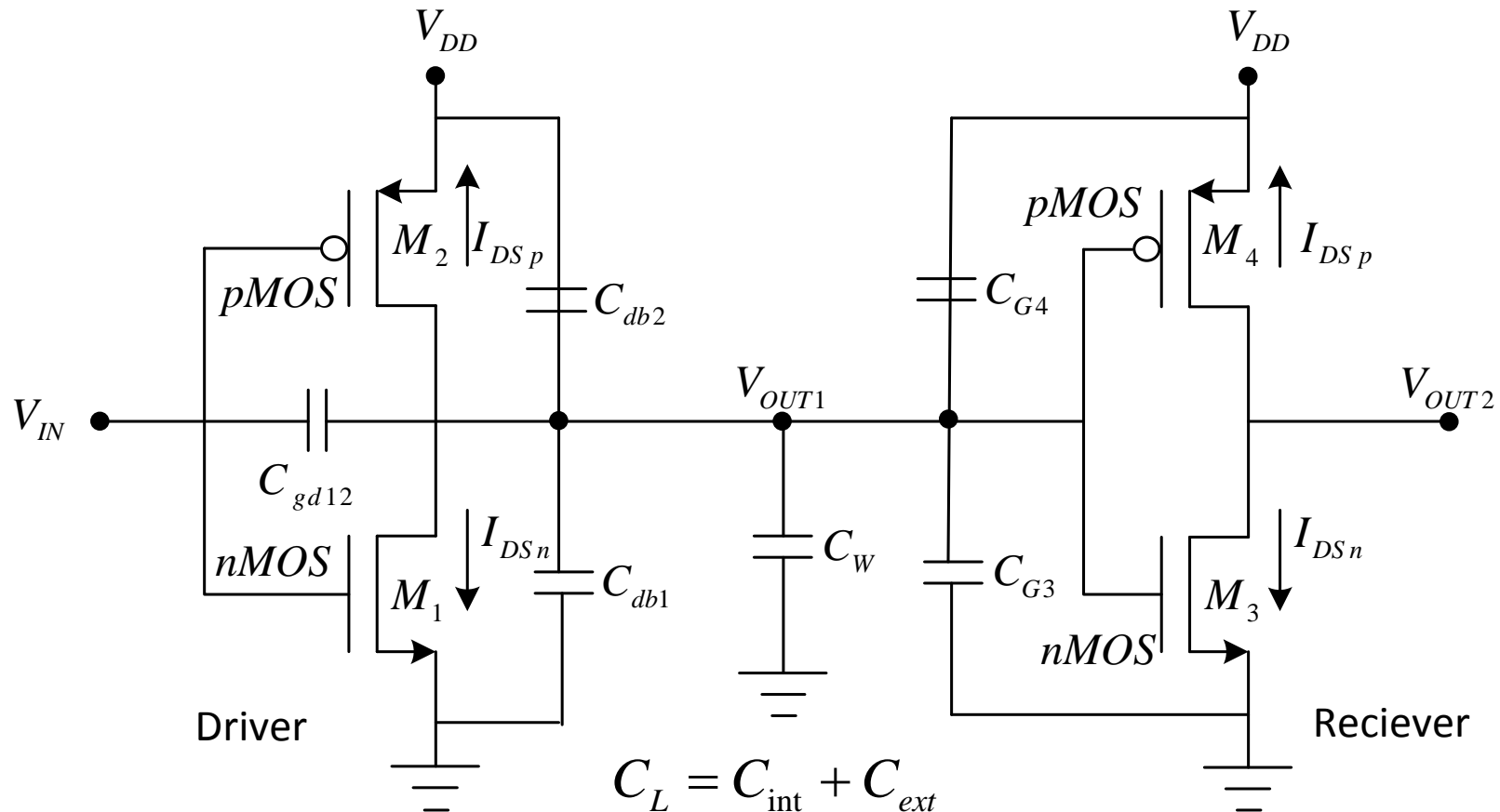- Effect of Capacitance (lumped capacitor model)



C_{int} = internal capacitance of driver


$C_{db,12}$ = junction capacitance

$C_{gd,12}$ = gate capacitance (including Miller capacitance) $C_{\text{int}} = C_{db,12} + C_{gd,12}$





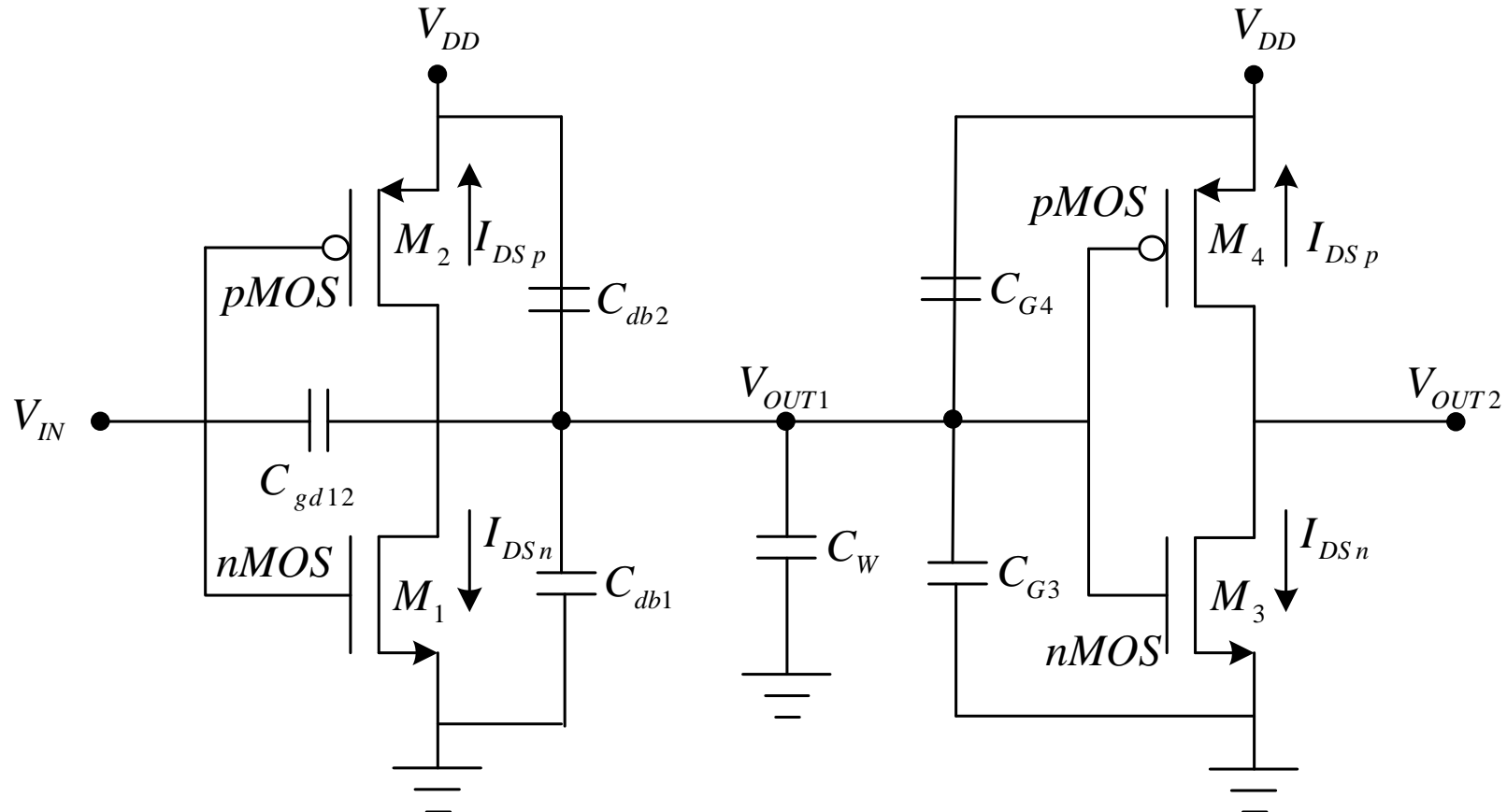- Effect of Capacitance (lumped capacitor model)



C_{ext} = external capacitance

$C_{g,43}$ = receiver gate capacitance


C_W = interconnect capacitance(wire)

$C_{ext} = C_W + C_{g,43}$





- Inverter Chain

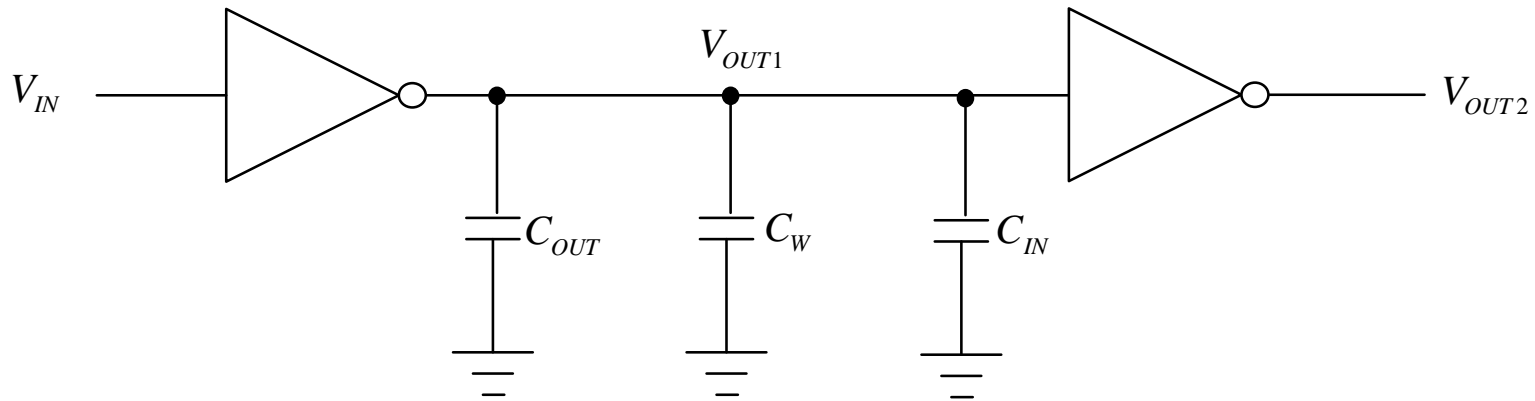


$$C_L = C_{OUT} + C_W + C_{IN}$$

$$C_{OUT} = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2}$$

$$C_{IN} = C_{g3} + C_{g4}$$



- Inverter Chain

 



- The dynamic of performance of a logic circuit is characterized by the propagation delay of its basic inverter.
- The inverter propagation delay τ_p is defined as the average of the low-to-high and the high-to-low propagation delay.

$$\tau_p = \frac{\tau_{pLH} + \tau_{pHL}}{2}$$

- The propagation delay τ_{pLH} and τ_{pHL} are defined as the time required for output voltage to reach between the low and high levels (%50 of V_{DD} in CMOS logic).
- The intrinsic propagation delay of the CMOS inverter that is loaded only by its own output capacitance C_{OUT}

$$\tau_{p0} = \frac{\tau_{pLH0} + \tau_{pHL0}}{2}$$



- The pMOS and nMOS transistors can be replaced by equivalent resistance R_{eqp} and R_{eqn} when charging and discharging the capacitor C_{OUT} in simplified analysis.
- The pMOS acts as a resistor R_{eqp} when C_{OUT} is charged to and output switches from low-to-high. The intrinsic V_{DD} propagation delay is

$$\tau_{pLH0} = 0.69R_{eqp}C_{OUT}$$

- The nMOS acts as a resistor R_{eqn} when C_{OUT} is discharged when output switches from high-to-low. The intrinsic propagation delay is

$$\tau_{pHL0} = 0.69R_{eqn}C_{OUT}$$

$$\tau_{p0} = \frac{0.69R_{eqp}C_{OUT} + 0.69R_{eqn}C_{OUT}}{2}$$



$$\tau_{p0} = \frac{0.69R_{eqp}C_{OUT} + 0.69R_{eqn}C_{OUT}}{2}$$



$$\tau_{p0} = \frac{0.69(R_{eqp} + R_{eqn})C_{OUT}}{2} = \frac{0.69(R_{eq})C_{OUT}}{2}$$

$$R_{eq} = R_{eqp} + R_{eqn}$$

$$C_L = C_{int} + C_{ext}$$

$$C_{int} = C_{OUT} + C_W$$

$$C_{ext} = C_{IN}$$

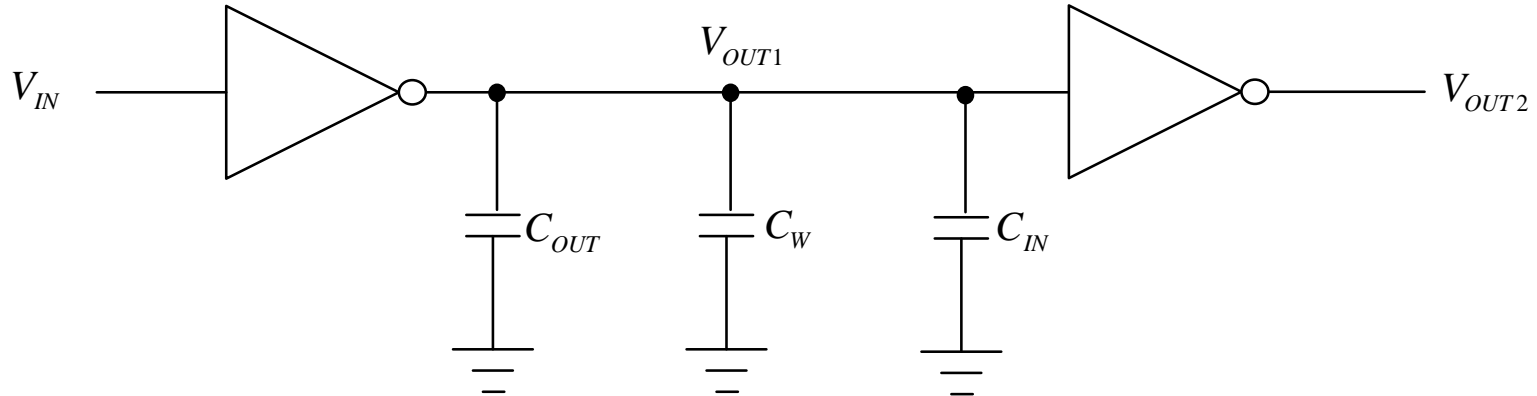 

$$C_L = C_{\text{int}} + C_{\text{ext}}$$

$$C_{\text{int}} = C_{OUT} + C_W$$

$$C_{\text{ext}} = C_{IN}$$

$$C_L = C_{\text{int}} (1 + \alpha)$$



- Intrinsic delay of CMOS inverter

$$\tau_p = 0.69 R_{eq} C_L$$

$$C_L = C_{int} + C_{ext}$$

$$\tau_p = 0.69 R_{eq} (C_{int} + C_{ext})$$

$$\tau_p = 0.69 R_{eq} C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

$$\tau_p = t_{po} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

$$\tau_{po} = \text{the intrinsic delay}$$



- Impact of sizing on gate delay
- S = sizing factor
- R_{ref} = The resistance of reference inverter (Usually a minimum size inverter)
- Reference gate = minimum size gate
- C_{iref} = The internal capacitance of the reference gate

$$C_{int} = SC_{iref}$$

$$R_{eq} = \frac{R_{ef}}{S}$$

$$t_p = 0.69 \left(\frac{R_{ef}}{S} \right) (C_{iref}) \left(1 + \frac{C_{ext}}{SC_{iref}} \right)$$

$$t_p = 0.69 (R_{ref}) (C_{iref}) \left(1 + \frac{C_{ext}}{SC_{iref}} \right)$$

$$t_p = t_{po} \left(1 + \frac{C_{ext}}{SC_{iref}} \right)$$




- Impact of sizing on gate delay

$$t_p = t_{po} \left(1 + \frac{C_{ext}}{SC_{iref}} \right)$$

- 1) Intrinsic delay is independent of gate sizing and determined only by technology and inverter layout
- 2) If S is made very large, gate delay approaches the intrinsic value but increases the area significantly.



- Inverter Chain

 

- Given C_L
- 1) How many stages of inverter are needed to minimize the delay?
- 2) How to size the inverter?



- Inverter delay
- Minimum length devices, $L = 0.25\mu m$
- Assumption : for example $W_p = 2W_N = 2W$
 - a) Same pull up and pull down currents
 - b) $R_N = R_P$: approximately equal resistance
 - c) $t_{pHL} = t_{pLH}$: equal rise and fall delay
- Analyze as an RC network
- Delay (D)

$$t_{pHL} = \ln 2 R_N C_N$$

$$t_{pLH} = \ln 2 R_p C_p$$



- Load for the next stage

$$C_{g,in} = 3 \frac{W}{W_{unit}} C_{unit}$$





- Voltage supply scaling

  

$$W_{unit} = 1$$


$$t_p = kR_W C_L$$

$$K = 0.69 = \text{constant}$$

- Assumption:
no load \rightarrow zero delay



- Inverter with load

 

$$C_N = C_{unit}$$

$$delay(t_p) = kR_W (C_{int} + C_{ext}) = kR_W C_{int} + kR_W C_{ext}$$

$$= kR_W C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right) = t_{po} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

$$t_{po} = kR_W C_W$$



- Delay formula: inverter chain

$$C_{\text{int}} = \gamma C_{\text{gin}}$$

$$\gamma \approx 1$$

$$f = \frac{C_{\text{ext}}}{C_{\text{gin}}} = \text{effective fanout}$$

$$t_{po} = 0.69 R_{eq} C_{\text{int}}$$

$$\text{delay} \approx R_{eq} (C_{\text{int}} + C_{\text{ext}})$$

$$t_p = 0.69 R_{eq} C_{\text{int}} \left(1 + \frac{C_{\text{ext}}}{C_{\text{int}}} \right) = t_{po} \left(1 + \frac{f}{\gamma} \right)$$



- Apply to inverter Chain

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{p,j} = t_{po} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$t_{p,j} = \sum_{j=1}^N t_{p,j} = t_{po} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$C_{gin,N+1} = C_L$$



- Optimal tapering for given N
- Delay equation has N-1 unknowns, $C_{g,2}, \dots, C_{g,N}$
- Minimize the delay, find N-1 partial derivatives
- Results:

$$\frac{C_{g,j+1}}{C_{g,j}} = \frac{C_{g,j}}{C_{g,j-1}} \quad \text{for } j = 2, \dots, N$$

- Size of each stage is the geometric mean of two neighbours

$$C_{g,j} = \sqrt{C_{g,j-1} \cdot C_{g,j+1}}$$

- Each stage has the same effective fanout $= f_j = f = \frac{C_{ext}}{C_{g,j}}$
- each stage has the same delay

$$t_p = t_{po} \left(1 + \frac{f}{\gamma} \right)$$



- Optimum delay and number of stages f

$$\frac{C_L}{C_{g,N}} = \frac{C_{g,N}}{C_{g,N-1}} = \dots\dots\dots = \frac{C_{g,2}}{C_{g,1}} = f$$

$$f^N = \frac{C_L}{C_{g,1}} = F$$

$$f = \sqrt[N]{F}$$

$$t_p = Nt_{po} \left(1 + \frac{\sqrt[N]{F}}{\gamma} \right)$$



- If N is too large, intrinsic delay of stages dominate, while if N is small, effective fanout of each stage(f) is large and the second term dominates.
- Example: How to choose N?
- $\frac{C_L}{C_1}$ has to be evenly distributed across N=3 stages

$$\frac{C_L}{C_{\text{int}}} = \frac{8C_1}{C_1} = 8$$

$$f = \sqrt[3]{8} = 2$$



- For a given load C_L and given input capacitance C_{in} find optimal sizing f .

$$C_L = FC_{in} = f^N C_{in}$$

$$N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{po} \left(\frac{\sqrt[N]{F}}{\gamma + 1} \right) = \frac{t_{po} \ln F}{\gamma} \left(\frac{f}{\ln f} + \frac{\gamma}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{po} \ln F}{\gamma} \bullet \frac{\ln f - 1 - \frac{\gamma}{f}}{\ln^2 f} = 0$$



- If self loading is ignored
- For $\gamma = 0, f = e, N = \ln F$

$$f = e^{1 + \frac{\gamma}{f}}$$

- Optimum f for given process defined by γ optimum tapering factor

$$f_{opt} = 3.6$$

$$\text{for } \gamma = 1$$



- Impact of self loading on t_p
- No self loading for $\gamma = 0$
- Optimal # of stages
- $N = \ln F$
- $t_p(\text{normalized}) = \frac{t_p}{t_{po}}$
- With self loading $\gamma^{po} = 1$
- If $f < f_{opt}$ (too many stages) will result in delay to increase
- Normalized delay function of F

$$t_p = N t_{po} \left(1 + \frac{\sqrt[N]{F}}{\gamma} \right)$$

$$\frac{t_p(\text{opt})}{t_{po}} \text{ for } \gamma = 1$$



- Buffer design
- | N | f | t_p |
|---|-----|-------|
| 1 | 64 | 65 |
| 2 | 8 | 18 |
| 3 | 4 | 15 |
| 4 | 2.8 | 15. |