
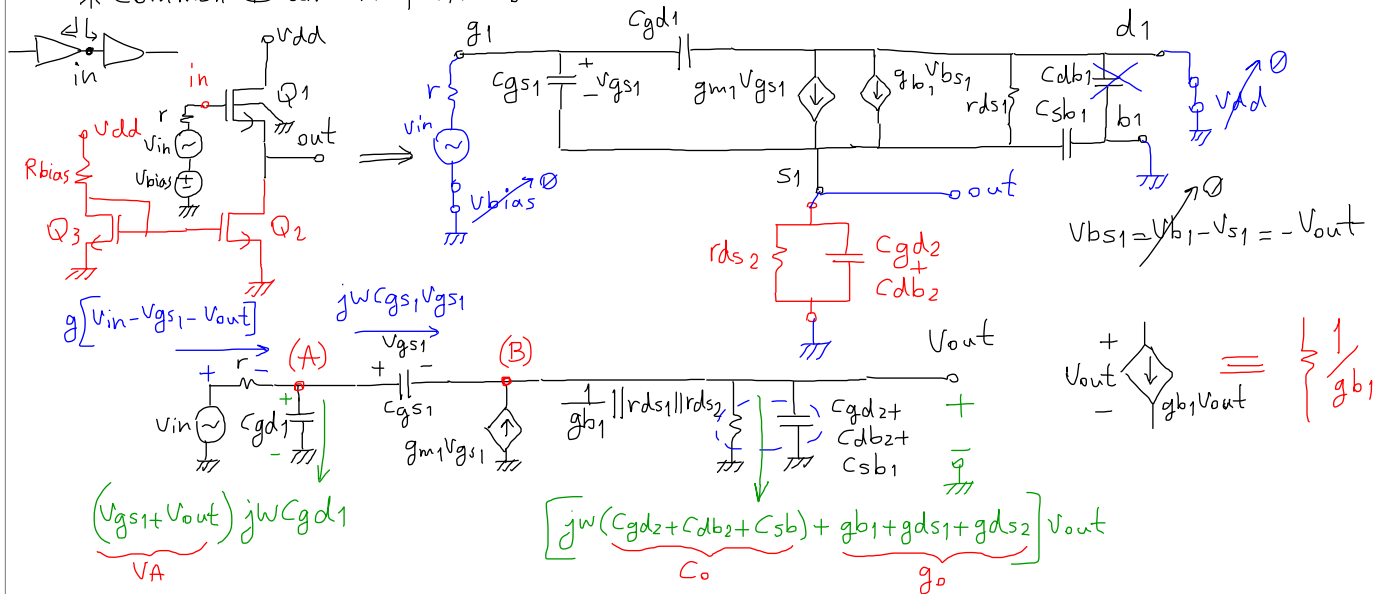
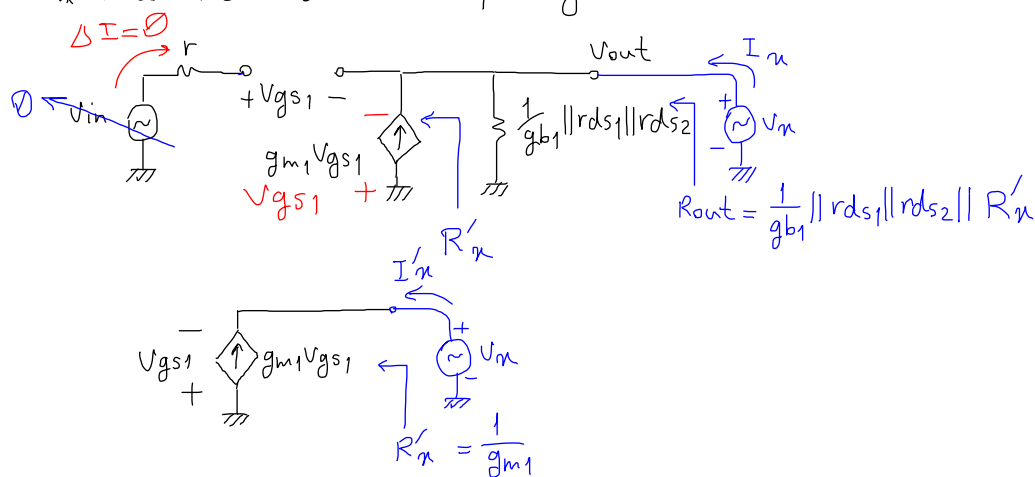
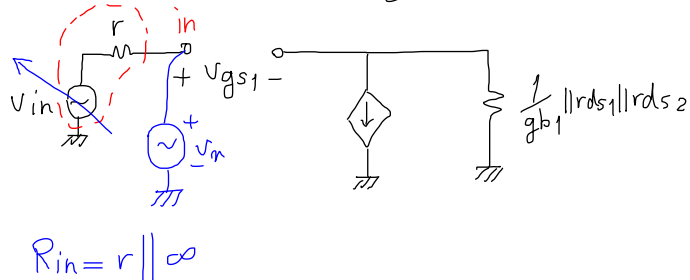


* Common Drain Amplifier :

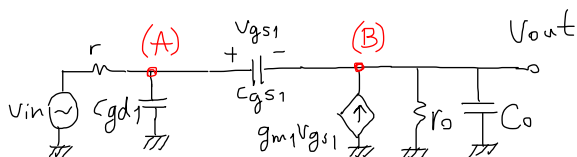* find R_{out} @ Low-frequency :* find R_{in} @ low frequency





$$r_o = \frac{1}{g_{d1}} \parallel r_{ds1} \parallel r_{ds2}$$

$$C_o = C_{gd2} + C_{db2} + C_{sb1}$$


* find total resistance seen at node (A) ?

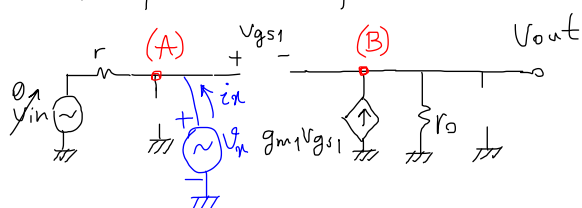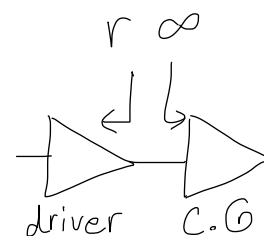- connect test source to node A
- short independent v_{in} source
- open all capacitors



$$R(A) = \frac{v_n}{i_n} = r \parallel \infty$$

* find total resistance at node (B) ?

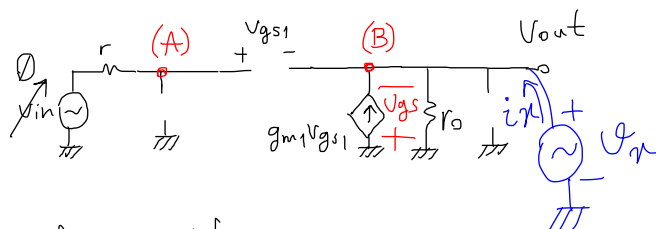


$$v_B = v_n = -v_{gs}$$


$$\text{Answer: } R(B) = r_o \parallel \frac{1}{g_m}$$

$$\text{or } R(B) = \frac{1}{g_o + g_m}$$

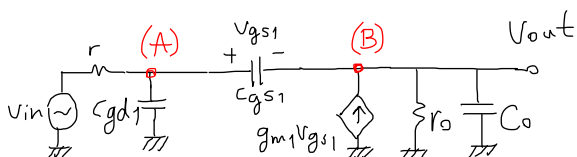* find total resistance between nodes (A) and (B) ?




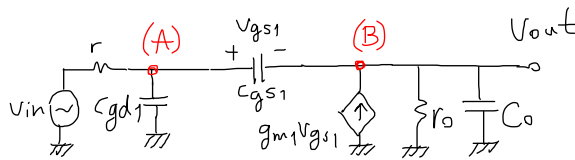* find total resistance between nodes (A) and (B) ?



Answer:
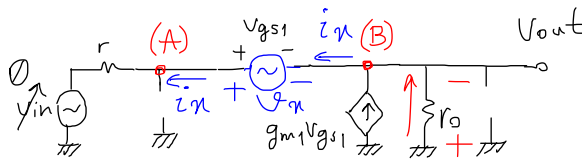
$$R_{AB} = \frac{V_x}{i_x} = \frac{r + r_o}{1 + g_{m1}r_o}$$



$$V_x = V_{gs1} = \underbrace{r \cdot i_x}_{V^+} - \underbrace{\left(-r_o [i_x - g_{m1}V_{gs1}] \right)}_{V^-}$$

$$\Rightarrow R_{AB} = \frac{V_x}{i_x} = \frac{r + r_o}{1 + g_{m1}r_o}$$

$$\omega_{3dB} = \frac{1}{rC_{gd1} + \frac{r+r_o}{1+g_{m1}r_o}C_{gs1} + \left(\frac{1}{g_{m1}} \parallel r_o \right) C_o}$$

$$r_o = \frac{1}{g_{b1}} \parallel r_{ds2} \parallel r_{ds1}$$

$$C_o = C_{sb1} + C_L + C_{gd2} + C_{db2}$$

$$\frac{(g+g_i)g_{m1} + g_o'(g+g_i)}{(g+g_i)C_{gs1} + g_{m1}C_{gd1} + g_o'(C_{gd1} + C_{gs1}) + (g+g_i)C_o}$$

$$\frac{r+r_o}{1+g_{m1}r_o} \times \frac{\frac{1}{r} \cdot \frac{1}{r_o}}{\frac{1}{r} \cdot \frac{1}{r_o}} = \frac{g_o + g}{g \cdot g_o + g_{m1}g}$$