
EE223 Analog Integrated Circuits


Fall 2018

Lecture 8: CS with Source Degeneration

Source Follower


Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

CS Amp with Diode-Connected Load

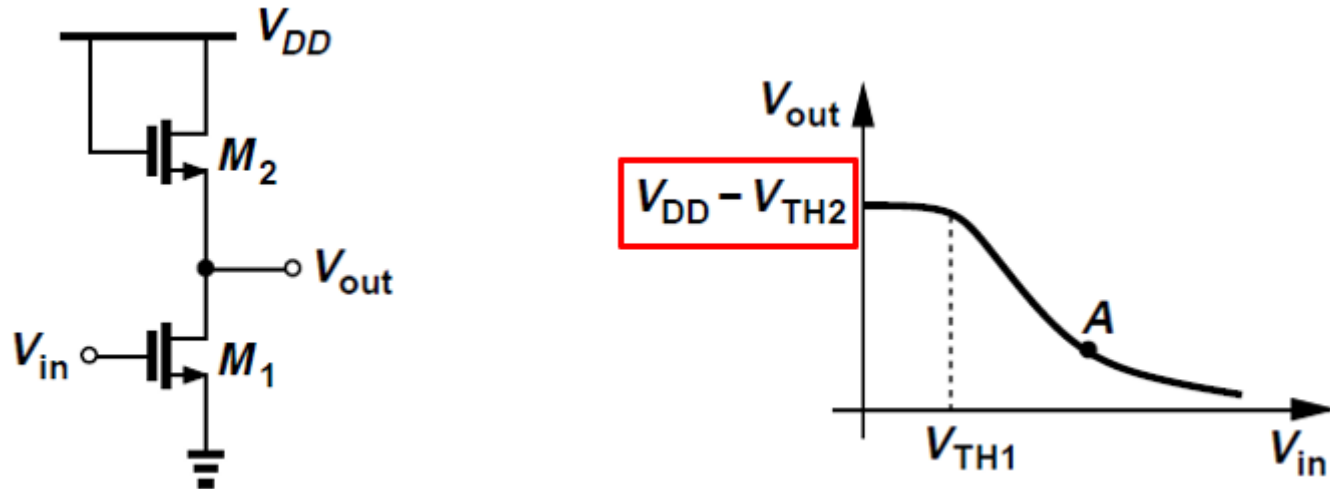

- For $V_{in} < V_{TH1}$, $V_{out} = V_{DD} - V_{TH2}$
- When $V_{in} > V_{TH1}$, previous large-signal analysis predicts that V_{out} approximately follows a single line
- As V_{in} exceeds $V_{out} + V_{TH1}$ (to the right of point A), M_1 enters the triode region and the characteristic becomes nonlinear.

CS Amp with Diode-Connected PMOS

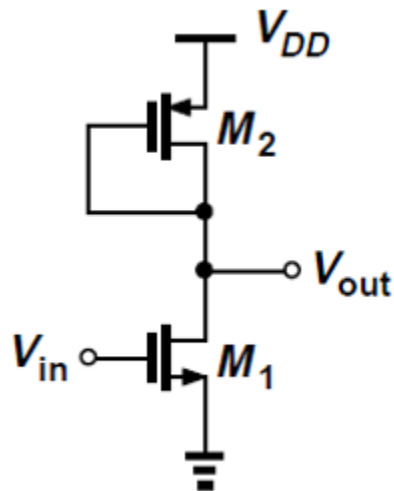

- Diode-connected load can be implemented as a PMOS device, free of body-effect
- Small-signal voltage gain neglecting channel-length modulation


$$A_v = -\sqrt{\frac{\mu_n(W/L)_1}{\mu_p(W/L)_2}}$$

- Gain is a relatively weak function of device dimensions
- Since $\mu_n \approx 2\mu_p$, high gain requires “strong” input device **wide** and “weak” load device **narrow**
- This limits voltage swings since for $\lambda = 0$, we get

$$\frac{|V_{GS2} - V_{TH2}|}{V_{GS1} - V_{TH1}} = A_v$$

- For diode-connected loads, swing is constrained by both required overdrive voltage and threshold voltage, i.e., for small overdrive, **output cannot exceed $V_{DD} - |V_{TH}|$.**


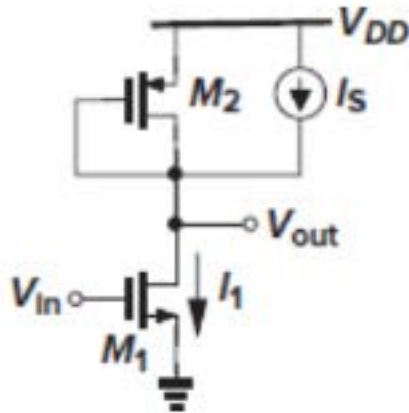
CS Amp with Diode-Connected PMOS and Current Source



**What is the gain of the Amp
if $(W/L)_1 = 2(W/L)_2$ and $I_s = 0.75 I_1$?
Assume $\mu_n = 2 \mu_p$**

$$A_v = \frac{v_{out}}{v_{in}} = - \frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_1}}{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_2 I_2}} = - \frac{\sqrt{2 \cdot 2\mu_p \cdot 2 \left(\frac{W}{L}\right)_2 I_1}}{\sqrt{2\mu_p \left(\frac{W}{L}\right)_2 0.25 I_1}} = -4$$

CS Stage with Source Degeneration

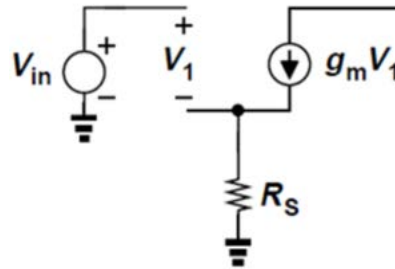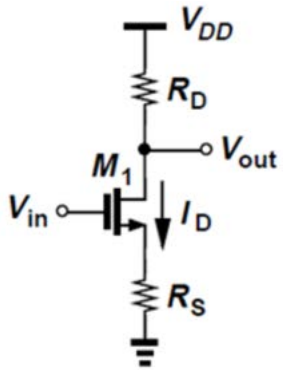


$$\begin{aligned} A_v &= -G_m R_D \\ &= \frac{-g_m R_D}{1 + g_m R_S} \end{aligned}$$

Complete the small-signal model and derive the gain expression.

Circuit Impedance - 1


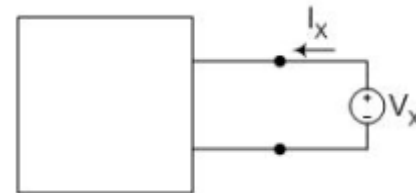
- It is often useful to determine the impedance of a circuit seen from a specific pair of terminals
- The following is the recipe to do so:
 1. Connect a voltage source, V_x , to the port
 2. Suppress all independent sources
 3. Measure or calculate I_x
 4. $R = V_x / I_x$ from Ohm's law




In general, $g_m > g_{mb} > g_o$

Circuit Impedance - 2

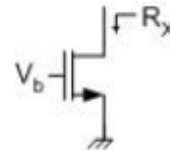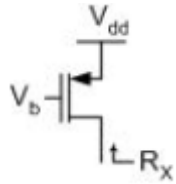- Find the small-signal impedance of the following circuits



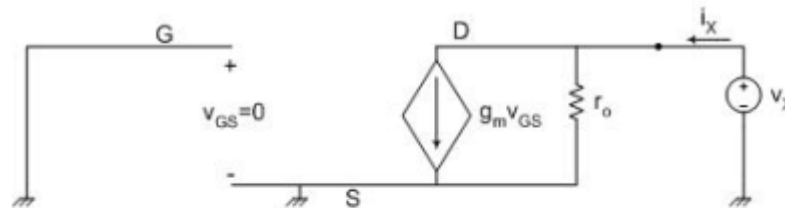- We draw the small-signal model, which is the same for both circuits, and connect a voltage source as shown below:





$$i_x = \frac{v_x}{r_o} + g_m \cdot v_{GS} = \frac{v_x}{r_o}$$


$$R_x = \frac{v_x}{i_x} = r_o$$

Circuit Impedance - 3

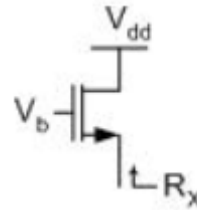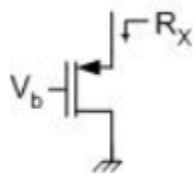- Find the small-signal impedance of the following circuits



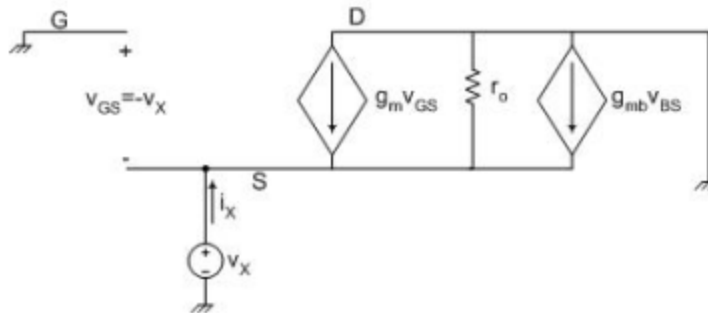- We draw the small-signal model, which is the same for both circuits, and connect a voltage source as shown below:





$$i_X = \frac{v_X}{r_o} - g_m \cdot v_{GS} - g_{mb} \cdot v_{BS} = \frac{v_X}{r_o} + g_m \cdot v_X + g_{mb} \cdot v_X$$

$$R_X = \frac{v_X}{i_X} = \frac{1}{\frac{1}{r_o} + g_m + g_{mb}} = r_o \left\| \frac{1}{g_m} \right\| \frac{1}{g_{mb}} \approx 1/g_m \quad \Leftarrow \quad \text{In general, } g_m > g_{mb} > g_o$$

Circuit Impedance - 4

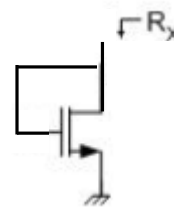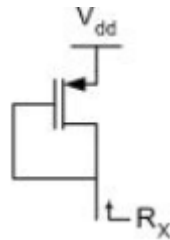
- Find the small-signal impedance of the following circuits



- We draw the small-signal model and connect a voltage source as shown below:

$$i_x = \frac{v_x}{r_o} + g_m \cdot v_{GS} = \frac{v_x}{r_o} + g_m \cdot v_x = v_x \cdot \left(\frac{1}{r_o} + g_m \right)$$
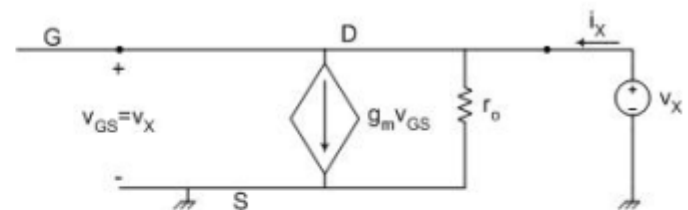
$$R_x = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_o} + g_m} = r_o \parallel \frac{1}{g_m}$$



If channel length modulation is ignored ($r_o = \infty$) we get:

$$R_x = r_o \parallel \frac{1}{g_m} = \infty \parallel \frac{1}{g_m} = \frac{1}{g_m}$$


⇐ In general, $g_m > g_{mb} > g_o$

Circuit Impedance Summary

- Looking into the Drain

- $g = g_o = g_{ds}$
- $C = C_{gd} + C_{db}$
- “High” Impedance node


$$r = r_o = r_{ds}$$

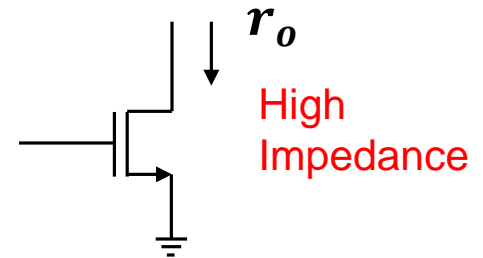

- Looking into the Source

- $g = g_m + g_{mb} + g_{ds} \sim g_m$
- $C = C_{gs} + C_{sb}$
- “Low” Impedance node

$$r = 1/g_m$$

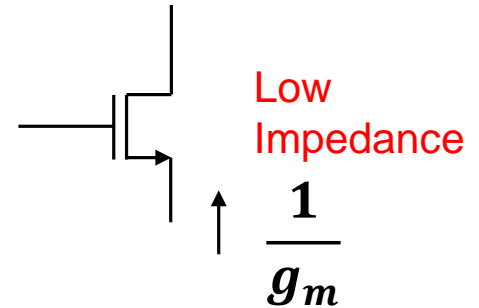

- Looking into the Source with Well diode


- $g = g_m + g_{ds} \sim g_m$
- $C = C_{gs} + C_{well}$

$$r = 1/g_m$$



- Looking into the Diode (Drain & Gate are connected)

- $g = g_m + g_o \sim g_m$
- $C = C_{gs} + C_{db}$
- “Low” Impedance node

$$r = 1/g_m$$

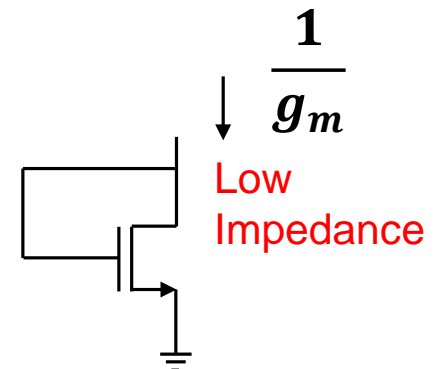


CS Stage with Source Degeneration

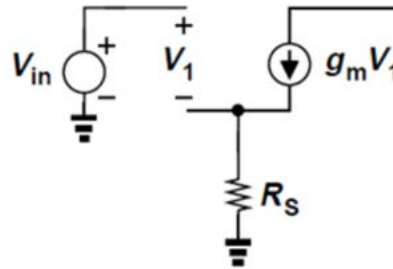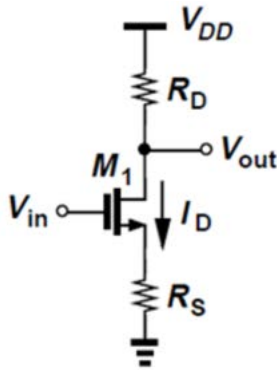

Complete the small-signal model and derive the gain expression.

CS Stage with Source Degeneration

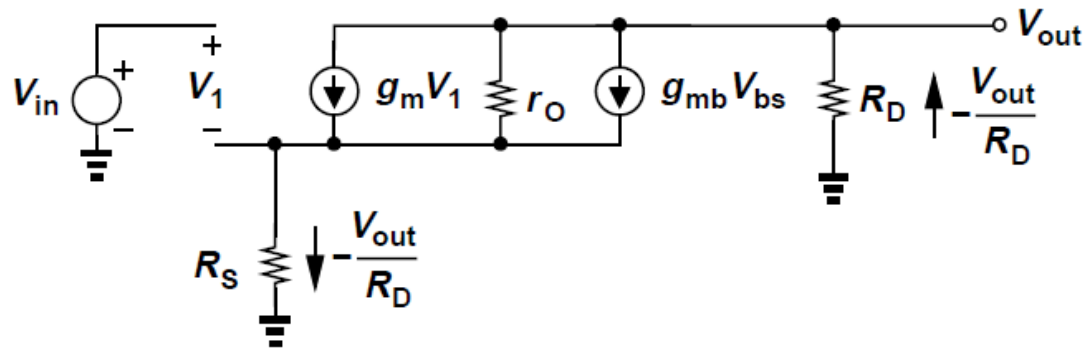

- To compute gain in the general case including body effect and channel-length modulation, consider above small-signal model


- From KVL at input,

$$V_1 = V_{in} + V_{out} R_S / R_D$$

- KCL at output gives

$$\begin{aligned} I_{rO} &= -\frac{V_{out}}{R_D} - (g_m V_1 + g_{mb} V_{bs}) \\ &= -\frac{V_{out}}{R_D} - \left[g_m \left(V_{in} + V_{out} \frac{R_S}{R_D} \right) + g_{mb} V_{out} \frac{R_S}{R_D} \right] \end{aligned}$$

CS Stage with Source Degeneration

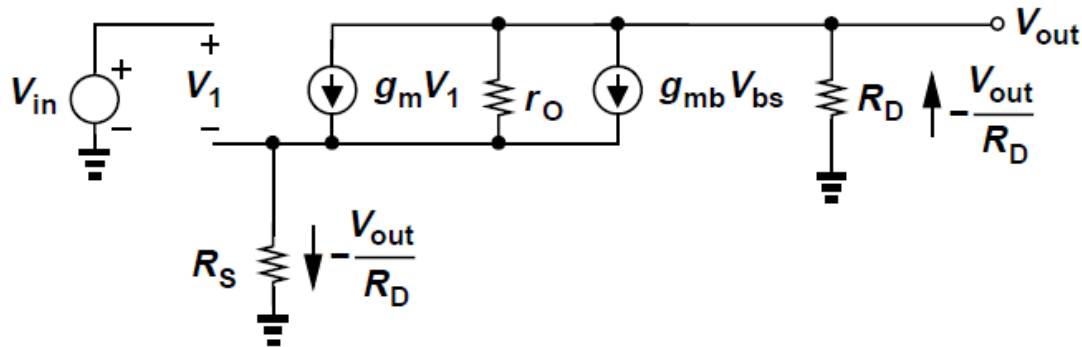

- Since voltage drops across r_O and R_S must add up to V_{out} ,

$$\begin{aligned}
 V_{out} &= I_{r_O} r_O - \frac{V_{out}}{R_D} R_S \\
 &= -\frac{V_{out}}{R_D} r_O - \left[g_m \left(V_{in} + V_{out} \frac{R_S}{R_D} \right) + g_{mb} V_{out} \frac{R_S}{R_D} \right] r_O - V_{out} \frac{R_S}{R_D}
 \end{aligned}$$

- Voltage gain is therefore

$$\frac{V_{out}}{V_{in}} = \frac{-g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb}) R_S r_O} \approx \frac{-g_m R_D}{1 + (g_m + g_{mb}) R_S} \approx \frac{-g_m R_D}{1 + g_m R_S}$$



CS Stage with Source Degeneration

- Small-signal gain can be written as



$$A_v = -\frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

- Magnitude of gain
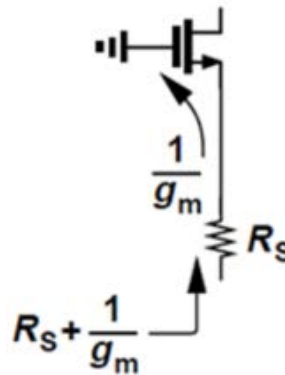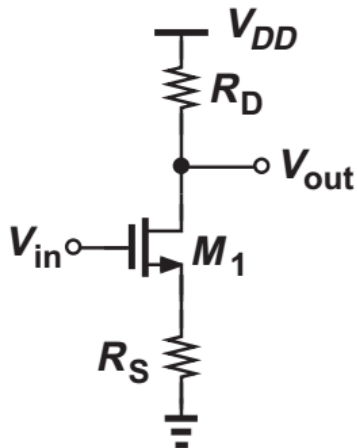
$$\frac{\text{Resistance seen at the drain}}{\text{Total resistance seen in the source path}}$$



Output Impedance of CS Amp with R_S

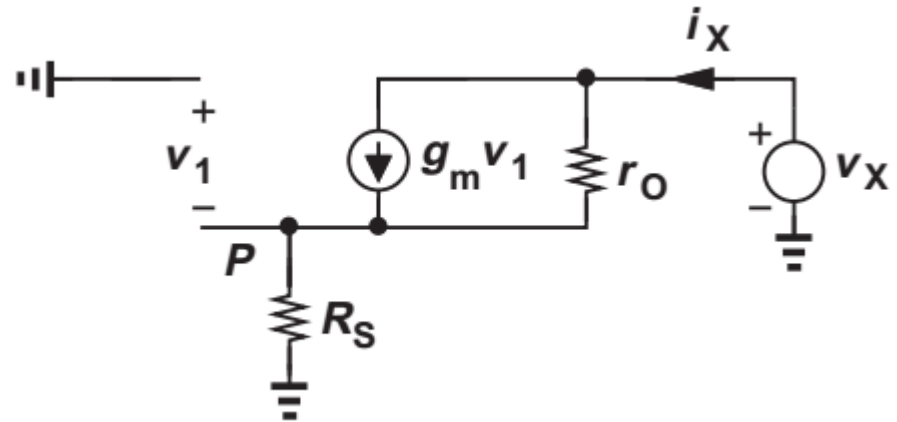
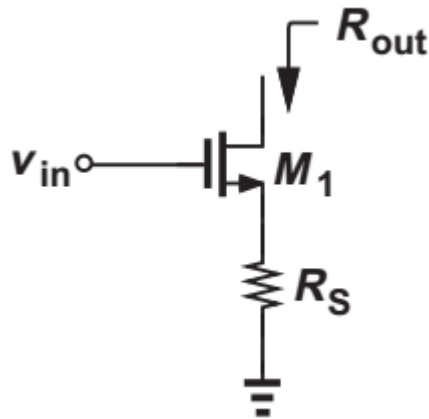


$$v_1 = -i_X R_S$$

$$\begin{aligned} v_X &= (i_X - g_m v_1) r_o - v_1 \\ &= (i_X + g_m i_X R_S) r_o + i_X R_S \\ &= i_X [(1 + g_m R_S) r_o + R_S] \end{aligned}$$



$$\begin{aligned} R_{out} &= \frac{v_X}{i_X} = (1 + g_m R_S) r_o + R_S \\ &= r_o + R_S + (g_m r_o) \cdot R_S \\ &\approx (g_m r_o) \cdot R_S \end{aligned}$$

Source Follower

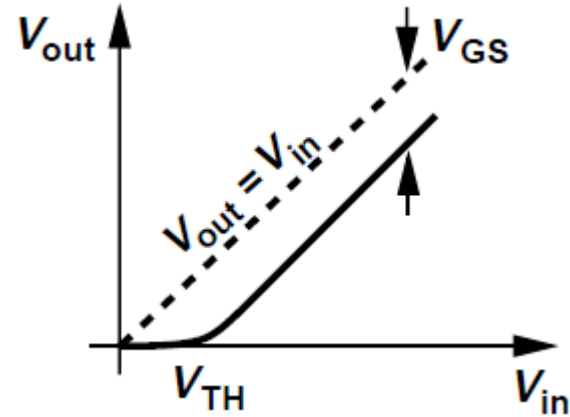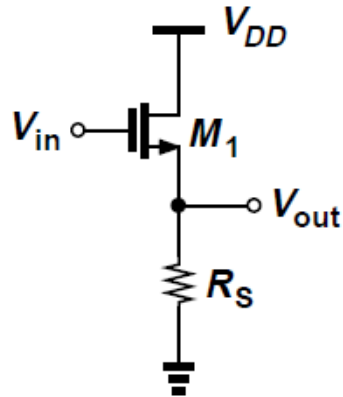


- For $V_{in} < V_{TH}$, M_1 is off and $V_{out} = 0$
- As V_{in} increases, V_{out} follows the input with a difference (level shift) equal to V_{GS}

Source Follower Gain

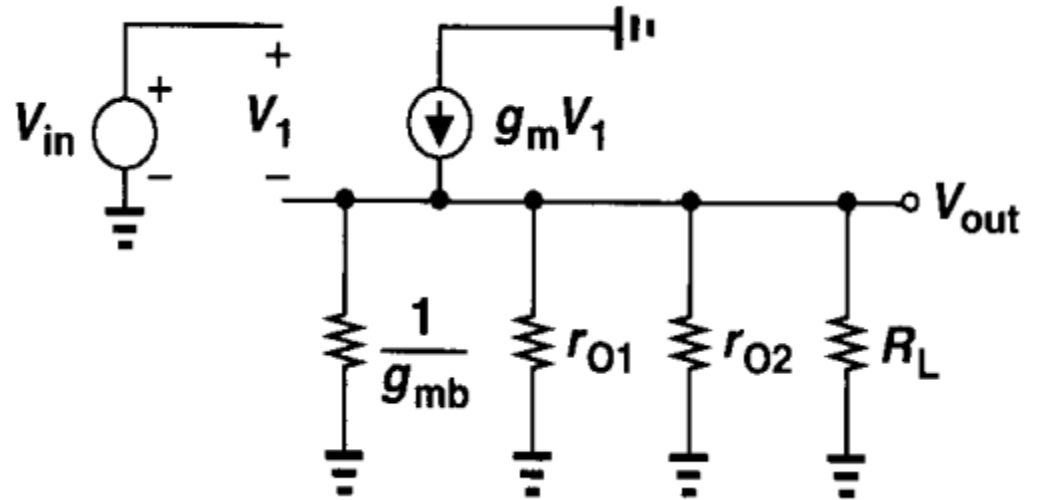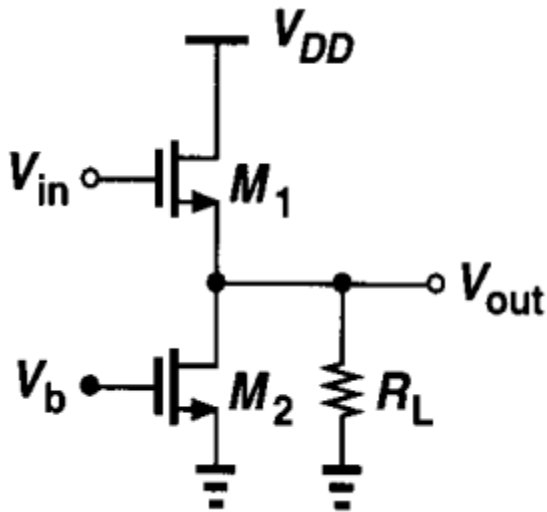

$$A_v = g_m R_{out} = g_m (R_{\uparrow} // R_{\downarrow}) = \frac{g_m}{g_{\uparrow} + g_{\downarrow}}$$

Source Follower Output Impedance



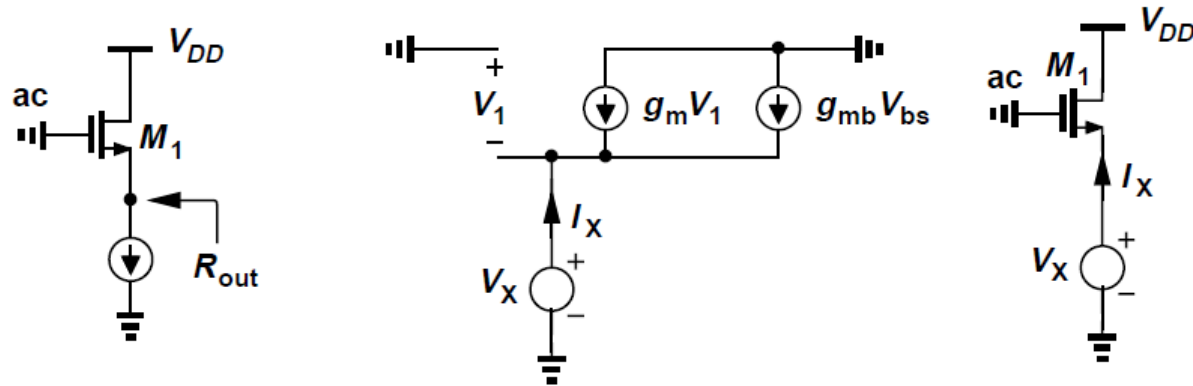


$$V_X = -V_{bs}$$

$$I_X - g_m V_X - g_{mb} V_X = 0$$

$$R_{out} = \frac{1}{g_m + g_{mb}}$$

Issue with Source Follower

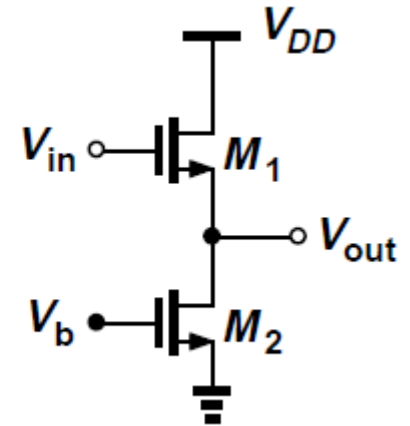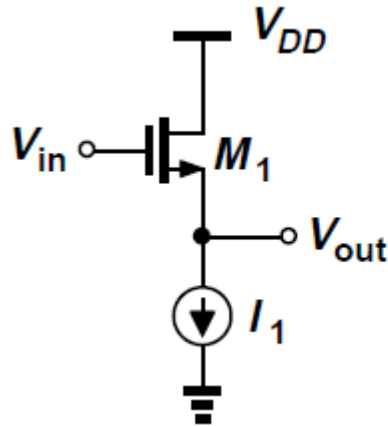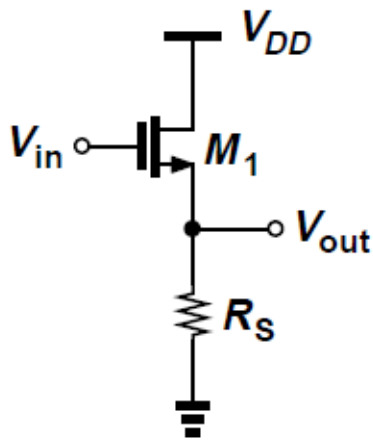

- Voltage headroom limitation
- Nonlinear dependence of V_{TH} on the source potential
- r_O changes substantially with V_{DS}

Issue with Source Follower

- Nonlinearity can be eliminated if the bulk is tied to the source
- PMOS source follower employing two separate n-wells can eliminate the body effect of M_1

