

# Circuit Design

*Tutorials and Insights in Electronics and Circuit Design*

[About](#)
[Google Search](#)
[Feedback \(Contact Us\)](#)
[Privacy](#)


## The case for the trans-conducting LNA

By POOJAN WAGH | Published: NOVEMBER 1, 2008

In this post, I will show an evolution of a trans-conducting LNA (rather than a voltage-gain LNA). This is a prime example of current-mode circuit design, which has benefits in terms of linearity—especially for low-voltage scaling in RFCMOS design.
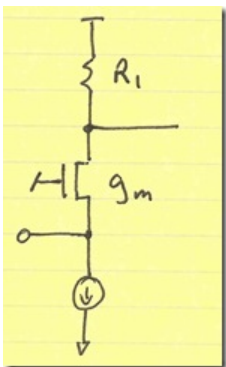
### Conventional common-gate LNA

Consider the conventional common-gate LNA on its own: \_\_\_\_\_



This LNA consists of an input at the source of the MOS transistor (or emitter of a BJT), a current-source to bias the transistor, and a resistor load. This configuration is typically used in broadband receivers (cable tuners, TV tuners, software-defined radio).

The gain of this stage is  $A_v = g_m \times R_1$ . This seems like a reasonable stage to produce a gain and therefore overcome noise.

Each of these circuits is presented as a single-ended version. However, there is absolutely no reason not to implement them as differential circuits. I merely draw them single-ended here to get the point across without obfuscating the primary ideas. If there is interest in seeing what the differential versions look like, please post a request in the comments section.

### CMOS LNM employing voltage-mode LNA

However, consider what happens when we couple this LNA into a CMOS switch-mode mixer:

#### Blogroll


- [Circuit Sage](#)
- [Poojan Blog](#)
- [Security Now](#)

#### Site Categories

- [Analog Professional](#)
- [Tutorials](#)

#### RSS Links

- [All posts](#)
- [All comments](#)

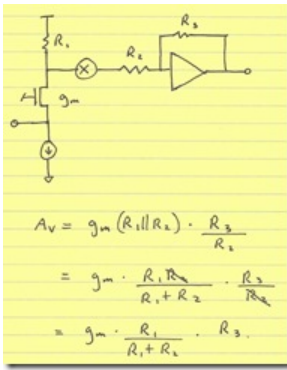


The  $\otimes$  symbol represents a set of commutating MOS mixers, typically capacitively coupled, to separate the dc bias voltages at the output of the LNA and the input of the post-mixer amplifier (PMA). You can essentially ignore them in this analysis, and just assume that they ideally convert from RF to baseband (direct conversion).

Consider the loss term  $R_1/(R_1 + R_2)$ . It doesn't have to be there.
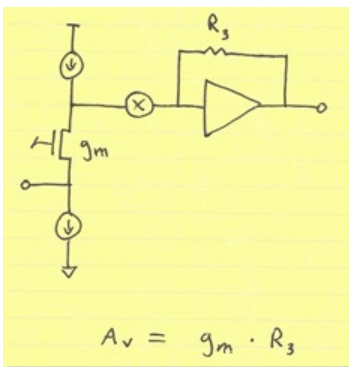
## Trans-conducting LNA

If we replace  $R_1$  with a current-source load and merely omit  $R_2$ , we'd have something like this:



You'll note that the previous loss term is now gone. We have greatly enhanced the gain at essentially no cost. Furthermore, the resulting architecture is even more linear: there is little swing at the output of the LNA; the summing junction of the PMA linearizes the LNA by presenting a low impedance to the LNA.

Due to the high output impedance of the LNA, a common-mode feedback circuit is necessary. I have detailed [two ways](#) of doing that.

## References

[Matt Miller](#) and I came up with these ideas at Motorola in 2004. We were not the only ones. Other people within Motorola came up with the same idea. In addition, I had seen it published somewhere around 2004—I thought by Michiel Steyaert or Thomas Lee. Despite my recollection, the closest references I have seen available are: [“A 72mW CMOS 802.11a direct conversion receiver with 3.5dB NF and 200kHz 1/f noise corner”](#) (albeit using an inductor load instead of PMOS loads) and [“A 1 V 1.1 GHz CMOS integrated receiver front-end”](#) (with a folded Gilbert cell mixer).

This entry was posted in *Analog Professional*. Bookmark the [permalink](#). Post a comment or leave a [trackback](#): [Trackback URL](#).

### 3 Comments



**ashvini vishvakarma**

Posted June 14, 2009 at 11:55 pm | [Permalink](#)

hi poojan,  
i love your analog design insight posts.

‘current mode design’ is a bit of a black art for me. and there is only ONE book in entire Amazon on it !

Can you pl write an article on rough rules of thumb to use for (1) when to use current mode and (2) how 2 go about designing in current mode.

can you pl also write a post on why the OTA [operational trans-conductance amplifier] failed to ‘take over the world’ ? what caused its demise ? and is it still used in some neiche ? what is that neiche ?

I know about the 4-20 ma current loop of Induatrial, and the teleco current loop for POTS onhook-offhook detection.

ashvini, new delhi , india.

[Log in to reply.](#)



**[Poojan Wagh](#)**

Posted December 28, 2008 at 10:22 pm | [Permalink](#)

@Robert Tso:

You’re right about the impedance going high outside of the gain-bandwidth of the op-amp. Typically, you’ll want to put a capacitor on the inputs of the PMA to maintain a low impedance when the PMA’s op-amp (OTA) runs out of steam (and to suck out any LO injection). The addition of such a capacitor is not trivial as it can really screw up stability.

I also recall that there’s a filter configuration (was it Tow-Thomas?) that includes such a capacitor.

I will admit ignorance on many of the details of the BBF, because there was either someone else to do that job (which, I will admit, is the crux of this configuration), or I was always pulled off to other tasks.

[Log in to reply.](#)



**Robert Tso**

Posted December 24, 2008 at 3:06 pm | [Permalink](#)

If the post mixer amplifier is a low bandwidth amplifier, then it will not do a very good job in presenting a low impedance at the mixer output or at the gm stage output, – so the benefits of improving gm stage linearity would not be realized  
The likely advantage of the 2nd schematic configuration is that it allows a filter to be placed between the mixer and baseband amp.

[Log in to reply.](#)

### One Trackback

- By [The benefits of differential circuits](#) on May 17, 2012 at 10:52 pm

### Post a Comment

You must be [logged in](#) to post a comment.

This site uses Akismet to reduce spam. [Learn how your comment data is processed.](#)

---

Powered by [WordPress](#). Built on the [Thematic Theme Framework](#).