
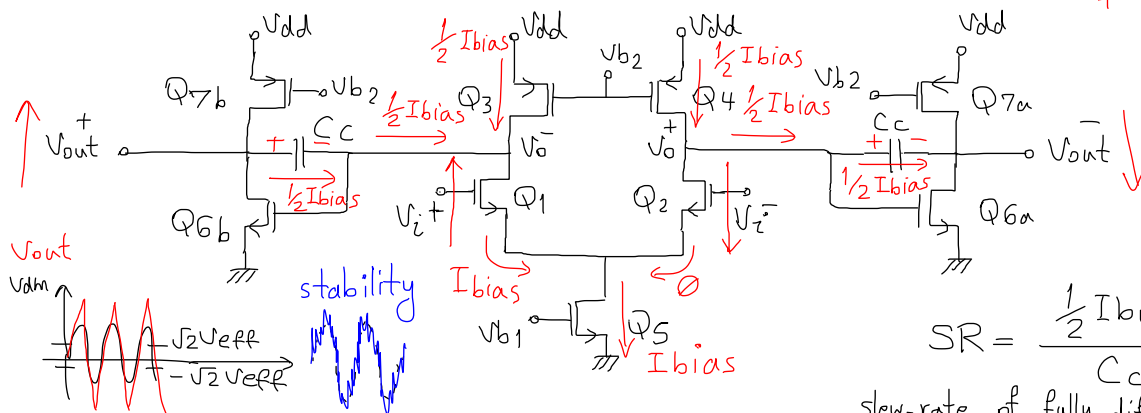



* Slew-rate

$$Q = CV = I \cdot t$$

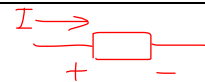

$$SR = \frac{\frac{1}{2} I_{bias}}{C_c} = \frac{\Delta V}{t}$$

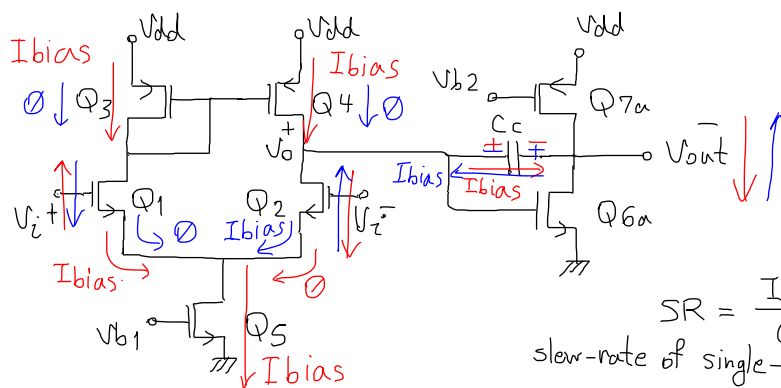slew-rate of fully differential amplifier




$$SR = \frac{I_{bias}}{C_c}$$

slew-rate of single-ended amplifier


* opamps with small Slew-rate
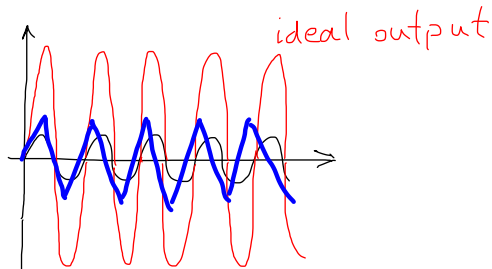
$$\frac{1V}{\mu s}, \quad SR = \frac{\Delta V}{t} = \frac{I}{C}$$






* opamps with large Slew-rate
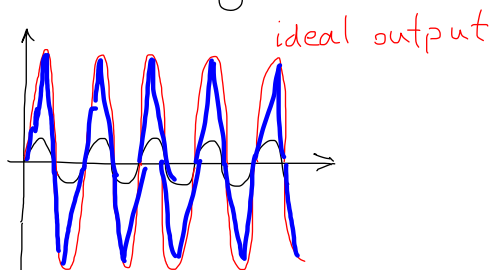
$$10 \frac{V}{\mu s}, \quad SR = \frac{\Delta V}{t} = \frac{I}{C}$$





* Settling time (t_s):

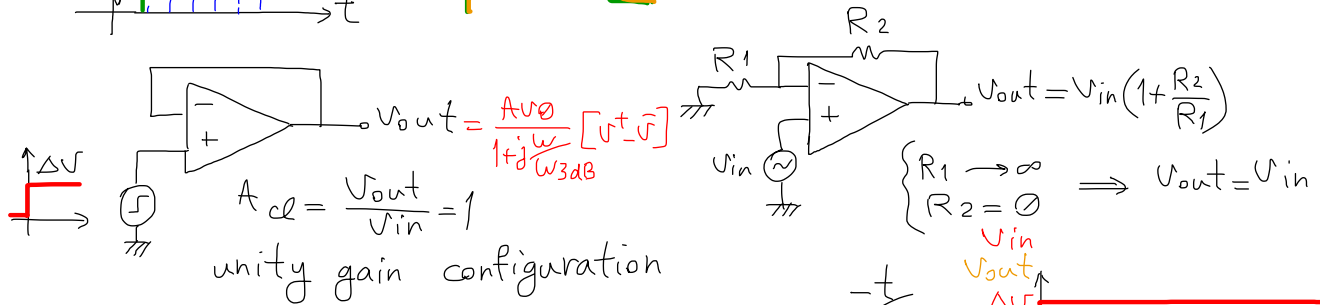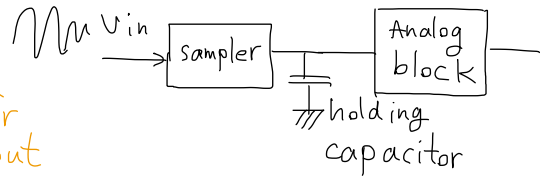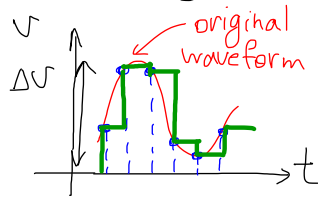

$$V_{out}(t) = V_{out}(\infty) - [V_{out}(\infty) - V_{out}(0)] e^{-\frac{t}{\tau}}$$

$$V_{out}(t) = \Delta V (1 - e^{-\frac{t}{\tau}}), \quad \tau = \frac{1}{\omega_{p1}}$$

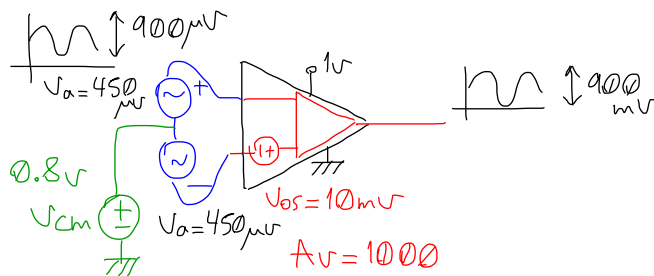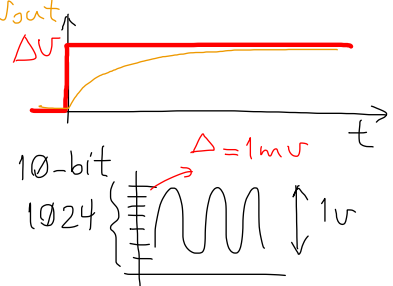if $\begin{cases} V_{out} = 90\% \Delta V \Rightarrow t_s = 2.3 \tau \Rightarrow 3-4 \text{ bit} \\ V_{out} = 99\% \Delta V \Rightarrow t_s = 4.6 \tau \Rightarrow 6-7 \text{ bit} \\ V_{out} = 99.9\% \Delta V \Rightarrow t_s = 7 \tau \Rightarrow 9-10 \text{ bit} \end{cases}$



after fabrication

