 


# Adder

## Lecture 18

Advanced Digital IC Design



Khosrow Ghadiri



- Addition:

$$\begin{array}{r} 111101 \text{ augend} \\ + 10111 \text{ addend} \\ \hline \end{array}$$

1111**1** carries

$$\begin{array}{r} 111**1**01 \text{ augend} \\ + 10**1**11 \text{ addend} \\ \hline \end{array}$$

1010**1**00 sum

111111 carries

$$\begin{array}{r} 111101 \text{ augend} \\ + 10111 \text{ addend} \\ \hline \end{array}$$




1010100 sum

- both the sum bit and carry bit are 1's

$$1+1+1 = (1+1)+1 = (10)_2 + (01)_2 = 11$$




   - Adders
- Adder or summer is a digital logic device used to carry binary addition of numbers.
- Typical uses involve calculating address in memory, table indices, incrementing or decrementing operators, etc.
- Two kinds of adder: Half Adder & Full Adder
- An n-th Bit Adder can be designed by cascading an arbitrary amount of Full Adders





- Quarter adder: Exclusive OR: No Carry

 

a	b	c
Low	Low	Low
Low	High	High
High	Low	High
High	High	Low

a	b	c
0+	0	0
0+	1	1
1+	0	1
1+	1	0

No Carry

$$\begin{aligned}
 f_{XOR}(a, b) &= a \oplus b = a\bar{b} + \bar{a}b = \bar{a}a + \bar{a}b + \bar{b}a + \bar{b}a \\
 &= \bar{a}(a + b) + \bar{b}(a + b) = (\bar{a} + \bar{b})(a + b)
 \end{aligned}$$



- Exclusive OR

$$a \oplus a = 0$$

$$a \oplus \bar{a} = 1$$

$$a \oplus 0 = a$$

$$a \oplus 1 = \bar{a}$$

$$\bar{a} \oplus \bar{b} = a \oplus b$$

$$a \oplus b = b \oplus a$$


$$a \oplus (b \oplus c) = (a \oplus b) \oplus c$$



- Exclusive OR IEEE Standard

a	b	sum(a,b)	sum(a,b)=1?	$f(a,b) = a \oplus b$
0	0	0	false	0
0	1	1	true	1
1	0	1	true	1
1	1	2	false	0

Output is modulo-2 sum of input

 


- Half-Adder


$$s_i = x_i \oplus y_i$$

$$c_i = x_i y_i$$



- Truth table

$x_i$	$y_i$	$c_i$	$s_i$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

 


- Half-Adder

  






- Full-Adder

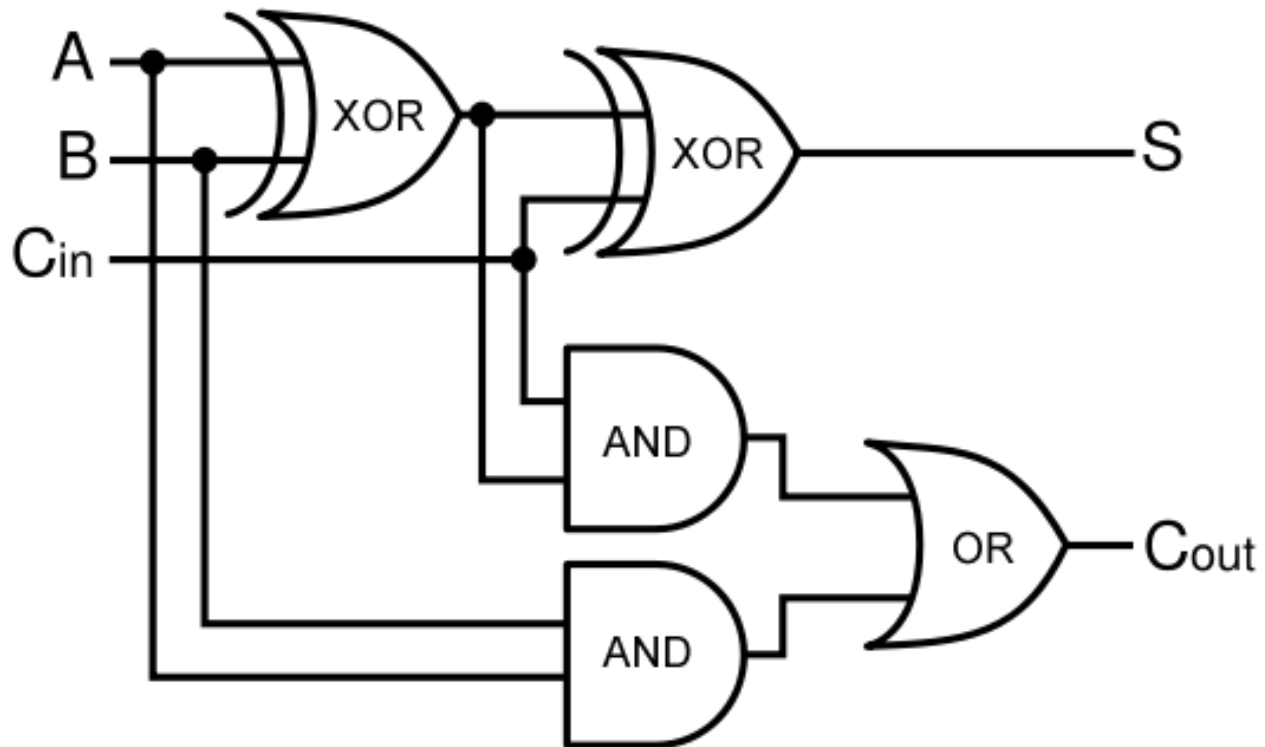




- One-bit Full-Adder
- Binary addition adding 2 bits + one carry bit
- Full adder 2-output combinational logic network that add 3 binary bits

$x_i$	$y_i$	$c_{i-1}$	$c_i$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$s_i = x_i \oplus y_i \oplus c_{i-1}$$
 
$$c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$$



- Full-Adder

 

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$

$$= \overline{x_i} \overline{y_i} \overline{c_{i-1}} + \overline{x_i} y_i c_{i-1} + x_i \overline{y_i} c_{i-1} + x_i y_i c_{i-1}$$

$$c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$$



- Steps to Designing the Full Adder
  - 1 Derive the Truth Table
  - 2 Devise the K-Map
  - 3 Obtain the Logic Expression
- Draw out the Logic Circuit
- Building Blocks
  - 1 NAND Gate
  - 2 NOR Gate
  - 3 NOT Gate



- Building Blocks
- 1** NAND Gate


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND Truth Table

A \ B	0	1
0	1	1
1	1	0



NAND Logic  
Expression:

$$Y = \overline{A} + \overline{B}$$

 



- Building Blocks
- **1** NAND Gate

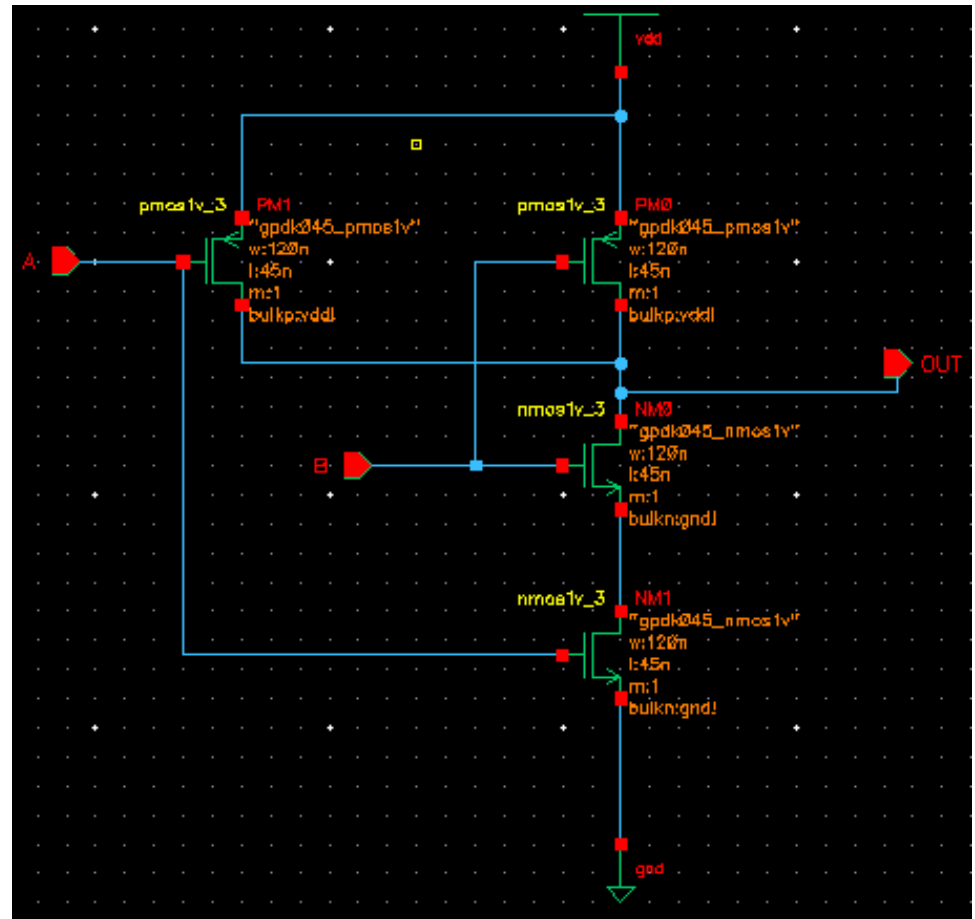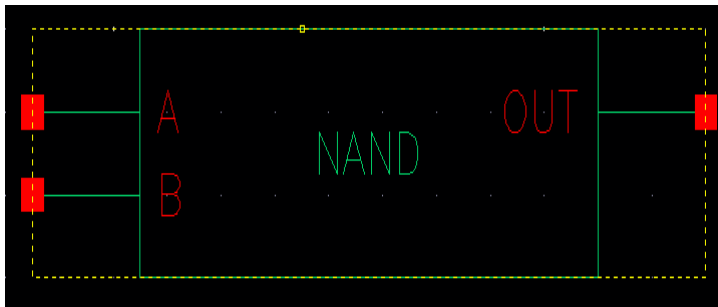




- Building Blocks
- **2** NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

NOR Truth Table

A \ B	0	1
	0	1
0	1	0
1	0	0

 
NOR Logic  
Expression:  $Y = \overline{A} \overline{B}$



NOR Logic Circuit



- Building Blocks
- **2** NOR Gate

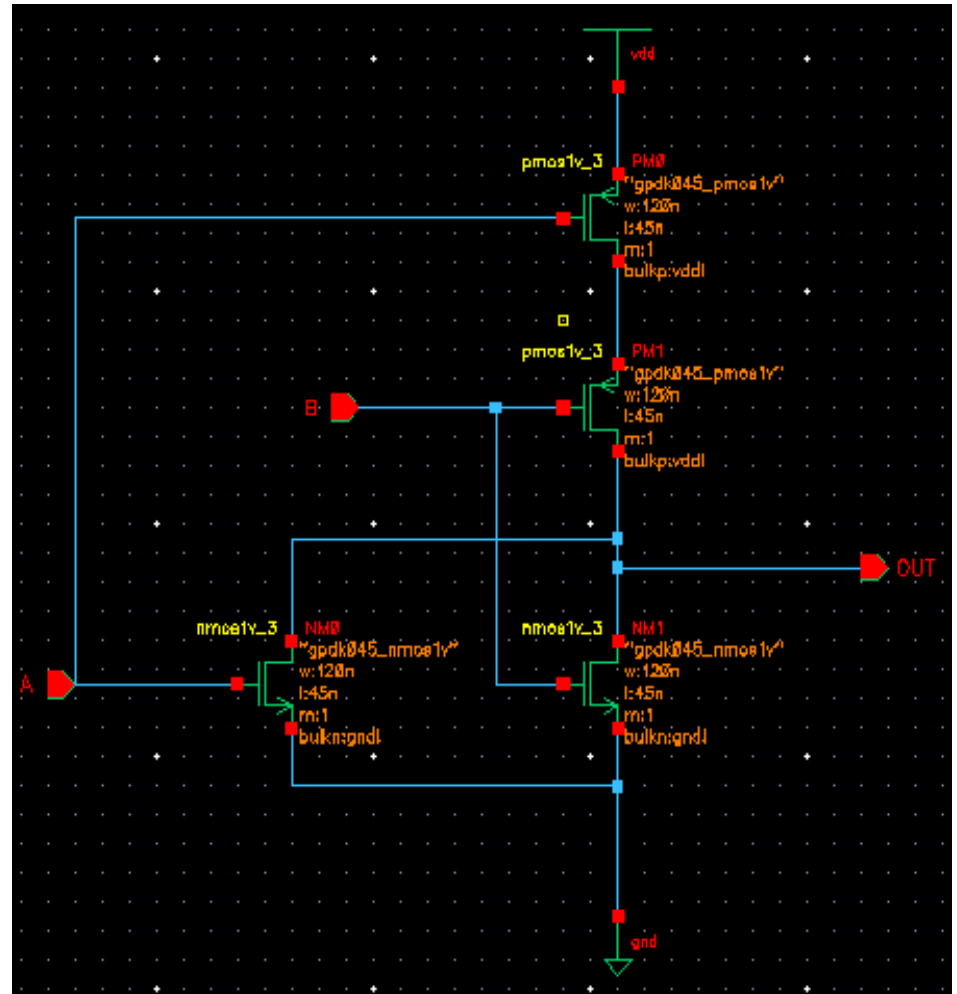






- Building Blocks
- **3** NOT Gate

A	Y
0	1
1	0

NOT Truth Table

K-MAP Not Needed For NOT Gate


NOT Logic  
Expression:

 

NOT Logic Circuit




- Building Blocks
- **3** NOT Gate

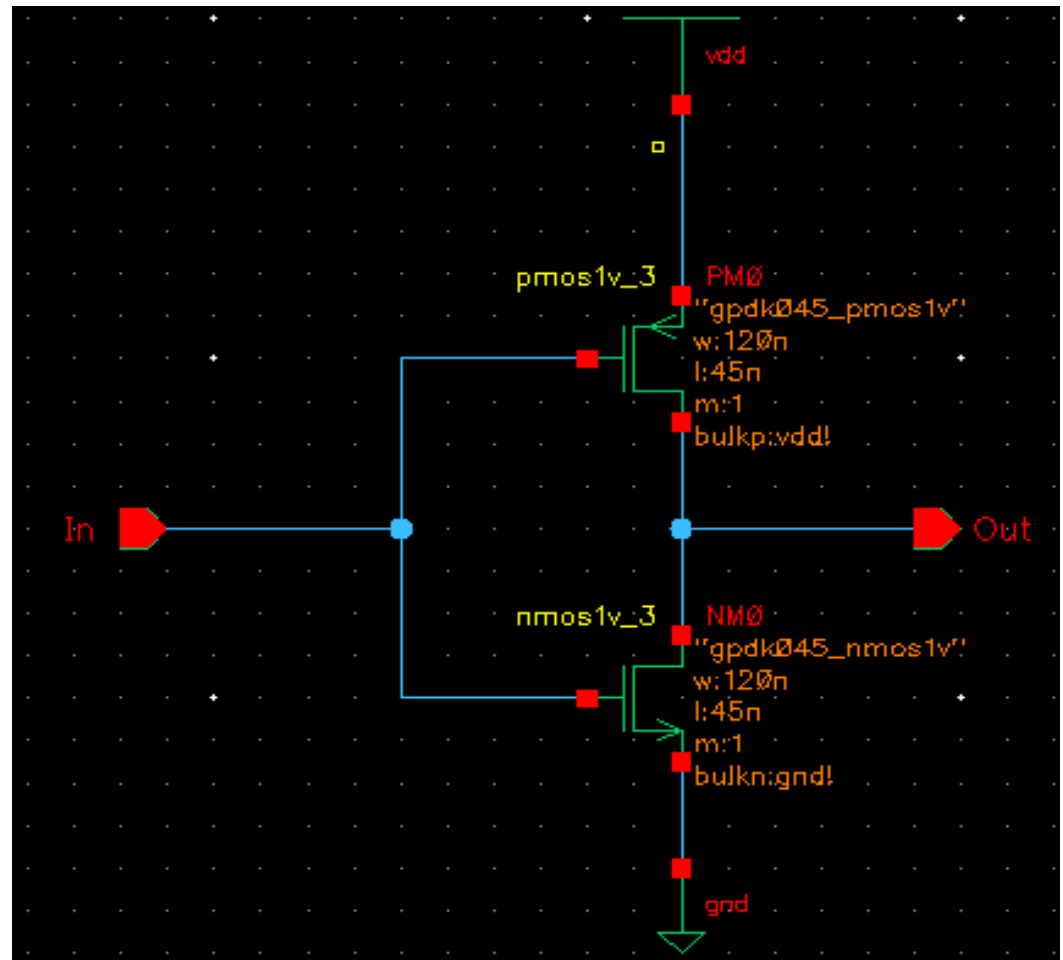



- Blocks
- **1** AND Gate

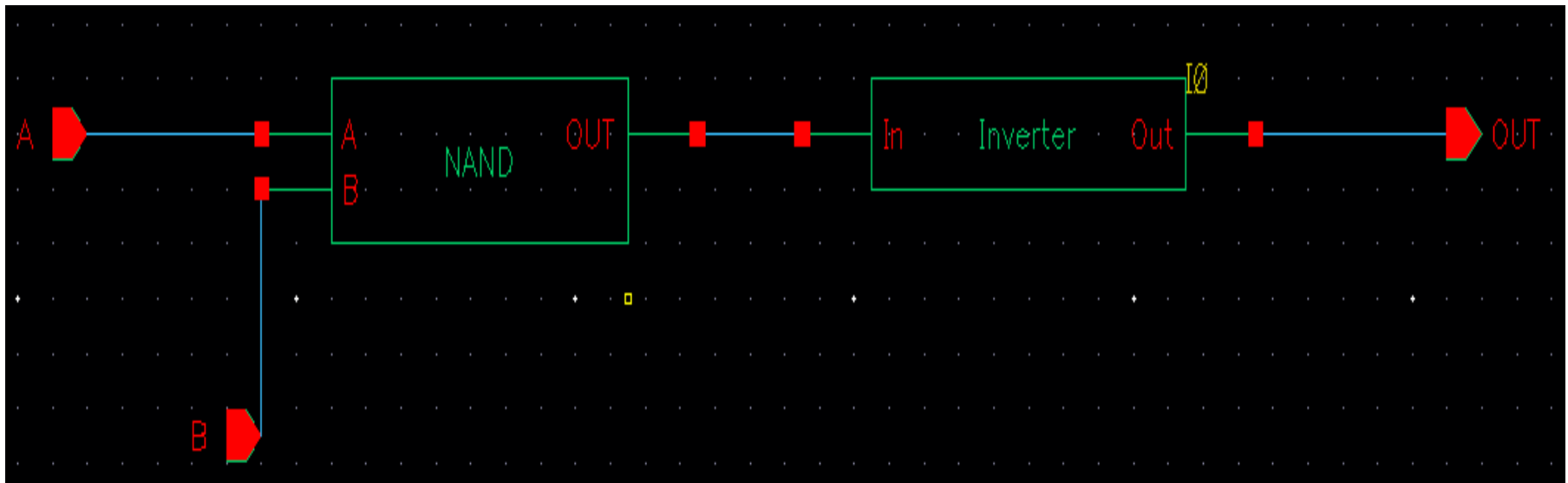



- Blocks
- **2** XOR Gate


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XOR Truth Table

A \ B	0	1
0	0	1
1	1	0

XOR K-Map


XOR

 Logic Expression:  $Y = A'B + AB'$  or  $Y = A \oplus B$ 

XOR Logic Circuit



- Building Blocks
- **1** XOR Gate

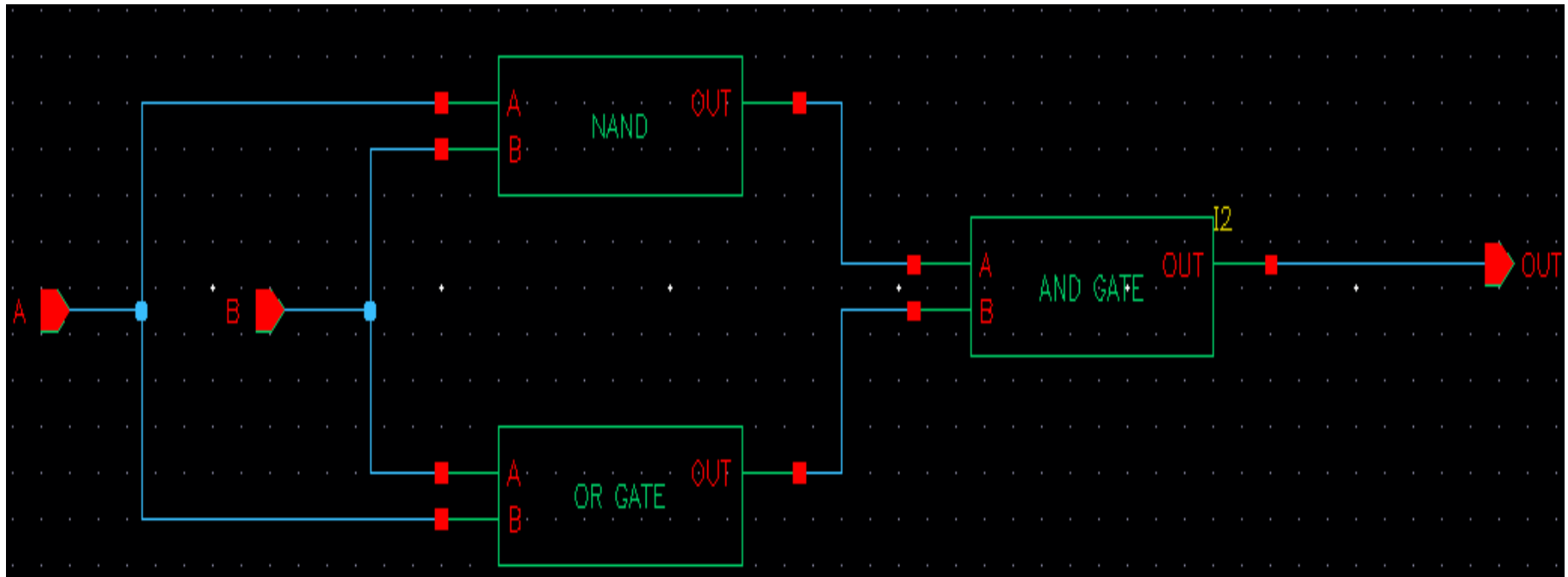



- Blocks
- **3** Full Adder

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder Truth Table

AB \ Cin	00	01	11	10
0		1		1
1	1		1	


Sum k-map

AB \ Cin	00	01	11	10
0			1	
1		1	1	1

Carry K-map

$$\begin{aligned} \text{Sum} &= A'B'Cin + A'BCin' + ABCin + AB'Cin \\ &= A \oplus B \oplus C \quad (1) \end{aligned}$$


 
$$\begin{aligned} \text{Cout: } Cout &= AB + ACin + BCin \\ &= ([A \oplus B]Cin) + (AB) \quad (2) \end{aligned}$$



Full Adder Logic Circuit




- Building Blocks
- **3** Full Adder

 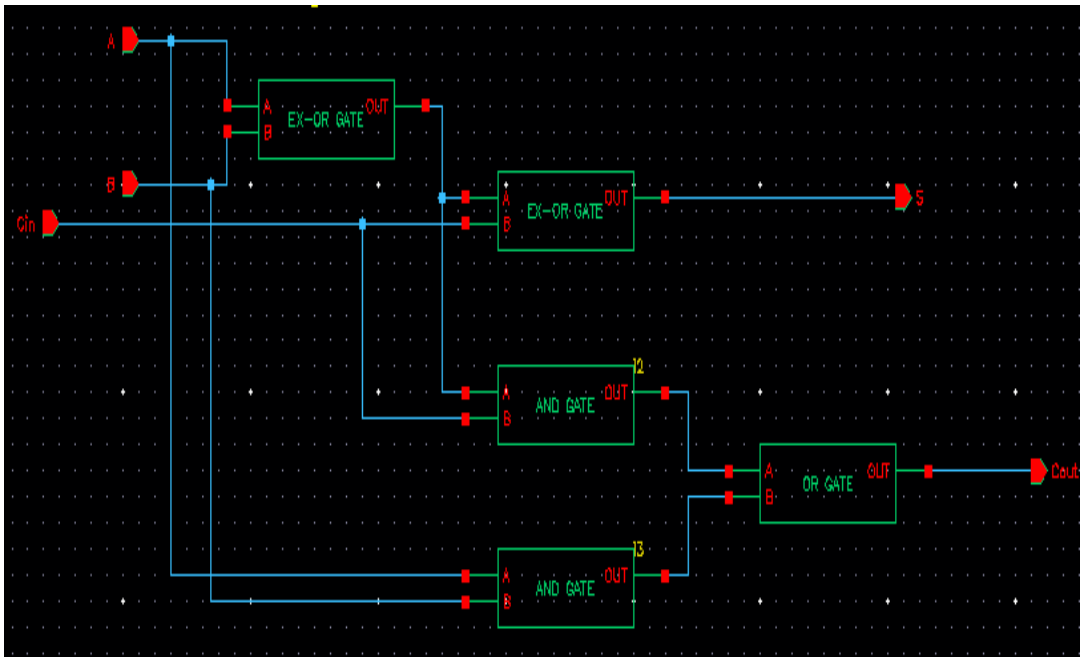




- Brute Force Implementation of Full Adder
- Inverter, OR, AND, XOR,

## Inverter Schematic

 

## OR Schematic

 








- Brute Force Implementation of Full Adder
- Inverter, OR, AND, XOR,

## AND Schematic

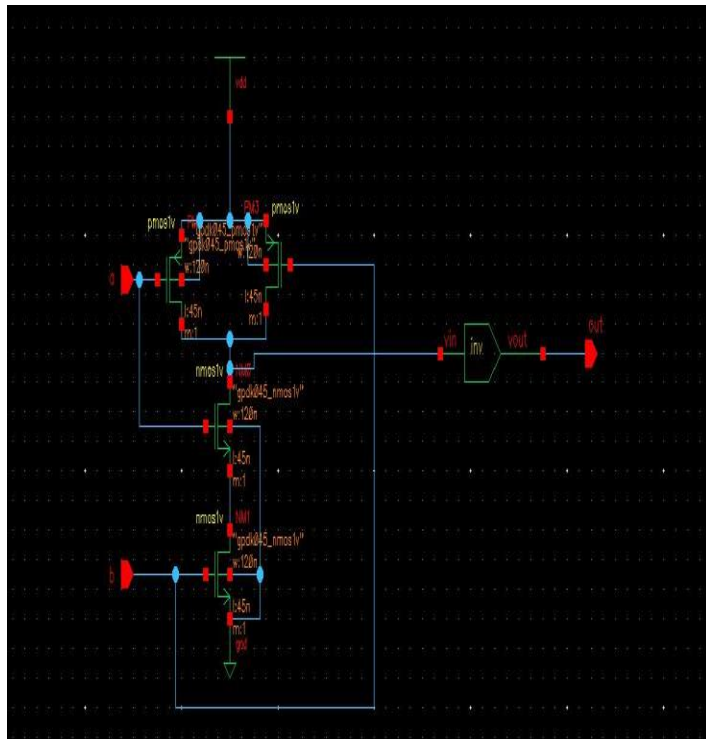


## XOR Schematic

 

 


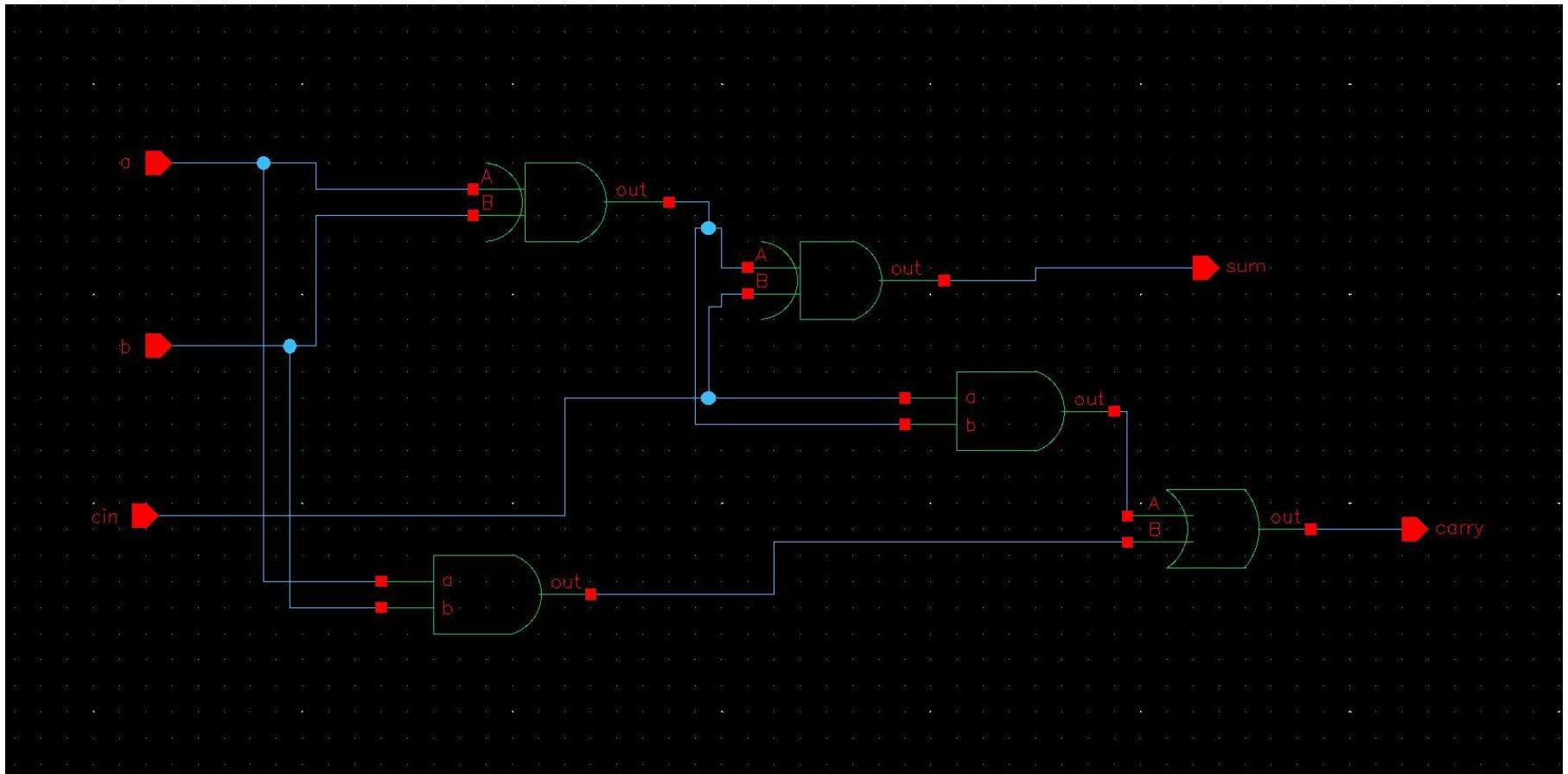
- Brute Force Implementation of Full Adder






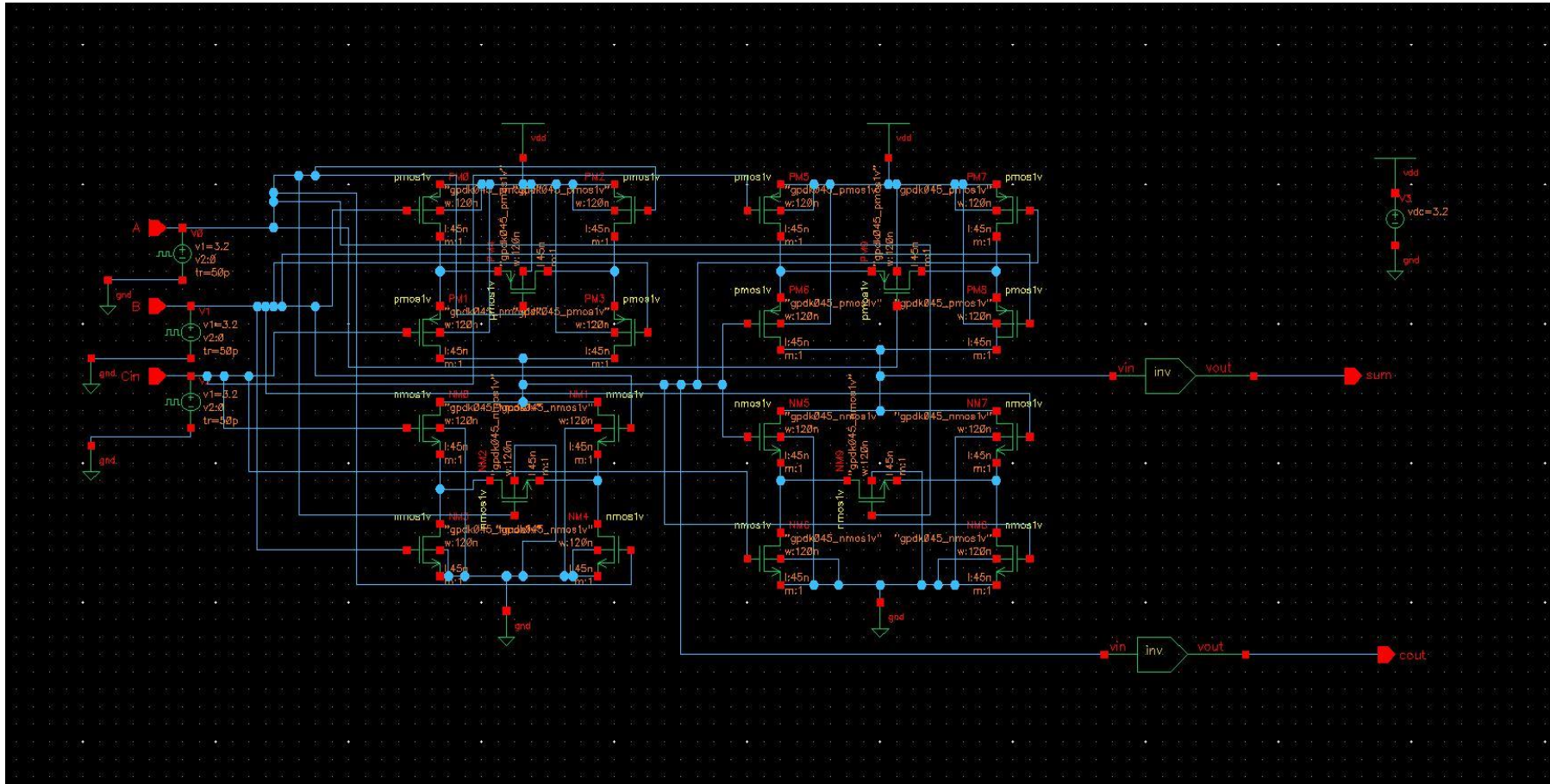
- Brute Force Implementation of Full Adder (Pass Transistor Logic)



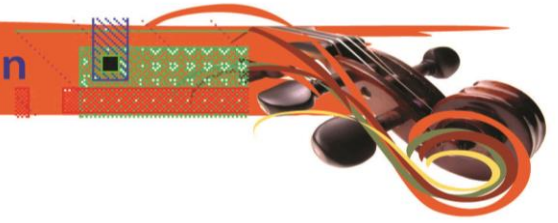


- CMOS Full Adder

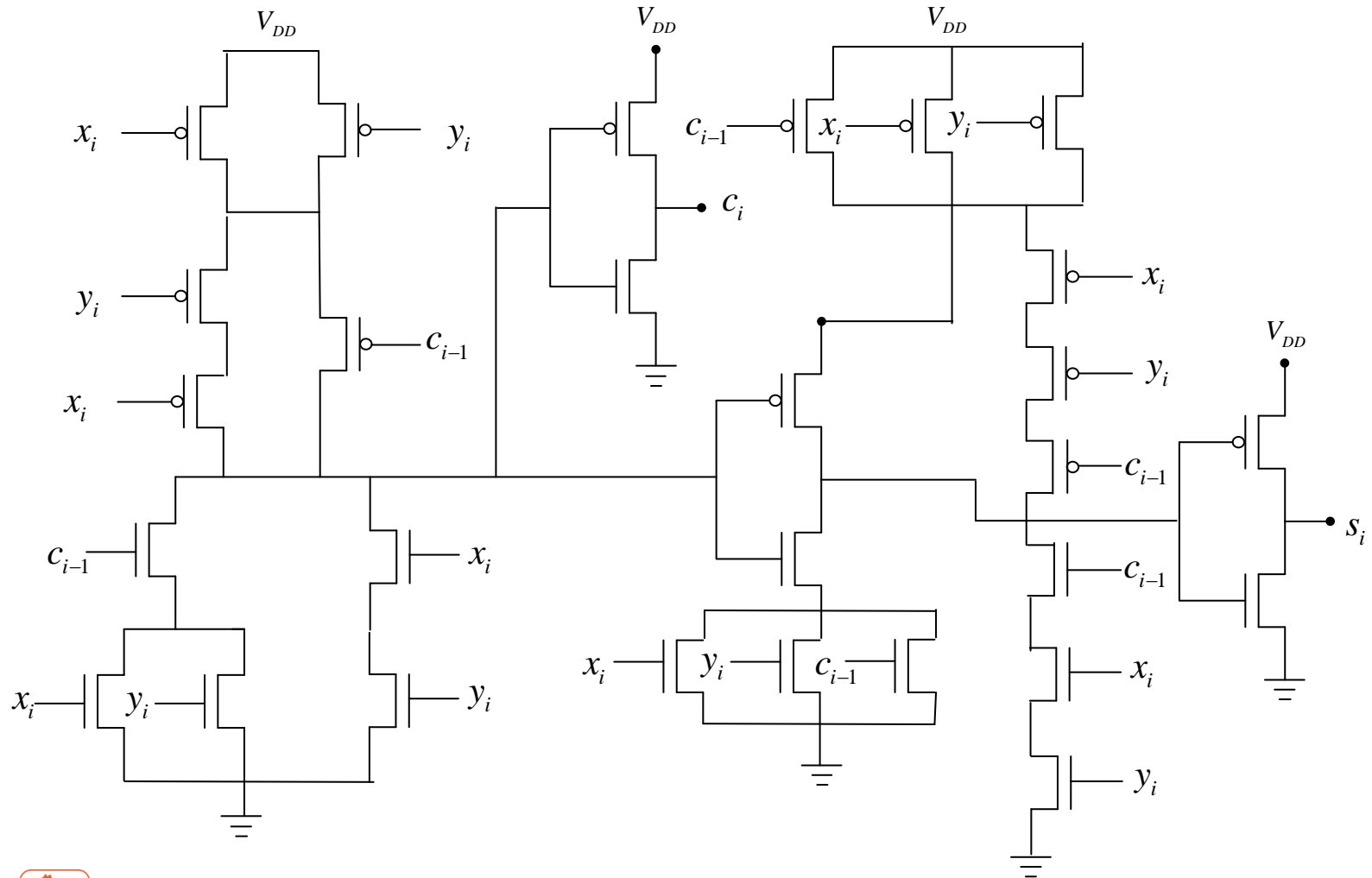

 

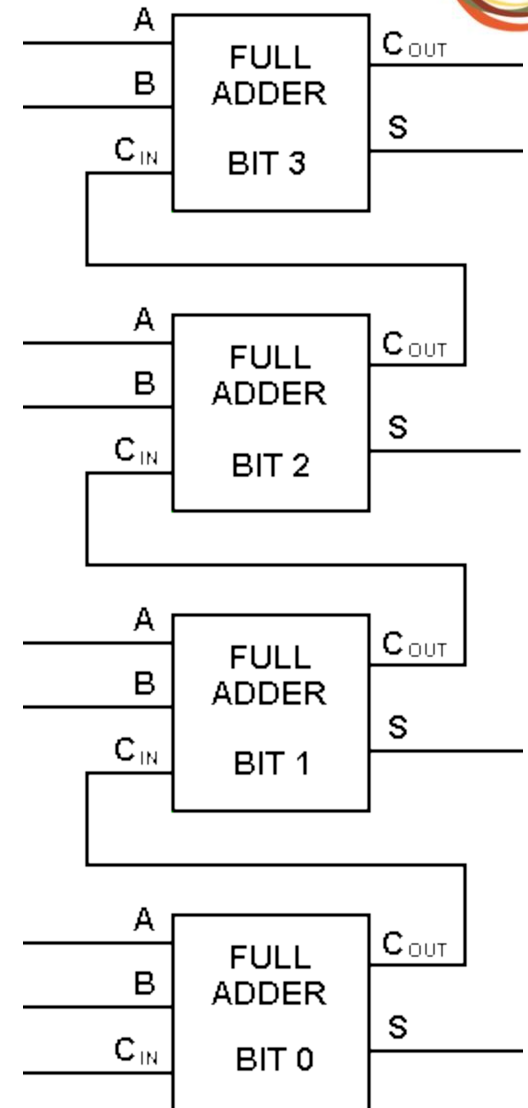- Full Adder
- If we have carryout propagating from bit 0 to bit 3, then the delay will be increased. The more bits we design the more critical delay it may have.








- Carry Skip Adder
- Calculate the “carry out” at the same time as the sum calculation
- Takes the “propagate” of each adder ( $a \oplus b$ ) into an AND gate as inputs
- If the AND gate output is “0” the output of the MUX is Cout of the final full adder
- If all propagates are “1” then the output of the AND gate is “1” and selector of the MUX chooses C0
- If




- Carry Skip Adder

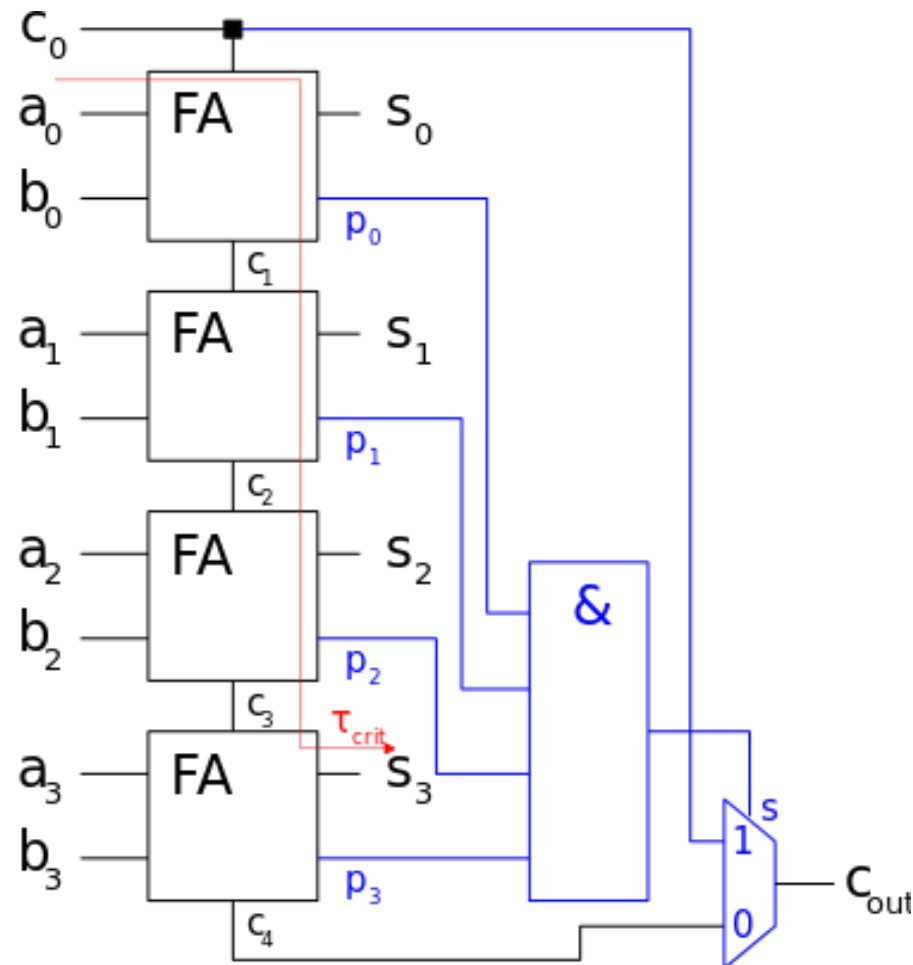




- 8-bit Carry Skip Adder

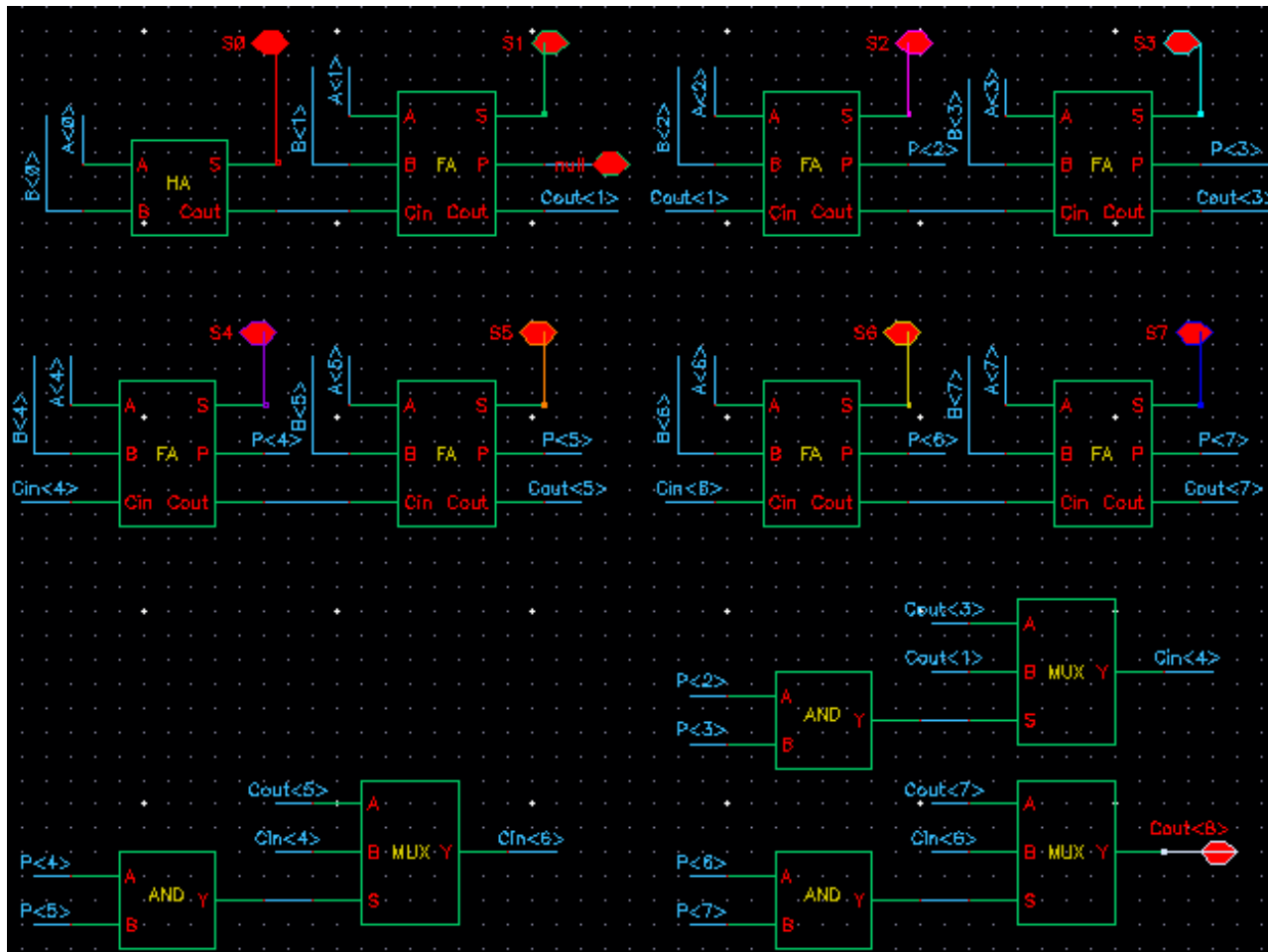







- 8-bit Carry Skip Adder
 
$$\begin{array}{r} 00000000 \\ +11111111 \\ \hline 01111111 \end{array}$$

  
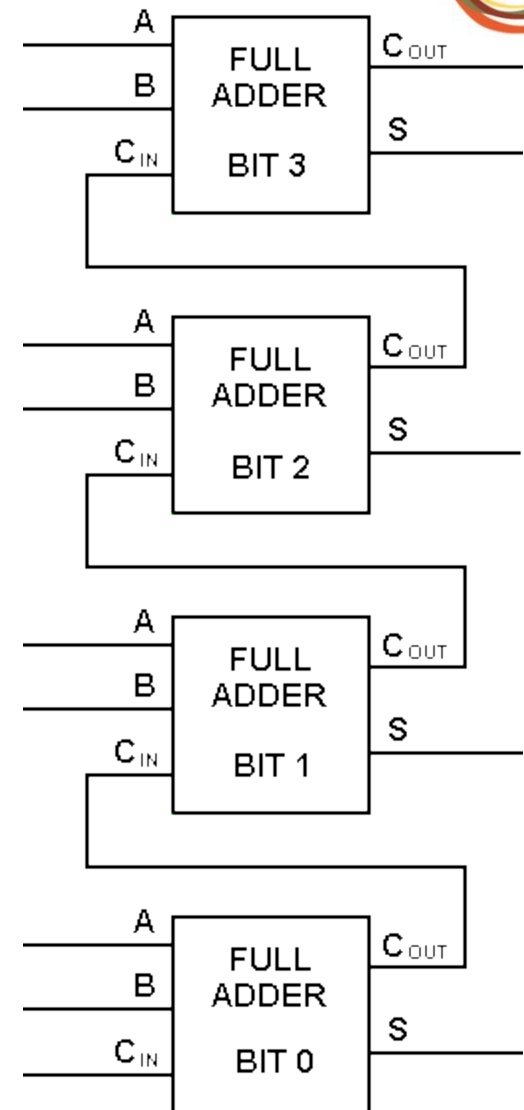


- 8-bit Carry Skip Adder

$$\begin{array}{r} 11111111 \\ +11111111 \\ \hline 111111110 \end{array}$$




- Full Adder
- If we have carryout propagating from bit 0 to bit 3, then the delay will be increased. The more bits we design the more critical delay it may have.





- Carry Lookahead Adder (CLA)
- **Advantage**
- Fast adder
- Good for high speed digital design.
- **Disadvantage**
- Area consumption
- Extra gates for the functions of 'Propagate' and 'Generate'.



- To resolve the delay issue on the Ripple-Carry Adder, they add some more logics to make the adder become CLA. The CLA's calculation does no longer depend on the previous carry bit; all the SUMs' calculations are depending on the first  $C_{in}(0)$  and the input values only. Therefore, the delay is greatly improve if you have a huge input # design.



- Defining 3 new variables that only depends on  $x_i$  and  $y_i$
- **1 Generate (g):**  $C_i = 1$  independent of  $C_{i-1}$   
$$g_i = x_i y_i$$
- **2 Propagate (p):**  $C_{i-1} = C_i$   
$$p_i = x_i \oplus y_i$$
- **3 Kill, Delete(d):**  $C_i = 0$  independent of  $C_{i-1}$   
$$d = \overline{x_i y_i}$$



- Full-Adder

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$

$$c_i = x_i y_i + x_i c_{i-1} + y_i c_{i-1}$$

$c_{i-1}$	$x_i$	$y_i$	$s_i$	$c_i$	
Inputs			Outputs		
0	0	0	0	0	Delete
0	0	1	1	0	Propagate
0	1	0	1	0	Propagate
0	1	1	1	1	Generate
1	0	0	1	0	Delete
1	0	1	0	1	Propagate
1	1	0	0	1	Propagate
1	1	1	1	1	Generate





- Expressing sum and carry in terms of generate, propagate, and delete.

$$c_0 = g_0$$

$$c_1 = g_1 + p_1 c_0 = g_1 + p_1 g_0$$

$$c_2 = g_2 + p_2 c_1 = g_2 + p_2 g_1 + p_2 p_1 g_0$$


$$s_i = x_i \oplus y_i \oplus c_{i-1} = p_i \oplus c_{i-1}$$


$$c_i(g, p) = g + p c_{i-1}$$






- Carry Lookahead Adder (CLA)

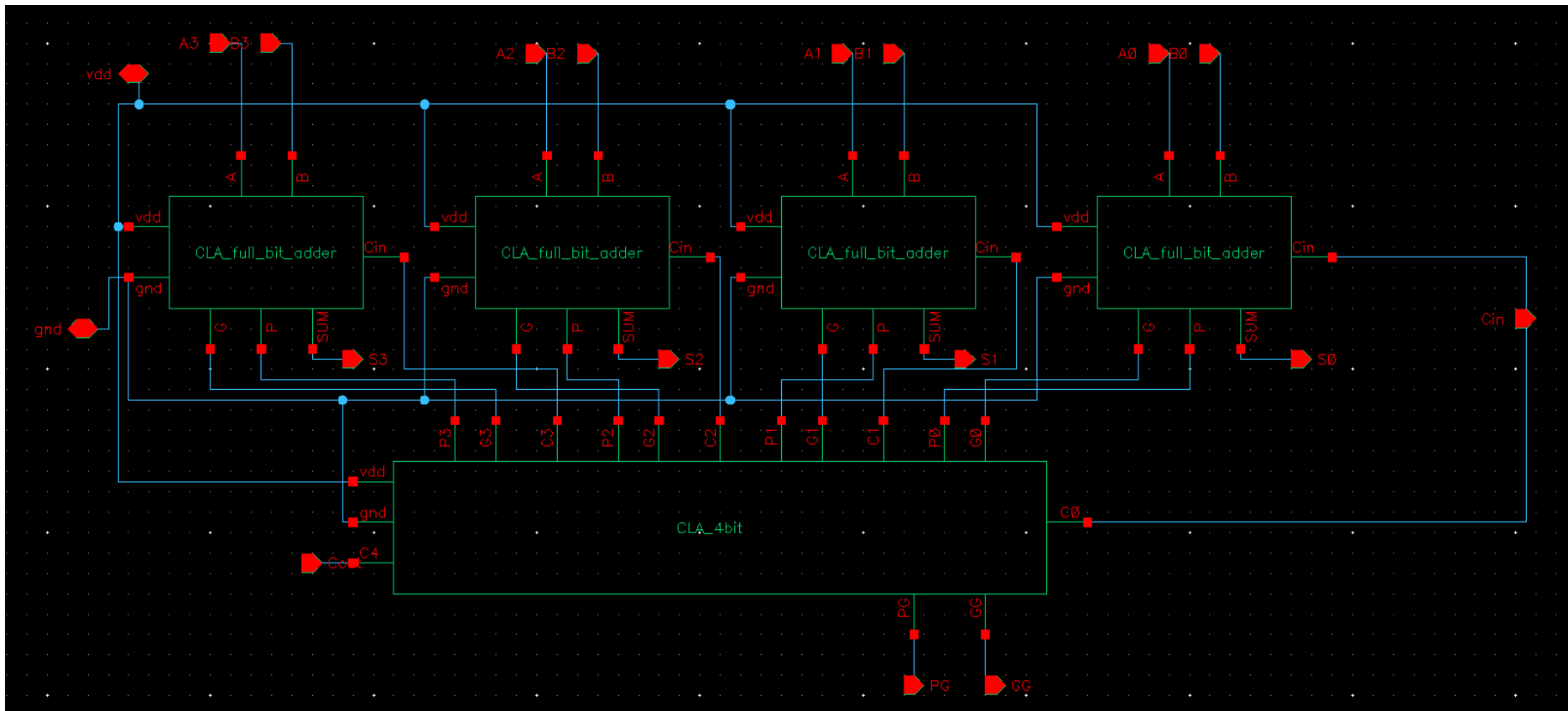

 

- The Ripple-Carry Adder

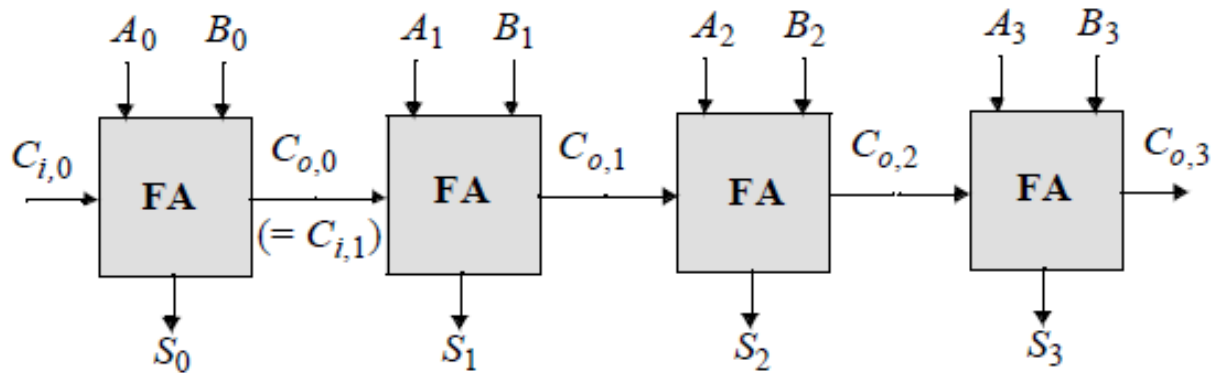

**Worst case delay linear with the number of bits**


$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N - 1)t_{\text{carry}} + t_{\text{sum}}$$

Goal: Make the fastest possible carry path circuit



- Inversion Properties

 


$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$




- Adder

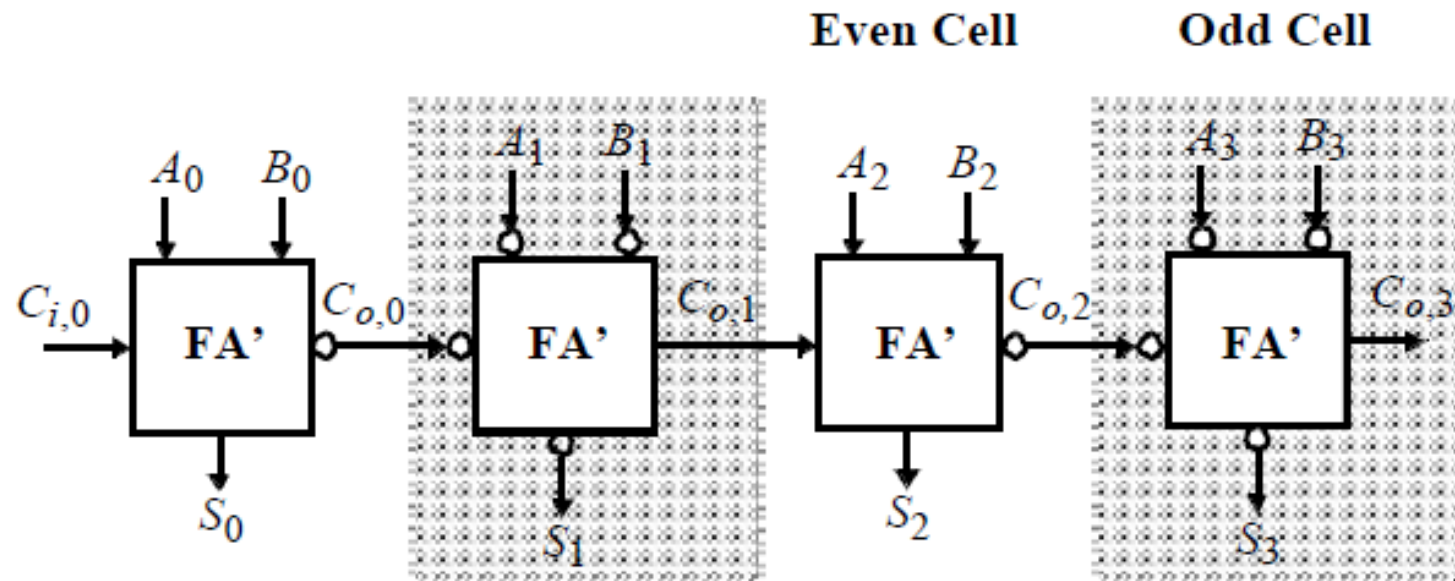

**Exploit Inversion Property**



- The Mirror Adder

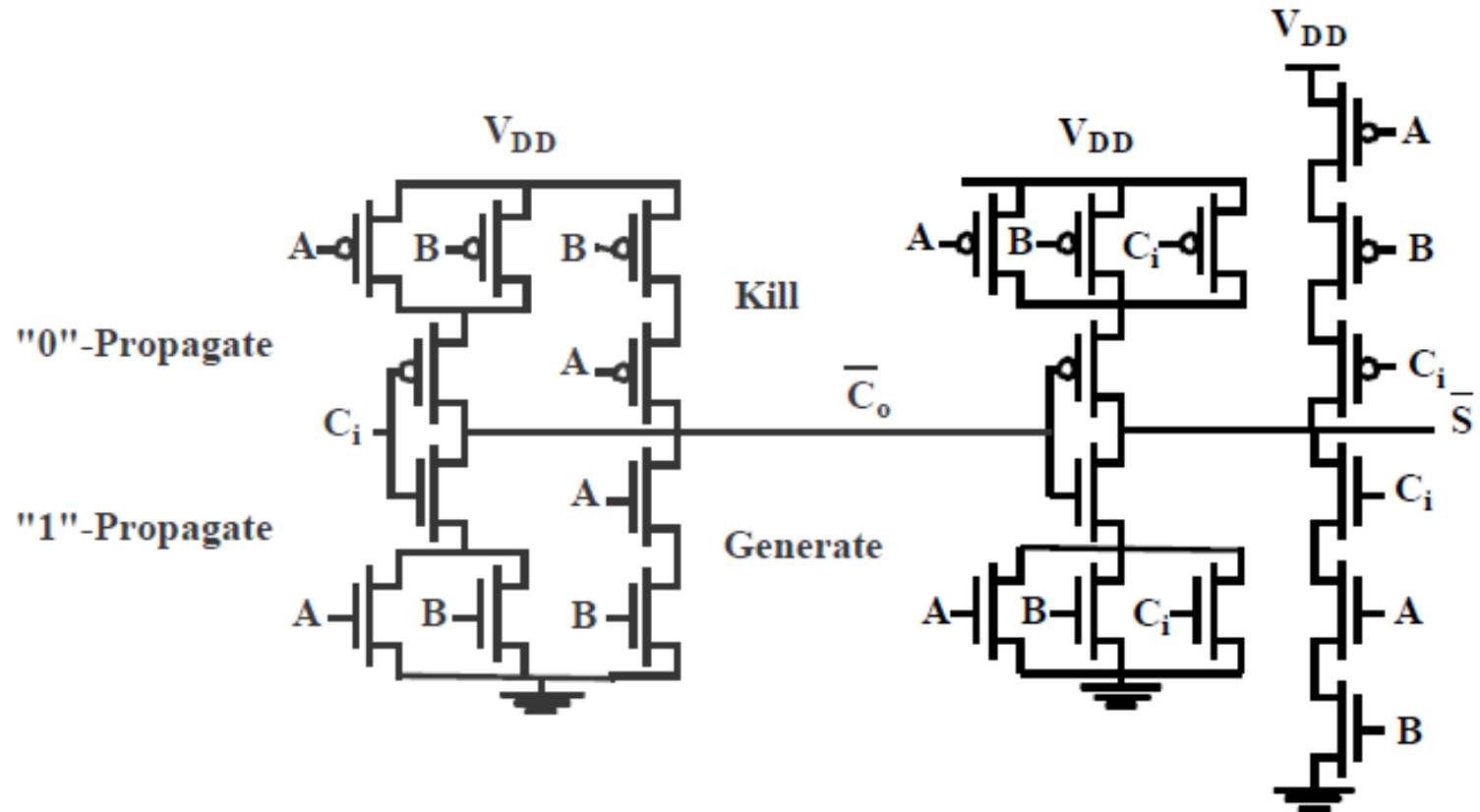


**24 transistors**






- The Mirror Adder

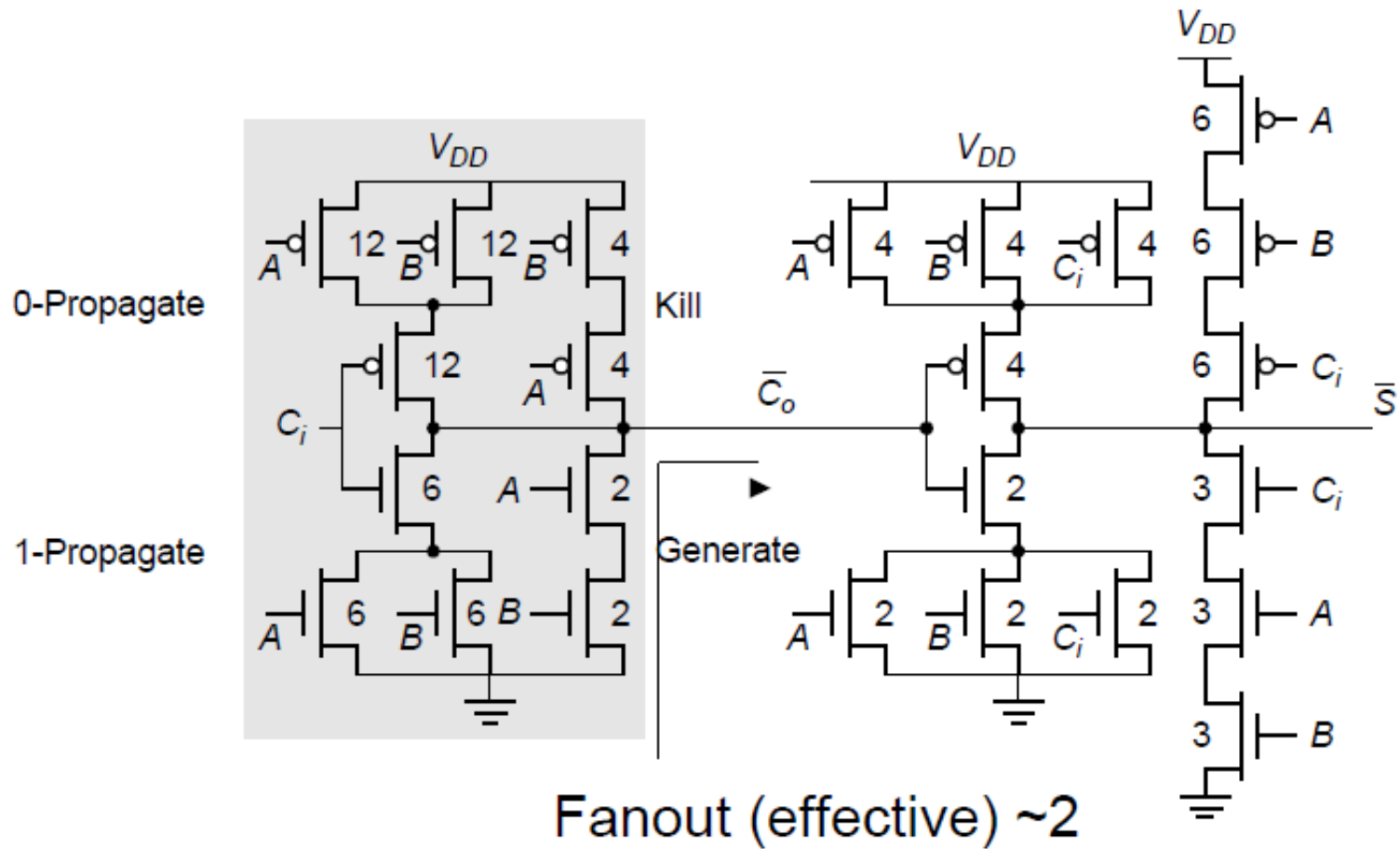




- Full Adder Implementation

 

Standard CMOS

 


Multiplexer-based






- TG-based Full adder

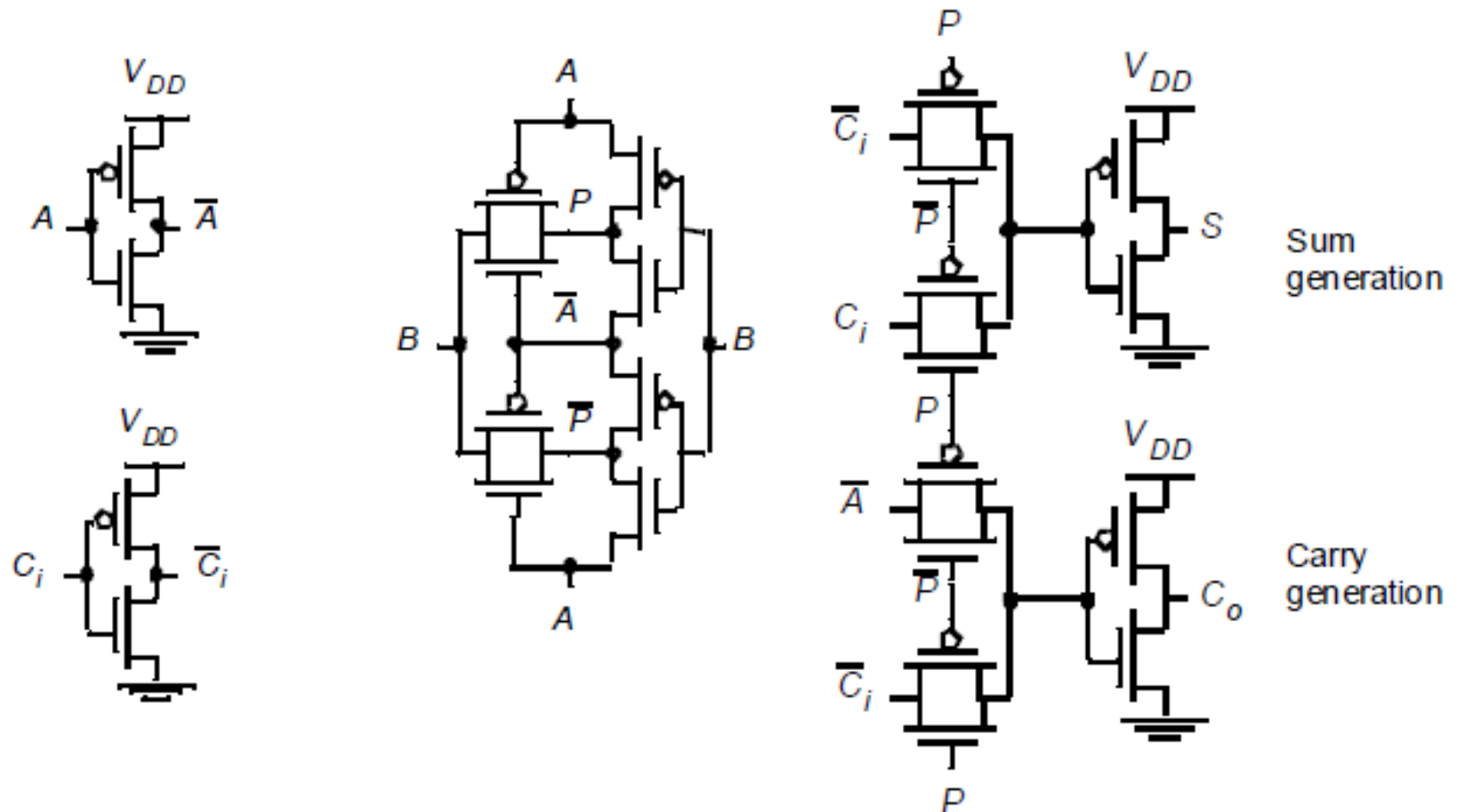




- Full Adder in DPL

 




- Manchester Carry Chain

Static

 

Dynamic

 




-





- Sizing Manchester Carry Chain

 

$$t_p = 0.69 \sum_{i=1}^N C_i \left( \sum_{j=1}^i R_j \right)$$

Tapering?

  




- Sizing Manchester Carry Chain
- Delay equation

$$t_p = 0.69 \sum_{i=1}^N C_i \left( \sum_{j=1}^i R_j \right) = 0.69 \frac{N(N+1)}{2} RC$$

 - Delay is quadratic with N
  - » Progressive sizing should help?



- Sizing Manchester Carry Chain

## Stick Diagram


$C_{fix}$  – fixed capacitance  
at the node ( pull-down,  
pull-up diffusions, metal,  
+ inverter  $\sim 15\text{fF}$

$C \sim 2\text{fF}/\mu\text{m}$

$R \sim 10\text{k}\Omega/\mu\text{m}$

When  $CW > C_{fix}$

 small improvements with  
sizing,  
Loading of the input stage



$$t_p = 0.69 \frac{N(N+1)}{2} RC = 0.69 \frac{N(N+1)}{2} \frac{R}{W} (C_{fix} + C \cdot W)$$




- Manchester Carry Chain
- Length of chain is limited to  $k = 4-8$
- Standard solution – add inverters
- The overall  $N$ -bit adder delay is a sum of  $N/k$  segments (linear)






- Carry-skip Adder

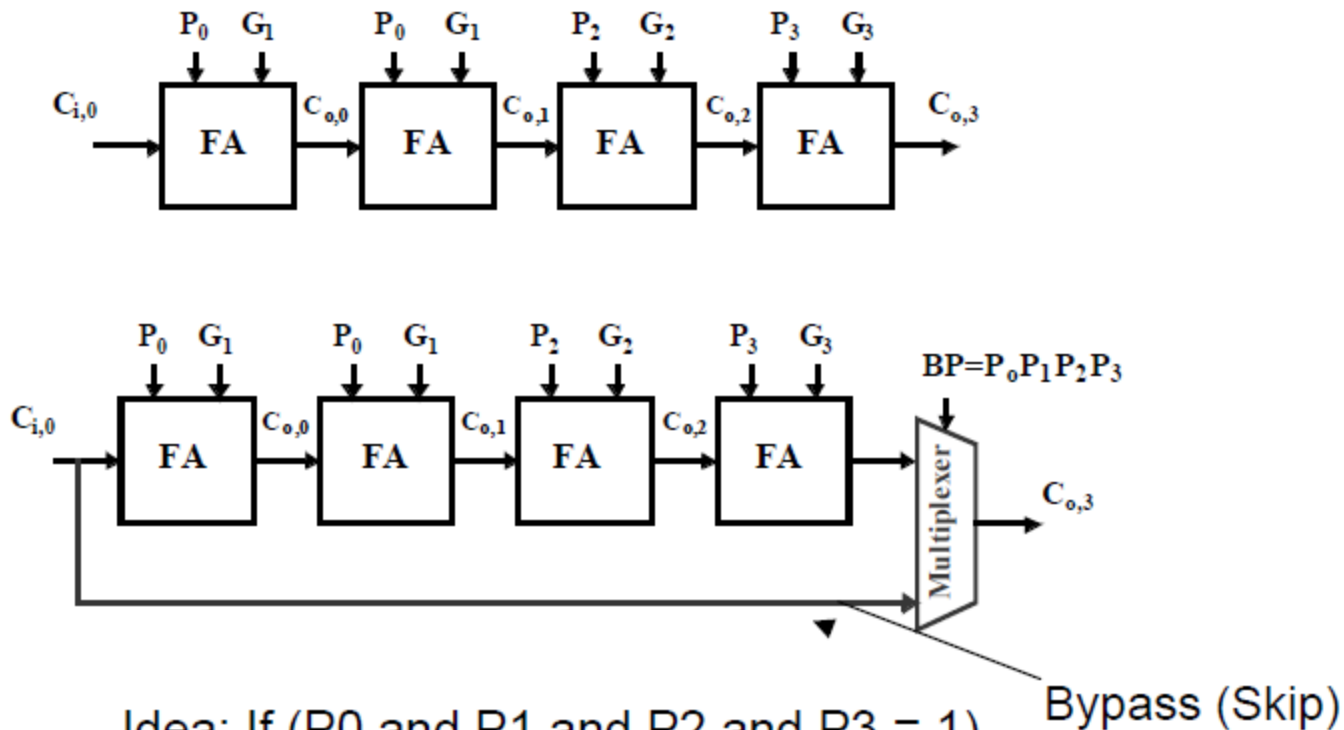


Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ )  
then  $C_{o3} = C_0$ , else “kill” or “generate”.

MacSorley, Proc IRE 1/61

Lehman, Burla, IRE Trans on Comp, 12/61

 

- Carry-skip Adder

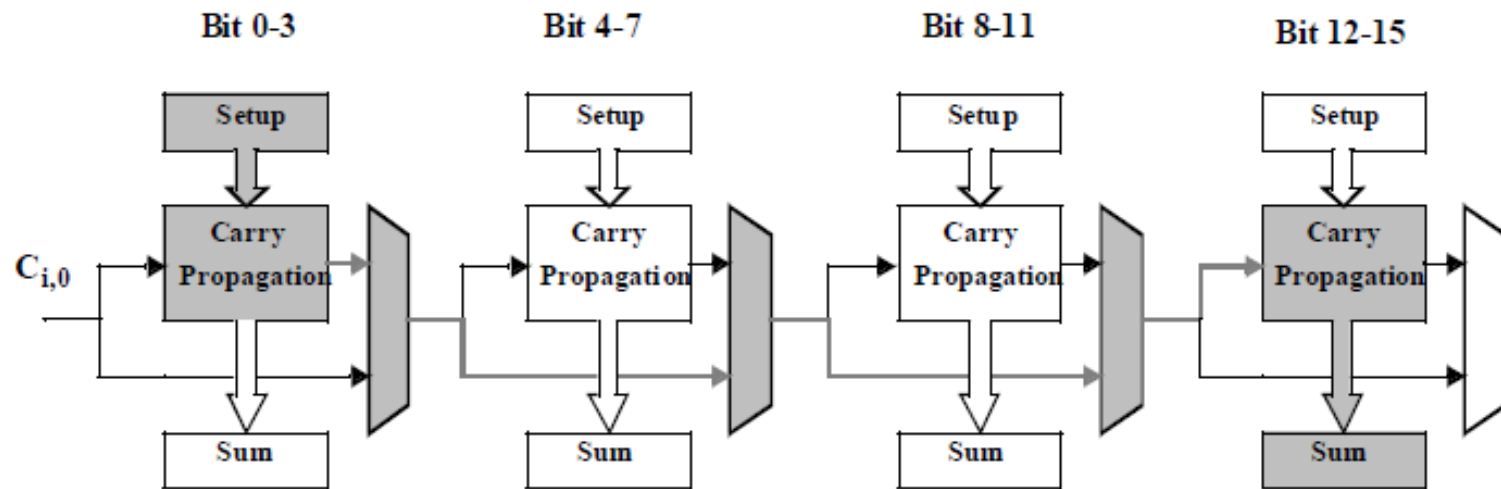


Critical Path

For N-bit adder with k-bit groups

$$t_d = (k-1)t_{RCA} + \left(\frac{N}{k} - 2\right)t_{SKIP} + (k-1)t_{RCA}$$



- Carry-skip Adder

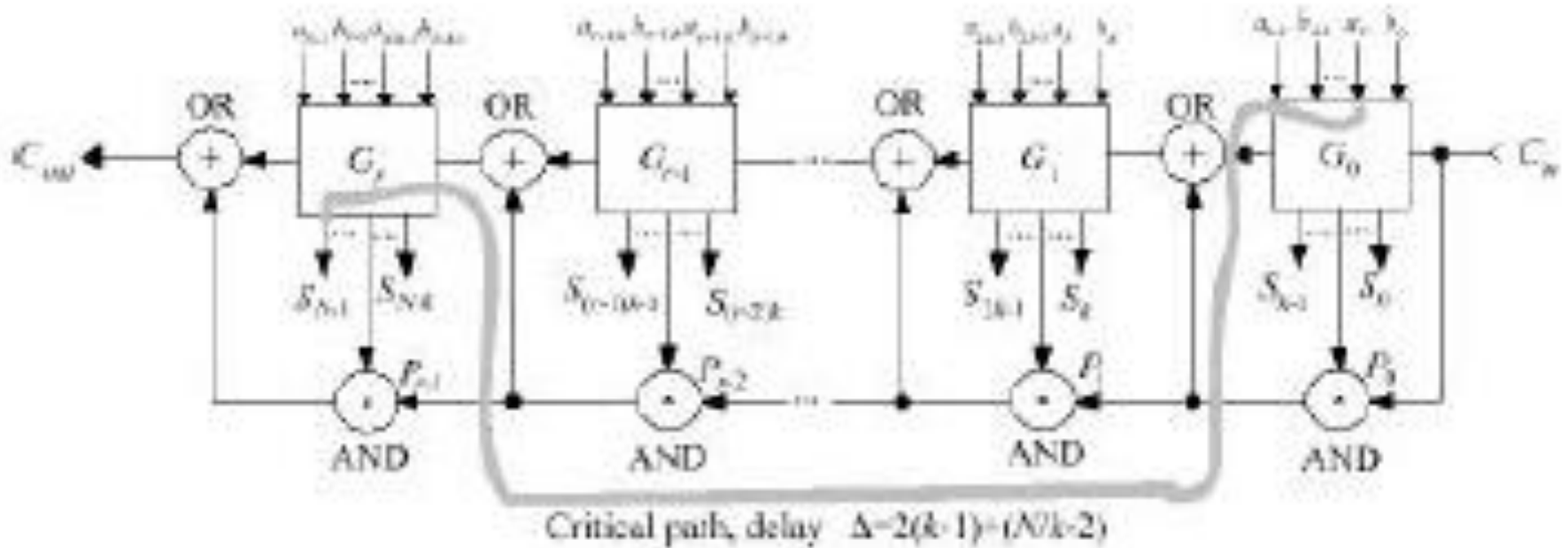




- Carry-skip Adder

Critical path delay with constant groups

 
$$t_d = 2(k-1)t_{RCA} + \left(\frac{N}{k} - 2\right)t_{SKIP}$$





- Carry-skip Adder

Variable Group Length

 


$$x_1 = x_4 = 4, \quad x_2 = x_7 = 7, \quad x_3 = x_6 = 10, \quad x_5 = x_8 = 11, \quad |$$

$$t_d = c_1 + \sqrt{c_2 N + c_3}$$

Oklobdzija, Barnes, Arith'85




- Carry-skip Adder

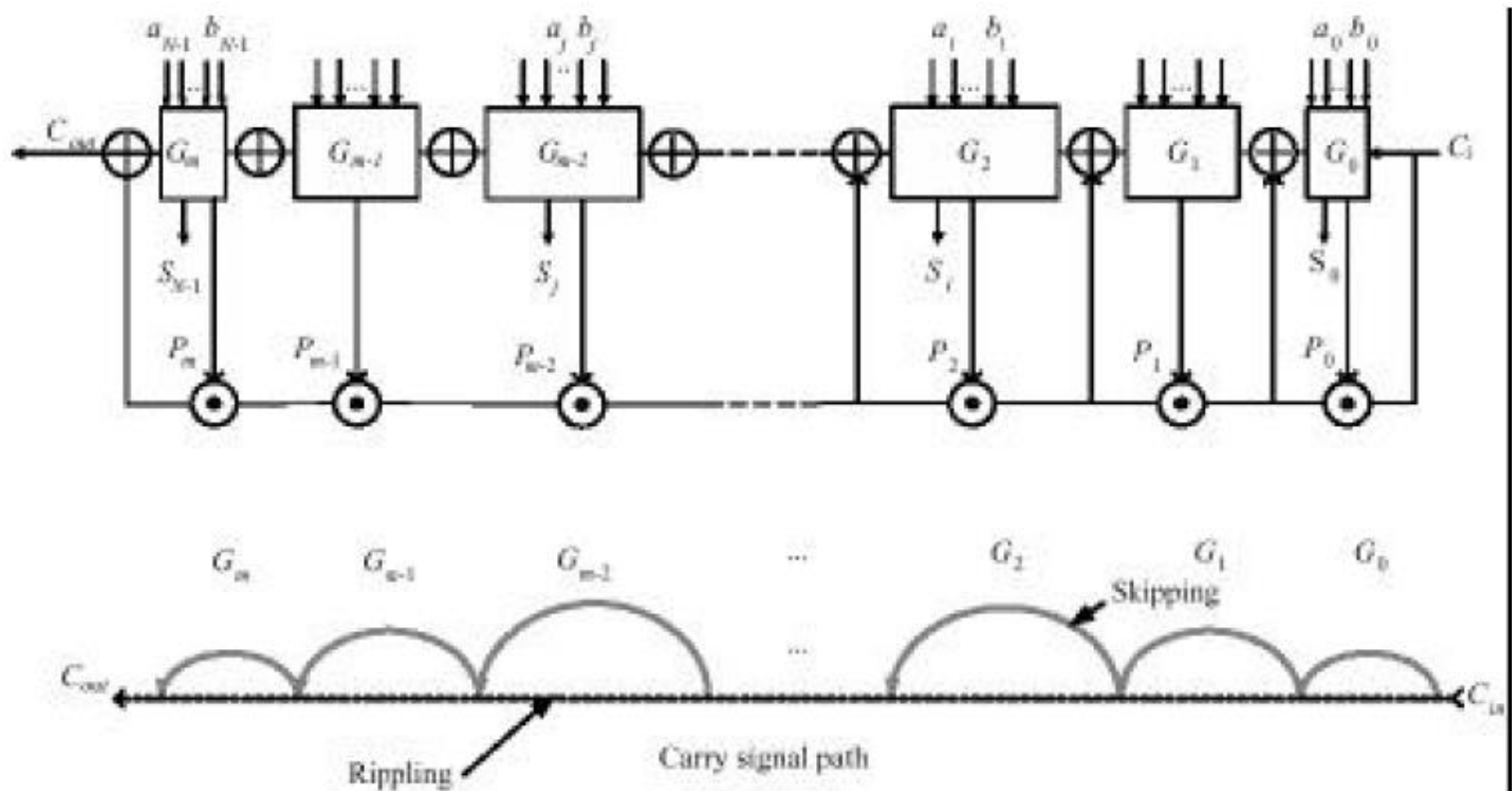



- Carry-skip Adder

Variable Block Lengths

 


Oklobdzija, Barnes, Arith'85






- Manchester Chain with Carry-skip Adder

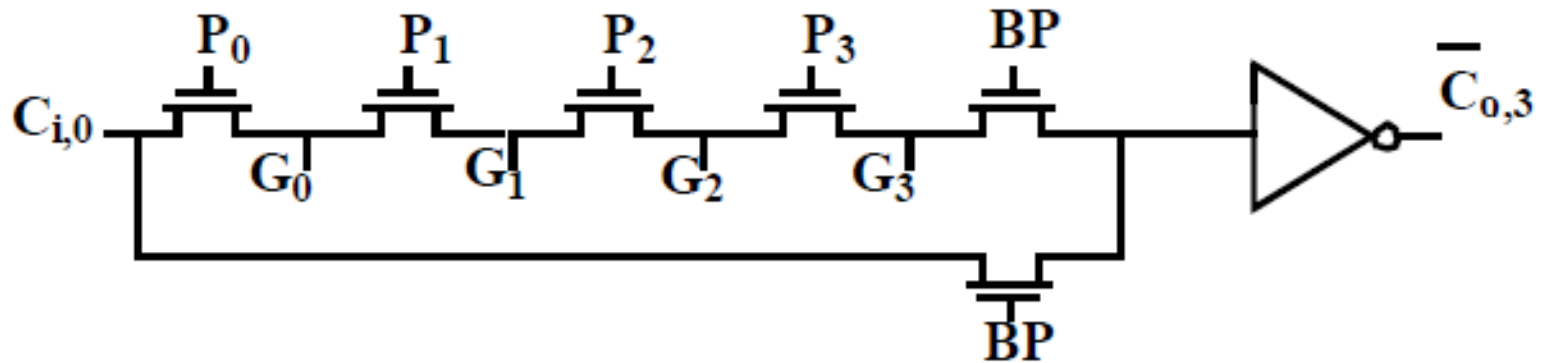


Delay model:

 





- PTL with SA-F Implementation

 

Matsui,  
JSSC 12/94

