

---

# EE230-02 RFIC II

## Fall 2018

### Lecture 16: Phase-Locked Loops


Prof. Sang-Soo Lee  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)  
ENG-259
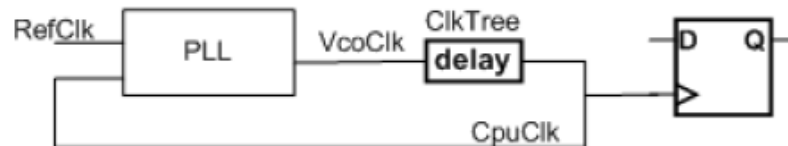
# How Are PLL's used?

- Frequency Synthesis (e.g. generating a 1 GHz clock from a 100 MHz reference in a CPU)




- Skew Cancellation (e.g. phase-aligning an internal clock to the I/O clock) (May use a DLL instead)


 
# How Are PLL's used?

- Extracting a clock from a random data stream (e.g. serial-link clock-data recovery)




- Reference Clean-Up (e.g. low-pass filter source-synchronous clock in high-speed I/O)


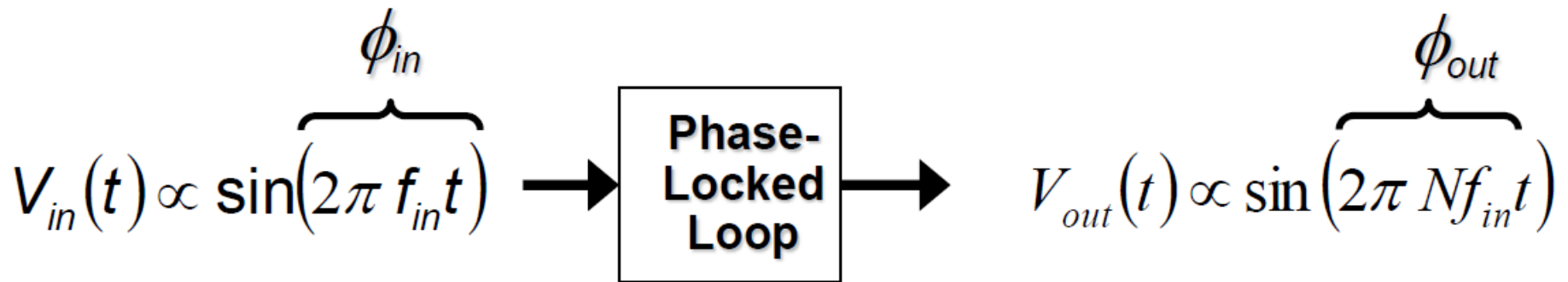
# What is a PLL?

- Negative feedback control system where  $f_{out}$  tracks  $f_{in}$  and rising edges of input clock align to rising edges of output clock
- Mathematical model of frequency synthesizer





- **Phase =  $\int$  frequency**

$$\phi(t) = 2\pi \int f(t) dt \leftrightarrow f(t) = \frac{1}{2\pi} \frac{d\phi(t)}{dt}$$


- **When phase-locked,**  $\phi_{out} = N\phi_{in} \rightarrow f_{out} = Nf_{in}$
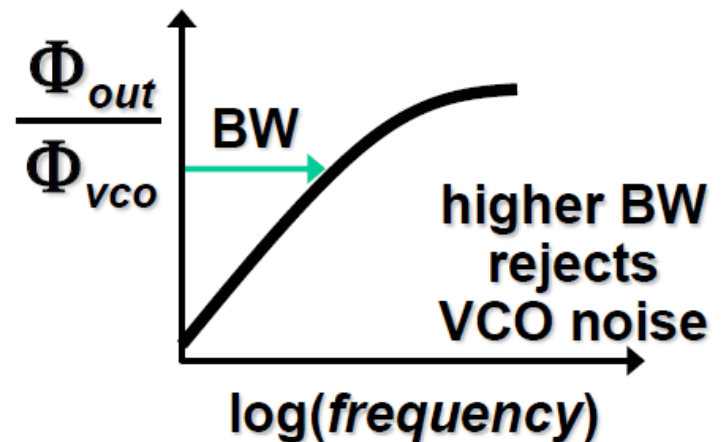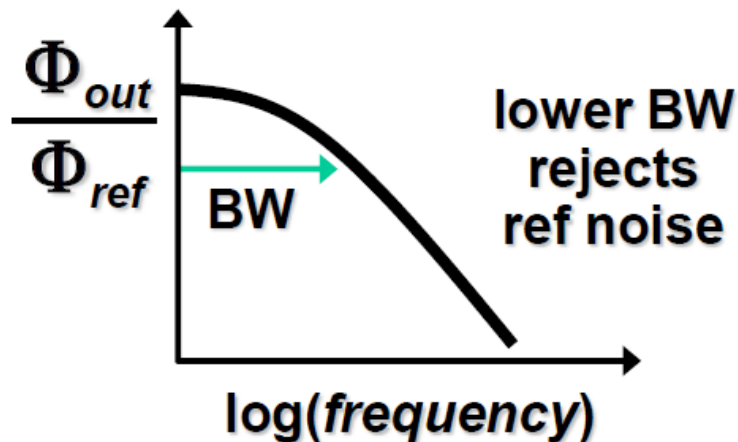
# What does PLL Bandwidth means?

- PLL acts as a low-pass filter with respect to the reference modulation. High-frequency reference jitter is rejected
- Low-frequency reference modulation (e.g., spread-spectrum clocking) is passed to the VCO clock
- PLL acts as a high-pass filter with respect to VCO jitter
- “Bandwidth” is the modulation frequency at which the PLL begins to lose lock with the changing reference (-3dB)





# Simple Type-I PLL and Loop Filter

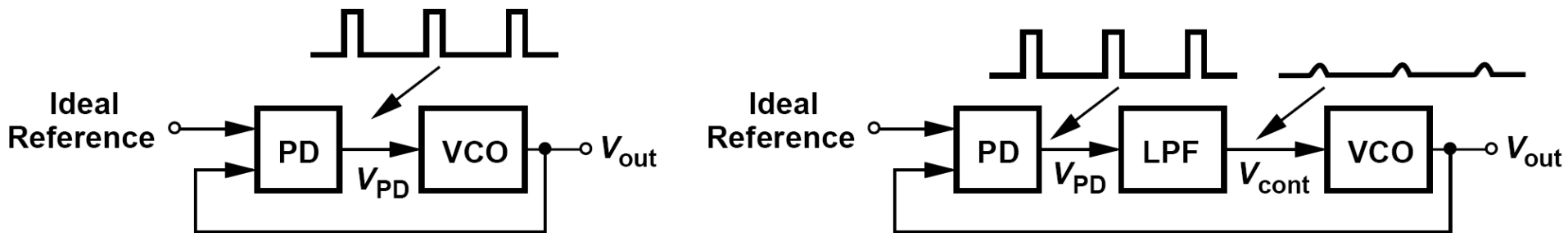

- Negative feedback loop: if the “loop gain” is sufficiently high, the circuit minimizes the input error.
- The PD produces repetitive pulses at its output, modulating the VCO frequency and generating large sidebands.
- Insert a low-pass filter between the PD and the VCO to suppress these pulses.

# Simple PLL: Phase Locking

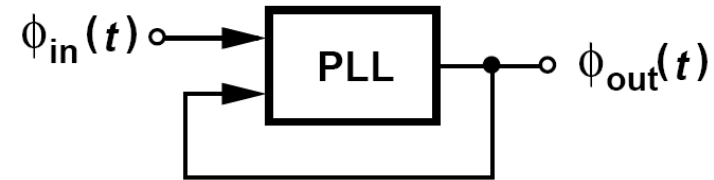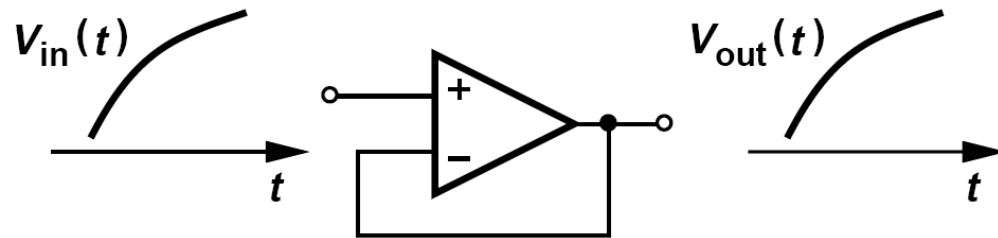


$$\phi_{out}(t) - \phi_{in}(t) = \text{constant}$$

$$\frac{d\phi_{out}}{dt} = \frac{d\phi_{in}}{dt}$$

- Loop is “locked” if  $\phi_{out}(t) - \phi_{in}(t)$  is constant with time.
- Phase locking makes the input and output frequencies of the PLL exactly equal.
 
# Example of Phase Error

If the input frequency changes by  $\Delta\omega$ , how much is the change in the phase error?  
Assume the loop remains locked.





$$V_{cont} \text{ change} = \Delta\omega / K_{VCO} \quad \longrightarrow \quad \Delta\phi_2 - \Delta\phi_1 = \frac{\Delta\omega}{K_{PD}K_{VCO}}$$

- Phase error varies with the frequency.
- To minimize this variation,  $K_{PD}K_{VCO}$  must be maximized.
- $K_{PD}K_{VCO}$  is called the “loop gain”.



 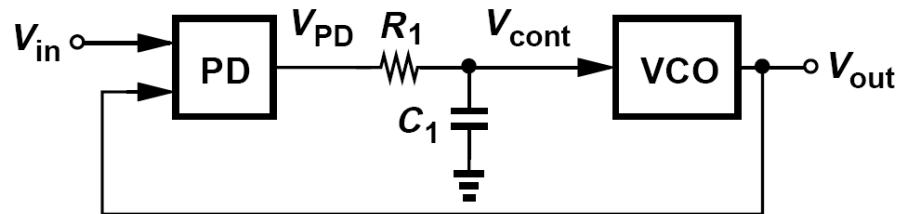
# Response of PLL to Input Frequency Step



- The loop locks only after two conditions are satisfied:
- (1)  $\omega_{out}$  becomes equal to  $\omega_{in}$
  - (2) the difference between  $\phi_{in}$  and  $\phi_{out}$  settles to its proper value

# Loop Dynamics: Phase Domain Model

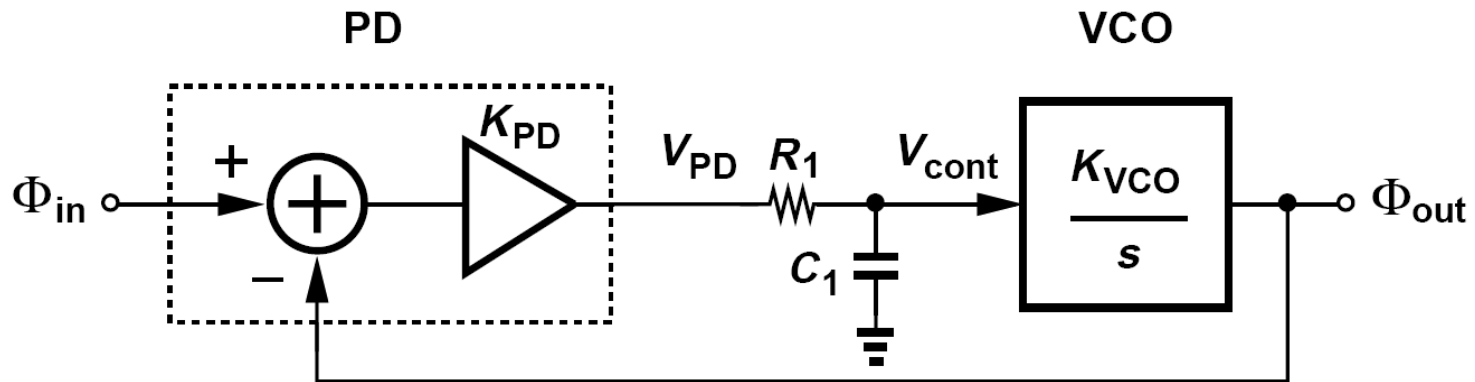

Open-loop transfer function

$$[K_{PD}/(R_1 C_1 s + 1)](K_{VCO}/s)$$

Closed-loop transfer function

$$H(s) = \frac{\phi_{out}}{\phi_{in}}(s) = \frac{K_{PD} K_{VCO}}{R_1 C_1 s^2 + s + K_{PD} K_{VCO}}.$$

# Damping Factor and Natural Frequency

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$

$$\omega_n = \sqrt{K_{PD}K_{VCO}\omega_{LPF}}$$


$\zeta$  is inversely proportional to  $K_{VCO}$ .

Behavior of the open-loop transfer function,  $H_{open}$ , for two different values of  $K_{VCO}$

As  $K_{VCO}$  increases, the unity-gain frequency rises, thus reducing the phase margin (PM).

➤ The damping factor is typically chosen to be  $\sqrt{2}/2$  or larger so as to provide a well-behaved (critical damped or overdamped) response.

➤  $\omega_{LPF} = 1/(R_1C_1)$

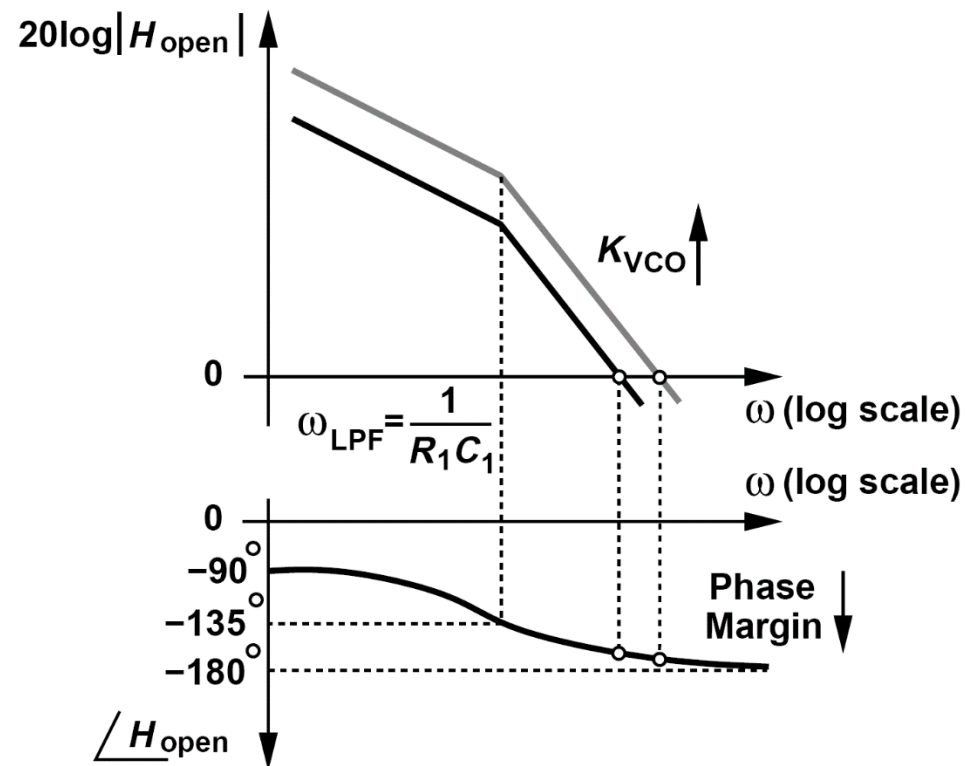




# Drawbacks of Type-I PLL

- Tight relation between the loop stability and the corner frequency of the low-pass filter. Ripple on the control line modulates the VCO frequency and must be suppressed by choosing a low value for  $\omega_{LPF}$ , leading to a less stable loop

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$


- Suffers from a limited “acquisition range”  
If the VCO frequency and the input frequency are very different at the start-up, the loop may never “acquire” lock.
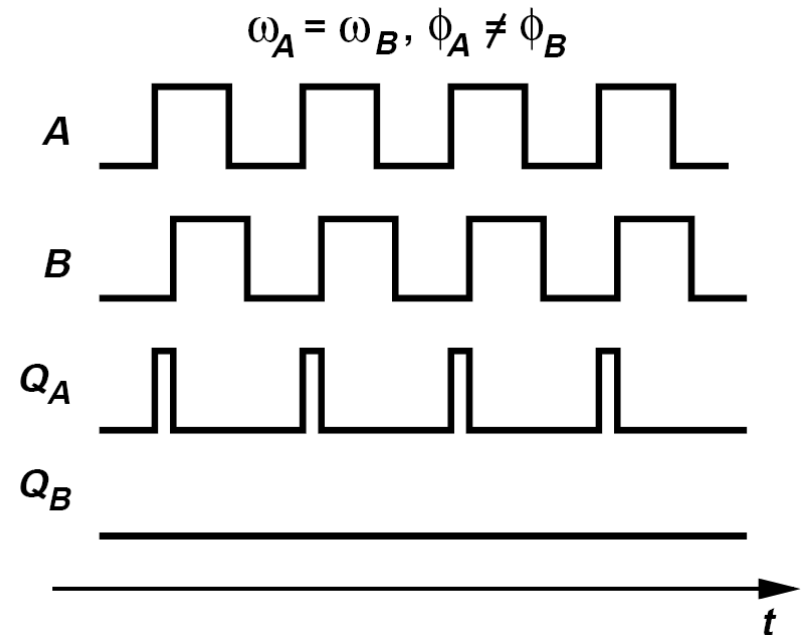 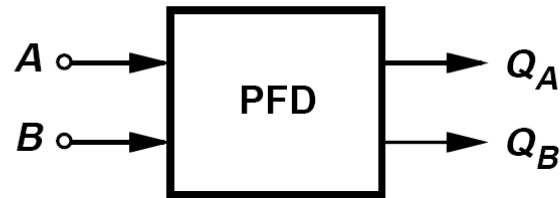
# Type-II PLLs: Phase/Frequency Detectors



- A rising edge on  $A$  yields a rising edge on  $Q_A$  (if  $Q_A$  is low)
- A rising edge on  $B$  resets  $Q_A$  (if  $Q_A$  is high)
- The circuit is symmetric with respect to  $A$  and  $B$  (and  $Q_A$  and  $Q_B$ )

# PFD: Logical Implementation

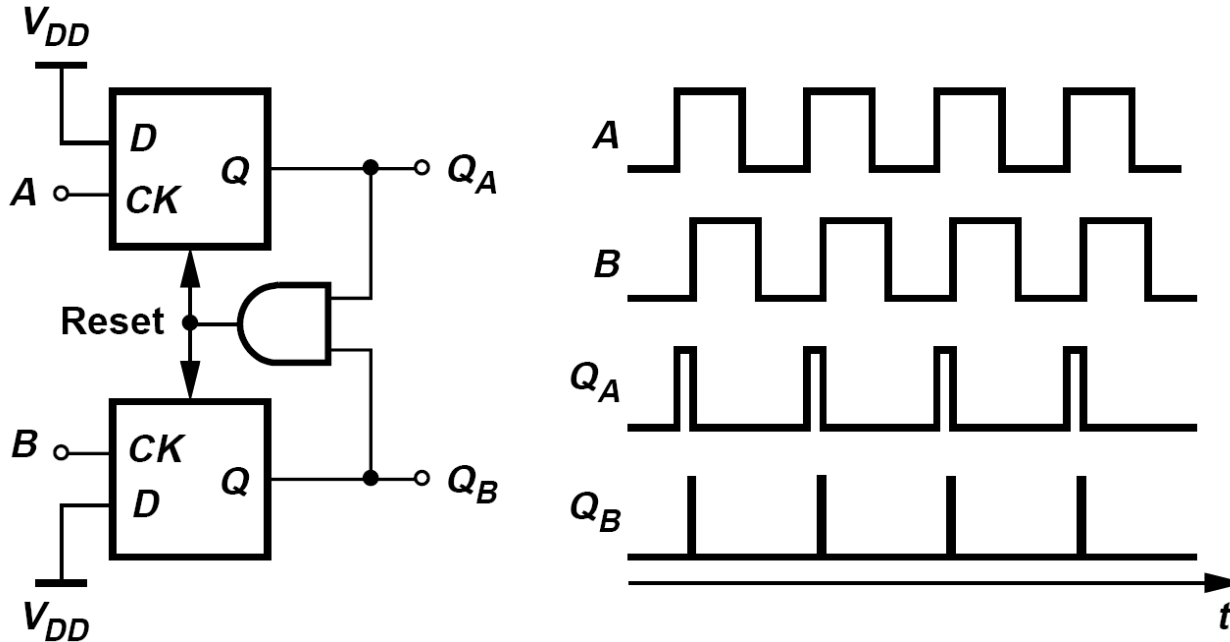

- $Q_A$  and  $Q_B$  are simultaneously high for a duration given by the total delay through the AND gate and the reset path of the flipflops.