
EE230-02 RFIC II

Fall 2018

Lecture 3: RF Basics Review2

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

Non-idealities in RF Circuits

- ☐ Definition: Signal Power
- ☐ Noise
- ☐ Linearity

Voltage Gain and Power Gain

Voltage Gain $A_{V|dB} = 20 \log \frac{V_{out}}{V_{in}}$


Power Gain $A_{P|dB} = 10 \log \frac{P_{out}}{P_{in}}$

If an amplifier having an input resistance of R_i and driving a load resistance of R_o ,

$$\begin{aligned} A_{P|dB} &= 10 \log \frac{\frac{V_{out}^2}{R_o}}{\frac{V_{in}^2}{R_i}} = 10 \log \frac{V_{out}^2}{V_{in}^2} + 10 \log \frac{R_i}{R_o} \\ &= 20 \log \frac{V_{out}}{V_{in}} + 10 \log \frac{R_i}{R_o} = A_{V|dB} + 10 \log \frac{R_i}{R_o} \end{aligned}$$

Voltage Gain \neq Power Gain if $R_{in} \neq R_{out}$.

Noise Factor and Noise Figure (dB)

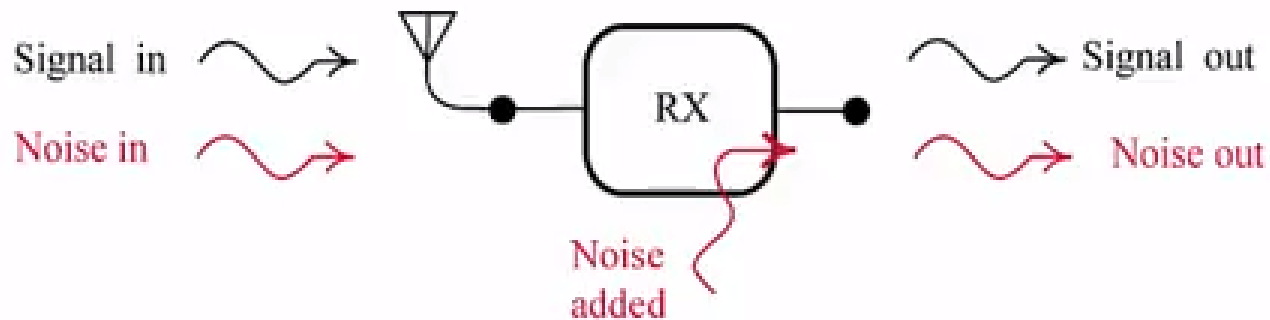

Signal Out = G x Signal In


Noise Out = G x Noise In

+ Noise added

$$NF = \frac{(SNR)_{in}}{(SNR)_{out}} \geq 1 \quad \text{A receiver degrades the SNR!}$$

Friis Formula

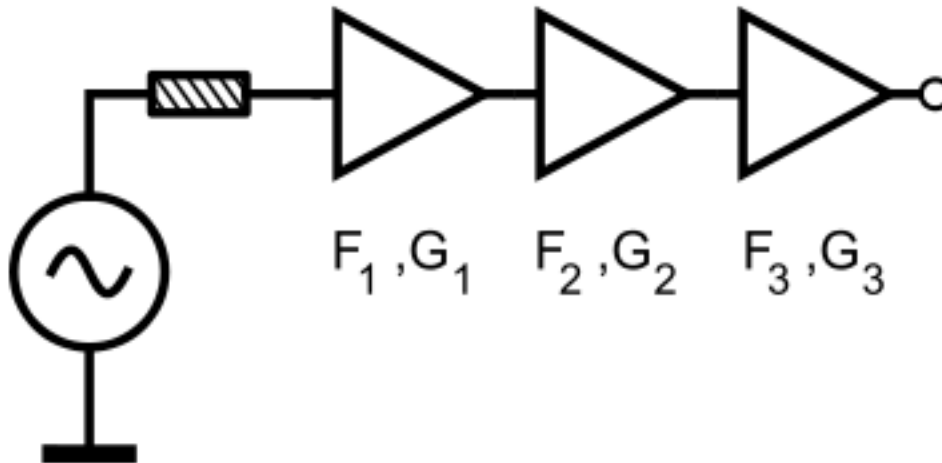Friis's formula is used to calculate the total noise factor of a cascade of stages, each with its own noise factor and gain where F_i and G_i are the noise factor and available [power gain](#). Note that both magnitudes are expressed as ratios, not in decibels.



$$F_{total} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} + \dots + \frac{F_n - 1}{G_1 G_2 \dots G_{n-1}}$$

Noise Figure of Cascaded Stages

- Which configuration is better in terms of noise?



- Filters are passive and usually lossy, i.e. $L (=1/G)$
- NF of a lossy stage is equal to its loss, i.e. $NF = L$

Noise Figure of Cascaded Stages


Example:

$$L = 1 \text{ dB} = 1.25$$


$$G_{\text{LNA}} = 10 \text{ dB} = 10$$

$$\text{NF}_{\text{LNA}} = 3 \text{ dB} = 2$$
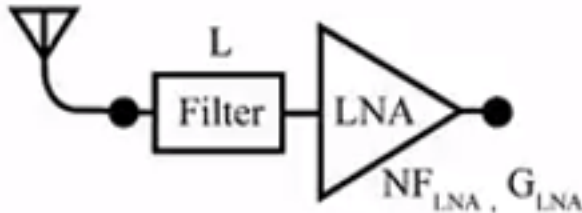
$$F_{\text{total}} = F_1 + \frac{F_2 - 1}{G_1}$$


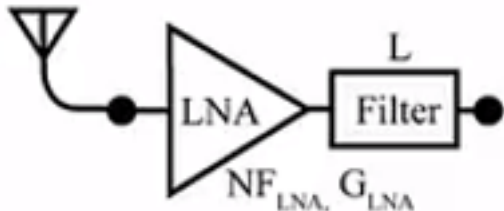
$$\begin{aligned} \text{NF}_{\text{tot}} &= L + (\text{NF}_{\text{LNA}} - 1) \cdot L \\ &= 1.25 + 1 \times 1.25 = 2.5 = 4\text{dB} \end{aligned}$$



$$\begin{aligned} \text{NF}_{\text{tot}} &= \text{NF}_{\text{LNA}} + (L - 1) / G_{\text{LNA}} \\ &= 2 + 0.25 / 10 = 2.025 = 3\text{dB} \end{aligned}$$

1. Place those components with lowest NF and highest gain at earlier stages
2. Avoid lossy components at the input

Linear vs. Nonlinear

Linear

$$y(t) = \alpha x(t)$$

Nonlinear

$$y(t) = \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t) + \dots$$

$$x(t) = A \cos \omega t$$


$$y(t) = \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 A^3 \cos^3 \omega t$$

$$= \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} (1 + \cos 2\omega t) + \frac{\alpha_3 A^3}{4} (3 \cos \omega t + \cos 3\omega t)$$

$$= \frac{\alpha_2 A^2}{2} + \left(\alpha_1 A + \frac{3\alpha_3 A^3}{4} \right) \cos \omega t + \frac{\alpha_2 A^2}{2} \cos 2\omega t + \frac{\alpha_3 A^3}{4} \cos 3\omega t$$

Gain Compression
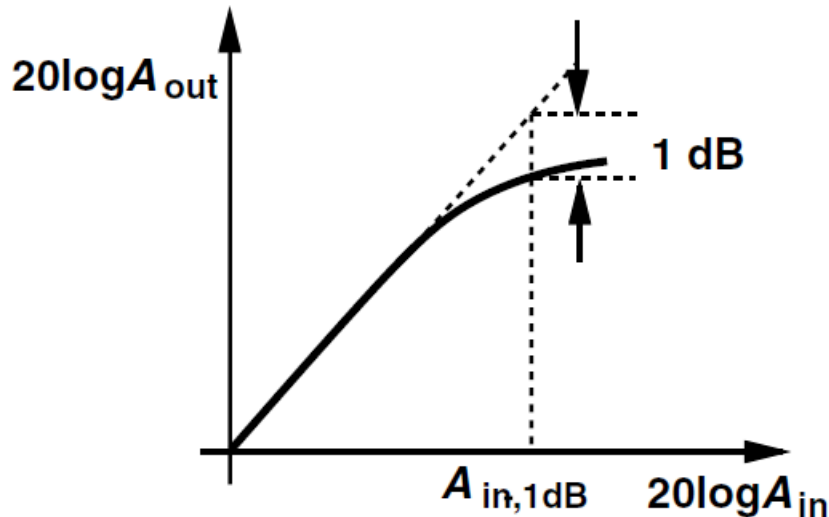
$$y(t) = \frac{\alpha_2 A^2}{2} + \left(\alpha_1 A + \frac{3\alpha_3 A^3}{4} \right) \cos \omega t + \frac{\alpha_2 A^2}{2} \cos 2\omega t + \frac{\alpha_3 A^3}{4} \cos 3\omega t$$



$$20 \log \left| \alpha_1 + \frac{3}{4} \alpha_3 A_{\text{in},1\text{dB}}^2 \right| = 20 \log |\alpha_1| - 1 \text{ dB}$$



$$A_{\text{in},1\text{dB}} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

Gain Desensitization

$$y(t) \approx \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t \quad A_1 \ll A_2$$
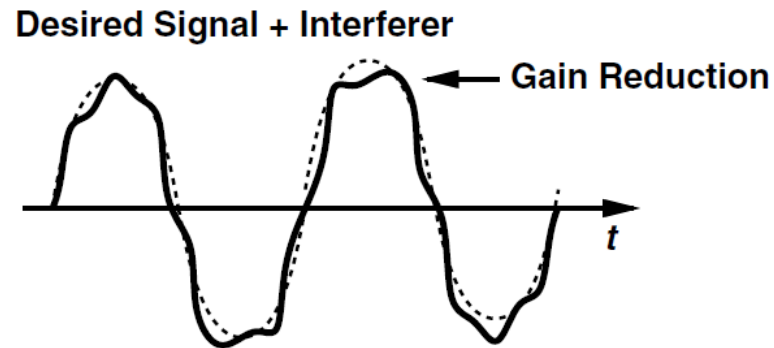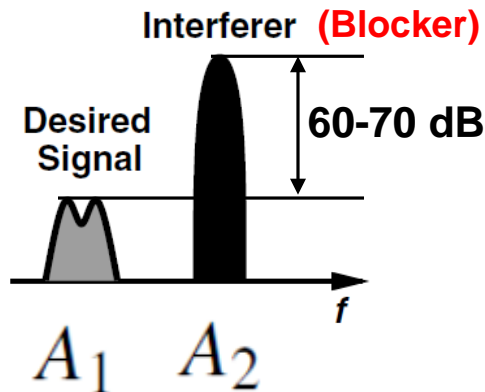
$$y(t) = \left(\alpha_1 + \frac{3}{4} \alpha_3 A_1^2 + \frac{3}{2} \alpha_3 A_2^2 \right) A_1 \cos \omega_1 t + \dots$$
$$\approx \left(\alpha_1 + \frac{3}{2} \alpha_3 A_2^2 \right) A_1 \cos \omega_1 t + \dots$$





Intermodulation


$$y(t) \approx \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

$$x(t) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$$

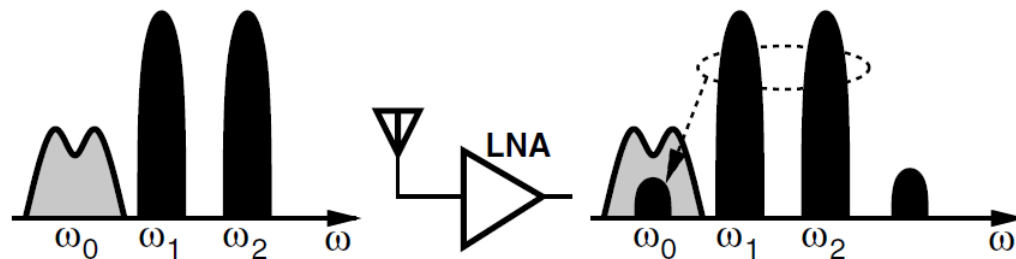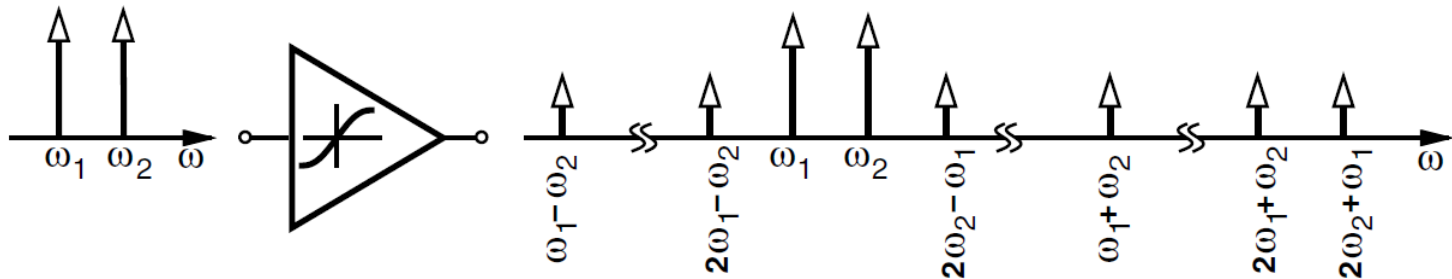
$$y(t) = \alpha_1 (A_1 \cos \omega_1 t + A_2 \cos \omega_2 t) + \alpha_2 (A_1 \cos \omega_1 t + A_2 \cos \omega_2 t)^2 + \alpha_3 (A_1 \cos \omega_1 t + A_2 \cos \omega_2 t)^3$$



Two-tone vs. Single-tone test

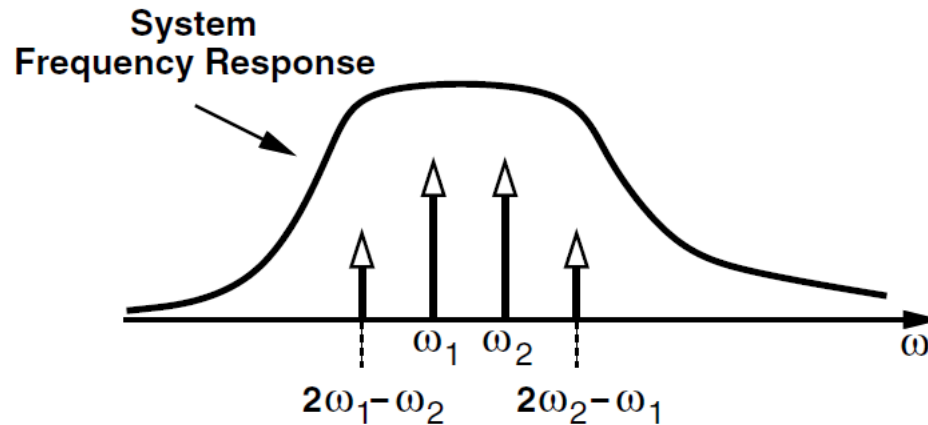


(a)

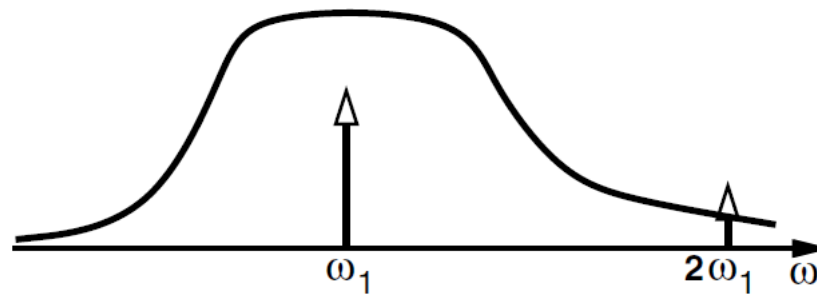



(b)

IP3 (Third Intercept Point)

$$\begin{aligned}y(t) &= \alpha_1 A \cos \omega t + \alpha_2 A^2 \cos^2 \omega t + \alpha_3 A^3 \cos^3 \omega t \\&= \alpha_1 A \cos \omega t + \frac{\alpha_2 A^2}{2} (1 + \cos 2\omega t) + \frac{\alpha_3 A^3}{4} (3 \cos \omega t + \cos 3\omega t) \\&= \frac{\alpha_2 A^2}{2} + \left(\alpha_1 A + \frac{3\alpha_3 A^3}{4} \right) \cos \omega t + \frac{\alpha_2 A^2}{2} \cos 2\omega t + \frac{\alpha_3 A^3}{4} \cos 3\omega t\end{aligned}$$

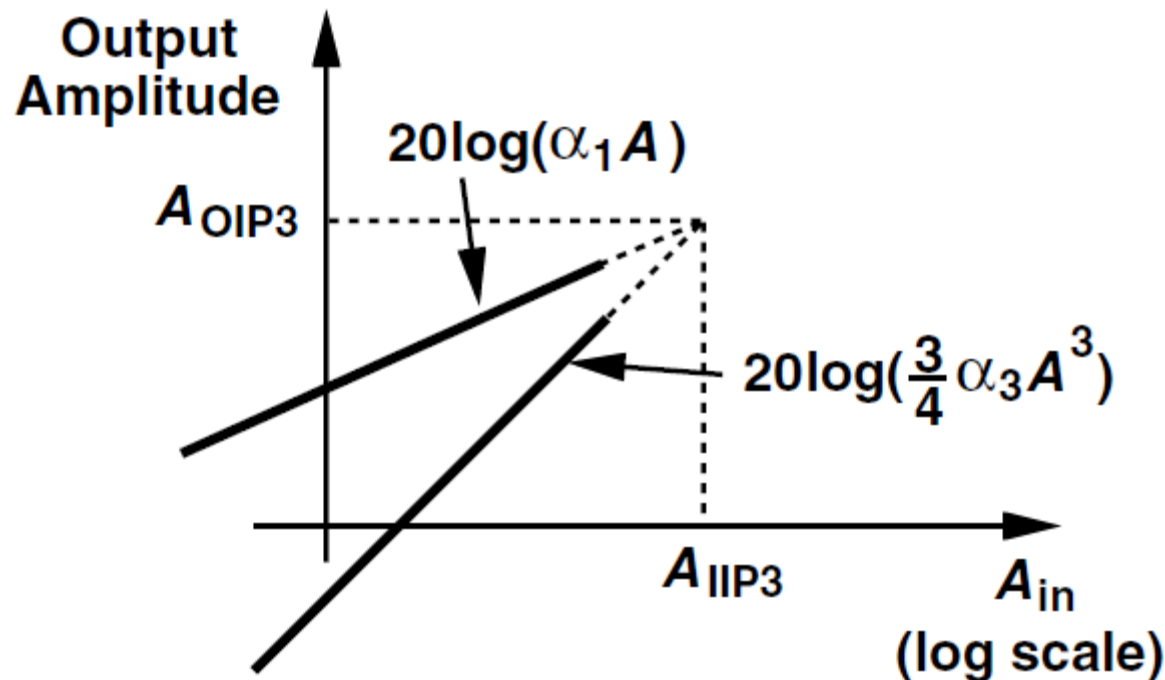



IP3

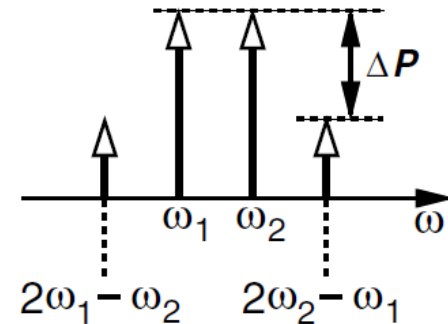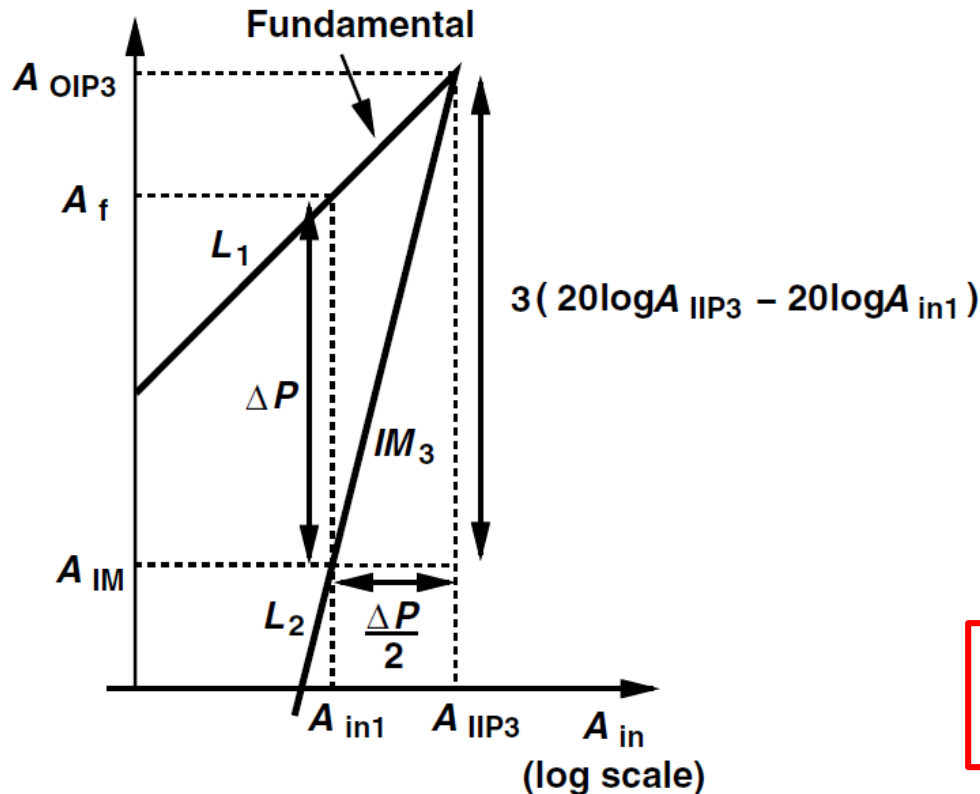


$$IIP3|_{dBm} = \frac{\Delta P|_{dB}}{2} + P_{in}|_{dBm}$$

For a given input level (well below $P1dB$), the IIP3 can be calculated by halving the difference between the output fundamental and IM levels and adding the result to the input level, where all values are expressed as logarithmic quantities.

Parallel RLC

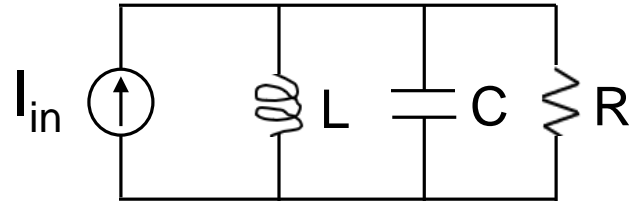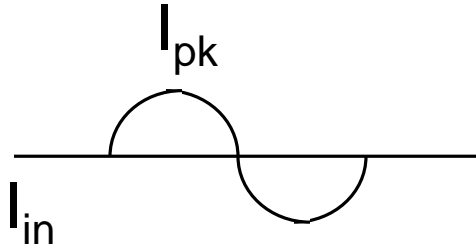


Low Frequency

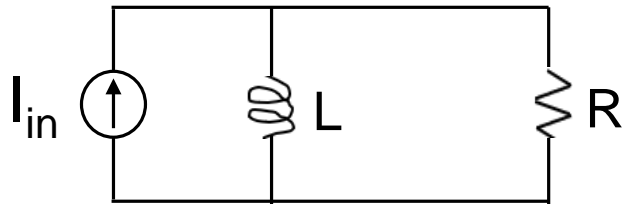


Inductive

High Frequency

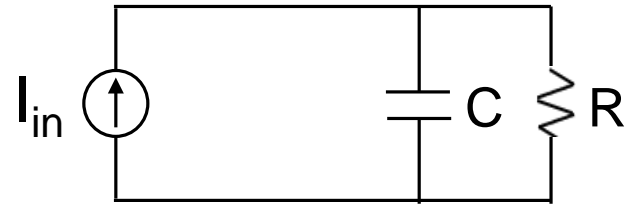

Capacitive

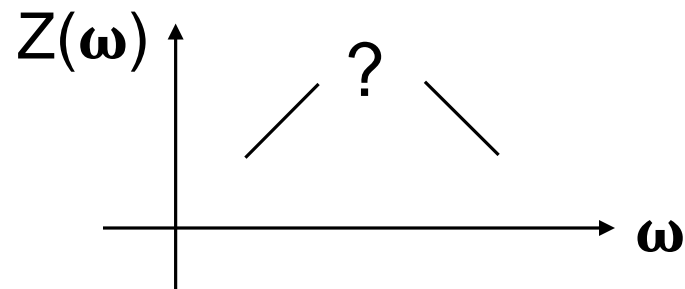


Admittance

$$Y(\omega) = \frac{1}{R} + j\omega C + \frac{1}{j\omega L} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$


$$\text{At resonance,} \quad \omega_0 C = \frac{1}{\omega_0 L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
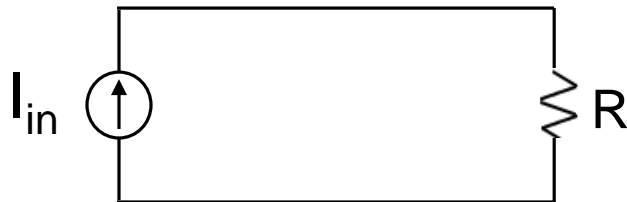
$$Y(\omega_0) = \frac{1}{R} \longrightarrow \text{Purely resistive}$$



Quality Factor

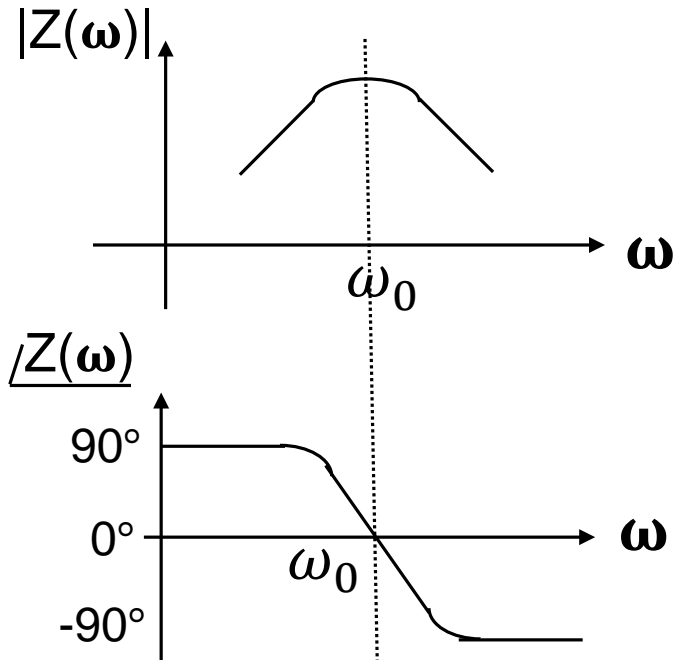


Convenient on-chip value
 $1\text{pF} \parallel 1\text{nH} \approx 5\text{ GHz}$

Quality Factor

$$Q \equiv \omega_0 \cdot \frac{\text{Energy Stored}}{\text{Avg Power Dissipated}}$$
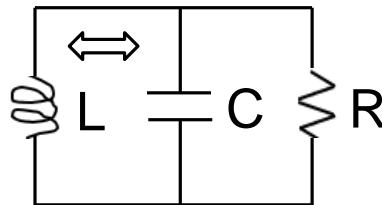
$$\text{At } \omega = \omega_0, \quad V_{out} = I_{in} \cdot R$$



Stored energy moves
back and forth
Between L and C

Quality Factor

$$V_{outpk} = I_{pk} \cdot R \quad \Longrightarrow \quad E_{tot.} = \frac{1}{2} C (I_{pk} \cdot R)^2$$

$$P_{ave} = (I_{rms})^2 \cdot R = \left(\frac{I_{pk}}{\sqrt{2}} \right)^2 \cdot R = \frac{1}{2} I_{pk}^2 \cdot R$$

$$Q \equiv \omega_0 \cdot \frac{E_{tot}}{P_{avg}} = \frac{1}{\sqrt{LC}} \cdot \frac{\frac{1}{2} C (I_{pk} \cdot R)^2}{\frac{1}{2} I_{pk}^2 \cdot R} = \frac{CR}{\sqrt{LC}} = \frac{R}{\sqrt{L/C}}$$

Check: If $R \rightarrow \infty$, $Q \rightarrow \infty$

$\sqrt{\frac{L}{C}}$ = Characteristic Impedance of network

At Resonance


$$|Z_L| = \omega_0 L = \frac{L}{\sqrt{LC}} = \sqrt{\frac{L}{C}}$$

$$|Z_C| = \frac{1}{\omega_0 C} = \frac{\sqrt{LC}}{C} = \sqrt{\frac{L}{C}}$$

Q for Parallel RLC

$$Q = \frac{R}{|Z_L|} = \frac{R}{\omega_0 L}$$

$$Q = \frac{R}{|Z_C|} = \omega_0 RC$$

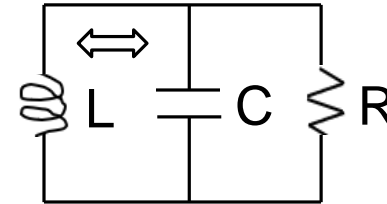


*Beware of
branch current at resonance*

$$|I_L| = |I_C| = \frac{|V_{out}|}{\omega_0 L} = \frac{|I_{in}|R}{\omega_0 L} = Q \cdot |I_{in}|$$

- Very large current can flow through L&C at resonance!
- Careful layout is necessary


BW & Q relationship

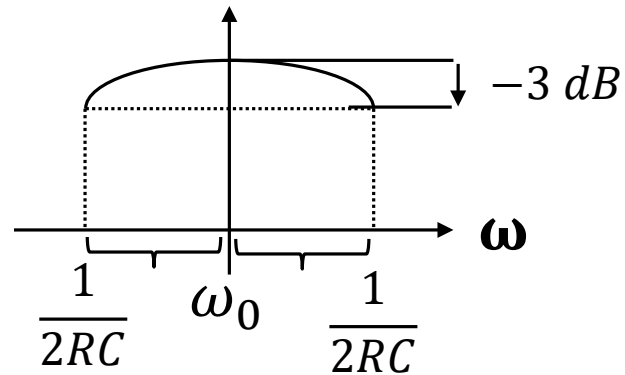


$$\text{Total BW} = \frac{1}{RC}$$

$$\frac{\omega_0}{\text{BW}} = \frac{RC}{\sqrt{LC}} = \frac{R}{\sqrt{L/C}} = Q$$

Series RLC

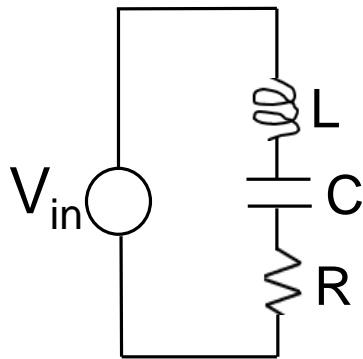


Low Frequency

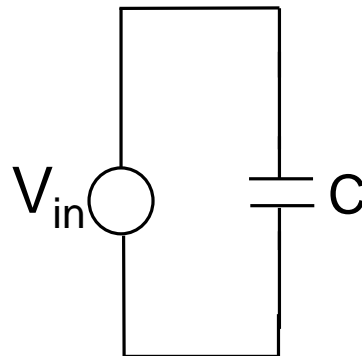

Capacitive

High Frequency

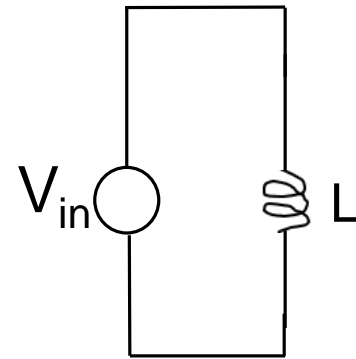


Inductive

$$Z(\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\text{At resonance, } \omega_0 L = \frac{1}{\omega_0 C} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$Z(\omega_0) = R \longrightarrow \text{Purely resistive}$$

At Resonance

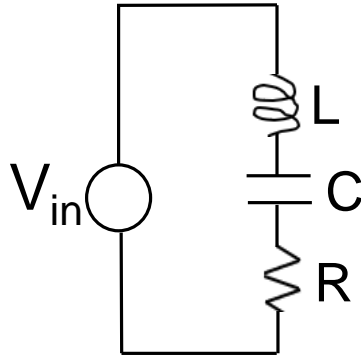

*Beware of
branch voltage at resonance*

$$|V_L| = |V_C| = Q \cdot |V_{in}|$$

- A very large voltage can be developed on L&C at resonance!
- Useful for passive voltage amplification in LNA
- Series LC is not just a short!