
EE288 Data Conversions/Analog Mixed-Signal ICs

Spring 2018

Lecture 16: DAC 2



Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

DAC Architectures

- Resistor-string DAC
- Charge-redistribution DAC
- Current-steering DAC

- Binary-weighted DAC
- Unit-element (thermometer-coded) DAC
- Segmented DAC


Binary Weighted Current Steering DAC

  


Ref: C.-H. Lin and K. Bult, "A 10-b, 500-MSample/s CMOS DAC in $0.6\mu\text{m}^2$," *IEEE Journal of Solid-State Circuits*, vol. 33, pp. 1948-1958, issue 12, 1998.

Glitches of Binary Weighted DAC

 - DAC output waveform depends on timing
 - Consider binary weighted DAC transition $0111... \rightarrow 1000...$




Output Glitches

 


- Cause: Signal and clock skew in circuits
- Especially severe at MSB transition where all bits are switching –
0111...111 →
1000...000

- Glitches cause waveform distortion, spurs and elevated noise floors
- High-speed DAC output is often followed by a de-glitching SHA

De-Glitching SHA

 


 SHA samples the output of the DAC after it settles and then hold it for T , removing the glitching energy.




SHA output must be smooth (exponential settling can be viewed as pulse shaping \rightarrow SHA BW does not have to be excessively large).

Thermometer Coded Unary DAC

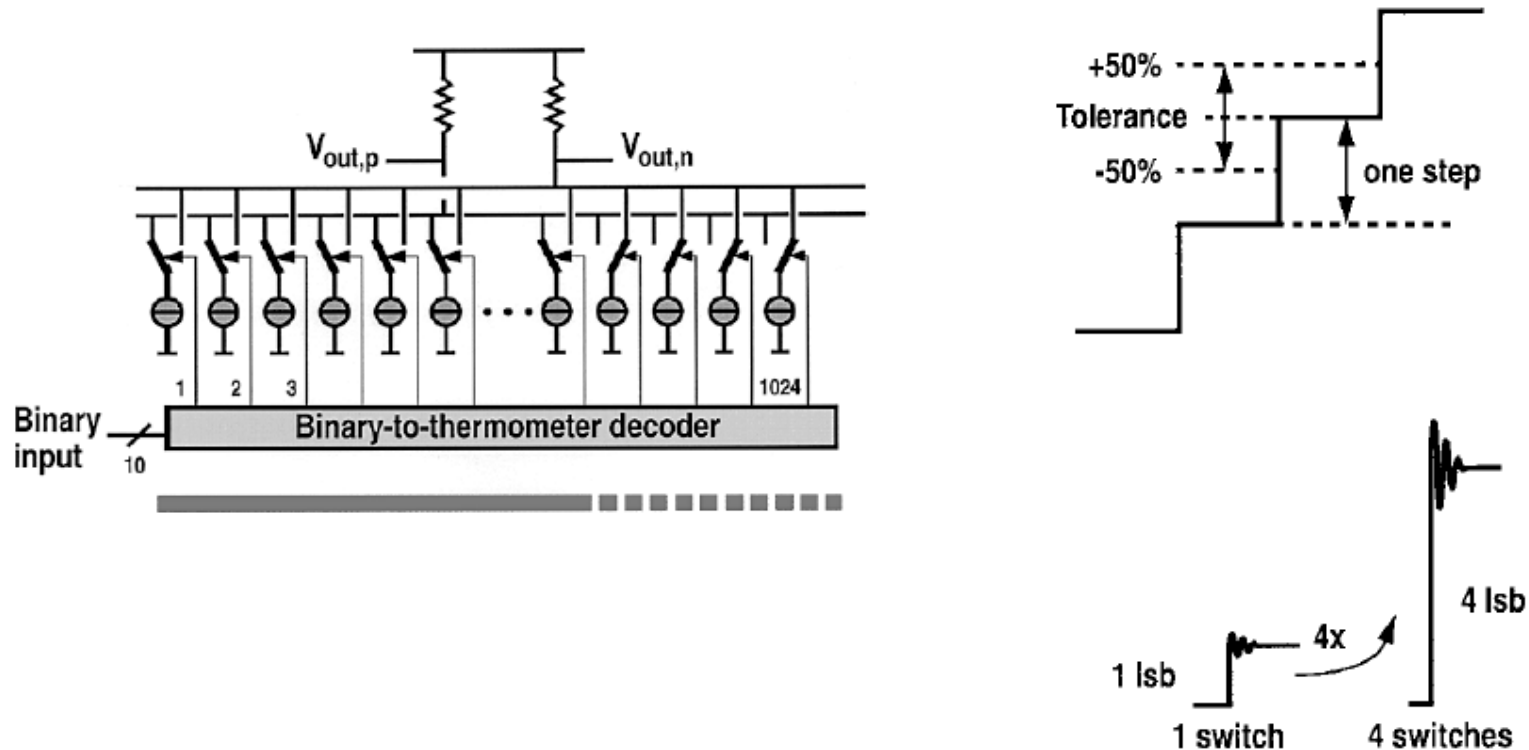


Ref: C.-H. Lin and K. Bult, "A 10-b, 500-MSample/s CMOS DAC in 0.6mm^2 ," *IEEE Journal of Solid-State Circuits*, vol. 33, pp. 1948-1958, issue 12, 1998.

Current Steering DAC

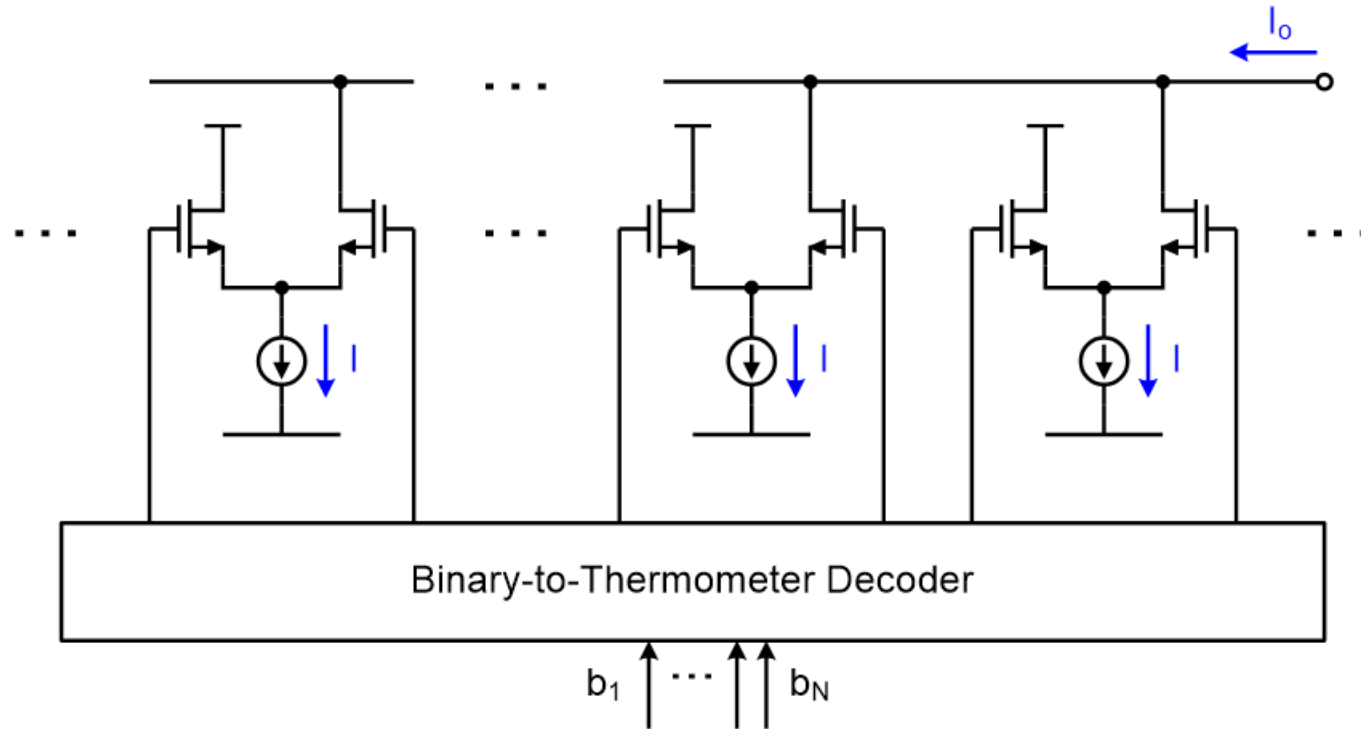


- Fast, inherently monotonic \rightarrow good DNL performance
- Complexity increases for large N , requires B2T decoder

Current Cell

 


- 2^N current cells typically decomposed into a $(2^{N/2} \times 2^{N/2})$ matrix
- Current source cascoded to improve accuracy (R_o effect)
- Coupled inverters improve synchronization of current switches


Ideal DAC Transfer Curve

 


Offset

 

Gain Error

 


DNL and INL

 

$$DNL_i = \frac{i^{th} \text{ Step Size} - \Delta}{\Delta}$$

- DNL = deviation of an output step from 1 LSB ($= \Delta = V_{FS}/2^N$)
- INL = deviation of the output from the ideal transfer curve


DNL and INL

 

$$INL_i = \sum_{j=0}^i DNL_j$$

INL = cumulative sum of DNL

Unit Element (or Unary) DAC Principle

 

DNL of Thermometer (or Unary) DAC


$$\text{DNL}(k) = \frac{\text{Step}(k) - \text{Step}_{\text{avg}}}{\text{Step}_{\text{avg}}} = \frac{I_k - \frac{1}{N} \sum_{j=1}^N I_j}{\frac{1}{N} \sum_{j=1}^N I_j} \cong \frac{I_k - I}{I} = \frac{\Delta I}{I}$$

$$\text{stdev}(\text{DNL}(k)) = \text{stdev}\left(\frac{\Delta I}{I}\right) = \sigma_u$$

Standard deviation of DNL for each code is simply equal to relative matching (σ_u) of unit elements

INL
 
$$\text{INL}(k) = \frac{l_{\text{out}}(k) - l_{\text{out,uniform}}(k)}{\text{Step}_{\text{avg}}}$$




Standard deviation of INL is maximum at mid-scale ($k=N/2$)

$$\sigma_{\text{INL}} \cong \sigma_u \sqrt{\frac{N}{2} \left(1 - \frac{N/2}{N} \right)} = \frac{1}{2} \sigma_u \sqrt{N} \cong \frac{1}{2} \sigma_u \sqrt{2^B}$$

For a more elaborate derivation of this result see
[Kuboki et al., IEEE Trans. Circuits & Systems, 6/1982]

Binary Weighted DAC Principle

 

DNL/INL of Binary Weighted DAC

INL same as for thermometer DAC


- Why?

DNL is not same for all codes, but depends on transition

Consider worst case: 0111 ... \rightarrow 1000 ...

- Turning on MSB and turning off all LSBs
 
$$\sigma_{\text{DNL}}^2 = \underbrace{(2^{B-1} - 1)\sigma_u^2}_{0111\dots} + \underbrace{(2^{B-1})\sigma_u^2}_{1000\dots} = (2^B - 1)\sigma_u^2$$



Example

- $B = 12$, $\sigma_u = 1\%$ $\rightarrow \sigma_{\text{DNL}} = 0.64$ LSB
- Much worse than thermometer DAC