



EE141-Spring 2010 Digital Integrated Circuits

Lecture 4 Switch Logic

EECS141

Lecture #4

1

Administrativa

- ❑ Assignment #1 due today!
- ❑ Assignment #2 to be posted right thereafter
- ❑ DIS 101 (Th 11am-noon) in GPB (Genetics and Plant Biology) 107 starting next week
- ❑ Office hours of TAs in 557 Cory
- ❑ Labs start next week (Monday)


EECS141

Lecture #4

2


Class Material

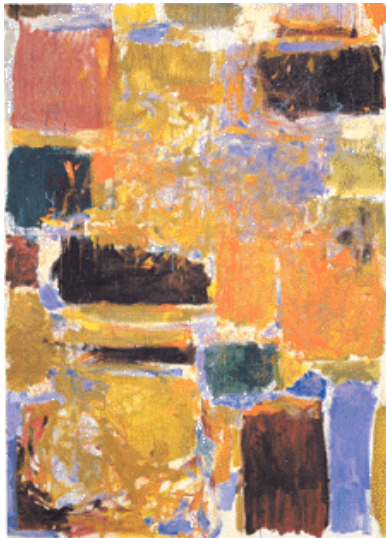- ❑ Last lecture
 - Basic metrics for IC design
 - Manufacturing
- ❑ Today's lecture
 - Design Rules
 - Introduction to switch logic
- ❑ Reading (2.3, 3.3.1-3.3.2)



Intermezzo: Design Rules

A Modern CMOS Process

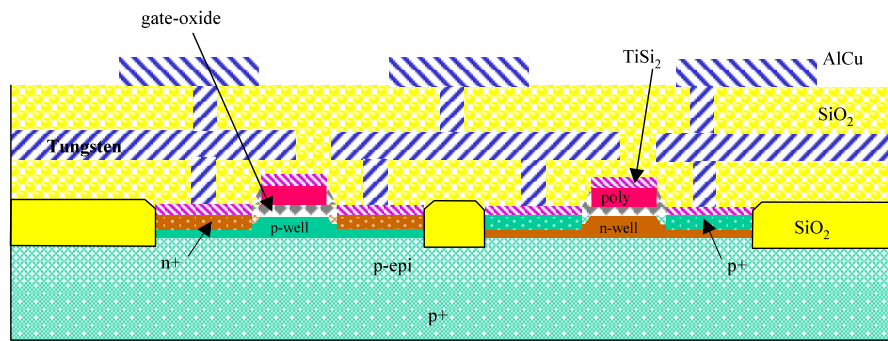

Dual-Well Shallow-Trench-Isolated CMOS Process


EECS141

Lecture #4


5

Transistor Layout

Cross-Sectional View

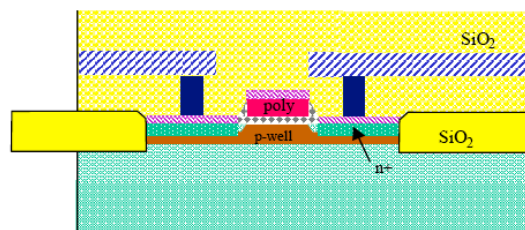

Layout View

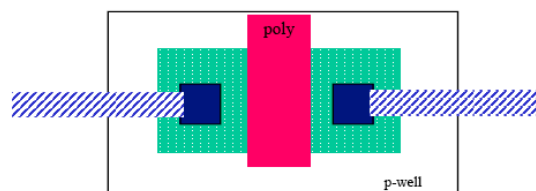



 






EECS141

Lecture #4

6

CMOS Process Layers




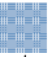














Layer	Color	Representation
Well (p,n)	Yellow	
Active Area (n+,p+)	Green	
Well contact (p+,n+)	Green	
Polysilicon	Red	
Metal1	Blue	
Metal2	Magenta	
Contact To Poly	Black	
Contact To Diffusion	Black	
Via	Black	

EECS141

Lecture #4

7

Layers in 0.25 μm CMOS process

Layer Description	Representation				
metal					
	m1	m2	m3	m4	m5
					
	nw				
polysilicon					
	poly				
contacts & vias					
	ct	v12,v23,v34,v45	nwc	pwc	
active area and FETs					
	ndif	pdif	nfet	pfet	
select (well contacts)					
	nplus	pplus	prb		

EECS141

Lecture #4

8

Design Rules

- ❑ Interface between designer and process engineer
- ❑ Guidelines for constructing process masks
- ❑ Unit dimension: Minimum line width
 - scalable design rules: lambda parameter
 - absolute dimensions (micron rules)

EECS141

Lecture #4

9

Design Rules


- ❑ Intra-layer
 - Widths, spacing, area
- ❑ Inter-layer
 - Enclosures, distances, extensions, overlaps
- ❑ Special rules (sub-0.25 μm)
 - Antenna rules, density rules, (area)

EECS141

Lecture #4

10

Intra-Layer Design Rules

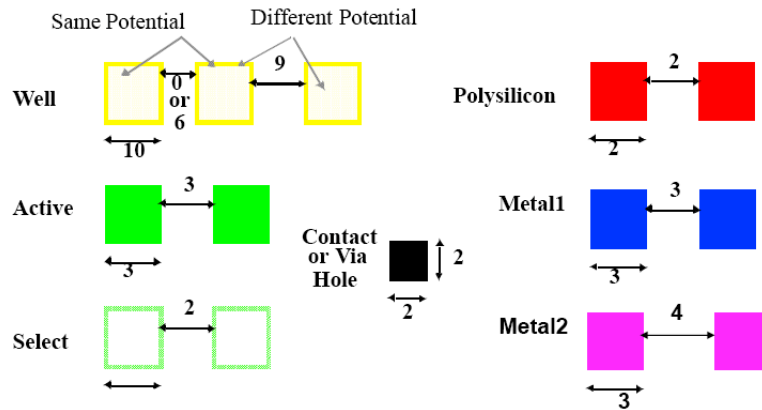


EECS141

Lecture #4

11

Inter-Layer: Transistor Layout

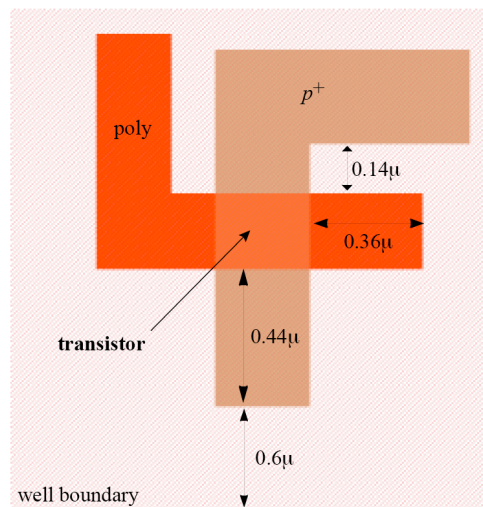


EECS141

Lecture #4

12

Inter-Layer: Vias and Contacts

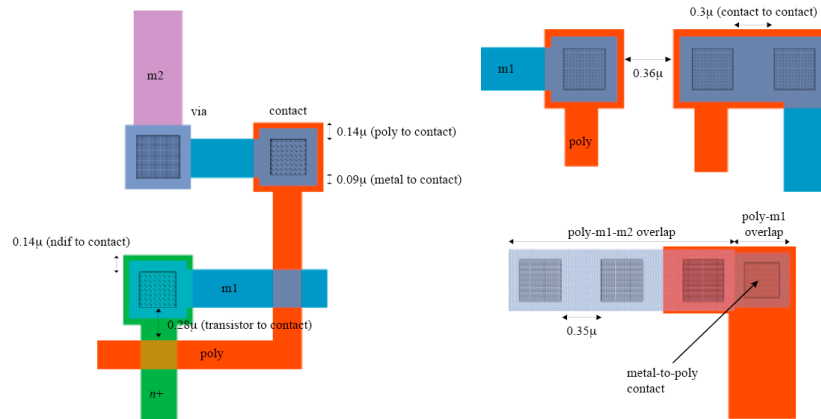


EECS141

Lecture #4

13

Inter-Layer: Well and Substrate

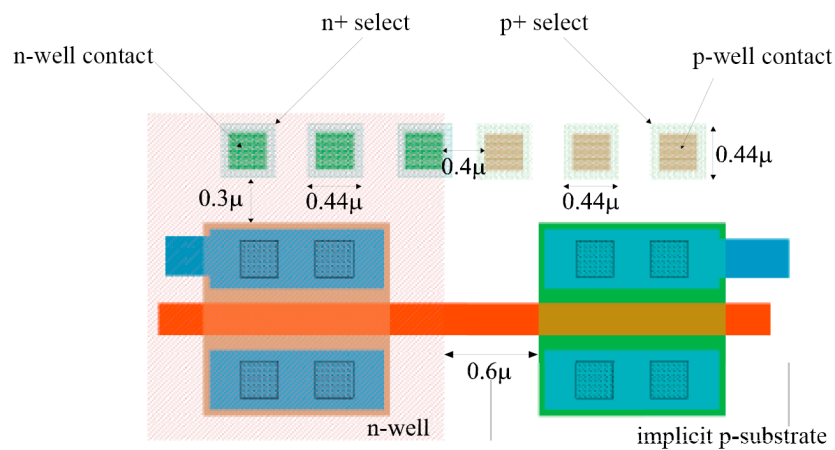


EECS141

Lecture #4

14

CMOS Inverter Layout

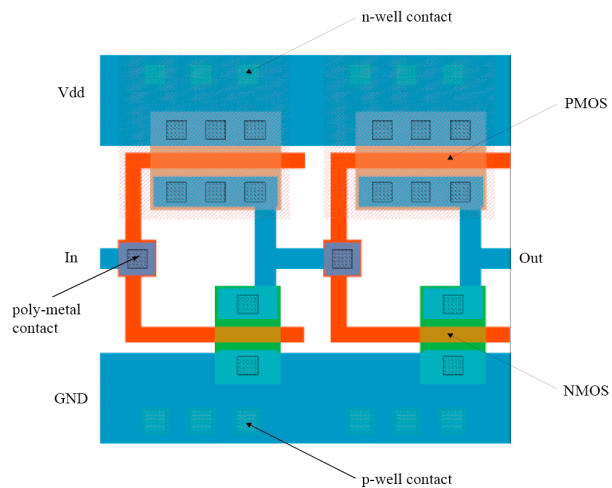


EECS141

Lecture #4

15

Layout Editor

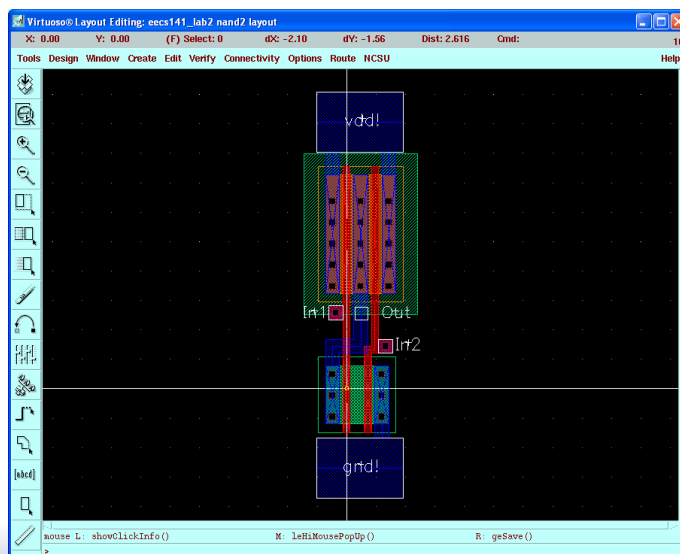


EECS141

Lecture #4

16

Design Rule Checker

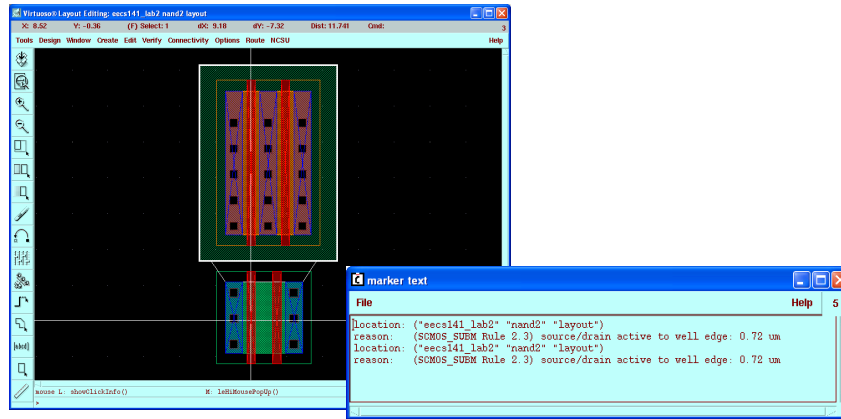


EECS141

Lecture #4

17

Sticks Diagram

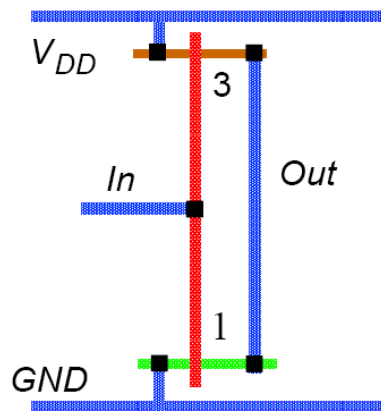

Stick diagram of inverter


- Dimensionless layout entities
- Only topology is important

EECS141

Lecture #4

18

Circuit Under Design


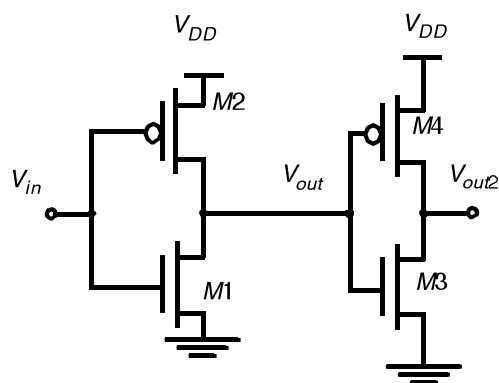


EECS141

Lecture #4

19

CMOS Inverter

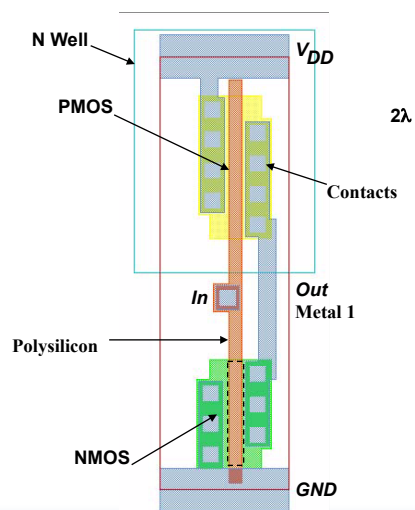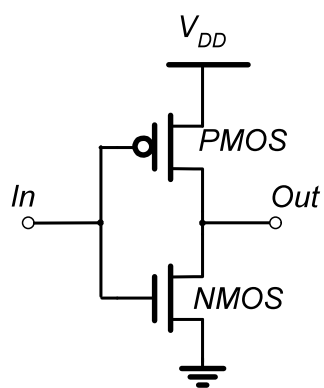


EECS141

Lecture #4

20

Two Inverters

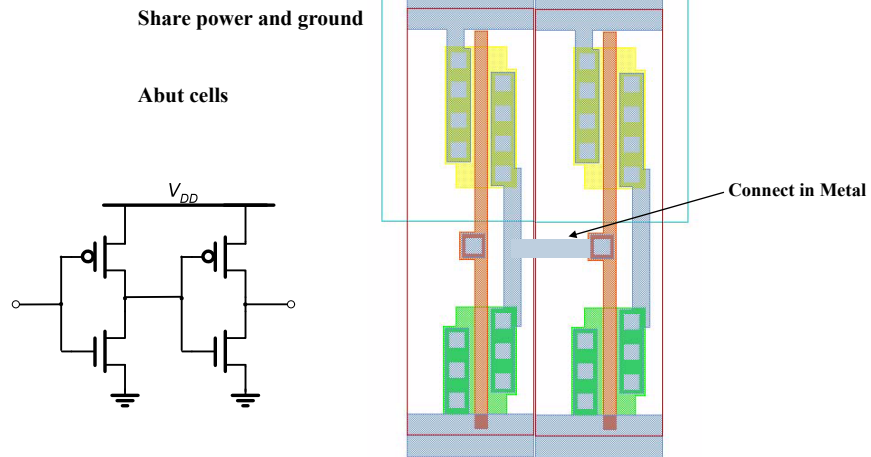

EECS141

Lecture #4

21



Switch Logic


EECS141

Lecture #4

22

What is a Transistor?

An MOS Transistor \longleftrightarrow A Switch!

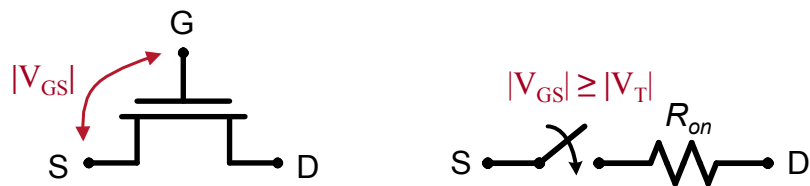


EECS141

Lecture #4

23

Switch Model of MOS Transistor

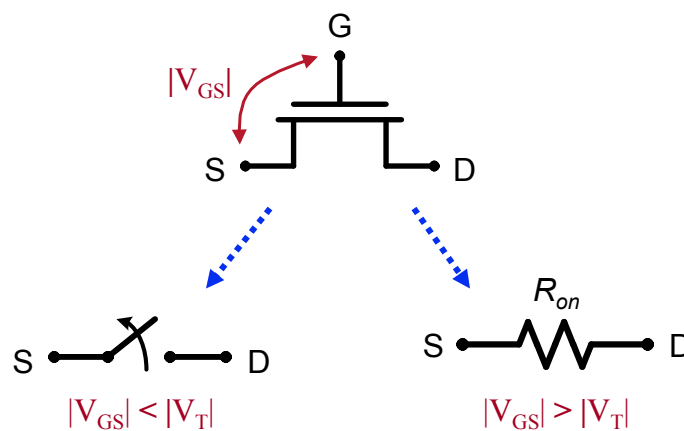


EECS141

Lecture #4

24

A Modern Sub-100 nm Look ...

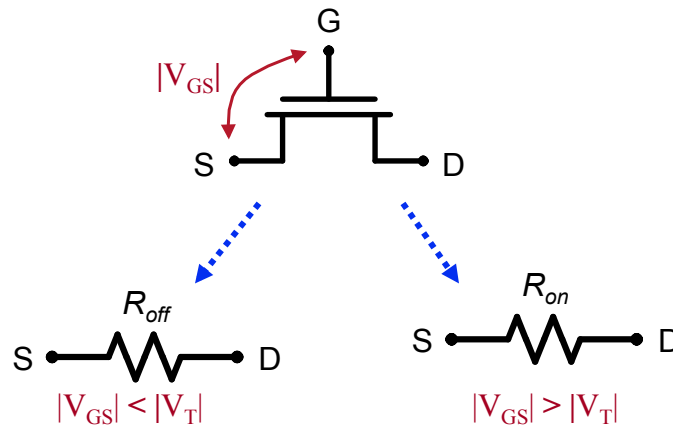


EECS141

Lecture #4


25

NMOS and PMOS

NMOS Transistor

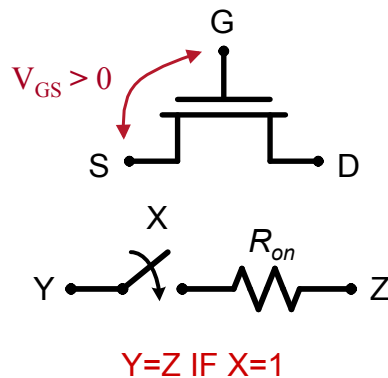

PMOS Transistor

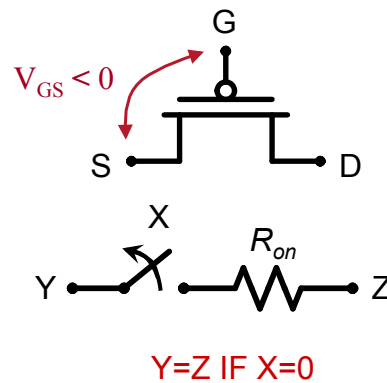

EECS141

Lecture #4

26


Building an Inverter with Switches

EECS141

Lecture #4

27

The CMOS Inverter: A First Glance

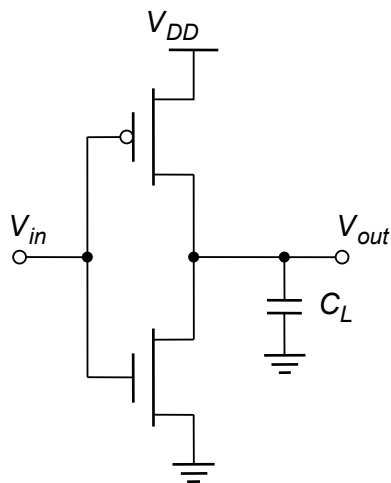


EECS141

Lecture #4

28

CMOS Inverter First-Order DC Analysis

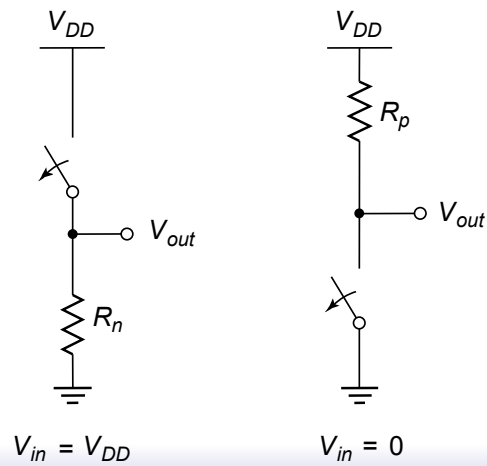


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

EECS141

Lecture #4

29

Simulated Inverter VTC (Spice)

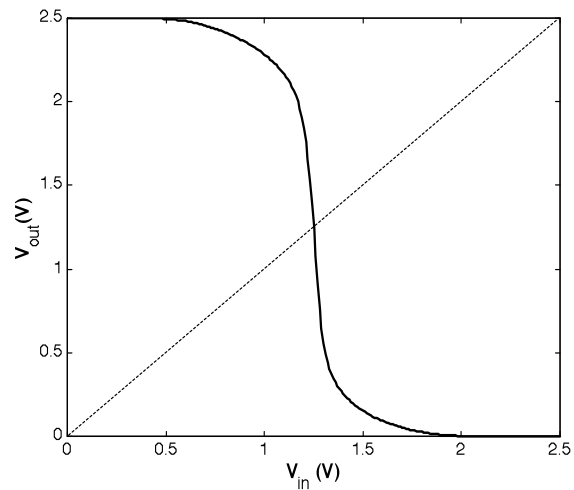

EECS141

Lecture #4

30

CMOS Inverter: DC Properties

- $V_{OH} =$
- $V_{OL} =$
- $V_{IL} =$
- $V_{IH} =$
- $N_{MH} =$
- $N_{ML} =$
- $V_M =$

EECS141

Lecture #4

31

CMOS Inverter: DC Properties


- $V_{OH} = V_{DD} = 2.5V$
- $V_{OL} = 0V$
- $V_M = 1.2V$
- $V_{IL} = 1.05V$
- $V_{IH} = 1.45V$
- $N_{MH} = 1.05V$
- $N_{ML} = 1.05V$

EECS141


Lecture #4

32

CMOS Inverter: Transient Response

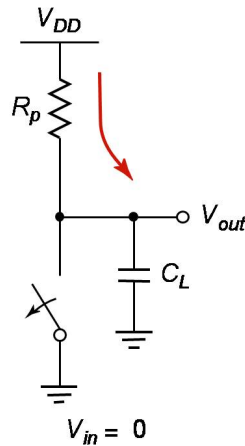

(a) Low-to-high

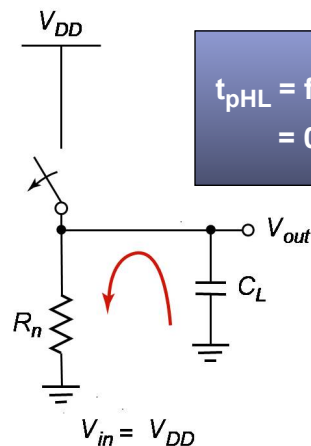

(b) High-to-low

$$t_{pHL} = f(R_{on}C_L) \\ = 0.69 R_n C_L$$

EECS141

Lecture #4

33

CMOS Properties

- ❑ Full rail-to-rail swing
- ❑ Symmetrical VTC
- ❑ Propagation delay function of load capacitance and resistance of transistors
- ❑ No static power dissipation
- ❑ Direct path current during switching

EECS141

Lecture #4

34

Impact on Reliability?

EECS141

Lecture #4

35

Impact on Performance?

EECS141

Lecture #4

36


Impact on Power/Energy

EECS141

Lecture #4

37

A Side Note: How Good a Switch is the MOS Transistor?

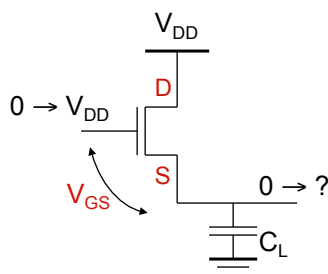


EECS141

Lecture #4

38

How Good a Switch is an MOS?

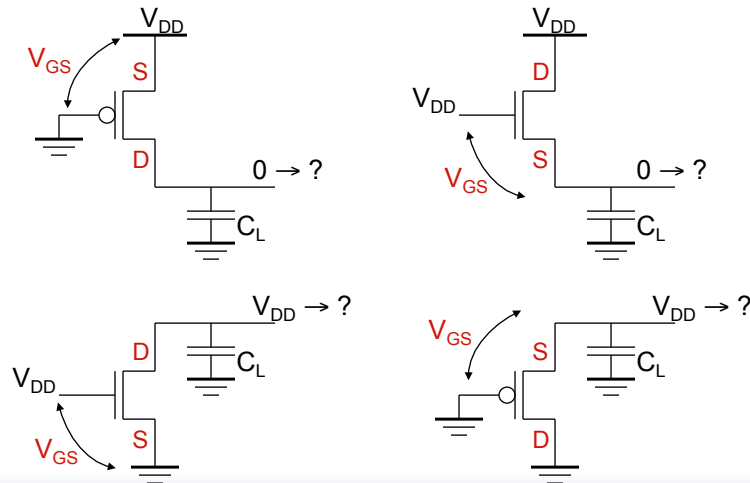


EECS141

Lecture #4

39

The Next Question: Inverter Chain

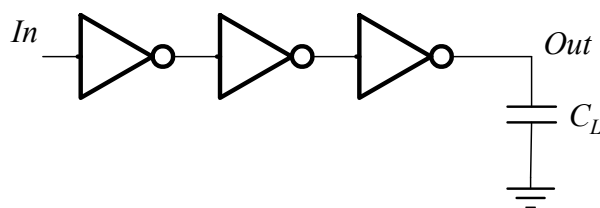

- For some given C_L :
 - How many stages are needed to minimize delay?
 - How to size the inverters?
- Anyone want to guess the solution?


EECS141

Lecture #4

40

Careful about Optimization Problems

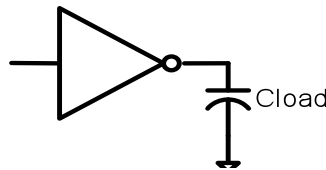- ❑ Get fastest delay if build one **very** big inverter
 - So big that delay is set only by self-loading



- ❑ Likely not the problem you're interested in
 - Someone has to drive this inverter...

Engineering Optimization Problems in General

- ❑ Need to have a set of constraints
- ❑ Constraints key to:
 - Making the result useful
 - Making the problem have a 'clean' solution
- ❑ For sizing problem:
 - Need to constrain size of first inverter

Delay Optimization Problem #1

- You are given:
 - A fixed number of inverters
 - The size of the first inverter
 - The size of the load that needs to be driven
- Your goal:
 - Minimize the delay of the inverter chain
- Need model for inverter delay vs. size

EECS141

Lecture #4

43


Inverter Delay

Delay: $t_{pHL} = (\ln 2) R_N C_L$ $t_{pLH} = (\ln 2) R_P C_L$

- Assume we want equal rise/fall delays

$$t_{pHL} = t_{pLH}$$

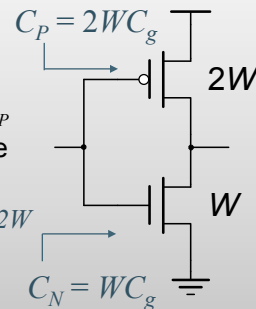- Need approximately equal resistances, $R_N = R_P$
- PMOS approximately 2 times larger resistance for same size;
- Must make PMOS 2 times wider, $W_P = 2W_N = 2W$
- $t_p = (\ln 2) (R_{inv}/W) C_L$ with R_{inv} resistance of minimum size NMOS




Loading on the previous stage: $C_{in} = WC_{ginv} = W(3C_G)$

EECS141

Lecture #4

44

Inverter Delay Model

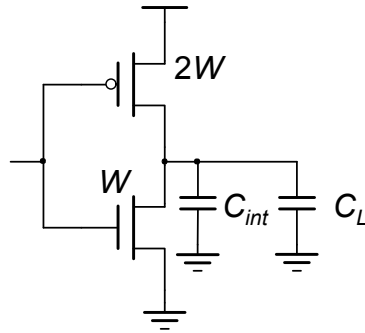

$$R = R_{inv}/W$$

$$C_{int} = W(3C_d) = WC_{dinv}$$

Replace $\ln(2)$ with k (a constant):

$$\text{Delay} = kR(C_{int} + C_L)$$



$$\text{Delay} = k(R_{min}/W)(WC_{dinv} + C_L)$$

EECS141

Lecture #4

45

Inverter with Load

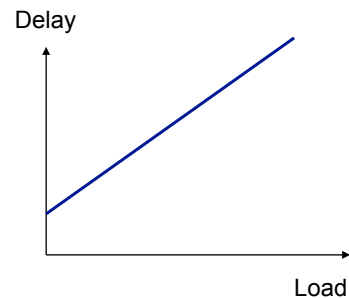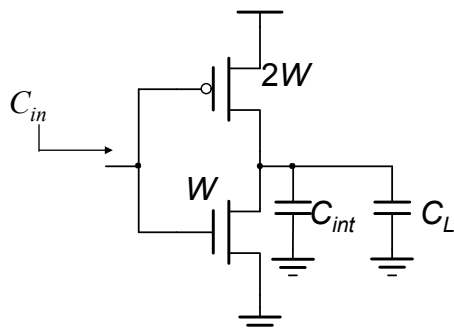

$$\begin{aligned} \text{Delay} &= kR C_{in}(C_{int}/C_{in} + C_L/C_{in}) \\ &= kR_{min} C_{ginv} [C_{dinv}/C_{ginv} + C_L/(WC_{ginv})] \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$

$$C_{dinv}/C_{ginv} = \gamma = \text{Constant independent of size}$$

EECS141

Lecture #4

46

Delay Formula

$$\text{Delay} \sim R_W (C_{int} + C_L)$$

$$t_p = kR_W C_{in} (C_{int}/C_{in} + C_L / C_{in}) = t_{inv} (\gamma + f)$$

$$C_{int} = \gamma C_{in} (\gamma \approx 1 \text{ for CMOS inverter})$$

$$f = C_L / C_{in} - \text{electrical fanout}$$

$$t_{inv} = kR_{min} C_{ginv}$$

t_{inv} is independent of sizing of the gate!!!