

---

# EE223 Analog Integrated Circuits

## Fall 2018

### Project Description

Updated on Oct. 29, 2018


Sang-Soo Lee  
Electrical Engineering Department  
San Jose State University  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)

# Project Logistics

---

1. A group of 3 students
2. Less number of students per group is fine
3. One Project Report per group
4. Report should be in IEEE conference paper format
5. Project Report due : 5 PM, Dec 10

# Project Description

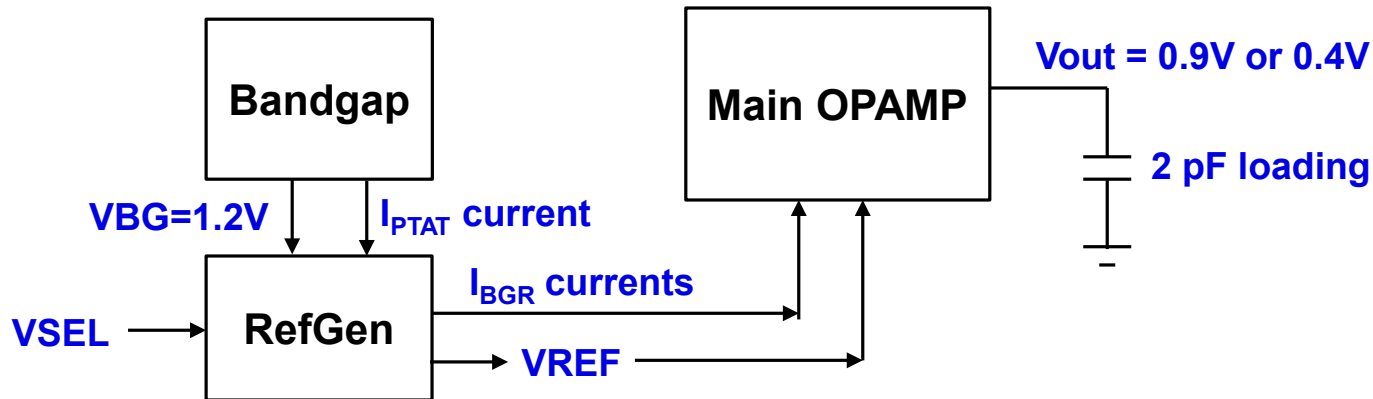


**VSEL pulse is used to create either  $V_{REF} = 0.9V$  or  $0.4V$ .  
See page 6 for the circuit diagram to implement this.**

## Main Circuit – High Gain OPAMP

## Auxiliary Circuits – Bandgap, RefGen

- $V_{DD}=1.8V$
- Device types available for the design
  - nmos2v, pmos2v, nmos2v\_nat, vnp5, resnsppoly, Ideal cap
- Results should meet the requirement over the following PVT corners
  - TT, 1.8V, 27C
  - SS, FF
  - 1.7V, 1.9V
  - -40C, 125C

# Bandgap

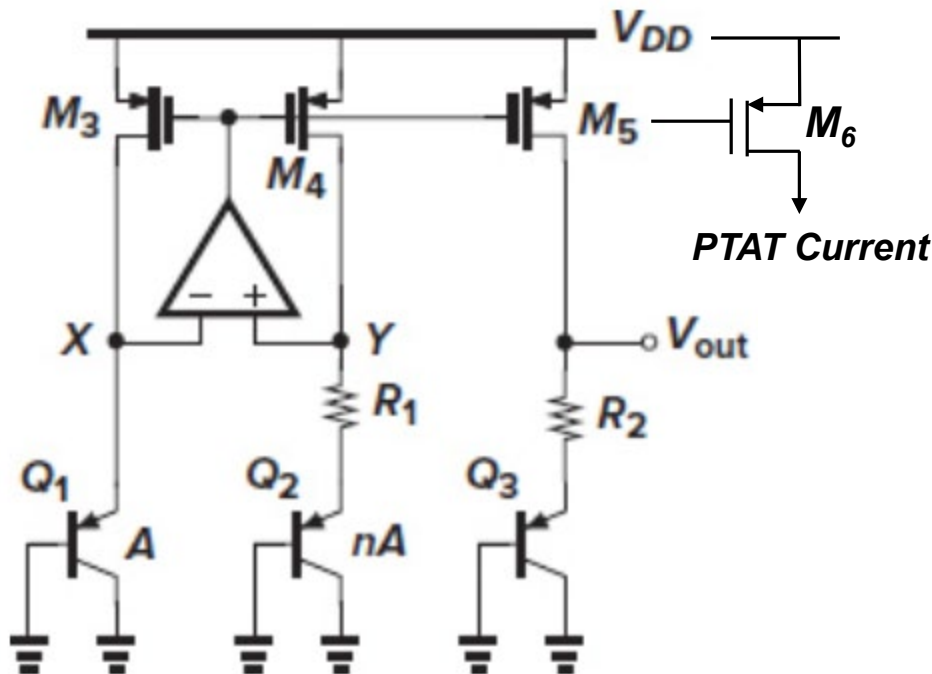

Use PMOS diff pair input  
for the Folded-cascode amplifier

## Key Spec

Vout should be 1.2V.

Vout variation less than  $\pm 1\%$  over PVT

PTAT current is nominally 25uA

## Design Procedure

Q1=1, Q2=8, Q3=3

Choose R1 to get the current around  $I=4\sim 5\mu A$

Then choose R2 to get around  $V_{out}=1.2V$


The OPAMP will force the node X and Y to be the same for the matching between M3 and M4.

M3, M4, M5 are generally sized to be the same to carry the same current.


Final Vout, the bandgap voltage output, should be around 1.2V.

Choose R2 to compensate temperature variation of the bandgap voltage.
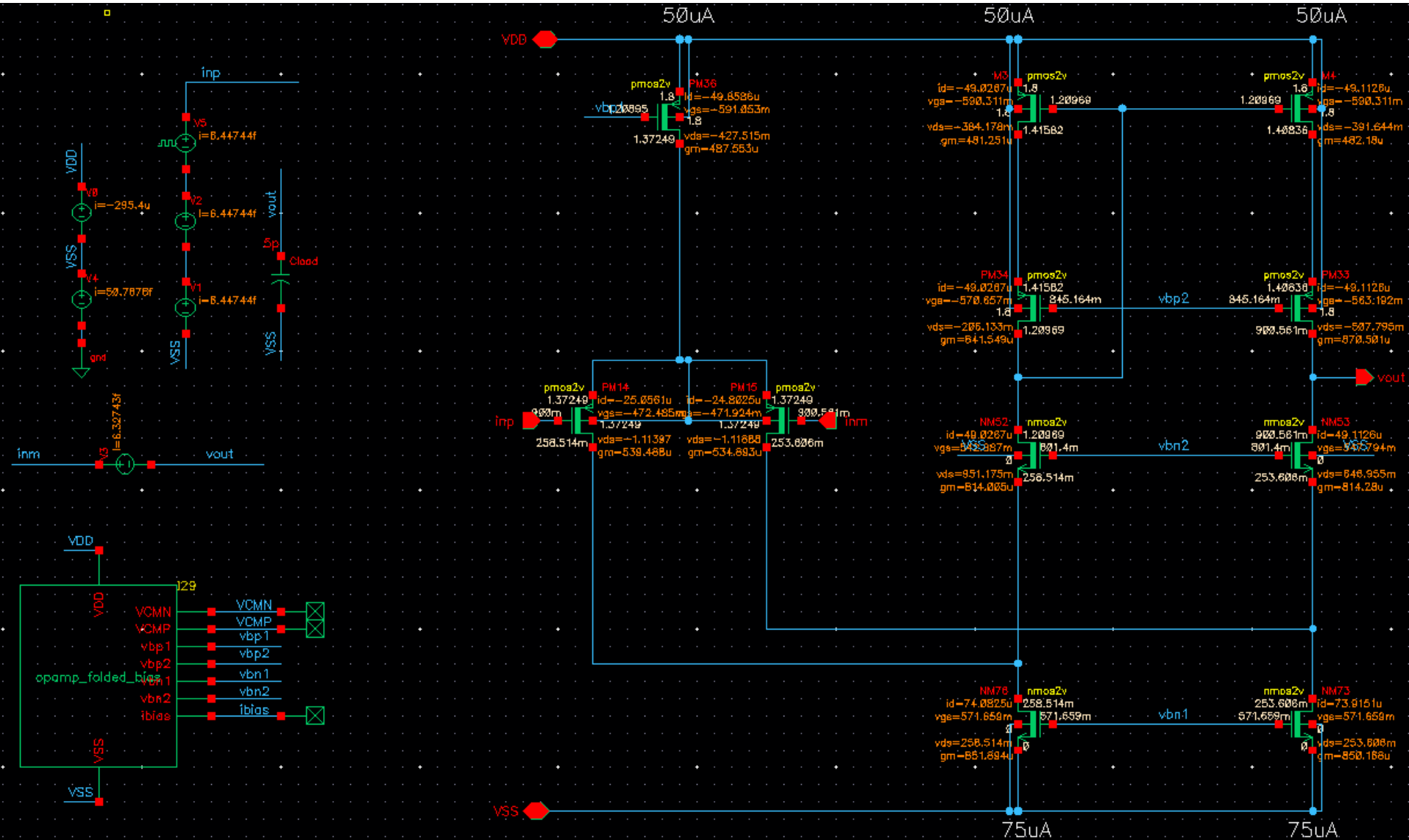
# Example Folded-Cascode Amplifier Circuit



# Reference Generator

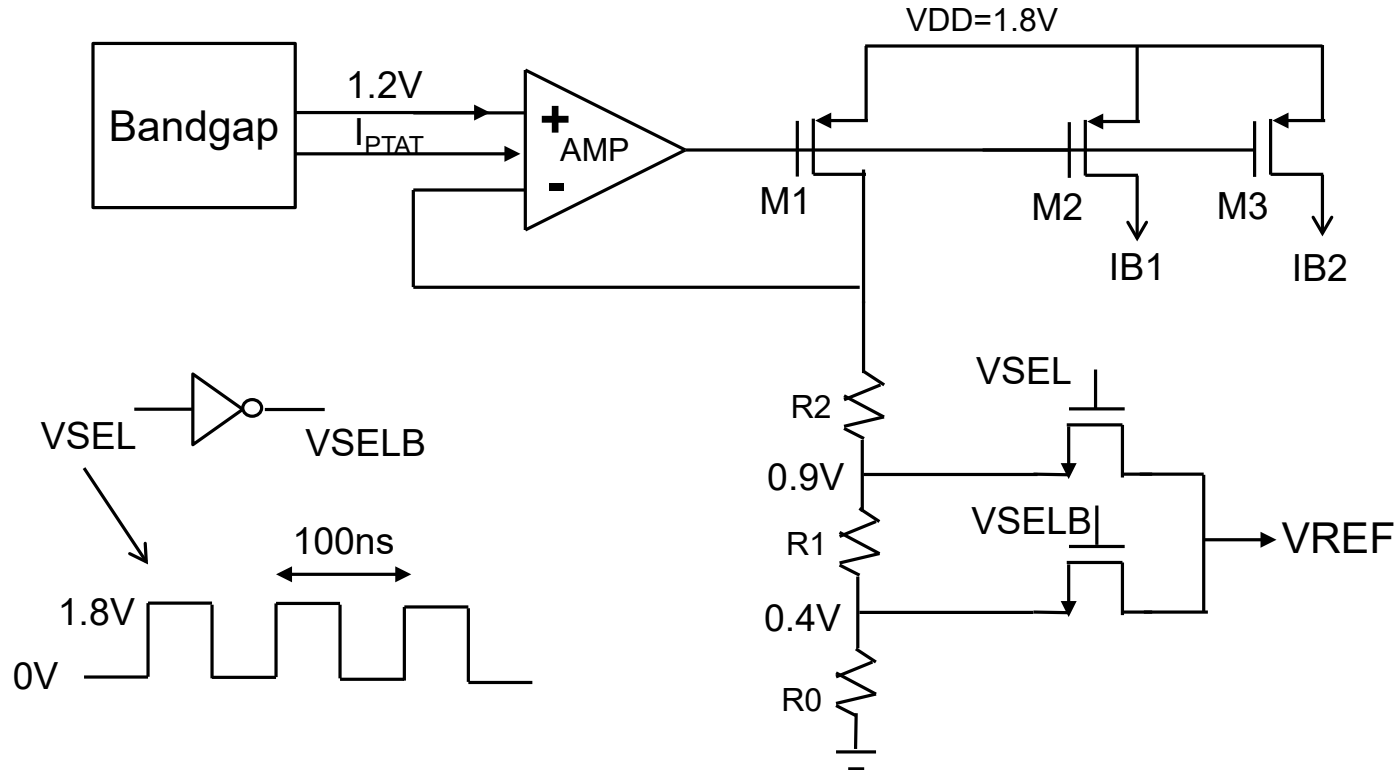

## Design Points


1. AMP and M1 will constitute a 2-stage RC compensated OPAMP.
2. AMP needs to be stable in unity gain configuration.
3.  $V_{REF}$  is the input voltage to the main OPAMP.
4.  $V_{SEL}$  is the input pulse you have to apply to measure the output of the main OPAMP.
5.  $I_{B1}$  and  $I_{B2}$  will supply the currents required in the Main Amplifier.

# Main OPAMP Spec

Parameter	Typical Result	PVT Result
DC Gain	80 dB	> 70 dB
Unity Gain Frequency	30 MHz	> 25 MHz
Phase Margin	60 Degree	> 55 Degree
Gain Margin	12 dB	> 9 dB
Slew Rate	15 V/us	> 10 V/us
Power	1.5 mW	< 2 mW

- Loading cap = 2 pF
- For Transient simulation, apply 10MHz input pulse at VSEL and run for 400 ns.

# Example Main OPAMP

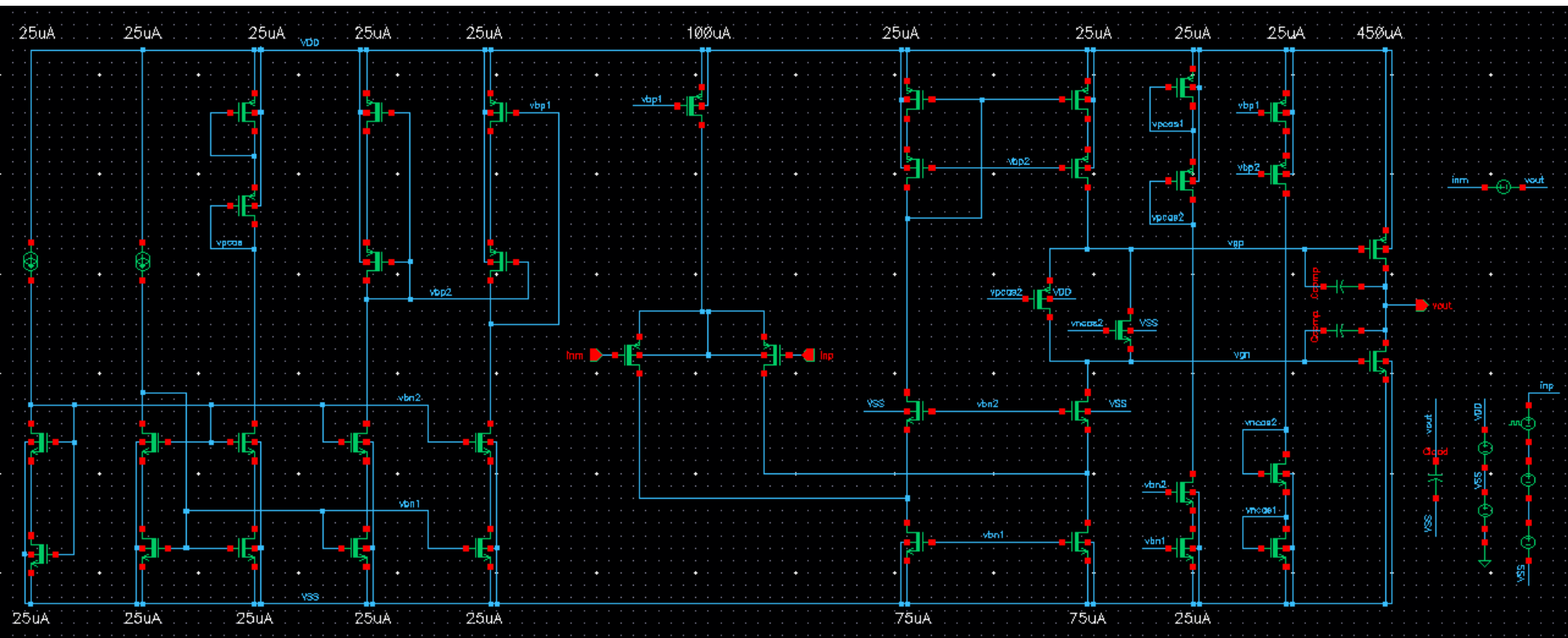



# ADE Test Editor for Main OPAMP

ADE XL Test Editor - ee223Fall17:project\_classAB\_tb:1

Session Setup Analyses Variables Outputs Simulation

cadence

27.0

Design Variables

	Name	Value
1	fin	5M
2	td	10n
3	tr	1n
4	Ccomp	1.2p
5	Cload	5p
6	VCM	400m
7	vstep	500m
8	VDD18	1.8

Analyses

	Type	Enable	Arguments
1	dc	<input checked="" type="checkbox"/>	t
2	ac	<input type="checkbox"/>	10 1G Automatic Start-Stop
3	stb	<input checked="" type="checkbox"/>	1 1G /V3 Automatic Start-Stop
4	tran	<input checked="" type="checkbox"/>	0 400n conservative

Outputs

	Name/Signal/Expr	Value	Plot	Save	Save Options
1	inp		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
2	vout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	deriv(v("vout" ?result "tr...		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
4	Loop Gain Phase		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
5	Loop Gain dB20		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
6	fu		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
7	DC gain		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
8	Phase Margin		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
9	fgm		<input type="checkbox"/>	<input type="checkbox"/>	
10	Gain Margin		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
11	V0/MINUS		<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	yes
12	average(IT("/V0/MINUS"))		<input checked="" type="checkbox"/>	<input type="checkbox"/>	


15(39) Edit Vari Status: Ready T=27.0 C Simulator: spectre State: ee223Fall17:project\_classAB\_tb:1\_active

# ADE output parameters of previous slide

- $f_u$ 
  - To get the unity gain frequency expression in ADE
  - Run stb analysis and plot the Loop Gain and Phase
  - In the plot window, choose Loop Gain dB20 and send it to Calculator → See next page Figure (a)
  - In Calculator, take “cross” of the Loop Gain dB20 → See next page Figure (b)
  - Send buffer expression to ADE → See next page Figure (c)
- DC gain
  - To get the DC gain in ADE
  - Send Loop Gain dB20 to Calculator
  - In Calculator, take “value” at 10 Hz of the Loop Gain 20dB → See Figure on page 12
  - Send buffer expression to ADE
- Phase Margin
  - To get Phase Margin in ADE,
  - Send Loop Gain Phase to Calculator
  - In Calculator, take “value” at  $f_u$  of the Loop Gain Phase
  - Send buffer expression to ADE
- Gain Margin
  - To get Gain Margin in ADE,
  - Send Loop Gain Phase to Calculator
  - In Calculator, take “cross” of the Loop Gain Phase
  - Send buffer expression to ADE and name it as fgm
  - Then, send Loop Gain dB20 to Calculator
  - In Calculator, take “value” at fgm of the Loop Gain 20dB
  - Send buffer expression to ADE

# ADE output parameter for fu

(a)

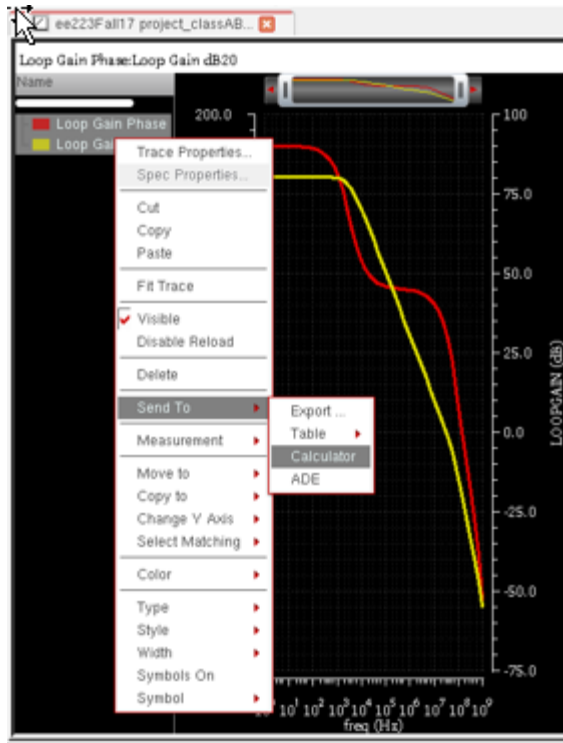

(b)

Key ...

7 8 9 /

4 5 6 \*

1 2 3 -

0 ± . +

cross db(mag(getData("loopGain" ?result "stb"))) 0 1 "either" nil nil

Function Panel

All

cross

Signal db(mag(getData("loopGain" ?result "stb")))

Threshold Value 0

Edge Number 1

OK Apply Defaults Close Help

Function Panel Stack

(c)

vt vf vdc vs op var vn sp vswr hp zm

it if ldc ls opt mp vn2 zp yp gd data


Off Family Wave Clip New Subwindow Rectangular

Key ...

cross db(mag(getData("loopGain" ?result "stb"))) 0 1 "either" nil nil


Send buffer expression to ADE L/XL Outputs.

# ADE output parameter for DC Gain

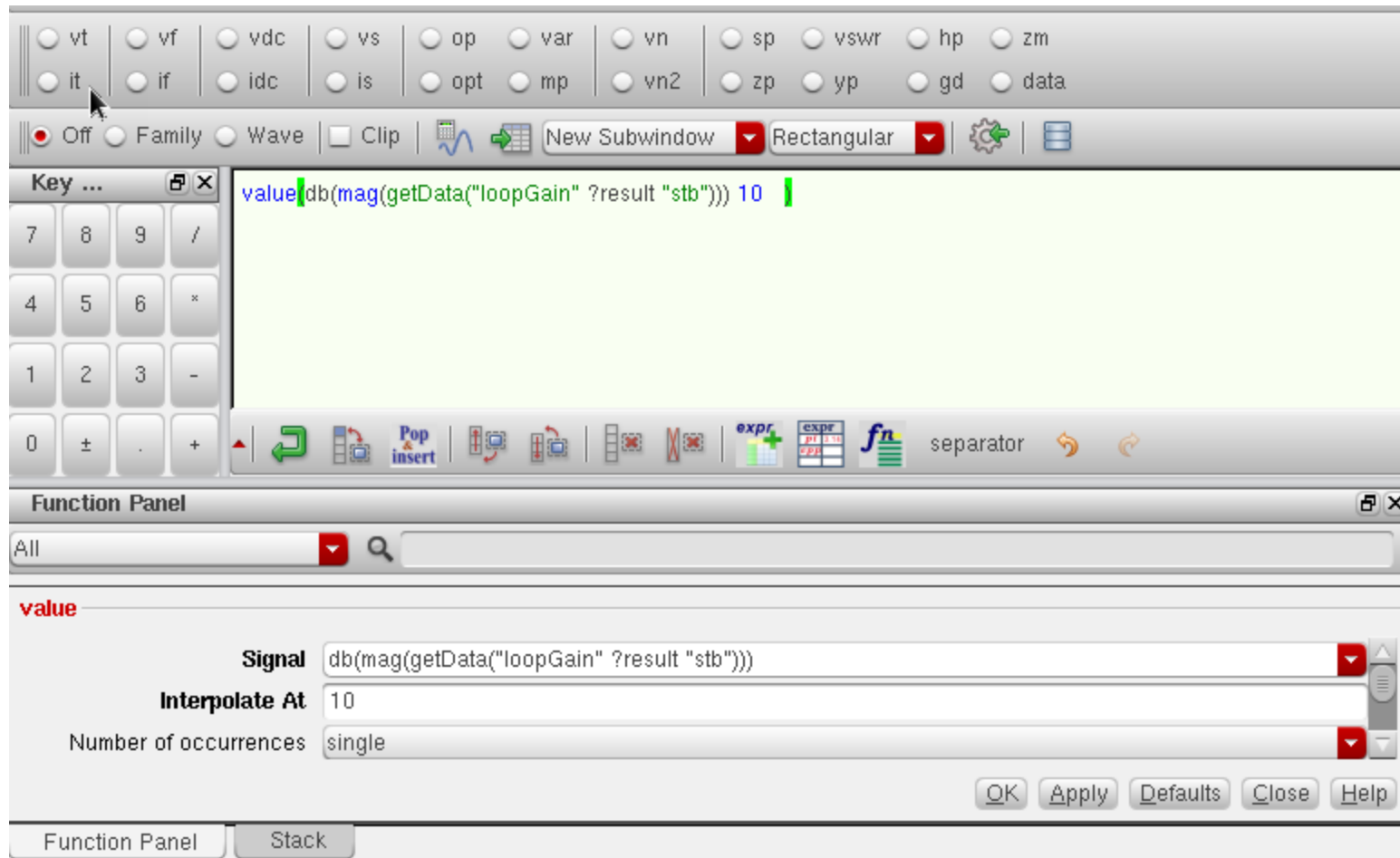

# Typical Result for Main OPAMP


stb analysis

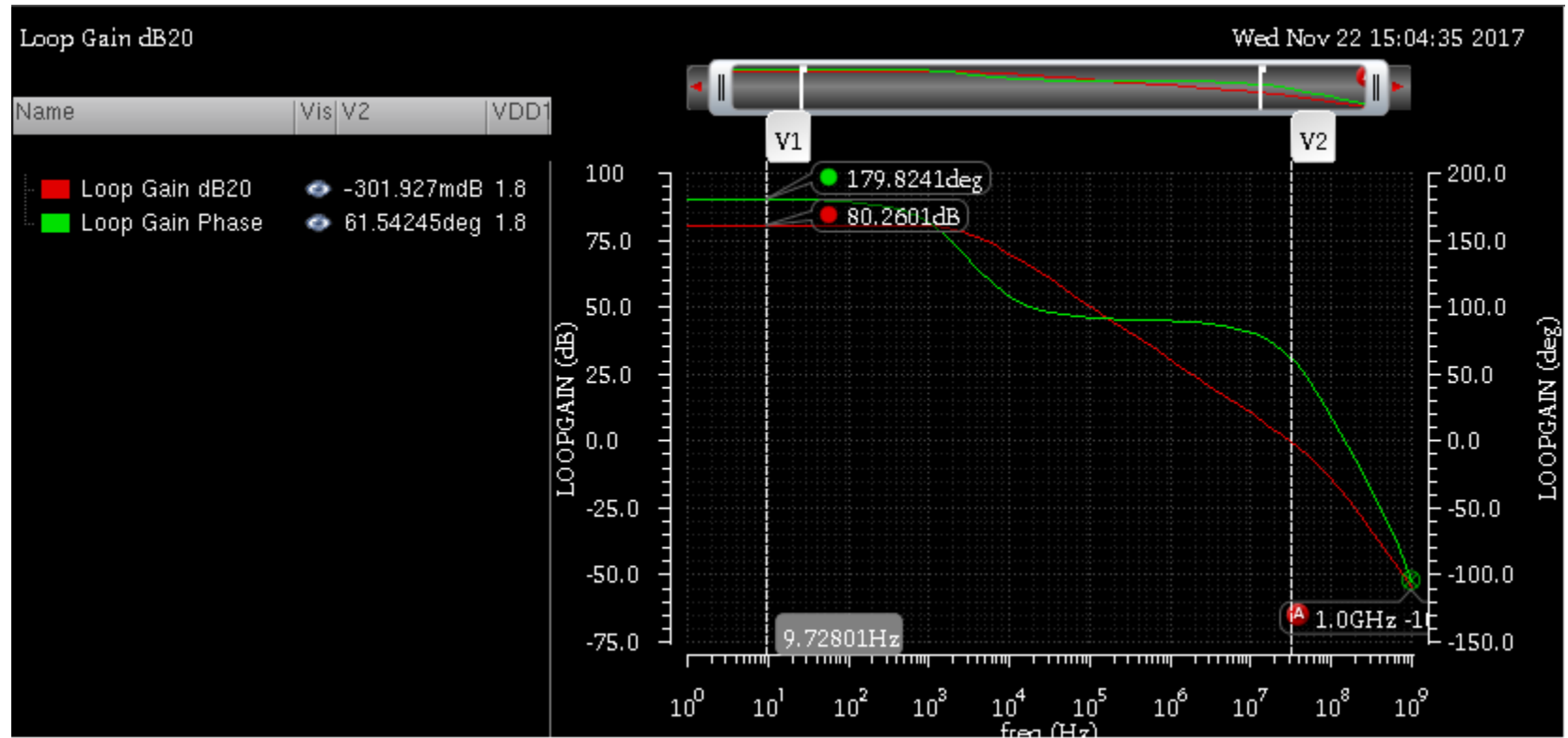
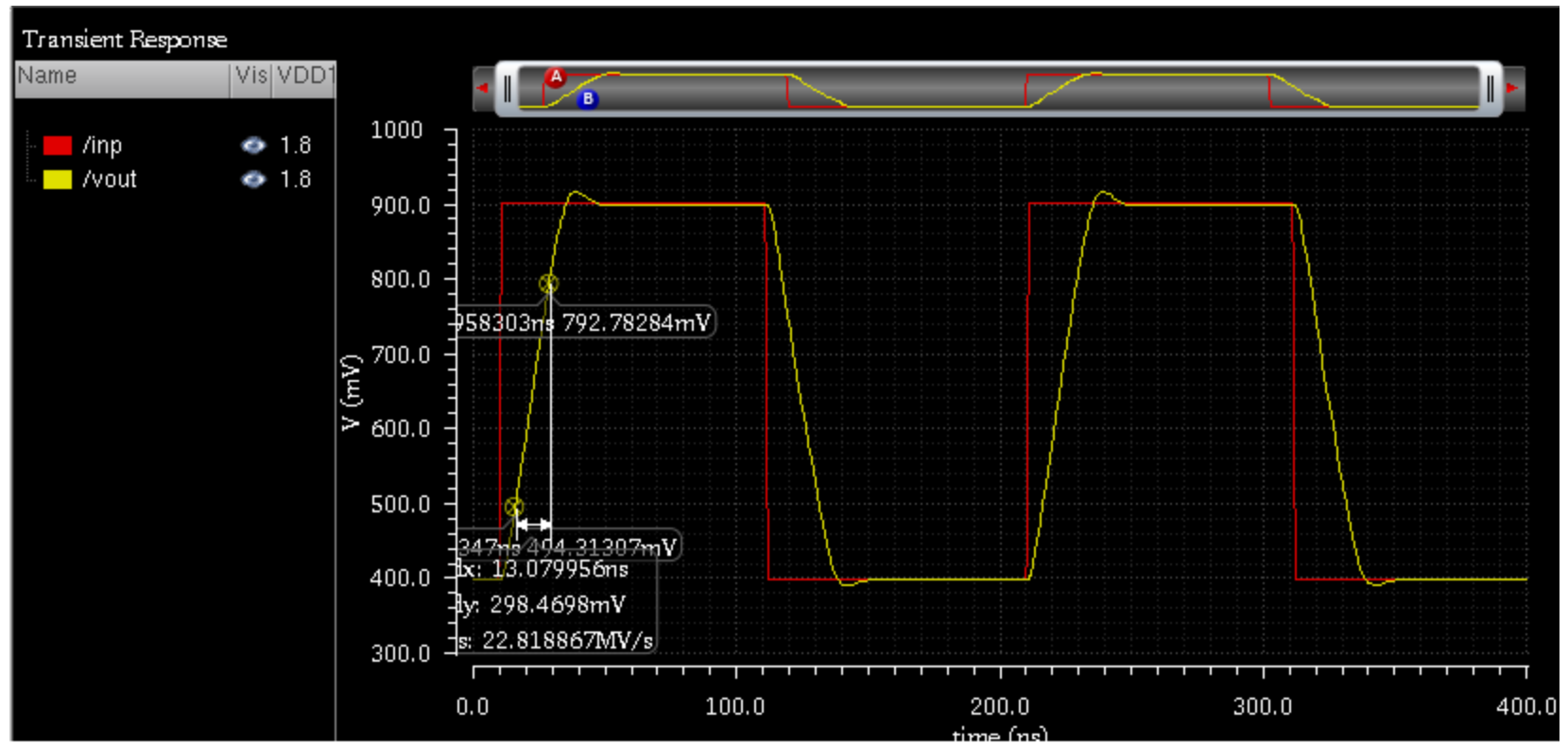
# Typical Result for Main OPAMP


Transient analysis- Input waveform will be different this time.

You will have to apply a 1.8V pulse at VSEL node. – See the description on page 6.



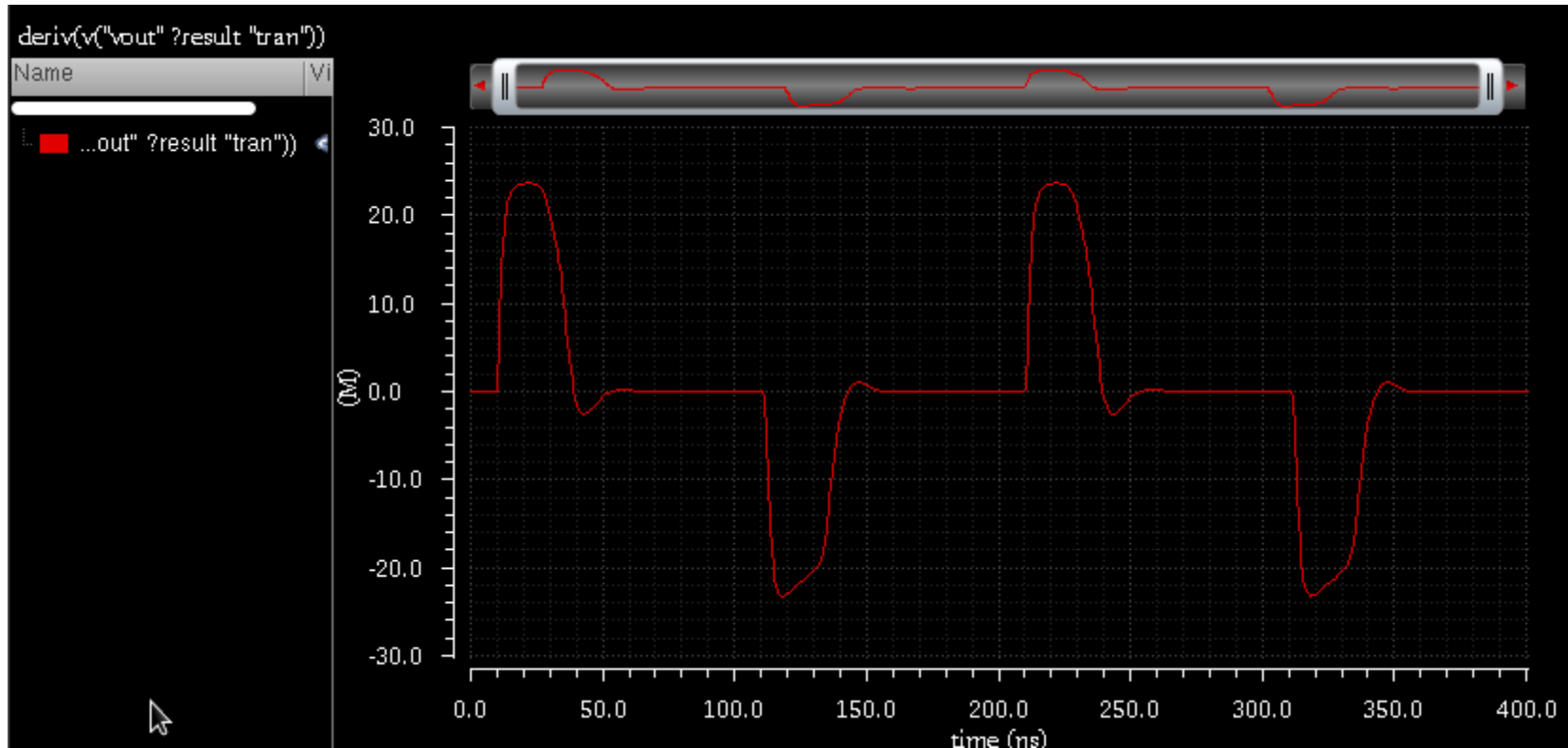
# Typical Result for Main OPAMP

Slew rate by taking “deriv” of the output signal in Cadence Calculator


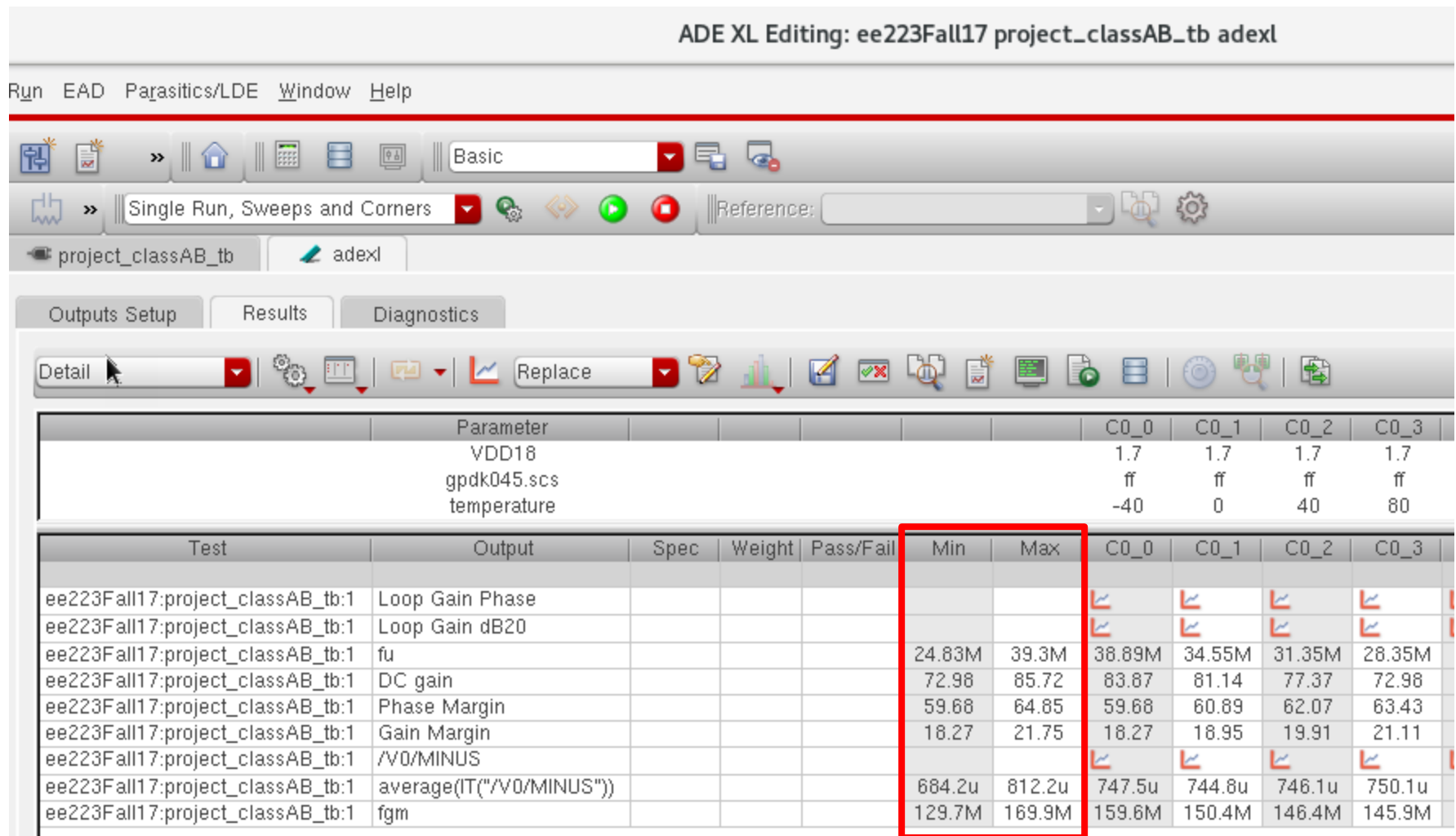
# PVT Simulation Result for Main OPAMP using ADE-XL



**PVT conditions :** TT, SS, FF, 1.7V, 1.8V, 1.9V, -40C, 0C, 40C, 80C – Total 36 corners



# References

---

## ➤ Bandgap

- Chapter 11 of the Textbook
- H. Banba, et al. “A CMOS Bandgap Reference Circuit with Sub-1-V Operation,” *IEEE Journal of Solid-State Circuits*, Vol. 34, no. 5, pp. 670–674, May 1999

## ➤ RefGen

- Ian Wheeler, *MS Thesis, California State University, Sacramento*, A fast settling reference generator with signal-dependent charge cancellation for an 8-bit 1.5 bit/stage pipeline ADC, 2013

## ➤ OPAMP

- K. Langen and J. Huijsing, “Compact low-voltage power-efficient operational amplifier cells for VLSI,” *IEEE Journal of Solid-State Circuits*, Vol. 33, no. 10, pp. 1482–1496, Oct 1998