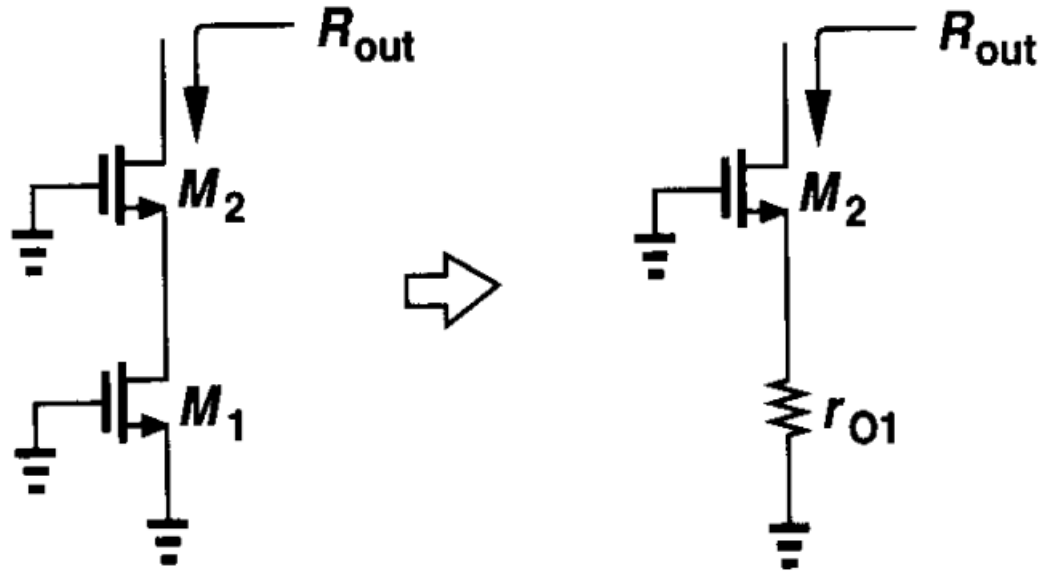

EE223 Analog Integrated Circuits

Fall 2018

Lecture 10: Folded –Cascode and Differential Pairs

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259



Output Impedance of Cascode Stage



$$R_{out} = r_{o1} + r_{o2} + (g_{m2}r_{o2})r_{o1}$$

$$R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1} \quad \text{if } g_{mb} \neq 0$$

Gain of Cascode Stage

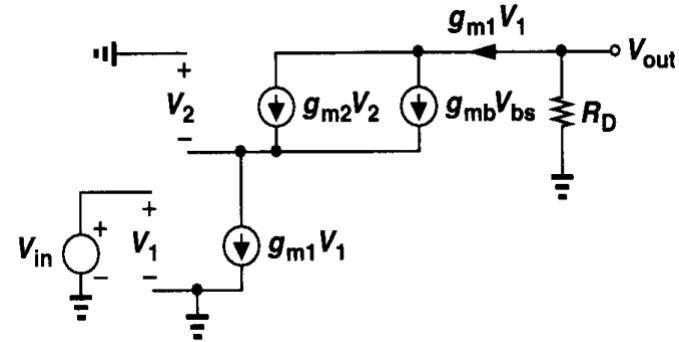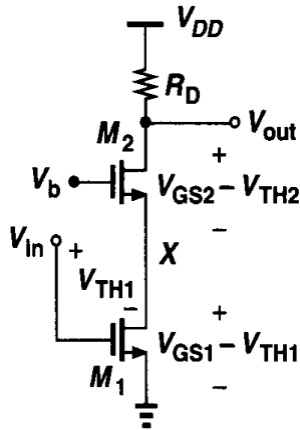


$$A_v = \frac{V_{out}}{V_{in}} = -g_{m1} R_{out}$$

$$R_{out} = \{r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}\} // R_D$$

$$\approx (g_{m2}r_{o2})r_{o1} // R_D$$

$$A_v \approx -g_{m1}(g_{m2}r_{o2})r_{o1} = -(g_m r_o)^2 \quad \text{if } R_D \text{ is neglected}$$




Cascode Amp with Cascode Current Source

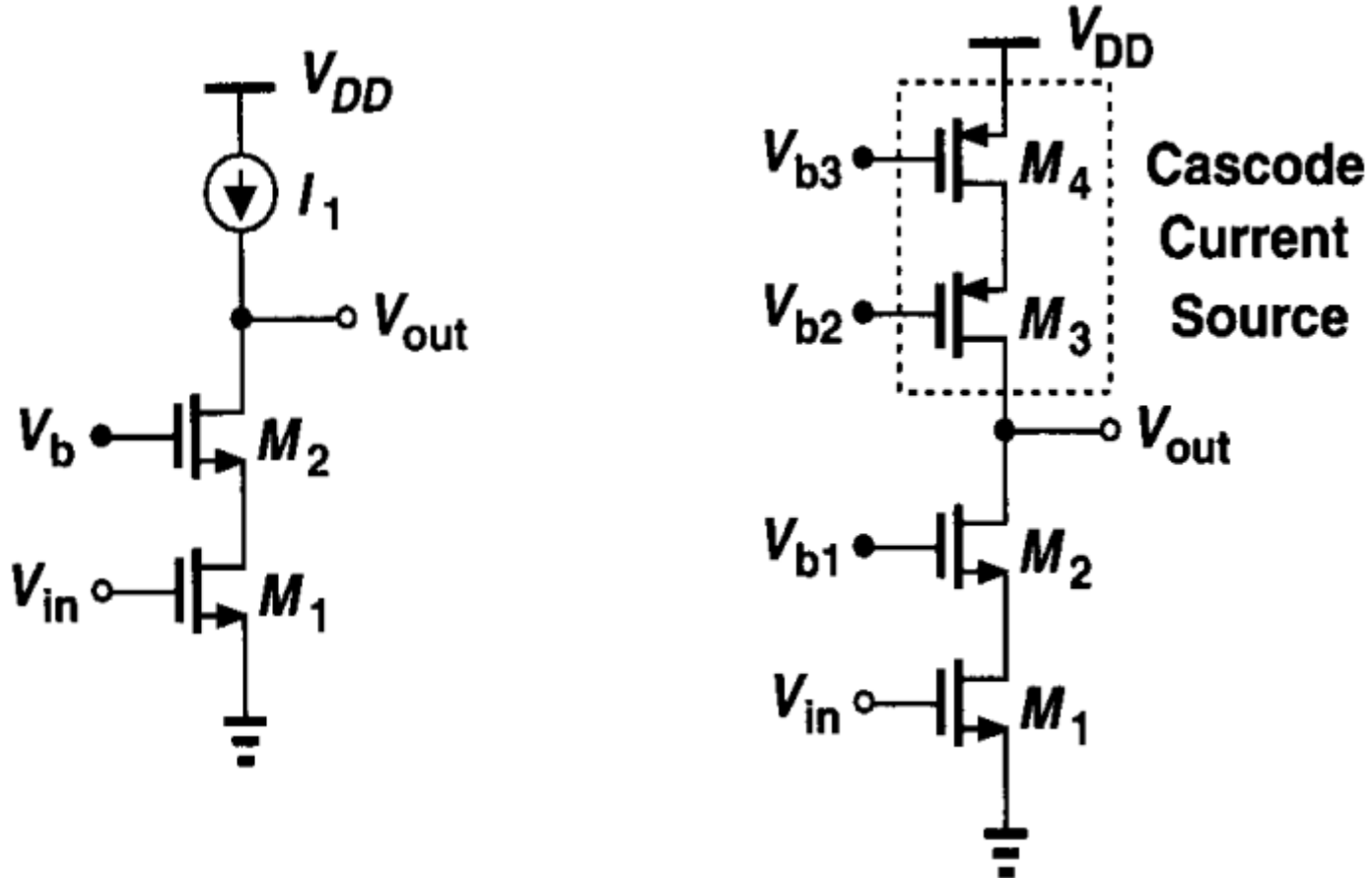

$$A_v \approx -g_{m1}[\{(g_{m2}r_{o2})r_{o1}\}||\{(g_{m3}r_{o3})r_{o4}\}] \approx -\frac{(g_m r_o)^2}{2}$$



Folded Cascode Structures

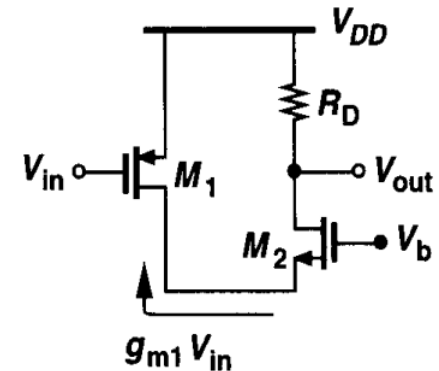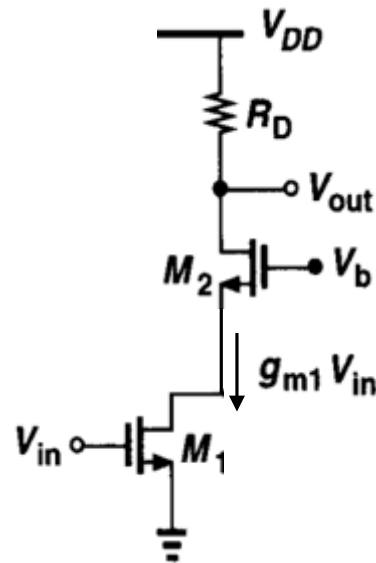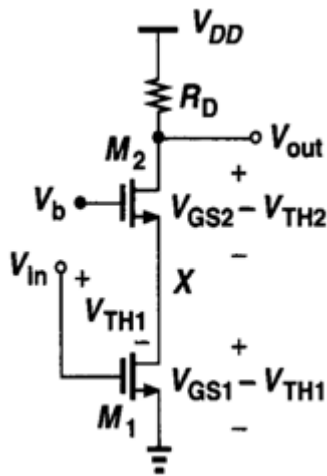Folded Cascode Topology : Cascade of CS stage and CG stage with different transistor types for CS and CG




Folded Cascode Structures

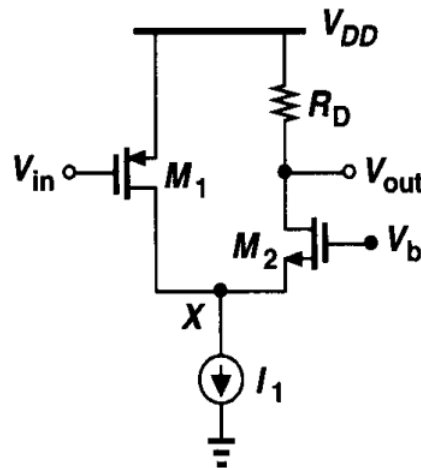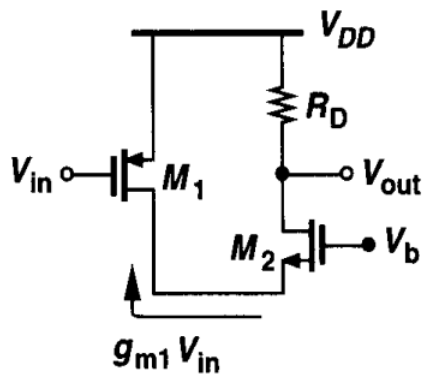Folded Cascode Topology : Cascade of CS stage and CG stage with different transistor types for CS and CG




PMOS CS
NMOS CG

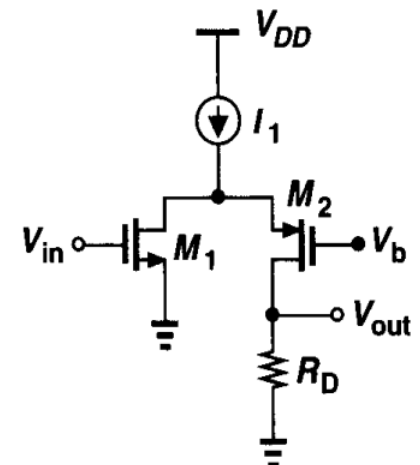

NMOS CS
PMOS CG

Output Impedance of Folded Cascode

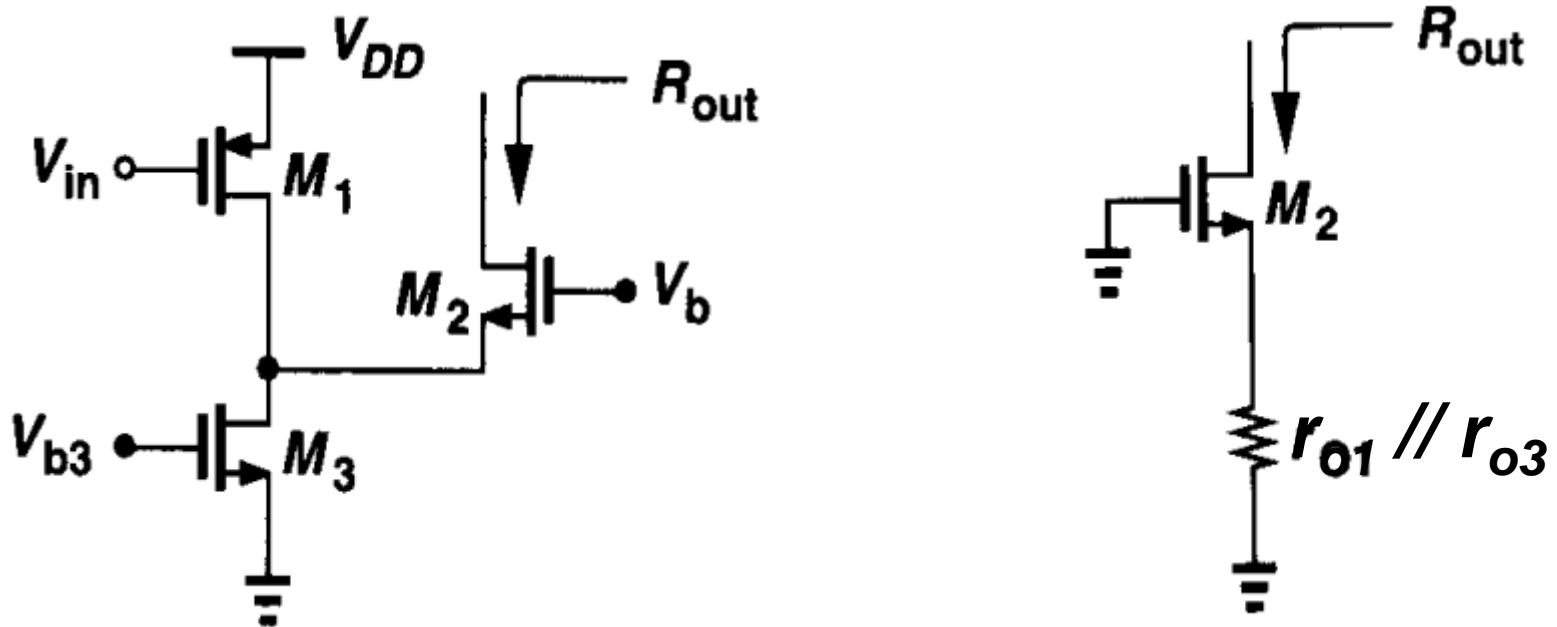


$$R_{out} = R_S + r_{o2} + (g_{m2} + g_{mb2})r_{o2}R_S$$


$$R_S = r_{o1} // r_{o3}$$

Single-Ended vs. Differential Operation

Single-ended

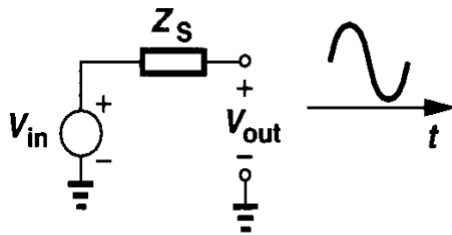


Differential

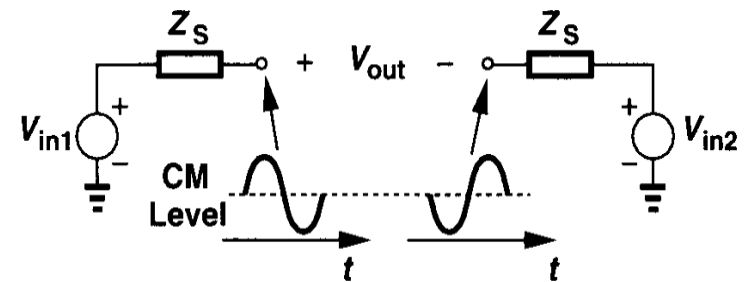


Advantages of Differential Operation

Single-ended

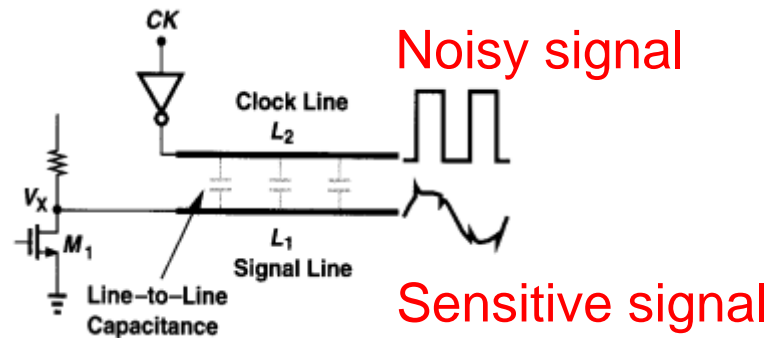


Differential

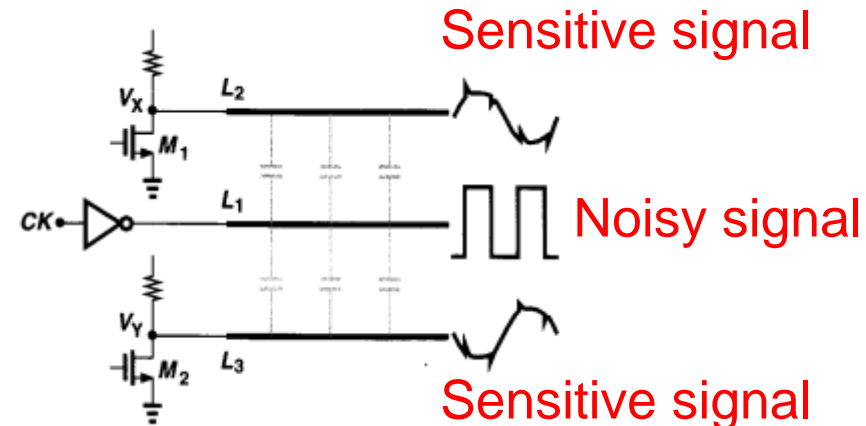


Immunity to environmental noise
→ Reject common-mode noise

Advantages of Differential Operation

Single-ended

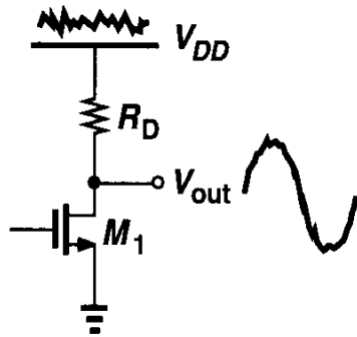

Differential

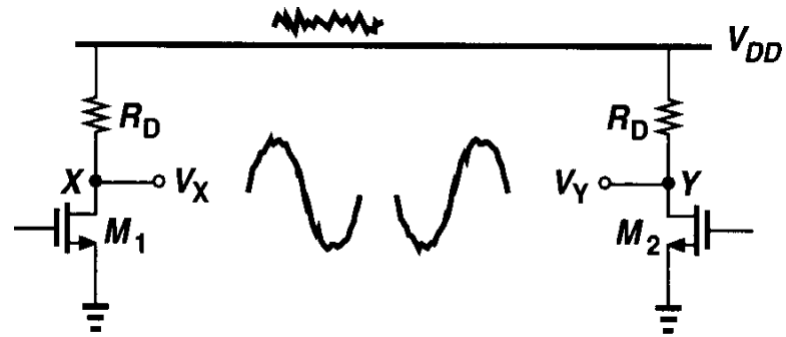



Immunity to environmental noise
→ Robust to supply noise

Other Advantages of Differential Operation

- Increased Swing
- Simpler Biasing
- Higher Linearity


- Disadvantage
 - Area Increase
 - Common-mode stabilization circuit necessary

Simple Differential Circuit



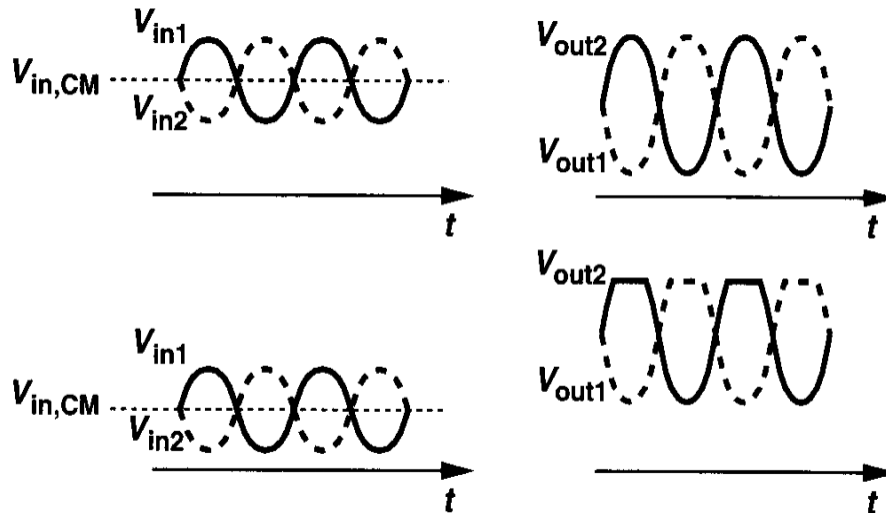
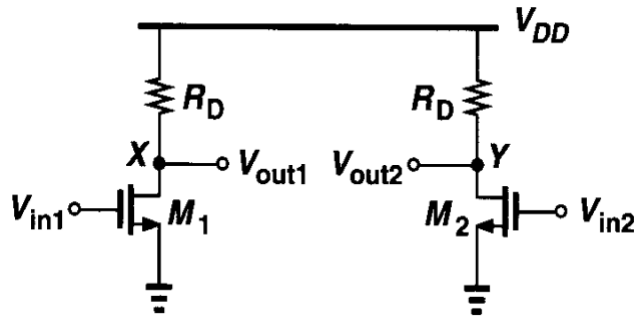


Sensitive to input common-mode level


MOS Differential Pair

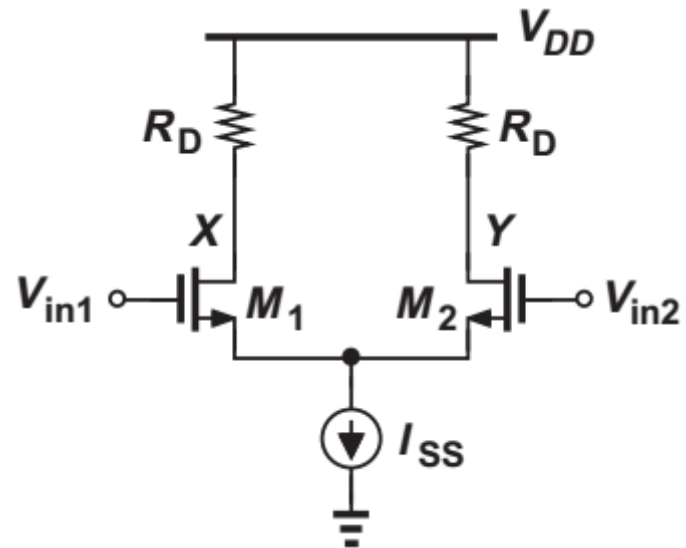

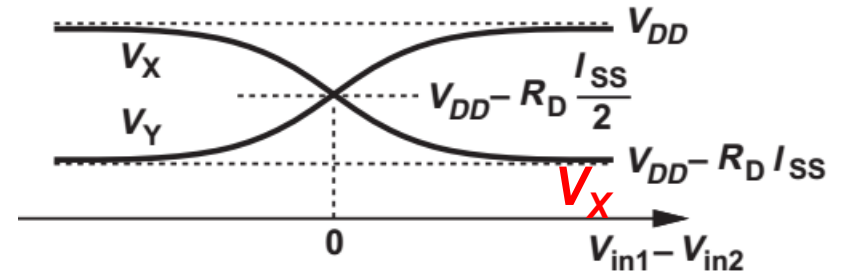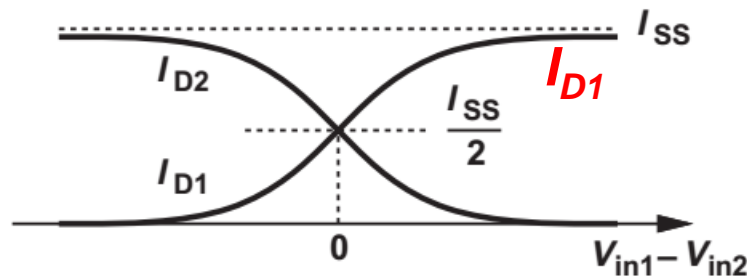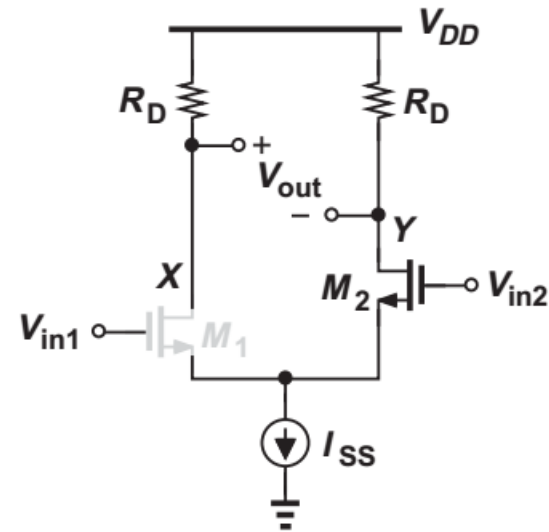
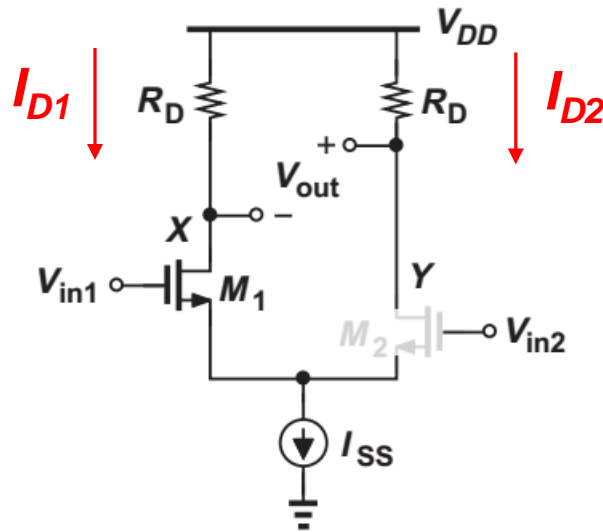
Input-Output Characteristics of Differential Pair



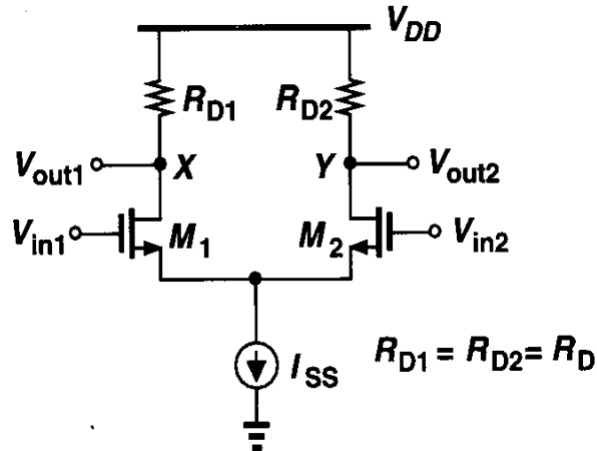
Input-Output Characteristics of Differential Pair



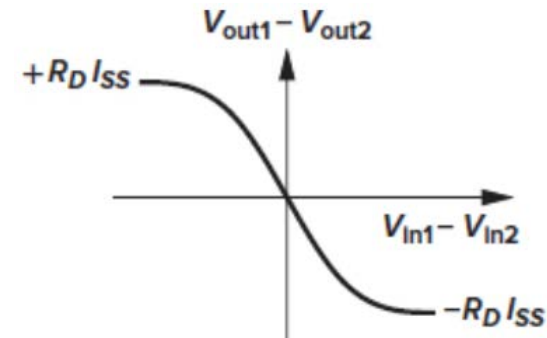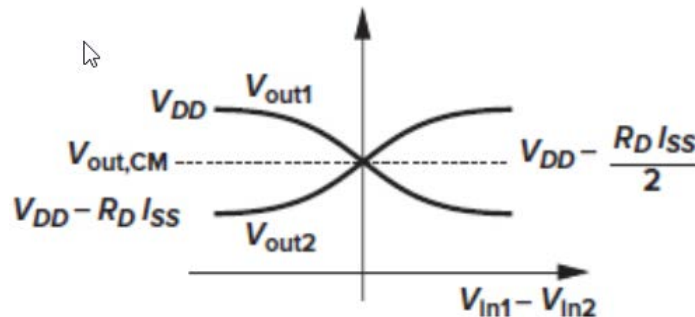- Output signal levels are well defined and independent of input CM level
- Circuit becomes nonlinear as input swing increases



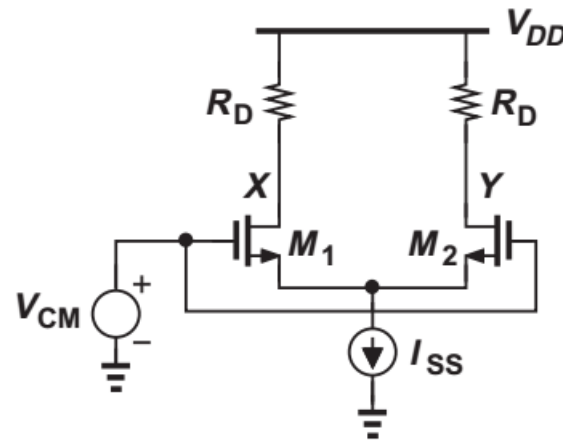CM Response of MOS Differential Amplifier








$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

$$V_X = V_Y = V_{DD} - R_D \frac{I_{SS}}{2}$$

$$(V_{GS} - V_{TH})_{equil.} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$


$$V_{DD} - R_D \frac{I_{SS}}{2} > V_{CM} - V_{TH}$$

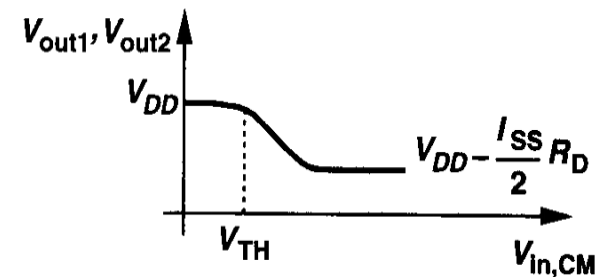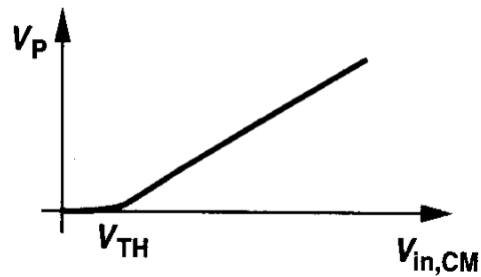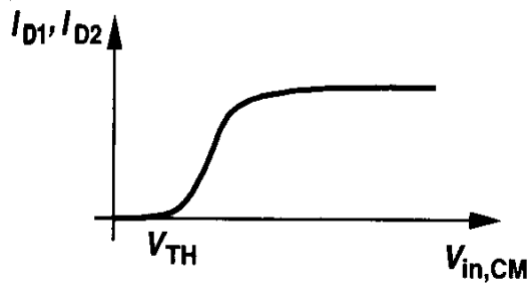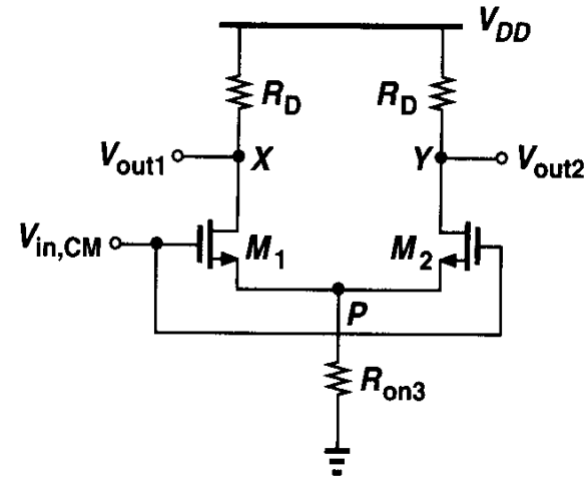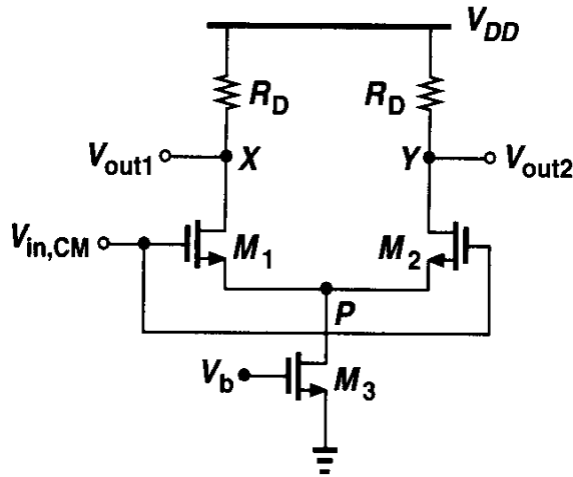Common-Mode Characteristics of Differential Pair




$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min \left[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH}, V_{DD} \right]$$

Differential Gain vs. $V_{in,CM}$

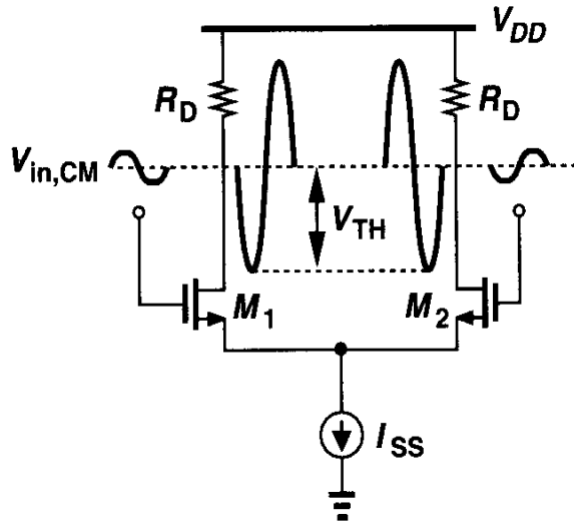


Tail current source enters Saturation

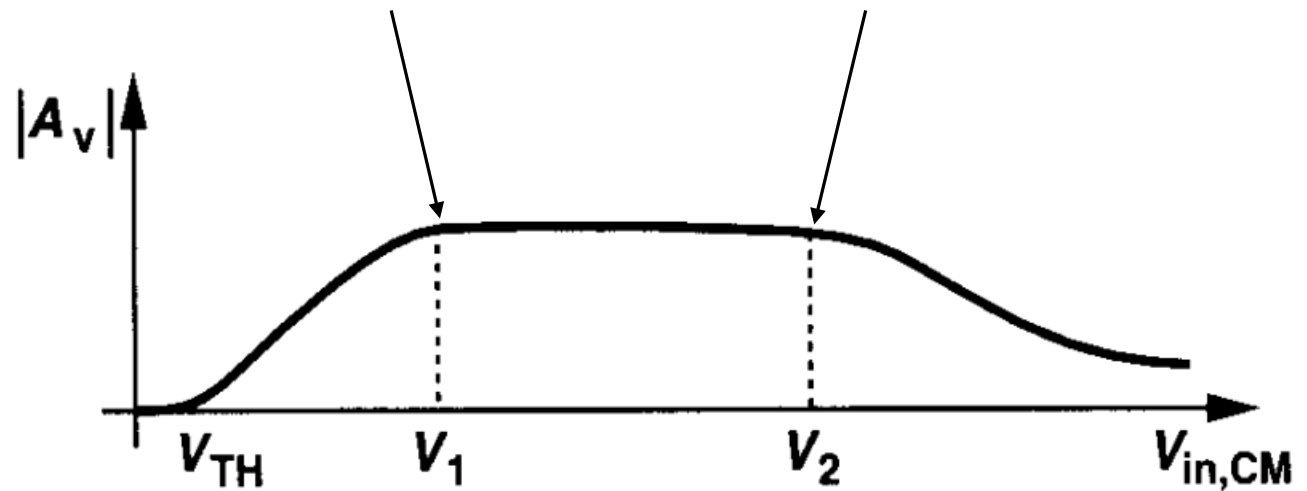Input transistors enter the Triode region



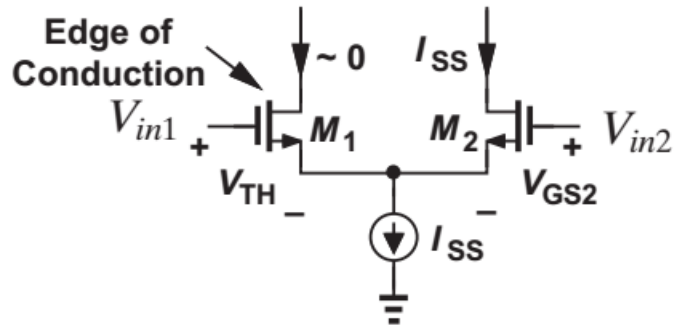Large Signal Analysis of Differential Pair



$$I_D = (1/2)\mu_n C_{ox}(W/L)(V_{GS} - V_{TH})^2$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$$

$$(V_{GS} - V_{TH})_{equil.} = \sqrt{\frac{2I_{D1}}{KP\left(\frac{W}{L}\right)}} = \sqrt{\frac{2\left(\frac{I_{SS}}{2}\right)}{KP\left(\frac{W}{L}\right)}}$$

$$V_{in1} - V_{GS1} = V_{in2} - V_{GS2}$$

$$I_{D1} + I_{D2} = I_{SS}$$


$$V_{GS1} = V_{TH}$$

$$V_{GS2} = V_{TH} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$|V_{in1} - V_{in2}|_{max} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$|V_{in1} - V_{in2}|_{max} = \sqrt{2}(V_{GS} - V_{TH})_{equil.}$$

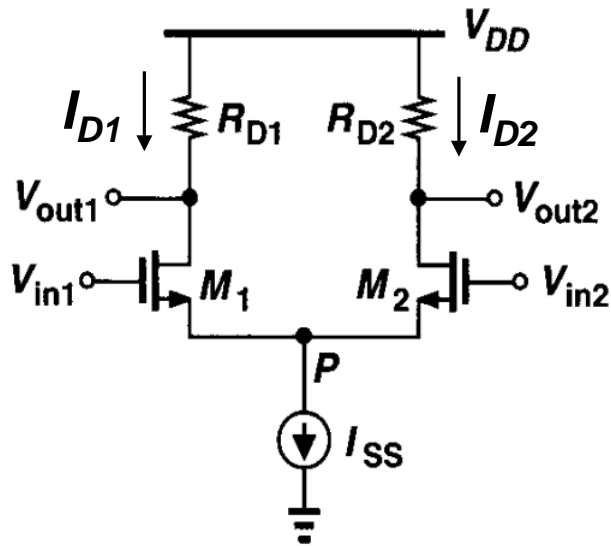Large Signal Analysis of Differential Pair



$\sqrt{2} V_{dsat}$ of M_1 & M_2 in equilibrium

