


EE 223 HW2

Enrique Hernandez

09/29/2018

1. MOS Small-Signal Analysis on Common Source Amplifier

a.

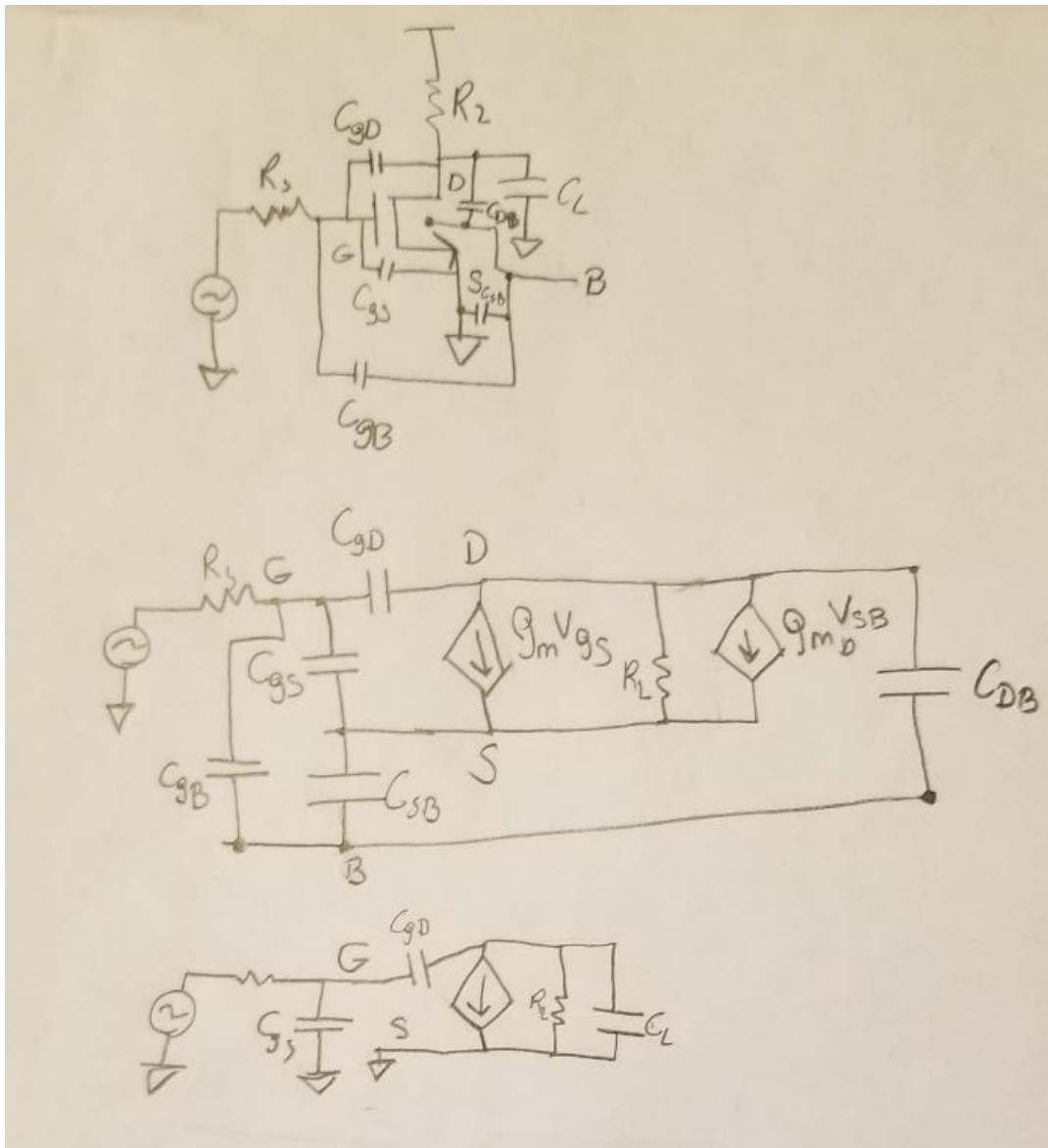

b.

(b)

↓

$$\frac{1}{R_o} + \frac{1}{R_L} + \frac{1}{X_{scL}} = \frac{1}{Z_{eq}}$$

$$\frac{1}{R_L} + sC_L$$

$$\frac{[1 + sC_L] R_L}{R_L} = \frac{1}{Z_{eq}}$$

$$\frac{R_L}{1 + sC_L R_L} = Z_{eq}$$

$$V_{gs} = V_g - V_s$$

$$V_{gs} = \frac{\frac{1}{sC_{gs}}}{R_s + \frac{1}{sC_{gs}}} V_{in} - V_s$$

$$V_{out} = -g_m V_{gs} Z_{eq}$$

$$= -g_m \left(\frac{\frac{1}{sC_{gs}}}{R_s + \frac{1}{sC_{gs}}} \cdot V_{in} \right) \left(Z_{eq} \right)$$

$$\frac{V_{out}}{V_{in}} = -g_m \left(\frac{\frac{1}{sC_{gs}}}{R_s + \frac{1}{sC_{gs}}} \right) \left(Z_{eq} \right)$$

$$= -g_m \left(\frac{\frac{1}{sC_{gs}} \cdot \frac{sC_{gs}}{1}}{\left(R_s + \frac{1}{sC_{gs}} \right) \frac{sC_{gs}}{1}} \right) \left(Z_{eq} \right)$$

$$= -g_m \left(\frac{1}{sC_{gs} R_s + 1} \right) \left(\frac{R_L}{1 + sC_L R_L} \right)$$

$$= \frac{-g_m R_L}{[sC_{gs} R_s + 1][1 + sC_L R_L]}$$

C.

$$1C) \quad \frac{V_{out}}{V_{in}} = \frac{-g_m R_L}{[s C_{gs} R_s + 1][1 + s C_L R_L]}$$


$$A_{DC} = \left. \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = \frac{-g_m R_L}{[0 \cdot C_{gs} R_s + 1][1 + 0 \cdot C_L R_L]} = -g_m R_L$$

Two Poles

$$s = \frac{1}{R_s C_{gs}}$$

$$s = \frac{1}{C_L R_L}$$

1D) When $R_L C_L \gg R_s C_{gs}$

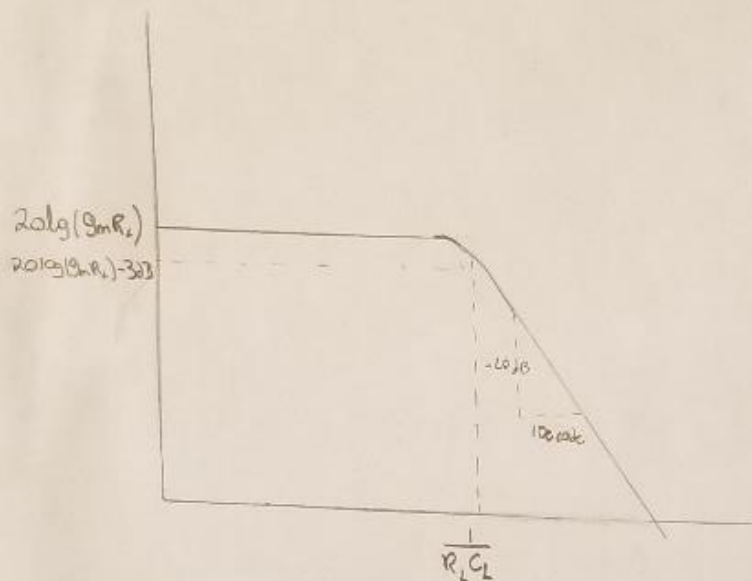

2. Cadence Spectre Simulation of Common-Source Amplifiers

a. Schematic and simulation

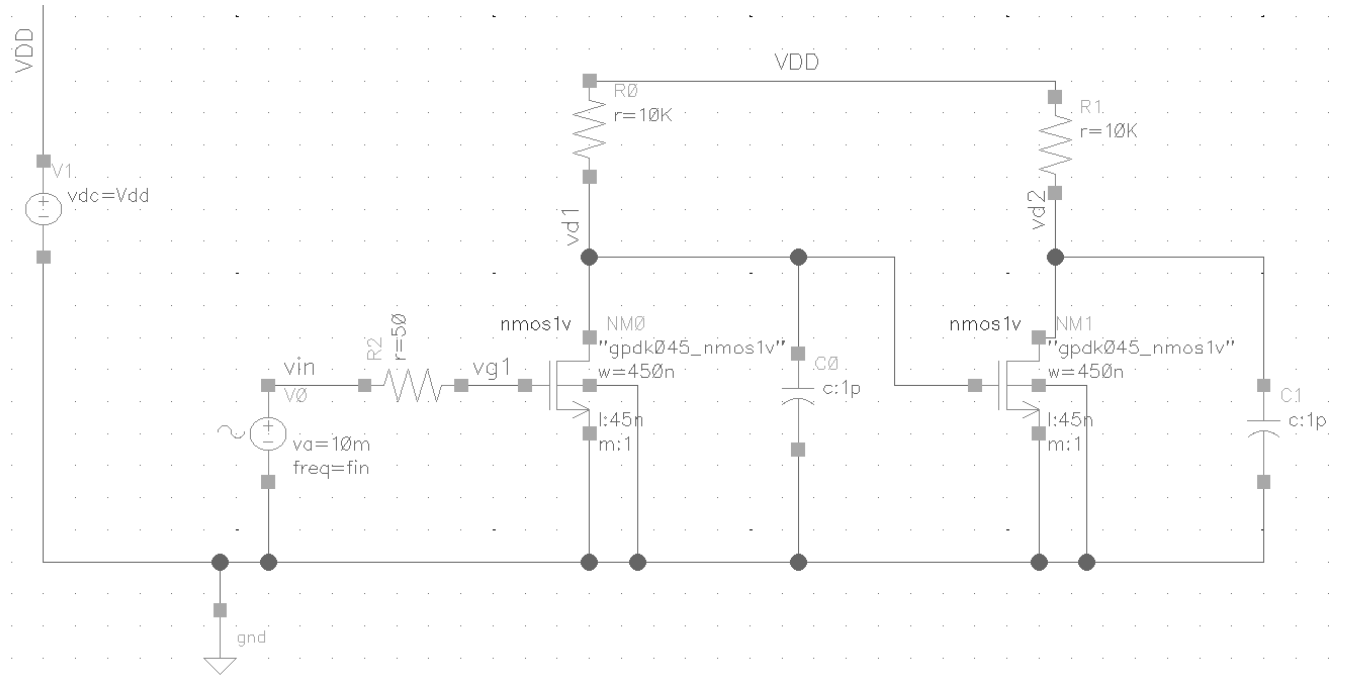


Figure 1: Schematic

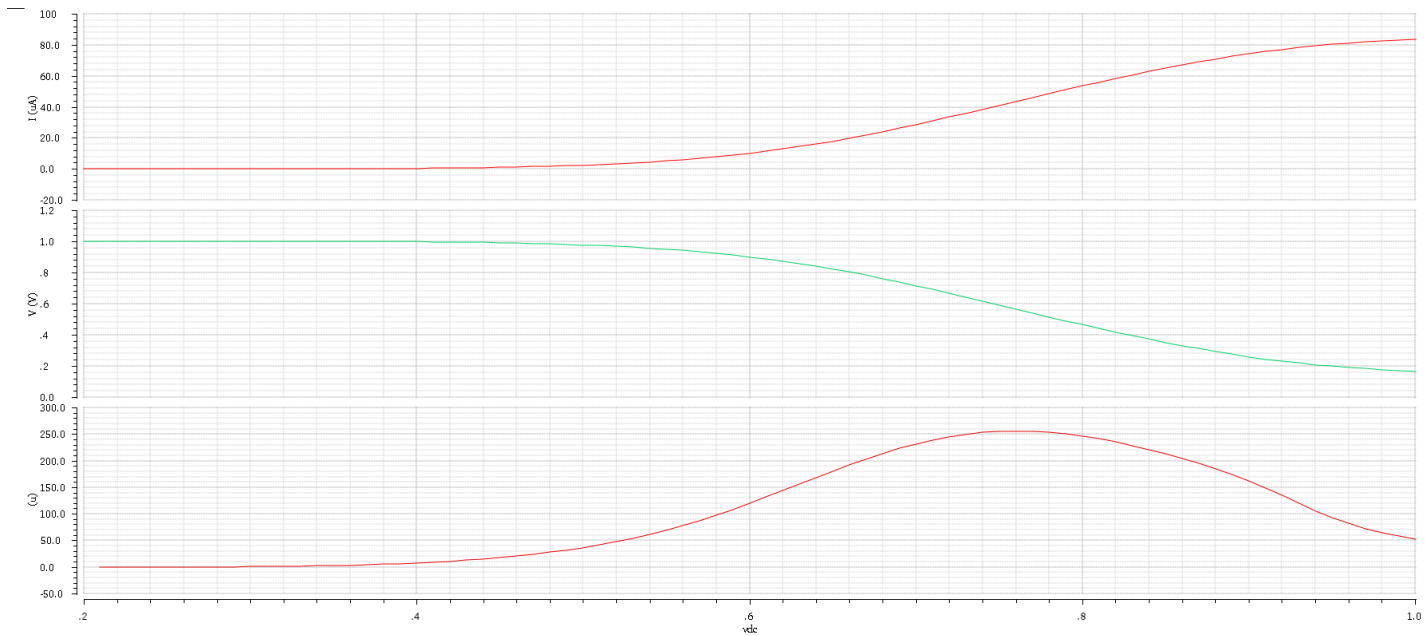


Figure 2: Red curve is I_d vs V_g , Green curve is V_d vs V_g and Orange curve is G_m vs V_g .

B.

$$2b) g_m = 271.848 \mu$$

$$R_L = 10 k$$

$$V_{th} = 619.06 mV$$

$$A = -10 \times 10^3 \cdot 271.848 \mu$$


$$= -(2718.48 \times 10^3)$$

$$= -2718.48$$

$$A = 20 \log(2718.48)$$

$$A = 8.69 dB$$

2d)

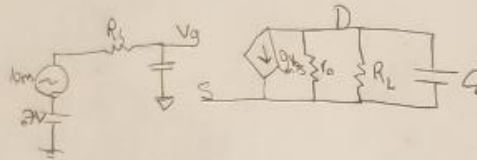

$$\frac{1}{R_o} + \frac{1}{R_L}$$

$$\frac{R_L + R_o}{R_o \cdot R_L} = \frac{1}{R_{eq}} = R_{eq} = \frac{R_o \cdot R_L}{R_L + R_o}$$

$$2e) A_1 = \frac{715}{700} = 1.02143 = 20 \log(1.02143) = 0.18417 dB$$

$$A_2 = \frac{679}{715} = 0.9510$$

2f)

$$W_{out} = \frac{1}{R_L C_L}$$

$$= \frac{1}{10k \cdot 1 \times 10^{-2}}$$

$$= \frac{1}{1 \times 10^4 \cdot 1 \times 10^{-2}}$$

$$= \frac{1}{1 \times 10^2}$$

$$= 1 \times 10^2 \text{ Actual} = 18.1569 MHz$$

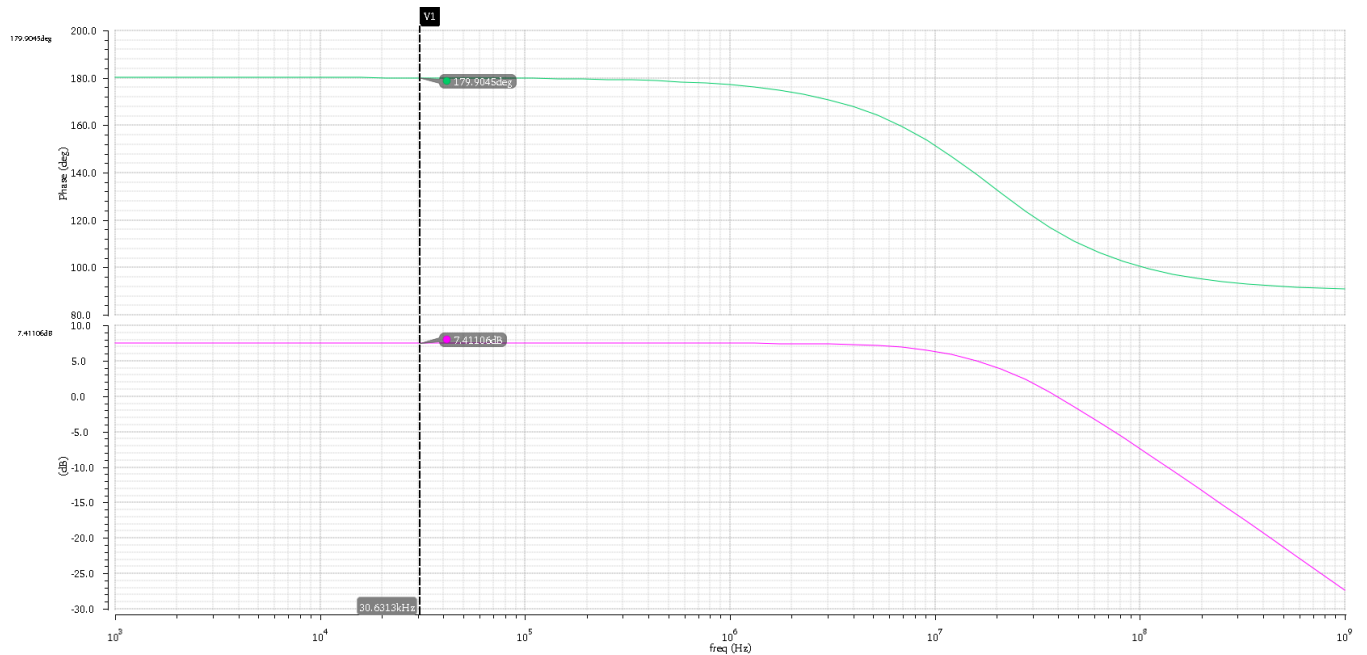


Figure 3: Gain Vs Frequency (pink trace)

- b. The reason the calculated result and the simulated result do not agree is because the r_o is not infinity. There is a channel length modulation that causes a gain change. This is because r_o is in parallel with the load resistance causing the gain to be smaller.

c.

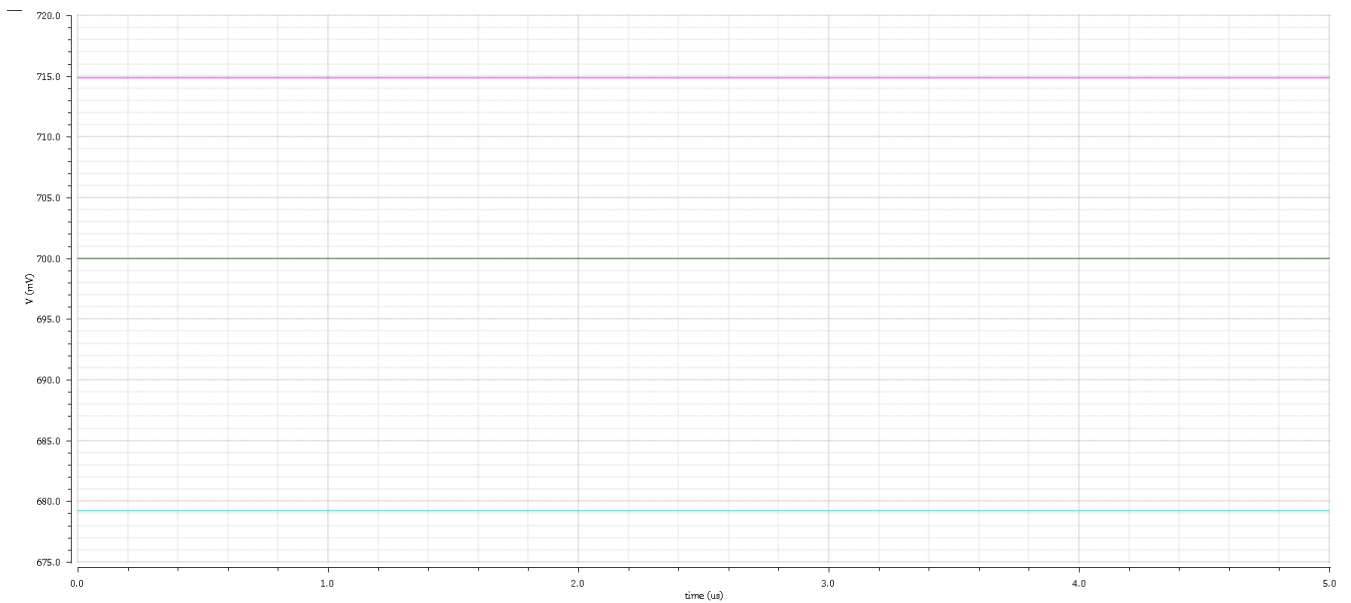


Figure 4: Transient simulation for V_{in} (Green), V_{d1} (pink) and V_{d2} (blue)

- d. The results of the calculated poles and the simulated poles do not agree is because the output capacitance is not only the load capacitor. There are other capacitances that contribute to the output capacitance. This causes the pole to take effect at a smaller frequency.


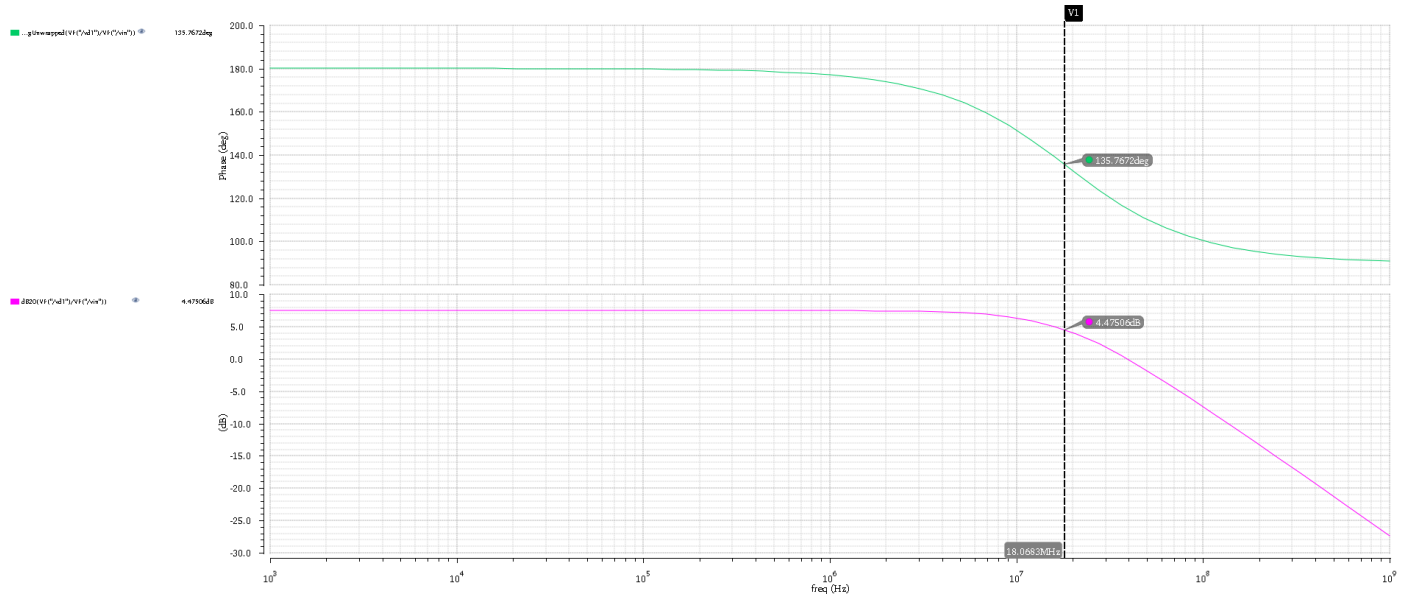


Figure 5: transfer function 3dB point (simulate 18MHZ, Calculated 100MHZ)

3. Body Effect on Threshold Voltage

3)

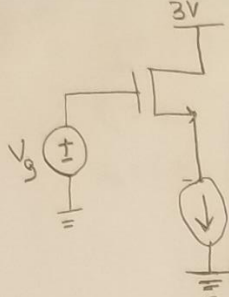

$V_{T0} = 0.5V$, $\gamma = 0.4V^{1/2}$, $2\phi_F = 0.9V$, $\mu_{Cox} = 130 \mu A/V^2$
 $\frac{W}{L} = \frac{2\mu}{200n}$

$$V_T = V_{T0} + \gamma \left(\sqrt{|2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|} \right)$$

$$\gamma = \frac{\sqrt{2q\epsilon_{Si} N_{sub}}}{C_{ox}}$$

$$I_D = \frac{1}{2} K' \frac{W}{L} (V_{GS} - V_{Th})^2$$

$$0.6V = 0.5V + (0.4V^{1/2}) \left(\sqrt{|0.9V + V_{SB}|} - \sqrt{0.9V} \right)$$

$$V_{DD} > V_{GS} - V_{Th}$$

$$10 \mu A = \frac{1}{2} \left(130 \mu A/V^2 \right) \left(\frac{2\mu}{200n} \right) (V_{GS} - V_{Th})^2$$

$$V_T = V_{T0} + \gamma \sqrt{|2\phi_F + V_{SB}|} - \gamma \sqrt{|2\phi_F|}$$

$$\left(\frac{V_T - V_{T0} + \gamma \sqrt{|2\phi_F|}}{\gamma} \right)^2 = \left(\sqrt{|2\phi_F + V_{SB}|} \right)^2$$

$$\left(\frac{V_T - V_{T0} + \gamma \sqrt{|2\phi_F|}}{\gamma} \right)^2 = |2\phi_F + V_{SB}|$$

$$\left(\frac{V_T - V_{T0} + \gamma \sqrt{|2\phi_F|}}{\gamma} \right)^2 - 2\phi_F = V_{SB} = V_S - V_{GS} > 0$$

$$\left(\frac{0.6 - 0.5 + (0.4)\sqrt{0.9}}{0.4} \right)^2 - 0.9 = V_S$$

$$\left(\frac{0.1 + (0.4)(0.94868)}{0.4} \right)^2 - 0.9 = V_S$$

$$2.37 - 0.9 = V_S$$

$$1.47 = V_S$$

$V_{DD} + V_{Th} > V_{GS}$
 $V_{GS} > V_{Th}$
 $V_G > V_{Th} + V_S$
 $V_{DD} + V_{Th} - V_G > V_S$

$$\sqrt{\frac{2I_D \cdot L}{K'W}} = \sqrt{(V_{GS} - V_{Th})^2}$$

$$\sqrt{\frac{2I_D \cdot L}{K'W}} = V_{GS} - V_{Th}$$

$$\sqrt{\frac{2I_D \cdot L}{K'W}} + V_S + V_{Th} = V_G$$

$$\sqrt{\frac{2 \cdot 10 \times 10^{-6} \cdot 200 \times 10^{-9}}{130 \times 10^{-6} \cdot 2 \times 10^{-6}}} + 1.47 + 0.6 = V_G$$

$$\sqrt{\frac{400 \times 10^{-16}}{260 \times 10^{-12}}} + 1.47 + 0.6 = V_G$$

$$\sqrt{\frac{400 \times 10^{-4}}{260}} + 1.47 + 0.6 = V_G$$

$$1.2403 \times 10^{-4} + 1.47 + 0.6 = V_G$$

$$V_G = 2.07$$

4. Layout & Transistor Capacitors

4)

$V_0 = 0.5V$
 $V_x = 0.4V$
 $V_y = 0V$
 $V_{g1} = 1V$
 $V_{g2} = 1.5V$
 $V_{t0} = 0.7V$
 $\gamma = 0$

$V_{th} = V_{t0} + \gamma (\sqrt{1.2\phi_F - V_{bs1}} - \sqrt{1.2\phi_F})$
 $V_{th} = V_{t0}$ when $\gamma = 0$

b)

$V_{g1} > V_{th}$
 $V_{g1} - V_{s1} > V_{th}$
 $1.0 - 0 > 0.7$
 $V_{DS1} > V_{g1} - V_{th}$
 $1.0 - 0 > 0.3$
 $0.4 > 0.3$
 M_1 is in saturation.

$V_{g2} > V_{th}$
 $V_{g2} - V_{s2} > V_{th}$
 $1.5 - 0.4 > 0.7$
 $1.1 > 0.7$
 $V_{DS2} > V_{g2} - V_{th}$
 $0.5 - 0.4 > 0.4$
 $0.1 > 0.4$
 M_2 is in linear region.

$C_{GC} = W L_{eff} C_{ox}$
 $C_{GSov} = W C_{ov}$
 $C_{GDov} = W C_{ov}$

M_1 is in saturation
 $C_{GD} = C_{GDov} = W C_{ov} \Rightarrow 10 \lambda (1fF/\mu m) = \frac{10(0.5\mu m)}{\mu m} \cdot 1fF = 5fF$
 $C_{GS} = C_{GSov} + \frac{2}{3} C_{GC} \Rightarrow W C_{ov} + \frac{2}{3} (W L_{eff} C_{ox}) = \frac{10(0.5\mu m)}{\mu m} \cdot 1fF + \frac{2}{3} \frac{10(0.5\mu m) \cdot 0.9\mu m}{\mu m^2} \cdot 7fF$
 $C_{GS} = 5fF + \frac{2}{3} (31.5fF) = 5fF + 21fF = 26fF$
 $C_{GB} = 0$

M_2 is linear region
 $C_{GD} = C_{GDov} + \frac{1}{2} C_{GC} = W C_{ov} + \frac{1}{2} W L_{eff} C_{ox} = \frac{10(0.5\mu m)}{\mu m} \cdot 1fF + \frac{1}{2} \frac{10(0.5\mu m) \cdot 0.9\mu m}{\mu m^2} \cdot 7fF$
 $C_{GS} = C_{GSov} + \frac{1}{2} C_{GC} = 41.5fF$

$C_{ox} = 7fF/\mu m^2$, $C_{ov} = 1fF/\mu m$, $C_{j0} = 0.01fF/\mu m$, $C_{cb} = 1fF/\mu m^2$, $L_{eff} = 1\mu m - 10(0.5)\mu m$
 $L_{eff} = 0.9\mu m$

$C_{gm1} = 57fF$
 $C_{gm2} = 83fF$

$C_{GD} = 5fF$
 $C_{GS} = 26fF$
 $C_{GB} = 0$
 $C_{GD} = 5fF$
 $C_{GS} = 41.5fF$

d)

$$A_S = A_D = WE$$

$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_{DS}}{\Phi_B}\right)}$$

$$C_{jsw}$$

$$C_j = 1 \text{ fF}/(\mu\text{m})^2 \quad C_{jsw} = 0.01 \text{ fF}/\mu\text{m}$$

$$P_S = P_D = 2(w+E)$$

$$C_{SB} = C_{DB} = AC_j + PC_{jsw} = WE C_j + 2(w+E)C_{jsw}$$

$$C_Y = \frac{[10 \cdot 0.5 \mu\text{m}][5 \cdot 0.5 \mu\text{m}][1 \text{ fF}]}{(\mu\text{m})^2} + \frac{2(10 \cdot 0.5 \mu\text{m} + 5 \cdot 0.5 \mu\text{m})0.01 \text{ fF}}{\mu\text{m}}$$

$$\begin{aligned} C_Y &= 5 \cdot 2.5 \cdot 1 \text{ fF} + 2(7.5) \cdot 0.01 \text{ fF} \\ &= 2(12.5 \text{ fF}) + 0.15 \text{ fF} \\ &= 25.15 \text{ fF} \end{aligned}$$

$$C_X = \frac{[10 \cdot 0.5 \mu\text{m}][6 \cdot 0.5 \mu\text{m}][1 \text{ fF}]}{(\mu\text{m})^2} + \frac{2[10 \cdot 0.5 \mu\text{m} + 6 \cdot 0.5 \mu\text{m}]0.01 \text{ fF}}{\mu\text{m}}$$

$$\begin{aligned} &= [5 \cdot 3] 1 \text{ fF} + 2[5+3]0.01 \text{ fF} \\ &= 15 \text{ fF} + 0.16 \text{ fF} \\ &= 30.16 \text{ fF} \end{aligned}$$

$$C_O = \frac{[10 \cdot 0.5 \mu\text{m}][6 \cdot 0.5 \mu\text{m}][1 \text{ fF}]}{(\mu\text{m})^2} + \frac{[10 \cdot 0.5 \mu\text{m} + 6 \cdot 0.5 \mu\text{m}]0.01 \text{ fF}}{\mu\text{m}}$$

$$\begin{aligned} &= [5 \cdot 3] 1 \text{ fF} + [5+3]0.01 \text{ fF} \\ &= 15 \text{ fF} + 0.08 \text{ fF} \\ &= 15.08 \text{ fF} \end{aligned}$$