
EE288 Data Conversions/Analog Mixed-Signal ICs


Spring 2018

Lecture 7: EE223 Review

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259


Cascode Biasing

Cascode Current Mirror

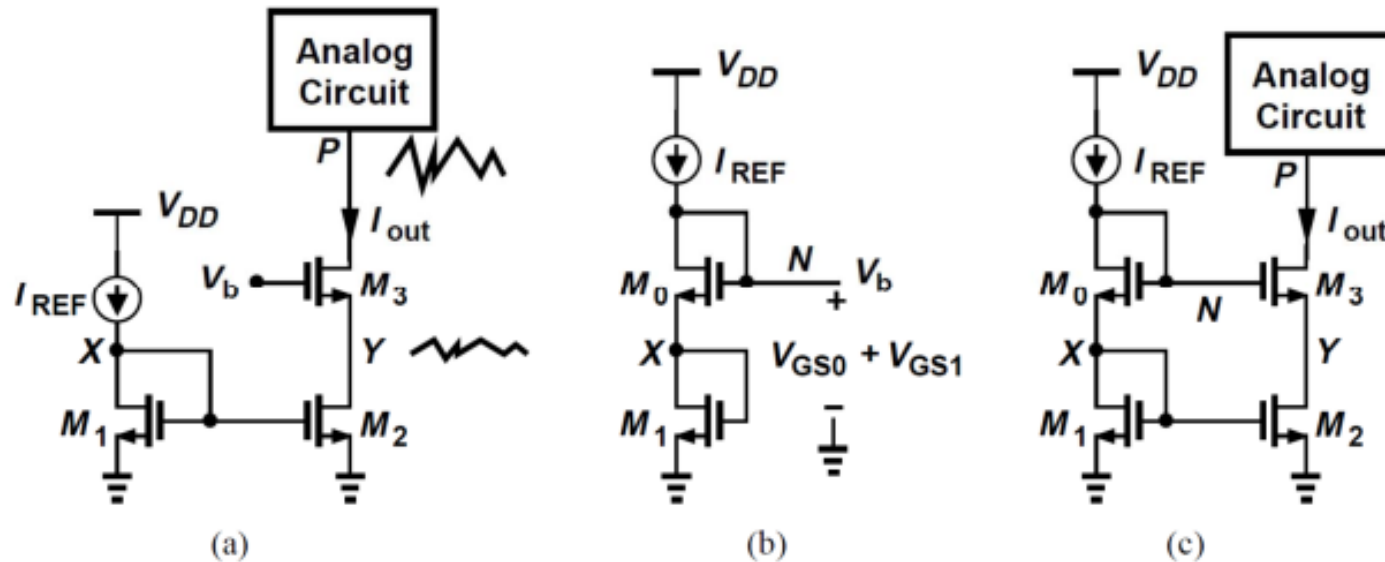


- A cascode device can shield a current source, thereby reducing the voltage variations across it.
- But, how do we ensure that $V_{DS2} = V_{DS1}$?
- We can generate V_b such that $V_b - V_{GS3} = V_{DS1}(=V_{GS1})$ with a stacked diode connected transistor

 Cascode Current Mirror Compliance Voltage



 (a) Regular cascode structure

Wide-Swing (High-Swing or Low-Voltage) Cascode




(b) Low-voltage (aka wide-swing) structure

Biasing High Swing Cascode Current Mirror

Another approach for cascode biasing

 → Will use this biasing scheme extensively




- M_A in Saturation
- M_B in Triode
- $(W/L)_A = (W/L)_3 = (W/L)_4$
- $(W/L)_B$ with large L
- Example:
 - $(W/L)_{A,3,4} = 5/0.18$
 - $(W/L)_B = 5/5$
 - Adjust L of M_B in Simulation to get the V_{ds} you want

If you make the current densities of M_A , M_3 and M_4 are equal, V_{ds} of M_B will be copied over to V_{ds} of M_1 and M_2


OTA

 Operational Transconductance Amplifiers (OTA)



- Important Parameters
 - Differential Gain
 - Gain-Bandwidth Product
 - Common-Mode Input Range
 - Common-Mode Gain
 - Common-Mode Rejection Ratio (CMRR)
 - Power-Supply Rejection Ratio (PSRR)
 - Slew Rate

OTA Gain and Bandwidth

 


$$A_{DM} = \frac{g_{m1}}{g_{o6} + g_{o2}}$$

The circuit will have 2 poles


ω_{po} at the output node and ω_{pm} at the "mirror" node

$$\omega_{po} \approx \frac{g_{o6} + g_{o2}}{C_L}, \quad \omega_{pm} \approx \frac{g_{m5}}{C_M}$$

 Assuming the poles are widely spaced and ω_{po} dominates



Simple OTA Summary

 

Transconductance $G_m = g_{m1} = \sqrt{KP_n \frac{W}{L_1} I_{TAIL}}$

Output Conductance $g_{out} = g_{o2} + g_{o6} = \frac{I_{TAIL}}{2} (\lambda_n + \lambda_p)$

DC Gain $A_v = G_m R_{out} = \frac{g_{m1}}{g_{o2} + g_{o6}} = \frac{2 \sqrt{KP_n \frac{W}{L_1} I_{TAIL}}}{\lambda_n + \lambda_p}$

Dominant Pole $\omega_{p1} = \frac{g_{o2} + g_{o6}}{C_L}$

Non - Dominant Pole $\omega_{p2} = \frac{g_{m6}}{C_M} \approx \frac{g_{mg}}{2C_{gs6}}$

Output Noise Current $i_{on}^2 = 2 \left(\frac{8}{3} kT \right) (g_{m1} + g_{m6})$


Input Noise Voltage $v_{in}^2 = 2 \left(\frac{8}{3} kT \right) \left(\frac{1}{g_{m1}} \right) \left(1 + \frac{g_{m6}}{g_{m1}} \right)$

GBW $= \frac{G_m}{C_L} = \frac{\sqrt{KP_n \frac{W}{L_1} I_{TAIL}}}{C_L}$

Slew Rate $SR = \frac{I_{tail}}{C_L}$

Feedback

Simple Feedback System


 


$$\frac{Y}{X} = \frac{A}{1 + \beta A}$$
$$\approx \frac{1}{\beta} \left(1 - \frac{1}{\beta A} \right)$$

where we have assumed $\beta A \gg 1$

Bandwidth Modification of Feedback System
  
$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$




$$\begin{aligned} \frac{Y}{X}(s) &= \frac{\frac{A_0}{1 + \frac{s}{\omega_0}}}{1 + \beta \frac{A_0}{1 + \frac{s}{\omega_0}}} = \frac{A_0}{1 + \beta A_0 + \frac{s}{\omega_0}} = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{(1 + \beta A_0)\omega_0}} \end{aligned}$$

OPAMP


Performance Parameters

 - Gain(Precision), Bandwidth(Speed): 3-dB, f_u
Output Swing, Power dissipation
- Noise, Linearity, Supply Rejection, Offset
- Input CM Range, Input/Output Impedance
- Large-Signal behavior (e.g. Slew rate)



OPAMP Gain Requirement

 The circuit has a nominal gain of 10. i.e., $1 + R_1/R_2 = 10$.
Determine the minimal value of A_1 for a gain error 1%:



Solution:

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{A_1}{1 + \frac{R_2}{R_1 + R_2} A_1} \\ &= \frac{R_1 + R_2}{R_2} \frac{A_1}{\frac{R_1 + R_2}{R_2} + A_1}\end{aligned}$$

$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left(1 - \frac{R_1 + R_2}{R_2} \frac{1}{A_1}\right)$$



$$\text{Gain error} = \frac{1}{\beta A}$$

OPAMP Speed Requirement

OPAMP open-loop transfer function

$$A(s) = A_0 / (1 + s/\omega_0)$$

  For a small step input, calculate the time required it to reach within 1% of its final value if $1+R_1/R_2=10$. What is the required unity-gain bandwidth of the amplifier for it to achieve 5ns settling time? Assume A_0 is very large.





OPAMP Speed Requirement

$$[V_{in} - \beta V_{out}]A(s) = V_{out}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + \beta A(s)}$$
  
$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$



$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + \beta A(s)} = \frac{\frac{A_0}{1 + \frac{s}{\omega_0}}}{1 + \beta \left[\frac{A_0}{1 + \frac{s}{\omega_0}} \right]} = \frac{A_0}{1 + \frac{s}{\omega_0} + \beta A_0} = \frac{\frac{A_0}{[1 + \beta A_0]}}{1 + \frac{s}{[1 + \beta A_0]\omega_0}} \approx \frac{1}{\beta} \frac{1}{1 + \frac{s}{\beta A_0 \omega_0}} = \frac{A_{dc}}{1 + \tau s}$$

where $A_{dc} = \frac{1}{\beta}$, $\tau = \frac{1}{\omega_{-3dB,CL}} = \frac{1}{\beta A_0 \omega_0} = \frac{1}{\beta \omega_u}$

$$V_{out}(s) = \frac{A_{dc}}{1 + \tau s} V_{in}(s) = \frac{A_{dc}}{1 + \tau s} \cdot \frac{a}{s} = a A_{dc} \left[\frac{1}{s} - \frac{\tau}{1 + \tau s} \right] = a A_{dc} \left[\frac{1}{s} - \frac{1}{1 + \frac{s}{\tau}} \right]$$


$$\rightarrow V_{out}(t) = a A_{dc} [1 - e^{-\frac{t}{\tau}}] u(t)$$

For 1% settling, $1 - e^{-\frac{t}{\tau}} = 0.99 \rightarrow t_{1\%} = \tau \ln 100 \approx 4.6\tau = 5 \text{ ns} \rightarrow \tau = 1.09 \text{ ns}$


$$\rightarrow \tau = \frac{1}{\beta \omega_u} = \frac{10}{\omega_u} \rightarrow \omega_u = \frac{10}{1.09 \text{ ns}} = 9.21 \text{ G rad/s} \rightarrow f_u = 1.47 \text{ GHz}$$

Folded Cascode Circuits

[Razavi]

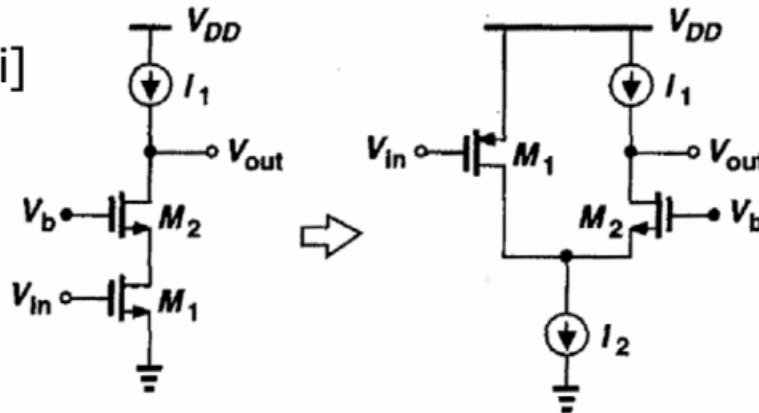


PMOS Input & NMOS Cascode

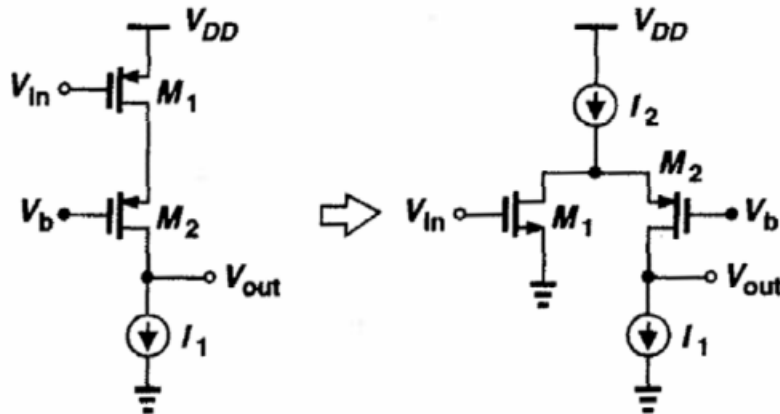


NMOS Input & PMOS Cascode

- "Folding" about the cascode node will increase input and output swing range


Folded Cascode OTA

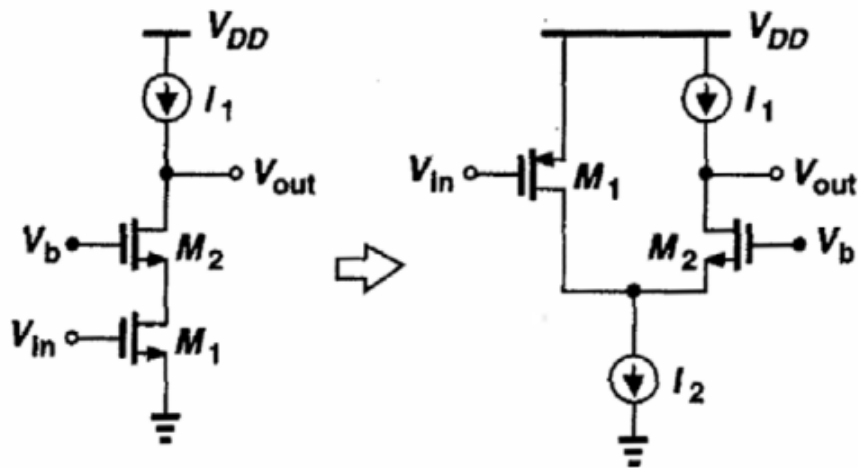

[Razavi]


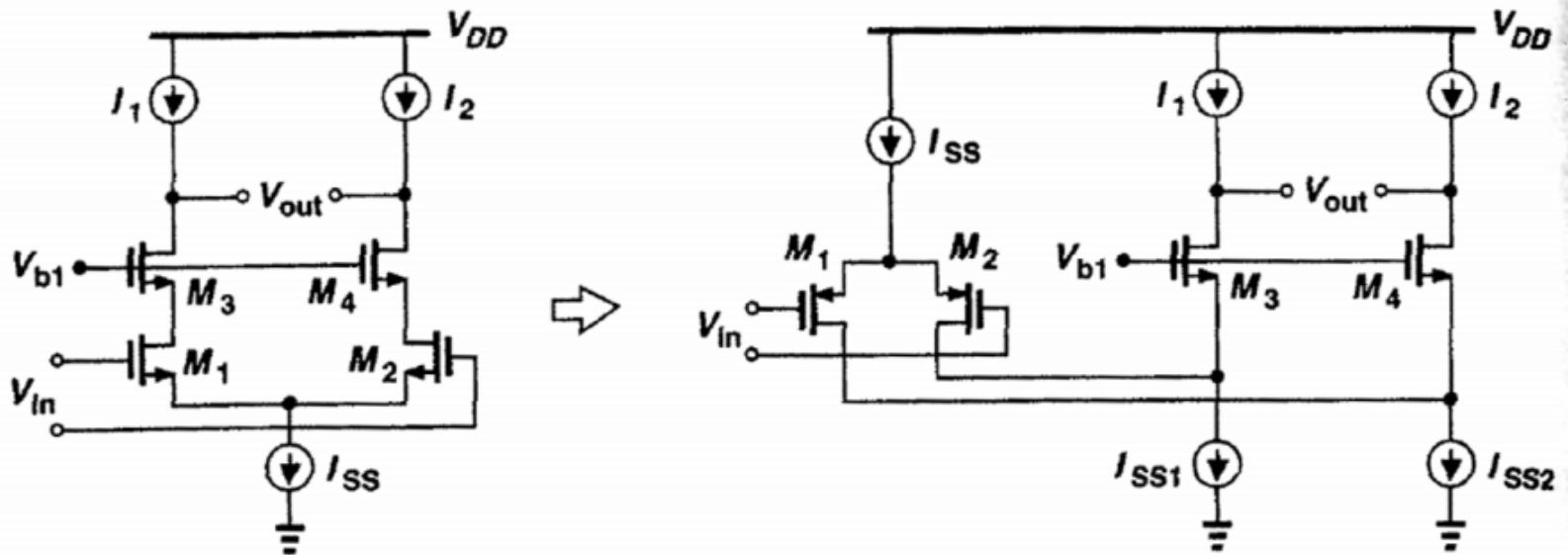


Folded Cascode OPAMP

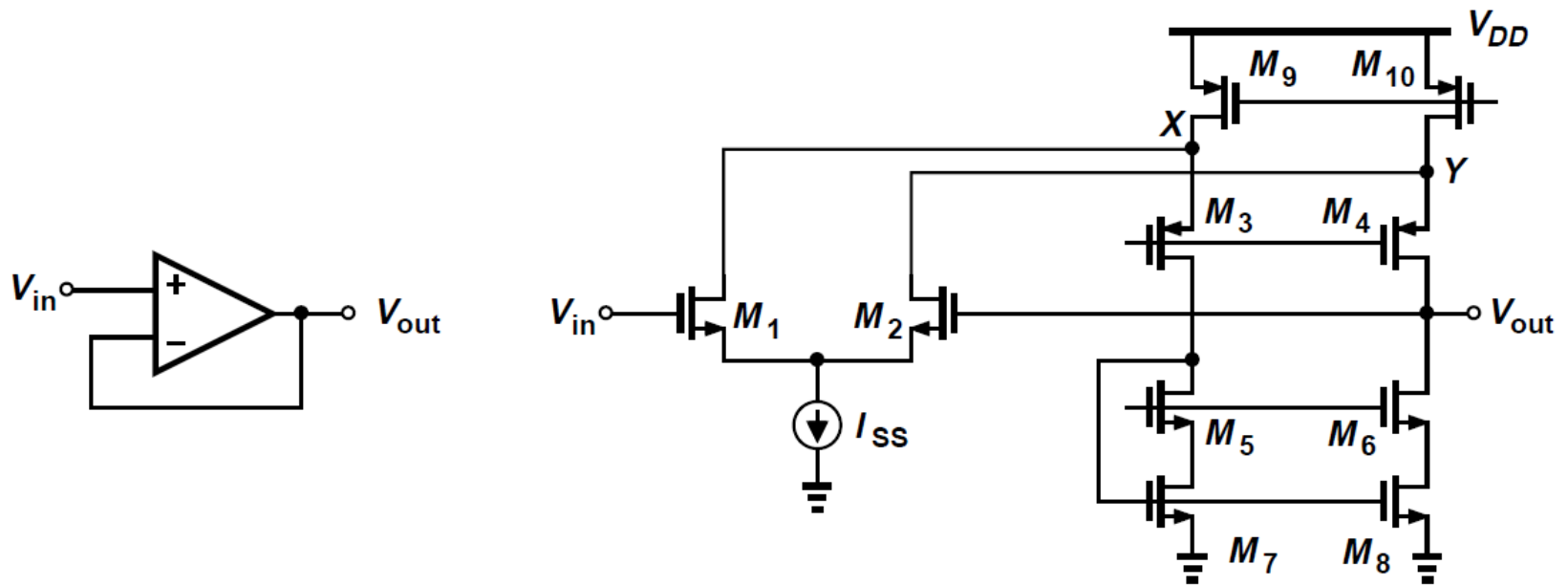


NMOS vs PMOS Input

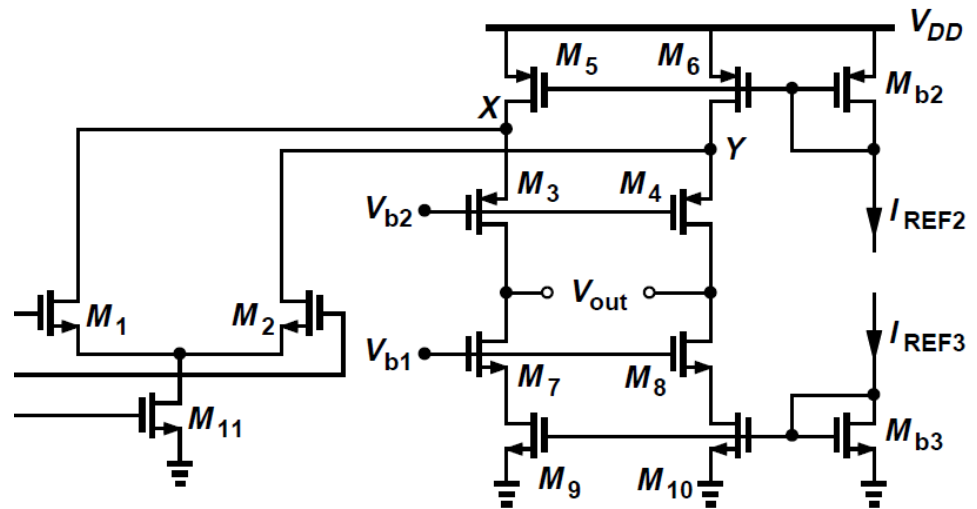 - Greater mobility from NMOS input leads to higher gain
- PMOS input is less sensitive to flicker noise (wider WL)
- Usually input common-mode level dictates which input to use




Multi-Stage Amplifiers

 

- Single-stage amplifiers typically have to trade-off gain and swing range
- Multi-stage amplifiers allow for higher gain without sacrificing swing range
- The major challenge with multi-stage amplifiers is achieving adequate phase margin to insure stability in a feedback configuration

Stability

Negative Feedback and Phase Shift

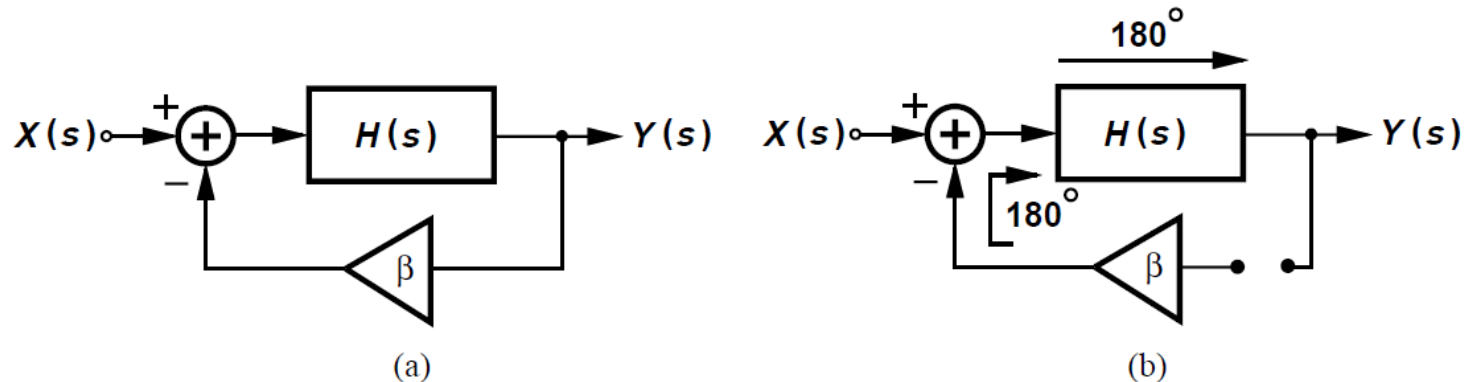


- Feedback systems suffer from potential instability and they may oscillate.
- Closed-loop transfer function: $\frac{Y}{X}(s) = \frac{H(s)}{1 + \beta H(s)}$
- What happens if the denominator goes to infinity

$$|\beta H(j\omega_1)| = 1 \quad \text{“Barkhausen’s criteria”}$$

$$\angle \beta H(j\omega_1) = -180^\circ$$


- Negative feedback itself provide 180 phase shift
- Loop transmission determines the stability issue

Bode Plots of Loop Gain

 


- Phase shift changes the negative feedback to positive
- Gain crossover when gain is unity
- Phase crossover when phase is -180 degrees
- PX must be behind GX, and GX is equal to unity-gain bandwidth in the open-loop system

One-Pole System – Unconditionally Stable

 

$$H(s) = A_0 / (1 + s/\omega_0)$$
$$\frac{Y}{X}(s) = \frac{\frac{A_0}{1 + \beta A_0}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}}$$



Multi-Pole System

 

- The system is stable if phase is less than -180 degrees at gain crossover
- If the feedback becomes weaker, the system is more stable

Phase Margin

How far should PX be from GX?

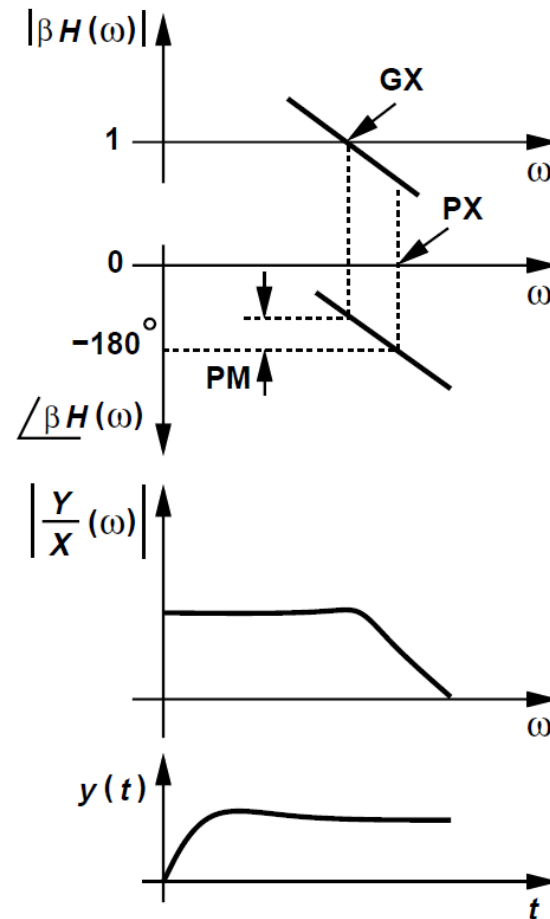 

Phase Margin

- Phase Margin(PM), defined as

$$\text{PM} = 180^\circ + \angle \beta H(\omega = \omega_1)$$

- A “well-behaved” closed-loop response will have a greater spacing between GX and PX
- The unity-gain bandwidth cannot exceed the second pole frequency
- For large-signal application, time-domain simulation of closed-loop system more relevant and useful than small-signal as computations

Phase Margin Comparison





- How much phase margin is adequate?

PM = 45 degrees

$$\begin{aligned}\frac{Y}{X} &= \frac{H(j\omega_1)}{1 + 1 \times \exp(-j135^\circ)} \\ &= \frac{H(j\omega_1)}{0.29 - 0.71j} \approx \frac{1.3}{\beta}\end{aligned}$$


PM = 60 degrees

$$Y(j\omega_1)/X(j\omega_1) = 1/\beta$$

    

Step Response and Phase Margin

 Consider the step response of second-order system which closely models the closed-loop gain of the op amp connected in unity gain.



A “good” step response is one that quickly reaches its final value.


Therefore, we see that phase margin should be at least 45° and preferably 60° or larger.

(A rule of thumb for satisfactory stability is that there should be less than three rings.)


Note that good stability is not necessarily the quickest rise time.

Basic Frequency Compensation

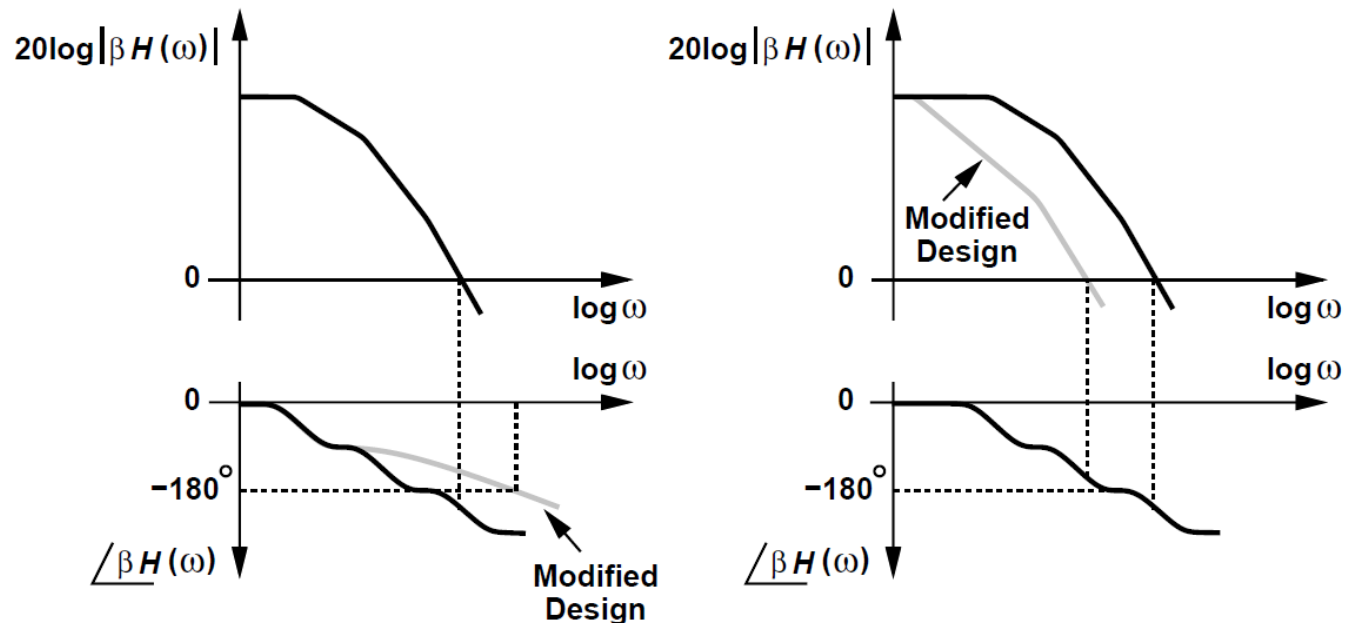
- Be “compensated”, the circuit open-loop transfer function must be modified such that closed-loop circuit is stable
 - minimizing the overall phase shift
 - dropping the gain with frequency





Miller Compensation

 

 - A larger C creating a dominating pole $R_{out1}^{-1}[C_E + (1 + A_{v2})C_C]^{-1}$
- Pole splitting



Two-Stage OPAMP with Miller Compensation

 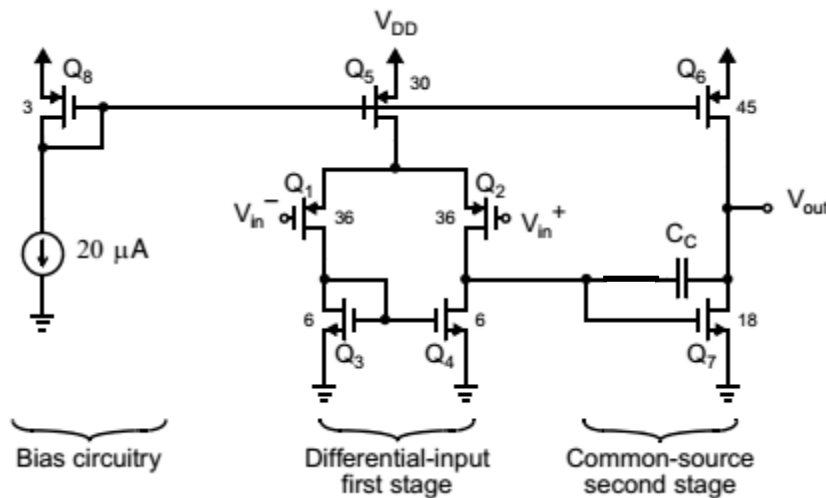

$$A(s) = \frac{A_0(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})}$$

$$A_{v1} = -g_{m1}(r_{ds2} \parallel r_{ds4})$$

$$A_{v2} = -g_{m7}(r_{ds6} \parallel r_{ds7})$$

$$R_1 = r_{ds4} \parallel r_{ds2}$$

$$C_1 = C_{db2} + C_{db4} + C_{gs7}$$

$$R_2 = r_{ds6} \parallel r_{ds7}$$

$$C_2 = C_{db7} + C_{db6} + C_{L2}$$



$$A_v(s) = \frac{V_{out}}{V_{in}} = \frac{g_{m1}g_{m7}R_1R_2\left(1 - \frac{sC_C}{g_{m7}}\right)}{1 + sa + s^2b}$$

$$a = (C_2 + C_C)R_2 + (C_1 + C_C)R_1 + g_{m7}R_1R_2C_C$$

$$b = R_1R_2(C_1C_2 + C_1C_C + C_2C_C)$$

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right) \cong 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$$

Two-Stage OPAMP with Miller Compensation

 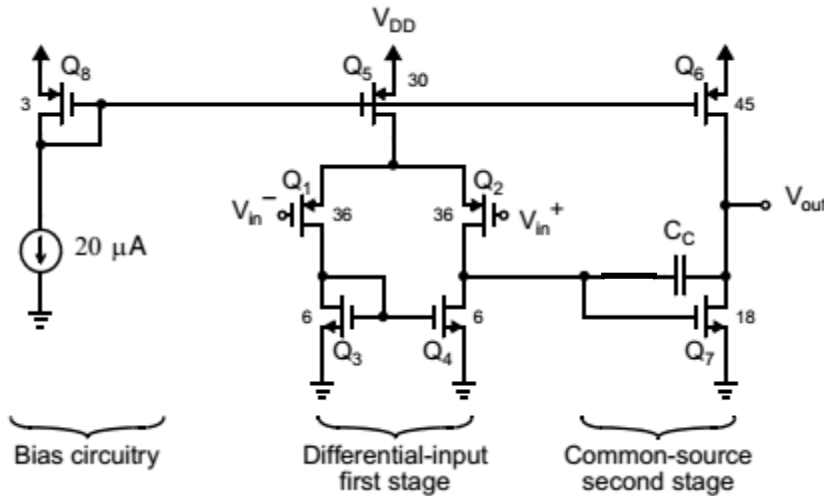

$$A(s) = \frac{A_0(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})}$$

$$A_{v1} = -g_{m1}(r_{ds2} \parallel dr_{ds4})$$

$$A_{v2} = -g_{m7}(r_{ds6} \parallel r_{ds7})$$

$$\begin{aligned} \omega_{p1} &\cong \frac{1}{R_1[C_1 + C_C(1 + g_{m7}R_2)] + R_2(C_2 + C_C)} \\ &\cong \frac{1}{R_1C_C(1 + g_{m7}R_2)} \\ &\cong \frac{1}{g_{m7}R_1R_2C_C} \end{aligned}$$


$$\begin{aligned} \omega_{p2} &\cong \frac{g_{m7}C_C}{C_1C_2 + C_2C_C + C_1C_C} \\ &\cong \frac{g_{m7}}{C_1 + C_2} \end{aligned}$$

$$\omega_z = \frac{-g_{m7}}{C_C} \quad \leftarrow \text{RHP Zero due to } C_C$$

$$\begin{aligned} \text{GBW} = \omega_u &= (A_{v1}A_{v2}) \left(\frac{1}{R_1A_{v2}C_C} \right) \\ &= \frac{A_{v1}}{R_1C_C} = \frac{g_{m1}R_1}{R_1C_C} = \boxed{\frac{g_{m1}}{C_C}} \end{aligned}$$

Two-Stage OPAMP with RC Compensation


2-stage opamp

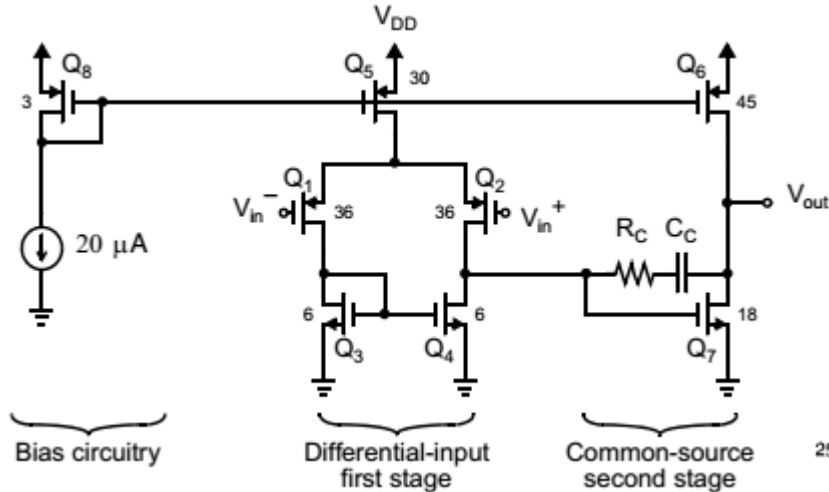

$$A(s) = \frac{A_0(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})}$$

$$\omega_z = \frac{-1}{C_c(\frac{1}{g_{m7}} - R_c)}$$

2-stage opamp with output stage

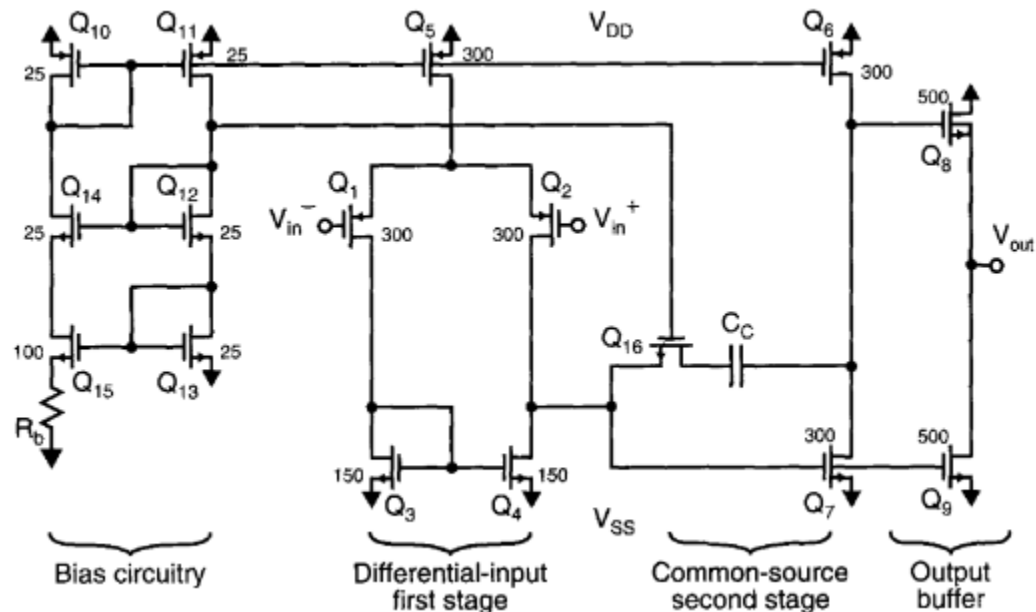

Choice of R_c

$$A(s) = \frac{A_0(1 + \frac{s}{\omega_z})}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})}$$

$$\omega_z = \frac{-1}{C_c(\frac{1}{g_{m7}} - R_c)}$$

- $R_c = 0 \rightarrow \omega_z = \frac{-1}{C_c(\frac{1}{g_{m7}})} = \frac{-g_{m7}}{C_c} \rightarrow$ **RHP Zero ! Stability Issue**

- $R_c = \frac{1}{g_{m7}} \rightarrow \omega_z = \infty$

- $R_c > \frac{1}{g_{m7}}$


$$\rightarrow \omega_z = \omega_{p2}$$

$$\frac{-1}{C_c(\frac{1}{g_{m7}} - R_c)} = \frac{g_{m7}}{C_1 + C_2}$$

$$\rightarrow R_c = \frac{1}{g_{m7}} \left(1 + \frac{C_1 + C_2}{C_c} \right)$$


- $R_c \gg \frac{1}{g_{m7}}$
 
$$\omega_z \approx \frac{1}{R_c C_c} = \alpha \omega_u = \alpha \frac{g_{m1}}{C_c}$$



Choosing $\alpha = 2$ is a good starting point.

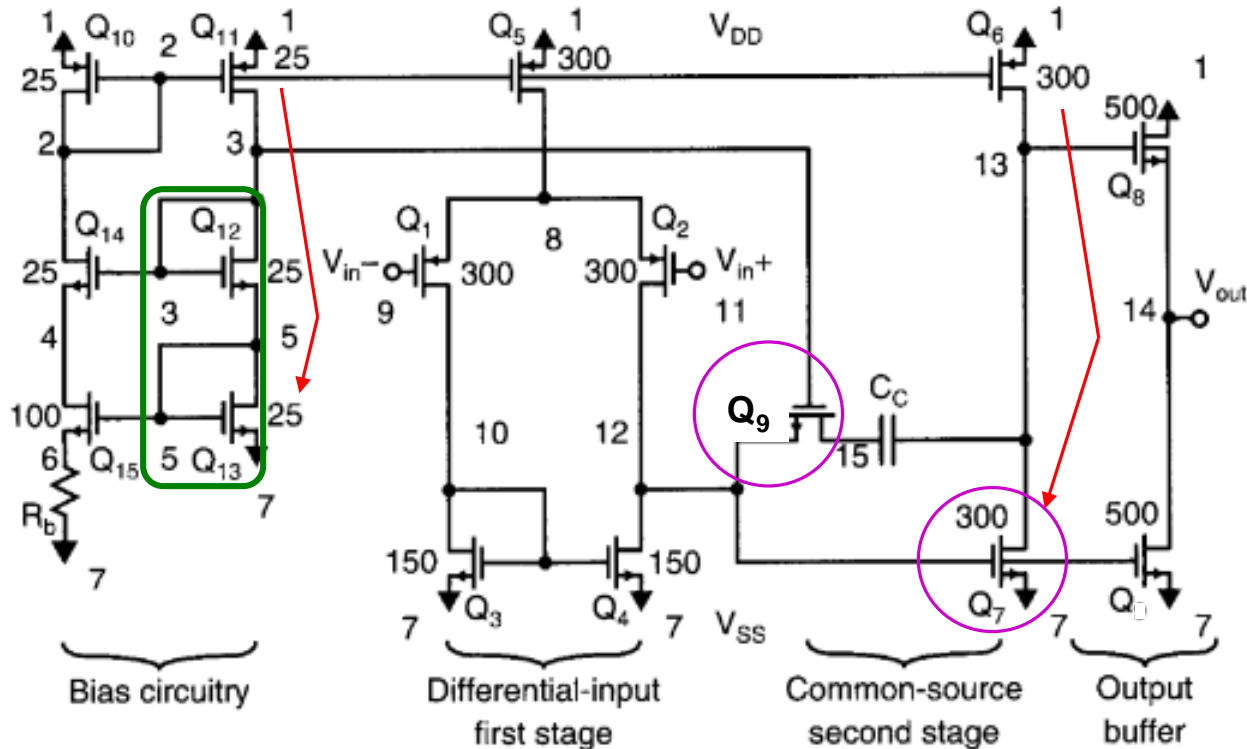Conclusion for Replacing R_z with Transistor




1. $\frac{(W/L)_6}{(W/L)_7} = \frac{(W/L)_{11}}{(W/L)_{13}}$
2. $(\frac{W}{L})_{12} = (\frac{W}{L})_{13}$
3. $(\frac{W}{L})_9 = 0.2 (\frac{W}{L})_7$


Output Stages

Two-Stage OPAMP with SF Output Stage


2-stage opamp

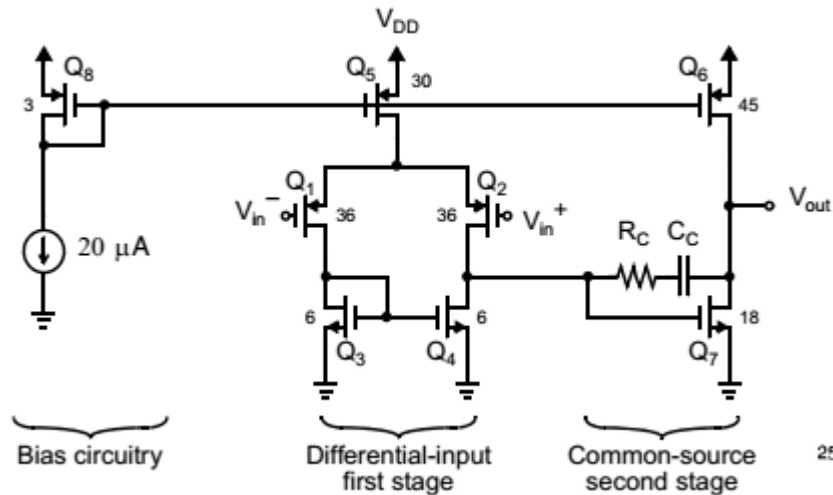


2-stage opamp with output stage

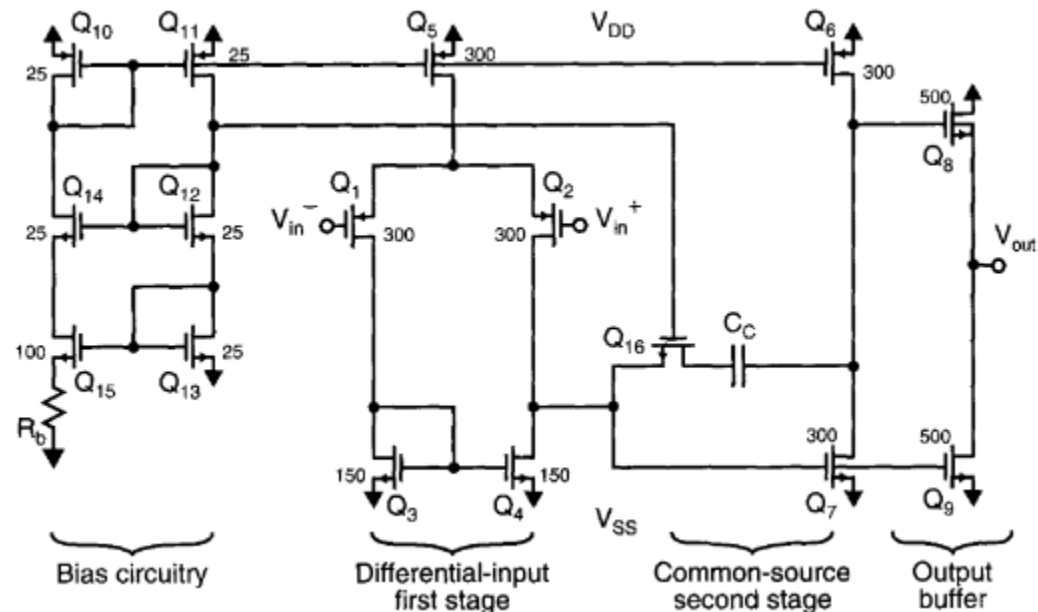

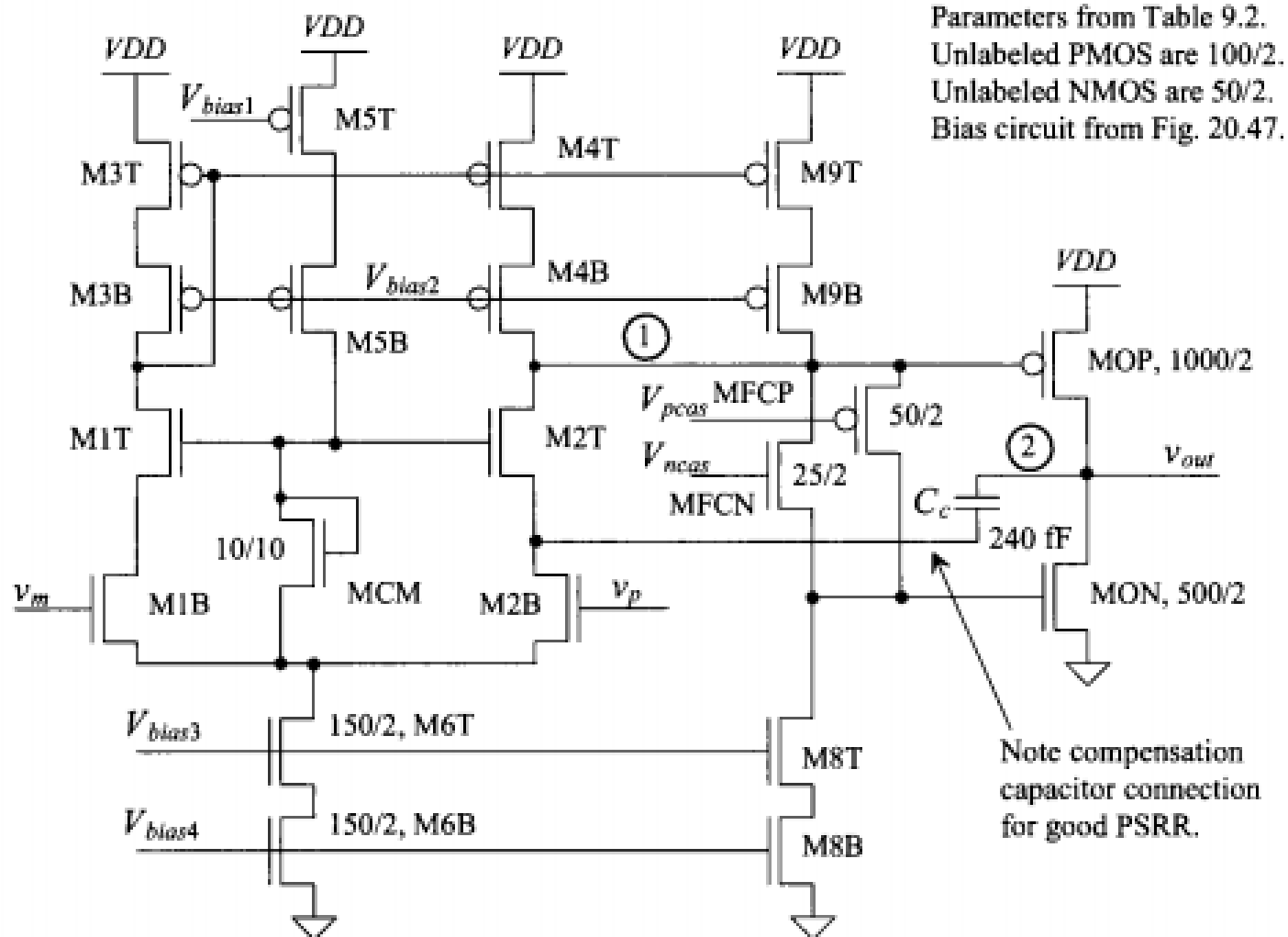Two-Stage OPAMP with Class AB Output Stage



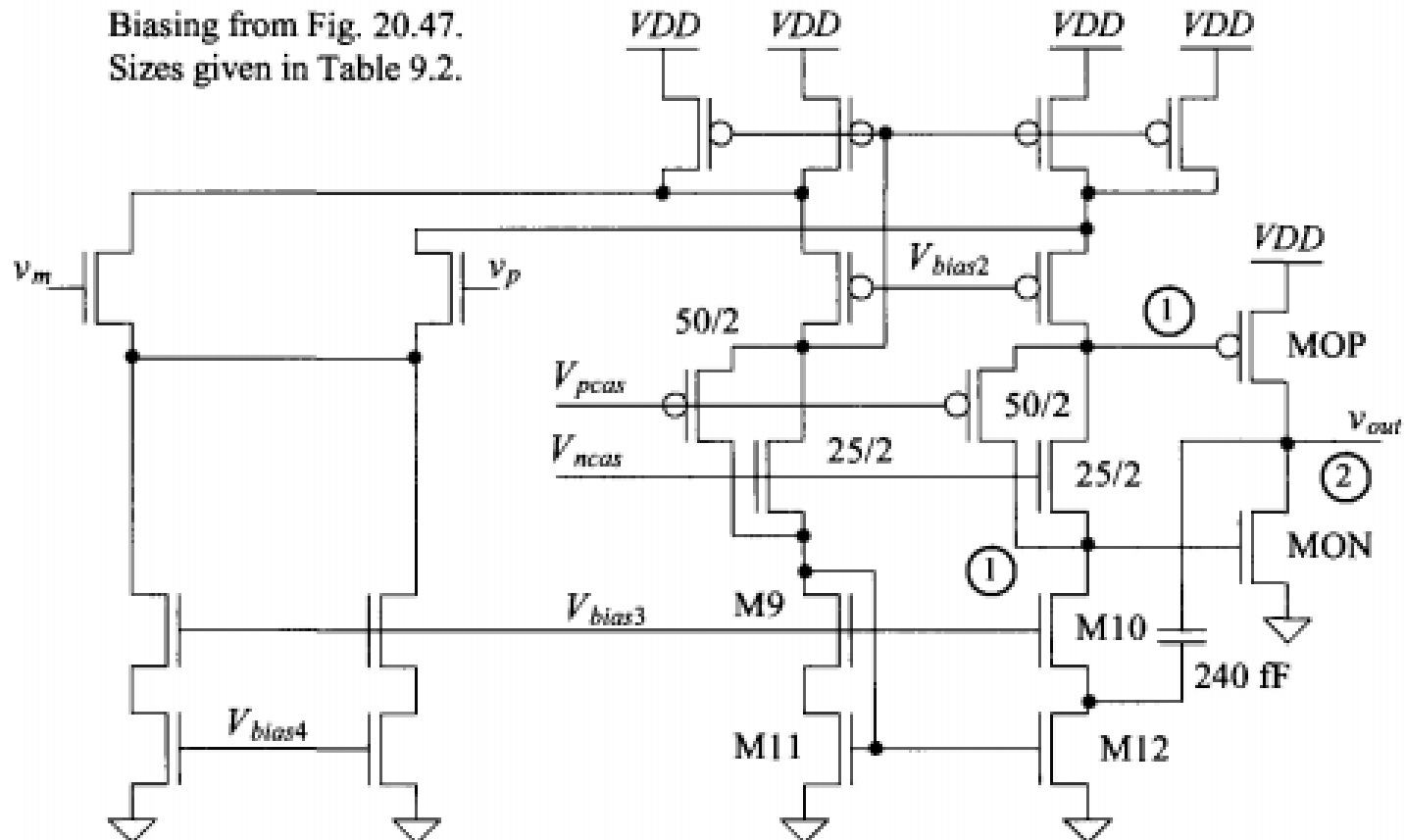
Folded-Cascode OPAMP with Class AB Output Stage



Gain Boosting

Gain Boosting

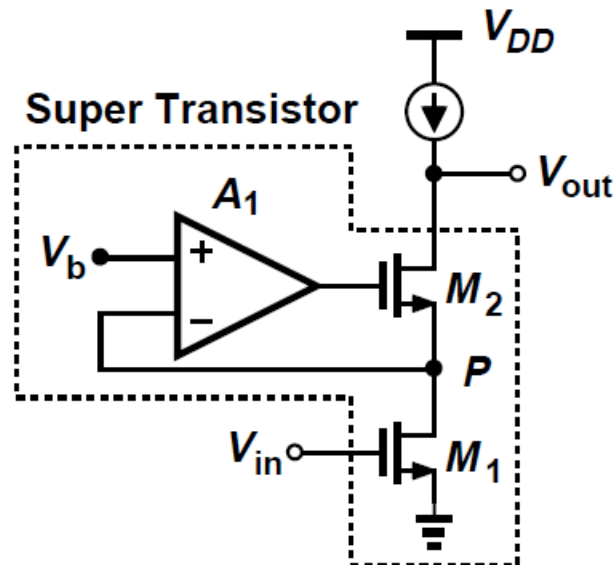- Increase the output impedance without adding more cascode devices.
- A transistor preceded by an ideal voltage amplifier exhibits an effective transconductance of $g_m \cdot A_1$




$$\begin{aligned}
 |A_v| &\approx g_{m1}[r_{O2} + (A_1 + 1)g_{m2}r_{O2}r_{O1} + r_{O1}] \\
 &\approx g_{m1}g_{m2}r_{O1}r_{O2}(A_1 + 1).
 \end{aligned}$$

Gain Boosting Circuit Implementation



- Simplest is a common-source stage

$$|V_{out}/V_{in}| \approx g_{m1}r_{O1}g_{m2}r_{O2}(g_{m3}r_{O3} + 1)$$

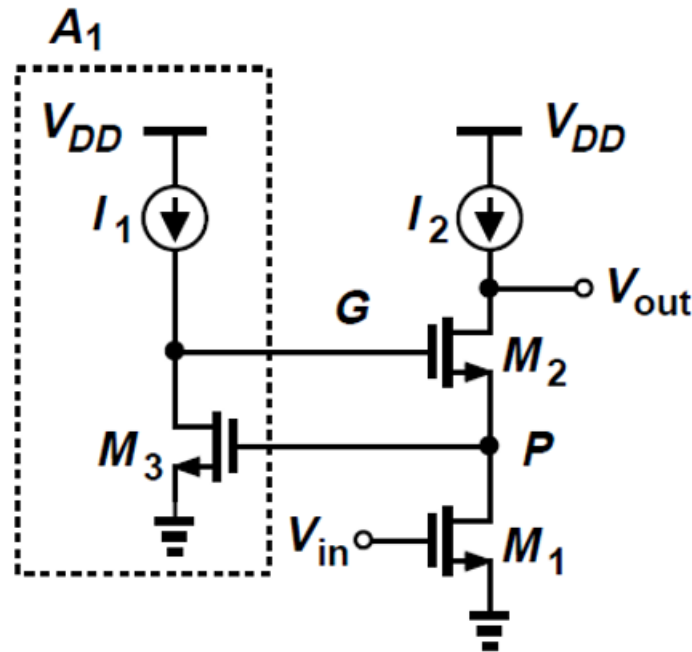


Gain Boosting in Signal Path and Load

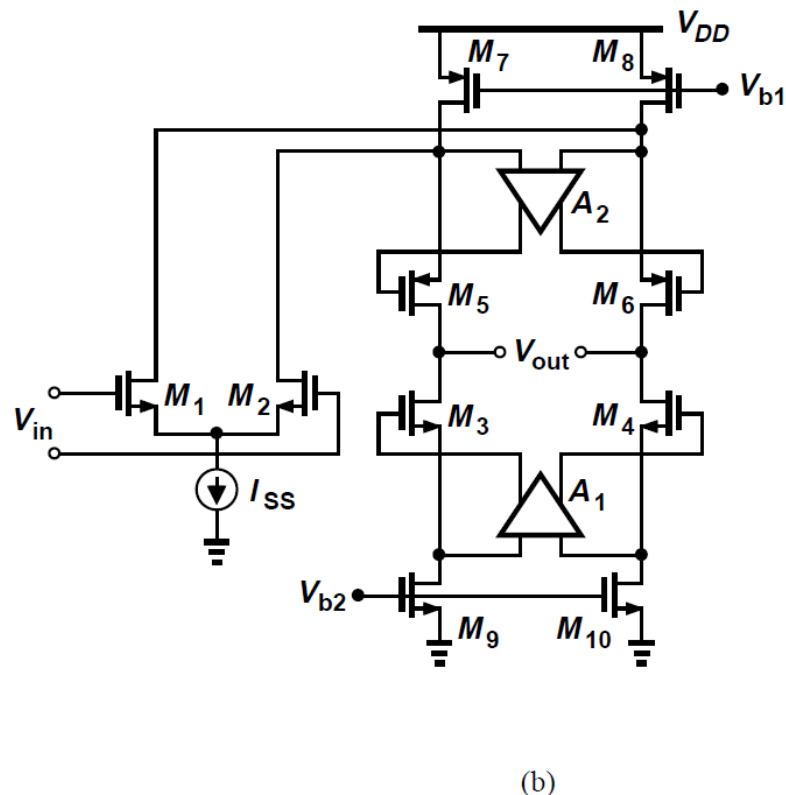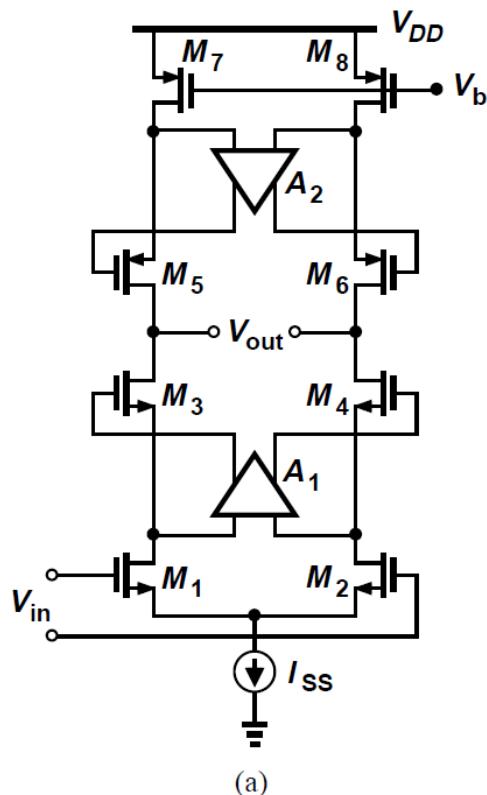
- Gain boosting can be utilized in the load current source
- To allow maximum swings, A_2 employs NMOS-input



Gain Boosting Amp Choice

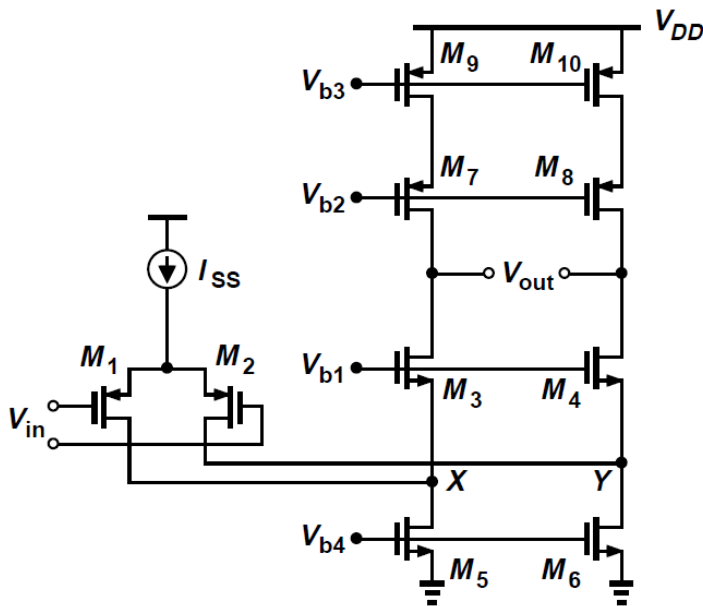


Good for Lower Common-Mode Input

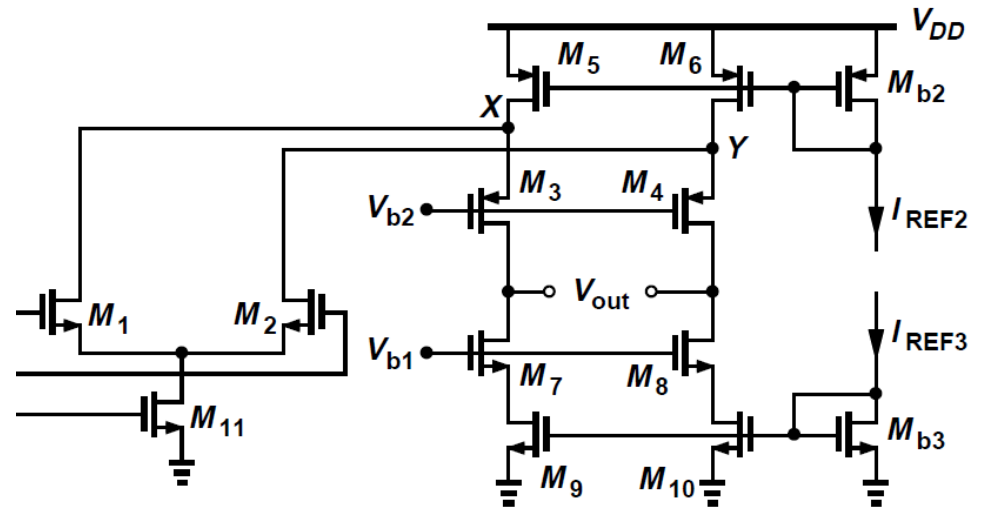

Good for Higher Common-Mode Input

Fully Differential Amplifiers


Fully Differential Amplifier

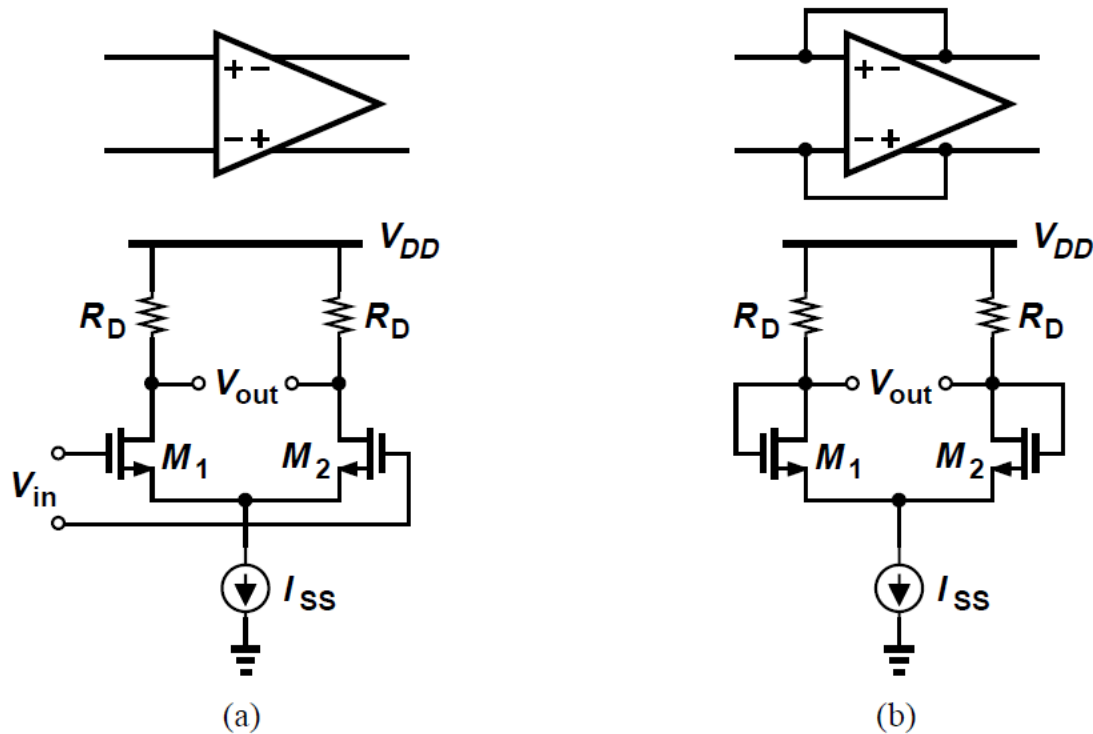


- $V_{cm(in)}$ and $V_{cm(out)}$: $V_{DD} - I_{SS}R_D/2$

Common-Mode Basic Concepts

 - In fully-differential op amps, the output CM level is usually not well defined.
 - Case 1: $I_{D3,4} < I_{SS}/2$, V_x, V_y decreases, I_{SS} triode;
 - Case 2: In reverse, V_x, V_y increases, M_3, M_4 triode.




(a)

 


(b)

Differential Pair Common-Mode Sensing

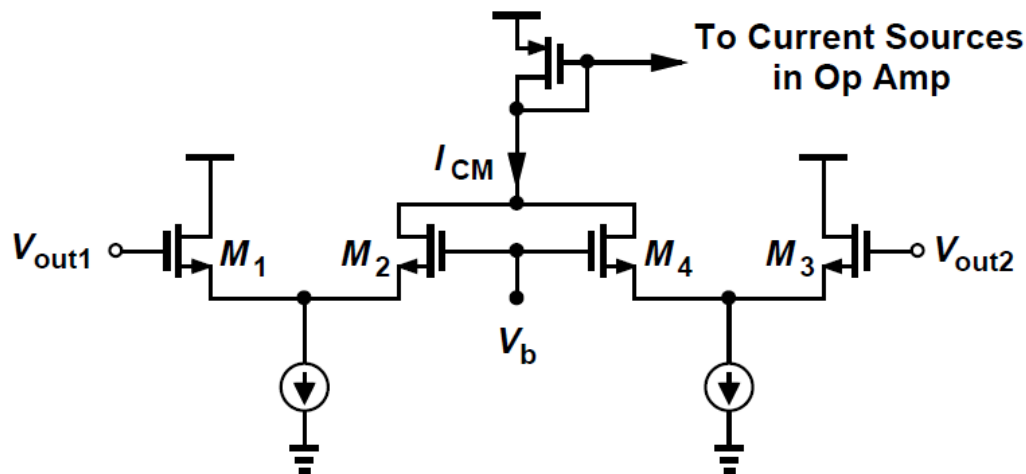
- $I_{CM} \propto V_{out1} + V_{out2}$ by small signal analysis
- Under Large swings situation, sensing is not valid due to large non-linearity.



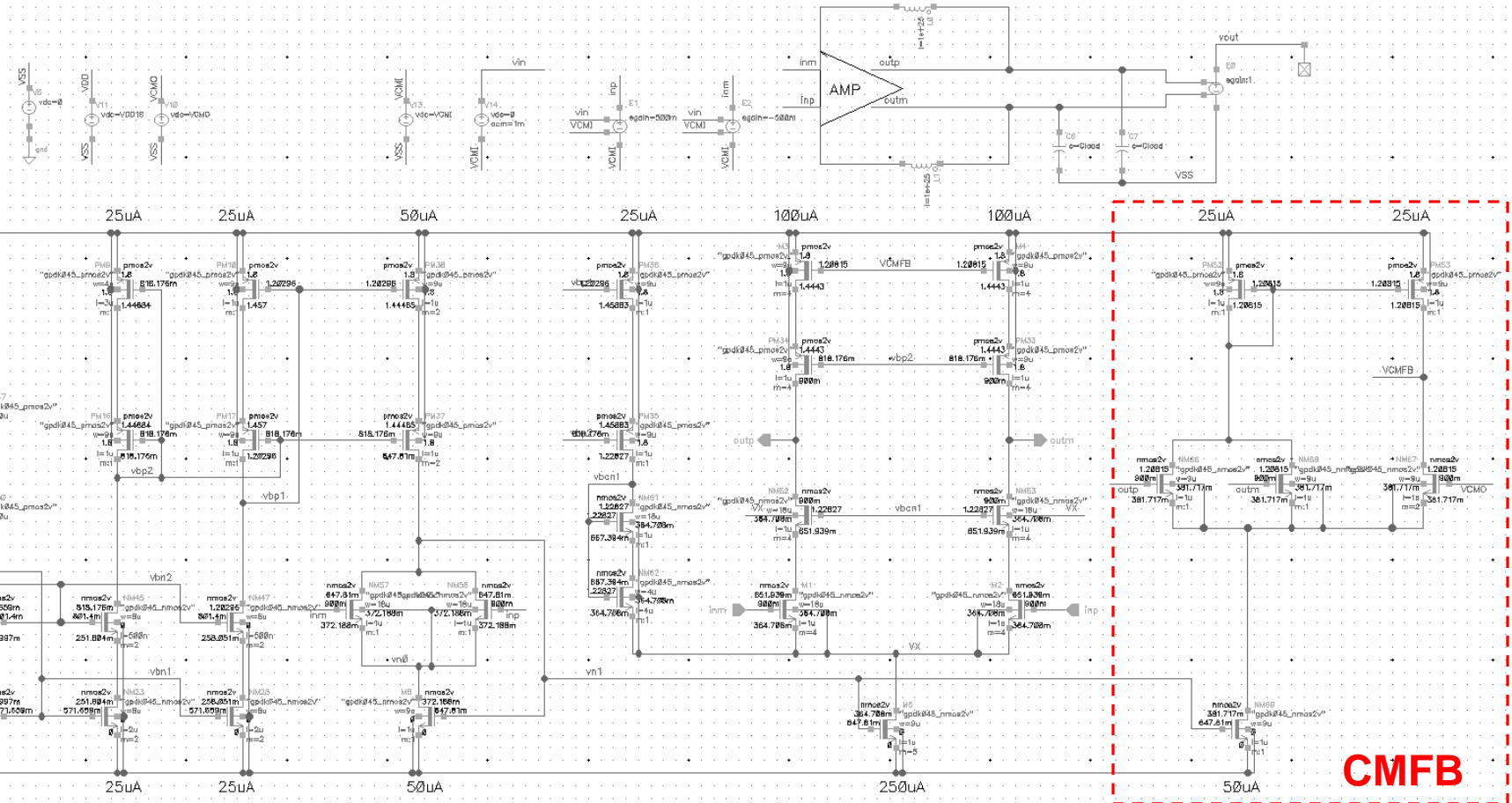Fully Differential Telescopic OTA with CMFB



Switched-Capacitor CMFB

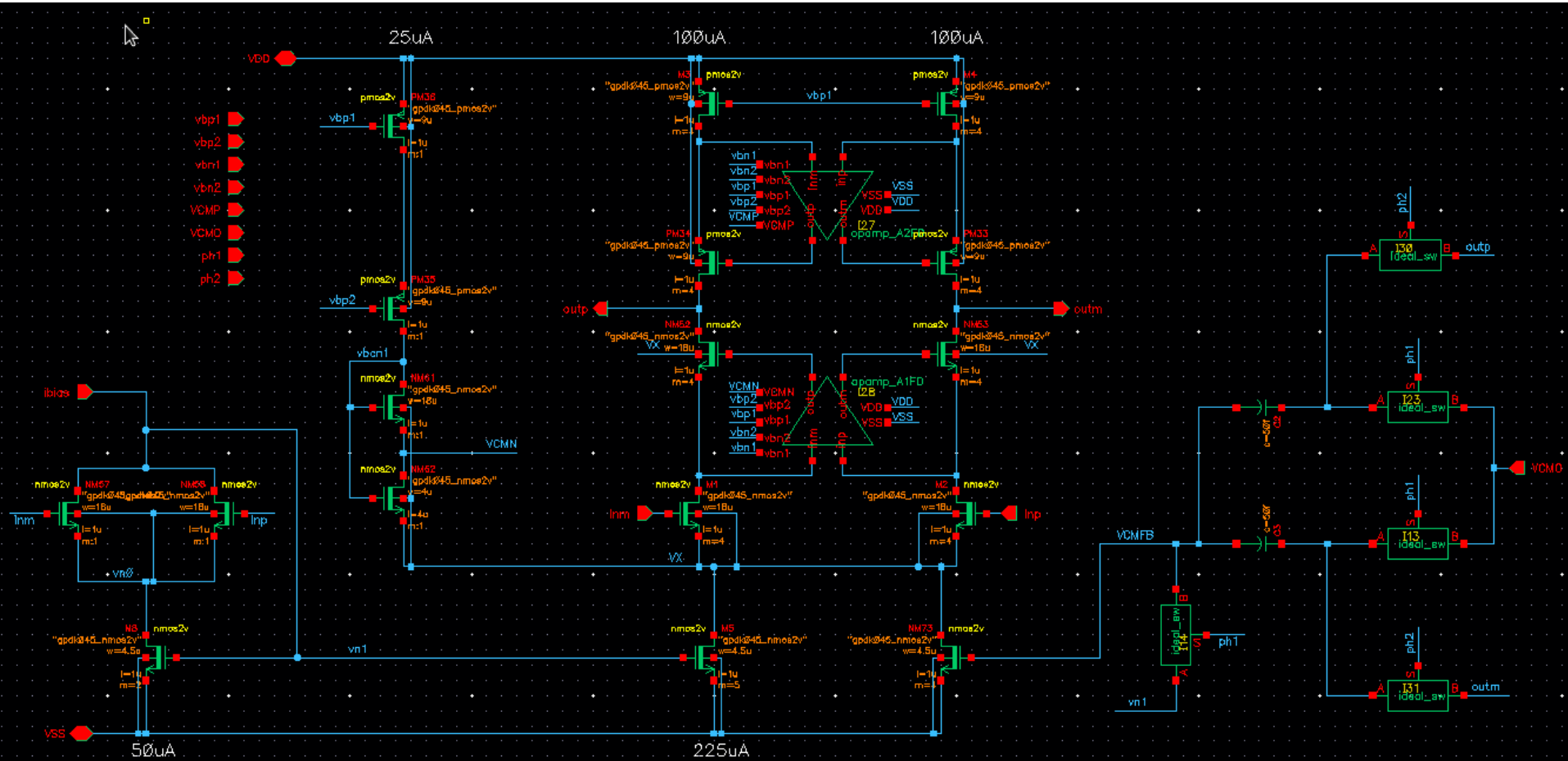



Noise

Resistor Thermal Noise


- Random motion of electrons in a conductor induces fluctuations in the voltage measured across it even though the average current is zero
- Thermal noise of a resistor R can be modeled by a series voltage source, with one-sided spectral density

$$S_v(f) = 4kTR, \quad f \geq 0$$

  - Here, $k = 1.38 \times 10^{-23}$ J/K is the Boltzmann constant
- $S_v(f)$ is expressed in V^2/Hz , we also write $\overline{V_n^2} = 4kTR$
- For a 50- Ω resistor at $T = 300$ K, thermal noise is 8.28×10^{-19} V^2/Hz , or 0.91 nV/ $\sqrt{\text{Hz}}$ **1kohm-> 4 nV/ $\sqrt{\text{Hz}}$**
- $S_v(f)$ is flat up to 100 THz, and is “white” for our purposes




Noise generated by R, but depends on C

 

$$v_{total}^2 = \int_0^{\infty} \left(\frac{1}{1 + (\omega RC)^2} \right) (4kTR) df = \frac{kT}{C}$$

 To get more insight, lets have a closer look on the operations!



Notice that:

When R increases thermal noise increases too but the corner frequency decreases, leading to a constant area under the curves!


- kT/C noise can only be decreased by increasing C (if T is fixed)

MOSFET Thermal Noise


- MOS transistors exhibit thermal noise with the most significant source being the **noise generated in the channel**
- For long-channel MOS devices operating in saturation, the channel noise can be modeled by a current source connected between the drain and source terminals with a spectral density

$$\overline{I_n^2} = 4kT\gamma g_m$$

 - The coefficient ' γ ' (not the body effect coefficient) is derived to be **2/3 for long-channel transistors** and is higher for submicron MOSFETs




MOSFET Thermal Noise

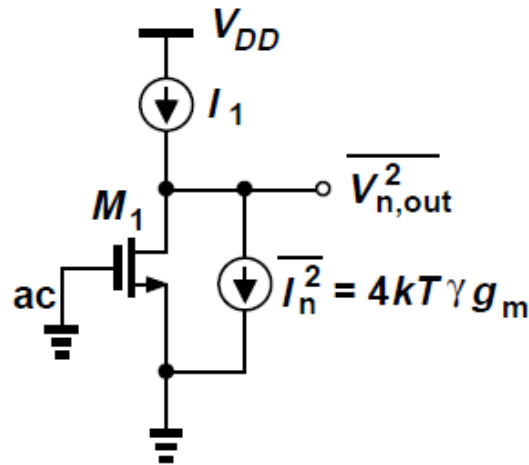

- Noise current of a MOS transistor decreases if the transconductance drops
- Noise measured at the output of the circuit does not depend on where the input terminal is because input is set to zero for noise calculation
- The output resistance r_o does not produce noise because it is not a physical resistor

MOSFET Flicker Noise

 

- At the interface between the gate oxide and silicon substrate, many “dangling” bonds appear, giving rise to extra energy states
- Charge carriers moving at the interface are randomly trapped and later released by such energy states, introducing “flicker” noise in the drain current
- Other mechanisms in addition to trapping are believed to generate flicker noise


MOSFET Flicker Noise

- Average power of flicker noise cannot be predicted easily
- It varies depending on cleanness of oxide-silicon interface and from one CMOS technology to another
- Flicker noise is more easily modeled as a voltage source in series with the gate and in the saturation region, is roughly given by

$$\overline{V_n^2} = \frac{K}{C_{ox}WL} \cdot \frac{1}{f}$$

- K is a process-dependent constant on the order of $10^{-25} \text{ V}^2\text{F}$


MOSFET Flicker Noise

 


- The noise spectral density is inversely proportional to frequency
 - Trap and release phenomenon occurs at low frequencies more often
- Flicker noise is also called “ $1/f$ ” noise
- To reduce $1/f$ noise, device *area* must be increased
- Generally, PMOS devices exhibit less $1/f$ noise than NMOS transistors
 - Holes are carried in a “buried” channel, at some distance from the oxide-silicon interface

Flicker Noise Corner Frequency

 
- At low frequencies, the flicker noise power approaches infinity
- Intersection point of thermal noise and flicker noise spectral densities is called “corner frequency” f_C



 Representation of Noise in Circuits Example



(a)

 

(b)

- To find: Total output noise voltage of common-source stage [Fig. (a)]
- Follow noise analysis procedure described earlier
- Thermal and flicker noise of M1 and thermal noise of R_D are modeled as current sources [Fig. (b)]

$$\overline{I_{n,th}^2} = 4kT\gamma g_m$$


$$\overline{I_{n,1/f}^2} = K g_m^2 / (C_{ox} W L f)$$

$$\overline{I_{n,RD}^2} = 4kT / R_D$$

- Output noise voltage per unit bandwidth, added as power quantities is

$$\overline{V_{n,out}^2} = \left(4kT\gamma g_m + \frac{K}{C_{ox} W L} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2$$

Input-Referred Noise

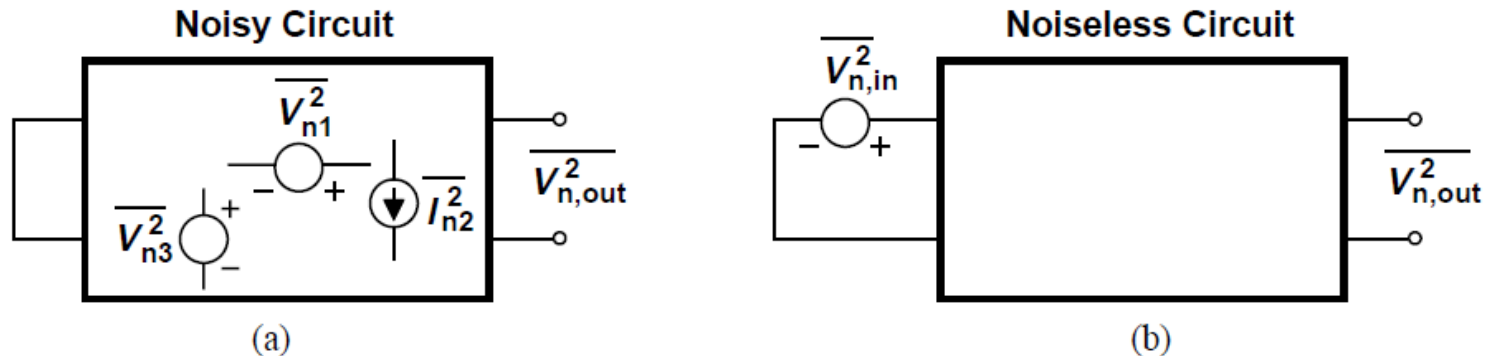


- Input-referred noise represents the effect of all noise sources in the circuit by a single source $\overline{V_{n,in}^2}$, at the input such that the output noise in Fig. (b) is equal to that in Fig. (a)
- If the voltage gain is A_v , then we must have


$$\overline{V_{n,out}^2} = A_v^2 \overline{V_{n,in}^2}$$

- The input-referred noise voltage in this simple case is simply the output noise divided by the gain squared.

Input-Referred Noise Example

 

(a)

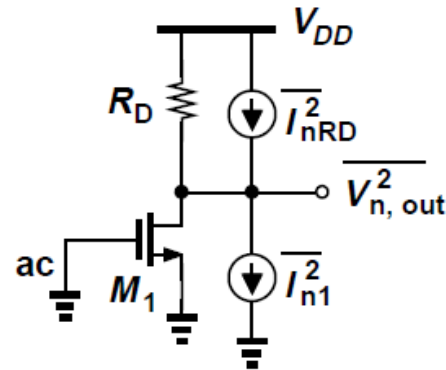


(b)


- For the simple CS stage, the input-referred noise voltage is given by

$$\begin{aligned}
 \overline{V_{n,in}^2} &= \frac{\overline{V_{n,out}^2}}{A_v^2} \\
 &= \left(4kT\gamma g_m + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2 \frac{1}{g_m^2 R_D^2} \\
 &= 4kT \frac{\gamma}{g_m} + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} + \frac{4kT}{g_m^2 R_D}.
 \end{aligned}$$

Common-Source Noise at the Output

 

(a)

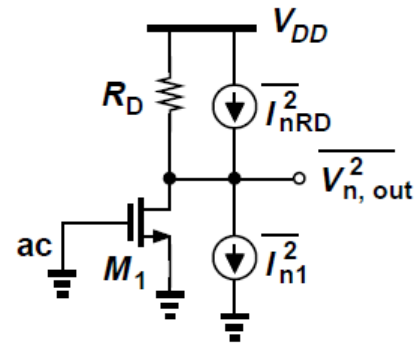

(b)


$$\overline{I_{n,th}^2} = 4kT\gamma g_m$$

$$\overline{I_{n,1/f}^2} = K g_m^2 / (C_{ox} W L f)$$


$$\overline{I_{n,RD}^2} = 4kT / R_D$$

$$\overline{V_{n,out}^2} = \left(4kT\gamma g_m + \frac{K}{C_{ox} W L} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2$$

Common-Source Input-Referred Noise

 


(a)

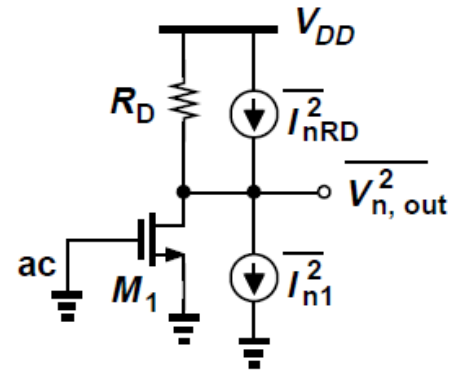

(b)


$$\begin{aligned}
 \overline{V_{n,in}^2} &= \frac{\overline{V_{n,out}^2}}{A_v^2} \\
 &= \left(4kT\gamma g_m + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2 \frac{1}{g_m^2 R_D^2} \\
 &= 4kT \frac{\gamma}{g_m} + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} + \frac{4kT}{g_m^2 R_D}.
 \end{aligned}$$

Cascode Stage

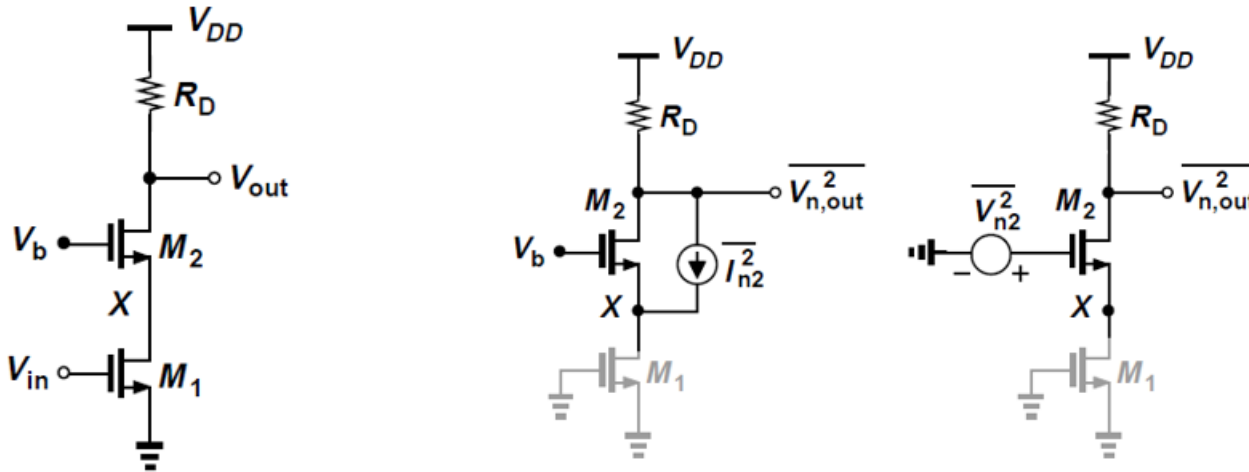

- M_2 contributes negligibly to noise at the output,
- Voltage gain from V_{n2} to the output is small if impedance at node X is large

Noise in Five-Transistor OTA

 

- The noise current of M_3 primarily circulates through the diode-connected impedance $1/g_{m3}$, producing a voltage at the gate of M_4 with spectral density $4kT\gamma/g_{m3}$

- This noise is multiplied by g_{m4}^2 as it emerges from the drain of M_4 ; the noise current of M_4 also flows directly through the output short-circuit, thus

$$\overline{I_{n,out}^2} = 4kT\gamma(2g_{m1,2} + 2g_{m3,4})$$


- Multiplying this noise by $R_{out}^2 \approx (r_{O1,2} || r_{O3,4})^2$ and dividing the result by $A_v^2 = G_m^2 R_{out}^2$, the total input-referred noise is

$$\overline{V_{n,in}^2} = 8kT\gamma \left(\frac{1}{g_{m1,2}} + \frac{g_{m3,4}}{g_{m1,2}^2} \right)$$

Noise in Telescopic OPAMP

- At low frequency the cascode devices contribute negligible noise

 
$$\overline{V_n^2} = 4kT \left(2 \frac{\gamma}{g_{m1,2}} + 2 \frac{\gamma g_{m7,8}}{g_{m1,2}^2} \right) + 2 \frac{K_N}{(WL)_{1,2} C_{ox} f} + 2 \frac{K_P}{(WL)_{7,8} C_{ox} f} \frac{g_{m7,8}^2}{g_{m1,2}^2}$$




Noise in Folded-Cascode OPAMP

- At low frequency the cascode devices contribute negligible noise
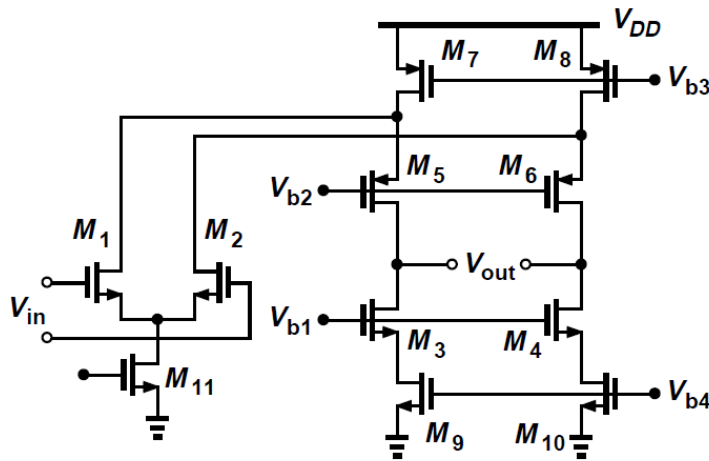
$$\overline{V_{n,int}^2} = 8kT \left(\frac{\gamma}{g_{m1,2}} + \gamma \frac{g_{m7,8}}{g_{m1,2}^2} + \gamma \frac{g_{m9,10}}{g_{m1,2}^2} \right)$$



(a)

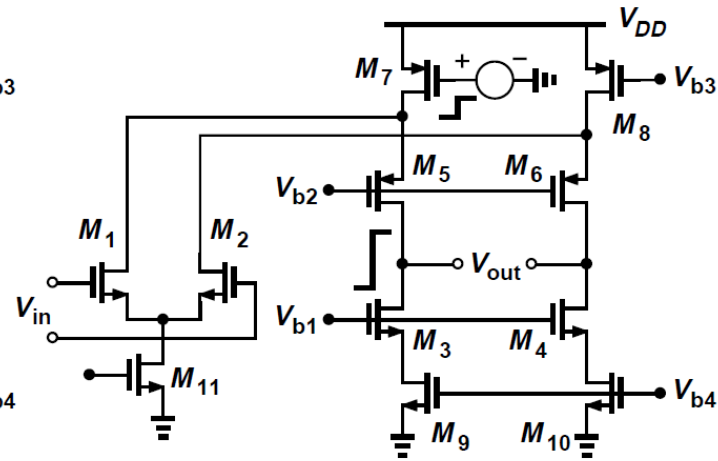


(b)

Noise in Two-Stage OPAMP

- The noise in the second stage contributes negligible noise

 
$$\overline{V_{n,tot}^2} = 8kT\gamma \frac{1}{g_{m1}^2} \left[g_{m1} + g_{m3} + \frac{g_{m5} + g_{m7}}{g_{m5}^2 (r_{O1} \parallel r_{O3})^2} \right]$$



Switched-Capacitor Circuits


Basic Building Blocks of Switched-Capacitor Circuits

 - OPAMP (OTA)
- Capacitor
- Switch
- Clock




(a)


Bottom Plate

 


(b)

 


(a)

 



(b)

 

(c)

 


(d)

  


(a)

$$f_s \equiv \frac{1}{T}$$

 

(b)


General Considerations

 

- For continuous-time amplifier, $V_{out}/V_{in} = -R_2/R_1$
- Difficult to implement in CMOS technology
- Typically, open-loop output resistance of CMOS op-amps is maximized to maximize A_v
- R_2 heavily drops open-loop gain, affecting precision


General Considerations

 - R_F can be replaced by a switch
- S_2 is turned on to place op amp in unity gain feedback to force V_X equal to V_B , a suitable common-mode value
- When S_2 turns off, node X retains the voltage allowing amplification
- When S_2 is on, circuit does not amplify V_{in}




S_2 status	Phase
On	Reset OTA or Sample input
Off	Amplify

General Considerations

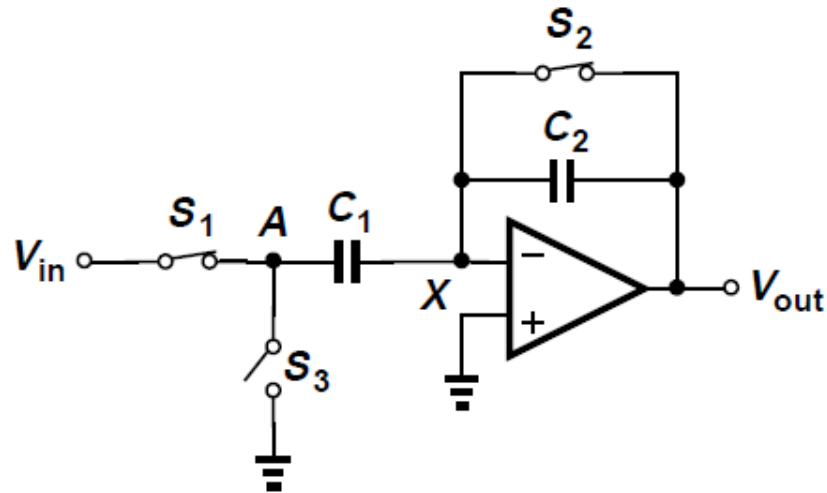


S_1, S_2 on, S_3 off

 

Sampling Phase


S_1, S_2 off, S_3 on

 



Amplifying Phase

General Considerations

Sampling Phase

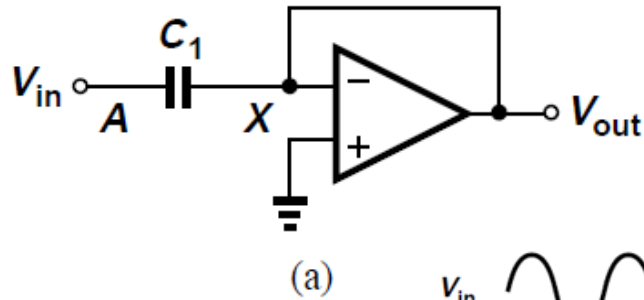


Amplifying Phase

 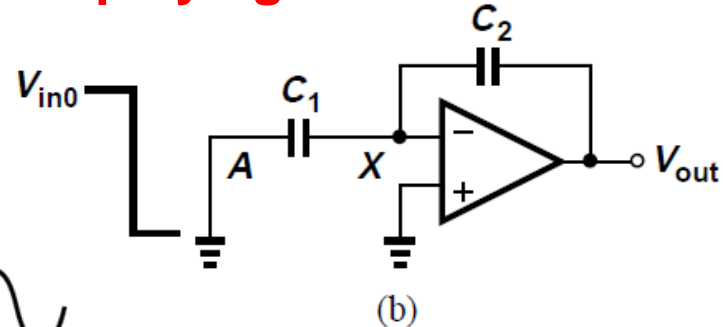

- Phase 1: Samples the input
- Phase 2: Amplify the signal
- *During Phase 2, V_A changes from V_{in} to 0, therefore V_{out} must change from zero to $V_{in0} C_1 / C_2$*



General Considerations

 - Switched-capacitor amplifiers operate in **two phases**: **Sampling and Amplification**
- Clock needed in addition to analog input V_{in}







MOSFET as Switches

  - Sampling circuit consists of a switch and a capacitor [Fig. (a)]
- MOS transistor can function as switch [Fig. (b)] since it can be on while carrying zero current







MOSFET as Switches

  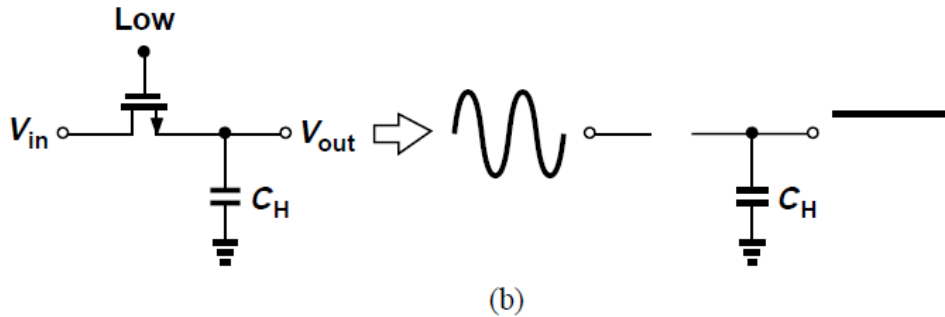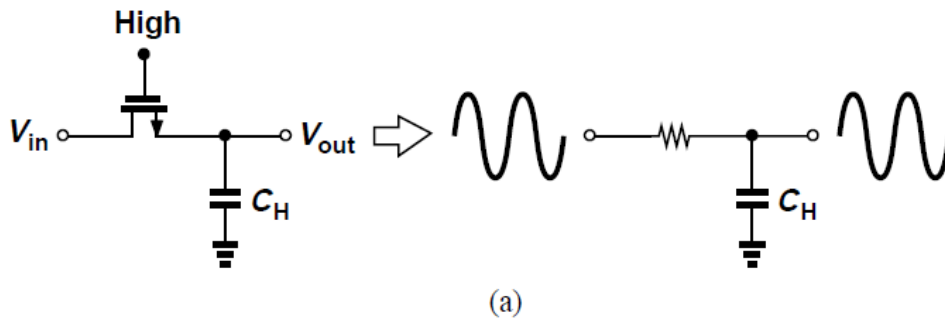


- When switch is on [Fig. (a)], V_{out} follows V_{in}
- When switch is off [Fig. (b)], V_{out} remains constant
- Circuit “tracks” signal when CK is high and “freezes” instantaneous value of V_{in} across C_H when CK goes low

MOSFET as Switches

    


MOSFET as Switches: Speed Considerations

 - Sampling speed is given by two factors: switch on-resistance and sampling capacitance
- For higher speed, large aspect ratio and small capacitance are needed
- On-resistance also depends on input level for both NMOS and PMOS




(a)

 


(b)

MOSFET as Switches: Speed Considerations

 - To allow greater input swings, we can use “complementary” switches, requiring complementary clocks [Fig. (a)]
- Equivalent on-resistance shows following behavior [Fig. (b)], revealing much less variation



(a)

 


(b)

MOSFET as Switches: Precision Considerations

- Speed trades with precision
- Channel Charge Injection:
- For MOSFET to be on, a channel must exist at the oxide-silicon interface
- Assuming $V_{in} \approx V_{out}$, total charge in the inversion layer is
 
$$Q_{ch} = WLC_{ox}(V_{DD} - V_{in} - V_{TH})$$



- When switch turns off, Q_{ch} exits through the source and drain terminals (“channel charge injection”)


MOSFET as Switches: Precision Considerations

- Clock Feedthrough:

- MOS switch couples clock transitions through C_{GD} or C_{GS}
- Sampled output voltage has error due to this given by


$$\Delta V = V_{CK} \frac{WC_{ov}}{WC_{ov} + C_H}$$

 - C_{ov} is the overlap capacitance per unit width
- Error ΔV is independent of input level, manifests as **constant offset** in the input/output characteristic




MOSFET as Switches: Precision Considerations

 
- kT/C Noise:
- Resistor charging a capacitor gives a total RMS noise voltage of $\sqrt{kT/C}$.
- On resistance of switch introduces thermal noise at output which is stored on the capacitor when switch turns off
- RMS voltage of sampled noise is still approximately equal to $\sqrt{kT/C}$.



Unity-Gain Sampler / Buffer

 



(a)

 


(b)

- For discrete-time applications, unity-gain amplifier [Fig. (a)] requires a sampling circuit [Fig. (b)]
- Accuracy limited by input-dependent charge injected by S_1 onto C_H

Unity-Gain Sampler / Buffer

  

Sample

 


Amplify

Unity-Gain Sampler / Buffer

Precision Considerations:


- Output in amplification mode

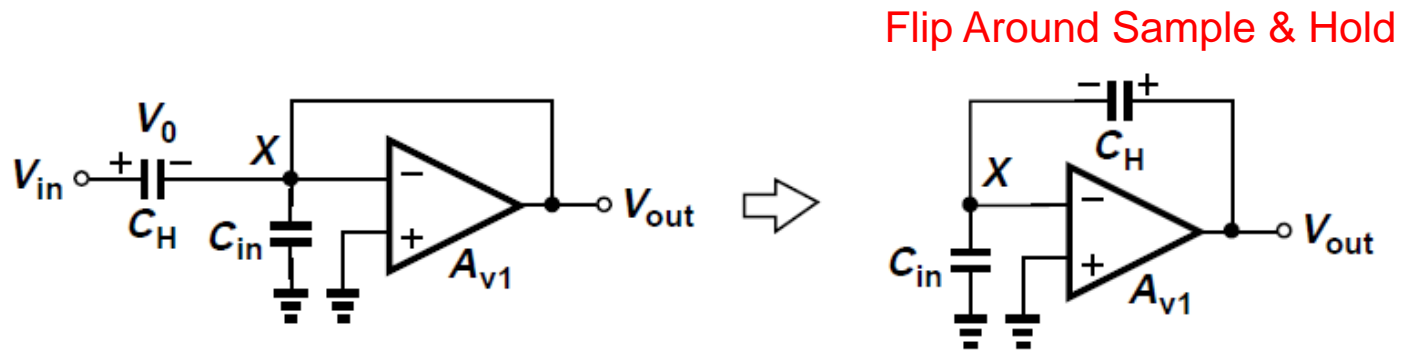

$$V_{out} = \frac{V_0}{1 + \frac{1}{A_{v1}} \left(\frac{C_{in}}{C_H} + 1 \right)}$$
$$\approx V_0 \left[1 - \frac{1}{A_{v1}} \left(\frac{C_{in}}{C_H} + 1 \right) \right]$$

Derive this using charge conservation

Unity-Gain Sampler / Buffer

 

Charge conservation during Ø1 and Ø2

During Ø1, total charge at node X is $Q1 = C_H(0 - V_{in})$

During Ø2, total charge at node X is $Q2 = C_{in}V_x + C_H(V_x - V_{out})$

Let $Q1 = Q2$

$$-V_{in}C_H = C_{in}V_x + C_H(V_x - V_{out}) = (C_{in} + C_H)V_x - C_HV_{out}$$

$$V_x(-A_{v1}) = V_{out}$$

$$-V_{in}C_H = (C_{in} + C_H)(-V_{out}/A_{v1}) - C_HV_{out}$$

$$V_{in}C_H = (C_{in} + C_H)(V_{out}/A_{v1}) + C_HV_{out}$$

$$V_{in}C_H = [(C_{in} + C_H)/A_{v1} + C_H]V_{out}$$


$$V_{in} = [(C_{in} + C_H)/(C_H A_{v1}) + 1]V_{out}$$

$$V_{out}/V_{in} = 1 / [(C_{in} + C_H)/(C_H A_{v1}) + 1] = 1 / [1 + 1/(\beta A_{v1})]$$

$$V_{out} \approx V_0 \left[1 - \frac{1}{\beta A_{v1}} \right] \quad \leftarrow \text{To reduce gain error, Increase } \beta A_v$$

$$\beta = \frac{C_H}{C_H + C_{in}}$$


Differential Unity-Gain Sampler / Buffer

 

- Input-independent charge injected by S_2 can be cancelled by differential operation as shown
- Charge injected by S_2 and S_2' appears as common-mode disturbance at nodes X and Y
- Charge injection mismatch between S_2 and S_2' resolved by adding another switch S_{eq} that turns off slightly after S_2 and S_2' , equalizing the charge at nodes X and Y

Non-Inverting Amplifier

- Precision Considerations:

 

$$Q_1 = C_1(0 - V_{in})$$

$$Q_2 = (C_1 + C_{in})V_x + C_2(V_x - V_{out})$$

$$V_x = \frac{V_{out}}{-A}$$

$$Q_1 = Q_2$$


$$C_1(0 - V_{in}) = (C_1 + C_{in})V_x + C_2(V_x - V_{out}) = (C_1 + C_{in})\left(\frac{V_{out}}{-A}\right) + C_2\left(\frac{V_{out}}{-A} - V_{out}\right)$$

$$-C_1V_{in} = -C_1\frac{V_{out}}{A} - C_{in}\frac{V_{out}}{A} - C_2\frac{V_{out}}{A} - C_2V_{out}$$


$$C_1V_{in} = \left(\frac{C_1 + C_{in} + C_2}{A} + C_2\right)V_{out} = C_2\left(\frac{C_1 + C_{in} + C_2}{C_2A} + 1\right)V_{out} = C_2\left(\frac{1}{\beta A} + 1\right)V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{C_1}{C_2\left(\frac{1}{\beta A} + 1\right)} \approx \frac{C_1}{C_2}\left(1 - \frac{1}{\beta A}\right)$$

Sample


 


Amplify

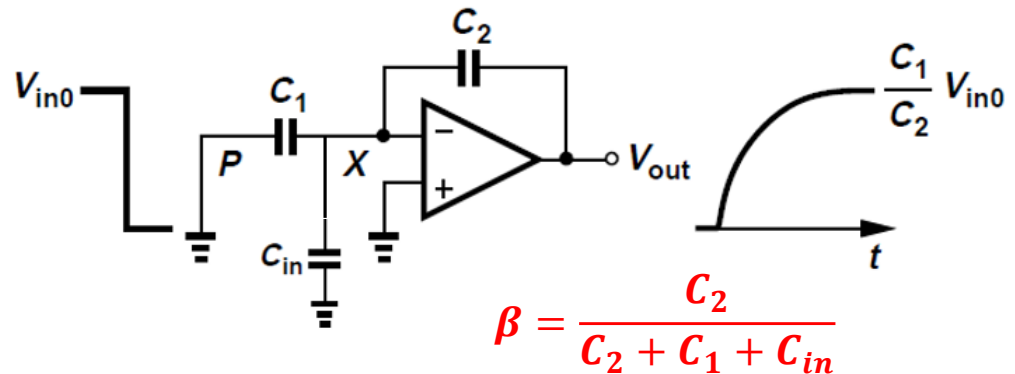


Connection of Capacitor

Capacitor

  



Unity-Gain Sampler

 Need to minimize the capacitance at the summing node



Non-Inverting Amplifier

- Speed Considerations:

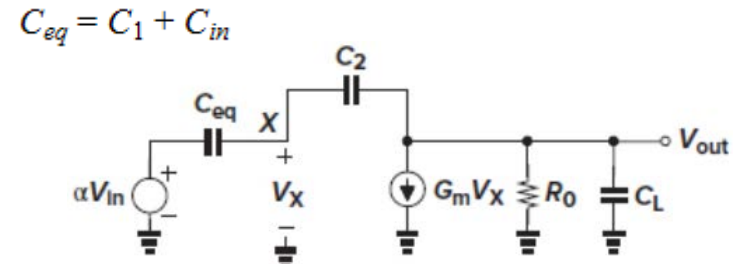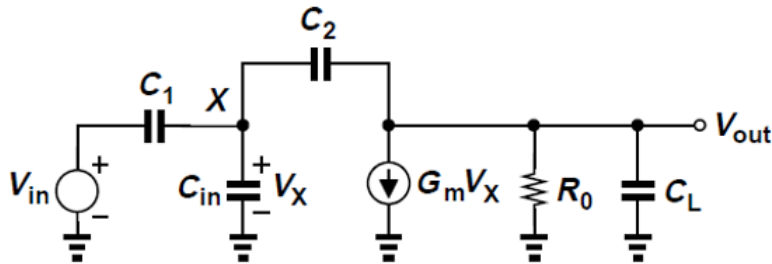

$$\frac{V_{out}}{V_{in}}(s) \approx \frac{-C_{eq} \frac{C_1}{C_1 + C_{in}} (G_m - C_2 s) R_0}{R_0 (C_L C_{eq} + C_L C_2 + C_{eq} C_2) s + G_m R_0 C_2}$$

$$\tau_{amp} = \frac{C_L C_{eq} + C_L C_2 + C_{eq} C_2}{G_m C_2}$$

$$= \frac{C_1 + C_2 + C_{in}}{C_2} \cdot \frac{C_L + \frac{C_2 (C_{in} + C_1)}{C_2 + C_{in} + C_1}}{G_m}$$

$$= \frac{C_{L,eq}}{\beta G_m} = \frac{1}{\beta \omega_u}$$



C_{in} needs to be minimized to increase β

$$\beta = \frac{C_2}{C_2 + C_1 + C_{in}}$$

$$\omega_u = \frac{G_m}{C_{L,eq}}$$

Multiply-by-Two Circuit

  
- Topology shown in Fig. (a) provides a nominal gain of two while achieving higher speed and lower gain error



- Incorporates two equal capacitors $C_1 = C_2 = C$
- In sampling mode [Fig. (b)], node X is a virtual ground, allowing voltage across C_1 and C_2 to track V_{in}

Multiply-by-Two Circuit

 - During transition to amplification mode [Fig. (c)], S_3 turns off first, placing C_1 around op-amp and left plate of C_2 is grounded
- At the moment S_3 turns off, total charge on C_1 and C_2 equals $2V_{in0}C$ and since voltage across C_2 approaches zero in amplification mode, final voltage across C_1 and hence output are approximately $2V_{in0}$



(c)

