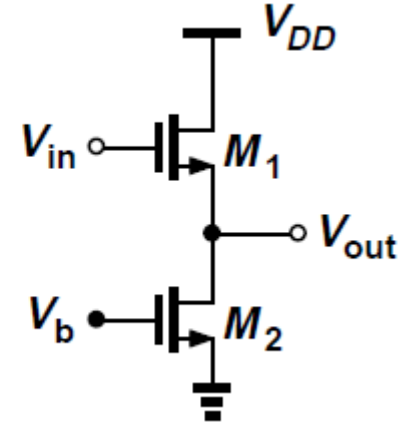
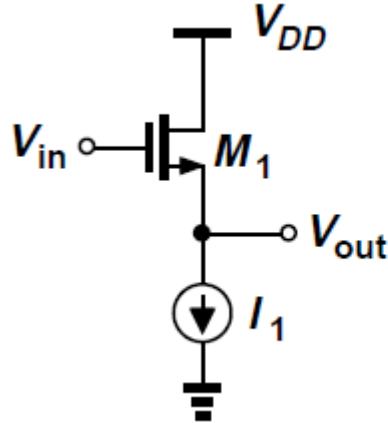
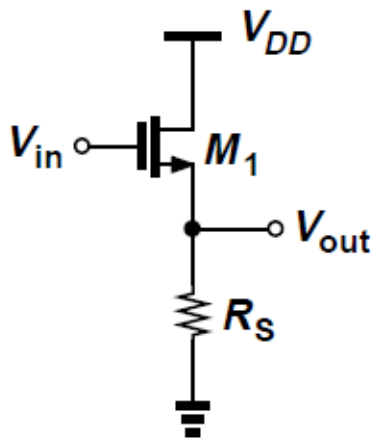

EE223 Analog Integrated Circuits

Fall 2018

Lecture 9: Common Gate Amplifiers

Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259


Issue with Source Follower



- Voltage headroom limitation
- Nonlinear dependence of V_{TH} on the source potential
- r_O changes substantially with V_{DS}


Issue with Source Follower

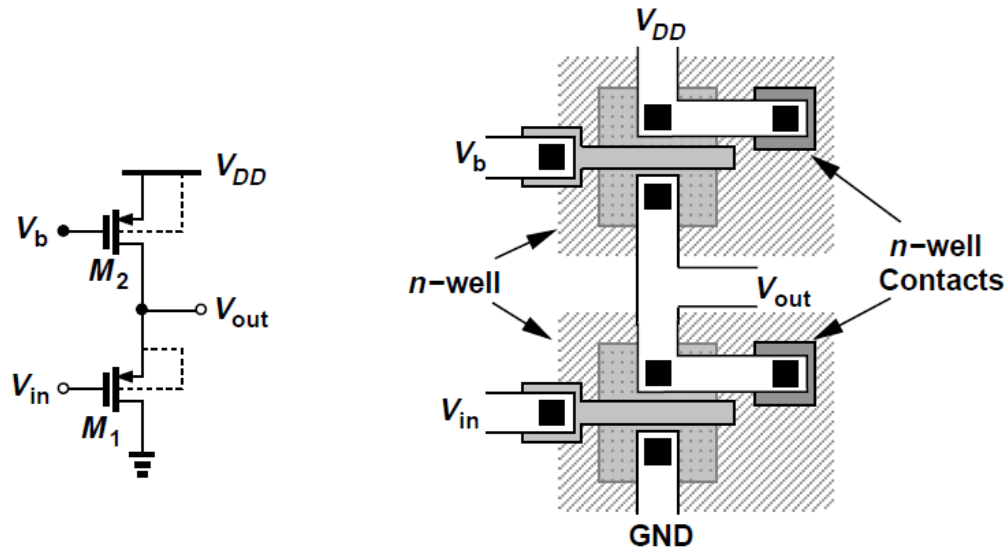- Nonlinearity can be eliminated if the bulk is tied to the source
- PMOS source follower employing two separate n-wells can eliminate the body effect of M_1



Issue with Source Follower

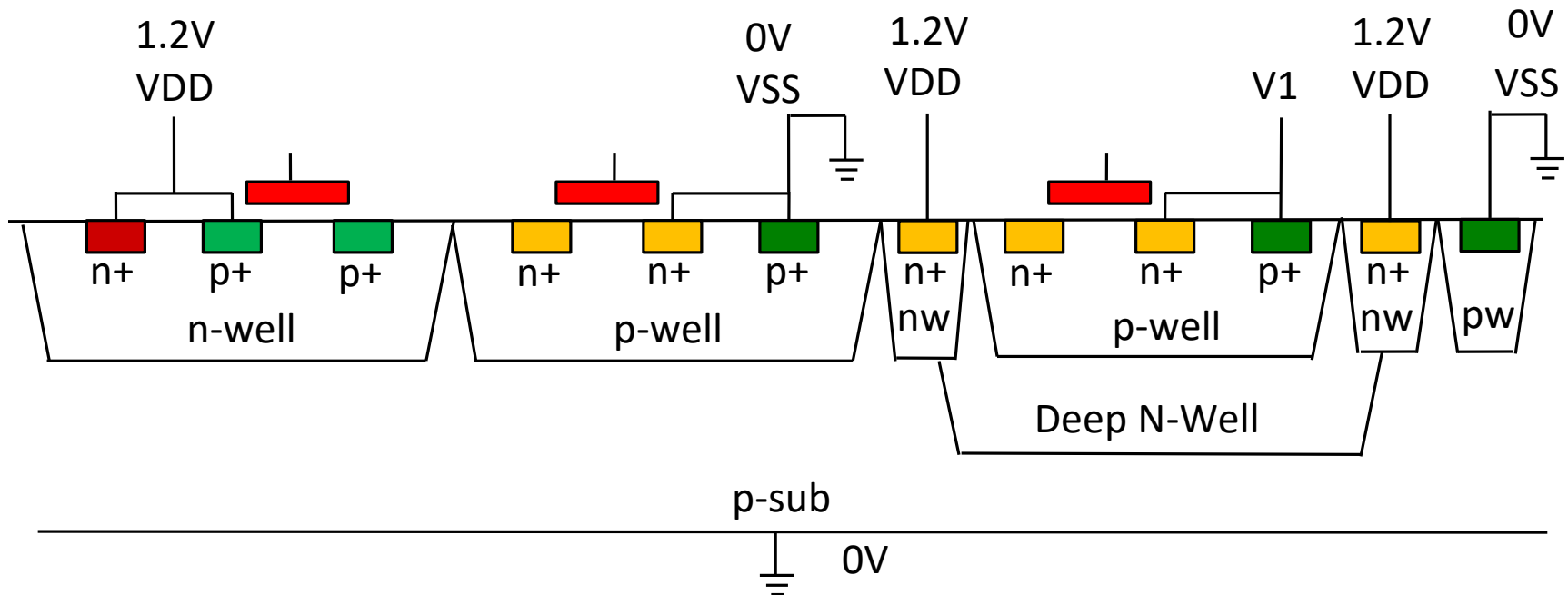- Can we create separate p-wells for NMOS Source Follower?




What voltage V1 should be?

All pn junctions must be reverse-biased at all times.


Layout of NMOS Source Follower

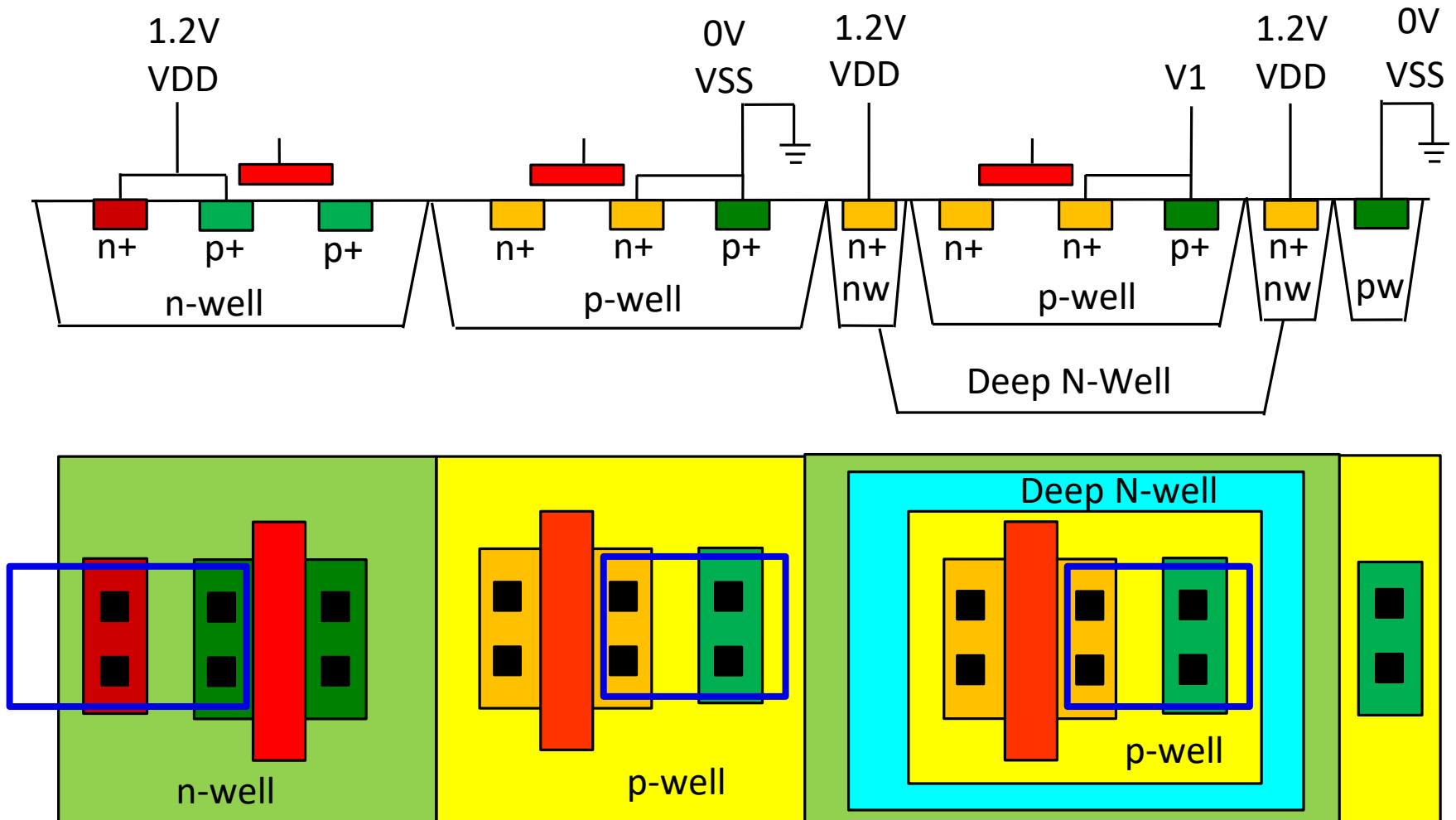- Can we create separate p-wells for NMOS Source Follower?




Issue with Source Follower

- Voltage headroom

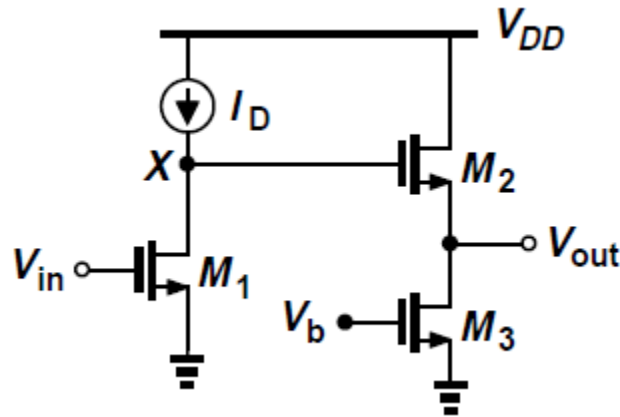


- CS Amp only : V_X needs $V_{DS} > V_{GS1} - V_{TH1}$
- With Source Follower, $V_X > V_{GS2} + (V_{GS3} - V_{TH3})$

Common-Gate Topology

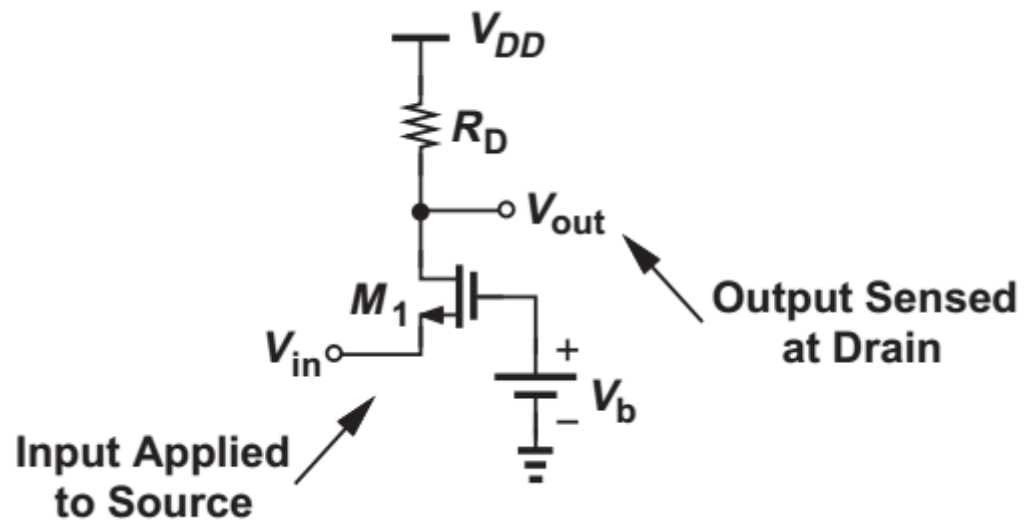

Common-Gate Amplifier


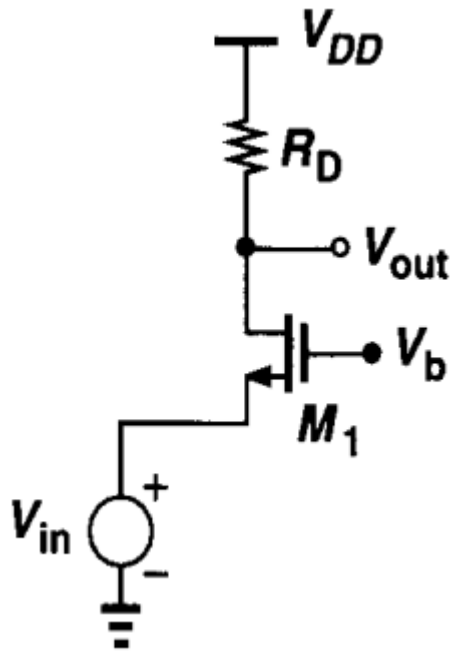


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$$

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

$$\begin{aligned} \frac{\partial V_{out}}{\partial V_{in}} &= + \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) R_D \\ &= g_m R_D \end{aligned}$$

CG Amplifier with R_S



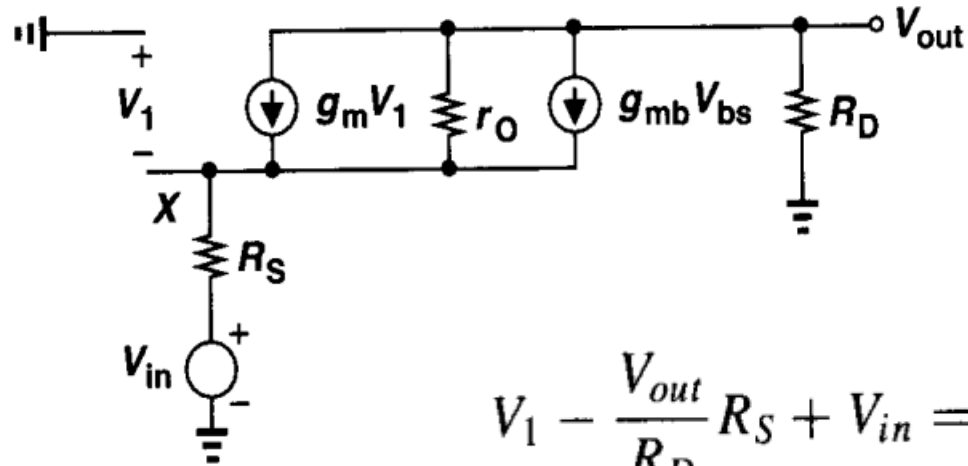
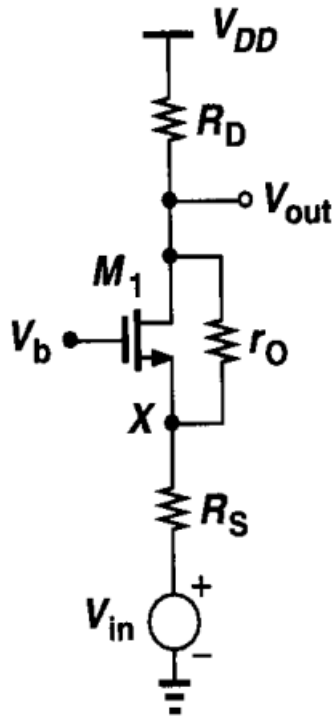


$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$$


$$r_O \left(\frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{(g_m + g_{mb})r_O + 1}{r_O + (g_m + g_{mb})r_O R_S + R_S + R_D} R_D \approx \frac{g_m r_O R_D}{r_O + g_m r_O R_S} = \boxed{\frac{R_D}{\frac{1}{g_m} + R_S}}$$


CG Amplifier vs. CS Amplifier

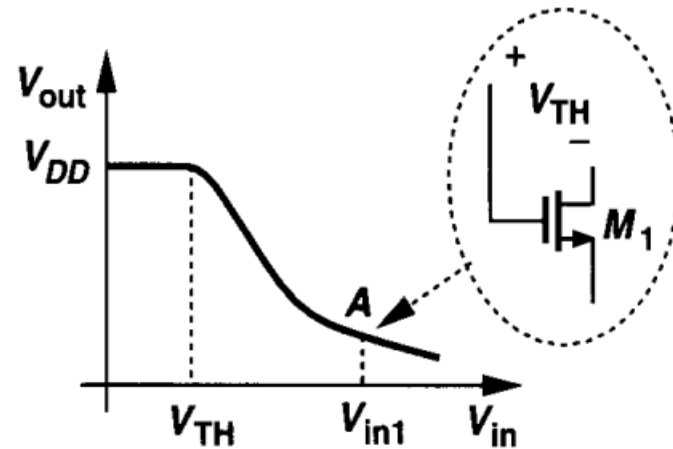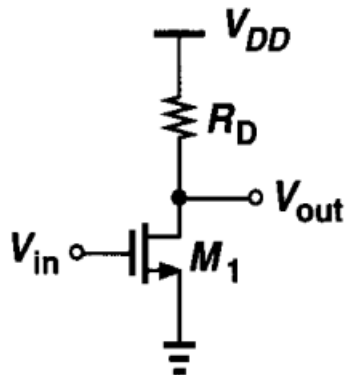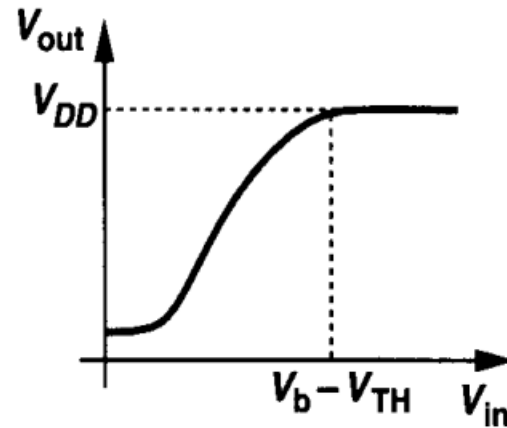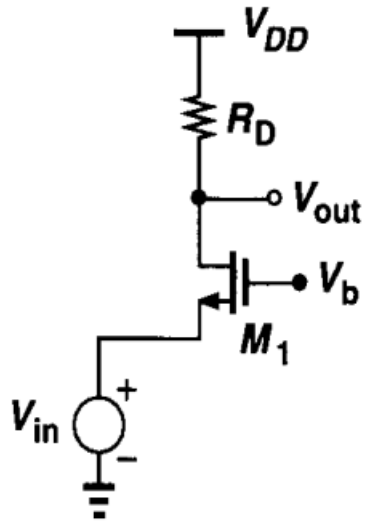

Summary : Gain of CG and CS with R_S

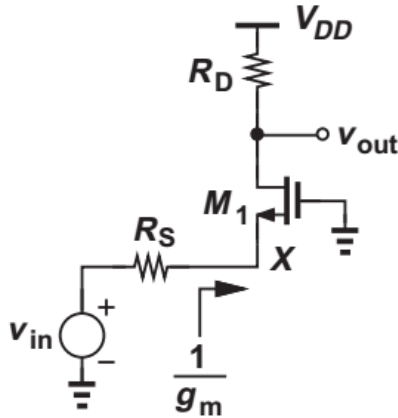
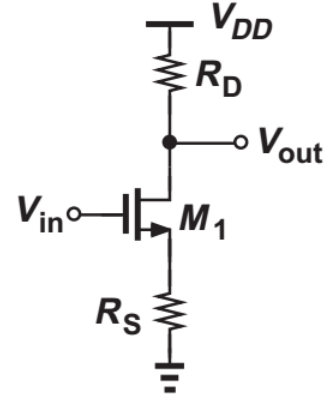
$$A_v = \frac{R_D}{\frac{1}{g_m} + R_S}$$



$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$


→ $\frac{\text{Resistance seen at the drain}}{\text{Total resistance seen in the source path}}$

Same magnitude for both structures


Summary : R_{out} of CG and CS with R_S

$$R_{out} = r_o + R_S + (g_m r_o) \cdot R_S \rightarrow \text{Same for both structures}$$

CS with R_S

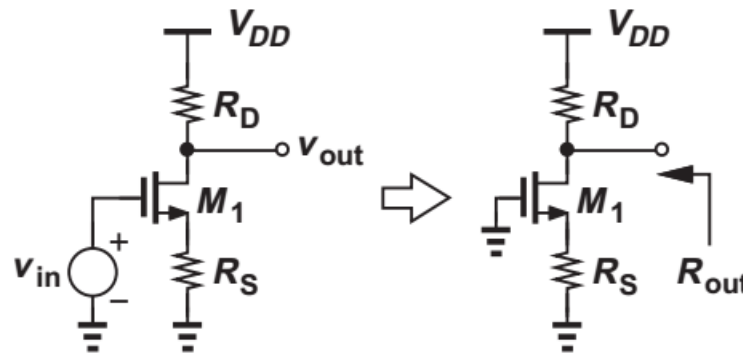


CG with R_S

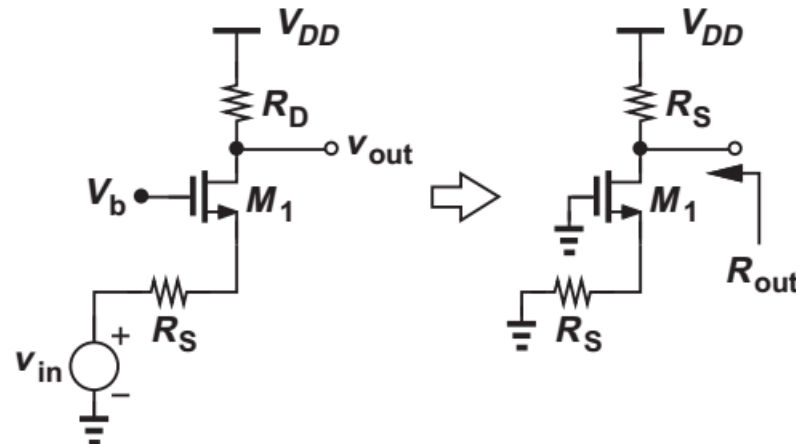

Summary of Amplifiers


CS Amp

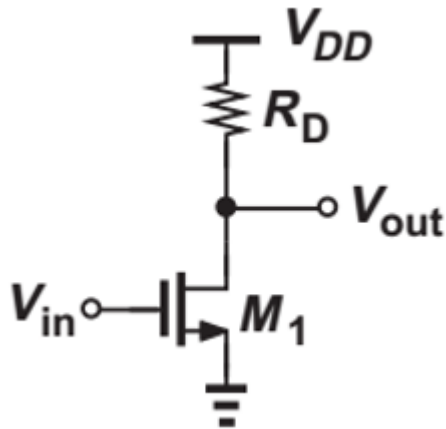

Inverting

$$\begin{aligned} A_v &= -g_m R_{out} \\ &= -g_{m1} (R \uparrow // R \downarrow) \\ &= -g_{m1} (R_D // r_{o1}) \end{aligned}$$


CG Amp

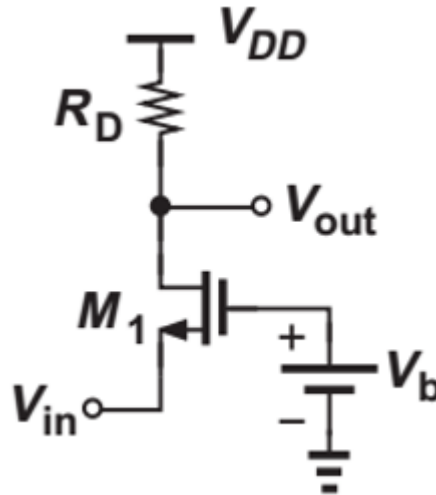

Non-Inverting

$$\begin{aligned} A_v &= g_m R_{out} \\ &= g_{m1} (R \uparrow // R \downarrow) \\ &= g_{m1} (R_D // r_{o1}) \end{aligned}$$


CD Amp

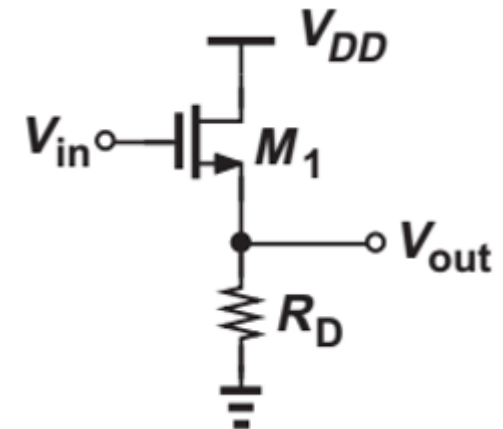

Non-Inverting



$$\begin{aligned} A_v &= g_m R_{out} \\ &= g_m (R \uparrow // R \downarrow) \\ &= g_m \left(\frac{1}{g_{m1}} // R_D \right) \end{aligned}$$

Cascode Stage

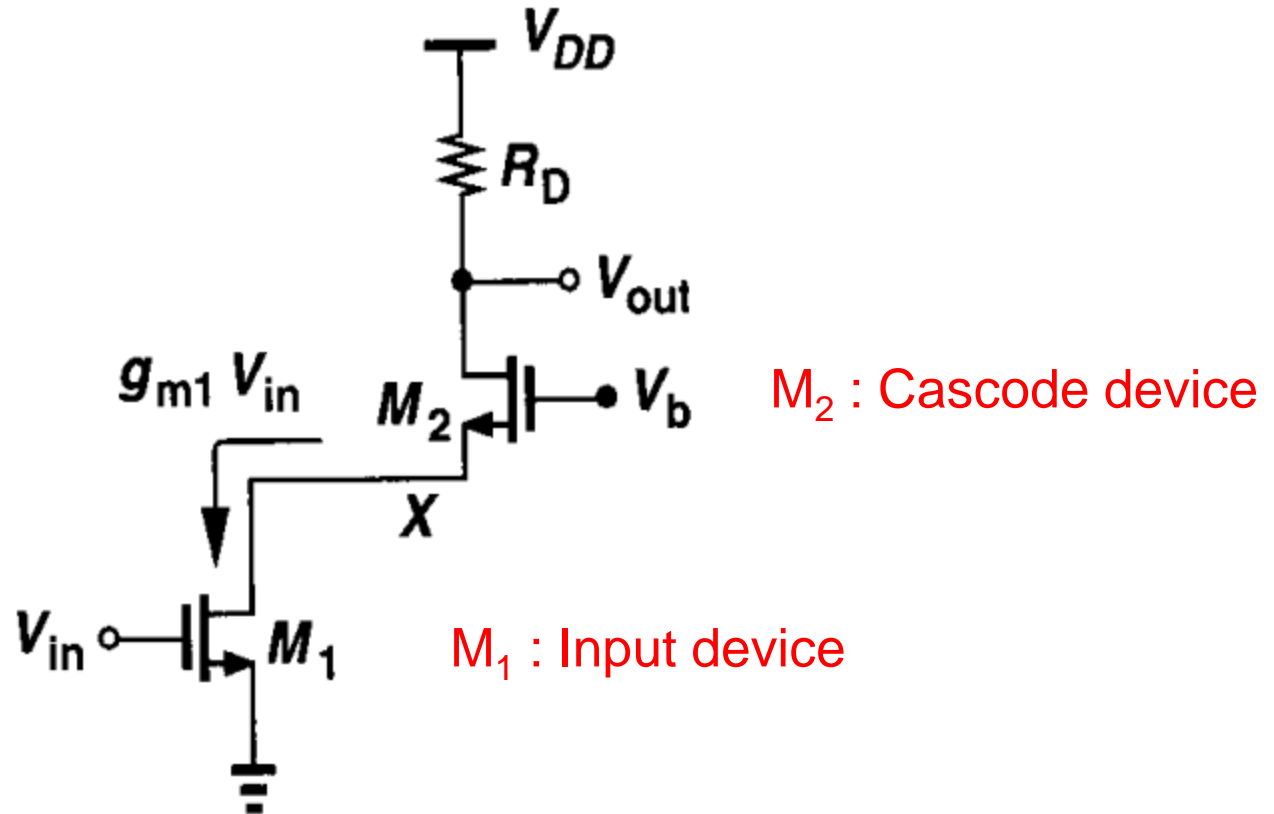


Cascode Topology : Cascade of CS stage and CG stage

I/O Characteristics of Cascode Stage

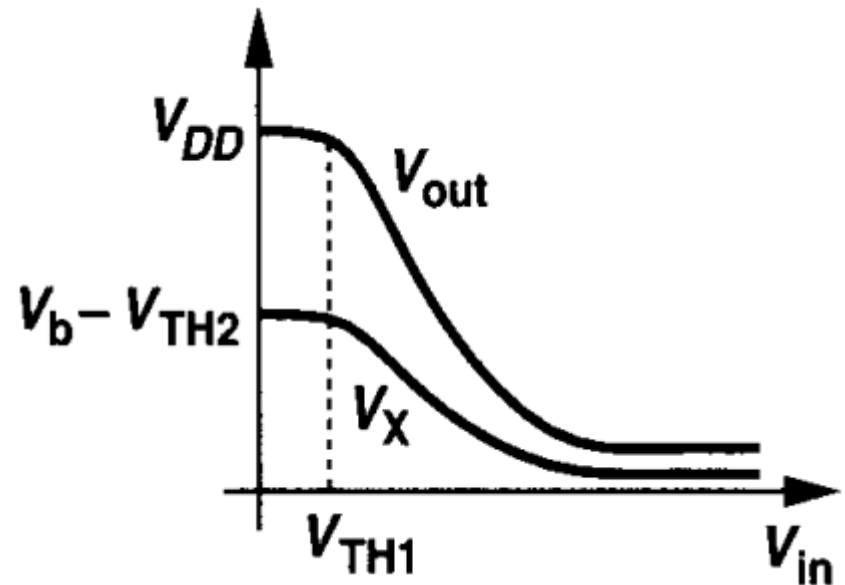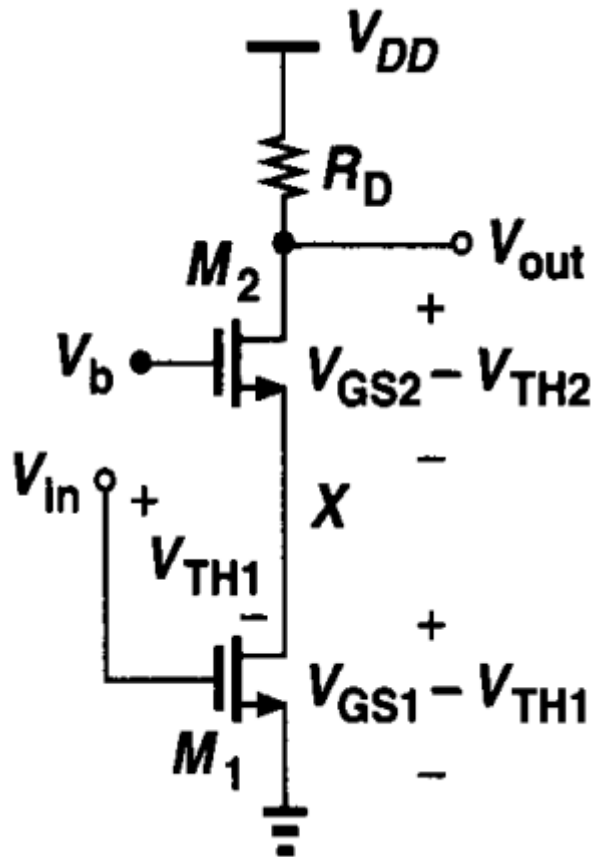



Output Impedance of Cascode Stage

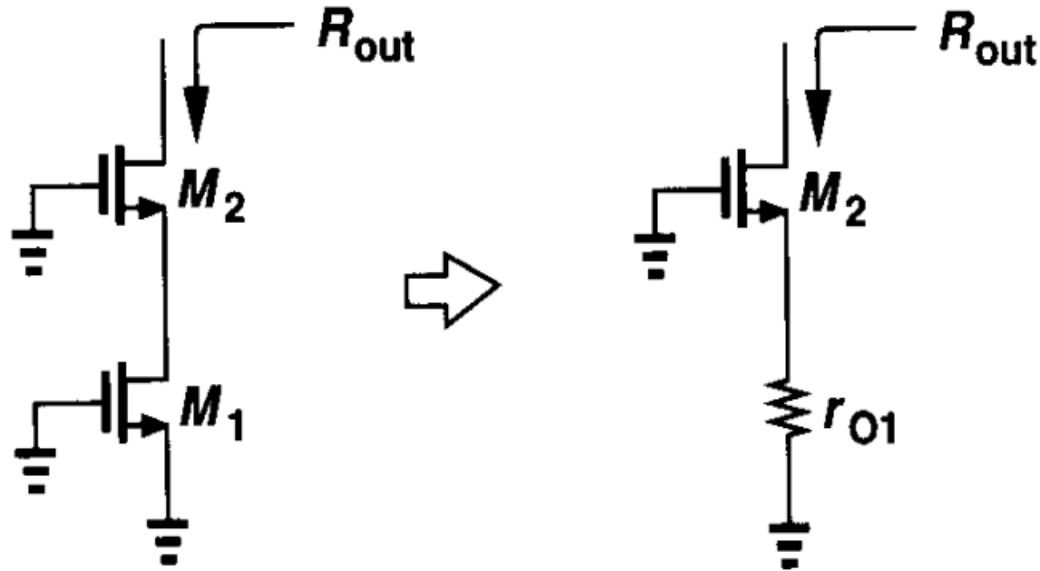

$$R_{out} = r_{o1} + r_{o2} + (g_{m2}r_{o2})r_{o1}$$

$$R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1} \quad \text{if } g_{mb} \neq 0$$

Gain of Cascode Stage

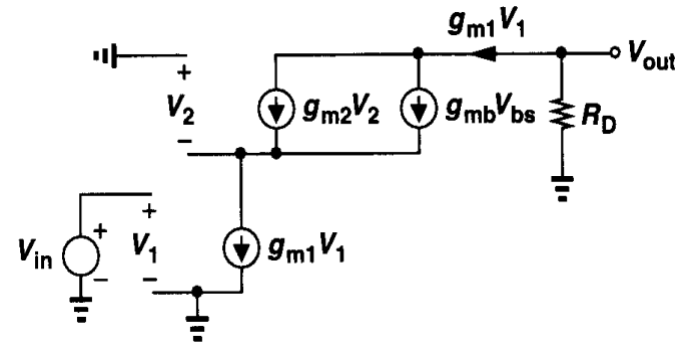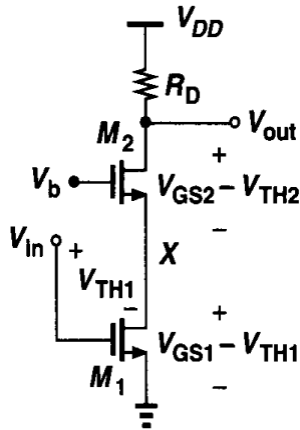


$$A_v = \frac{V_{out}}{V_{in}} = -g_{m1}R_{out}$$

$$R_{out} = \{r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1}\} // R_D$$

$$\approx (g_{m2}r_{o2})r_{o1} // R_D$$

$$A_v \approx -g_{m1}(g_{m2}r_{o2})r_{o1} = -(g_m r_o)^2 \quad \text{if } R_D \text{ is neglected}$$

Cascode Amp with Cascode Current Source

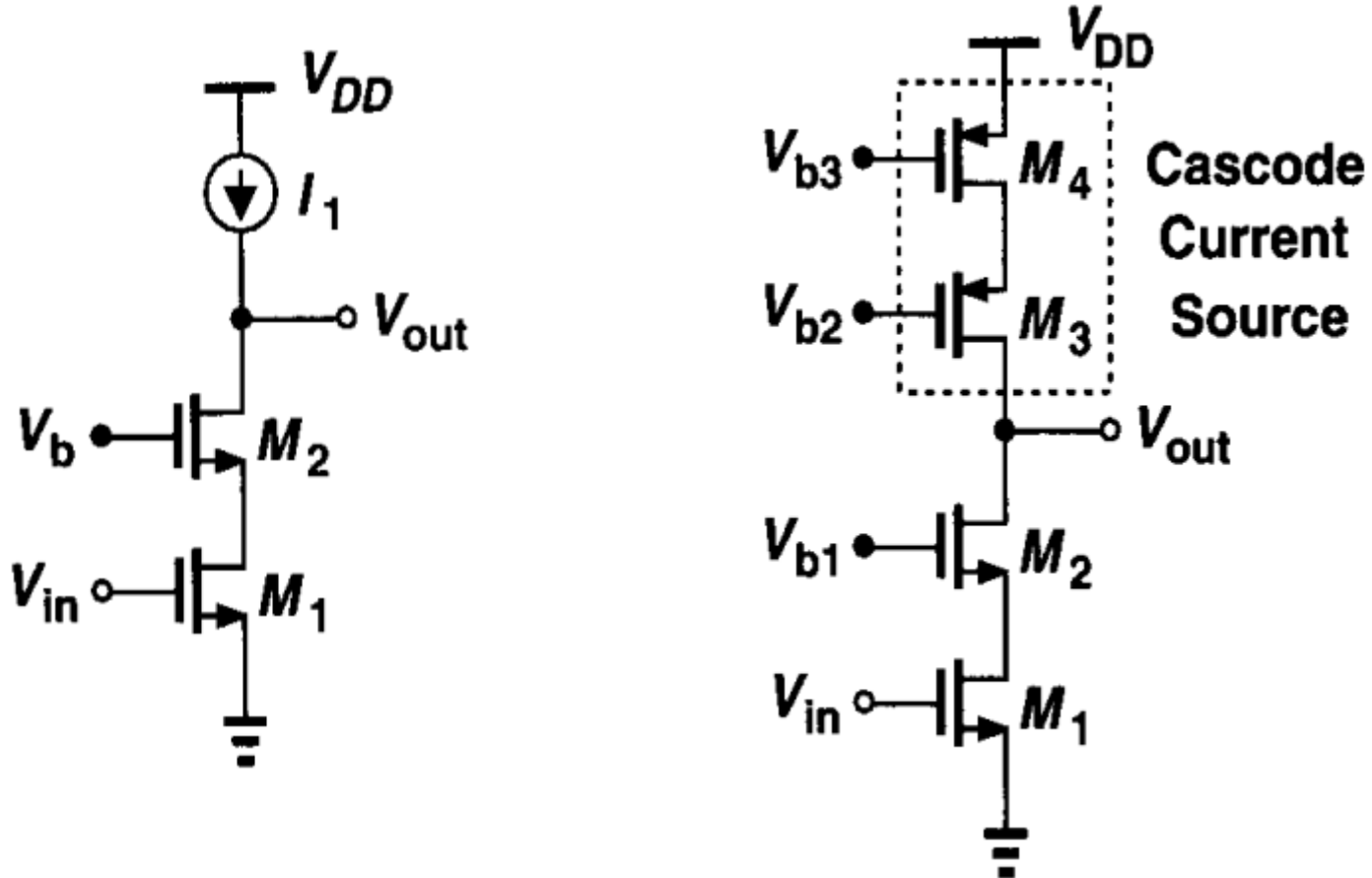

$$A_v \approx -g_{m1}[\{(g_{m2}r_{o2})r_{o1}\}||\{(g_{m3}r_{o3})r_{o4}\}] \approx -\frac{(g_m r_o)^2}{2}$$