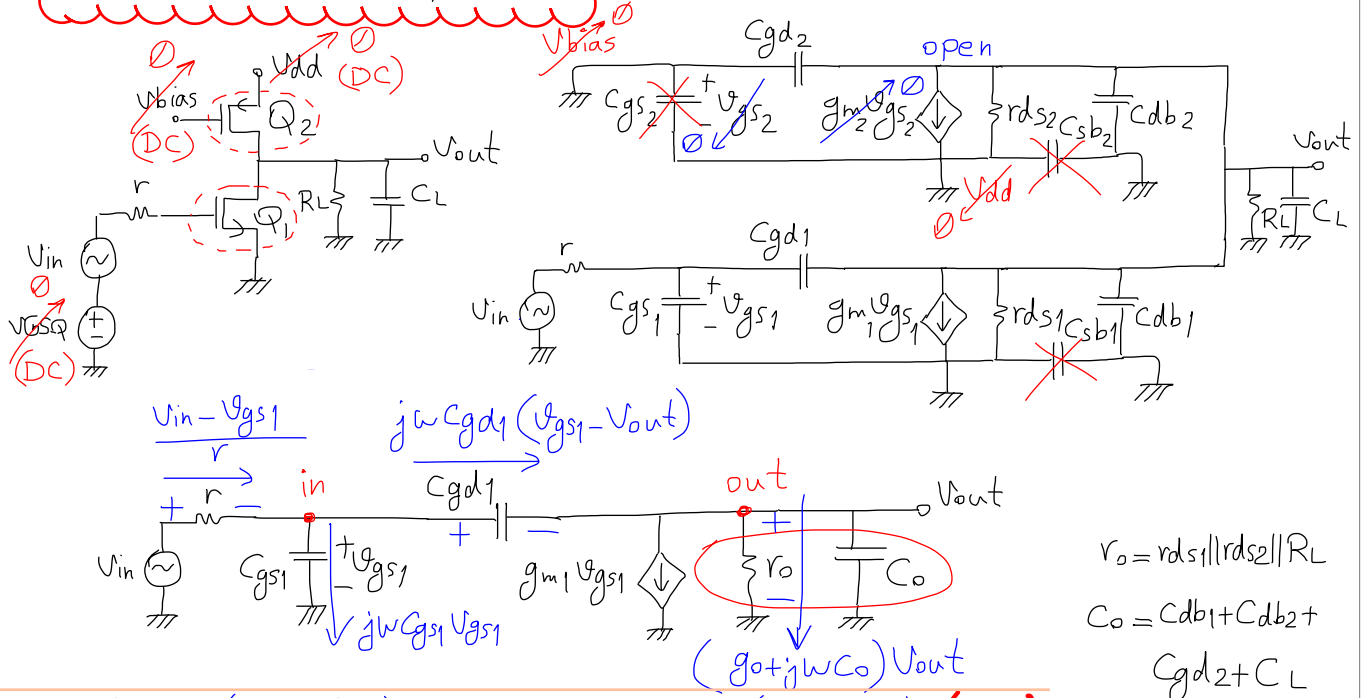


* Common Source Amplifier :



$$\text{KCL (in): } g(V_{in} - V_{gs1}) = j\omega C_{gs1} V_{gs1} + j\omega C_{gd1} (V_{gs1} - V_{out}) \quad (\text{EQ.1})$$

$$\text{KCL (out): } j\omega C_{gd1} (V_{gs1} - V_{out}) = g_m V_{gs1} + (g_o + j\omega C_o) V_{out} \quad (\text{EQ.2})$$

$$g = \frac{1}{r}, \quad g_{ds1} = \frac{1}{r_{ds1}}$$

$$a || b = \frac{1}{\frac{1}{a} + \frac{1}{b}}$$

$$\text{From EQ.2} \Rightarrow V_{gs1} = V_{out} \left[\frac{g_o + j\omega(C_{gd1} + C_o)}{j\omega C_{gd1} - g_{m1}} \right] \quad (\text{EQ.3})$$

$$\text{From (EQs. 1 and 3)} \Rightarrow g V_{in} = V_{out} \left[-j\omega C_{gd1} + \frac{[g + j\omega(C_{gs1} + C_{gd1})][g_o + j\omega(C_{gd1} + C_o)]}{j\omega C_{gd1} - g_{m1}} \right]$$

$$\Rightarrow g V_{in} = V_{out} \left[\frac{g \cdot g_o + j\omega(g_{m1} C_{gd1} + g(C_{gd1} + C_o) + g_o(C_{gs1} + C_{gd1})) + (j\omega)^2 [C_{gs1}(C_{gd1} + C_o) + C_{gd1} C_o]}{j\omega C_{gd1} - g_{m1}} \right]$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-g \cdot g_{m1} \left(1 - j\omega \frac{C_{gd1}}{g_{m1}} \right)}{g \cdot g_o + j\omega [g_{m1} C_{gd1} + g(C_{gd1} + C_o) + g_o(C_{gs1} + C_{gd1})] + (j\omega)^2 [C_{gs1}(C_{gd1} + C_o) + C_{gd1} C_o]}$$

* All single-stage amplifiers are modelled with:

$$\frac{V_{out}}{V_{in}} = \frac{A_{v0} (1 \pm j\frac{\omega}{\omega_z})}{(1 + j\frac{\omega}{\omega_{p1}})(1 + j\frac{\omega}{\omega_{p2}})} \Rightarrow \text{Left-hand poles (inherently stable)}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_{v0} (1 \pm j \frac{\omega}{\omega_z})}{(1 + j \frac{\omega}{\omega_{p1}})(1 + j \frac{\omega}{\omega_{p2}})}$$
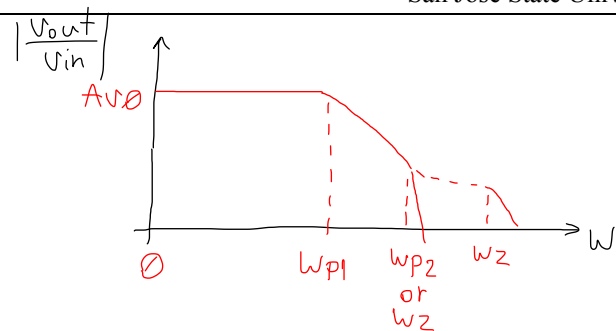
$$\omega_{p1} \ll \omega_{p2} \text{ or } \omega_z$$



$$\frac{V_{out}}{V_{in}} = \frac{A_{v0} (1 \pm j \frac{\omega}{\omega_z})}{1 + j\omega \left[\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right] + (j\omega)^2 \frac{1}{\omega_{p1} \cdot \omega_{p2}}} = \frac{A_{v0} k_1 (1 \pm j \frac{\omega}{\omega_z})}{k_2 + j\omega k_3 + (j\omega)^2 k_4}$$

$\frac{1}{\omega_{p1}}$ (under the first term in the denominator)
 $\frac{1}{\omega_{p1} \cdot \omega_{p2}} = \frac{k_4}{k_2}$ (under the second term in the denominator)
 $\frac{1}{\omega_{p1}}$ (under the first term in the denominator)
 $\frac{1}{\omega_{p2}}$ (under the second term in the denominator)

$$A_{v0} = \frac{k_1}{k_2}$$

$$\omega_{p1} = \frac{k_2}{k_3}$$

$$\omega_{p2} = \frac{k_3}{k_4}$$

$$\frac{1}{\omega_{p1} \cdot \omega_{p2}} = \frac{k_4}{k_2}$$

$$\frac{1}{\omega_{p2}} = \frac{k_4}{k_2} \cdot \omega_{p1} = \frac{k_4}{k_2} \frac{k_2}{k_3} = \frac{k_4}{k_3}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-g_m g_{m1} (1 - j\omega \frac{C_{gd1}}{g_{m1}})}{g_o g_o + j\omega [g_{m1} C_{gd1} + g(C_{gd1} + C_o) + g_o (C_{gs1} + C_{gd1})] + (j\omega)^2 [C_{gs1} (C_{gd1} + C_o) + C_{gd1} C_o]}$$

$$\Rightarrow A_{v0} = \frac{-g_m g_{m1}}{g_o g_o} = \frac{-g_{m1}}{g_o} = -g_{m1} r_o = -g_{m1} (r_{ds1} || r_{ds2} || R_L)$$



$$\Rightarrow \omega_z = \frac{g_{m1}}{C_{gd1}} \quad \text{RHZ ; right hand zero}$$

$$\Rightarrow \omega_{p1} = \frac{g_o g_o}{g_{m1} C_{gd1} + g(C_{gd1} + C_o) + g_o (C_{gs1} + C_{gd1})}$$

$$\Rightarrow \omega_{p2} = \frac{g_{m1} C_{gd1} + g(C_{gd1} + C_o) + g_o (C_{gs1} + C_{gd1})}{C_{gs1} (C_{gd1} + C_o) + C_{gd1} C_o}$$


*OpAmps:

$$\frac{V_{out}}{V_{in}}; \text{open-loop gain} = \underbrace{-100}_{-100} = -g_{m1}(r_{ds1} || r_{ds2})$$

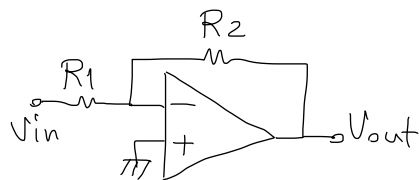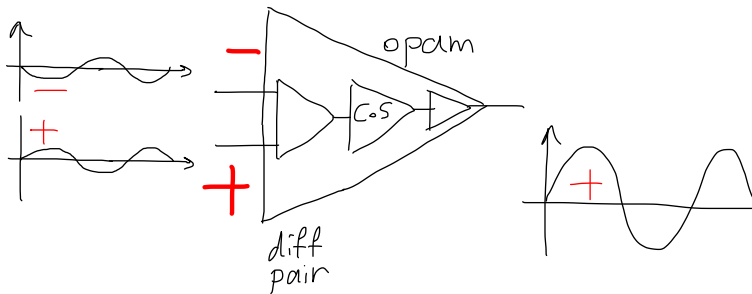

inverting
closed-loop
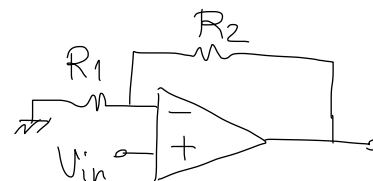
$$\frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1} = \frac{100k}{1k} = -100$$



non-inverting
closed-loop

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

* FOM in any
Analog Design:

$P_{dc} = 1\text{mW}$ ↓
voltage swing = 800mV ↑
voltage gain = 20 ↑
bandwidth = 100MHz ↑

$$\text{Figure of Merit (FOM)} = \frac{\text{swing} \times \text{gain} \times \text{bandwidth}}{P_{dc}}$$

Parameters
needed to be
increased

Parameters needed to
be decreased