



EE141-Spring 2010 Digital Integrated Circuits

Lecture 7 Wires

EECS141

Lecture #7

1

Administrativa

- ❑ No lab next week
- ❑ Midterm on Fr Febr 19 6:30-8pm in 2060 Valley LSB
- ❑ Review Session: TBA (most likely on Th)

EECS141

Lecture #7

2

Class Material

- Last lecture
 - Optimizing complex logic
- Today's lecture
 - Applying what we learned on memory decoders
- Reading (Ch 6.2, 12.1, 12.3)

Logical Effort

$$t_{pgate} = t_{inv} (p\gamma + LE \times f)$$

Measure everything in units of t_{inv} (divide by t_{inv}):

p – intrinsic delay ($k\gamma_g$) – gate parameter $\neq f(W)$

LE – logical effort (k) – gate parameter $\neq f(W)$

f – electrical effort (effective fanout)

Normalize everything to an inverter:

$LE_{inv} = 1, p_{inv} = \gamma$


Method of Logical Effort

- Compute the path effort: $PE = (\Pi LE)BF$
- Find the best number of stages $N \sim \log_4 PE$
- Compute the effective fanout/stage $EF = PE^{1/N}$
- Sketch the path with this number of stages
- Work either from either end, find sizes:

$$C_{in} = C_{out} * LE/EF$$

Reference: Sutherland, Sproull, Harris, "Logical Effort, Morgan-Kaufmann 1999.


Example – 8-Input AND

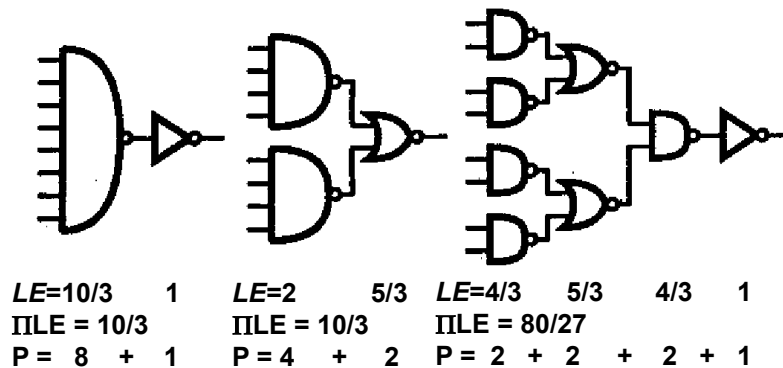

Add Branching Effort

Branching effort:

$$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$$

 


EECS141

Lecture #7

7

Branching Example 1

 

$$\begin{aligned} LE &= 1 \\ FO &= 90/5 = 18 \\ PE &= 18 \text{ (wrong!)} \\ SE_1 &= (15+15)/5 = 6 \\ SE_2 &= 90/15 = 6 \\ PE &= 36, \text{ not } 18! \end{aligned}$$

Introduce new kind of effort to account for branching:

- **Branching Effort:** $b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$

- **Path Branching Effort:** $B = \prod b_i$

Now we can compute the path effort:

- **Path Effort:** $PE = \prod LE \cdot FO \cdot B$

EECS141

Lecture #7

8

Branching Example 2

Select gate sizes y and z to minimize delay from A to B

Logical Effort: $LE = (4/3)^3$


Electrical Effort: $FO = C_{out}/C_{in} = 9$

Branching Effort: $B = 2 \cdot 3 = 6$

Path Effort: $PE = \prod LE \cdot FO \cdot B = 128$

Best Stage Effort: $SE = PE^{1/3} \approx 5$

Delay: $D = 3 \cdot 5 + 3 \cdot 2 = 21$

 

Work backward for sizes:

$$z = \frac{9C \cdot (4/3)}{5} = 2.4C$$

$$y = \frac{3z \cdot (4/3)}{5} = 1.9C$$

Method of Logical Effort

- Compute the path effort: $PE = (\prod LE)BF$
- Find the best number of stages $N \sim \log_4 PE$
- Compute the effective fanout/stage $EF = PE^{1/N}$
- Sketch the path with this number of stages
- Work either from either end, find sizes:

$$C_{in} = C_{out} \cdot LE/EF$$

Reference: Sutherland, Sproull, Harris, "Logical Effort, Morgan-Kaufmann 1999.




Wires

EECS141


Lecture #7

11

The Wire

 

Schematic

 


Physical

EECS141


Lecture #7

12

Wire Models

 

All-inclusive model

 

Capacitance-only

EECS141

Lecture #7

13

Impact of Interconnect Parasitics


- ❑ Interconnect and its parasitics can affect all of the metrics we care about
 - Cost, reliability, performance, power consumption
- ❑ Parasitics associated with interconnect:
 - Capacitance
 - Resistance
 - Inductance

EECS141

Lecture #7

14


Interconnect Length Distribution

 


From Magen et al., "Interconnect Power Dissipation in a Microprocessor"

INTERCONNECT

Capacitance

 

Capacitance: The Parallel Plate Model

 


$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

Permittivity

Material	ϵ_r
Free space	1
Aerogels	~ 1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7

Fringing Capacitance

$$c_{wire} = c_{pp} + c_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$

 


EECS141

Lecture #7

19

Fringing versus Parallel Plate

 


(from [Bakoglu89])

EECS141

Lecture #7

20

Interwire Capacitance

 

EECS141

Lecture #7

21

Capacitive coupling and noise

EECS141

Lecture #7

22


Coupling Capacitance and Delay

EECS141

Lecture #7

23

Impact of Interwire Capacitance

 

(from [Bakoglu89])

EECS141

Lecture #7

24

Wiring Capacitances (0.25 μm CMOS)

Bottom plate

Top plate



	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88	$aF/\mu\text{m}^2$					
	54	$aF/\mu\text{m}$					
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52

EECS141

Lecture #7

25

Wiring Capacitances

  

$$C = C_{pp} \cdot W \cdot L + 2C_{fringe} L$$

EECS141

Lecture #7

26

INTERCONNECT

Resistance




EECS141

Lecture #7

27

Wire Resistance

 

EECS141

Lecture #7

28

Interconnect Resistance

Material	ρ ($\Omega\text{-m}$)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

EECS141

Lecture #7

29

Dealing with Resistance


- ❑ **Use Better Interconnect Materials**
 - e.g. copper, silicides
- ❑ **More Interconnect Layers**
 - reduce average wire-length
- ❑ **Selective Technology Scaling**
 - (More later)

EECS141

Lecture #7

30

Polycide Gate MOSFET

 

Silicides: WSi_2 , TiSi_2 , PtSi_2 and TaSi

Conductivity: 8-10 times better than Poly

Sheet Resistance

Material	Sheet Resistance (Ω/\square)
n- or p-well diffusion	1000 – 1500
n^+ , p^+ diffusion	50 – 150
n^+ , p^+ diffusion with silicide	3 – 5
n^+ , p^+ polysilicon	150 – 200
n^+ , p^+ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1




Interconnect Modeling

EECS141

Lecture #7

33

The Lumped Model

 


EECS141

Lecture #7

34

The Distributed RC-line

 


- Analysis method:
 - Break the wire up into segments of length dx
 - Each segment has resistance ($r dx$) and capacitance ($c dx$)

EECS141

Lecture #7

35

The Distributed RC-line

 

$$I_C = c \Delta L \frac{\partial V}{\partial t} = \frac{(V_{i-1} - V_i) - (V_i - V_{i+1})}{r \Delta L} \longrightarrow \boxed{rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}}$$

$$\boxed{\tau = \frac{L^2}{2} rc}$$

EECS141

Lecture #7

36

Wire Model

Model the wire with N equal-length segments:

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$


For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$


RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% (t_p)	0.69 RC	0.38 RC
0→63% (τ)	RC	0.5 RC
10%→90% (t_p)	2.2 RC	0.9 RC

 Step Response of Lumped and Distributed RC Networks:
Points of Interest.



Driving an RC-line

 

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w C_w L^2$$

$$t_p = 0.69 R_s C_w + 0.38 R_w C_w$$