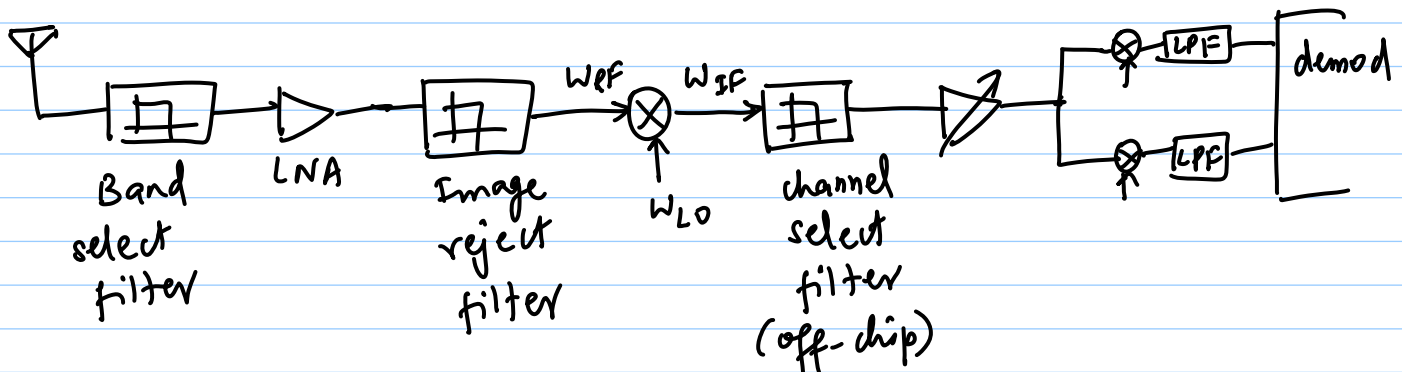


# Lecture 26: Heterodyne Rx; Image-Reject Rx

## II Heterodyne Receivers

{ studied this in Lecture #10 }



\* Image problem  $\Rightarrow$  IR Filter

\* NO DC problems


\* high IF = easy IR filtering

low IF = easy IF design (high gain, high-Q filtering)

i.e. Tradeoff between

image rejection (sensitivity) and  
channel-selection (selectivity)


### Half-IF problem

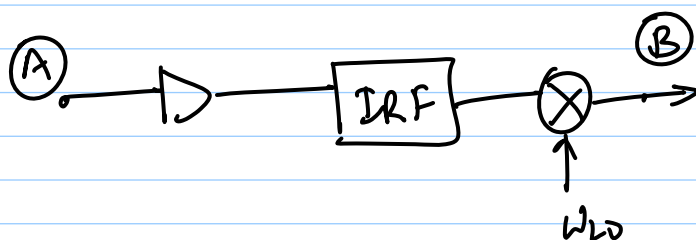

\* Mixer has significant second order distortions


\* LO has 2<sup>nd</sup> harmonic

(A)

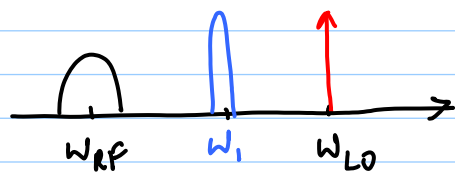

$$\omega_1 = \frac{\omega_{RF} + \omega_{LO}}{2}$$

(B)

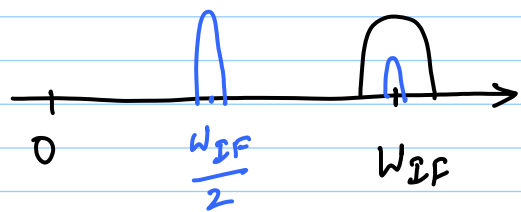

\* IF component @  $|2\omega_1 - 2\omega_{LO}| = \omega_{IF}$   
 second-order distortion in mixer  $\nearrow$   $\nearrow$  LO has second harmonic

\* If BB has second-order distortion,  
 IF component @  $|\omega_1 - \omega_{LO}| = \omega_{IF}/2$   
 BB component @  $\omega_{IF}$  (2nd order distortion)

Solutions:

- minimise 2nd-order distortion in RF/IF path
- 50% LO duty cycle (no  $2\omega_{LO}$ )

Dual-IF topology  $\equiv$  two stages of down-conversion

- partial channel selection @ each IF
- each filter Q is relaxed
- Second IF has image problem too!

### III Image-reject Receivers


\* IR filters  $\rightarrow$  off-chip, on-chip etc.

$\rightarrow$  impact on noise, power consumption

$\Rightarrow$  motivates other RF system architectures for image rejection


Basic idea: process signal & image differently: cancel image with negative replica (IM & RF on opposite sides of LO)

shift-by- $90^\circ$  operation

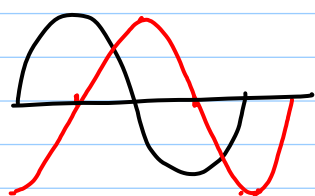

$$\begin{aligned} \text{—} &= \sin \omega t \\ \text{—} &= -\cos \omega t \end{aligned}$$

} Shifting in time domain

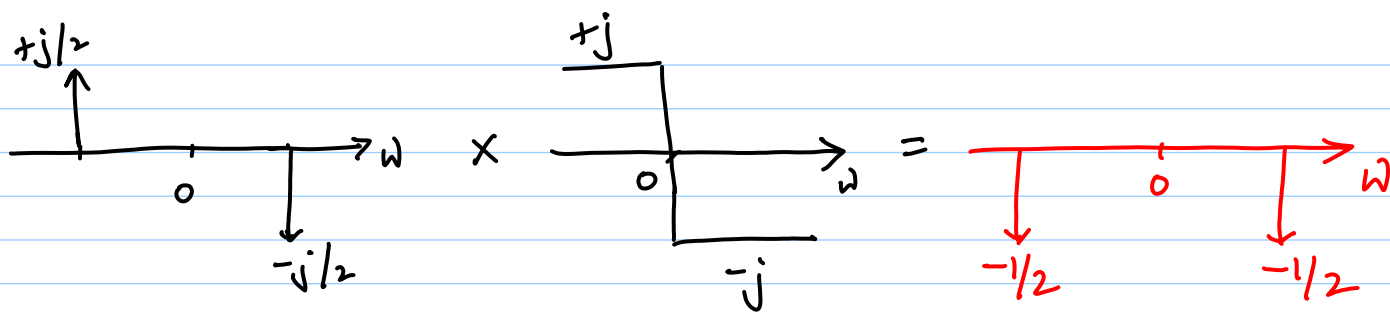

shifting by  $90^\circ$  in freq. domain


multiply by  $G(\omega) = -j \operatorname{sgn}(\omega)$  } equivalent to taking Hilbert Transform

$$t \rightarrow t - T/4$$

$$\sin \omega t \rightarrow -\cos \omega t$$

$$\cos \omega t \rightarrow \sin \omega t$$

One Ckt implementation

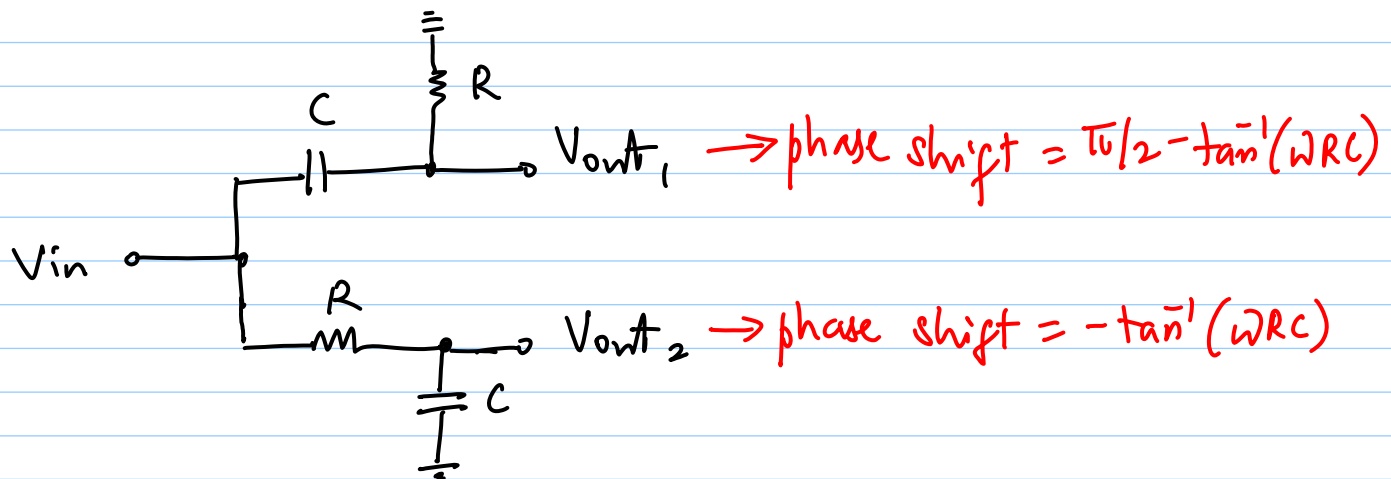


\*  $V_{out1}$  &  $V_{out2}$  have a  $90^\circ$  phase difference

@ all  $\omega$

\* Amplitudes are equal only @  $\omega = \frac{1}{RC} \left\{ \begin{array}{l} 45^\circ \text{ on} \\ \text{each} \\ \text{side} \end{array} \right\}$

## 1) Hartley Architecture

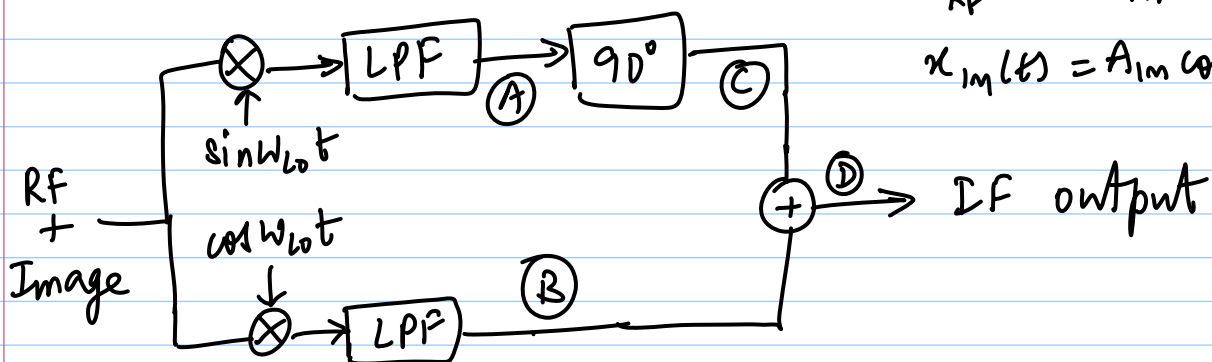

$$x_{RF}(t) = A_{RF} \cos \omega_{RF} t$$

$$x_{IM}(t) = A_{IM} \cos \omega_{IM} t$$

assume low-side injection:  $\omega_{RF} - \omega_{LO} = \omega_{LO} - \omega_{IM}$

$$\begin{aligned} x_A(t) &= \frac{A_{RF}}{2} \sin(\omega_{LO} - \omega_{RF})t + \frac{A_{IM}}{2} \sin(\omega_{LO} - \omega_{IM})t \\ &= -\frac{A_{RF}}{2} \sin(\omega_{RF} - \omega_{LO})t + \frac{A_{IM}}{2} \sin(\omega_{LO} - \omega_{IM})t \end{aligned}$$

$$x_B(t) = \frac{A_{RF}}{2} \cos(\omega_{LO} - \omega_{RF})t + \frac{A_{IM}}{2} \cos(\omega_{LO} - \omega_{IM})t$$

$$\Rightarrow x_c(t) = +\frac{A_{RF}}{2} \cos(\omega_{RF} - \omega_{LO})t - \frac{A_{IM}}{2} \cos(\omega_{LO} - \omega_{IM})t$$

$$x_D(t) = x_B(t) + x_c(t)$$


$$= A_{RF} \cos(\omega_{LO} - \omega_{RF})t$$

\* RF signal - same polarity; IM signal - opposite polarity

\*  $90^\circ$  shift operation distinguishes between

$$\omega_{LO} - \omega_{RF} < 0 \quad \& \quad \omega_{LO} - \omega_{IM} > 0$$

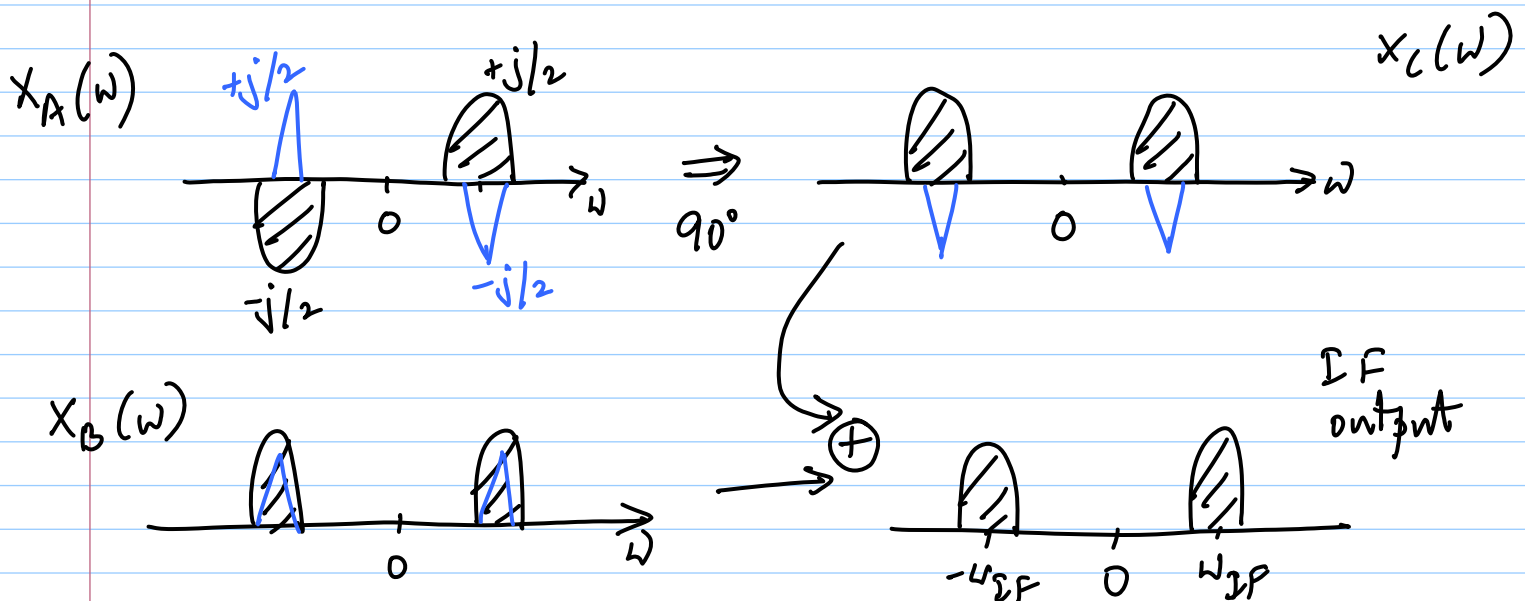\* In practice,  $90^\circ$  is achieved by applying  $45^\circ$  &  $-45^\circ$  phase shifts on  $x_A(t)$  &  $x_B(t)$  respectively



\* Key drawback: sensitivity to mismatches

→ LOs not in quadrature

→ gains & phase shifts in two paths are not identical

⇒ Image cancellation is incomplete & signal is corrupted

Assume: LO inputs are  $A_{LO} \sin \omega_{LO} t$  and

$(A_{LO} + \epsilon) \cos(\omega_{LO} t + \theta)$

$\epsilon \rightarrow$  amplitude mismatch

$\theta \rightarrow$  phase imbalance

$$x_A(t) = \frac{A_{LO} A_{RF}}{2} \sin(\omega_{LO} - \omega_{RF})t + \frac{A_{LO} A_{IM}}{2} \sin(\omega_{LO} - \omega_{IM})t$$

$$x_B(t) = (A_{LO} + \epsilon) \frac{A_{RF}}{2} \cos[(\omega_{LO} - \omega_{RF})t + \theta] \\ + (A_{LO} + \epsilon) \frac{A_{IM}}{2} \cos[(\omega_{LO} - \omega_{IM})t + \theta]$$

$$x_C(t) = A_{LO} \left[ \frac{A_{RF}}{2} \cos(\omega_{LO} - \omega_{RF})t - \frac{A_{IM}}{2} \cos(\omega_{LO} - \omega_{IM})t \right]$$

$$x_D(t) = x_B(t) + x_C(t)$$

$$= y_{IF}(t) + y_{IM}(t)$$

desired signal

fraction of  
down-converted image

$$y_{IF}(t) = (A_{LO} + \epsilon) \frac{A_{RF}}{2} \cos[(\omega_{LO} - \omega_{RF})t + \theta] \\ + \frac{A_{LO} A_{RF}}{2} \cos(\omega_{LO} - \omega_{RF})t$$

$$y_{IM}(t) = (A_{LO} + \epsilon) \frac{A_{IM}}{2} \cos[(\omega_{LO} - \omega_{IM})t + \theta] \\ - \frac{A_{LO} A_{IM}}{2} \cos(\omega_{LO} - \omega_{IM})t$$

$$\left. \begin{array}{l} \text{Image-to-} \\ \text{signal ratio} \end{array} \right\} = \frac{\text{image power @ IF port}}{\text{signal power @ IF port}}$$

$$= \frac{A_{IM}^2}{A_{RF}^2} \cdot \frac{A^2 - 2AB \cos \theta + B^2}{A^2 + 2AB \cos \theta + B^2}$$

where  $A = A_{LO}$ ;  $B = A_{LO} + \epsilon$

Note that : image-to-signal ratio @ input =  $\frac{A_{IM}^2}{A_{RF}^2}$

Define Image Rejection Ratio (IRR) as

$$IRR = \frac{\text{Image-to-signal ratio @ output}}{\text{" " @ input}}$$

$$= \frac{A^2 - 2AB \cos \theta + B^2}{A^2 + 2AB \cos \theta + B^2}$$

If  $\epsilon \ll A_{LO}$  &  $\theta \ll 1$  rad,

$$IRR = \frac{(\Delta A/A)^2 + \theta^2}{4}$$

where  $\frac{\Delta A}{A} = \frac{\epsilon}{A_{LO}}$


typical IC matching:

$$1RR \sim 30-40dB$$

$$\frac{\Delta A}{A} \sim 0.2-0.6dB$$

$$\theta \sim 1 \text{ to } 5^\circ$$

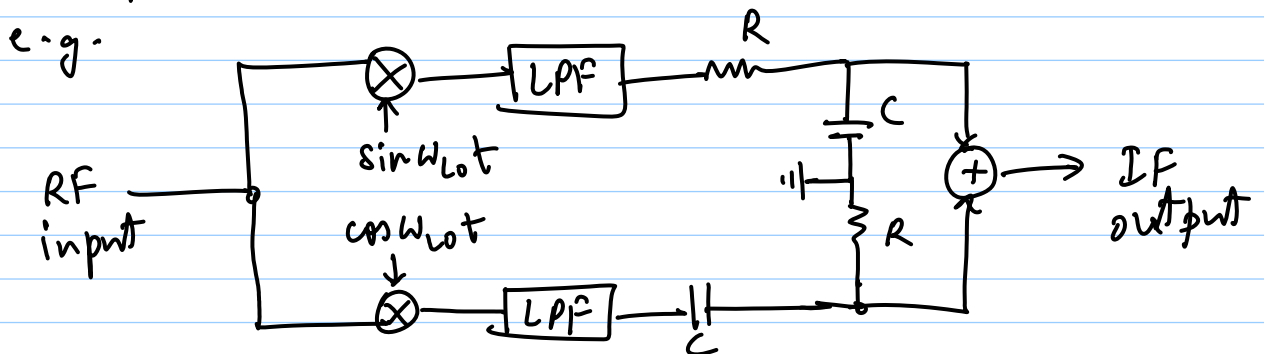\* Gain mismatch from  $90^\circ$  phase shift operation is critical



Say, resistors are  $R, R+\Delta R$   
caps are  $C, C+\Delta C$

Remember: equal gains only @  $\omega_{IF} = \frac{1}{RC}$

$\Rightarrow$  Gain imbalance is a function

of process, temperature

$$\frac{\Delta A}{A} = \frac{(R+\Delta R)(C+\Delta C)\omega - 1}{\sqrt{1 + (R+\Delta R)^2(C+\Delta C)^2\omega^2}} \div \frac{1}{\sqrt{1 + R^2C^2\omega^2}}$$

using  $RC\omega \approx 1$  around  $\omega_{IF}$ ,

$$\frac{\Delta A}{A} \approx \frac{\frac{\Delta R}{R} + \frac{\Delta C}{C}}{\sqrt{2 + \frac{\Delta R}{R} + \frac{\Delta C}{C}}} \div \frac{1}{\sqrt{2}} \approx \frac{\Delta R}{R} + \frac{\Delta C}{C}$$

$$\frac{\Delta R}{R} = 20\% \Rightarrow 1RR \sim 20dB !$$



\* Frequency deviation can cause gain imbalance

→ image cancellation only @  $\omega_{IF} = \frac{1}{RC}$

→ if  $\omega_{channel} \ll \omega_{IF}$ , IRR can degrade near edges of channel

\* We want overall image suppression  $\sim 60-70dB$


→ large IF = better image attenuation

+ 1R arch. can give 60-70dB

\* Linearity of adder is critical (adjacent channel interfer)

\* Noise & lots of  $90^\circ$  stage are significant


## 2) Weaver Architecture

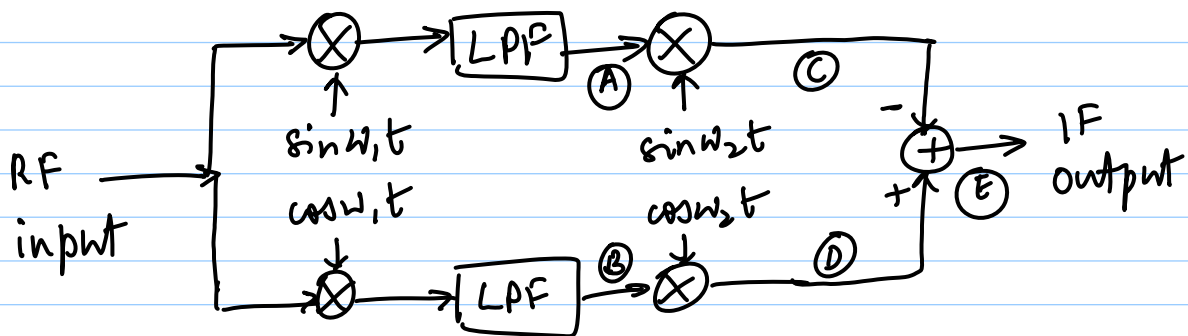

Second quadrature mixer → performs  $90^\circ$  operation  
assume  $\omega_2 \ll \omega_1$

$X_A(\omega)$  is convolved with  $\frac{j}{2} [\delta(\omega + \omega_2) - \delta(\omega - \omega_2)] \rightarrow X_C(\omega)$

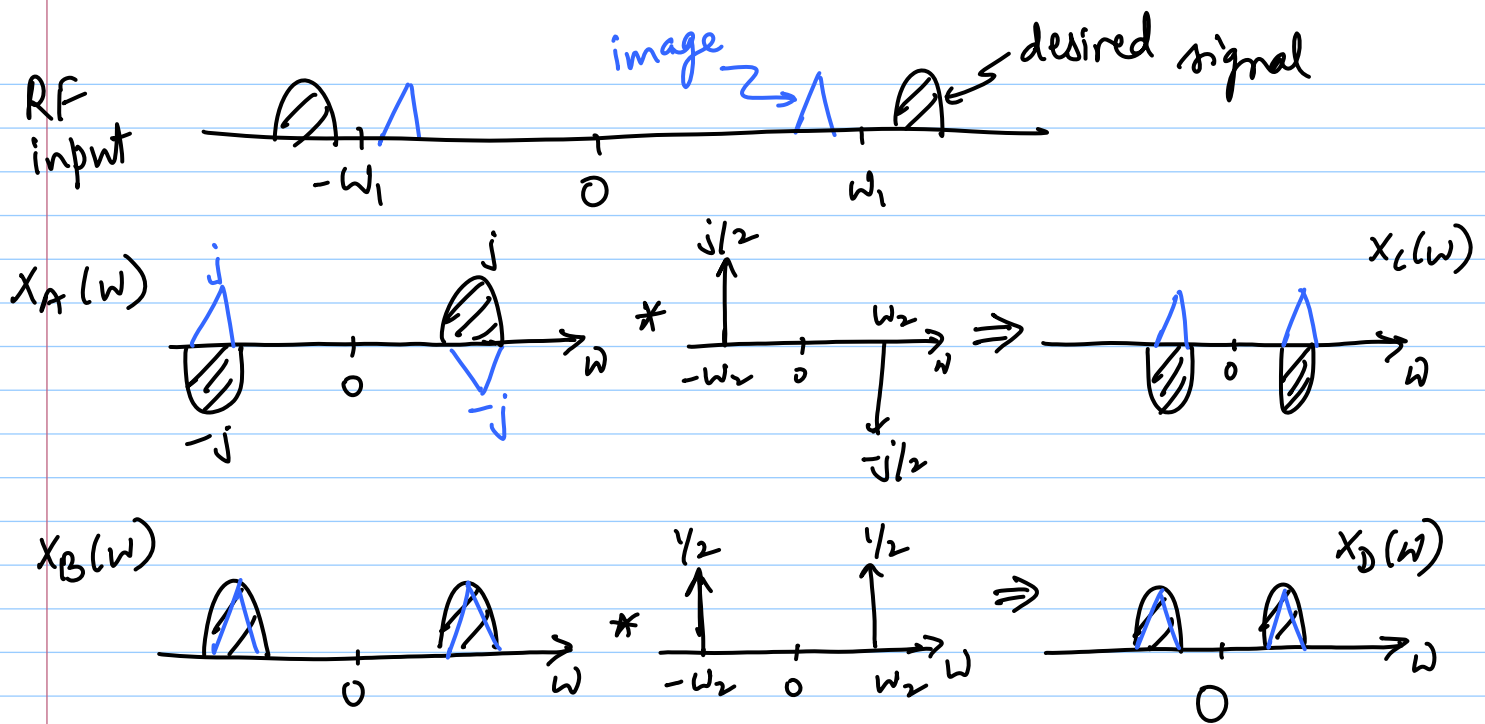
$X_B(\omega)$  is convolved with  $\frac{1}{2} [\delta(\omega + \omega_2) + \delta(\omega - \omega_2)] \rightarrow X_D(\omega)$



$X_D(\omega) - X_C(\omega)$  gives the desired output  
(signal additive, image cancels)

\* image is still present @  $\omega_2 + \omega_{IF}$  &  $-(\omega_2 + \omega_{IF})$   
→ LPF @ output

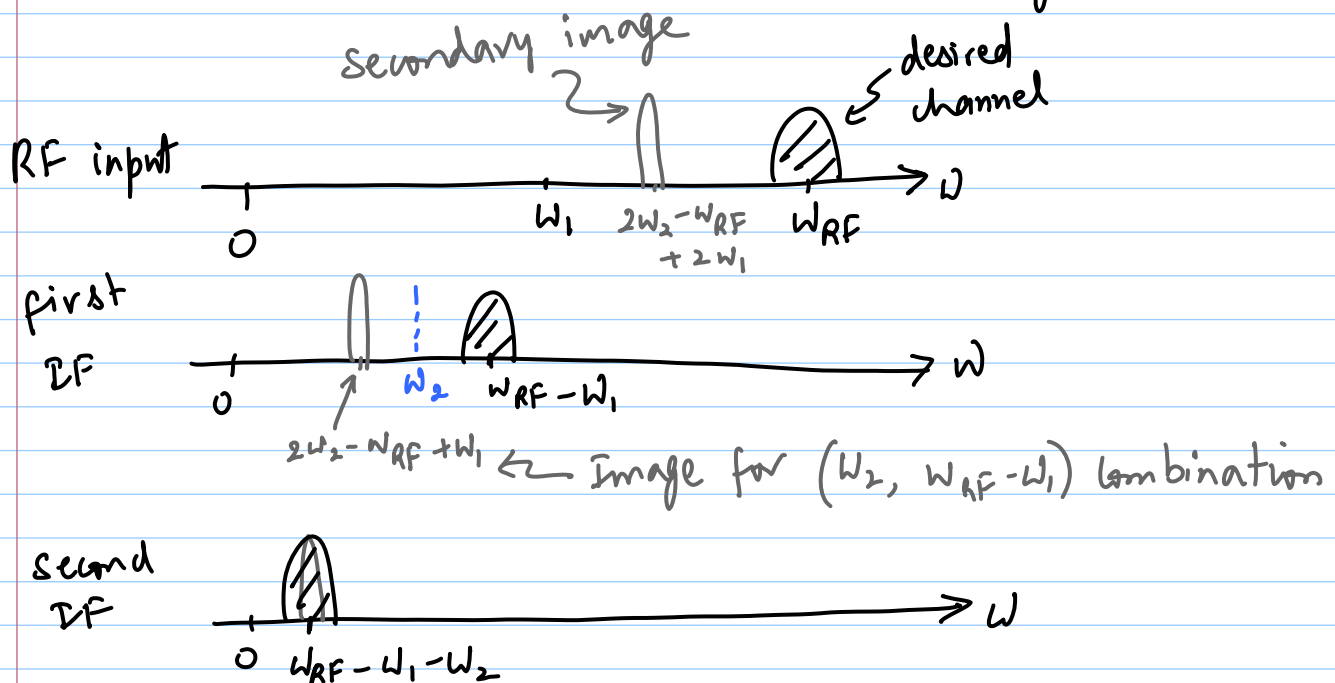\* If final  $\omega_{IF} \neq 0$  → "secondary image" problem



\* interferer is on same side of LO as desired RF

\* LPF should be replaced by BPFs to suppress "secondary image"

\*  $\omega_1 \pm \omega_2 = \omega_{RF} \Rightarrow$  final output is @ BB  
 $\rightarrow$  no secondary image