

SAN JOSÉ STATE UNIVERSITY

EE178 Spring 2017

Lecture Module 5

Eric Crabill

Goals

- ❖ Considerations for synchronizing signals
 - Clocks
 - Resets
- ❖ Considerations for asynchronous inputs
- ❖ Methods for crossing clock domains

Clocks

- ❖ The “academic” clock distribution is one that would deliver clock events to all synchronous elements in the system with zero delay, zero skew, and zero jitter
 - This is what you see in functional simulation
 - Not representative of physical reality
- ❖ Some designs can actually make constructive use of clock delay and clock skew

- ❖ Most FPGA devices have special routing intended for use with high fan-out, low skew signals such as clocks
 - Typically a limited (precious) resource
 - Usually driven by a “global buffer” primitive
 - Synthesis tool usually infers these
 - You can instantiate them if you want
 - Better delay and skew characteristics than normal routing resources

Clocks

- ❖ Since most FPGA devices have a limited number of these clock distribution resources, it makes sense to minimize the number of unique clocks in your design
 - Avoid “gating the clock”, use clock enables instead
 - Avoid things like ripple counters
- ❖ Side benefit is that your static timing analysis will be less complicated!

Resets

- ❖ Most designs use other synchronization signals, “resets”, to put the design in a known (initial) state
- ❖ This state does not need to be all zero or all one, it can be whatever you need
- ❖ You may not need (or want) to initialize every state element
- ❖ Reset signals can be synchronous (to the system clock) or asynchronous

Synchronous Resets

- ❖ You may consider a synchronous reset as “just another synchronous input” to state elements in the design
- ❖ The synchronous reset will have priority over other inputs, such as the D input
- ❖ When the reset is asserted and the clock event takes place, the flip-flop will transition

Synchronous Resets

- ❖ A synchronous reset input to a flip flop has the same timing requirements as other synchronous inputs to the flip-flop
- ❖ If the synchronous reset signal is from an external source, it must meet input setup and hold requirements
- ❖ If the synchronous reset signal is coming from an internal source (say, another flip flop), it must meet the period requirement

Asynchronous Resets


- ❖ An asynchronous reset is not synchronized to the clock; when it is asserted, the state element will immediately transition
- ❖ Typically, these types of asynchronous control signals have priority over all other inputs to the flip-flop, even the clock
- ❖ No clock event is needed for asynchronous resets to work

Asynchronous Resets

- ❖ In contrast to a synchronous reset, this reset has a potential problem when deasserted
 - It can occur at any time, even near clock edges
 - Skew on the signal distribution can result in different portions of the design “waking up” at different times, sending the design into some state other than what was intended
 - Can build logic in such a way that waking up in the wrong state is either harmless or correctable

Asynchronous Resets

```
module hang_yourself (  
    output reg  detonate,  
    input  wire clk,  
    input  wire rst  
);  
  
    reg flop1, flop2;  
  
    always @(posedge clk or posedge rst)  
    begin  
        if (rst) flop1 <= 1'b0;  
        else flop1 <= !flop1;  
    end  
  
    always @(posedge clk or posedge rst)  
    begin  
        if (rst) flop2 <= 1'b0;  
        else flop2 <= !flop2;  
    end  
  
    always @(posedge clk or posedge rst)  
    begin  
        if (rst) detonate_warhead <= 1'b0;  
        else detonate_warhead <= flop1 ^ flop2;  
    end  
  
endmodule
```

 

Xilinx FPGA Resets

- ❖ Xilinx FPGA global control signals
 - GSR, the global set/reset
 - GTS, the global three state control
- ❖ These are used to keep the FPGA “well behaved” while your design is being loaded
 - All flip flops are held in their initial state by GSR
 - All chip outputs are held in three-state by GTS

Xilinx FPGA Resets

- ❖ After your design is loaded, GSR and GTS are released; your design begins to operate
- ❖ Key point to note: GSR is an asynchronous reset and it's connected globally, even if you didn't code any resets in your RTL at all
- ❖ Remind me, why is this important?

Asynchronous Inputs

- ❖ Asynchronous inputs, like buttons, switches, and anything not synchronized to the system clock will inevitably cause input setup or input hold violations
 - May not be an issue on data path circuits
 - Can be fatal on control circuits
 - Why is metastability a problem?

Asynchronous Inputs

- ❖ Synchronizer circuits add delay (latency)
- ❖ Synchronizer circuits are not guarantees
 - Place flops close to each other to minimize delay
 - How good is good enough? (MTBF calculations)
- ❖ When a signal comes on-chip, synchronize it once and then fan signal out as required
 - Do not fan out, then synchronize at multiple places
 - Variations in timing can create different results

Clock Domains

- ❖ A clock domain is a group of logic elements and related signals that are synchronized to one clock
- ❖ The emphasis of this course and the labs is fully synchronous design -- that is, design with only one clock domain
- ❖ Many designs do not fit into this “paradigm”

Clock Domains

❖ Why would you have multiple clock domains?

- Independent sub-systems with different reference clocks, needing to share/exchange information
- Impractical to distribute or use a reference clock
- Many other reasons, I'm sure...

❖ How may clocks in two domains be related?

- Synchronous (degenerate case, same clock)
 - Same frequency
 - Zero phase difference

❖ How may clocks in two domains be related?

– Derived, Synchronous

- Frequencies related to a common reference
- Phase difference is a function of time
- Example: Multiplied or divided clock from an MMCM

– Mesochronous

- Same frequency
- Constant phase difference
- Example: Phase shifted clock from an MMCM

❖ How may clocks in two domains be related?

– Plesiochronous

- Different frequencies, nominally the same
- Phase difference is slowly varying
- Example: Two oscillators, both marked 1.000000 MHz

– Asynchronous

- Different frequencies or non-periodic clocks
- Arbitrary phase difference
- Example: Two clocks of unknown relationship



Crossing Clock Domains

- ❖ For asynchronous clock domain relationships:
 - For a single signal, use a synchronizer like you do for asynchronous inputs
 - For multi-bit signals, simply synchronizing each of the bits is not sufficient because each instance of the synchronizer may resolve at different times
 - No way to know when multi-bit quantity is valid, other than waiting a long time...
 - Use four phase or two phase handshaking (a single point of synchronization)

Crossing Clock Domains

- ❖ For asynchronous clock domain relationships:
 - Four phase handshaking (RTZ, level based flags)
 - Source domain provides DATA and asserts its VALID flag
 - Destination domain sees synchronized VALID flag assert and takes DATA, then asserts its ACK flag
 - Source domain sees synchronized ACK flag assert and deasserts its VALID flag
 - Destination domain sees synchronized VALID flag deassert and deasserts its ACK flag
 - Process can then repeat...

Four Phase Handshake

 
 


[Adapted from VLSI Architectures Spring 2004 www.ee.technion.ac.il/courses/048878 by Ran Ginosar]

Crossing Clock Domains

- ❖ For asynchronous clock domain relationships:
 - Two phase handshaking (NRZ, transition flags)
 - Source domain provides DATA and changes VALID flag
 - Destination domain sees synchronized VALID flag change and takes DATA, then changes its ACK flag
 - Source domain sees synchronized ACK flag change
 - Process can then repeat...

Two Phase Handshake

  

[Adapted from VLSI Architectures Spring 2004 www.ee.technion.ac.il/courses/048878 by Ran Ginosar]

Crossing Clock Domains

- ❖ For asynchronous clock domain relationships:
 - For bulk data transfer, but low bandwidth, use memory with handshaking to indicate which domain is in control at a given time
 - “Fill and spill” buffers -- high latency, low throughput
 - “Ping-pong” (double buffering) -- some improvement
 - With a dual ported RAM, can I be clever about this and start “spilling” while it’s still “filling”?

Crossing Clock Domains

- ❖ For asynchronous clock domain relationships:
 - Yes, it is called an asynchronous FIFO
 - Usually implemented with a dual ported memory
 - On the source (write) domain, data can be written into the FIFO as long as the FIFO is not FULL
 - On the destination (read) domain, data can be read out of the FIFO as long as the FIFO is not EMPTY
 - See “Simulation and Synthesis Techniques for Asynchronous FIFO Design” by Cliff Cummings

Crossing Clock Domains

- ❖ For other clock domain relationships:
 - There are a variety of other methods to deal with clock domain crossing, if more is known about the nature of the clock signals
 - Pretending things are asynchronous always works...



SAN JOSÉ STATE
UNIVERSITY