 



Inverter

Lecture 4

Advanced Digital IC Design



Khosrow Ghadiri

 


- Enhancement mode MOSFET transistor region of operation

	Cut-off	Resistive	Saturation
nMOS	$V_{GSn} < V_{Tn}$ $V_{IN} < V_{Tn}$	$V_{GSn} > V_{Tn}$ $V_{IN} > V_{Tn}$ $V_{DSn} < V_{GSn} - V_{Tn}$ $V_{OUT} < V_{IN} - V_{Tn}$	$V_{GSn} > V_{Tn}$ $V_{IN} > V_{Tn}$ $V_{DSn} > V_{GSn} - V_{Tn}$ $V_{OUT} > V_{IN} - V_{Tn}$
pMOS	$V_{GS p} > V_{Tp}$ $V_{IN} > V_{Tp} + V_{DD}$	$V_{GS p} < V_{Tp}$ $V_{IN} < V_{Tp} + V_{DD}$ $V_{DS p} > V_{GS p} - V_{Tp}$ $V_{OUT} > V_{IN} - V_{Tp}$	$V_{GS p} = V_{Tp}$ $V_{IN} < V_{Tp} + V_{DD}$ $V_{DS p} < V_{GS p} - V_{Tp}$ $V_{OUT} < V_{IN} - V_{Tp}$



- Inverter operating regions

 
- ① nMOS Off
pMOS Res.
- ② nMOS Sat.
pMOS Res.
- ③ nMOS Sat.
pMOS Sat.
- ④ nMOS Res.
pMOS Sat
- ⑤ nMOS Res.
pMOS off






Inverter operating regions

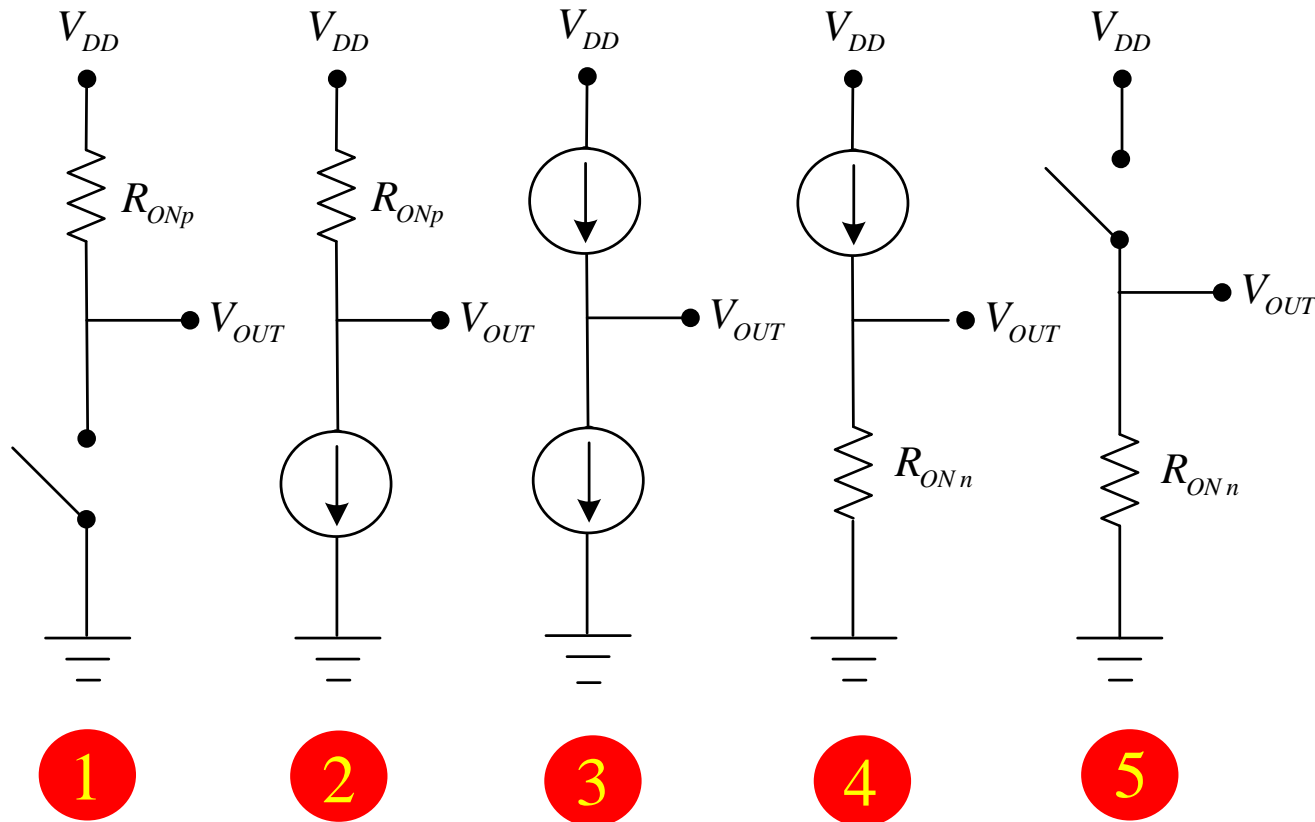- 1 nMOS Off
pMOS Res.
- 2 nMOS Sat.
pMOS Res.
- 3 nMOS Sat.
pMOS Sat.
- 4 nMOS Res.
pMOS Sat.
- 5 nMOS Res.
pMOS off



 

- Inverter operating regions


- **1** nMOS Off
pMOS Res.

$$I_{DSn} = -I_{DSp} = 0$$

$$V_{DSp} = V_{OUT} - V_{DD}$$

$$V_{DSp} = 0$$

$$V_{OUT} = V_{DD}$$

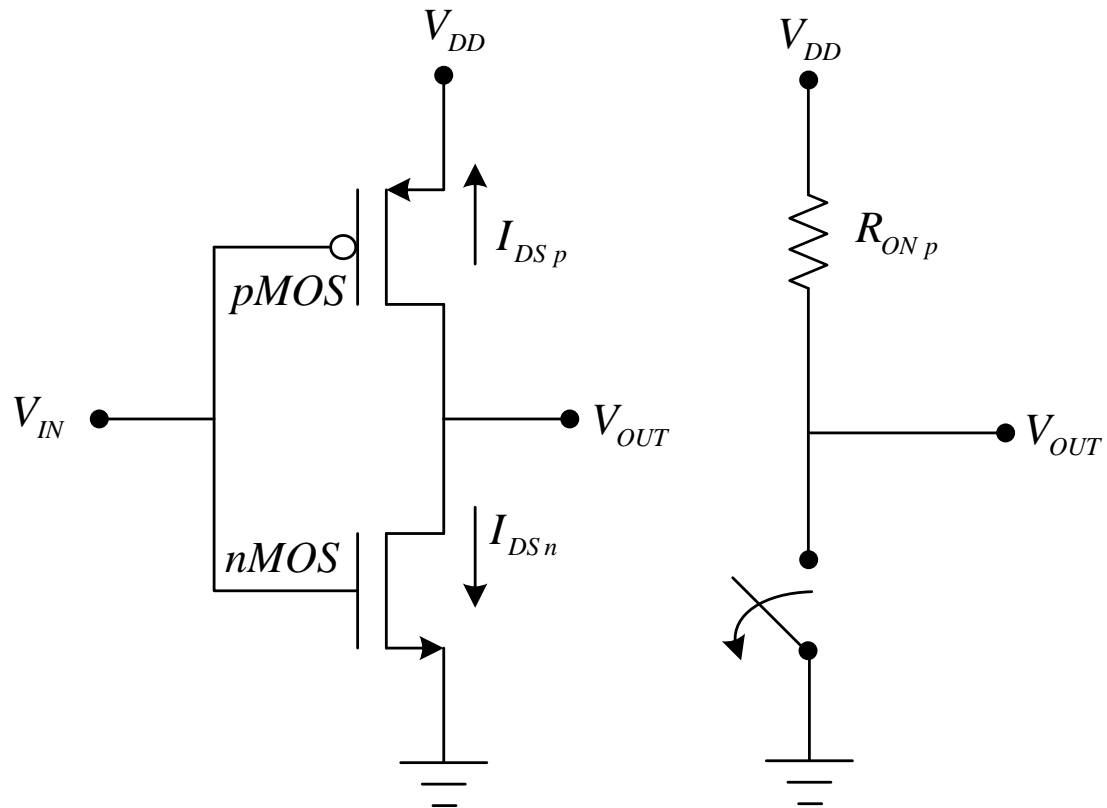



- Inverter operating regions

- 2** nMOS Sat.
 pMOS Res.


$$V_{IN} \leq V_{OUT} \leq \frac{V_{DD}}{2}$$

$$I_{DSn} = k_n \frac{(V_{IN} - V_{Tn})^2}{2}$$

$$V_{GS p} = V_{IN} - V_{Tn}$$


$$V_{DS p} = V_{OUT} - V_{DD}$$
 
$$I_{DS p} = -k_p \left[(V_{IN} - V_{DD} - V_{Tp})(V_{OUT} - V_{DD}) - \frac{(V_{OUT} - V_{DD})^2}{2} \right]$$





 - Inverter operating regions
- **2** nMOS Sat.
pMOS Res.



$$I_{DSn} = -I_{DSp}$$

$$V_{OUT} = (V_{IN} - V_{Tp}) + \sqrt{(V_{IN} - V_{Tp})^2 - 2 \left(V_{IN} - \frac{V_{DD}}{2} - V_{Tp} \right) V_{DD} - \frac{k_n}{k_p} (V_{IN} - V_{Tp})^2}$$



- Inverter operating regions
- **3** nMOS Sat.


pMOS Sat.

$$I_{DSn} = k_n \frac{(V_{IN} - V_{Tn})^2}{2}$$

$$I_{DSp} = -k_p \frac{(V_{IN} - V_{DD} - V_{Tp})^2}{2}$$

$$I_{DSn} = -I_{DSp}$$
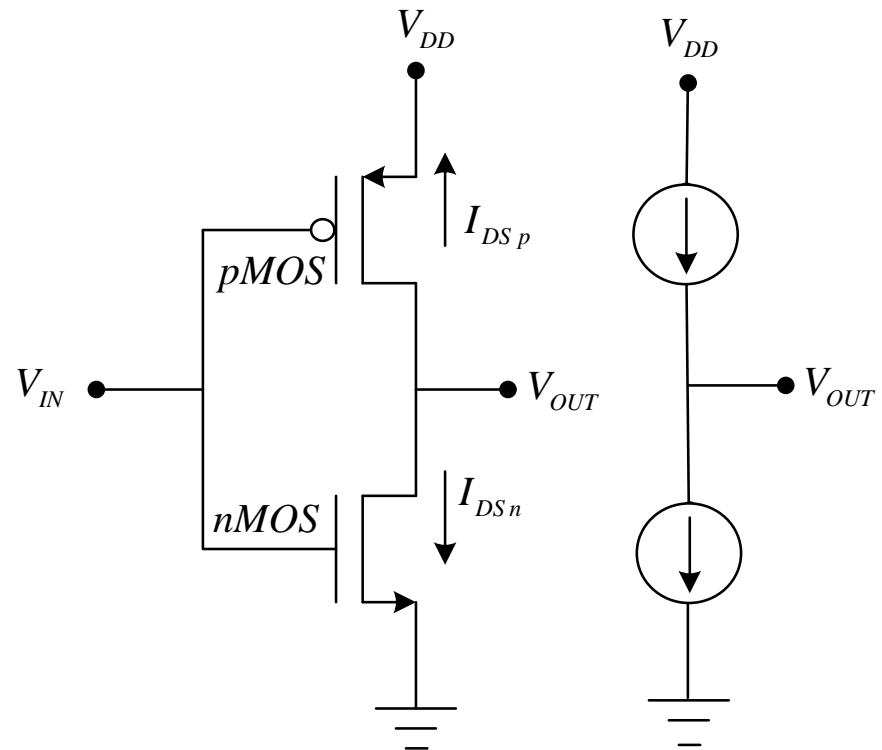
$$V_{IN} = \frac{V_{DD} + V_{Tp} + V_{IN} \sqrt{\frac{k_n}{k_p}}}{1 + \sqrt{\frac{k_n}{k_p}}}$$





- Inverter operating regions

- 4 nMOS Res.


pMOS Sat

$$I_{DSn} = k_n \left[(V_{IN} - V_{Tn}) V_{OUT} - \frac{V_{OUT}^2}{2} \right]$$

$$I_{DSp} = -k_p \frac{(V_{IN} - V_{DD} - V_{Tn})^2}{2}$$

$$I_{DSn} = -I_{DSp}$$
 
$$V_{OUT} = (V_{IN} - V_{Tn}) + \sqrt{(V_{IN} - V_{Tn})^2 - \frac{k_p}{k_n} \left(V_{IN} - \frac{V_{DD}}{2} - V_{Tp} \right)^2}$$






- Inverter operating regions


- **5** nMOS Res.
pMOS off

$$I_{DSp} = 0$$



$$V_{GS p} = V_{IN} - V_{DD}$$

$$V_{OUT} = 0$$

 

 

- Ideal Inverter

  



- Switching Threshold
- The switching threshold defined as a voltage
- Where



$$V_M = V_{OUT} = V_{IN}$$

- Since

$$V_{GS} = V_{DS}$$

- Both pMOS and nMOS are in saturation.
- For velocity saturation
- Ignoring the channel modulation $\lambda = 0$
  
$$k_n V_{DSn}(sat) \left(V_M - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right) + k_p V_{DSP}(sat) \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSP}(sat)}{2} \right) = 0$$





- Switching Threshold



$$V_M = \frac{\left(V_{Tn} + \frac{V_{DSATn}}{2} \right) + r \left(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2} \right)}{1 + r}$$

- Where r compares the relative strength of pMOS and nMOS

$$r = \frac{k_p V_{DSp} (sat)}{k_n V_{DSn} (sat)} = \frac{\mu_p (sat) W_p}{\mu_n (sat) W_n}$$

- For the $t_{ox} (pMOS) = t_{ox} (nMOS)$
  
$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}$$







- Switching Threshold
- For comparable high and low noise margin

$$V_M \approx \frac{rV_{DD}}{1+r} = \frac{V_{DD}}{2}$$

- Which requires $r = 1$
- Then the pMOS device should be sized to

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSn}(sat)}{k'_p V_{DSp}(sat)}$$

  - Making W_p wider results in $r > 1$ and move V_M upper than the middle closer to V_{DD} and increasing the strength of nMOS move the switching voltage V_M closer to GND.





- Switching Threshold

- For desired value of the threshold voltage V_M , the pMOS to nMOS transistor sizes to set



$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSn}(sat) \left(V_M - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right)}{k'_p V_{DSp}(sat) \left(V_{DD} - V_M + V_{Tp} + \frac{V_{DSp}(sat)}{2} \right)}$$

- For $V_{DS}(sat) > V_M - V_T$ where the saturation velocity is not occur, then

$$V_M = \frac{V_{Tn} + r(V_{DD} + V_{Tp})}{1 + r}$$

- Where

$$r = \sqrt{\frac{-k_p}{k_n}}$$

  

V_{DD}



- Noise Margin

- The input voltage high V_{IH} and out put voltage low is V_{IL} defined as

$$g = \frac{dV_{out}}{dV_{in}} = -1$$

- The piecewise linear approximation for VTC

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

- Then the V_{IH} is

$$V_{IH} = V_M - \frac{V_M}{g}$$

- The V_{IL}



$$V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

- and the high noise margin is

$$NM_H = V_{DD} - V_{IH}$$

- And the low noise margin is

- $$NM_L = V_{IL}$$

  



- Length Modulation
- Ignoring length modulation results in infinite gain
- Considering length modulation results in infinite gain

$$k_n V_{DSn}(sat) \left(V_{IN} - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right) (1 + \lambda V_{OUT})$$

$$+ k_p V_{DSp}(sat) \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{DSp}(sat)}{2} \right) (1 + \lambda_p V_{OUT} - \lambda_p V_{DD}) = 0$$

- Differentiating the output with respect to the input


$$\frac{dV_{out}}{dV_{in}} = \frac{k_n V_{DSn}(sat) (1 + \lambda_n V_{OUT}) + k_p V_{DSp}(sat) (1 + \lambda_p V_{OUT} - \lambda_p V_{DD})}{\lambda_n k_n V_{DSn}(sat) \left(V_{IN} - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right) + \lambda_p k_p V_{DSp}(sat) \left(V_{IN} - V_{DD} - V_{Tp} - \frac{V_{DSp}(sat)}{2} \right)}$$

- Ignoring some second-order terms and setting $V_{IN} = V_M$ results in gain

$$g = \frac{1}{I_{DS}(V_M)} \frac{k_n V_{DSn}(sat) + k_p V_{DSp}(sat)}{\lambda_n - \lambda_p} = \frac{1 + r}{\left(V_M - V_{Tn} - \frac{V_{DSn}(sat)}{2} \right) (\lambda_n - \lambda_p)}$$





- Device variation

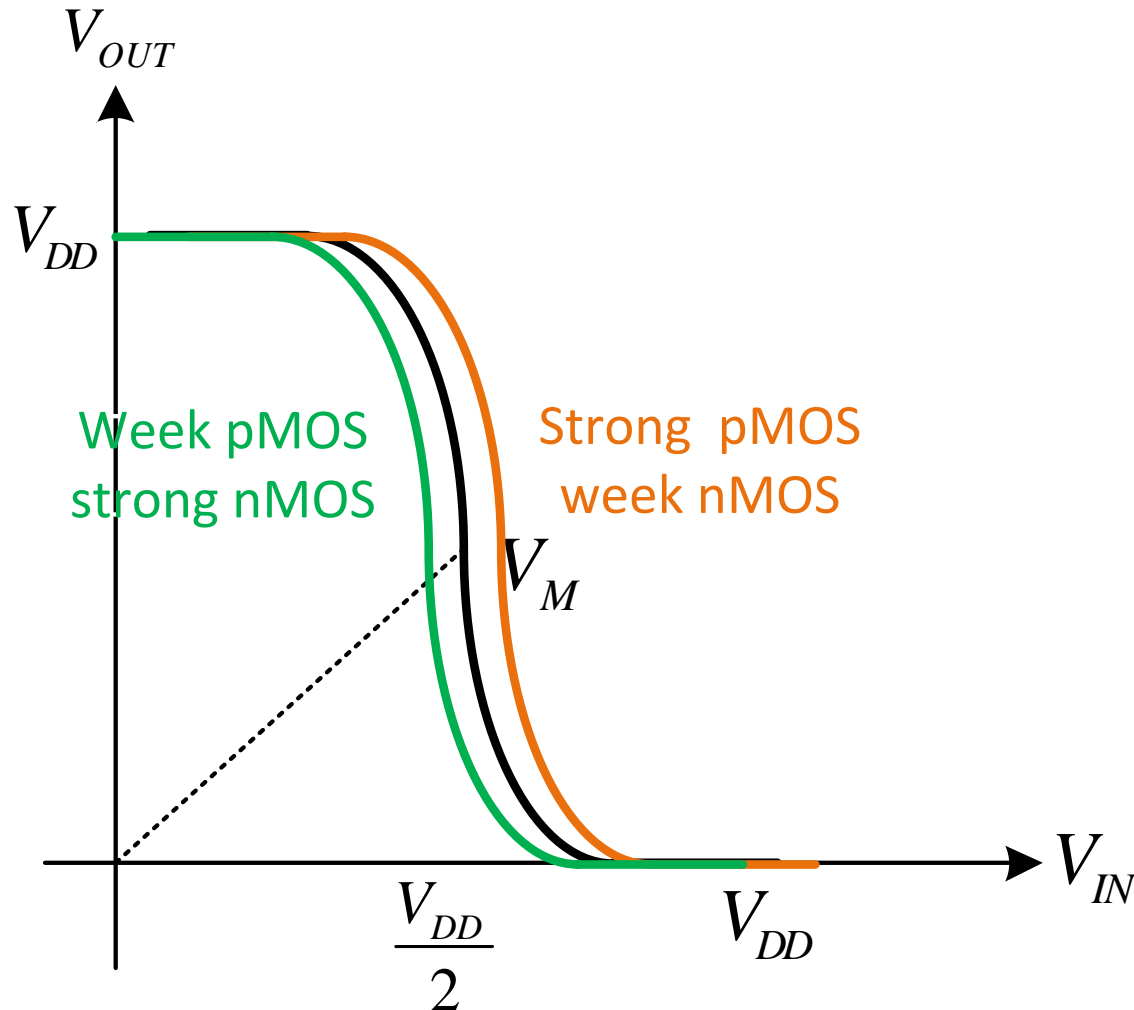




- Voltage supply scaling

 

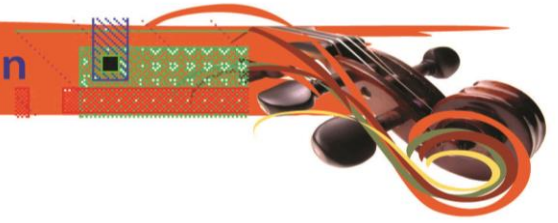


- Device variation

 



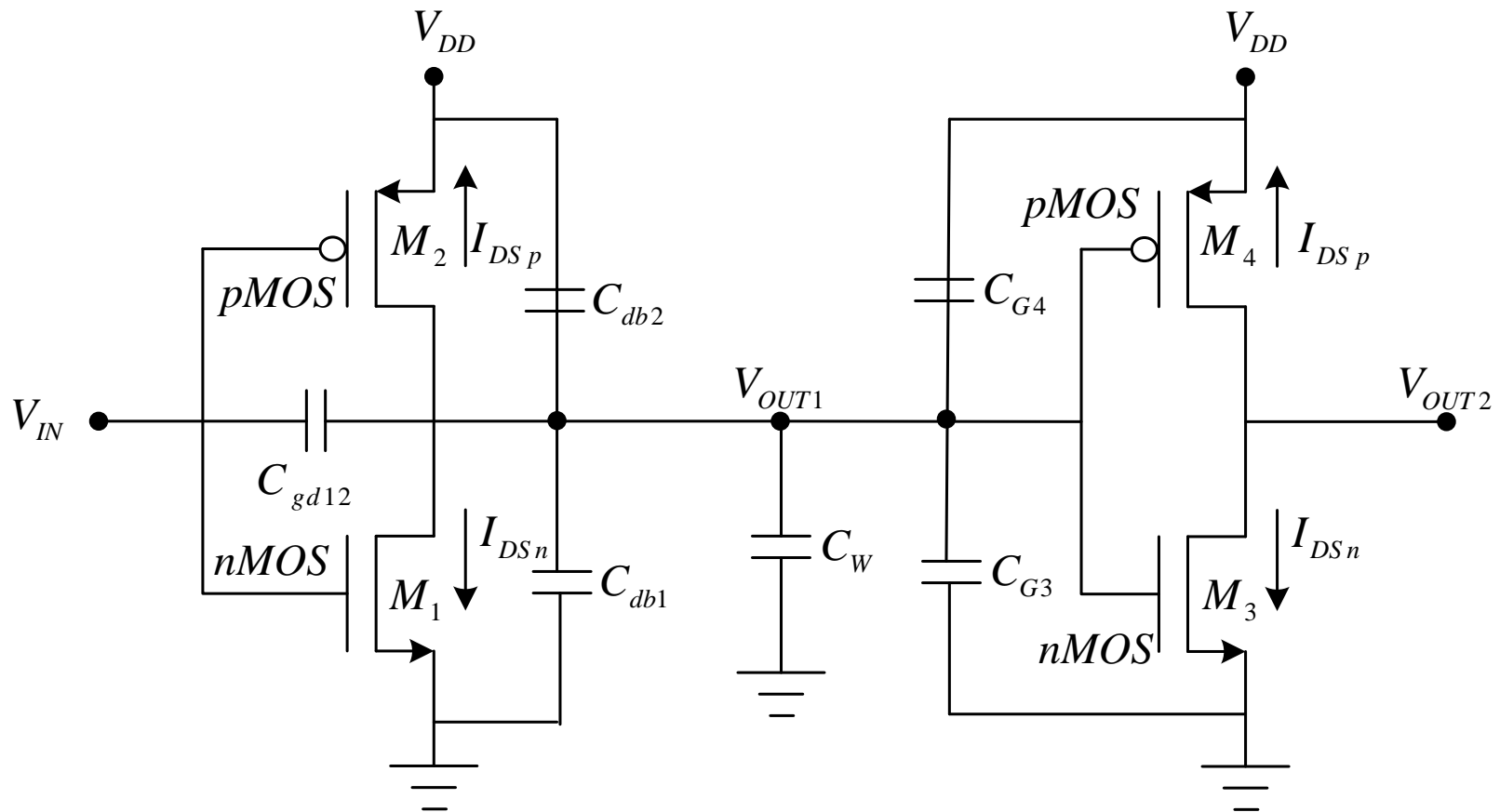- Effect of Capacitance (lumped capacitor model)






- Gate-Drain Capacitance
- The capacitance between the gate and drain C_{gd12} of the first inverter is overlap capacitance of M1 and M2.
- M1 and M2 are either in cut-off or in saturation mode during the first half of output transient.
- The gate-drain capacitance C_{gd12} with respect to ground in lumped circuit model.

$$C_{gd12} = 2C_{GD0}W$$

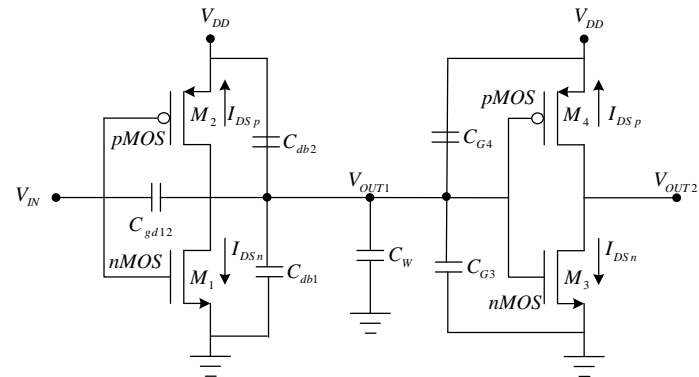- The factor of two is due to the Miller effect. The C_{GD0} is the overlapped capacitor





- Diffusion Capacitances
- The nonlinear voltage dependent diffusion capacitances C_{db1} and C_{db2} is due to the reversed bias pn-junction.
- The diffusion capacitor linearized over the voltage range of interest

$$C_{eq} = k_{eq} C_{jo}$$

- The C_{jo} is the junction capacitor per unit area under zero-bias condition.
- The bottom plate and sidewall zero bias value as can be obtained from the SPICE model CJ and CJSW.
- The k_{eq} is

$$k_{eq} = \frac{-V_0^m}{(V_{high} - V_{low})(1-m)} \left[(V_0 - V_{high})^{1-m} - (V_0 - V_{low})^{1-m} \right]$$



- Wire Capacitance
- The wire capacitance. C_w Depends on length and width of interconnecting wire



- Gate Capacitances
- The gate capacitances C_{g3} and C_{g4} includes both overlap and gate capacitance of each transistor.

$$\begin{aligned} C_{fan-out} &= C_{gate}(nMOS) + C_{gate}(pMOS) \\ &= (C_{GSON} + C_{GDO_n} + W_n L_n C_{OX}) + (C_{GSOP} + C_{GDO_p} + W_p L_p C_{OX}) \end{aligned}$$