

---

# EE288 Data Conversions/Analog Mixed-Signal ICs

## Spring 2018

### Lecture 15: DAC Introduction

Prof. Sang-Soo Lee  
[sang-soo.lee@sjsu.edu](mailto:sang-soo.lee@sjsu.edu)  
ENG-259


# Course Schedule – Subject to Change

Date	Topics
24-Jan	Course introduction and ADC architectures
29-Jan	Converter basics: AAF, Sampling, Quantization, Reconstruction
31-Jan	ADC dynamic performance metrics, Spectrum analysis using FFT
5-Feb	ADC & DAC static performance metrics, INL and DNL
7-Feb	OPAMP and bias circuits review
12-Feb	SC circuits review
14-Feb	Sample and Hold Amplifier - Reading materials
19-Feb	Flash ADC and Comparators: Regenerative Latch
21-Feb	Comparators: Latch offset, preamp, auto-zero
26-Feb	<del>Finish Flash ADC</del>
28-Feb	<del>DAC Architectures - Resistor, R-2R</del>
5-Mar	<del>DAC Architectures - Current steering, Segmented</del>
7-Mar	<del>DAC Architectures - Capacitor-based</del>
12-Mar	<del>SAR ADC with bottom plate sampling</del>
14-Mar	SAR ADC with top plate sampling
19-Mar	Midterm Review
21-Mar	Midterm exam
26-Mar	Spring break
28-Mar	Spring break
2-Apr	Pipelined ADC stage - comparator, MDAC, x2 gain
4-Apr	Pipelined ADC bit sync and alignment using Full adders
9-Apr	Pipelined ADC 1.5bit vs multi-bit structures
11-Apr	Fully-differential OPAMP and Switched-capacitor CMFB
16-Apr	Single-slope ADC
18-Apr	Oversampling & Delta-Sigma ADCs
23-Apr	Second- and higher-order Delta-Sigma Modulator.
25-Apr	Hybrid ADC - Pipelined SAR
30-Apr	Hybrid ADC - Time-Interleaving
2-May	ADC testing and FoM
7-May	Project presentation 1
8-May	Project presentation 2
14-May	Final Review
20-May	Project Report Due by 6 PM

← DAC 1


Midterm Exam on  
March 21

# DAC

 

$$V_{out} = V_{ref}(b_1 2^{-1} + b_2 2^{-2} + \cdots + b_N 2^{-N}) = V_{ref} B_{in}$$

# DAC

 

$N = \# \text{ of bits}$

$V_{FS} = \text{full scale output}$

$\Delta = \text{min. step size} \rightarrow 1\text{LSB}$

$$\Delta = \frac{V_{FS}}{2^N}$$


$$\text{or } N = \log_2 \frac{V_{FS}}{\Delta} \rightarrow \text{resolution}$$

# DAC Architectures


---

- Various D/A architecture
  - Resistor string DAC
  - Charge Redistribution DAC
  - Current source type
- Static performance
  - Limited by component matching
  - Architectures
    - Unit element
    - Binary weighted
    - Segmented
  - Performance improvement via dynamic element matching
- Dynamic performance
  - Limited by timing errors causing glitches


# Resistor String DAC

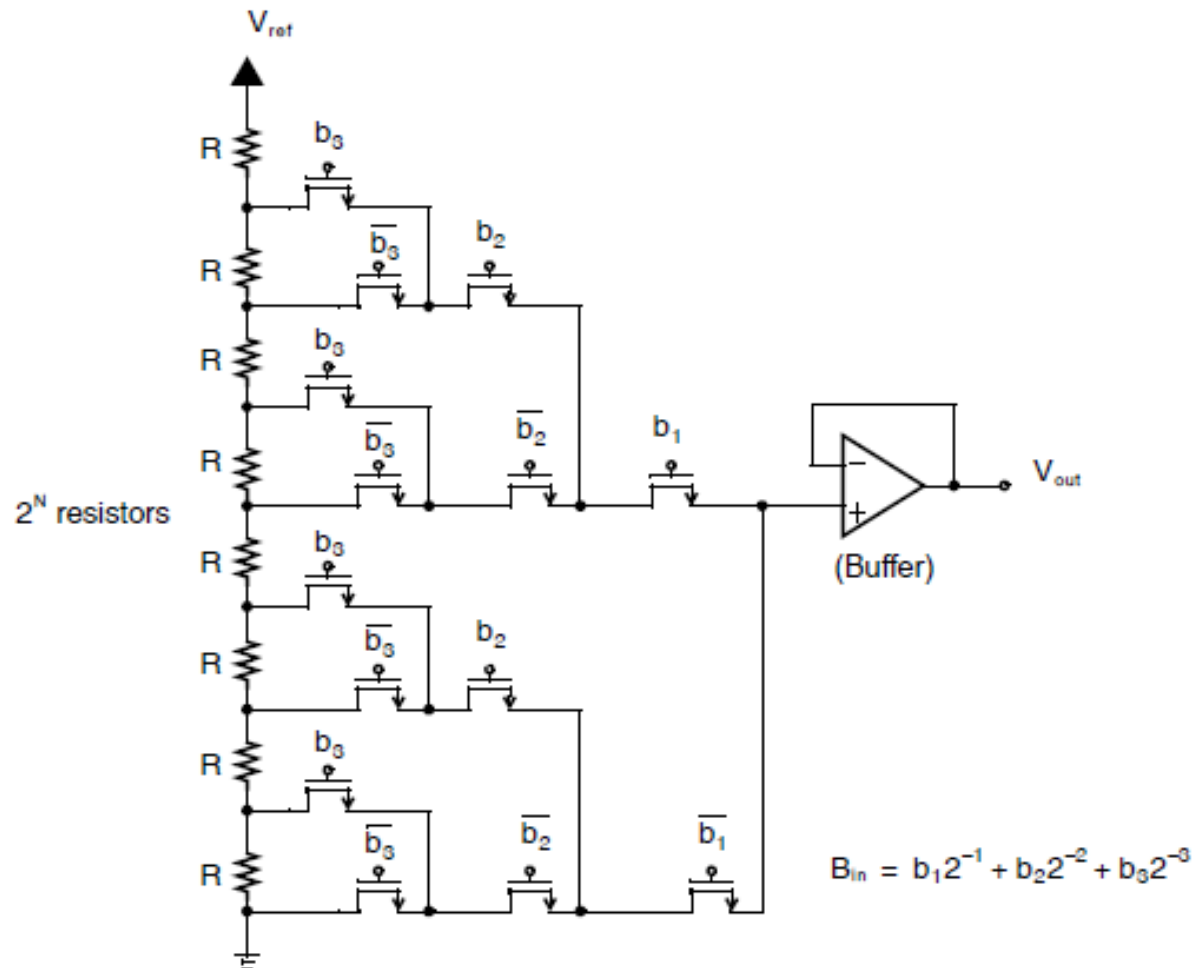

# Resistor String DAC with Decoder

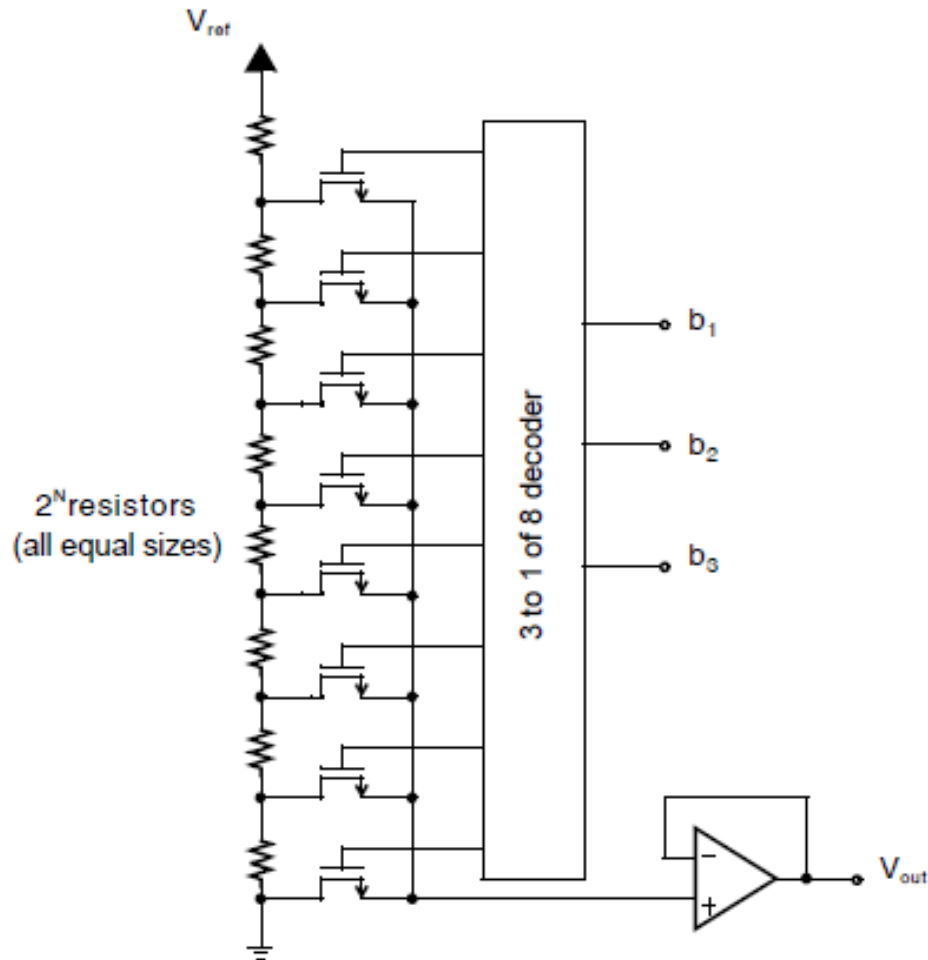


# Folded Resistor String DAC

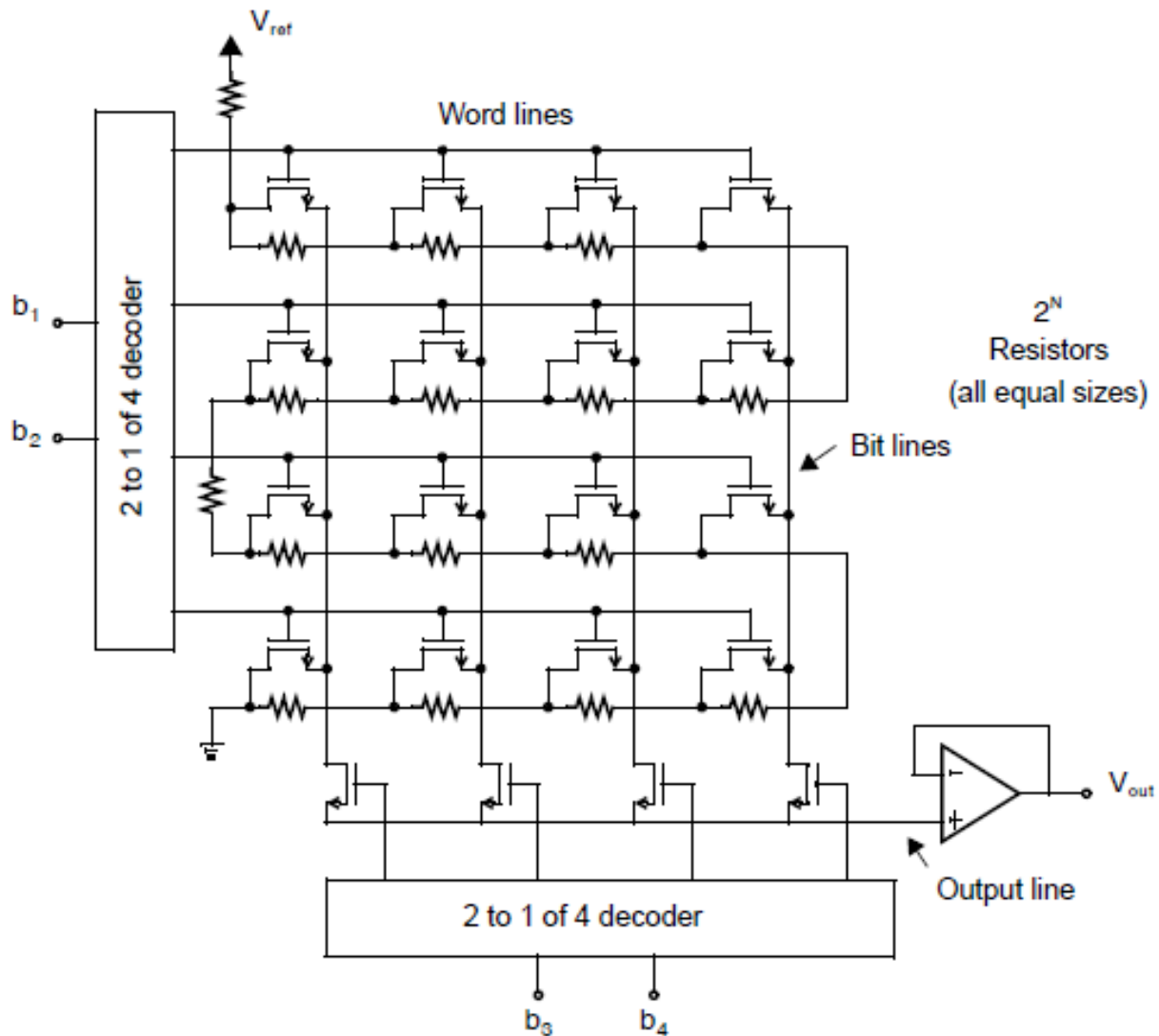




# Multiple Resistor String DAC

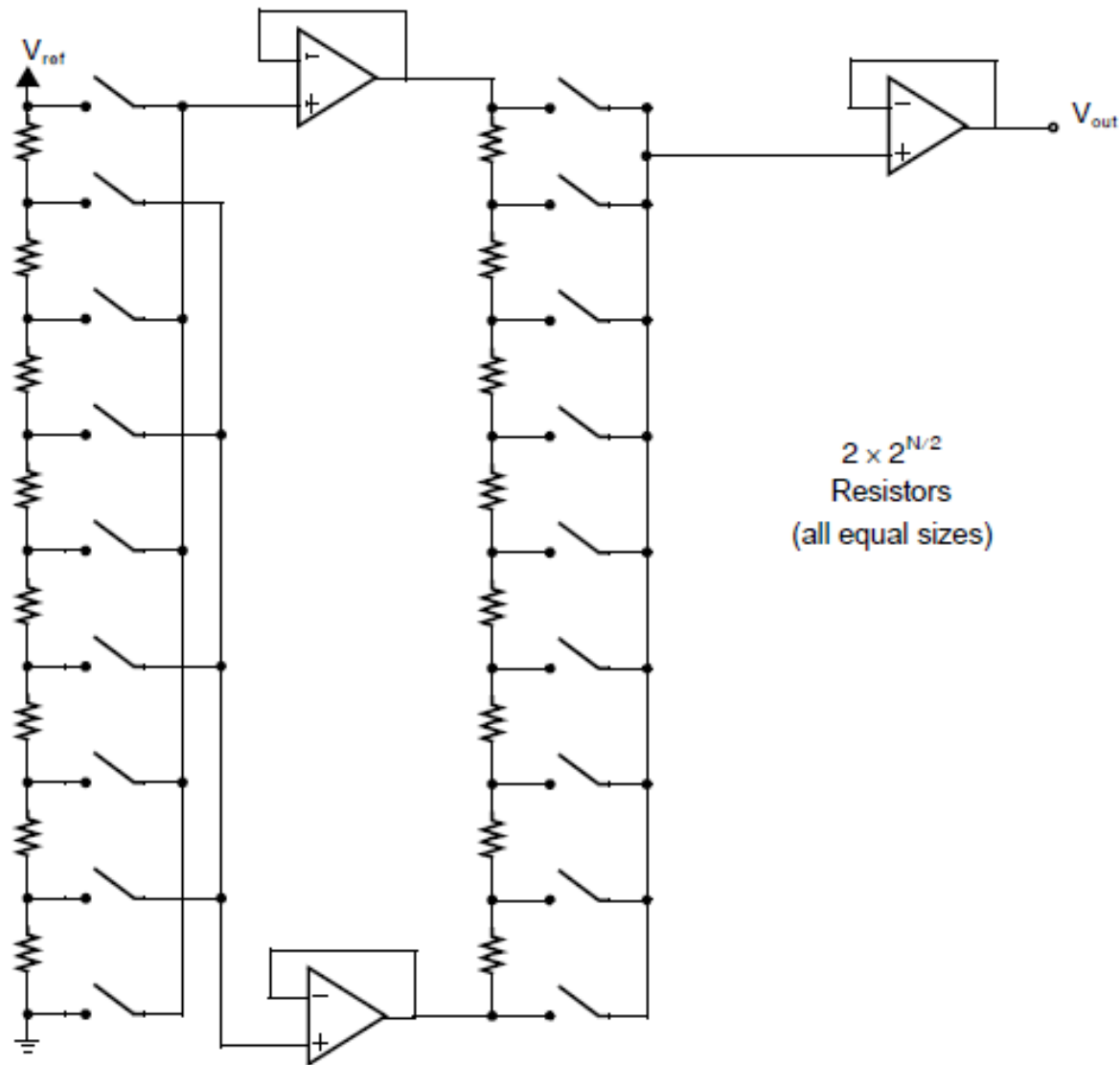
 
# Charge Redistribution DAC


- DAC operation based on capacitive voltage division



$$V_{out} = \frac{C_x}{C_x + C_y + C} V_{ref}$$

→ Make  $C_x$  &  $C_y$  function of incoming DAC digital word

# Charge Redistribution DAC


 


- E.g. “Binary weighted”
- B+1 capacitors & B switches  
(Cs built of unit elements →  
 $2^B$  units of C)

$$V_{out} = \frac{\sum_{i=0}^{B-1} b_i 2^i C}{2^B C} V_{ref}$$


# Charge Redistribution DAC

Example: 4Bit DAC- Input Code 1011

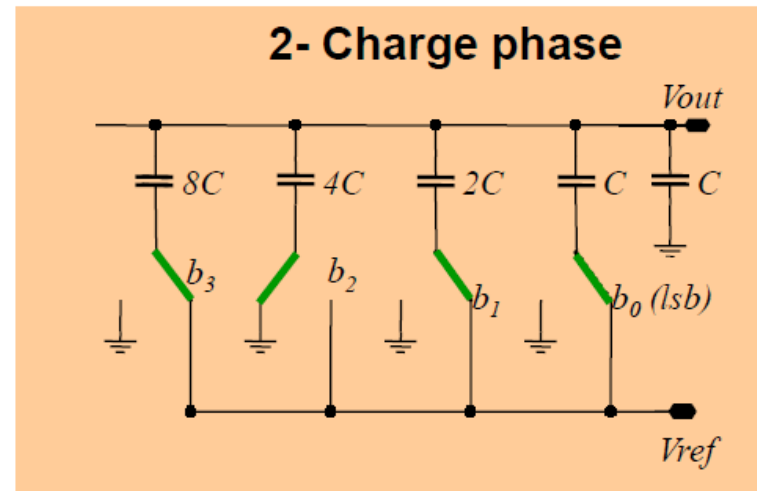 


$$V_{out} = \frac{2^0 C + 2^1 C + 2^3 C}{2^4 C} V_{ref} = \frac{11}{16} V_{ref}$$

# Charge Redistribution DAC

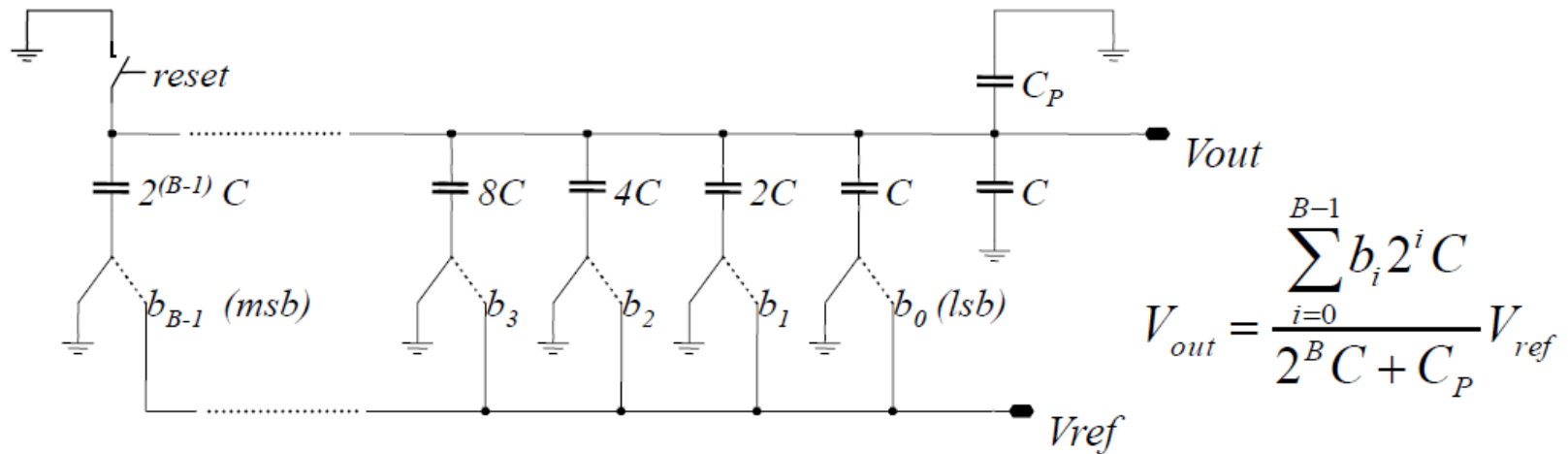

- Sensitive to parasitic capacitor @ output
  - If  $C_p$  constant  $\rightarrow$  gain error
  - If  $C_p$  voltage dependant  $\rightarrow$  DAC nonlinearity
- Large area of caps for high DAC resolution (10bit DAC ratio 1:512)
- Monotonicity depends on element matching (more later)


# Charge Redistribution DAC

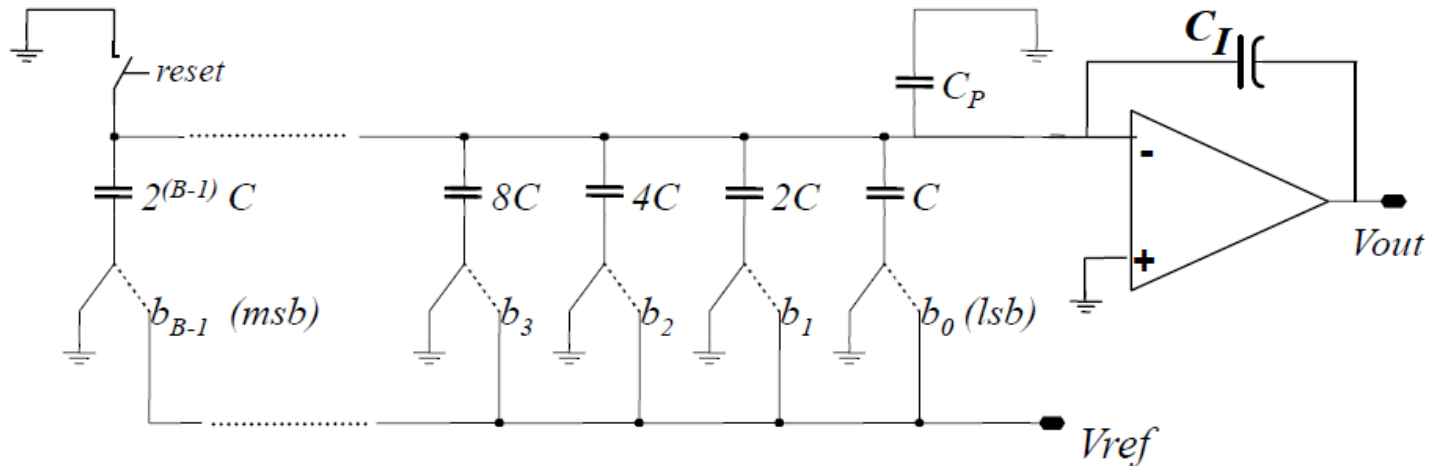

$$V_{out} = -\frac{\sum_{i=0}^{B-1} b_i 2^i C}{C_I} V_{ref}, \quad C_I = 2^B C \rightarrow V_{out} = -\frac{\sum_{i=0}^{B-1} b_i 2^i}{2^B} V_{ref}$$


- Opamp helps eliminate the parasitic capacitor effect by producing virtual ground at the sensitive node since  $C_P$  has zero volts at start & end
  - Issue: opamp offset & speed- also double capacitor area
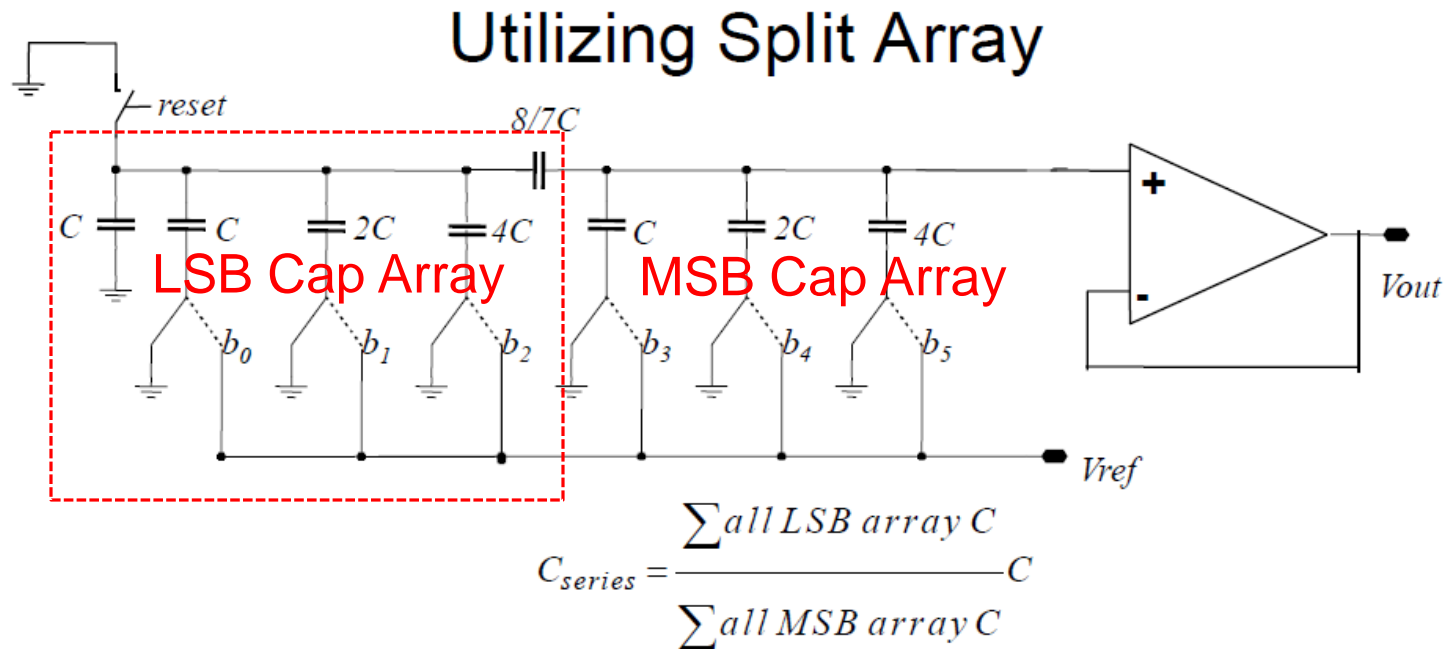
# Charge Redistribution DAC with Split Cap



- Split array → reduce the total area of the capacitors required for high resolution DACs
  - E.g. 10bit regular binary array requires 1024 unit Cs while split array (5&5) needs 64 unit Cs
  - Issue: Sensitive to series capacitance parasitic capacitor

# Bridge Cap

 

$$C = \frac{C_B C_L}{C_B + C_L}$$

$$C_B + C_L = C_B C_L$$


$$C_B(C_L - 1) = C_L$$

$$C_B(C_L - 1) = C_L$$

$$C_B = \frac{C_L}{C_L - 1}$$


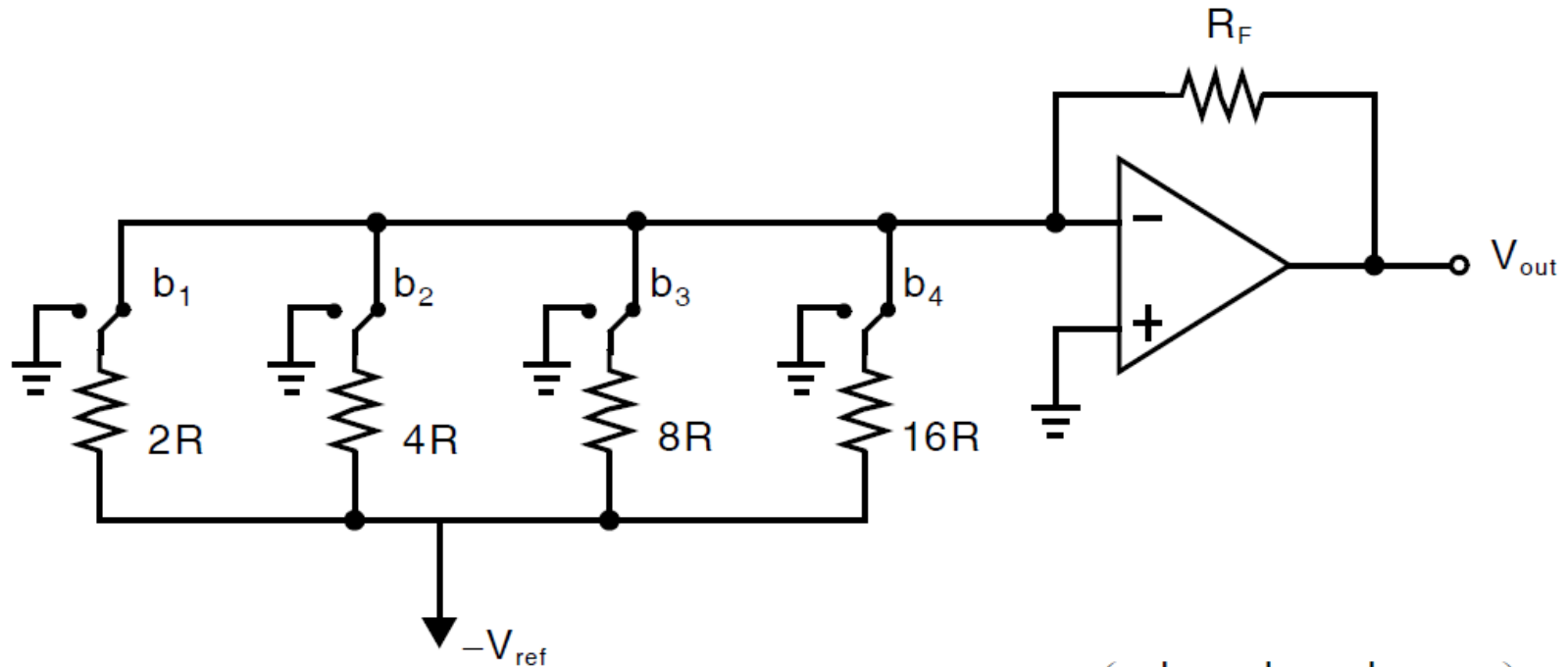
# Current Based DAC using Binary Weighted R




$$\begin{aligned} V_{out} &= -R_F V_{ref} \left( -\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} - \dots \right) \\ &= \left( \frac{R_F}{R} V_{ref} \right) B_{in} \end{aligned}$$

$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots$$

 
# Current Based DAC using R-2R Ladder

- R-2R DAC basics:
  - Simple R network divides both voltage & current by 2



Increase # of bits by replicating circuit

# R-2R Resistance Ladder

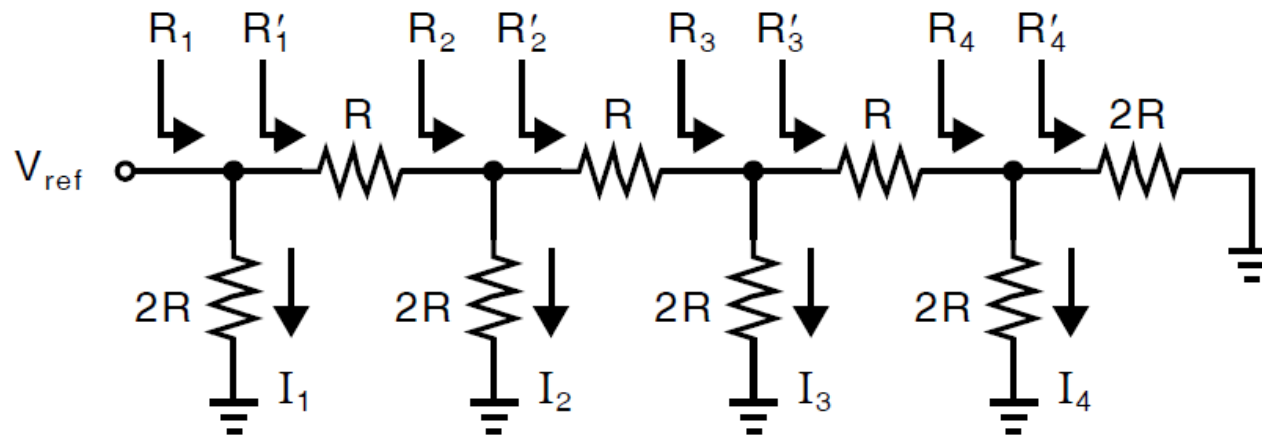


$$\begin{aligned}
 R'_4 &= 2R \\
 R_4 &= 2R \parallel 2R = R \\
 R'_3 &= R + R_4 = 2R \\
 R_3 &= 2R \parallel R'_3 = R
 \end{aligned}$$

$$I_1 = \frac{V_{\text{ref}}}{2R}$$

$$I_2 = \frac{V_{\text{ref}}}{4R}$$

$$I_3 = \frac{V_{\text{ref}}}{8R}$$

# Current Based DAC using R-2R Ladder

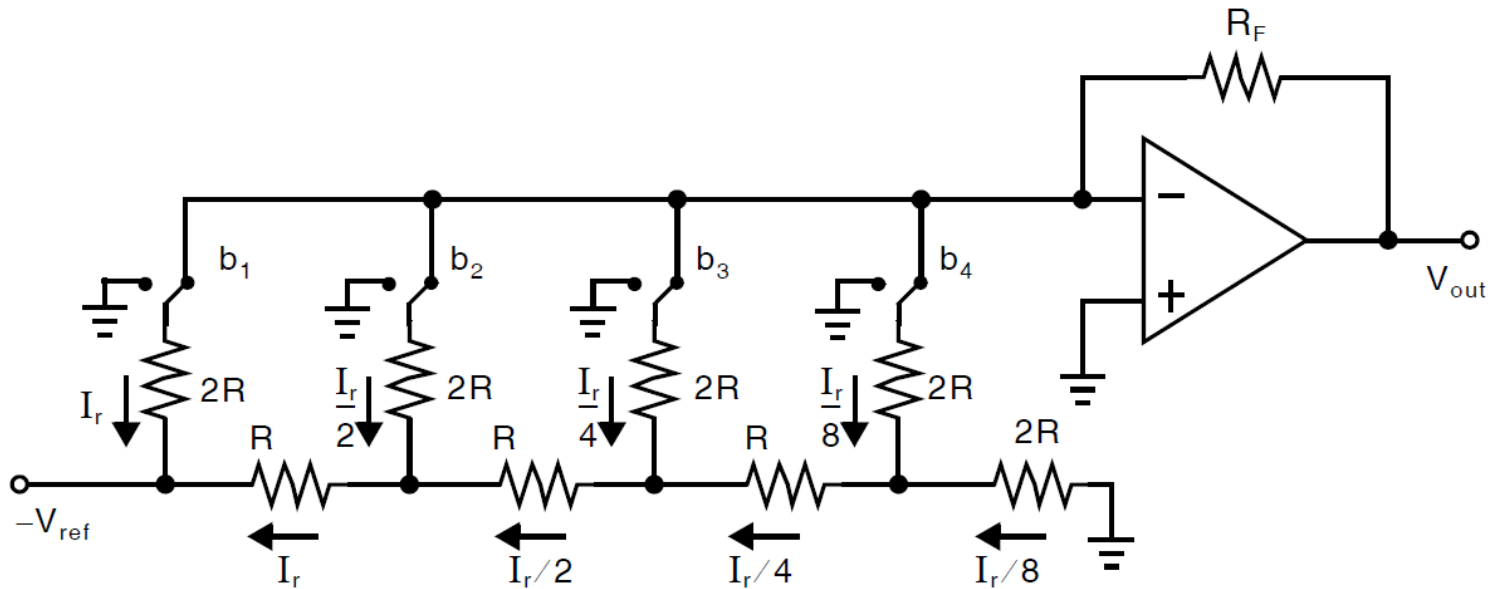


$$I_r = V_{ref}/(2R)$$

$$V_{out} = R_F \sum_{i=1}^N \frac{b_i I_r}{2^{i-1}} = V_{ref} \left( \frac{R_F}{R} \right) \sum_{i=1}^N \frac{b_i}{2^i}$$


**Key Point:** R-2R ladder D/A converters produce binary-weighted currents without the need for a complete array of binary-weighted resistors. Instead, only 2:1 component ratios are needed, a significant savings for high-resolution converters.

# Unit Element Current Source DAC

 


- “Unit elements” or thermometer
- $2^B - 1$  current sources & switches
- Suited for both MOS and BJT technologies
- Monotonicity does not depend on element matching and is guaranteed
- Output resistance of current source  $\rightarrow$  gain error
  - Cascode type current sources higher output resistance  $\rightarrow$  less gain error

# Unit Element DAC Principle

 


# Binary Weighted Current Source DAC

 


- “Binary weighted”
- B current sources & switches ( $2^B - 1$  unit current sources but less # of switches)
- Monotonicity depends on element matching  $\rightarrow$  not guaranteed

# Binary Weighted DAC Principle

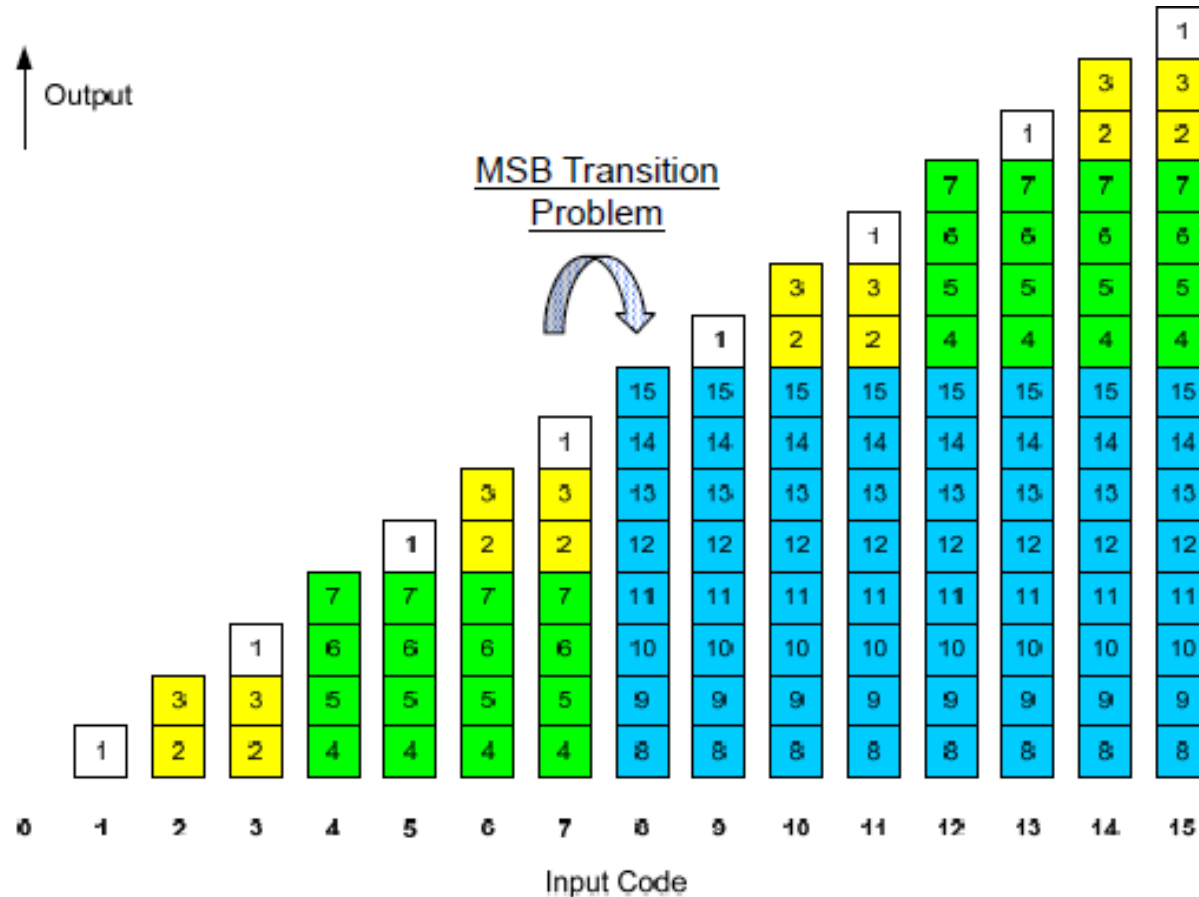




# Implementation of Weighted Elements

 
 
# Segmented DAC

- Objective:  
Compromise between unit-element and binary-weighted DAC



$$B_{Total} = B_1 + B_2$$

- Approach:  
 $B_1$  MSB bits  $\rightarrow$  unit elements  
 $B_2$  LSB bits  $\rightarrow$  binary weighted
- INL: unaffected same as either architecture
- DNL: Worst case occurs when LSB DAC turns off and one more MSB DAC element turns on  $\rightarrow$  Same as binary weighted DAC with  $(B_2+1)$  # of bits
- Number of switched elements:  $(2^{B_1}-1) + B_2$