
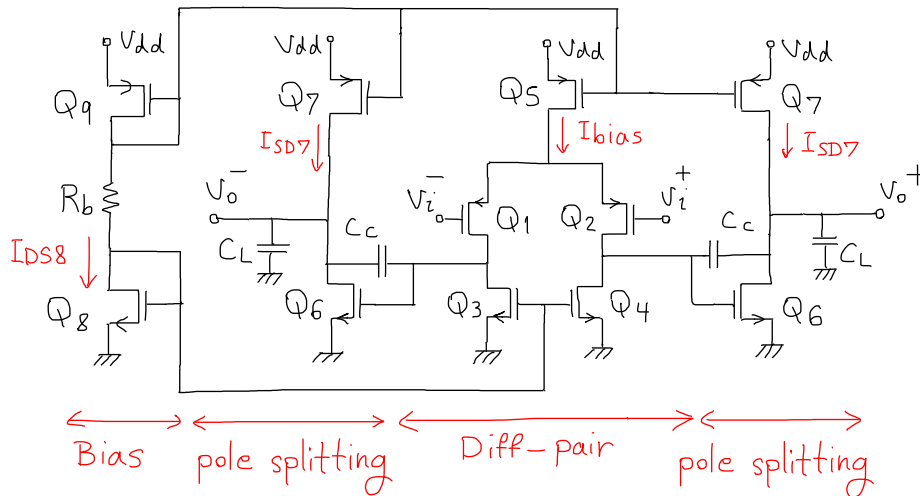


* Question:

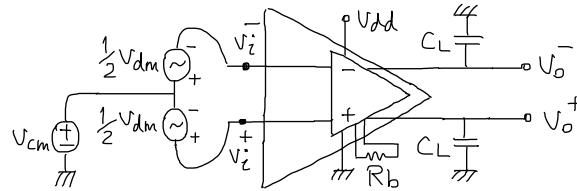

Q3 and Q4 are matched and their currents must be half of the current in Q5.

$$\frac{I_{DS5}}{I_{DS9}} \approx \frac{W5/L5}{W9/L9} \Rightarrow I_{DS5} = 10 I_{DS9} = 10 I_{DS8} \Rightarrow I_{DS3} = 5 I_{DS8}$$

$$\frac{I_{DS3}}{I_{DS8}} = \frac{W3/L3}{W8/L8} = 5 \Rightarrow \frac{W3}{L3} = \frac{W4}{L4} = 50$$

* Q8 and Q9 are operating in saturation:

$$\begin{cases} I_{DS8} = \frac{1}{2} \mu_n C_{ox} \frac{W8}{L8} (V_{GS8} - V_{th})^2 [1 + \lambda V_{th}] \\ I_{DS9} = \frac{1}{2} \mu_p C_{ox} \frac{W9}{L9} (V_{SG9} - V_{th})^2 [1 + \lambda V_{th}] \\ I_{DS9} = I_{DS8} \\ V_{DD} = V_{SG9} + R_b \cdot I_{DS8} + V_{GS8} \end{cases}$$

$$\Rightarrow 50 \mu \times 25 \times (V_{SG9} - 0.3)^2 = 125 \mu \times 10 \times (V_{GS8} - 0.3)^2$$

$$\Rightarrow V_{SG9} - 0.3 = \pm (V_{GS8} - 0.3)$$

$$\Rightarrow \begin{cases} V_{SG9} = V_{GS8} \\ V_{SG9} = -V_{GS8} + 0.6 \quad (\text{not acceptable}) \end{cases}$$

$$\Rightarrow 1.5 = 2 V_{GS8} + 62.5 \times 10^3 \times 10 \times (V_{GS8} - 0.3)^2 \times 1.003$$

$$\Rightarrow .627 (V_{GS8}^2 - 0.6 V_{GS8} + 0.09) + 2 V_{GS8} - 1.5 = 0$$

$$\Rightarrow V_{GS8}^2 + 2.59 V_{GS8} - 2.3 = 0 \Rightarrow V_{GS8} = 0.7_V$$

$$\Rightarrow V_{SG9} = 0.7_V \quad \text{and} \quad I_{DS8} = 100 \mu A$$

V_{DD}	1.5V
C_c	1pF
C_L	100fF
C_{gs}	$0.2 \frac{W}{L}$ fF
C_{gd}	$0.1 \frac{W}{L}$ fF
C_{db}	$0.05 \frac{W}{L}$ fF
C_{sb}	$0.1 \frac{W}{L}$ fF
R_b	1k Ω
λ	0.01 $\frac{1}{V}$
$\mu_n C_{ox}$	125 $\mu \frac{A}{V^2}$
$\mu_p C_{ox}$	50 $\mu \frac{A}{V^2}$
V_{th}	0.3 V
$W1/L1$	300
$W2/L2$	300
$W5/L5$	250
$W6/L6$	300
$W7/L7$	125
$W8/L8$	10
$W9/L9$	25

* Q_5 and Q_9 are current mirrors.

$$I_{bias} \approx I_{SD9} \cdot \frac{W_5}{W_9} = 100\mu \times \frac{250}{25} = 1\text{mA}$$

* Q_7 and Q_9 are also current mirrors.

$$I_{SD7} = I_{SD9} \cdot \frac{W_7}{W_9} = 100\mu \times \frac{125}{25} = 0.5\text{mA}$$


$$P_{diss} = V_{dd} (I_{SD9} + I_{bias} + 2 I_{SD7}) = 1.5 \times 2.1\text{mA} = 3.15\text{mW}$$

$$\begin{cases} r_{ds} = \frac{1}{\lambda I_{DS}} \\ g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) = \frac{2 I_{DS}}{V_{GS} - V_{th}} = \sqrt{2 I_{DS} \mu_n C_{ox} \frac{W}{L}} \\ V_{eff} = \frac{2 I_{DS}}{g_m} \end{cases}$$

	Q_1, Q_2	Q_3, Q_4	Q_5	Q_6	Q_7
I_{DS}	0.5mA	0.5mA	1mA	0.5mA	0.5mA
g_m	3.87mA/V	2.5mA/V	5mA/V	6.12mA/V	2.5mA/V
r_{ds}	$200\text{k}\Omega$	$200\text{k}\Omega$	$100\text{k}\Omega$	$200\text{k}\Omega$	$200\text{k}\Omega$
V_{eff}	0.258V	0.4V	0.4V	0.163V	0.4V

$$V_{cm-max} < V_{dd} - V_{eff5} - V_{th1} \Rightarrow V_{cm-max} < 0.8\text{V}$$
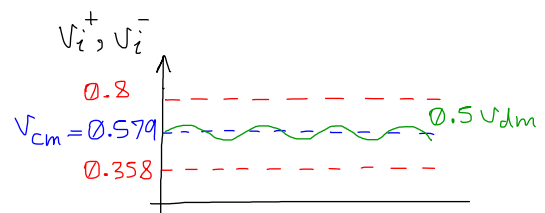
$$V_{cm-min} > V_{eff3} + V_{eff1} - V_{th1} \Rightarrow V_{cm-min} > 0.358\text{V}$$



$$V_{o-max} < V_{dd} - V_{eff7} \Rightarrow V_{o-max} < 1.1\text{V}$$

$$V_{o-min} > V_{eff6} \Rightarrow V_{o-min} > 0.163\text{V}$$

