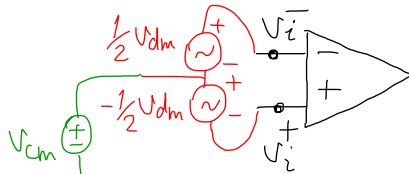



# \* Voltage swing of diff-pair amplifiers :



$$V_i^- = \frac{1}{2} V_{dm} + V_{cm}$$

$$V_i^+ = -\frac{1}{2} V_{dm} + V_{cm}$$

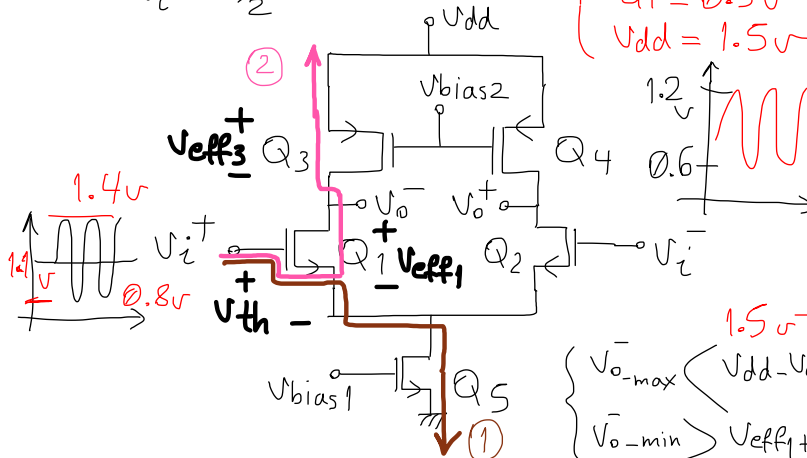\* Assume  
 $V_{th} = 0.5V$   
 $V_{eff} = 0.3V$   
 $V_{dd} = 1.5V$



$V_{eff}$  (effective voltage)  
 $V_{ov}$  (overdrive voltage)

\*  $V_{eff}$  is the minimum voltage across drain/source terminals so that transistor operates in the active


\*  $V_{th}$  is the voltage that depletes the channel and makes it ready for inversion

\* look for conditions that keep all transistors in a circuit in the active region


$$① V_{i_{min}}^+ > V_{GS1} + V_{DS1} \Rightarrow V_{i_{min}}^+ > 0.8V$$

$$② V_{i_{max}}^+ < V_{dd} - V_{SD3} - V_{SD1} + V_{GS1} \Rightarrow V_{i_{max}}^+ < 1.4V$$

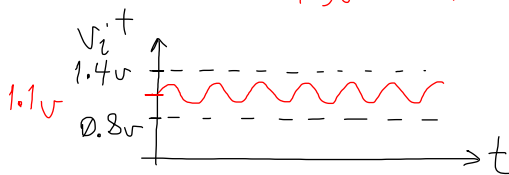$\begin{matrix} 1.5V & 0.3 & 0.3 & 0.5 \end{matrix}$


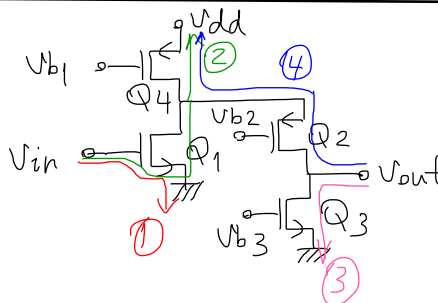
$$\begin{cases} V_{dd} = 1.5V, V_{th} = 0.5V, V_{eff} = 0.3V \\ A_{vo} = 20 \text{ } V/V \end{cases}$$




$$① V_{in-min} > V_{th}$$

$$② V_{in-max} < V_{dd} + V_{th} - 2V_{eff}$$




$$③ V_{out-min} > V_{eff}$$

$$④ V_{out-max} < V_{dd} - 2V_{eff}$$

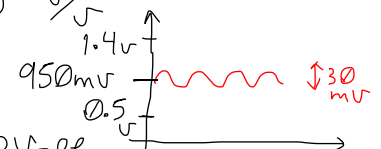

$$A_{v0} = -g_m(r_{ds1} || r_{ds3})$$
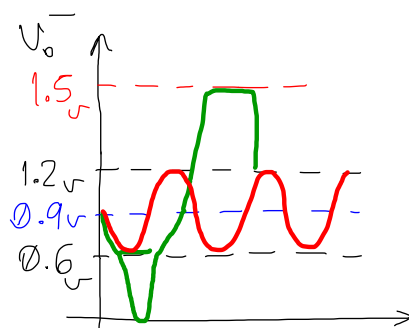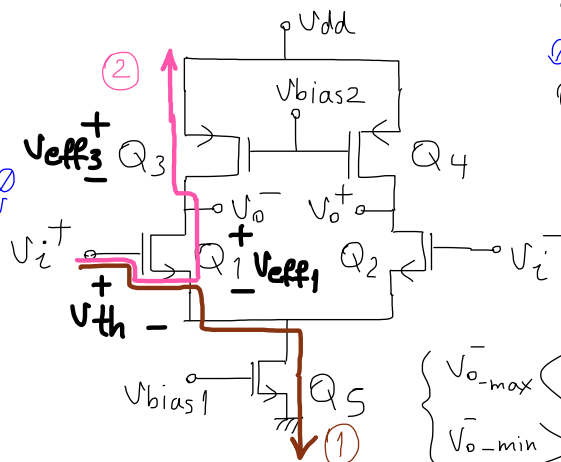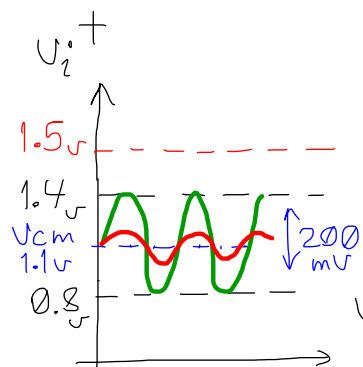
$$= -10 \text{ } \cancel{\text{V}}/\cancel{\text{V}}$$



$$\begin{cases} V_{o-\max} < V_{DD} - V_{eff3} \\ V_{o-\min} > V_{eff1} + V_{eff5} \end{cases}$$

$$1.5 \text{ V} - 0.3 \text{ V}$$

$$0.3 \text{ V} + 0.3 \text{ V}$$